




Indian Institute of Information Technology Design and Manufacturing, Kancheepuram  
Department of Electronics and Communication Engineering  
Assignment III

Subject: Electrical Circuits for Engineers


Date: 26/11/2023

Due Date : 04/12/2023

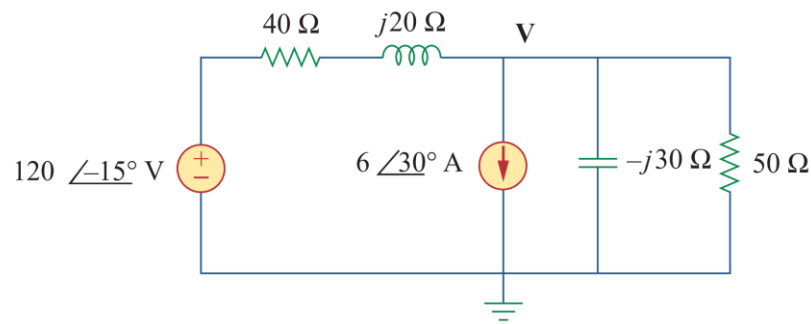
1. Use nodal analysis to find  $V$  in the circuit



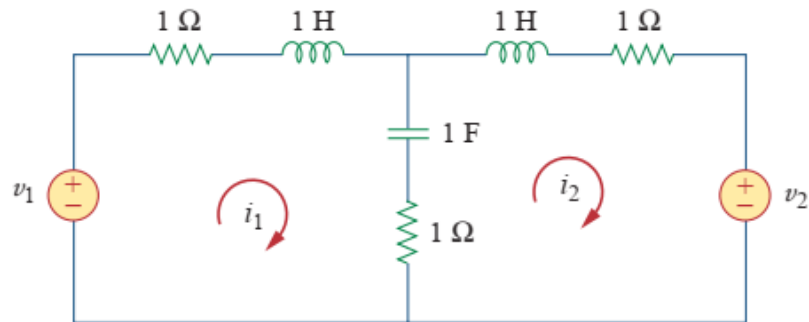2. In the circuit of Fig. , determine the mesh currents  $i_1$  and  $i_2$ . Let  $v_1 = 10 \cos 4t$  V and  $v_2 = 20 \cos(4t - 30^\circ)$  V.




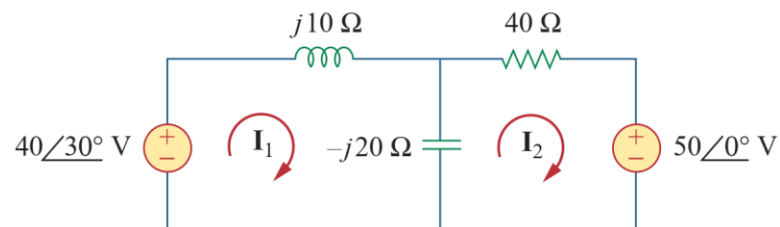3. Using mesh analysis, find  $I_1$  and  $I_2$  in the circuit




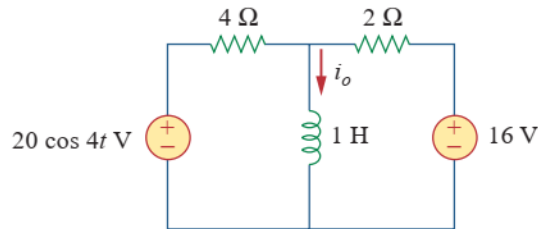- 4.

Find  $i_o$  in the circuit shown in Fig. using superposition.



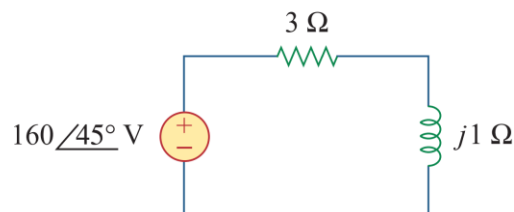
5. In the circuit of Fig. calculate the average power absorbed by the resistor and inductor. Find the average power supplied by the voltage source.



6. Obtain the power factor and the apparent power of a load whose impedance is  $\mathbf{Z} = 60 + j40 \Omega$  when the applied voltage is  $v(t) = 160 \cos(377t + 10^\circ) \text{ V}$ .


7. A sinusoidal source supplies 20 kVAR reactive power to load  $\mathbf{Z} = 250 \angle -75^\circ \Omega$ . Determine: (a) the power factor, (b) the apparent power delivered to the load, and (c) the rms voltage.

8. Find the  $V_s$

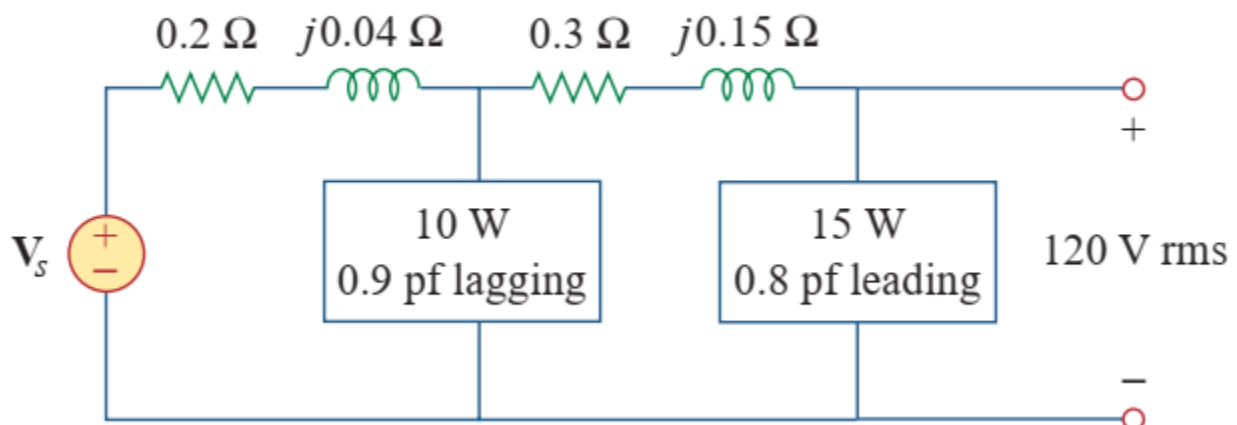


9. Calculate

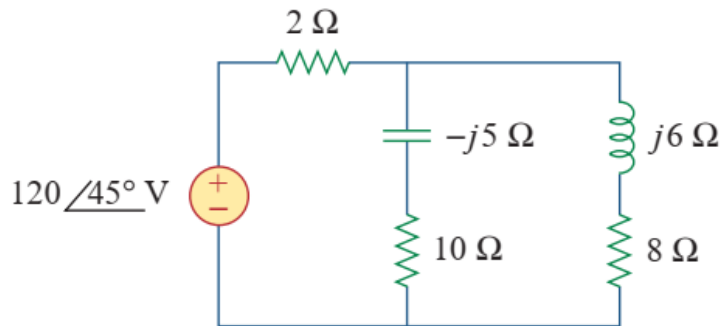- (a) the power factor
- (b) the average power delivered by the source
- (c) the reactive power
- (d) the apparent power
- (e) the complex power



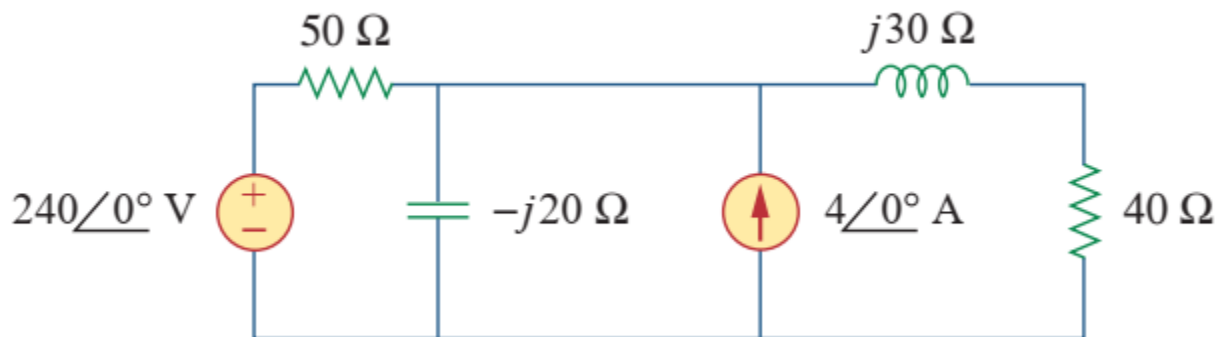10. Calculate the reactive in energy storage elements in the circuit



11. Find  $I_o$  in the circuit

