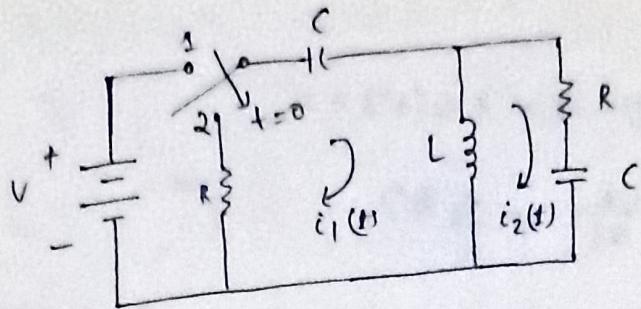



QII



Det. $i_1(0^+)$

(a) 0 (b) $-\frac{V}{R}$ (c) $-\frac{V}{2R}$ (d) $\frac{V}{2R}$

(A)

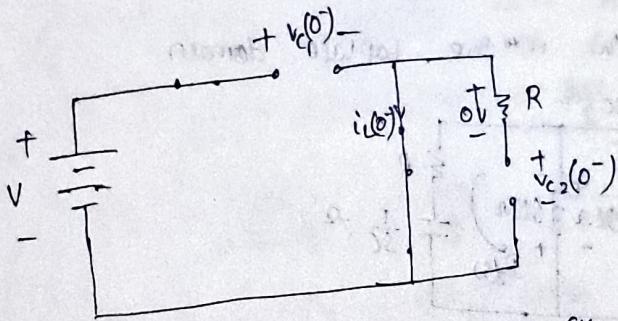


At $t = 0^-$: S.S! A ref. CKt.


By KVL $\Rightarrow V - V_{C1}(0^-) = 0 \Rightarrow V_{C1}(0^-) = V = V_C(0^+)$.

$$i_L(0^-) = 0 \Rightarrow i_L(0^+)$$
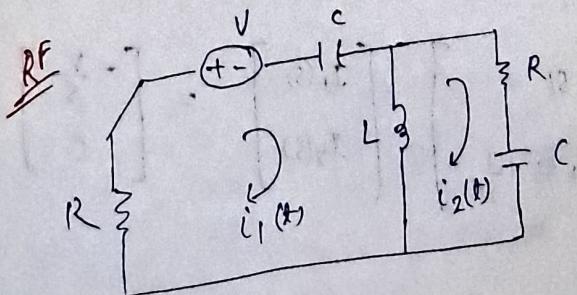
$$V_{C2}(0^-) = 0 \Rightarrow V_{C2}(0^+)$$



für $t \geq 0$:

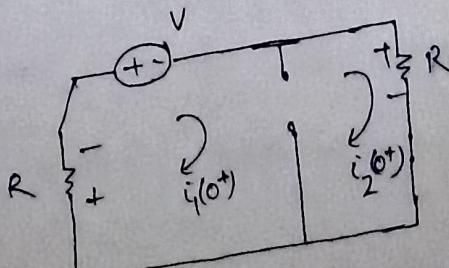

At $t = 0^+$: Ref. CKt: NW is in TR. State


$$i_1(0^+) = i_2(0^+)$$

By KVL $\Rightarrow -R \cdot i_1(0^+) - v - R i_1(0^+) = 0$

$$\Rightarrow i_1(0^+) = \frac{-v}{2R} = i_2(0^+).$$

Q1 Let $I_1(s)$ and $I_2(s)$ are the L.T of $i_1(t)$ and $i_2(t)$ respectively then det. the expressions for $I_1(s)$ and $I_2(s)$

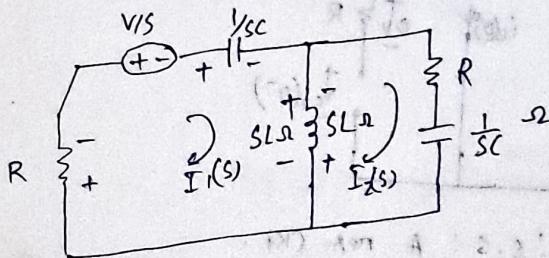(A) Transform the RF n/w into the Laplace domain



$$v(s) = Z(s) \cdot I(s)$$


By KVL in $s-D \Rightarrow$

$$-RI_1(s) - \frac{v}{s} - \frac{1}{sC} \cdot I(s) - SL (I_1(s) - I_2(s)) = 0$$

$$-RI_1(s) - \frac{v}{s} - \frac{1}{sC} \cdot I_2(s) - SL (I_2(s) - I_1(s)) = 0.$$

$$\begin{bmatrix} R + SL + \frac{1}{sC} & -SL \\ -SL & R + SL + \frac{1}{sC} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{v}{s} \\ 0 \end{bmatrix}$$

Q2 Det. i_L & i_1 for $t > 0$.

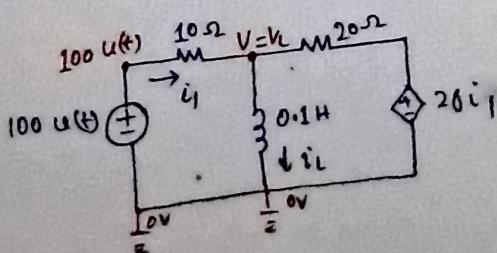

$$i_L(0^-) = 0A = i_L(0^+)$$

$$i_L = \frac{100 u(t) - v_L}{10} \quad \left| \quad v_L = 0.1 \cdot \frac{d i_L}{dt} \right.$$

$$\Rightarrow i_L = 10 u(t) - \frac{1}{100} \frac{d i_L}{dt}$$

NODAL $-i_1 + i_L + \frac{v_L - 20 i_1}{20} = 0$

$$\Rightarrow -2i_1 + i_L + \frac{1}{200} \frac{d i_L}{dt} = 0$$

$$\Rightarrow \frac{d i_L}{dt} + 40 i_L = 800 u(t) \rightarrow \text{A state eqn.}$$

$$s I_L(s) + I_L(0^+) + 40 i_L(s) = \frac{800}{s}$$

$$\Rightarrow I_L(s) = \frac{800}{s(s+40)} = \frac{20}{5} - \frac{20}{s+40}$$


$$\Rightarrow i_L(t) = 20(1 - e^{-40t}) u(t)$$

$$\tau = \frac{1}{40} \text{ sec.}$$

$$i_1 = 10 u(t) - \frac{1}{100} \frac{d i_L}{dt} = (10 - \frac{8}{10} e^{-40t}) u(t)$$

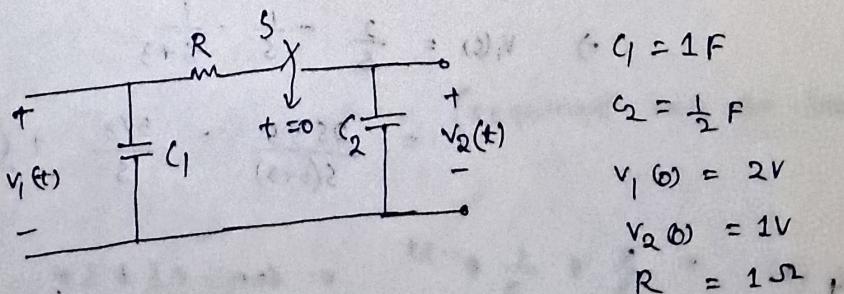13.11.10

Q/ Determine the S.S voltages across the capacitors.




(A) get a source free R.C Ckt, but the energy in S.S is non-zero, provided the capacitors are said to be ideal.

$$v_1(\infty) = v_2(\infty) = \frac{v_1 C_1 + v_2 C_2}{C_1 + C_2} = \frac{\frac{2}{1} + \frac{1}{2}}{1 + \frac{1}{2}} = \frac{5}{3} = \frac{5}{3} V$$


$$v_1 = v_1(0) = \frac{2}{1 + \frac{1}{2}} = \frac{4}{3} V$$
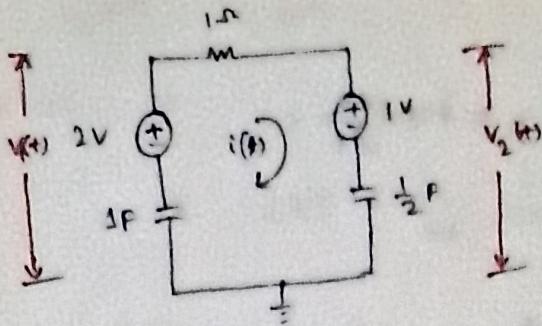
$$v_2 = v_2(0) = \frac{1}{1 + \frac{1}{2}} = \frac{2}{3} V$$



for $t \geq 0$:

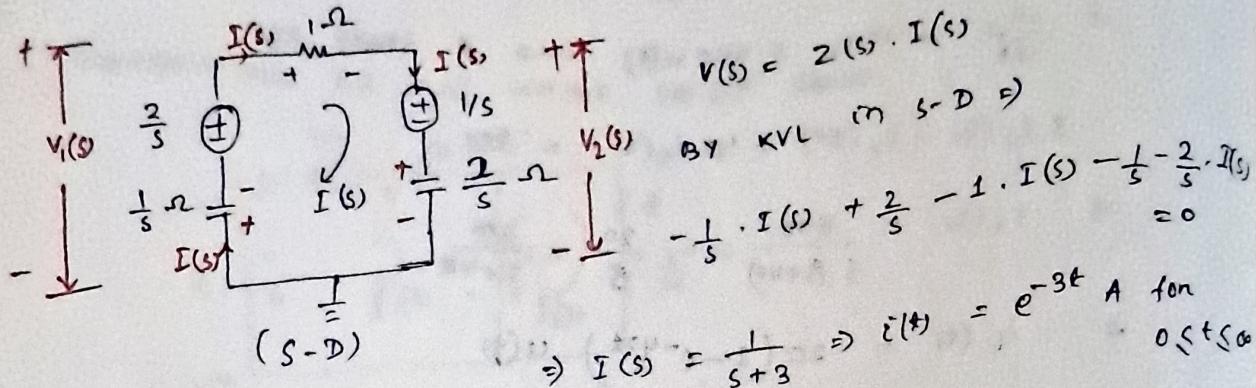Transform the above now into the Laplace domain



Check: $i(0^+) = 1 \text{ A}$.

$$i(\infty) = 0 \text{ A: } \tau = \frac{1}{3} \text{ sec} = R C_{eq} = \frac{R C_1 C_2}{C_1 + C_2}$$

By KVL in $s\text{-D} \Rightarrow V_1(s) - \frac{2}{s} + \frac{1}{s} \cdot I(s) = 0$

$$\Rightarrow V_1(s) = \frac{2}{s} - \frac{1}{s} \cdot \frac{1}{s+3}$$

$$= \frac{2s+5}{s(s+3)} = \frac{5/3}{s} + \frac{(1/3)}{s+3}$$

$$V_1(t) = \frac{5}{3} + \frac{1}{3} e^{-3t} \text{ V for } 0 \leq t \leq \infty.$$

Check: $V_1(0) = \frac{5}{3} + \frac{1}{3} = 2 \text{ V}$

$$V_1(\infty) = \frac{5}{3} \text{ V.}$$

$$\text{Similarly, } V_2(s) - \frac{1}{s} = \frac{2}{s} I(s) = 0$$

$$\Rightarrow V_2(s) = \frac{1}{s} + \frac{2}{s} \cdot \frac{1}{s+3}$$


$$= \frac{s+5}{s(s+3)} = \frac{5/3}{s} - \frac{2/3}{s+3}$$

$$V_2(t) = \frac{5}{3} - \frac{2}{3} e^{-3t} \text{ v, for } 0 \leq t \leq \infty.$$

Check!

$$V_2(0) = \frac{5}{3} - \frac{2}{3} = 1 \text{ v.}$$

$$V_2(\infty) = \frac{5}{3} \text{ v.}$$

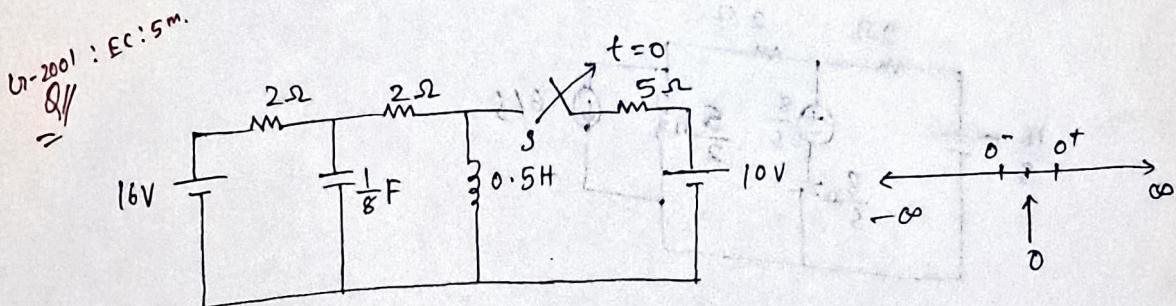

Det. (a) $e_1(0^+)$ (b) $i_L(0^+)$ (c) $e_1(t)$ for $t \geq 0$ (d) $i_L(t)$ for $t \geq 0$.

(a) Evaluation of initial condn :- (must for any procedure)

$$i_L(0^+) = 6 \text{ A}$$

$$e_1(0^+) = 8 \text{ V}$$

Evaluation of final condn :- (Required only for short cut)

$$i_L(\infty) = 4 \text{ A}$$


$$e_1(\infty) = 8 \text{ V}$$

Evaluation of first derivative initial condn . (Required only for short cut)

$$\left. \frac{di_L(t)}{dt} \right|_{t=0^+} = -\frac{8 \text{ A}}{\text{sec}}$$



$$\left. \frac{de_1(t)}{dt} \right|_{t=0^+} = -\frac{16 \text{ V}}{\text{sec}}$$

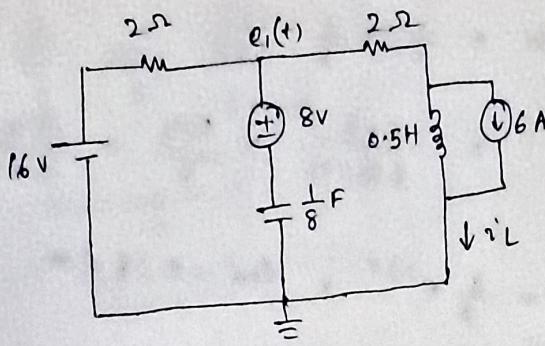Evaluation of $i_L(t)$ and $e_1(t)$ or for $t > 0$ by LTA :-



(for $t > 0$)

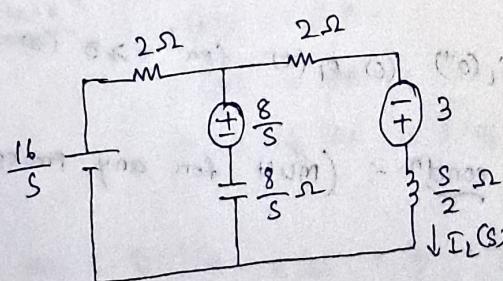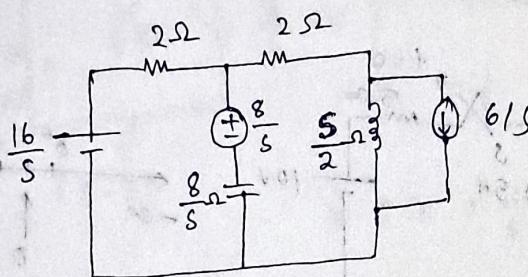Transform the above NW into the Laplace domain



(S - D)

Nodal in S-D \Rightarrow


$$\frac{E_1(s) - \frac{16}{s}}{2} + \frac{E_1(s) - \frac{8}{s}}{8/s} + \frac{E_1(s) + 3}{2 + \frac{s}{2}} = 0$$

$$\Rightarrow E_1(s) = \frac{8}{s} \left(\frac{s^2 + 6s + 8^2}{s^2 + 8s + 32} \right)$$

$$= \frac{8}{s} \left(1 - \frac{2s}{(s+4)^2 + 4^2} \right)$$


$$= \frac{8}{s} - \frac{4 \cdot 4}{(s+4)^2 + 4^2}$$
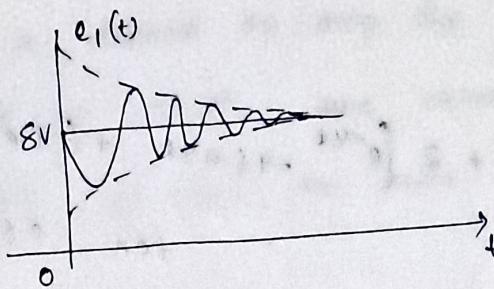
$$\Rightarrow e_1(t) = 8 - 4e^{-4t} \sin 4t \text{ v for } t \geq 0.$$



$$I_L(s) = \frac{E_1(s) + 3}{2 + \frac{s}{2}}$$
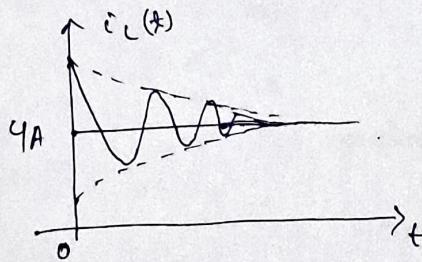
$$\Rightarrow I_L(t) = 4 + 2e^{-4t} \cos 4t \text{ A for } t \geq 0.$$



$$\gamma = \frac{1}{4} \text{ sec} = \frac{1}{\sqrt{LC}} \quad | \omega_n = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{\frac{1}{2} \cdot \frac{1}{8}}} = 4\pi \text{ rad/sec.}$$

$\Rightarrow \xi = 1 \Rightarrow$ A critically damped sys/NW.

$$e_1(t) = 8 - 4e^{-4t} \sin 4t \text{ v for } t \geq 0.$$

$\sin \omega_n t.$

Evaluation of $i_L(t)$ and $e_1(t)$ for $t \geq 0$ directly from choices by applying the short cut procedure :-

$$\underline{e_1(t)} : \quad (i) \quad e_1(0^+) = 8 \text{ v.}$$

$$(ii) \quad e_1(\infty) = 8 \text{ v.}$$

$$(iii) \quad \frac{de_1(t)}{dt} = 0 - 4 \left[e^{-4t} 4 \cos 4t + (-4e^{-4t}) \cdot \sin 4t \right] \text{ v/s}$$

for $0 \leq t \leq \infty$

$$\Rightarrow \frac{de_1(t)}{dt} \Big|_{t=0^+} = -4 \times 4 = -16 \text{ v/s.}$$

$i_L(t)$:

(i) $i_L(0^+) = 6 \text{ A}$

(ii) $i_L(\infty) = 4 \text{ A}$

(iii) $\frac{di_L(t)}{dt} = 0 + 2 \left[e^{-4t} - 4 \sin 4t + (-4e^{-4t}) \cdot \cos 4t \right] \text{ A/s}$
for $0 \leq t \leq \infty$

$$\Rightarrow \frac{di_L(t)}{dt} \Big|_{t=0^+} = 2 \times -4 = -8 \text{ A/s}$$

H.W
Q/II
Repeat the above problem procedure for all the R,L,C
circuit case (2).

The phasor representation - !

It is defined to only for sinusoidal signals.

All the sinusoidal signals are converted in to the sinusoidal by subtracting 90° from the phase.

$$\rightarrow V(t) = V_m \cos(\omega t + \phi)$$

$$= \text{Real part} [V_m (e^{j(\omega t + \phi)})]$$

$$= R.P [V_m e^{j\phi}, e^{j\omega t}]$$

$$= R.P [V \cdot e^{j\omega t}]$$

$$V = V_m e^{j\phi} \rightarrow \begin{matrix} \text{The exponential form of the phasor} \\ \text{Div & mul.} \end{matrix}$$

$$= V_m (\underline{\theta}) \rightarrow \begin{matrix} \text{The polar} \\ \text{" " " " } \end{matrix}$$

$$= V_m (\cos \phi + j \sin \phi) \rightarrow \begin{matrix} \text{The rect. form of the phasor} \\ \rightarrow \text{for Add & Sub.} \end{matrix}$$

$$\rightarrow i(t) = I_m \cos(\omega t + \theta)$$

$$I = I_m (\underline{\theta})$$

$$= I_m e^{j\theta}$$

$$= I_m (\cos \theta + j \sin \theta)$$

e.g. $V(t) = 10 \cos(2t + 30^\circ)$

$$V = 10 \underline{30^\circ}$$

$$= 10 e^{j30^\circ}$$

$$= 10 (\cos 30^\circ + j \sin 30^\circ)$$

$$= 10 \left(\frac{\sqrt{3}}{2} + j \cdot \frac{1}{2} \right)$$

$$\begin{aligned}
 \text{eq} \quad i(t) &= 10 \sin(2t + 30^\circ) \\
 &= 10 \cos(2t + 30^\circ - 90^\circ) \\
 &= 10 \cos(2t - 60^\circ) \\
 &= 10 \underbrace{-60^\circ}_{\text{Ans}} \\
 &= 10 e^{-j60^\circ} \\
 &= 10 \left(\frac{1}{2} - j \frac{\sqrt{3}}{2} \right)
 \end{aligned}$$




$$\rightarrow \boxed{\frac{V}{I} = Z} \quad \text{Ans} \quad \Rightarrow V = Z \cdot I$$

$$\Rightarrow I = \frac{V}{Z}$$

$$\rightarrow \boxed{\frac{I}{V} = Y} \quad \text{Ans} \quad \Rightarrow I = Y \cdot V$$


$$\Rightarrow V = \frac{I}{Y}$$
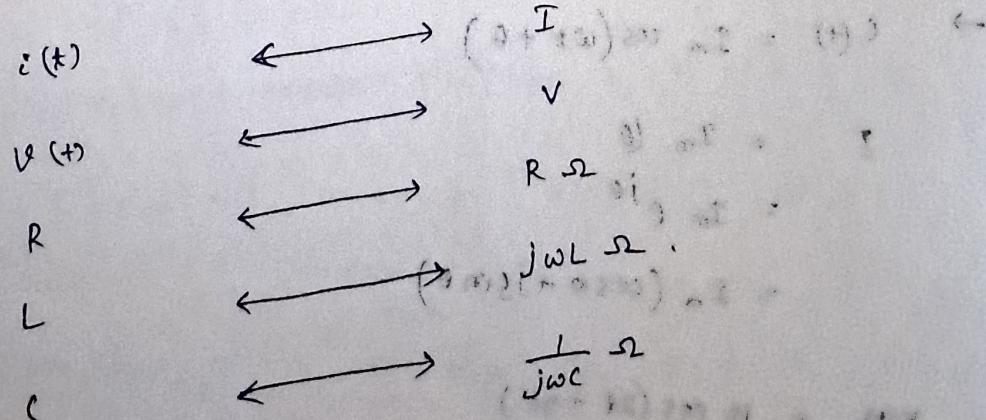
$$\rightarrow \boxed{Y = \frac{1}{Z}} \quad \text{Ans} \quad \text{Time domain} \leftrightarrow \text{Phasor Domain}$$



Note - The analysis of A.C is generally carried on the phasor domain i.e the KCL, KVL, NODAL, MESH, ohm's law and the source transformation are written only in the phasor domain.

A.C - Transients

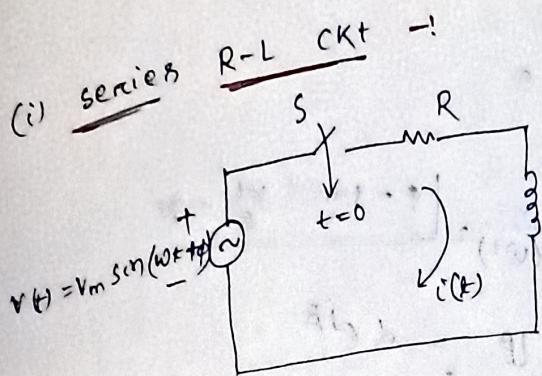


$$\rightarrow C.S. = C.F. + P.I.$$

$$= \text{Natural resp.} + \text{Forced resp.}$$

= Resp. up to 5τ + Resp. after 5τ


$$i(t) = i_{tr}(t) + i_{ss}(t) = e^{-Rt/L} + i_{ss}(t)$$

$$i(t) = e^{-Rt/L} + i_{ss}(t)$$

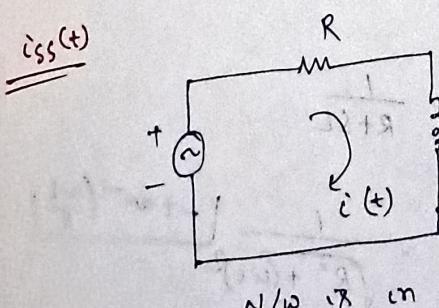

Method ①: By phasor approach:

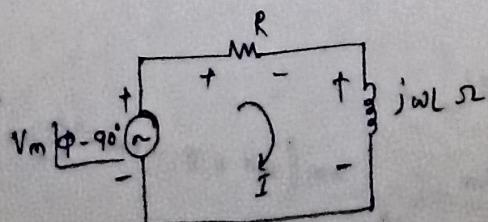transform the above into the phasor domain



N/W i.e. in P-D

$$V = Z \cdot I$$

By KVL in P-D \Rightarrow

$$V_m [\phi - 90^\circ] - R \cdot I - j\omega L \cdot I = 0$$

$$\Rightarrow I = \frac{V_m [\phi - 90^\circ]}{R + j\omega L} = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \left[\phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ \right]$$

$$= \alpha [I_p] = \alpha e^{j\beta}$$

$$\rightarrow i(t) = R \cdot P \cdot [I \cdot e^{j\omega t}] A$$

$$\Rightarrow i(t) = \alpha \cos(\omega t + \beta)$$

$$= \alpha \cos(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} - 90^\circ)$$

$$= \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t + \phi - \tan^{-1} \frac{\omega L}{R}) = i_{ss}(t)$$

Method ② : By L.T.

$$v(t) = V_m \sin(\omega t + \phi)$$

$$\xrightarrow{\text{desired resp. L.T.}}$$

$$\frac{I(s)}{V(s)} = H(s) = Y(s) = \frac{1}{Z(s)} = \frac{1}{R + sL}$$

$$\xrightarrow{\text{excitation L.T.}}$$

$$\Rightarrow H(j\omega) = \frac{1}{R + j\omega L} = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \left[-\tan^{-1} \left(\frac{\omega L}{R} \right) \right]$$

$$\rightarrow I(s) = H(s) \cdot V(s)$$

$$\Rightarrow i(t) = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \cdot V_m \sin \left(\omega t + \phi - \tan^{-1} \frac{\omega L}{R} \right) A = i_{ss}(t)$$

$$\rightarrow i(t) = i_{tr}(t) + i_{ss}(t)$$

$$= K e^{-R/L t} + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \sin \left(\omega t + \phi - \tan^{-1} \left(\frac{\omega L}{R} \right) \right)$$

$$i(0^-) = 0 A = i(0^+)$$

$$\Rightarrow K = \frac{-V_m}{\sqrt{R^2 + (\omega L)^2}} \sin \left(\phi - \tan^{-1} \frac{\omega L}{R} \right) \ll 1$$

$$V_L(t) = L \frac{di(t)}{dt} \quad | \text{ by ohm's law}$$

$$\rightarrow \text{Suppose } \phi - \tan^{-1} \frac{\omega L}{R} = 0 \Rightarrow K=0 \Rightarrow i_{trn}(t)=0$$

$$\Rightarrow i(t) = i_{ss}(t) \quad | \text{ A tr. free resp.}$$

So, the condition for the transient free response at $t=0$ is

$$\boxed{\phi = \tan^{-1} \frac{\omega L}{R}}$$

$$\text{i.e. } (\omega t + \phi) \Big|_{t=0} = \tan^{-1} \frac{\omega L}{R}$$

Note:- i.e. if the total phase of the excitation at the time of switching is equal to $\tan^{-1} \frac{\omega L}{R}$ then no transients will result in the system at the time of switching for the sinusoidal excitation.

\rightarrow If the switch is closed at $t=t_0$ then the condn for the transient free response at $t=t_0$ is

$$(\omega t + \phi) \Big|_{t=t_0} = \tan^{-1} \frac{\omega L}{R}$$

$$\Rightarrow \boxed{\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R}}$$

\rightarrow If the excitation is $V(t) = V_m \cos(\omega t + \phi)$ then sine is replaced by cosine in the steady state response and hence K is a function of cosine

$$\rightarrow \text{Suppose } \phi - \tan^{-1} \frac{\omega L}{R} = \frac{\pi}{2} \Rightarrow K=0 \Rightarrow i_{tr}(t) = 0$$

$\rightarrow i(t) = i_{ss}(t)$ A transient free resp.

$$\boxed{\phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2}} \rightarrow \text{at } t=0$$

$$\boxed{\omega t_0 + \phi = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2}} \rightarrow \text{at } t=t_0$$

\rightarrow In the above cases, if L is replaced by C then

$$T = \frac{L}{R} \text{ is replaced by } T = RC$$

\rightarrow The above condn are the same even if the elements are connected in parallel with current excitation i.e., for the parallel $R-L$ and $R-C$ circuit.

Note:- The transient free condn is not possible for the n/w with both the energy storing elements i.e. for the RLC n/w.


Reason:-

$$S_1, S_2 = \alpha \pm j\beta$$

$$\begin{aligned} \rightarrow i(t) &= i_{tr}(t) + i_{ss}(t) \\ &= e^{\alpha t} (K_1 \cos \beta t + K_2 \sin \beta t) + i_{ss}(t) \end{aligned}$$

By applying the initial condn $i_L(0+)$ and $V_C(0+)$, K_1 is a funcn of sine and K_2 is a funcn of cosine (viceversa), hence no term will satisfy both K_1 and K_2 simultaneously to zero, so, the transient term is always present in the complete response.

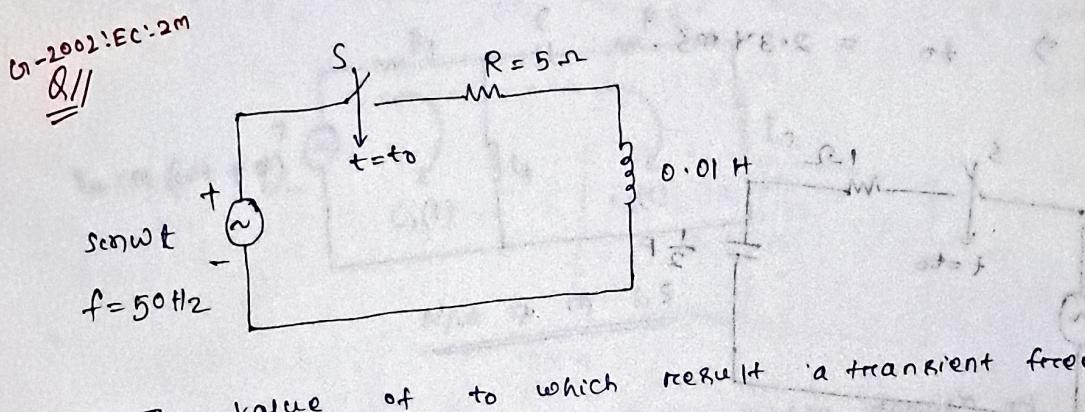Obs: So, the transient free time (t_0) value in R-L and R-C CIRCUITS with ac excitation will depends on the source freq. (ω), its initial phase (Π), on the CIRCUIT constants (R, L, C values) and the nature of the excitation (Sine or cosine), but not on the max. value of the excitation. (V_m or I_m)



The value of t_0 to which result a transient free response.

$$\textcircled{A} \quad \omega t \Big|_{t=t_0} = \tan^{-1} \frac{\omega L}{R}$$

$$\Rightarrow \omega t_0 = \tan^{-1} \frac{\omega L}{R}$$

$$\Rightarrow 2\pi \times 50 \times t_0 = \tan^{-1} \left(\frac{2\pi \times 50 \times 0.01}{5} \right)$$

$$= 32.14^\circ \times \frac{\pi}{180}$$

$$\Rightarrow t_0 = 1.78 \text{ ms}$$

Q1/ In the above case if the excitation is $\cos \omega t$ then,

$$\omega t \Big|_{t=t_0} = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2}$$

$$\Rightarrow \omega t_0 = \tan^{-1} \frac{\omega L}{R} + \frac{\pi}{2}$$

$$\Rightarrow 2\pi \times 50 \times t_0 = \tan^{-1} \left(\frac{2\pi \times 50 \times 0.01}{5} \right) + \frac{\pi}{2}$$

$$= 32.14^\circ \times \frac{\pi}{180} + \frac{\pi}{2}$$

$$\Rightarrow t_0 = 6.78 \text{ ms}$$

Q// In the above case if the excitation is $\sin(\omega t - 10^\circ)$

$$\textcircled{A} \quad \omega t - 10 \Big|_{t=t_0} = \tan^{-1} \frac{\omega L}{R}$$


$$\Rightarrow \omega t_0 = \tan^{-1} \frac{\omega L}{R} + 10^\circ$$

$$\rightarrow 2\pi \times 50 \times t_0 = \tan^{-1} \left(\frac{2\pi \times 50 \times 0.01}{5} \right) + 10^\circ$$

$$= 42.14^\circ \times \frac{\pi}{180^\circ}$$

$$\Rightarrow t_0 = 2.34 \text{ ms.}$$

Q//

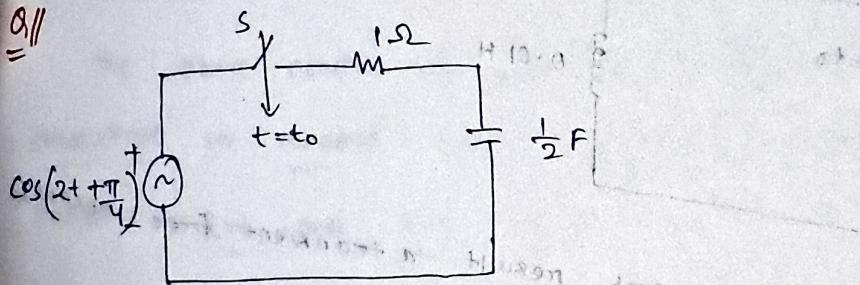

\textcircled{A}

$$\omega t_0 + \phi = \tan^{-1} \omega C R + \frac{\pi}{2}$$

$$\Rightarrow 2t_0 + \frac{\pi}{4} = \tan^{-1} (2 \cdot \frac{1}{2} \cdot 1) + \frac{\pi}{2}$$


$$\Rightarrow 2t_0 + \frac{\pi}{4} = \frac{\pi}{4} + \frac{\pi}{2}$$

$$\Rightarrow 2t_0 = \frac{\pi}{2} \Rightarrow t_0 = \frac{\pi}{4} = \frac{3.14}{4} = 0.785 \text{ sec.}$$


IV / A.C. Analysis.

sinusoidal steady state analysis →

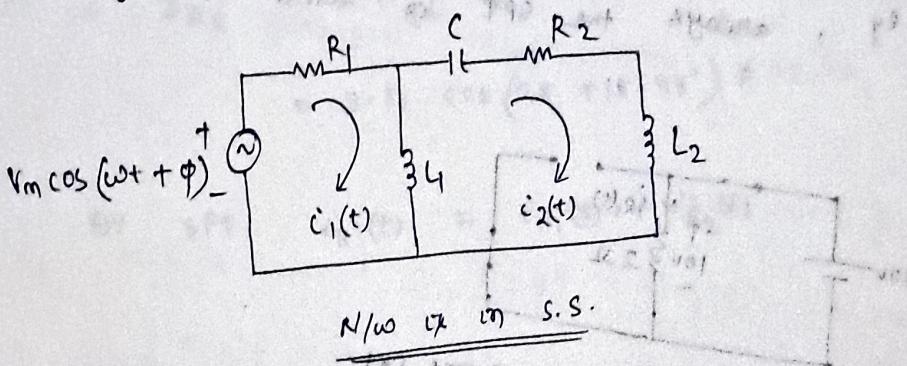steady state indicates the absence of transients, it is achieved practically after '5T' constants of the switching action and the analysis in steady state is generally carried out by using phasors.



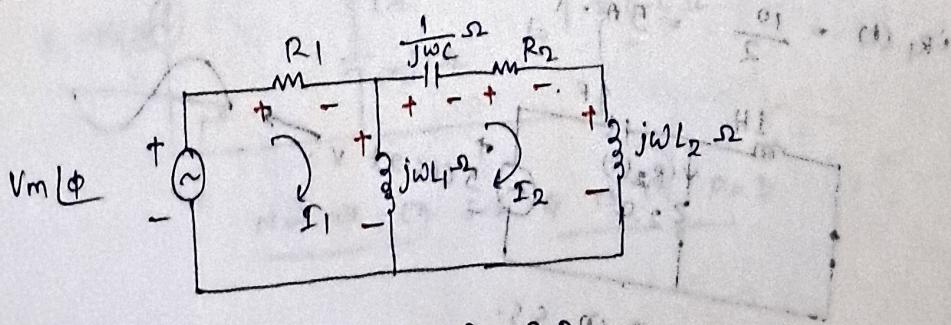Transform the above N/W into the phasor domain →



N/W is in P.D.

$$V = Z \cdot I$$


By KVL in P-D →

$$V_m |\phi| - R_1 \cdot I_1 - jwL_1 \cdot (I_1 - I_2) = 0$$

$$-\frac{1}{jwC} \cdot I_2 - R_2 \cdot I_2 - jwL_2 \cdot I_2 - jwL_1 \cdot (I_2 - I_1) = 0$$


$$\Rightarrow I_1 = \frac{\Delta_1}{\Delta} \quad | \quad i_1(t) = R.P [I_1 \cdot e^{j\omega t}]^n$$

$$I_2 = \frac{\Delta_2}{\Delta} \quad | \quad i_2(t) = R.P [I_2 \cdot e^{j\omega t}]^n$$

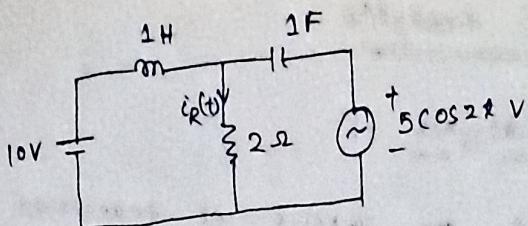


Def. the current $i_R(t)$, provided the n/w is in the S.S.

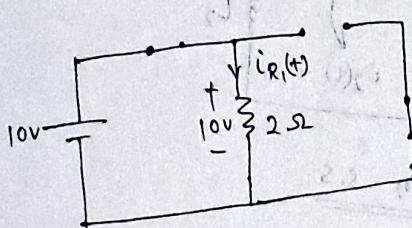Note: Since two diff. frequencies are operating on the n/w simultaneously, always the SPT is used to evaluate the responses.




N/W is in S.S. : A res. Ckt.
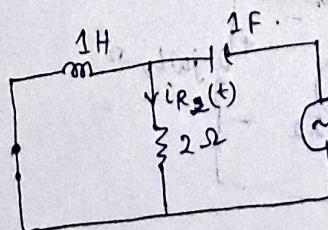
$$i_{R_1}(t) = \frac{10}{2} = 5 \text{ A.}$$



N/W is in S.S.

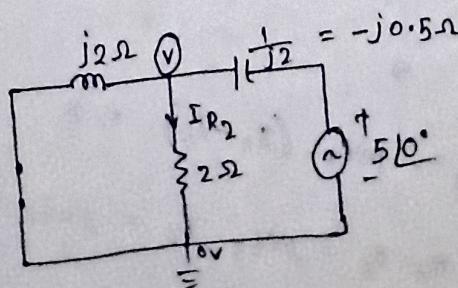Transform the above n/w into the phasor domain.



N/W is in P.D.

Nodal in P-D \Rightarrow

$$\frac{V}{j2} + \frac{V}{2} + \frac{V - 50^\circ}{-j0.5} = 0$$


$$\Rightarrow V = 6.32 \angle 18.44^\circ$$

$$I_{R_2} = \frac{V}{Z} = 3.16 \angle 18.44^\circ = 3.16 e^{j18.44^\circ}$$

$$I_{R_2} = R \cdot P [I_{R_2} e^{j2\omega t}] A$$

$$= 3.16 \cos(2t + 18.44^\circ) A$$
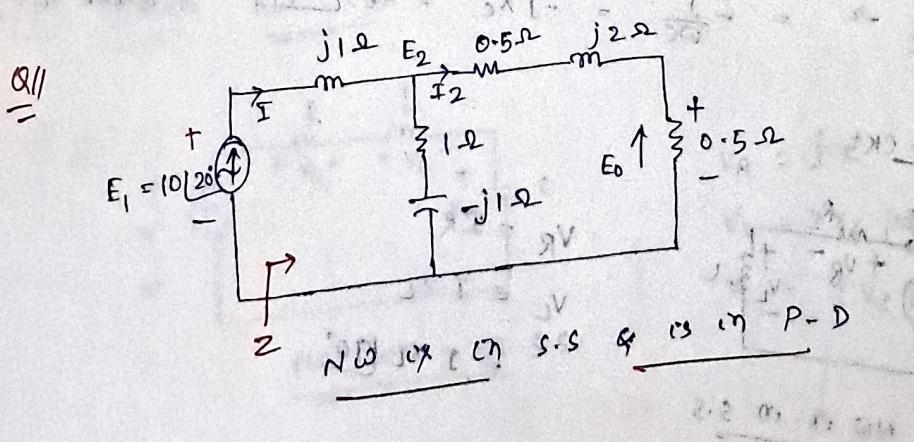
$$\text{By SPT } i_R(t) = i_{R_1}(t) + i_{R_2}(t)$$



Dkt. I_1, I_2, E_0, E_2 .

$$z = j_1 + (1-j_1) \parallel (1+j_2)$$

=

$$I = \frac{E_1}{z} \quad | \text{ By Ohm's Law.}$$

$$I_1 = \frac{I \cdot (1+j_2)}{1-j_1+1+j_2}$$

$$I_2 = \frac{I \cdot (1-j_1)}{1-j_1+1+j_2}$$

$$E_2 = (1 - j1) \cdot I_1$$

$$E_0 = 0.5 I_2 \quad | \text{ By Ohm's Law}$$

The phasor diagrams. \rightarrow

\rightarrow Phasor diagram is a pictorial representation of all the phase voltages and their respective currents in a n/w.


\rightarrow The phasor is a rotating vector, which rotates in the anticlockwise direction with angular frequency ω in the time domain.

$$\rightarrow Z_R = R \Omega = R [0^\circ] \Omega \quad | \text{ where } X_L = \omega L.$$


$$Z_L = j\omega L = jX_L \Omega = X_L [90^\circ] \Omega \quad | \text{ where } X_C = \frac{1}{\omega C}.$$

$$Z_C = \frac{1}{j\omega C} \Omega = -\frac{j}{\omega C} = -jX_C = X_C [-90^\circ] \Omega \quad | \text{ where } X_C = \frac{1}{\omega C}.$$

① Series RL-CKT:

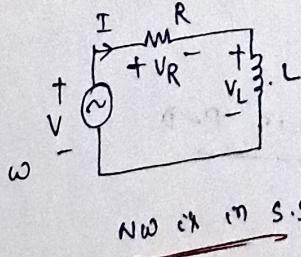
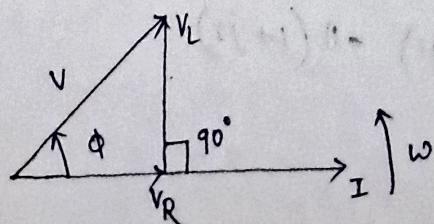
$$\begin{aligned} V_R &= IR \\ V_L &= IZ_L \\ &= IXL [90^\circ] \end{aligned}$$




$$V = \sqrt{V_R^2 + V_L^2}$$

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \text{imp. angle} = \text{Adm. angle}.$$

$$\cos \phi = P.F. = \frac{V_R}{V} (100)$$


②

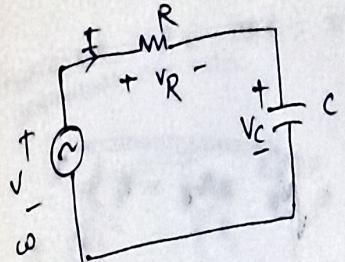

$$V_R = IR$$

$$V_C = I Z_C$$

$$= I X_C \angle -90^\circ$$

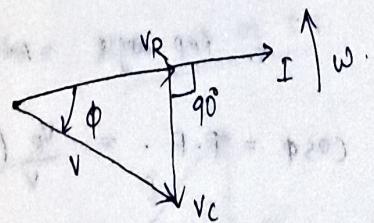

$$V = \sqrt{V_R^2 + V_C^2}$$


$$\phi = \tan^{-1} \frac{V_C}{V_R} = \text{imp. angle.}$$

= Adm. angle.

$$\cos \phi = \text{P.F.} = \left(\frac{V_R}{V} \right) \text{ lead.}$$

③

Series RLC - C.K.t.

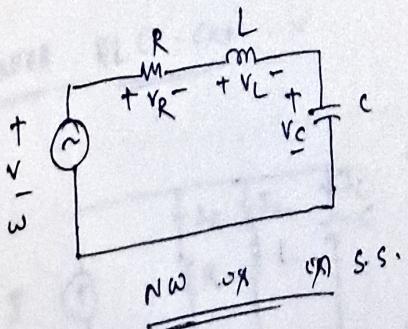


$$V_R = IR$$

$$V_L = I X_L \angle 90^\circ$$

$$V_C = I X_C \angle -90^\circ$$

(i) $V_L > V_C$

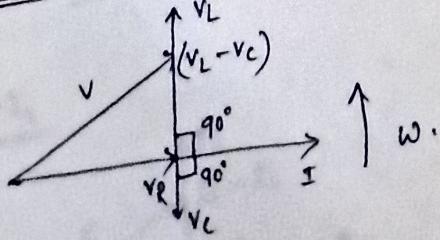


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right) = \text{Impedance angle} = \text{Adm. angle.}$$

$$\cos \phi = \text{P.F.} = \frac{V_R}{V} \quad (\text{lag})$$

(ii) $v_c > v_L$

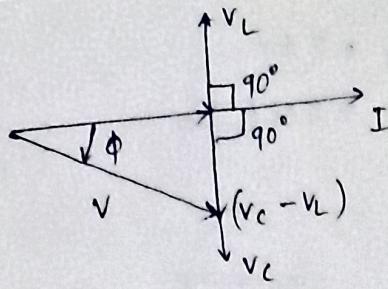


$$V = \sqrt{v_R^2 + (v_c - v_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{v_c - v_L}{v_R} \right)$$

= imp. angle = adm. angle

$$\cos \phi = P.F. = \frac{v_R}{V} \text{ (real)}$$



(iii) $v_L = v_c$

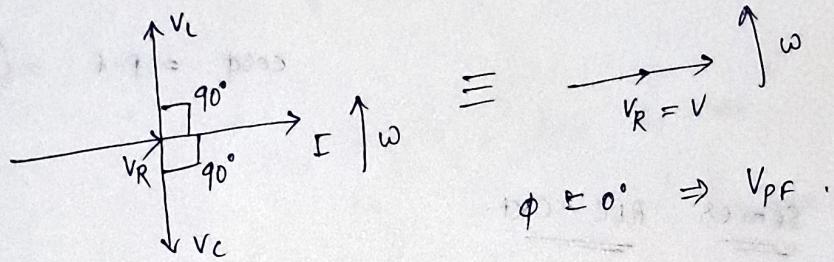

$$\phi = 0^\circ \Rightarrow V_{PF}$$


(4)

parallel RL - Ckt

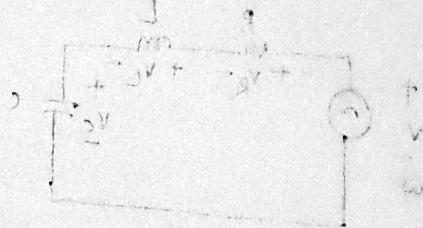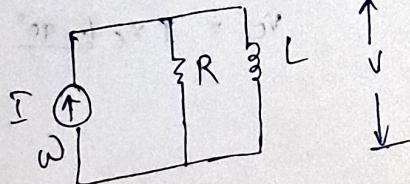

$$V$$


(5) Parallel RC - Ckt

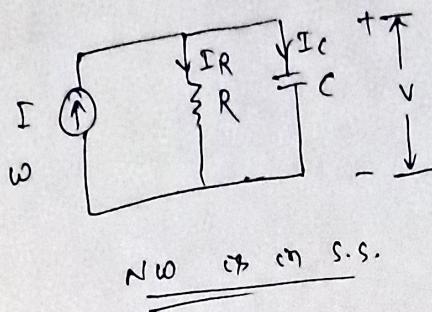

$$I_R = \frac{V}{R}$$

$$I_C = \frac{V}{Z_C}$$
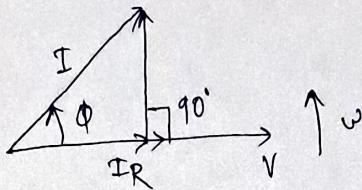
$$= \frac{V}{X_C} \underbrace{[90^\circ]}_{\text{in phase}}$$




$$I = \sqrt{I_R^2 + I_C^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C}{I_R} \right) = \text{imp. angle}$$

$= \text{Adm. angle}$

$$\cos \phi = \text{P.f.} = \left(\frac{I_R}{I} \right) \text{ (lead.)}$$

(6) Parallel RLC - Ckt

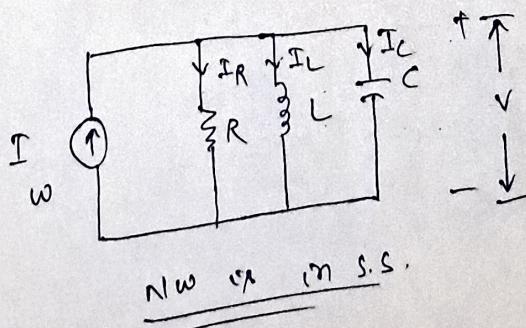


$$I_R = \frac{V}{R}$$

$$I_L = \frac{V}{X_L} \underbrace{[90^\circ]}_{\text{lagging}}$$

$$I_C = \frac{V}{X_C} \underbrace{[90^\circ]}_{\text{leading}}$$

(i)

$I_C > I_L$

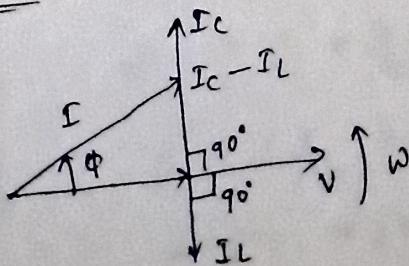


$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$

$$\phi = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$$

$= \text{imp. angle} = \text{Adm. angle}$
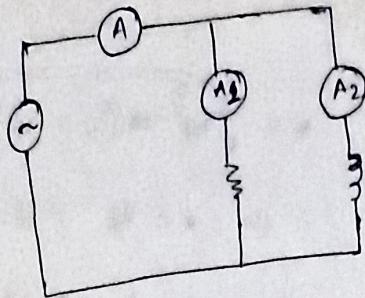
$$\cos \phi = \text{P.f.} = \frac{I_R}{I} \text{ (lead)}$$



A₁ reads 8 A

A₂ reads 6 A

Then A reads .


Now it is in S.S.

By KCL in P-D \Rightarrow

$$\begin{aligned} I &= I_R + I_L = \frac{V}{Z_R} + \frac{V}{Z_L} \\ &= \frac{V}{R} - j \frac{V}{X_L} \\ &= (8 - j6) \text{ A} \end{aligned}$$

$$I = \sqrt{8^2 + 6^2} = 10 \text{ A}$$
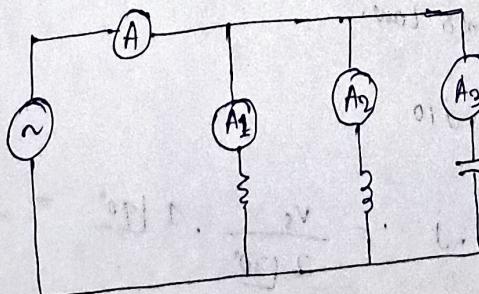
$$\text{P.F.} = \frac{I_R}{I} = \frac{8}{10} = 0.8 \text{ (lag)}$$



A₁ reads 6 A

A₂ reads 12 A

A₃ reads 20 A

Then A reads .

By KCL in P-D \Rightarrow


$$\begin{aligned} I &= I_R + I_L + I_C \\ &= \frac{V}{Z_R} + \frac{V}{Z_L} + \frac{V}{Z_C} \\ &= \frac{V}{R} - j \frac{V}{X_L} + j \frac{V}{X_C} \\ &= 6 - j12 + j20 \\ &= (6 + j8) \text{ A} \end{aligned}$$

$$I = \sqrt{6^2 + 8^2} = 10 \text{ A}$$

$$\text{P.F.} = \frac{I_R}{I} = \frac{6}{10} = 0.6 \text{ (load)}$$

A)

Det - I.

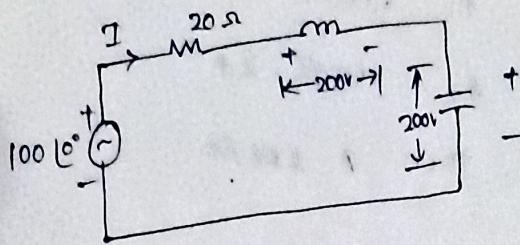

$$v = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\Rightarrow v = V_R = I \cdot R$$


$$\Rightarrow 100 = I \cdot 20 \Rightarrow I = 5A$$

N.W. is in S.S.

$$\therefore P.F. = \frac{V_R}{V} = \frac{V_R}{V_R} = 1$$

B)

The angle betw. V_L & V_S is

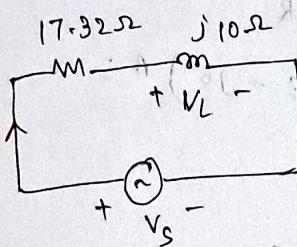

N.W. is in S.S.

$$V_L = I \cdot Z_L \quad | \text{ by Ohm's Law}$$


$$= \frac{V_S}{10\sqrt{3} + j10}$$

$$= \frac{V_S}{\sqrt{3} + j} \cdot j$$

$$= \frac{V_S}{2} \angle 30^\circ \cdot 1 \angle 90^\circ = \frac{V_S}{2} \angle 60^\circ$$

C)

Det I.

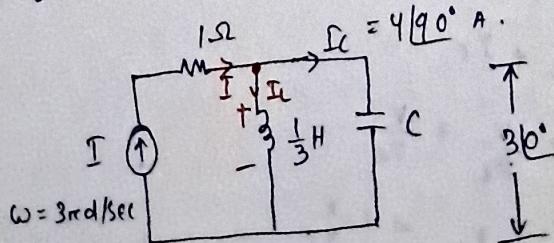

N.W. is in S.S.

$$I_L = \frac{V}{Z_L} = \frac{V}{j\omega L} = \frac{30^\circ}{j3 \cdot \frac{1}{3}} = \frac{30^\circ}{1190^\circ} = 31 - 90^\circ A$$


By KCL in P-D $\Rightarrow I = I_L + I_C$

$$= 31 - 90^\circ + 4190^\circ$$

$$= -j3 + j4$$

$$= j1 = 1190^\circ A$$


Q11 The phasor I_1 leads I_2 by —

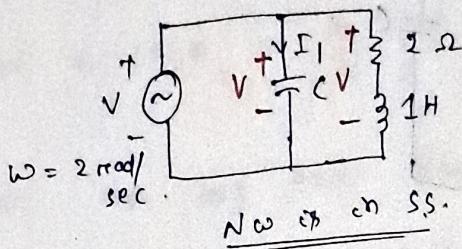


Soln

$$I_1 = I_C = \frac{V}{Z_C} = \frac{V}{j\omega C} = \frac{V}{j2 \cdot 10^{-6}} = 1190^\circ$$
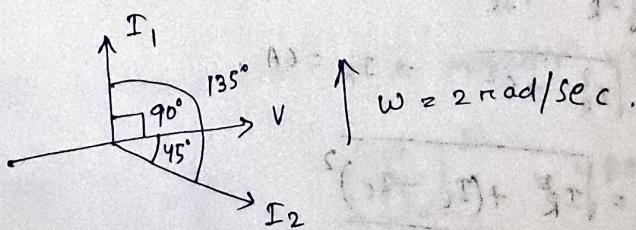
$$I_2 = \frac{V}{Z + j\omega L} = \frac{V}{2 + j2} = \frac{V}{2\sqrt{2}} = 1145^\circ$$



Q11

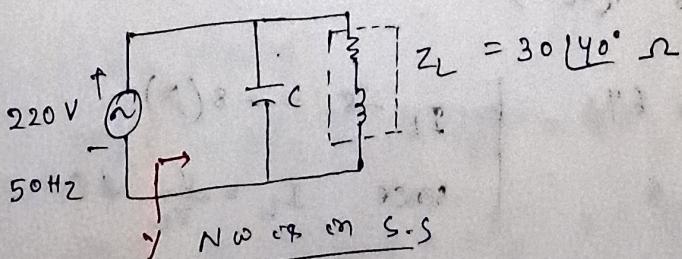

what value of 'C' will result a unity P.F at the a.c source

(A)

$$Y = \frac{1}{Z_C} + \frac{1}{Z_L}$$

$$= \frac{1}{(\frac{1}{j\omega C})} + \frac{1}{30140^\circ}$$

$$Y = j\omega C + \frac{1}{30} \left[-40^\circ \right]$$


$$Y = j\omega C + \frac{1}{30} (\cos 40^\circ - j \sin 40^\circ)$$

$$j\omega term = 0 \Rightarrow$$

$$\Rightarrow \omega C = \frac{\sin 40^\circ}{30}$$

$$\Rightarrow C = \frac{\sin 40^\circ}{2\pi \times 50 \times 30} = 68.1 \mu F$$

Q1

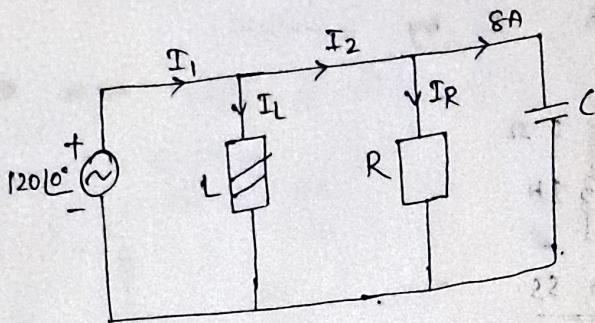

Now in SS

$$\text{if } |I_1| = |I_2| = 10 A$$

then I_L & I_R are

$$I_2 = \sqrt{I_R^2 + I_C^2}$$

$$\Rightarrow 10 = \sqrt{I_R^2 + 8^2} = I_R = 6 A$$

$$I = I_1 = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$10 = \sqrt{6^2 + (I_L - 8)^2}$$

$$\Rightarrow (I_L - 8)^2 = 64$$

$$\Rightarrow I_L - 8 = \pm 8$$


$$I_L - 8 = -8 \quad (\text{X})$$

$$\text{since } I_L = \frac{V}{Z_L} \neq 0$$

$$\text{so, } I_L - 8 = 8$$

$$\Rightarrow I_L = 16 A$$

$I_L > I_C$

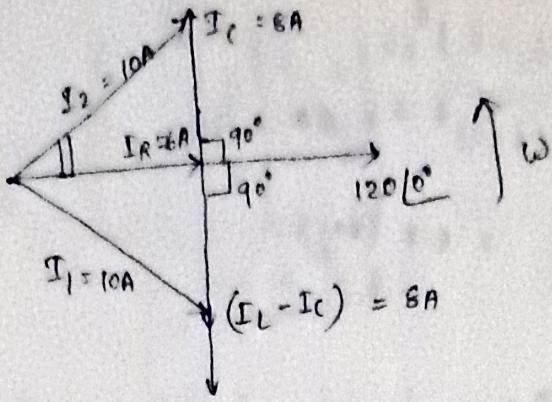


$\rightarrow I_2$ leads 120° by $\tan^{-1} \frac{8}{6}$

$\rightarrow I_1$ lags " " "

$$\rightarrow \text{P.f.} = \cos \phi = \frac{I_R}{I} = \frac{\text{Re}}{I} = \frac{6}{10} = 0.6 \text{ (lag)}$$

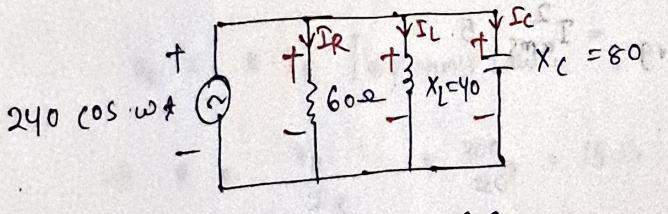Q11 Det. the avg. power dissipated and the P.F. of the Ckt.



N.W. op. on S.S.

$V_R(t) = 240 \cos \omega t$ = A periodic voltage.

$$\Rightarrow P_{\text{avg.}} = \frac{V_{\text{rms}}^2}{R} = \frac{(240/\sqrt{2})^2}{60} = 480 \text{ W.}$$

$$V = 240 \text{ } 120^\circ$$

$$|I_R| = \left| \frac{V}{R} \right| = \frac{240}{60} = 4 \text{ A.}$$

$$|I_L| = \left| \frac{V}{Z_L} \right| = \frac{V}{X_L} = \frac{240}{40} = 6 \text{ A.}$$


$$|I_C| = \left| \frac{V}{Z_C} \right| = \frac{V}{X_C} = \frac{240}{80} = 3 \text{ A}$$

Since $I_L > I_C \Rightarrow$ inductive nature of the Ckt.

$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$= \sqrt{4^2 + (6-3)^2} = 5A$$
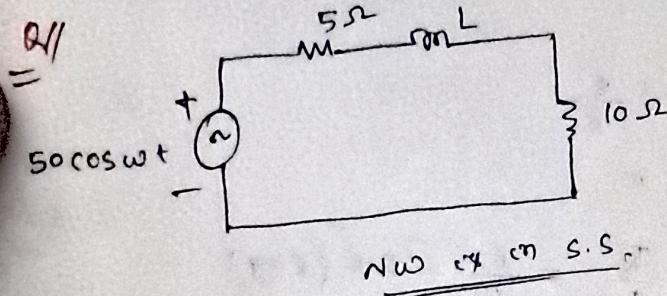
$$P_f = \frac{I_R^2}{I} = \frac{4}{5} = 0.8 \text{ (lag)}$$



if the power dissipated in 5Ω resistor is 10Watt, then
the p.f. of the Ckt.

A) $P_{5\Omega} = 10W = P_{avg} = I_{rms}^2 \cdot 5$

$$\Rightarrow I_{rms} = \sqrt{2} A$$

$$P_{diss} = P_{abs.}$$


$$\Rightarrow V_{rms} \cdot I_{rms} \cdot \cos\phi = I_{rms}^2 \cdot (5 + 10)$$

$$\Rightarrow \frac{50}{\sqrt{2}} \cdot \sqrt{2} \cdot \cos\phi = (\sqrt{2})^2 \cdot 15$$

$$\Rightarrow \text{p.f.} = \cos\phi = \frac{30}{50} = 0.6 \text{ (lag.)}$$

~~ans~~ A $159.23 \mu F$ capacitor is parallel with a resistor

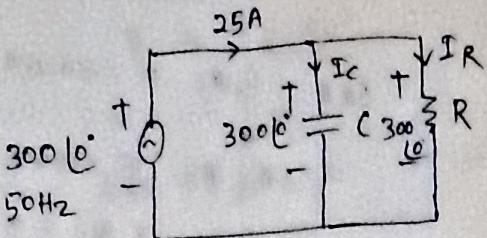'R' draws a current of 25A from a 300V, 50Hz supply. Det. the freq. at which the ckt draws the same 25A from a 360V supply.



No in m.s.s

$$|I_C| = \left| \frac{V}{Z_C} \right| = \left| \frac{V}{\frac{1}{j\omega C}} \right| = V \omega C$$

$$= 300 \times 2\pi \times 50 \times 159.23 \times 10^{-6}$$


$$\approx 15 A$$

$$\Rightarrow I_R = \sqrt{I^2 - I_C^2}$$

$$= \sqrt{25^2 - 15^2} = 20 A$$

$$V_R = R \cdot I_R \quad | \text{ By ohm's Law}$$
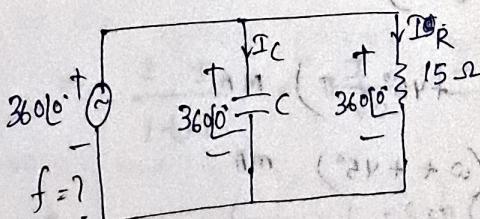
$$\Rightarrow R = \frac{V_R}{I_R} = \frac{300}{20} = 15 \Omega$$



$$\text{The new } I_R = \frac{V_R}{R} = \frac{360}{15} = \frac{360}{15} = 24 A$$

So, the required

$$I_C = \sqrt{25^2 - 24^2}$$

$$\Rightarrow V \omega C = 7$$


$$\Rightarrow 360 \times 2\pi \times f \times 159.23 \times 10^{-6} = 7$$

$$\Rightarrow f = 19.4 \text{ Hz}$$


Obs:

$$I_C = \frac{V}{Z_C} \quad Z_C = \frac{1}{j\omega C} \Omega$$
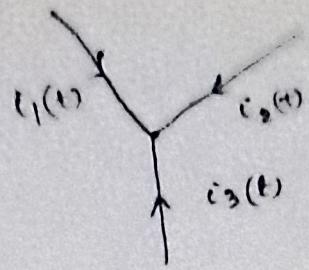
$$f \downarrow \Rightarrow Z_C \uparrow \Rightarrow I_C \downarrow$$



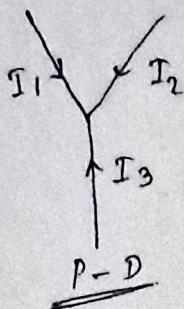Let $i_1(t) = -\sin \omega t \text{ mA}$
 $i_2(t) = \cos \omega t \text{ mA}$
 then $i_3(t) = ?$



BY KCL \Rightarrow

$$-I_1 - I_2 - I_3 = 0$$

$$\Rightarrow I_3 = -(I_1 + I_2)$$

$$i_1(t) = \cos(\omega t + 90^\circ) \text{ mA}$$

$$I_1 = 1(90^\circ) = j1$$

$$I_2 = 1(0^\circ) = 1+j0$$

$$I_3 = -1-j1 = -a-jb = \sqrt{a^2+b^2} \left[\pi + \tan^{-1} b/a \right]$$


$$= \sqrt{2} \left[\pi + 45^\circ \right] = \sqrt{2} e^{j(\pi+45^\circ)}$$

$$i_3(t) = R.P [I_3 \cdot e^{j\omega t}] \text{ mA.}$$

$$= \sqrt{2} \cos(\omega t + 45^\circ + \pi) \text{ mA}$$

$$= -\sqrt{2} \cos(\omega t + 45^\circ) \text{ mA.}$$

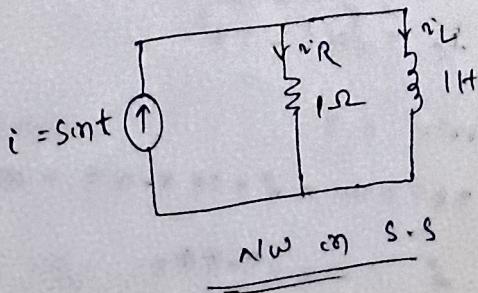Q11 Det. the steady state current i_R & i_L .



$$I = 1 \angle -90^\circ$$

$$Z_R = 1 \Omega$$

$$Z_L = j\omega L \Omega = j1 \Omega$$

$$i_R = \frac{I \cdot j1}{1+j1} = \frac{I \cdot 1 \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = \frac{I}{\sqrt{2}} \angle 45^\circ$$

$$\Rightarrow i_R = \frac{1}{\sqrt{2}} \cdot 1 \cdot \sin(t + 45^\circ) A$$

Another method :-

$$\text{By inverse phasor approach} \Rightarrow i_R = \frac{I \times j1}{1+j1}$$

$$i_R = \frac{I}{\sqrt{2}} \angle 45^\circ = \frac{1 \angle 90^\circ}{\sqrt{2}} \angle 45^\circ = \frac{1}{\sqrt{2}} \angle 45^\circ - 90^\circ e^{j(45-90)}$$

$$\Rightarrow i_R = R \cdot P [i_R \cdot e^{j1 \cdot t}]$$

$$\Rightarrow i_R = \frac{1}{\sqrt{2}} \cos(t + 45^\circ - 90^\circ)$$

$$= \frac{1}{\sqrt{2}} \sin(t + 45^\circ) A$$

$$i_L = \frac{I \cdot 1}{1+j1} = \frac{I}{\sqrt{2}} \angle -45^\circ$$

$$\Rightarrow i_L = \frac{1}{\sqrt{2}} \cdot 1 \cdot \sin(t - 45^\circ) A$$


Check:

$$\text{By KCL} \Rightarrow i_R + i_L = \sin t = i$$

The Resonance.

Resonance in the electric Ckt is because of the presence of both the energy storing elements called the inductor and the capacitor. At a fixed freq. called ' ω_0 ', the 'L & C' element will exchange the energy freely as a func of time, which results the sinusoidal oscillations either across-inductance or across capacitor.

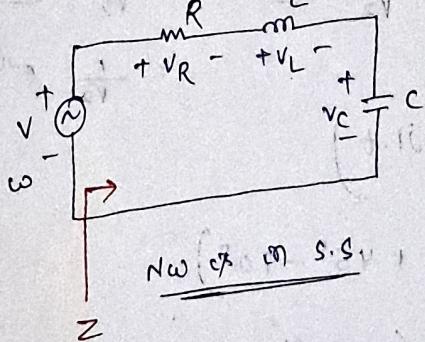① The series RLC Ckt \rightarrow Series Resonance.



Important


$$\rightarrow V = Z \cdot I$$


in series the current flowing through all the elements are the same.

As $Z \propto$ more $\Rightarrow V \propto$ more \Rightarrow that nature of the Ckt

$$\rightarrow Z = Z_R + Z_L + Z_C$$
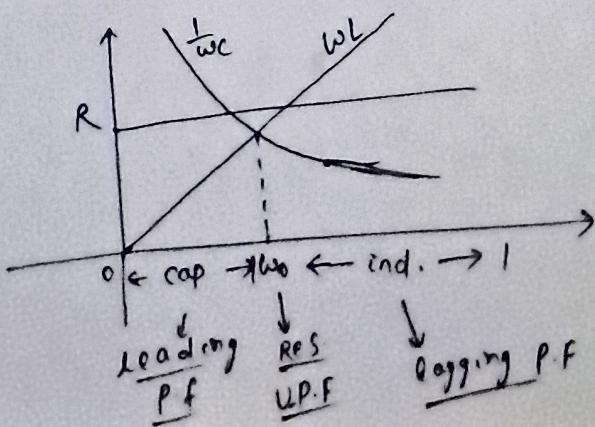
$$Z(j\omega) = R + j \left(\omega L - \frac{1}{\omega C} \right)$$



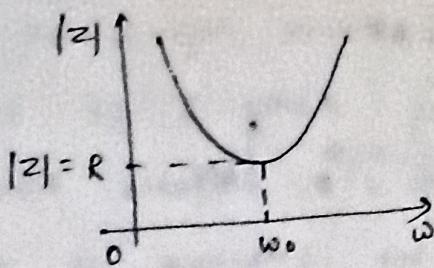

$$\rightarrow \omega = \omega_0 \Rightarrow \frac{1}{\omega_0 C} = \omega_0 L \\ \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$\Rightarrow Z(\omega_0) = R$$

Since $I = \frac{V}{Z}$.

$$\Rightarrow I = \frac{V}{R} = \text{The response at resonance.}$$

$$\rightarrow \underline{\omega = \omega_0}$$

$$V_R = IR = \frac{V}{R} \cdot R \Rightarrow V_R = V$$

$$V_L = I \cdot Z_L = \frac{V}{R} \cdot j\omega_0 L \Rightarrow V_L = QV [90^\circ]$$

$$\text{where } Q = \frac{\omega_0 L}{R}$$

$$V_C = I \cdot Z_C = \frac{V}{R} \cdot \frac{1}{j\omega_0 C} \Rightarrow V_C = QV [-90^\circ]$$

$$\text{where } Q = \frac{1}{\omega_0 CR}$$


Check:

$$\text{By KVL} \Rightarrow V_R + V_L + V_C = V + jQV - jQV \\ = V.$$

Obs! Here $V_L + V_C = 0$ \Rightarrow LC-combination \propto like

a S.C.

The phasor dia.

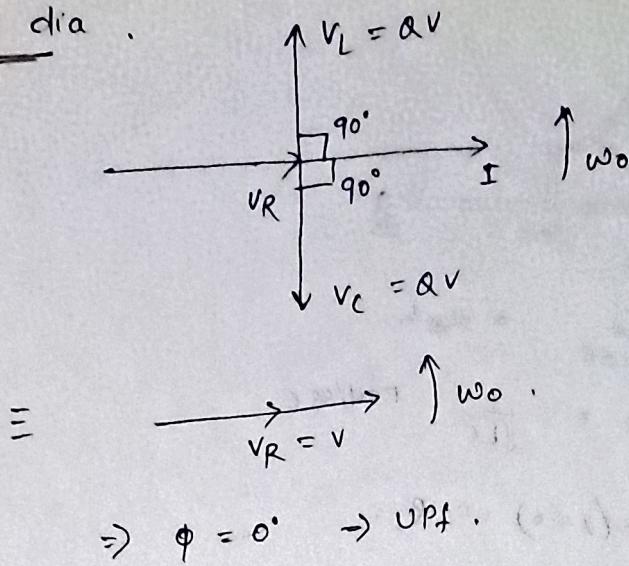


→ The freq. resp.

$$|I| = \left| \frac{V}{Z} \right| = \frac{V}{R^2 + (WL - \frac{1}{\omega C})^2}$$

$$\omega = 0 \Rightarrow |I| = 0$$

$$\omega = \omega_0 \Rightarrow |I| = \frac{V}{R} = I_m$$

$$\omega = \infty \Rightarrow |I| = 0$$

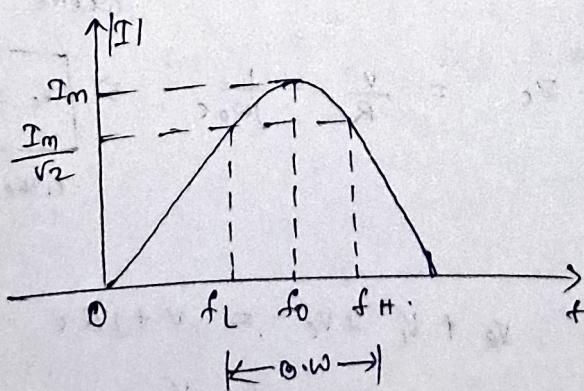

$\therefore \Delta \omega = f_H - f_L = f_0/Q$
$\sqrt{f_H \cdot f_L} = f_0$

where $Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$

→ At resonance the impedance reaches a minimum value, and hence the ckt acts as max. current ($I = \frac{V}{Z}$), so called ACCEPTOR Ckt.

→ Since the voltages across 'L' & 'C' elements are magnified by Q-times (Their amplification is due to the stored energies in L & C elements), the series RLC Ckt at Resonance are called as the voltage magnification Ckts.

The oscillations phenomenon →

$$\text{Let } V(t) = V_m \cos \omega_0 t$$

$$\omega = \omega_0 \Rightarrow Z = R$$

$$\Rightarrow i(t) = \frac{V_m}{R} \cos \omega_0 t = \frac{V_m}{R} \equiv i_L = i_C$$

$$\rightarrow V_C = \frac{1}{C} \int i_C dt$$

$$= \frac{V_m}{R \omega_0 C} \sin \omega_0 t = \frac{1}{2} \omega_0 C = \frac{1}{2} \omega_0 \cdot \frac{1}{\omega_0} = \frac{1}{2}$$

$$\rightarrow P_{avg} = I_{rms}^2 \cdot R$$

$$= \left(\frac{V_m}{R} \right)^2 \cdot R = \frac{V_m^2}{2R} (\omega)$$

→ The total energy stored in the Ckt at resonance of

$$W(t) = W_L(t) + W_C(t)$$


$$= \frac{1}{2} L \cdot i_L^2(t) + \frac{1}{2} C \cdot V_C^2(t)$$

$$= \frac{1}{2} L \cdot \frac{V_m^2}{R^2} \cos^2 \omega_0 t + \frac{1}{2} C \cdot \frac{V_m^2}{R^2 \omega_0^2 C^2} \sin^2 \omega_0 t$$

$$\left(\because \omega_0 = \frac{1}{\sqrt{LC}} \right)$$

$$\Rightarrow \omega_0^2 L = \frac{1}{C} \Rightarrow \omega_0^2 C = \frac{1}{L}$$
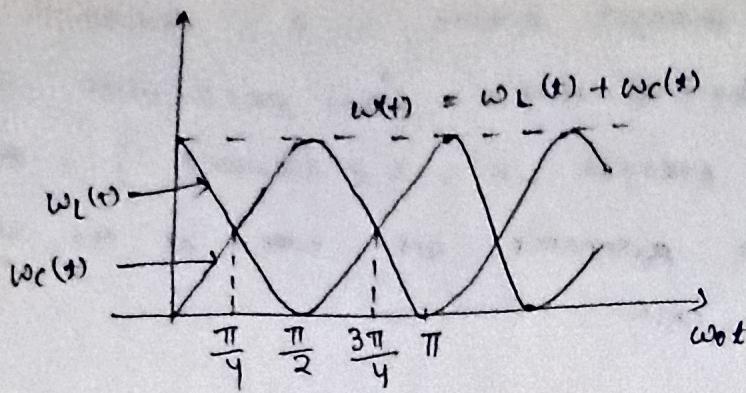
$$W(t) = \frac{1}{2} \cdot \frac{V_m^2}{R^2} (J)$$



$$\rightarrow Q = \frac{w_0 \times \text{max. energy stored in } L \text{ or } C \text{ at resonance}}{\text{Avg. power dissipated at resonance.}}$$

$$= w_0 \times \frac{\frac{1}{2} L \frac{V_m^2}{R^2}}{\frac{1}{2} \frac{V_m^2}{R}} = \frac{w_0 L}{R} = \frac{w_0^2 L}{w_0 R} = \frac{1}{w_0 C R}$$

$$\Rightarrow Q = \frac{w_0 L}{R} = \frac{1}{w_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


\rightarrow so, the Q-factor is a function of CKT constants. As Q is more than the CKT is said to be more selective and hence the oscillations produced are high quality in nature.

\rightarrow As $R \rightarrow 0 \Rightarrow z \rightarrow 0 \Rightarrow \phi \rightarrow \infty \Rightarrow B.W \rightarrow 0$

$\Rightarrow f_H - f_L \rightarrow 0 \Rightarrow f_H = f_L = f_0 \times (\text{not possible})$

which is impossible to achieve, since the violation of KVL in the CKT i.e. the voltage source gets short circuited.

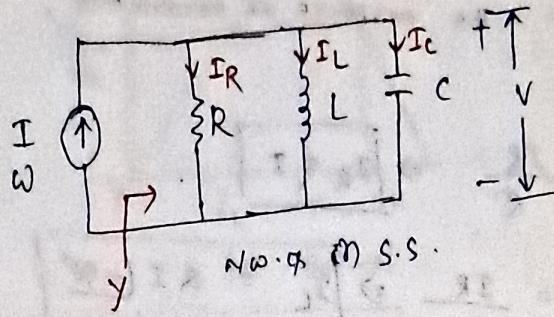② The parallel RLC CKT \rightarrow (parallel Resonance)





Important \rightarrow $I = Y \cdot V$

in parallel the voltage across all the elements are the same.

AS Y is more $\Rightarrow I$ is more \Rightarrow that nature of the CKT.

$$\rightarrow Y = Y_R + Y_L + Y_C$$
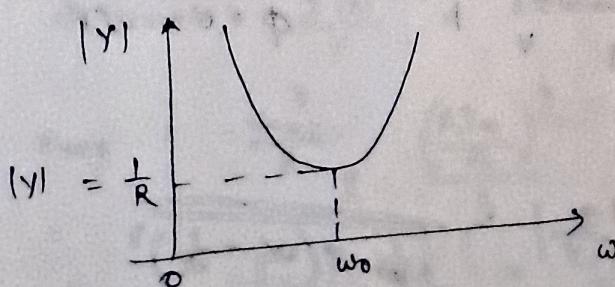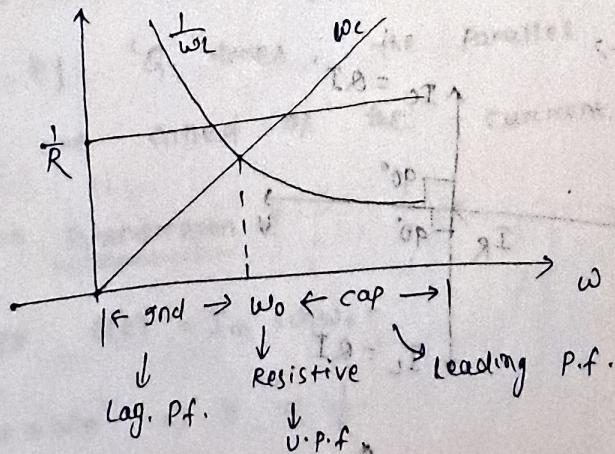
$$\Rightarrow Y(j\omega) = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$



$$\rightarrow \omega = \omega_0 \Rightarrow \frac{1}{\omega_0 L} = \omega_0 C \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$

$$\Rightarrow Y(j\omega_0) = \frac{1}{R}$$

$$\text{Since } V = \frac{I}{Y} = \frac{I}{(\frac{1}{R})}$$

$V = IR$ = The response at resonance.

$$IR = \frac{V}{R} = \frac{IR}{R} \Rightarrow IR = I$$

$$IL = \frac{V}{Z_L} = \frac{IR}{j\omega L} \Rightarrow IL = QI (-90^\circ)$$

where $Q = \frac{R}{\omega_0 L}$

$$IC = \frac{V}{Z_C} = \frac{IR}{\frac{1}{j\omega C}} \Rightarrow IC = QI 90^\circ$$


where $Q = \omega_0 C R$

Check:

$$\text{BY KCL} \Rightarrow IR + IL + IC = I - jQI + jQI = I$$

OBS: Hence $IL + IC = 0 \Rightarrow$ LC-combination ex. like an O.C.

The phasor dia. \rightarrow

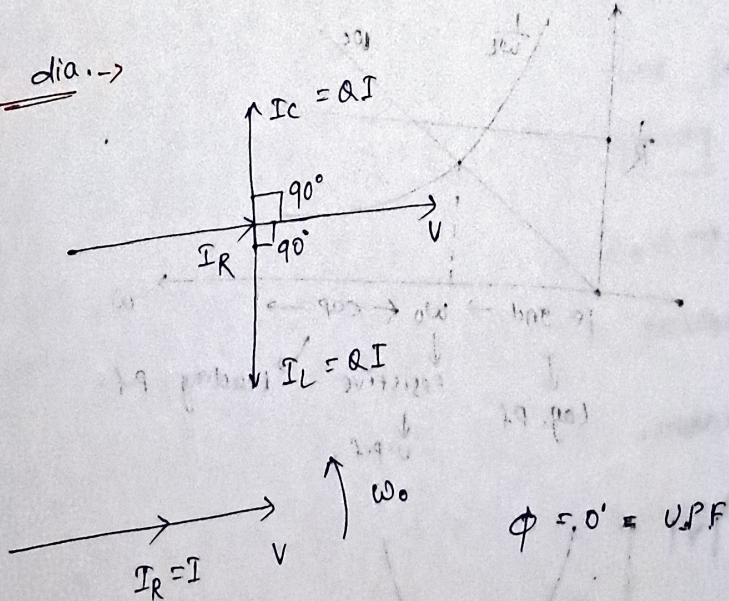


The freq. resp. :-

$$V = \left| \frac{I}{Y} \right| = \sqrt{\frac{I^2}{R^2} + \left(\omega C - \frac{1}{\omega L} \right)^2}$$

$$\omega = 0 \Rightarrow |V| = 0$$

$$\omega = \omega_0 \Rightarrow |V| = IR = V_m$$

$$\omega = \infty \Rightarrow |V| = 0$$

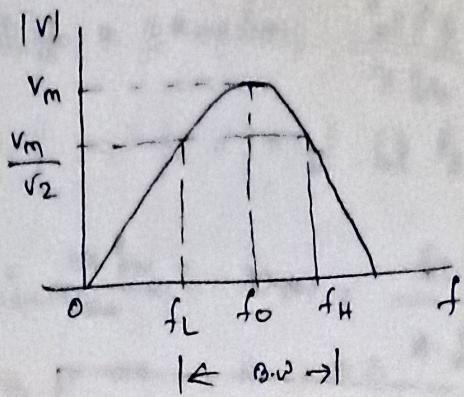

$$B \cdot \omega = f_H - f_L = \frac{f_0}{Q}$$

where $Q = \frac{R}{\omega_0 C} = \omega_0 C R$

$$\sqrt{f_H \cdot f_L} = f_0$$

- At resonance admittance reaches a min. value and hence the circuit rejects minimum current. ($I = Y \cdot V$), so called the rejector circuit.
- Since the currents through 'L' and 'C' elements are magnified by ' Q ' times, the parallel RLC circuit at resonance are called as the current magnification circuit.

The oscillation phenomenon

$$\text{Let } i(t) = I_m \sin \omega t$$

$$\omega = \omega_0 \Rightarrow Y = \frac{1}{R}$$

$$\Rightarrow V(t) = \frac{I(t)}{Y} = R I_m \sin \omega t = V_R(t) = V_L(t) = V_C(t)$$

$$\rightarrow P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R} = \frac{\left(R I_m \right)^2}{\frac{\sqrt{2}}{R}} = \frac{1}{2} I_m^2 \cdot R (\omega)$$

$$\rightarrow i_L = \frac{1}{L} \int V_L dt = - \frac{R I_m}{\omega_0 L} \cos \omega t$$

$$\begin{aligned} \rightarrow \omega(t) &= \omega_C(t) + \omega_L(t) \\ &= \frac{1}{2} (V_C^2(t) + \frac{1}{2} L \cdot i_L^2) \end{aligned}$$

$$= \frac{1}{2} L \cdot \frac{R^2 I_m^2}{\omega_0^2 L^2} \cos^2 \omega_0 t + \frac{1}{2} C R^2 I_m^2 \sin \omega_0 t.$$

$$w(t) = \frac{1}{2} C R^2 I_m^2 \sin \omega_0 t.$$


$$\rightarrow Q = \omega_0 \times \frac{\frac{1}{2} C R^2 I_m^2}{\frac{1}{2} I_m^2 \cdot R} = \omega_0 C R = \frac{\omega_0^2 R C}{\omega_0} = \frac{R}{\omega_0 L},$$

$$Q = \omega_0 C R = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$

$$\rightarrow \text{As } R \rightarrow \infty \Rightarrow Y = \frac{1}{R} \rightarrow 0 \Rightarrow Z \rightarrow \infty \Rightarrow Q \rightarrow \infty$$

$$\rightarrow B \cdot \omega \rightarrow 0 \Rightarrow f_H - f_L \rightarrow 0 \Rightarrow f_L = f_H = f_0 (X)$$

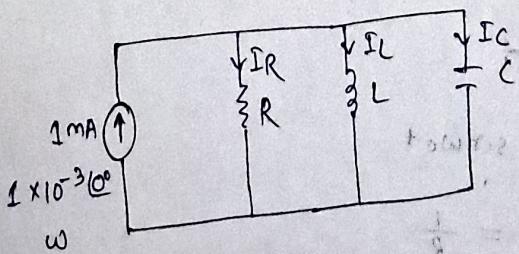\rightarrow So, the CKT operation approaches to a single frequency called the resonant frequency, which is impossible to achieve, since the current source gets open circuited i.e. the violation of KCL of the CKT



$$(a) |I_R| < 1 \text{ mA}$$

$$(b) |I_R + I_L| < 1 \text{ mA}$$

$$(c) |I_R + I_C| > 1 \text{ mA}$$

$$(d) |I_L + I_C| > 1 \text{ mA}$$

At resonance which one of the statements is true.

$$I_R = I, \quad \underline{\omega = \omega_0}$$

$$I_L = Q I \underbrace{-90^\circ}_{= -jQ I}$$

$$I_C = Q I \underbrace{90^\circ}_{= jQ I}$$

$$I_L + I_C = 0$$

$$\rightarrow |I_R + I_L| = |I - j\omega I| = I \sqrt{1+\omega^2} > I$$

$$\rightarrow |I_R + I_C| = |I + j\omega I| = I \sqrt{1+\omega^2} > I$$

Q1 In a series RLC Ckt.

$$V_S = 100, R = 10 \Omega, X_L = 20 \text{ & } X_C = 20,$$

the voltage across the capacitor is

$$\textcircled{A} \quad X_L = X_C \Rightarrow \omega = \omega_0 \Rightarrow V_C = Q V_S [-90^\circ]$$

$$Q = \frac{\omega_0 L}{R} = \frac{X_L}{R} = 2$$

$$Q = \frac{1}{\omega_0 CR} = \frac{X_C}{R} = 2$$

$$\Rightarrow V_C = 200 [-90^\circ] = -j200 \text{ V}$$

Q2 In a series RLC Ckt the Q factor is 100. If all the component are doubled then

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{2R} \sqrt{\frac{2L}{2C}} = \frac{1}{2R} \sqrt{\frac{L}{C}} = \underline{\underline{\frac{1}{2} Q}}$$

Q3 In the above case if the Ckt is parallel.


$$Q = R \sqrt{\frac{C}{L}} = 2R \sqrt{\frac{2C}{2L}} = \underline{\underline{2Q}}$$

Q4 In a series RLC Ckt, the P.F at $f = f_L$ is


$$|I| = \frac{I_m}{R} \quad |I_m| = \frac{V}{R}$$

$$\Rightarrow |Z| = \frac{V}{\sqrt{2}R} \Rightarrow |Z| = \sqrt{2}R$$

$$Z = R + jX = \frac{V}{I}$$

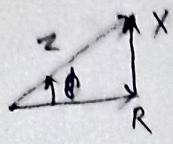

$$Z = R + jX$$

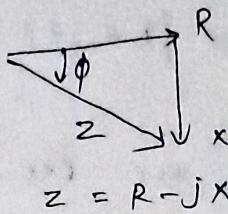

$$Z = R - jX$$

$$\text{P.F.} = \cos\phi = \left(\frac{R}{Z}\right)$$

$$\rightarrow f = f_L \Rightarrow \text{P.F.} = \frac{R}{\sqrt{2}R} = 0.707 \text{ (lead)}$$

$$\rightarrow f = f_H \Rightarrow \text{P.F.} = 0.707 \text{ (lag)}$$

$$\rightarrow f = f_0 \Rightarrow Z = R \Rightarrow \text{P.F.} = \frac{R}{Z} = \frac{R}{R} = 1$$

Q/



in the above case if the Ckt is a parallel RLC then

$$f = f_L \Rightarrow |V| = \frac{V_m}{\sqrt{2}} \quad | V_m = IR |$$

$$\rightarrow \left| \frac{I}{Y} \right| = \frac{IR}{\sqrt{2}} = \frac{I}{\sqrt{2} \text{ ohm}}$$

$$\Rightarrow |Y| = \sqrt{2} \text{ ohm}$$

$$Y = G \pm jB = \frac{I}{V}$$

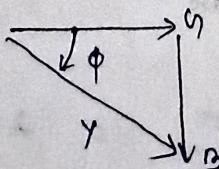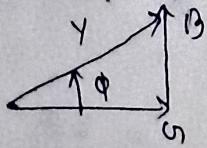


$$\text{P.F.} = \cos\phi = \left(\frac{G}{Y}\right)$$

$$\rightarrow f = f_L \Rightarrow \text{P.F.} = \frac{G}{\sqrt{2} \text{ ohm}} = 0.707 \text{ (lag)}$$

$$\rightarrow f = f_H \Rightarrow \text{P.F.} = 0.707 \text{ (lead)}$$

$$\rightarrow f = f_0 \Rightarrow Y = \frac{1}{R} = G \Rightarrow \text{P.F.} = \frac{G}{Y} = \frac{G}{\frac{1}{R}} = G \cdot R = 1$$

84

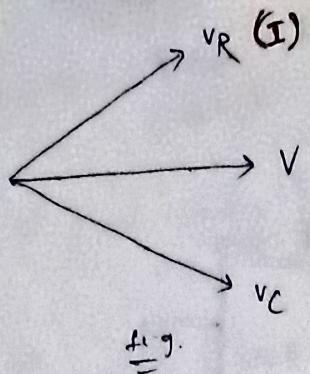

$$(a) f = 0$$

$$(b) f = f_0$$

$$(c) f < f_0$$

$$(d) f > f_0$$

on a series RLC ckt the phasor dia. at a certain freq. is shown in fig., the operating freq.


ex

- (A) $V_R = IR$ (since current reads the voltage, the nature of the ckt is capacitive and hence the operating freq. is $f < f_0$.)

- (B) At resonance, the parallel ckt of the fig. constituted by an iron cored coil and the capacitor will behave like

- (a) an open ckt (b) a s.c (c) pure Resistor of R' .
 (d) A pure resistor of value much higher than R' .

(A)

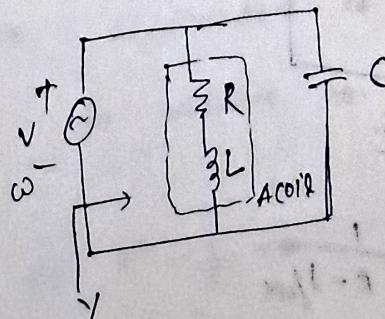

$$\gamma = \gamma_L + \gamma_C = \frac{1}{j\omega L} + \frac{1}{j\omega C}$$

$$= \frac{1}{R+j\omega L} + \frac{1}{j\omega C}$$

$$\Rightarrow \gamma = \frac{R-j\omega L}{R^2 + (\omega L)^2} + j\omega C$$


$$i \text{ term} = 0 \Rightarrow \omega = \omega_0$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{C}{R^2}} \text{ rad/sec.}$$

$$\Rightarrow \gamma = \frac{R}{R^2 + (\omega L)^2} \omega$$

$$z = \frac{1}{Y} = R + \frac{(w_0 L)^2}{R} \gg R$$

QV Det. w_0

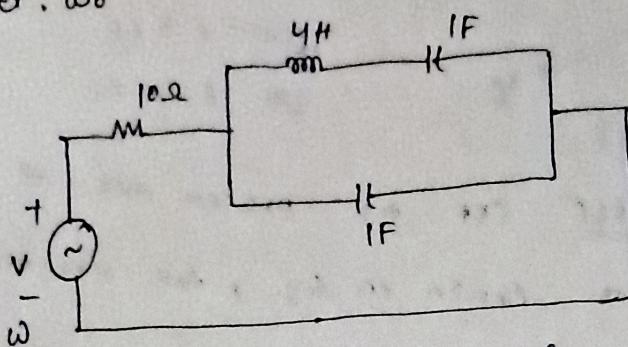

NW exp m S.S

$$z = 10 + \left(j 4 \omega + \frac{1}{j \omega} \right) \parallel \left(\frac{1}{j \omega} \right)$$


$$= 10 + \frac{4 - \frac{1}{\omega^2}}{j(4\omega - \frac{2}{\omega})}$$

$$= 10 - j \left(4 - \frac{1}{\omega^2} \right) \quad \cancel{\text{or}} \quad 4\omega - \frac{2}{\omega}$$

j term. is zero \Rightarrow

$$4 - \frac{1}{\omega^2} = 0 \Rightarrow \omega_0 = \frac{\pi}{2} \text{ rad/sec.}$$

QV

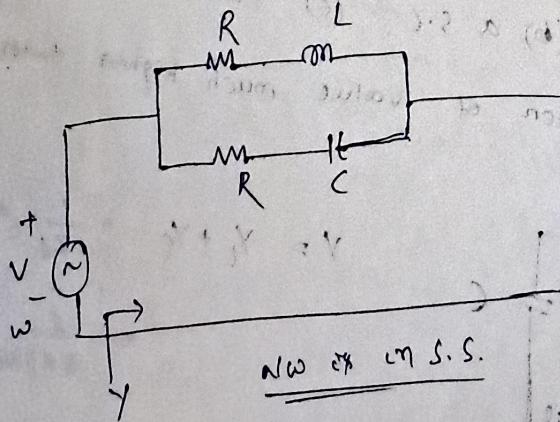

Det. w_0 . what happens
when $L = CR^2$

(A)

$$Y = \frac{1}{R + j\omega L} + \frac{1}{R - j/\omega C}$$

$$= \frac{R - j\omega L}{R^2 + (\omega L)^2} + \frac{R + j/\omega C}{R^2 + (\frac{1}{\omega C})^2}$$

j term = 0 \Rightarrow

$$\frac{w_0 L}{R^2 + (w_0 L)^2} = \frac{\frac{1}{w_0 C}}{R^2 + (\frac{1}{w_0 C})^2}$$

$$\Rightarrow \omega_0 L R^2 + \frac{\omega_0 L}{(\omega_0 C)^2} = \frac{R^2}{\omega_0 C} + \frac{(\omega_0 L)^2}{\omega_0 C}$$

$$\Rightarrow R^2 \left(\omega_0 L - \frac{1}{\omega_0 C} \right) - \frac{\omega_0 L}{\omega_0 C} \left(\omega_0 L - \frac{1}{\omega_0 C} \right) = 0$$

$$\Rightarrow \left(R^2 - \frac{1}{C} \right) \left(\omega_0 L - \frac{1}{\omega_0 C} \right) = 0$$

case (i) if $R^2 - \frac{1}{C} \neq 0$ then $\omega_0 L - \frac{1}{\omega_0 C} = 0$ must for

" j term to be zero

i.e. the ckt will resonant at only one freq. called

$\omega_0 = \frac{1}{\sqrt{LC}}$ rad/sec. then

$$Y = \frac{R}{R^2 + (\omega_0 L)^2} + \frac{R}{R^2 + (\frac{1}{\omega_0 C})^2} \quad \left| \begin{array}{l} \omega_0 = \frac{1}{\sqrt{LC}} \\ R^2 = \frac{1}{C} \end{array} \right.$$

$$\Rightarrow Y = \boxed{\frac{2R}{R^2 + \frac{L}{C}}} \quad \text{Ans}$$

case - ii)

$$\text{if } R^2 - \frac{1}{C} = 0$$

$$\Rightarrow R^2 = \frac{1}{C} \Rightarrow L = CR^2 \quad \text{then j term is zero}$$

and it is independent of frequency. so, the ckt will resonant for infinite no. of frequencies.

case - (iii)

$$\text{if } R^2 - \frac{1}{C} = 0 \quad \text{and} \quad \omega_0 L - \frac{1}{\omega_0 C} = 0$$

$$\text{then } R^2 = \frac{L}{C} \quad \& \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$

i.e. out of infinite no. of resonant frequencies we are

selecting one frequency called ' ω_0 '


$$\Rightarrow Y = \frac{R}{R^2 + (\omega_0 L)^2} + \frac{R}{R^2 + (\frac{1}{\omega_0 C})^2} \quad \left| \begin{array}{l} \omega_0 = \frac{1}{\sqrt{LC}} \\ R^2 = L/C \end{array} \right.$$

$$Y = \frac{2R}{R^2 + \frac{L}{C}}$$

-V

$$R^2 = L/C \Rightarrow Y = \frac{2R}{2R^2} = \frac{1}{R} \Rightarrow Z = R.$$

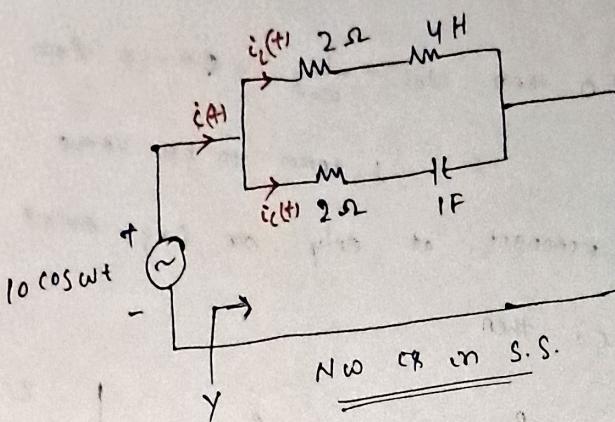Q/ Deter. the avg power dissipated in the ckt at resonance.



A) $\frac{L}{C} = R^2 \rightarrow$ ckt will resonate for all the frequencies.

out of infinite no. of resonant frequencies we are selecting one frequency called $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{2}$ rad/sec

$$\Rightarrow Z = R = 2\Omega$$

$$I = \frac{V}{Z} = \frac{10 \angle 0^\circ}{2} = 5 \angle 0^\circ$$

$$\Rightarrow i(t) = 5 \cos \frac{\pi t}{2} \text{ A.}$$

$$Z_L = j\omega_0 L = j2\Omega$$

$$Z_C = \frac{1}{j\omega_0 C} = -j2\Omega$$

$$I_L = \frac{I \cdot (2 - j2)}{2 + j2 + 2 - j2} = \frac{I}{\sqrt{2}} \angle -45^\circ$$

$$\Rightarrow i_L(t) = \frac{5}{\sqrt{2}} \cos \left(\frac{\pi t}{2} - 45^\circ \right) A.$$

$$I_C = \frac{I}{2-j_2 + 2+j_2}$$


$$= \frac{I}{\sqrt{2}} \angle 45^\circ$$

$$\Rightarrow i_C = \frac{5}{\sqrt{2}} \cos(t+45^\circ) A$$

$$P_{avg} = I_{L_{rms}}^2 R + I_{C_{rms}}^2 R$$

$$= \left(\frac{5}{\sqrt{2}}\right)^2 \cdot 2 + \left(\frac{5/\sqrt{2}}{\sqrt{2}}\right)^2 \cdot 2 = 25 W$$

Q1

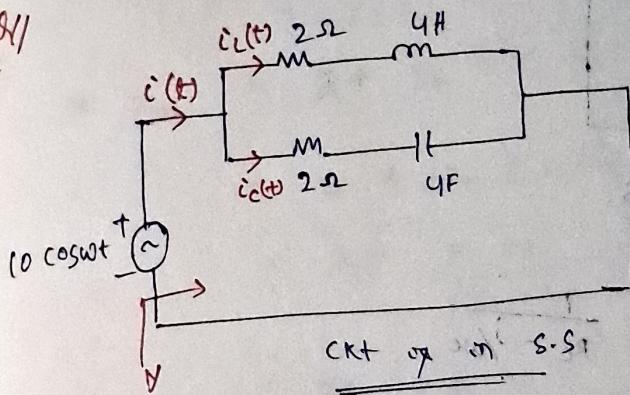

Since $L_C = R^2$, CKt will resonate at only one freq.

$$\text{called } \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \cdot 4}} = \frac{1}{4} \text{ rad/sec.}$$

$$\gamma = \frac{2R}{R^2 + \frac{L}{C}} \omega = \frac{4}{5} \omega$$

$$\omega = \frac{5}{4} \omega$$

$$I = \frac{V}{Z} = \frac{10 \angle 0^\circ}{5/4} = 8 \angle 0^\circ$$

$$\Rightarrow i(t) = 8 \cos \frac{\pi}{4} t$$

$$z_L = j\omega_0 L = j1 \Omega$$


$$z_C = \frac{1}{j\omega_0 C} = -j1 \Omega$$

$$I_L = \frac{I(2 - j1)}{2 + j1 + 2 - j1}$$

$$I_C = \frac{I \cdot (2 + j1)}{2 + j1 + 2 - j1}$$

$$\Rightarrow P_{\text{avg}} = I_{L\text{rms}}^2 \cdot 2 + I_{C\text{rms}}^2 \cdot 2 \quad (\omega)$$

Q/H

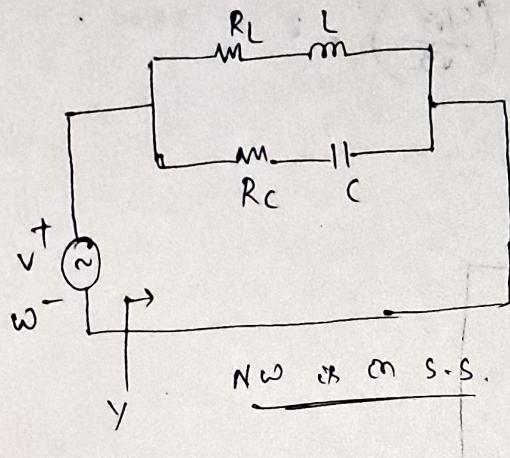

$$Y = \frac{1}{R_L + j\omega L} + \frac{1}{R_C - j/\omega C}$$

$$= \frac{R_L - j\omega L}{R_L^2 + (\omega L)^2} + \frac{R_C + j/\omega C}{R_C^2 + (\frac{1}{\omega C})^2}$$

$$j\text{-term} = 0$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}} \text{ rad/sec.}$$


$$(i) \text{ if } R_L = R_C = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$

$$(ii) \text{ if } R_L = R_C = R \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$

$$(iii) \text{ if } R_C = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{C}{L} R_L^2} \text{ rad/sec.}$$

$$(iv) \text{ if } R_L = 0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \sqrt{1 - \frac{L}{C} R_C^2} \text{ rad/sec.}$$

U-2000 EC 15
8/11

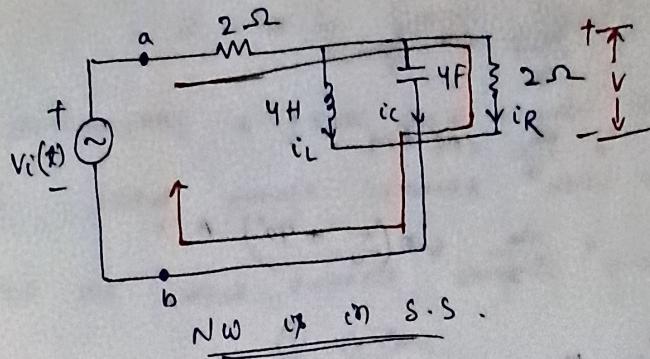

Det. (a) $\omega = \omega_0$ at which Z_{ab} is min.

$$(b) Z_{ab} \Big|_{\omega=\omega_0} = ?$$

(c) if $Vi(t) = V_m \sin \omega_0 t$ then i_R, i_L & i_C are.

$$\textcircled{A} (a) Z_{ab} = 2 + Z_b \parallel Z_C \parallel 2$$

$$= 2 + jX_L \parallel -jX_C \parallel 2$$

$$= 2 + \frac{X_L X_C}{j(X_L - X_C)} \parallel 2.$$

$$Z_{ab} = 2 + \frac{2 X_L X_C}{X_L X_C + j 2(X_L - X_C)}$$

$$= 2 + \frac{2 X_L X_C (X_L X_C - j 2(X_L - X_C))}{(X_L X_C)^2 + 4(X_L - X_C)^2}$$

$$j - \text{term} = 0$$

$$\Rightarrow -2(X_L - X_C) = 0$$

$$\Rightarrow X_L = X_C$$

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{4 \cdot 4}} = \frac{1}{4} \text{ rad/sec}$$

$$(b) Z_{ab} \Big|_{\omega=\omega_0} = 2 + 2 = 4 \Omega$$

$$\text{or } X_L = X_C$$

$$(c) V_i(t) = V_m \sin \omega_0 t = V_m \sin \frac{\pi}{4} t \quad ; \quad Z = 4 \Omega$$

$$i(t) = \frac{V_i(t)}{2} = \frac{V_m}{4} \sin \frac{\pi}{4} t = i_R$$

$$V = 2 \cdot i_R = \frac{V_m}{2} \cdot \sin \frac{t}{4} = V_C = V_L$$

$$i_C = C \frac{dV_C}{dt} = \frac{V_m}{2} \cos \frac{t}{4}$$

$$= \frac{V_m}{2} \sin \left(\frac{t}{4} + 90^\circ \right) A$$

$$\rightarrow i_L = \frac{1}{L} \int V_L dt$$

$$= -\frac{V_m}{2} \cos \frac{t}{4}$$

$$= \frac{V_m}{2} \sin \left(\frac{t}{4} - 90^\circ \right) A$$

OBS!

Hence $i_L + i_C = 0 \Rightarrow LC$ -combination is like an ac.

$$\begin{aligned} & \text{Simplifying } \frac{1}{L} \int (-jX_C) dt + jX_L \\ & \cdot \frac{1}{L} \int \frac{-jX_C}{(jX_L - jX_C)} dt + jX_L \\ & \left(\frac{jX_C}{(jX_L - jX_C)} \right) \frac{1}{jX_C} dt + jX_L \end{aligned}$$