

# CHAPTER-5

# Synchronous Sequential Logic

Digital Design (with an introduction to the Verilog HDL) 6<sup>th</sup> Edition,  
M. Morris Mano, Michael D. Ciletti



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY,  
DESIGN AND MANUFACTURING,  
KANCHEEPURAM

ECE, IIITDM Kancheepuram


# Outline

---

- **Sequential Circuit**
- **Storage Elements: Latches**
- **Storage Elements: Flip-flops**
- **Analysis of Clocked Sequential Circuits**
- **HDL models (Skipped)**
- **State Reduction and Assignment**
- **Design Procedure**
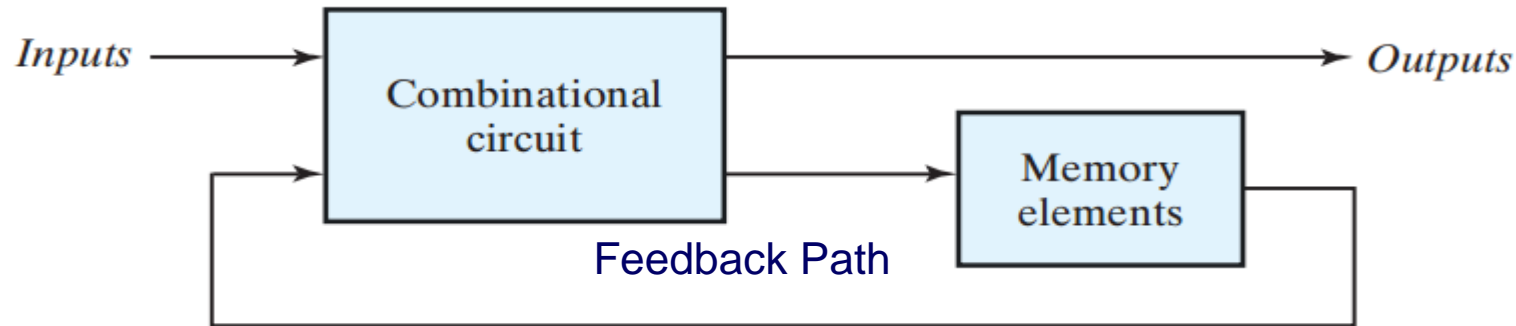
# Sequential Circuits


- Sequential circuits employ **storage elements or feedback path** besides logic gates. The outputs depend on both **memory values** (in the past) and **present values of inputs**.



- Inputs, present state
- Outputs, next state
- A sequential circuit is **specified by a time sequence of inputs, outputs, and internal states**.
 
# Synchronous and Asynchronous

- A **synchronous** sequential circuit: behavior defined at determined discrete instants of time.
- A **asynchronous** sequential circuit: at any instant of time.
- Synchronization is achieved by a timing device called a clock generator, commonly denoted by “clock” or “clk”.



(a) Block diagram




(b) Timing diagram of clock pulses

**FIGURE 5.2**

**Synchronous clocked sequential circuit**



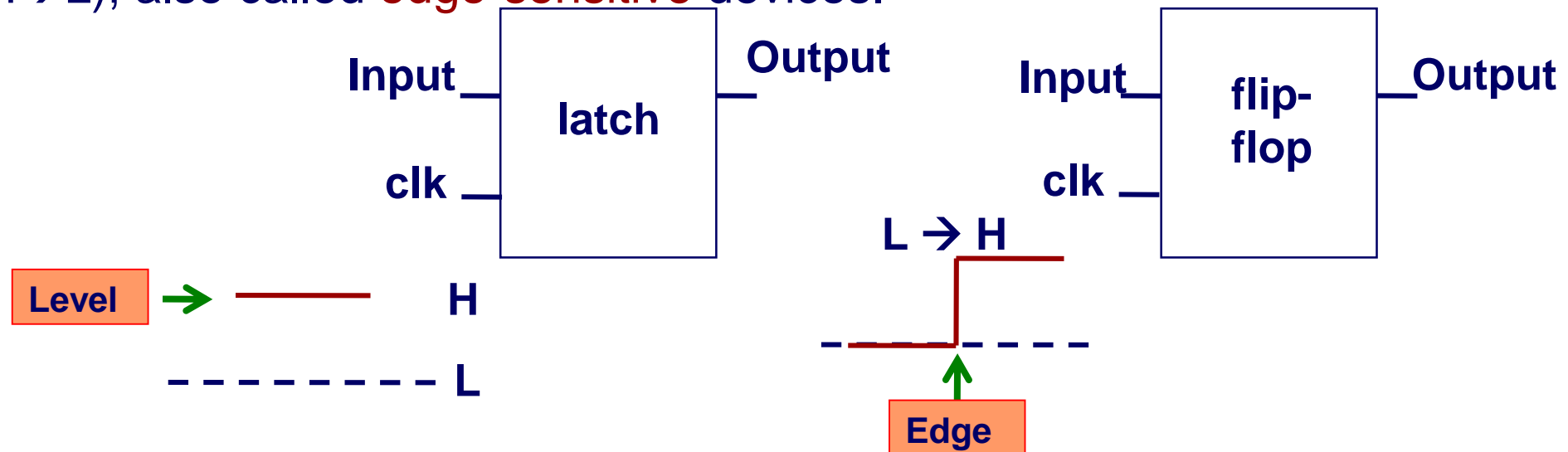
# Storage Elements

- An electronic device that can be used to store one bit of information.
- Two main types of storage elements
  - latch
  - flip-flop
- Latch: the storage element is controlled by signal levels (usually H or L), also called **level sensitive** devices.
- Flip-flop: the storage element is controlled by a clock transition (i.e. L→H or H→L), also called **edge-sensitive** devices.



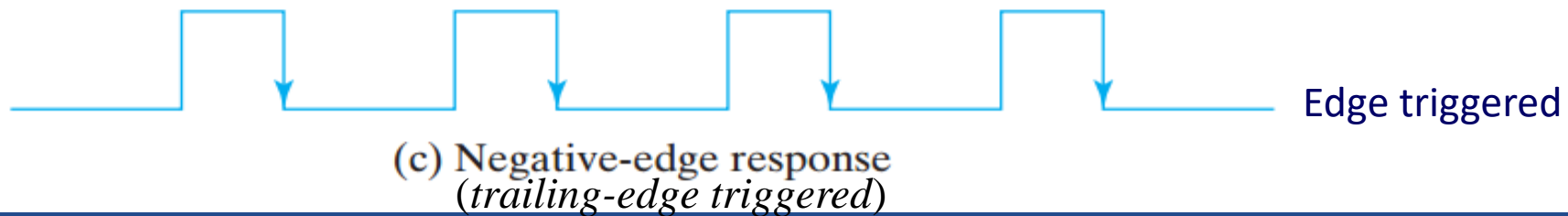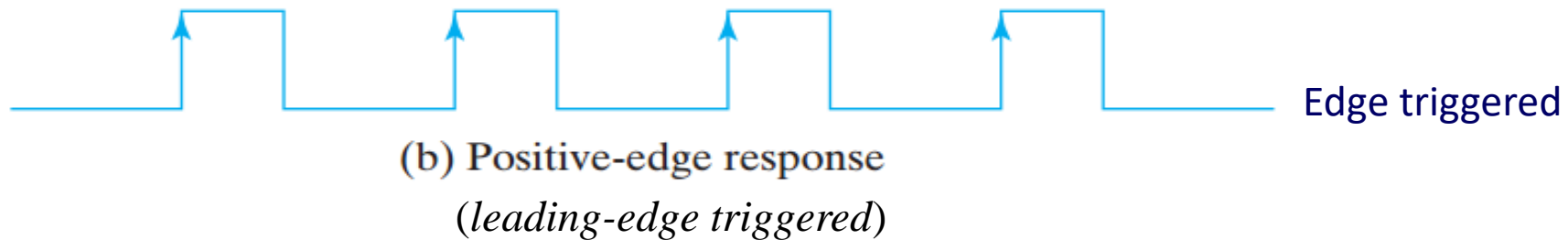 
# Storage Elements

- **Trigger**
  - The state of a latch or flip-flop is switched by a change in the control input.
- Level triggered → latches
- Edge triggered → flip flops


 
# SR Latches with NOR Gates

- The SR latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates, and two inputs labeled  $S$  for set and  $R$  for reset.
- $Q$  and  $Q'$  are normally the complement of each other.  $Q = 1$  and  $Q' = 0$ , the latch is said to be in the **set state**.  $Q = 0$  and  $Q' = 1$ , it is in the **reset state**.
- The SR latches constructed with two cross-coupled NOR gates are **active-high**.










$S$	$R$	$Q$	$Q'$	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$ )
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$ )
1	1	0	0	(forbidden)

(b) Function table

**FIGURE 5.3**  
SR latch with NOR gates

- $S=1, R=0 \rightarrow$  set state ( $Q$  will become 1)
- $S=0, R=1 \rightarrow$  reset state ( $Q$  will become 0)
- When  $S=0$  and  $R=0 \rightarrow$  keep the current value

# SR Latches with NOR Gates

       


$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

(b) Function table

- $S=1, R=0 \rightarrow$  set state ( $Q$  will become to 1)
- $S=0, R=1 \rightarrow$  reset state ( $Q$  will become to 0)
- When  $S=0$  and  $R=0 \rightarrow$  keep the current value




# SR Latch Timing Waveform

 


Assume initial value  $Q_{\text{init}} = 0$

$S$	$R$	$Q$
1	0	1
0	1	0
0	0	Hold

 
 
# SR Latches with NAND Gates

- The SR latches constructed with two cross-coupled NAND gates are **active-low**
  - $S=1, R=0 \rightarrow$  reset state ( $Q$  will become to 0)
  - $S=0, R=1 \rightarrow$  set state ( $Q$  will become to 1)
  - $S=1, R=1 \rightarrow$  unchanged









$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)

(b) Function table

**FIGURE 5.4**  
**SR latch with NAND gates**


What is the difference between SR latches with NOR gates and NAND gates?

# SR Latches with NAND Gates

      

Not mutually complementary

Forbidden!!!

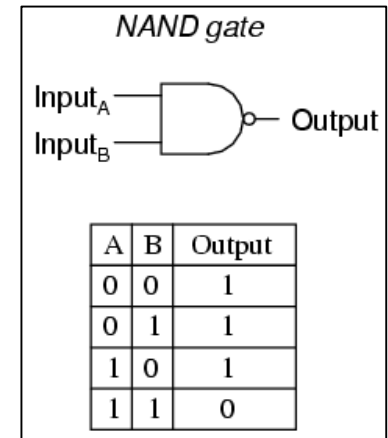


$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)

(b) Function table

- $S=1, R=0 \rightarrow$  reset state ( $Q$  will become 0)
- $S=0, R=1 \rightarrow$  set state ( $Q$  will become 1)
- When  $S=1$  and  $R=1 \rightarrow$  keep the current value
 
# SR Latch with Control Input

- Add an additional control input to determine when the state of the latch can be changed
- $En = 0$ : S and R are disabled (no change at outputs)
- $En = 1$ : S and R are active-high



(a) Logic diagram

$En$	$S$	$R$	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate


(b) Function table

**FIGURE 5.5**

SR latch with control input
 
# D Latch (Transparent Latch)

- Eliminate the indeterminate state in the SR latches
- D latch has only two inputs: D (data) and En (control)
- Use the value of D to set the output value
- The D input goes directly to the S input and its complement is applied to the R input
  - $D=1 \rightarrow S=1, R=0 \rightarrow Q=1$




(a) Logic diagram

<i>En</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

**FIGURE 5.6**  
D latch


# D Latch Timing Waveform

 


Assume initial value  $Q_{\text{init}} = 0$

$En$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state

(b) Function table

 

# Graphic symbols for Latches

 

**FIGURE 5.7**

Graphic symbols for latches

- You should know the operation in your mind when seeing the block diagrams of latches.
- SR latch:  $(S,R) = (1,0) (0,1) (0,0)$
- S'R' latch:  $(S,R) = (0,1) (1,0) (1,1)$ 
  - In the case of a NAND gate latch, bubbles are added to the inputs to indicate that setting and resetting occur with a logic-0 signal.

➤ D latch:  $En, D$

# Storage Elements: Flip-flops

- The state of a latch or flip-flop is switched by a change in the control input. This momentary change is called a **trigger**, and the transition it causes is said **to trigger** the flip-flop.



(a) Response to positive level




(b) Positive-edge response  
(leading-edge  
triggered)



(c) Negative-edge response  
(trailing-edge  
triggered)



# Negative Edge-Triggered D Flip-flops

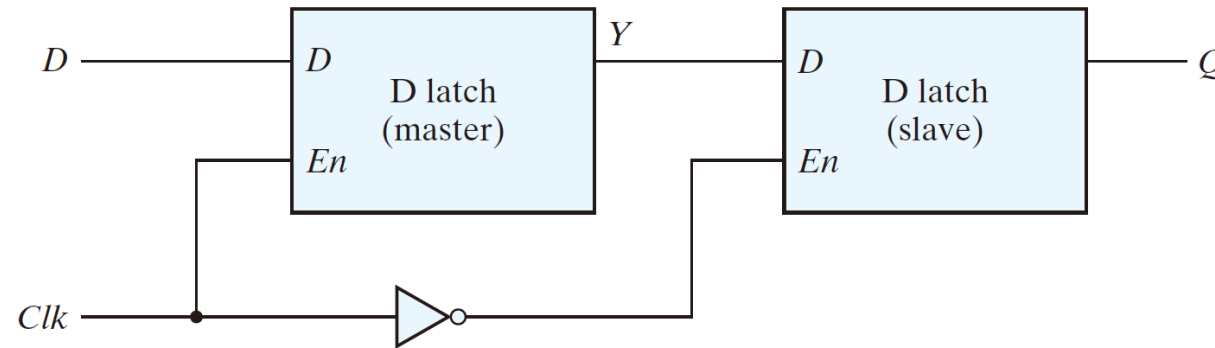


**FIGURE 5.9**  
Master-slave  $D$  flip-flop

- Constructed with two D latches and an inverter
- The first latch (master) is enabled when  $CLK=1$ 
  - the data from the external  $D$  input are transferred to the master
- The second latch (slave) is enabled when  $CLK=0$ 
  - When the clock pulse returns to 0, the master is disabled and is isolated from the  $D$  input.
  - At the same time, the slave is enabled and the value of  $Y$  is transferred to the output of the flip-flop at  $Q$ .
- The circuit samples the  $D$  input and changes its output  $Q$  only at the **negative-edge** of the controlling clock



# Negative Edge-Triggered D Flip-flops

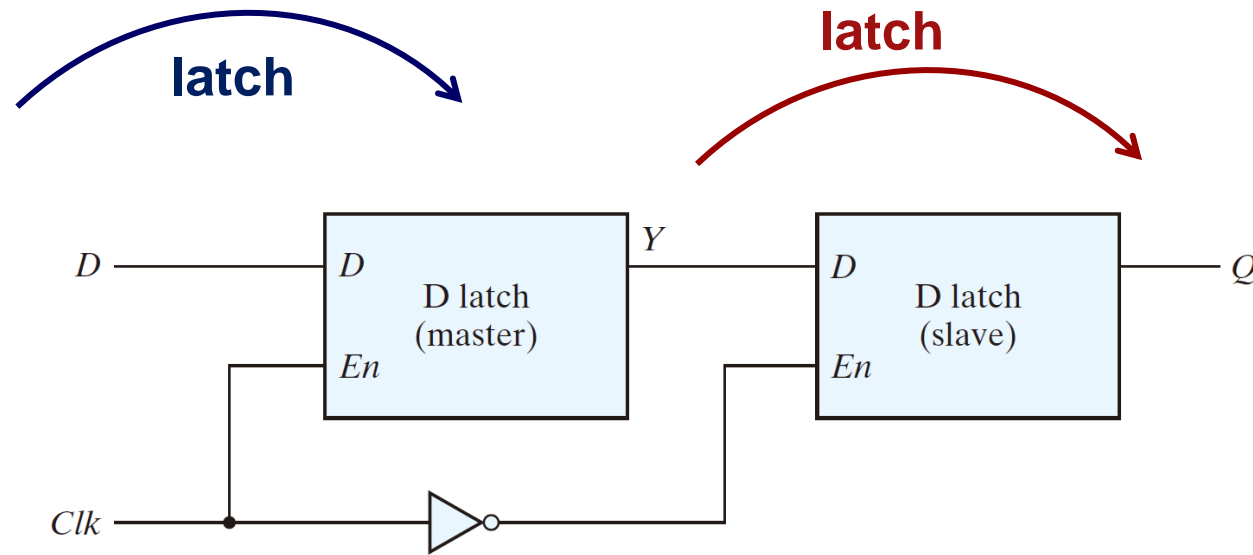

**FIGURE 5.9**  
Master-slave  $D$  flip-flop

H  
L




- Only the transition from high to low, the input  $D$  can be passed over the cascaded latches
- Negative edge-triggered
- How do you change it to positive edge-triggered?



# Positive Edge-Triggered D Flip-flops


- An edge-triggered D flip-flop uses three SR latches
- Two latches respond to the external D (data) and Clk (clock) inputs.
- The third latch provides the outputs for the flip-flop.
- When the input clock in the positive-edge-triggered flip-flop makes a positive transition, the value of D is transferred to Q.
- A negative transition of the clock (i.e., from 1 to 0) does not affect the output, nor is the output affected by changes in D when Clk is in the steady logic-1 level or the logic-0 level.
- Hence, this type of flip-flop responds to the transition from 0 to 1 and nothing else.

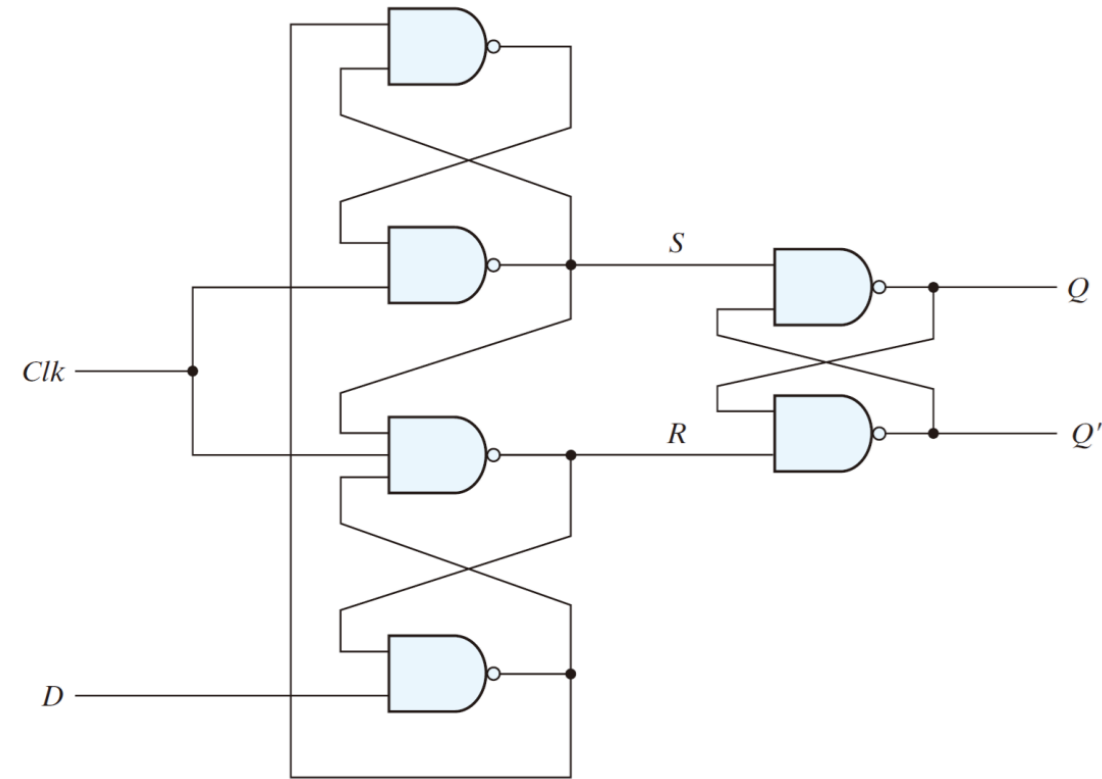

**FIGURE 5.10**  
D-type positive-edge-triggered flip-flop
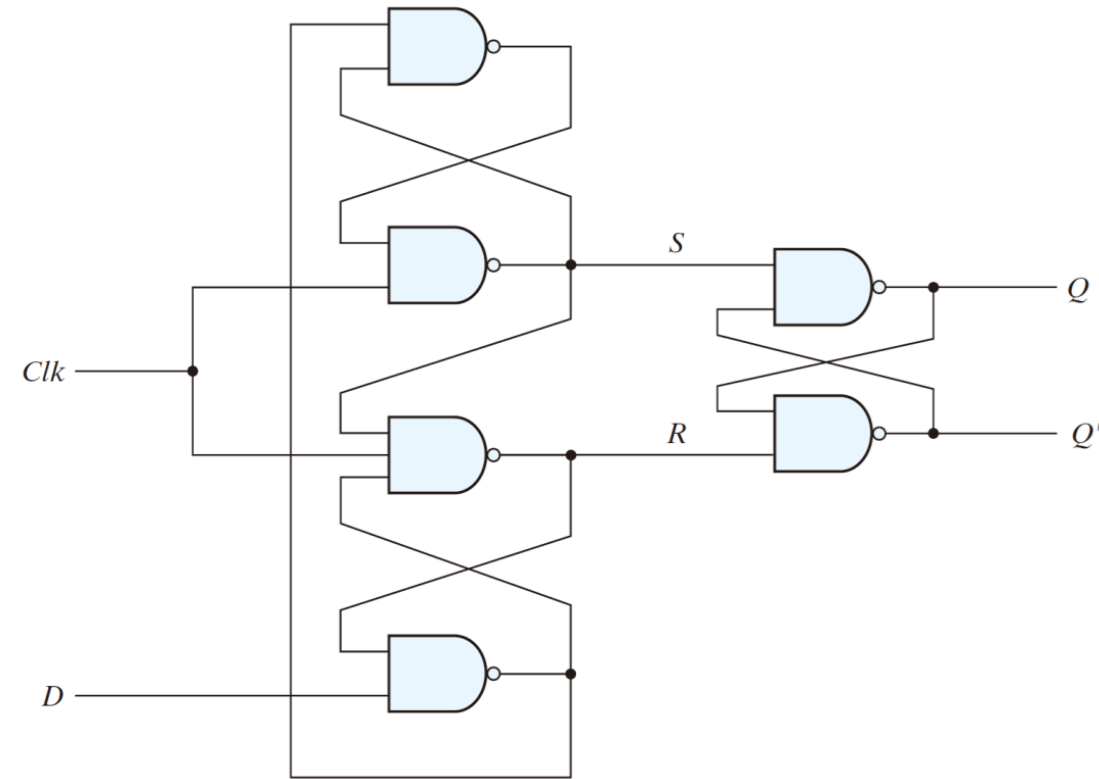
# Positive Edge-Triggered D Flip-flops

- $\text{Clk}=0$ ; S and R are maintained at 1::Q and Q' in the present state
- If  $D=0$ ; and  $\text{Clk}=0$  to 1::  $R=0$  which makes  $Q=0$  (reset)
- If there is a change in the input if clk is 1 :: Flip-flop is locked.
- $\text{Clk}=0$ :: $R=1$ :: No change in the output
- If  $D=1$ ;  $\text{Clk}=0$  to 1,  $S=0$  and  $Q=1$


 


**FIGURE 5.10**  
D-type positive-edge-triggered flip-flop

# D Flip-flop


**D Flip-Flop**

<b><i>D</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	Reset
1	1	Set

 

 
# Setup Time and Hold Time

- The timing of the response of a flip-flop to input data and to the clock must be taken into consideration when one is using edge-triggered flip-flops.
- There is a minimum time called the **setup time** during which the  $D$  input must be maintained at a constant value prior to the occurrence of the clock transition.
- Similarly, there is a minimum time called the **hold time** during which the  $D$  input must not change after the application of the positive transition of the clock.
- The **propagation delay time** of the flip-flop is defined as the interval between the trigger edge and the stabilization of the output to a new state.



 
# DFF (D Flip-Flop) Symbol

- The dynamic indicator (  $\triangleright$  ) denotes the fact that the flip-flop responds to the edge transition of the clock.
- A bubble (  $\circ$  ) outside the block adjacent to the dynamic indicator designates a negative edge trigger.



(a) Positive-edge

 


(a) Negative-edge

**FIGURE 5.11**

Graphic symbol for edge-triggered *D* flip-flop
 
# Characteristic Table

- A characteristic table defines the logical properties of a flip-flop by describing its operation in tabular form.
- The table defines the next state as a function of the inputs and the present state.
- $Q(t)$  refers to the present state (i.e., the state present prior to the application of a clock edge).  
 $Q(t + 1)$  is the next state one clock period later.
- Note that the clock edge input is not included in the characteristic table, but is implied to occur between times  $t$  and  $t + 1$ .
  - $Q(t) \rightarrow$  state of the flip-flop immediately before the clock edge
  - $Q(t + 1) \rightarrow$  state that results from the clock transition



Characteristic Table

***D* Flip-Flop**

<b><i>D</i></b>	<b><i>Q(t + 1)</i></b>
0	0      Reset
1	1      Set

Characteristic Equation

$$Q(t + 1) = D$$



# Other Flip-Flops

---

- JK and T flip-flops
- There are three operations that can be performed with a flip-flop:
  - Set it to 1
  - reset it to 0
  - Complement its output
- With only a single input, the **D flip-flop** can set or reset the output, depending on the value of the D input immediately before the clock transition.
- Synchronized by a clock signal, the **JK flip-flop** has two inputs and performs all three operations.
- The **T (toggle) flip-flop** is a complementing flip-flop.

# JK Flip-Flops

$$Q(t + 1) = JQ' + K'Q$$

- JK flip-flop function: The J input sets the flip-flop to 1, the K input resets it to 0, and when both inputs are enabled, the output is complemented.

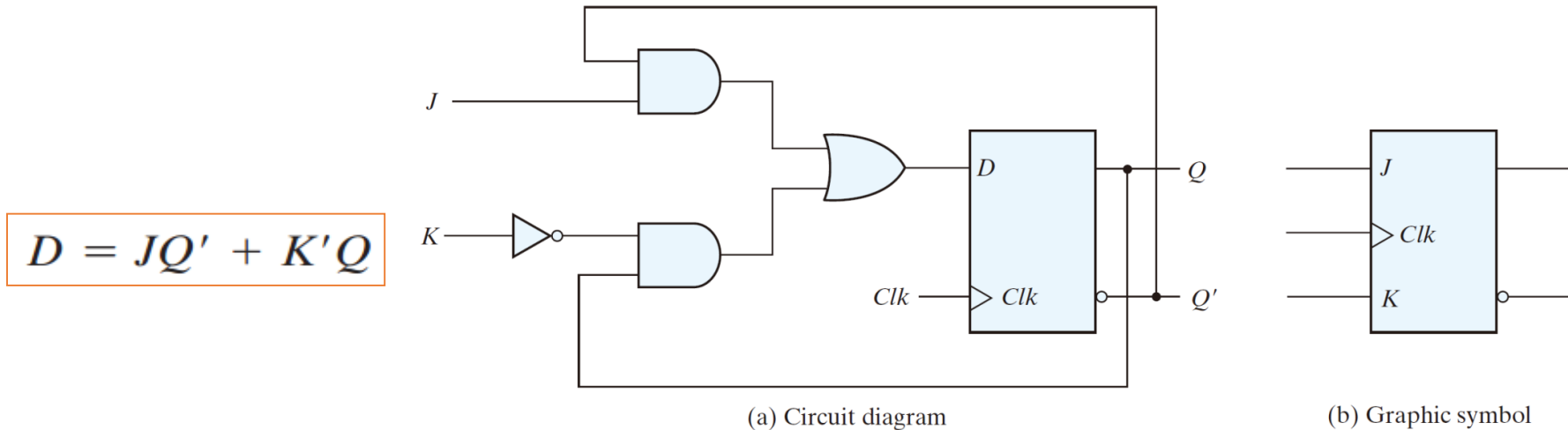


FIGURE 5.12  
JK flip-flop

- (1).  $(J=1, K=0) \rightarrow D = JQ' + K'Q = 1 \cdot Q' + 1 \cdot Q = Q' + Q = 1$
- (2).  $(J=0, K=1) \rightarrow D = JQ' + K'Q = 0 \cdot Q' + 0 \cdot Q = 0 + 0 = 0$
- (3).  $(J=1, K=1) \rightarrow D = JQ' + K'Q = 1 \cdot Q' + 0 \cdot Q = Q'$
- (4).  $(J=0, K=0) \rightarrow D = JQ' + K'Q = 0 \cdot Q' + 1 \cdot Q = Q$  , **No change**

# Characteristic Table

## JK Flip-Flop



### Characteristic Table

$J$	$K$	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

### Characteristic Equation


$$Q(t + 1) = JQ' + K'Q$$

### Graphic symbol

  
 
# T Flip-Flops

- **T flip-flop: “toggle”** flip-flop → complementing flip-flop
- Constructed with JK flip-flop when inputs J and K are tied together
- When  $T = 0$  ( $J = K = 0$ ), a clock edge does not change the output.
- When  $T = 1$  ( $J = K = 1$ ), a clock edge complements the output.




(a) From JK flip-flop

$$(3). (J=1, K=1) \rightarrow D = JQ' + K'Q = 1 \cdot Q' + 0 \cdot Q = Q'$$

$$(4). (J=0, K=0) \rightarrow D = JQ' + K'Q = 0 \cdot Q' + 1 \cdot Q = Q$$
 
# T Flip-Flops

- T flip-flop can be constructed with a D flip-flop and an exclusive-OR gate




(b) From D flip-flop

$$\Rightarrow D = T \oplus Q = TQ' + T'Q$$

- When  $T = 0$ ,  $D = Q \rightarrow$  no change
- When  $T = 1$ ,  $D = Q' \rightarrow$  complement

# Characteristic Table


## T Flip-Flop

 

Assume initial value  $Q_{\text{init}} = 0$



$T$	$Q(t + 1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

$$Q(t + 1) = T \oplus Q = TQ' + T'Q$$

 
  
# DFF with Asynchronous Reset

- Some flip-flops have asynchronous inputs that are used to force the flip-flop to a particular state independently of the clock.
- The input that sets the flip-flop to 1 is called preset or direct set.
- The input that clears the flip-flop to 0 is called clear or direct reset.




(b) Graphic symbol

$R$	$Clk$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0
 
# DFF with Asynchronous Reset

- Asynchronous reset is used to force the flip-flop to reset to 0, independently of the clock.



- Active high reset: a circuit is reset when  $R = "1"$ .
- Active low reset: a circuit is reset when  $R = "0"$ .




# Analysis of Clocked Sequential Circuits

---

- Analysis describes what a given circuit will do under certain operating conditions.
- The behavior of a clocked sequential circuit is determined from the inputs, the outputs, and the state of its flip-flops.
- The analysis of a sequential circuit consists of obtaining a table or a diagram for the time sequence of inputs, outputs, and internal states.
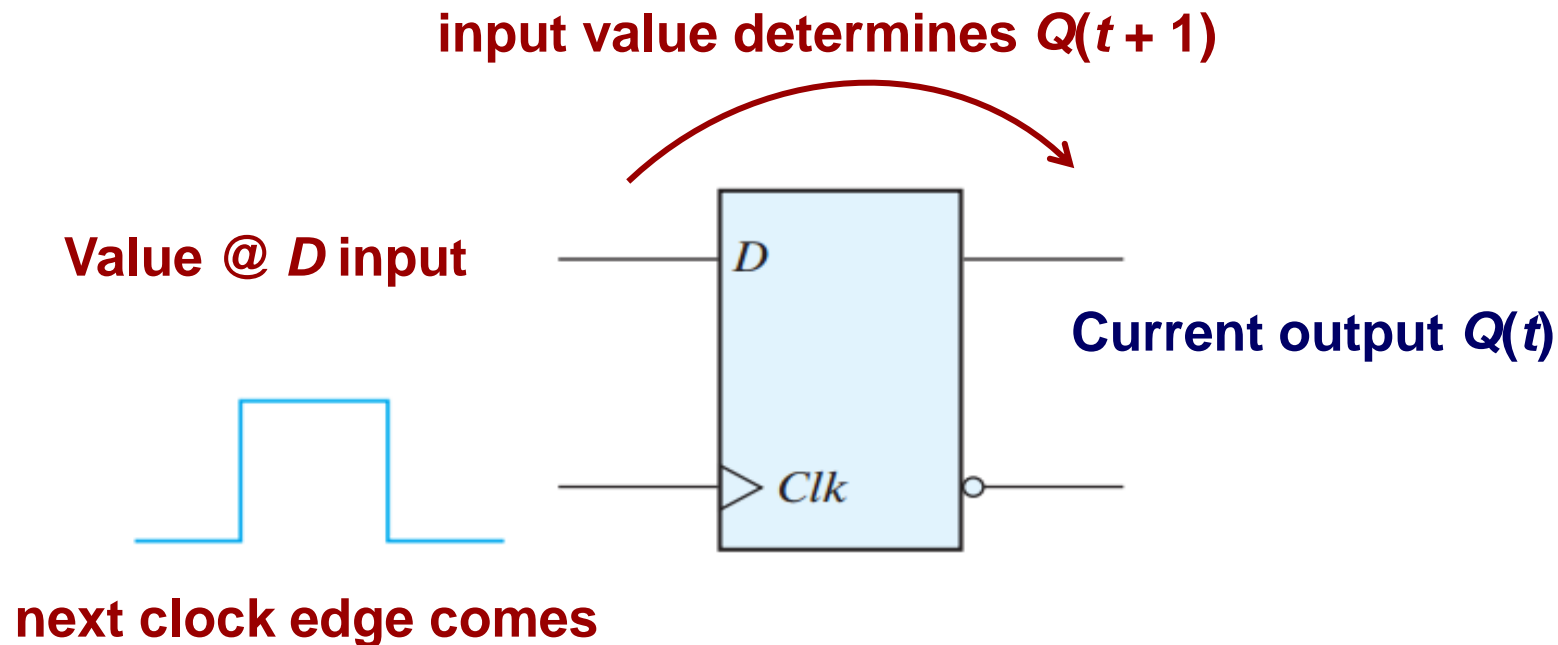
# Analysis of Clocked Sequential Circuits

- The next state of a flip-flop is determined by
  - Input values
  - Current state of the FF
  - Clock trigger




# State Equations (Transition Equations)

---

- The behavior of a clocked sequential circuit can be described algebraically by means of **state equations**.
- A **state equation** (also called a **transition equation**) specifies the next state as a function of the present state and inputs.
- A state equation is an algebraic expression that specifies the condition for a flip-flop state transition.

# State Equations (Transition Equations)

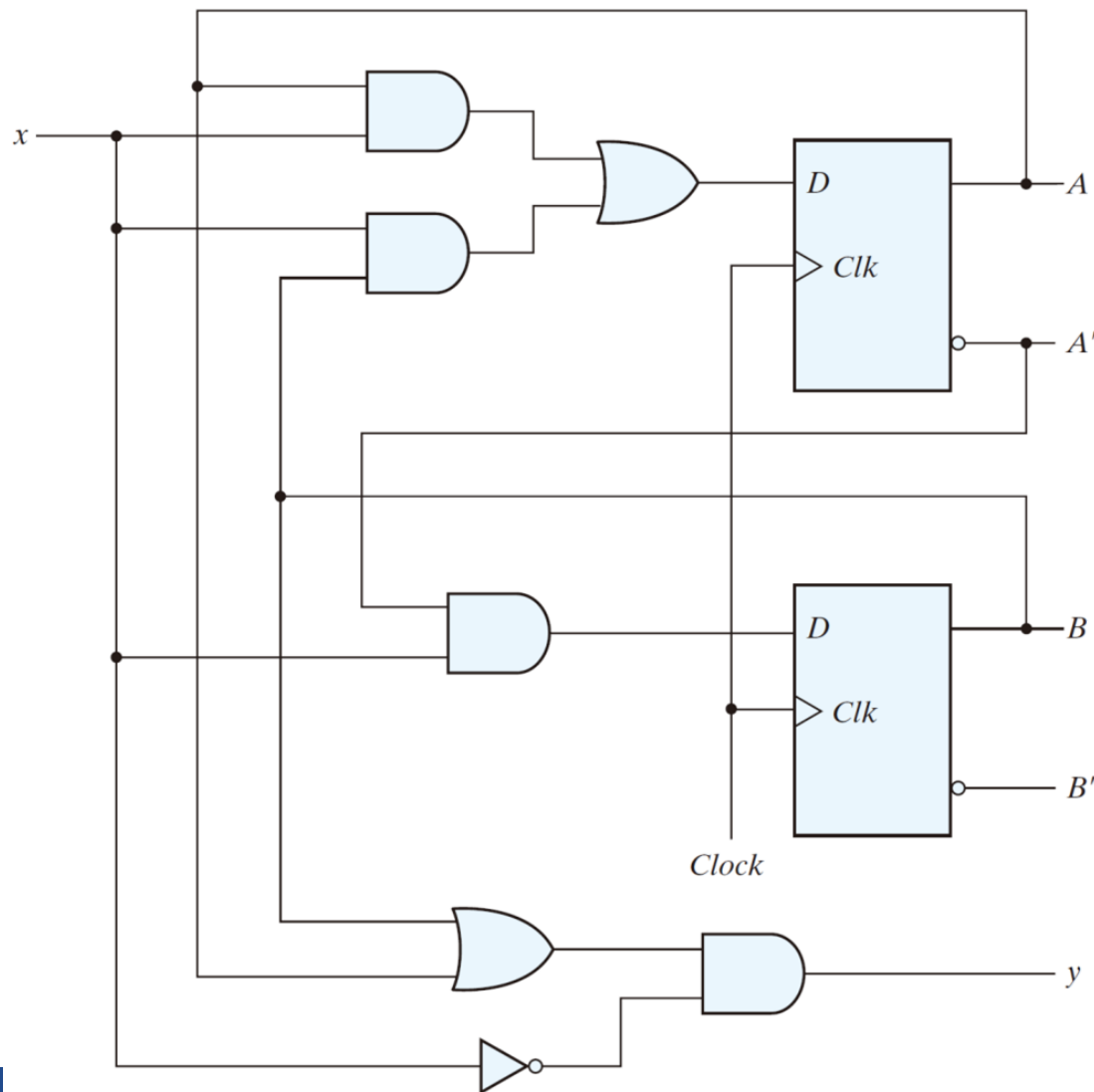

$D$  input of a flip-flop determines the value of the next state

$$A(t + 1) = A(t)x(t) + B(t)x(t)$$

$$B(t + 1) = A'(t)x(t)$$

$$y(t) = [A(t) + B(t)]x'(t)$$

# State Equations

- The left side of the equation, with  $(t + 1)$ , denotes the next state of the flip-flop one clock edge later.
- The right side of the equation is a Boolean expression that specifies the present state and inputs.

$$A(t + 1) = A(t)x(t) + B(t)x(t)$$

$$B(t + 1) = A'(t)x(t)$$

$$y(t) = [A(t) + B(t)]x'(t)$$

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

# State Table

- The time sequence of inputs, outputs, and flip-flop states can be enumerated in a **state table** (or **transition table**).
- The table consists of four sections labeled **present state**, **input**, **next state**, and **output**.
- The derivation of a state table requires **listing all possible binary combinations of present states and inputs**.

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$


# State Table

- It is sometimes convenient to express the state table in a slightly different form having only three sections: present state, next state, and output.

**Table 5.2**

*State Table for the Circuit of Fig. 5.15*

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 

**Table 5.3**

*Second Form of the State Table*


Present State		Next State				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

# State Diagram

- The information available in a state table can be represented graphically in the form of a state diagram.


**Table 5.2**  
*State Table for the Circuit of Fig. 5.15*

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

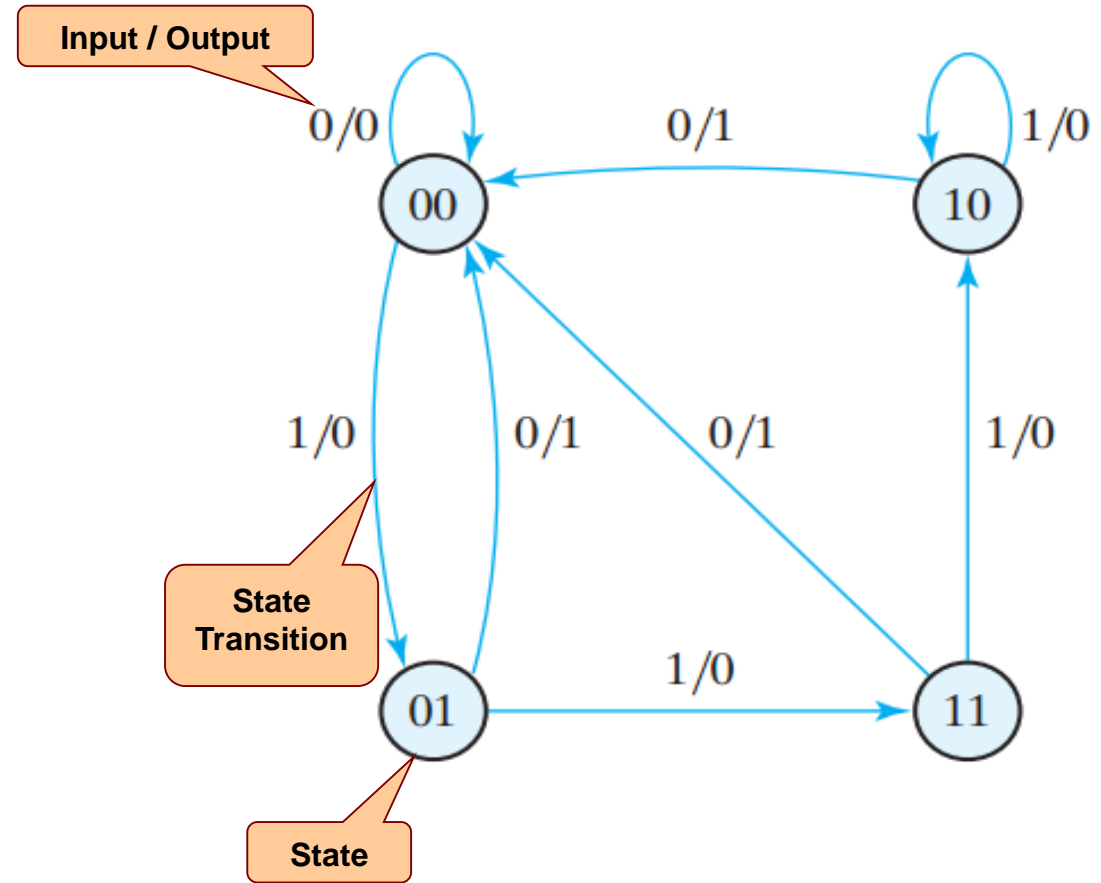




# State Diagram

 

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
$A$	$B$	$A$	$B$	$A$	$B$	$y$	$y$
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

 

# State Table & State Diagram

---


- Summarized procedure:

Circuit diagram → Equations – State table → State diagram

- There is no difference between a state table and a state diagram.
- The **state table** is easier to derive from a given logic diagram and the state equation.
- The **state diagram** is the form more suitable for human interpretation of the circuit's operation.
  - Easier for an HDL model in the form of gate-level description or in the form of a behavior description
  - Easier for the design of an automatic synthesis tool
 
# Flip-Flop Input Equations (Excitation Equations)


- The part of the circuit that **generates the inputs to flip-flops** is described algebraically by a set of Boolean functions called flip-flop input equations.
- The flip-flop input equations can be used to obtain state equations.



$$D_A = Ax + Bx$$

D flip-flop with output A

# Output Equations

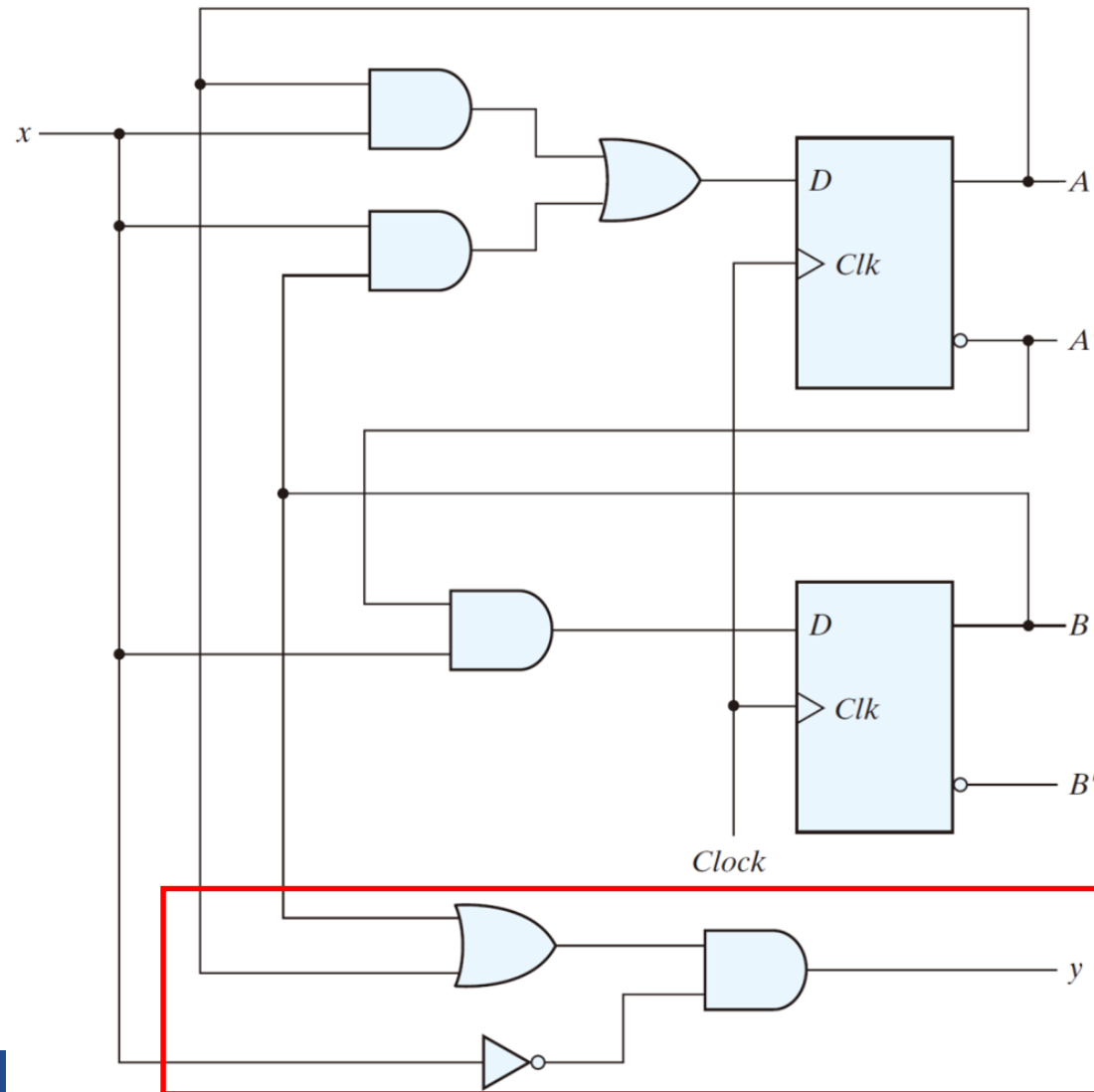

- External outputs are described algebraically by a set of Boolean functions called output equations.

$$D_A = Ax + Bx$$

$$D_B = A'x$$

$$y = (A + B)x'$$

- The Boolean expressions associated with the input/output equations specify the combinational circuit part of the sequential circuit

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

**FIGURE 5.15**  
Example of sequential circuit


# Analysis with DFF

## ➤ Input equation

$$D_A = A \oplus x \oplus y$$

The state equation


$$A(t + 1) = A \oplus x \oplus y$$

 

(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

 


(c) State diagram

**FIGURE 5.17**

Sequential circuit with *D* flip-flop

# Analysis with JK Flip-Flop

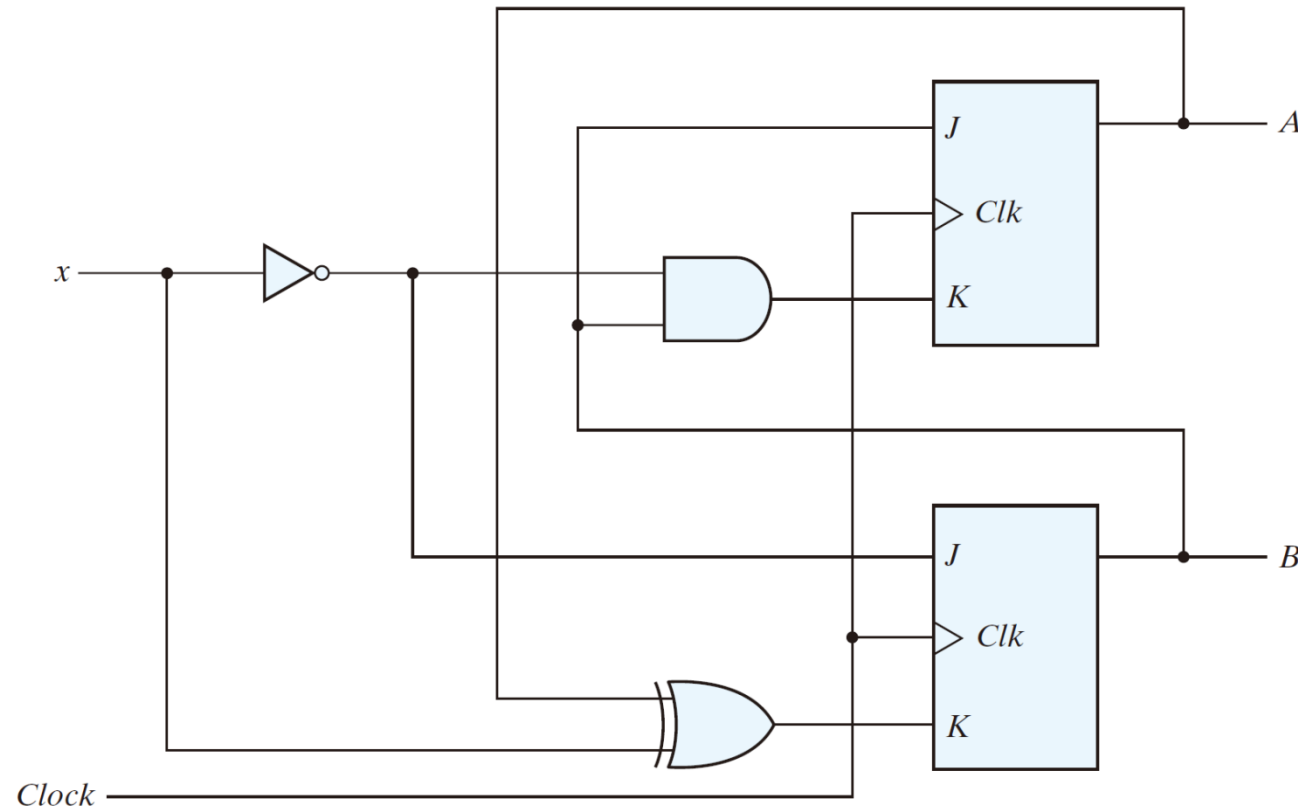


**FIGURE 5.18**  
Sequential circuit with JK flip-flop

Characteristic equation for JK flip-flop:

$$Q(t + 1) = JQ' + K'Q$$

**Write state equations**

# Analysis with JK Flip-Flop

 

**FIGURE 5.18**  
Sequential circuit with JK flip-flop

Characteristic equation for JK flip-flop:

$$Q(t + 1) = JQ' + K'Q$$

➤ Characteristic equations of a JK flip-flop.

$$A(t + 1) = JA' + K'A$$

$$B(t + 1) = JB' + K'B$$

➤ Input equations of the circuit

$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax' = A \oplus x$$

➤ State equations of the circuit

$$A(t + 1) = BA' + (Bx')'A = A'B + AB' + Ax$$

$$B(t + 1) = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'$$

# Analysis with JK Flip-Flop

$$A(t + 1) = BA' + (Bx')' A = A'B + AB' + Ax$$

$$B(t + 1) = x'B' + (A \oplus x)' B = B'x' + ABx + A'Bx'$$

$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax' = A \oplus x$$

*State Table for Sequential Circuit with JK Flip-Flops*


Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0




# Analysis with JK Flip-Flop

## State Diagram of the Circuit

Present State		Input	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 

# Analysis with TFF

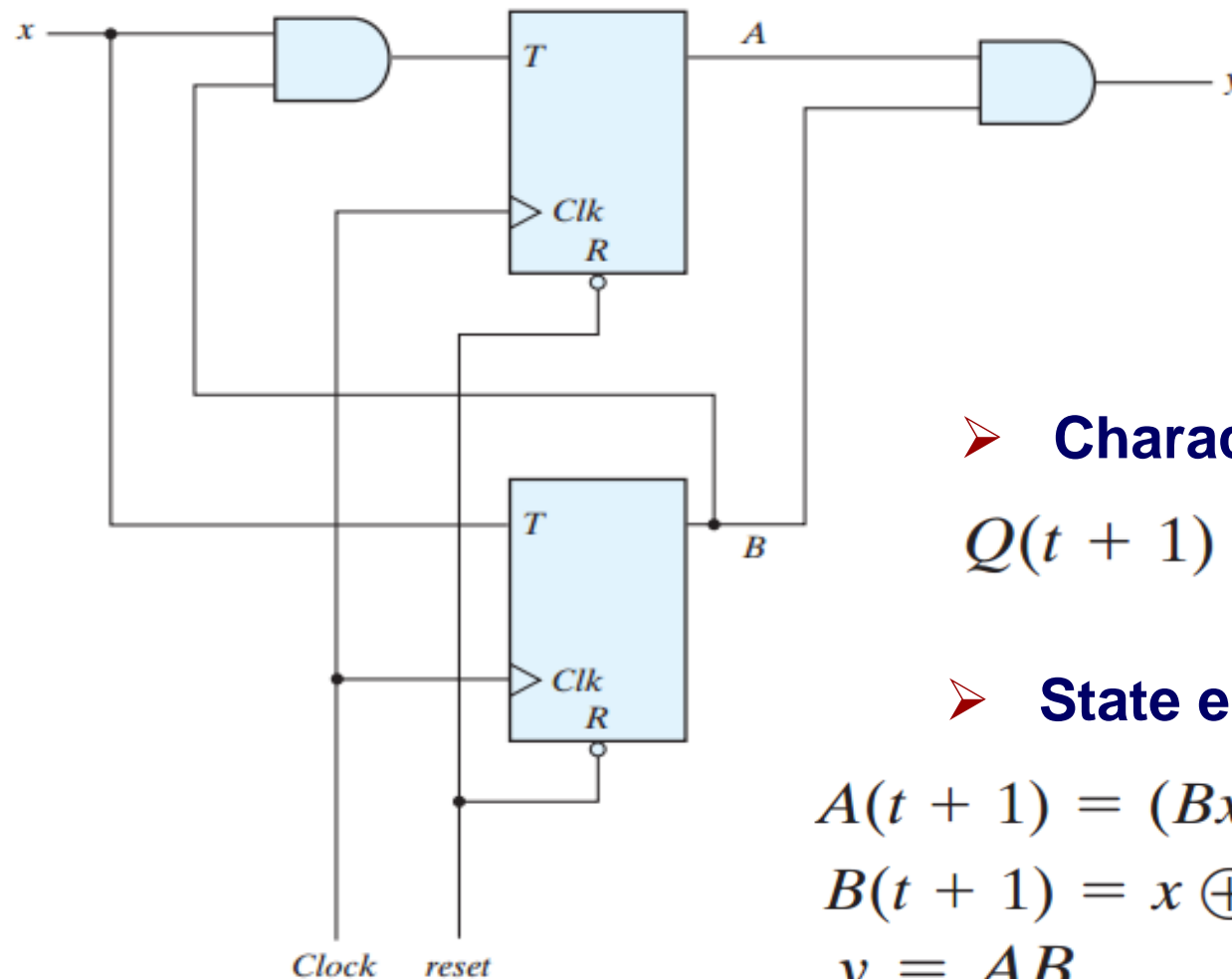

## ➤ Input equations

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

## ➤ Characteristic equations

$$Q(t + 1) = T \oplus Q = T'Q + TQ'$$

## ➤ State equations of the circuit

$$A(t + 1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx$$

$$B(t + 1) = x \oplus B$$

$$y = AB$$

# Analysis with TFF


$$A(t + 1) = (Bx)'A + (Bx)A' = AB' + Ax' + A'Bx$$

$$B(t + 1) = x \oplus B$$

$$y = AB$$

**State Table**

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

 

- As long as input  $x$  is equal to 1, the circuit behaves as a binary counter.
- Here, the output depends on the present state only and is independent of the input.
- The two values inside each circle and separated by a slash are for the present state and output.