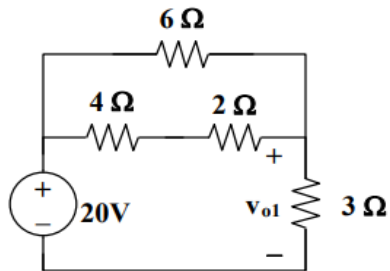


Solution set for chapter-04 (CIRCUITS THEOREMS)

SUPERPOSITION THEOREM:


Q1.

Let $v_o = v_{o1} + v_{o2} + v_{o3}$, where v_{o1} , v_{o2} , and v_{o3} , are due to the 20-V, 1-A, and 2-A sources respectively. For v_{o1} , consider the circuit below.




$$6 \parallel (4 + 2) = 3 \text{ ohms}, v_{o1} = \left(\frac{1}{2}\right)20 = 10 \text{ V}$$

For v_{o2} , consider the circuit below.

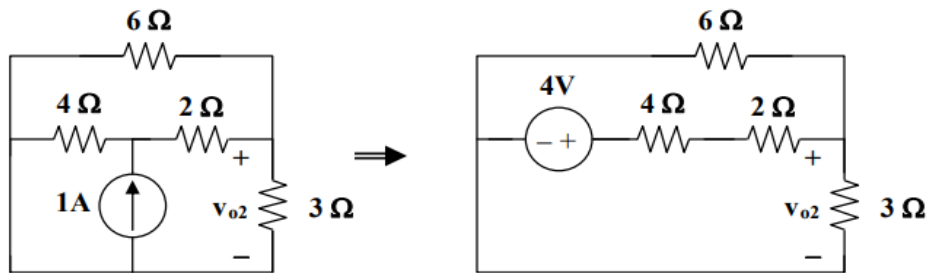

$$3 \parallel 6 = 2 \text{ ohms}, v_{o2} = [2/(4 + 2 + 2)]4 = 1 \text{ V}$$

For v_{o3} , consider the circuit below.

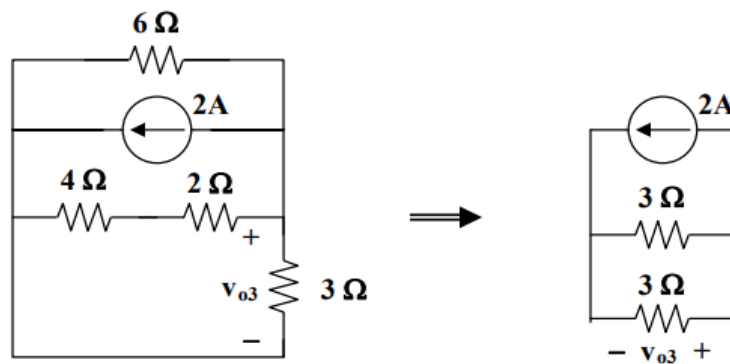


$$6 \parallel (4 + 2) = 3, v_{o3} = (-1)3 = -3$$

$$v_o = 10 + 1 - 3 = 8 \text{ V}$$

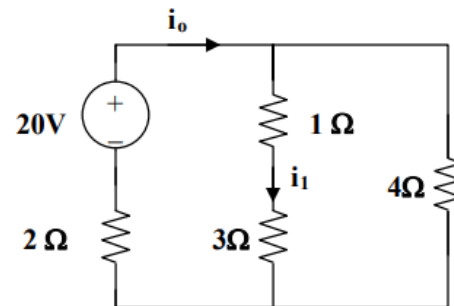
Q2.

Let $i = i_1 + i_2 + i_3$, where i_1 , i_2 , and i_3 are due to the 20-V, 2-A, and 16-V sources. For i_1 , consider the circuit below.



$$4 \parallel (3 + 1) = 2 \text{ ohms, Then } i_o = [20/(2 + 2)] = 5 \text{ A, } i_1 = i_o/2 = 2.5 \text{ A}$$


For i_3 , consider the circuit below.

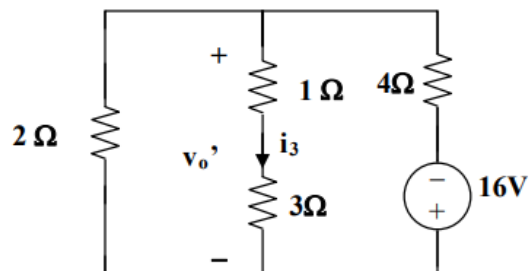

$$2 \parallel (1 + 3) = 4/3, v_o' = [(4/3)/((4/3) + 4)](-16) = -4$$

$$i_3 = v_o'/4 = -1$$

For i_2 , consider the circuit below.

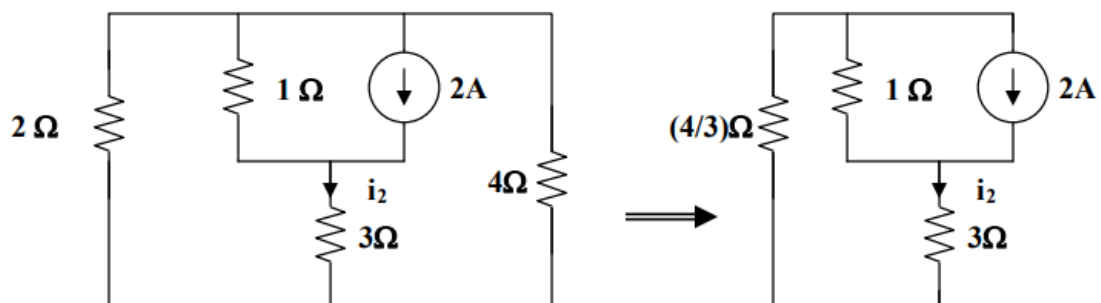

$$2 \parallel 4 = 4/3, 3 + 4/3 = 13/3$$

Using the current division principle.


$$i_2 = [1/(1 + 13/3)]2 = 3/8 = 0.375$$

$$i = 2.5 + 0.375 - 1 = \mathbf{1.875\text{ A}}$$

$$p = i^2 R = (1.875)^2 3 = \mathbf{10.55\text{ watts}}$$

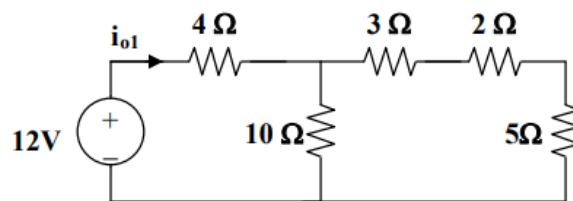
Q3.

Let $i_o = i_{o1} + i_{o2} + i_{o3}$, where i_{o1} , i_{o2} , and i_{o3} are due to the 12-V, 4-A, and 2-A sources. For i_{o1} , consider the circuit below.



$$10 \parallel (3 + 2 + 5) = 5 \text{ ohms}, i_{o1} = 12/(5 + 4) = (12/9) \text{ A}$$


For i_{o2} , consider the circuit below.

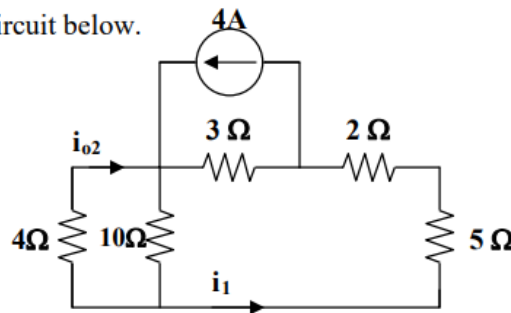

$$2 + 5 + 4 \parallel 10 = 7 + 40/14 = 69/7$$

$$i_1 = [3/(3 + 69/7)]4 = 84/90, i_{o2} = [-10/(4 + 10)]i_1 = -6/9$$

For i_{o3} , consider the circuit below.

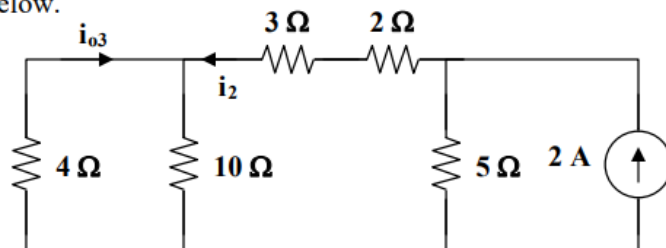

$$3 + 2 + 4 \parallel 10 = 5 + 20/7 = 55/7$$


$$i_2 = [5/(5 + 55/7)]2 = 7/9, i_{o3} = [-10/(10 + 4)]i_2 = -5/9$$

$$i_o = (12/9) - (6/9) - (5/9) = 1/9 = \mathbf{111.11\text{ mA}}$$

SOURCE TRANSFORMATION:

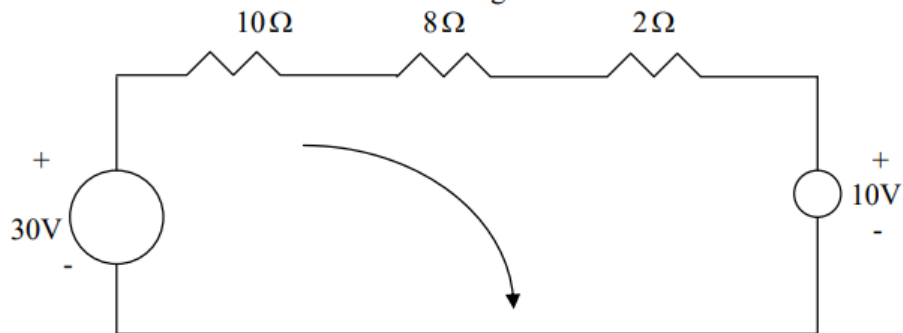Q1.

$3//6 = 2\text{-ohm}$. Convert the current sources to voltages sources as shown below.



Applying KVL to the loop gives

$$-30 + 10 + I(10 + 8 + 2) = 0 \longrightarrow I = 1 \text{ A}$$


$$p = VI = I^2 R = 8 \text{ W}$$

Q2.

Transform the two current sources in parallel with the resistors into their voltage source equivalents yield,

a 30-V source in series with a 10-Ω resistor and a $20V_x$ -V sources in series with a 10-Ω resistor.

We now have the following circuit,

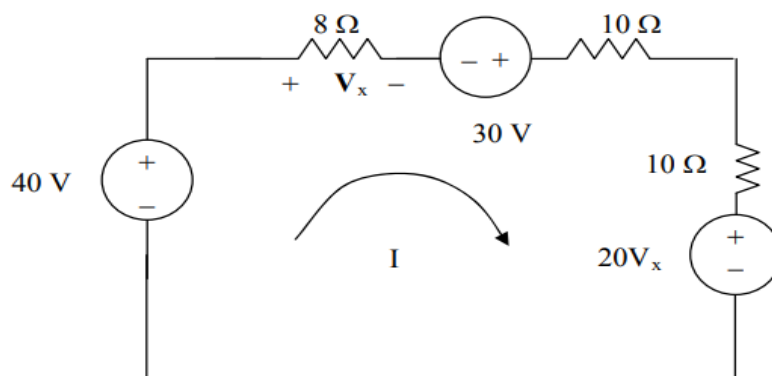


We now write the following mesh equation and constraint equation which will lead to a solution for V_x ,

$$28I - 70 + 20V_x = 0 \text{ or } 28I + 20V_x = 70, \text{ but } V_x = 8I \text{ which leads to}$$

$$28I + 160I = 70 \text{ or } I = 0.3723 \text{ A or } V_x = 2.978 \text{ V.}$$

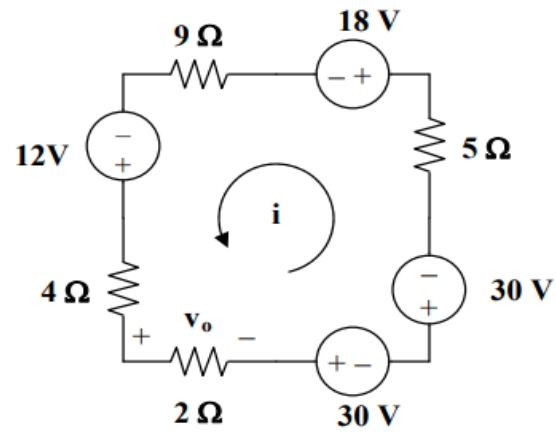Q3.

Transforming only the current source gives the circuit below.



Applying KVL to the loop gives,

$$-(4 + 9 + 5 + 2)i + 12 - 18 - 30 - 30 = 0$$


$$20i = -66 \text{ which leads to } i = -3.3$$

$$v_o = 2i = -6.6 \text{ V}$$

THEVENIN AND NORTON THEOREM:

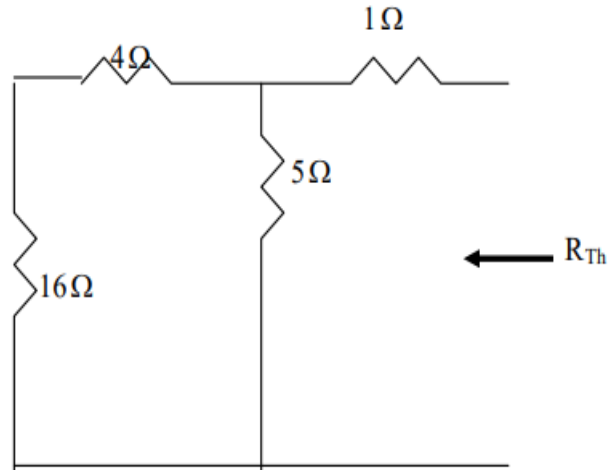
Q1.

We find Thevenin equivalent at the terminals of the 10-ohm resistor. For R_{Th} , consider the circuit below.



$$R_{Th} = 1 + 5 // (4 + 16) = 1 + 4 = 5\Omega$$

For V_{Th} , consider the circuit below.

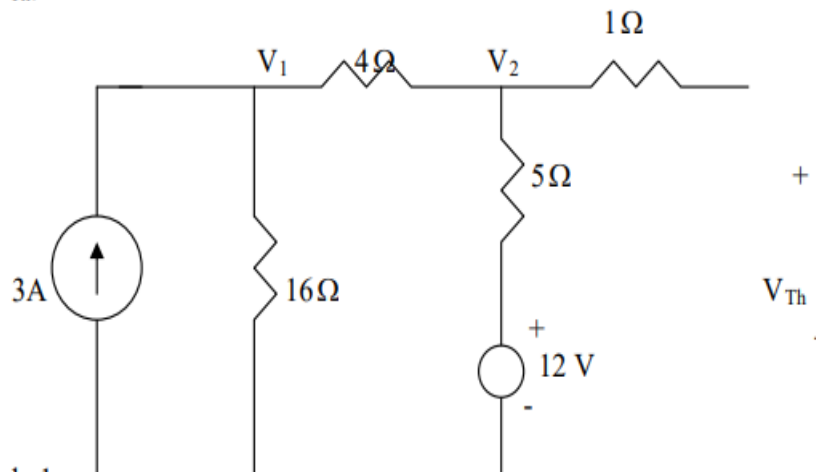

At node 1,

$$3 = \frac{V_1}{16} + \frac{V_1 - V_2}{4} \longrightarrow 48 = 5V_1 - 4V_2 \quad (1)$$

At node 2,


$$\frac{V_1 - V_2}{4} + \frac{12 - V_2}{5} = 0 \longrightarrow 48 = -5V_1 + 9V_2 \quad (2)$$

Solving (1) and (2) leads to

$$V_{Th} = V_2 = 19.2$$

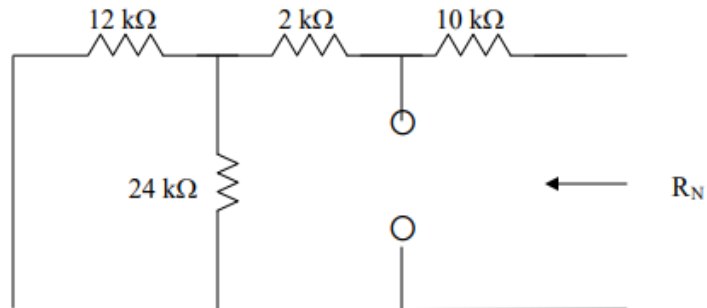
Q2.

We remove the $1\text{-k}\Omega$ resistor temporarily and find Norton equivalent across its terminals. R_{eq} is obtained from the circuit below.




$$R_{eq} = 10 + 2 + (12 // 24) = 12 + 8 = 20\text{ k}\Omega$$


I_N is obtained from the circuit below.

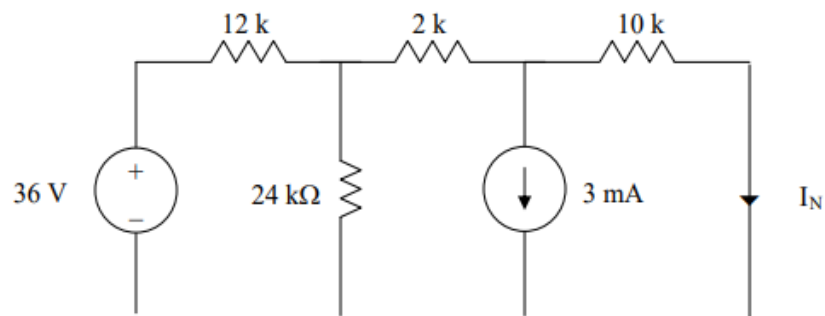

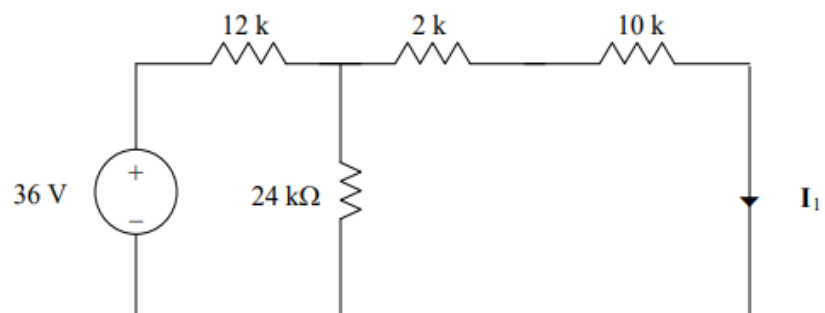We can use superposition theorem to find I_N . Let $I_N = I_1 + I_2$, where I_1 and I_2 are due to 16-V and 3-mA sources respectively. We find I_1 using the circuit below.



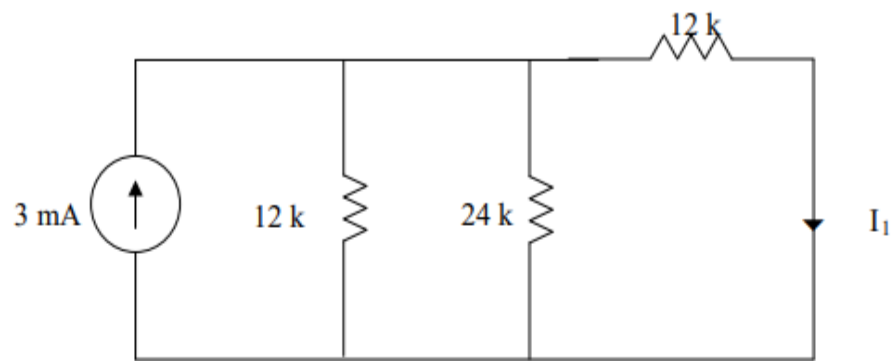
Using source transformation, we obtain the circuit below.



$$12 // 24 = 8 \text{ k}\Omega$$

$$I_1 = \frac{8}{8+12}(3\text{mA}) = 1.2 \text{ mA}$$

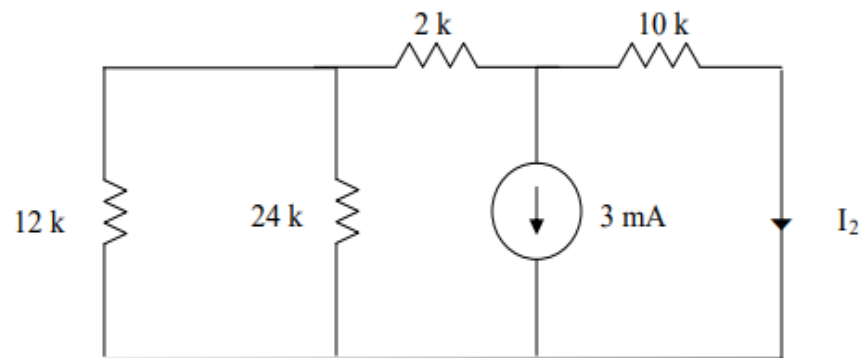To find I_2 , consider the circuit below.




$$2\text{k} + 12\text{k} // 24\text{k} = 10 \text{ k}\Omega$$

$$I_2 = 0.5(-3\text{mA}) = -1.5 \text{ mA}$$

$$I_N = 1.2 - 1.5 = -0.3 \text{ mA}$$



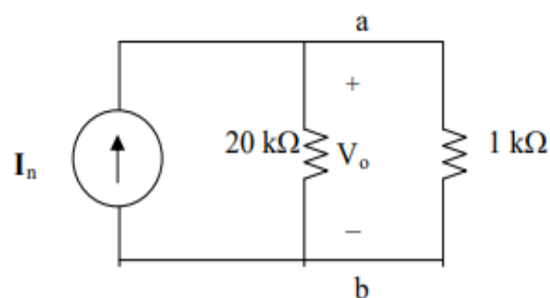
The Norton equivalent with the 1-kΩ resistor is shown below




$$V_o = 1\text{k}(20/(20+1))(-0.3 \text{ mA}) = \mathbf{-285.7 \text{ mV}}.$$

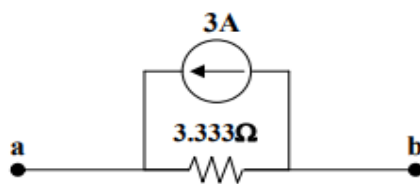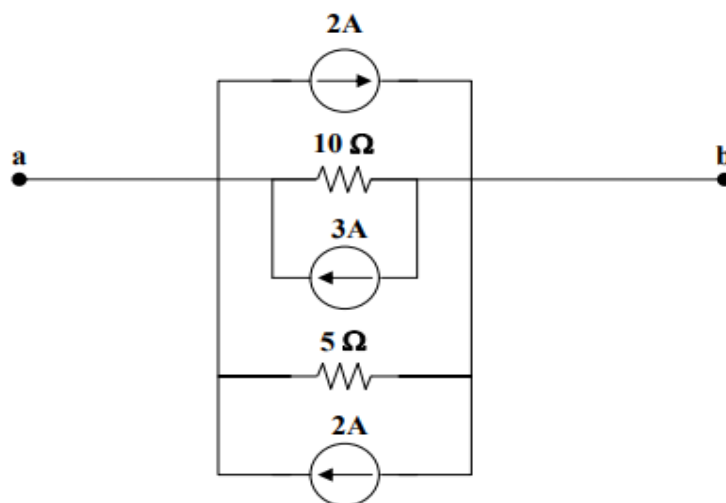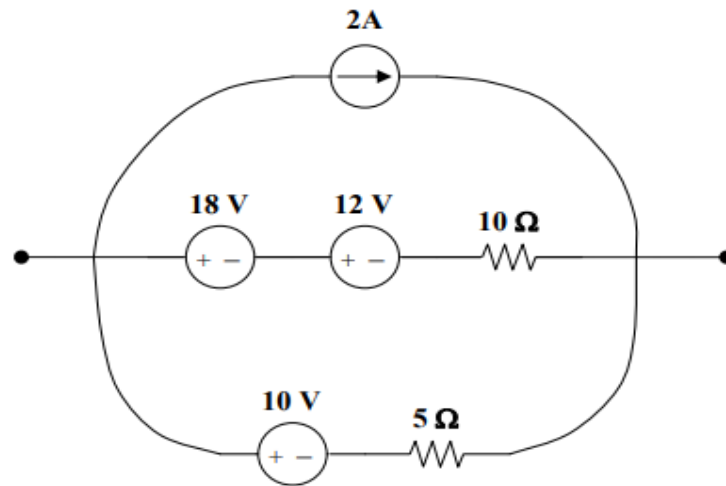Q3.

The circuit can be reduced by source transformations.




Norton Equivalent Circuit

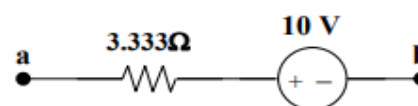

Thevenin Equivalent Circuit

SUPER MESH ANALYSIS:

Q1.

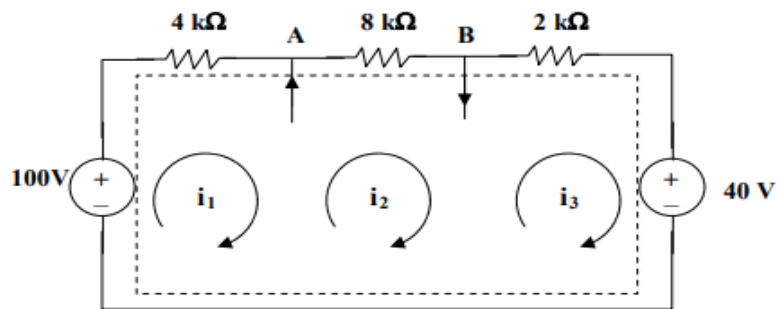

We have a supermesh. Let all R be in kΩ, i in mA, and v in volts.


$$\text{For the supermesh, } -100 + 4i_1 + 8i_2 + 2i_3 + 40 = 0 \text{ or } 30 = 2i_1 + 4i_2 + i_3 \quad (1)$$

$$\text{At node A, } i_1 + 4 = i_2 \quad (2)$$

$$\text{At node B, } i_2 = 2i_1 + i_3 \quad (3)$$

Solving (1), (2), and (3), we get $i_1 = 2 \text{ mA}$, $i_2 = 6 \text{ mA}$, and $i_3 = 2 \text{ mA}$.

Q2.

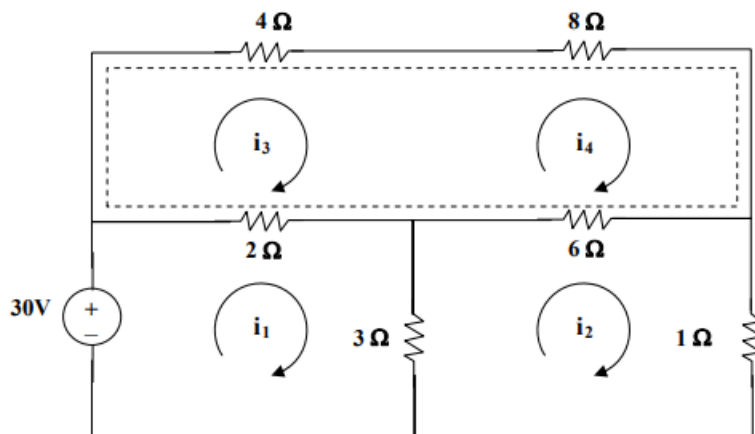

$$\text{For loop 1, } 30 = 5i_1 - 3i_2 - 2i_3 \quad (1)$$


$$\text{For loop 2, } 10i_2 - 3i_1 - 6i_4 = 0 \quad (2)$$

$$\text{For the supermesh, } 6i_3 + 14i_4 - 2i_1 - 6i_2 = 0 \quad (3)$$

$$\text{But } i_4 - i_3 = 4 \text{ which leads to } i_4 = i_3 + 4 \quad (4)$$

Solving (1) to (4) by elimination gives $i = i_1 = 8.561 \text{ A}$.

Q3.

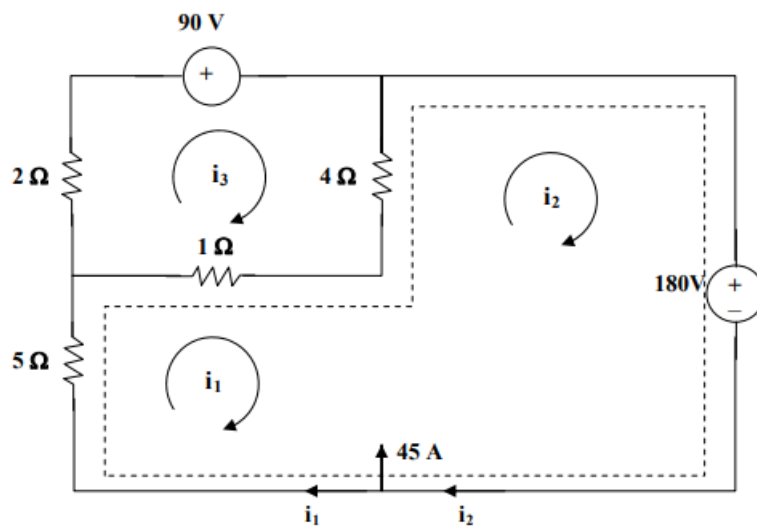

Loop 1 and 2 form a supermesh. For the supermesh,

$$6i_1 + 4i_2 - 5i_3 + 180 = 0 \quad (1)$$

For loop 3, $-i_1 - 4i_2 + 7i_3 + 90 = 0 \quad (2)$

Also, $i_2 = 45 + i_1 \quad (3)$

Solving (1) to (3), $i_1 = -46$, $i_3 = -20$; $i_o = i_1 - i_3 = -26 \text{ A}$