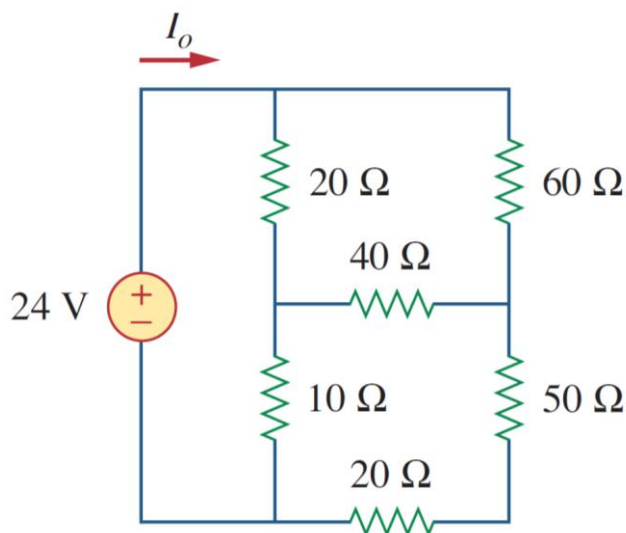





Note: Answer all the questions in sequence


1. (a). A 600-W TV receiver is turned on for 4 h with nobody watching it. If electricity costs 10 rupees per unit, how much money is wasted? **(1 mark)**
(b). A flashlight battery has a rating of 0.8 ampere-hours (Ah) and a lifetime of 10 hours. (i) How much current can it deliver? (ii) How much power can it give if its terminal voltage is 6 V? (iii) How much energy is stored in the battery in Wh? **(2 marks)**
2. Determine R_{eq} and I_o in the below circuit **(3 marks)**



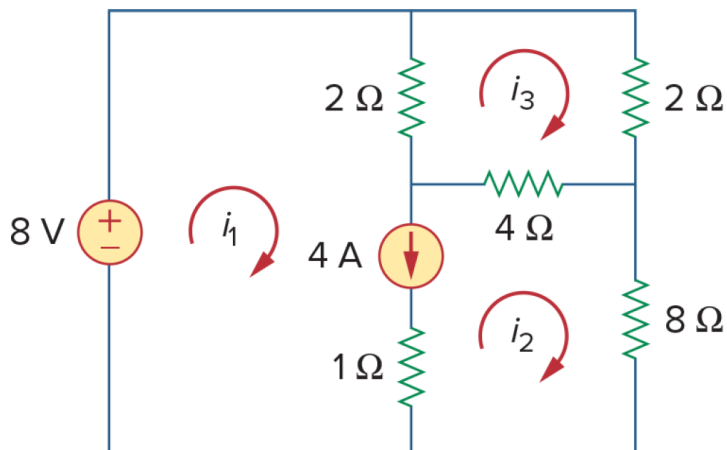
3. Use mesh analysis to determine i_1 , i_2 , and i_3 in the following circuit. **(4 marks)**



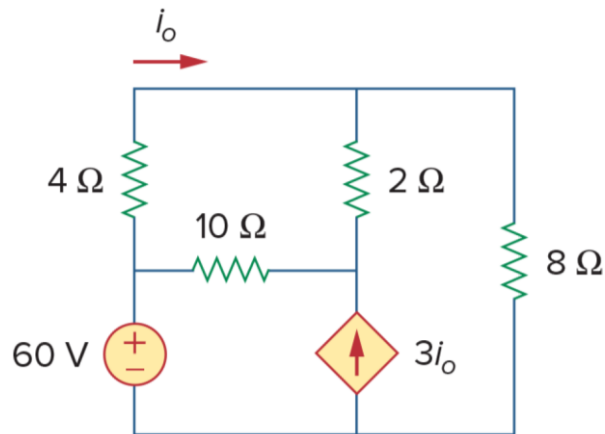
4. Using nodal analysis, find current i_o in the following circuit. **(4 marks)**



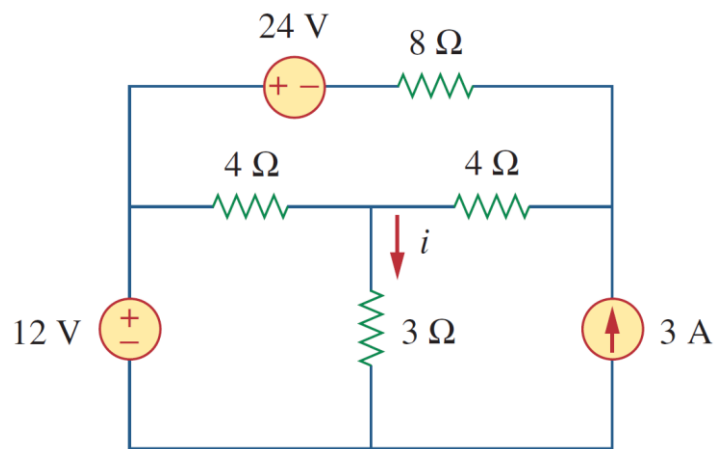5. For the circuit in Figure below, use the superposition theorem to find i . **(4 marks)**



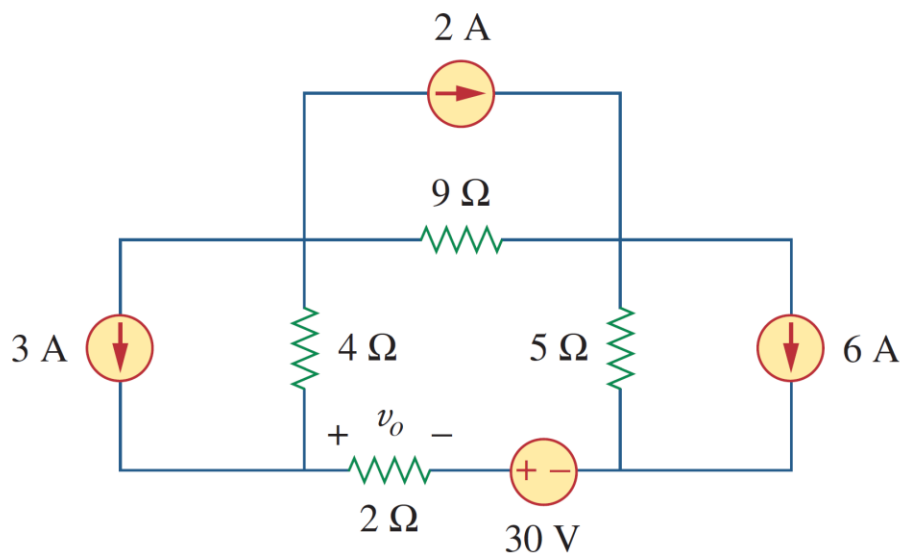6. Obtain v_o in the circuit of figure using source transformation. **(2 marks)**



*****Best Wishes*****