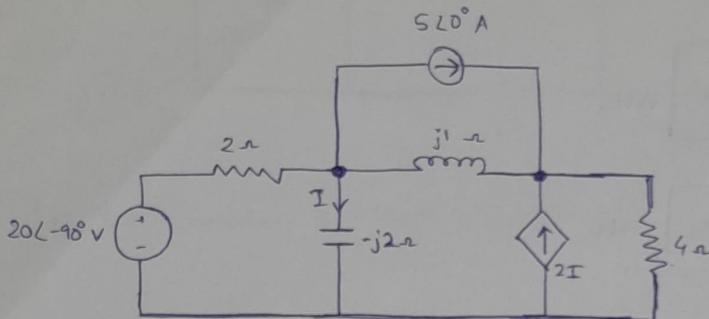


ASSIGNMENT - II
(EC1000)

(Q1)




To find :

I

Process :

Nodal Analysis

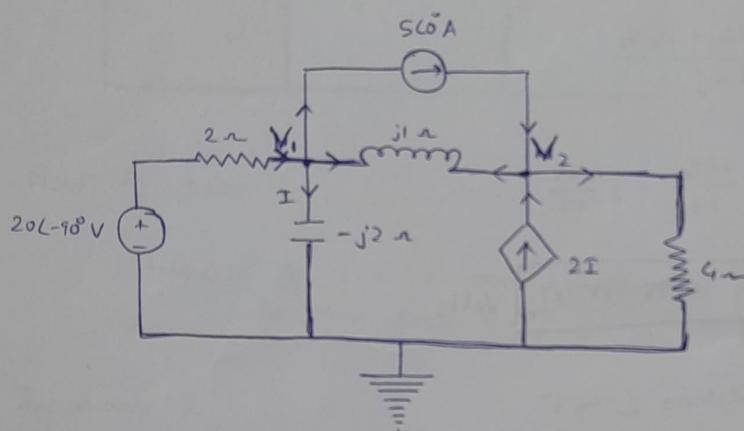A1) Let's first indicate two available nodes and the reference node.



Applying Nodal Analysis at Node 1 :

$$\frac{20\angle-90^\circ - V_1}{2} = 5\angle0^\circ + \frac{V_1 - V_2}{j1} + \frac{V_1 - 0}{-j2}$$

where,

$$I = \frac{V_1 - 0}{-j2}$$

$$\therefore I = \frac{jV_1}{2}$$

$$\Rightarrow 20\angle-90^\circ - V_1 = 10\angle0^\circ + (2V_2 - 2V_1)j + jV_1$$

$$\Rightarrow 20\angle-90^\circ - 10\angle0^\circ = V_1(1-j) + V_2(2j)$$

$$\Rightarrow -20j - 10 = V_1(1-j) + V_2(2j)$$

$$\Rightarrow 10 + 20j = V_1(-1+j) + V_2(-2j) - \textcircled{1}$$

Applying Nodal Analysis at Node 2 :

$$2I + 5\angle0^\circ = \frac{V_2 - V_1}{j1} + \frac{V_2 - 0}{4}$$

$$\Rightarrow V_1j + 5 = V_1j - V_2j + \frac{V_2}{4}$$

$$\Rightarrow S = V_2 \left(\frac{1}{4} - j \right)$$

$$\therefore V_2 = \frac{S}{\frac{1}{4} - j} = \frac{20}{17} + j \frac{80}{17}$$

$$\boxed{\therefore V_2 = \frac{20}{\sqrt{17}} \angle 75.964^\circ} \text{ Volts}$$

$$(OR) \boxed{V_2 = 1.176 + 4.706j} \text{ Volts}$$

Now substituting in ① :

$$\Rightarrow 10 + 20j = V_1(-1+j) + V_2(-2j)$$

$$\Rightarrow V_1(-1+j) = 10 + 20j + 2j(V_2)$$

$$\Rightarrow V_1 = \frac{10 + 20j + 2jV_2}{-1+j}$$

$$\Rightarrow V_1 = \frac{18S}{17} - j \frac{19S}{17}$$

$$\boxed{\therefore V_1 = 10.88 - 11.47j} \text{ Volts}$$


$$(OR) V_1 = 5\sqrt{10} \angle -46.5^\circ$$

$$\boxed{\therefore V_1 = 15.81 \angle -46.5^\circ} \text{ Volts}$$

$$\text{Now } I = \frac{jV_1}{2}$$

$$\boxed{\therefore I = 5.73 + 5.44j} \text{ A}$$
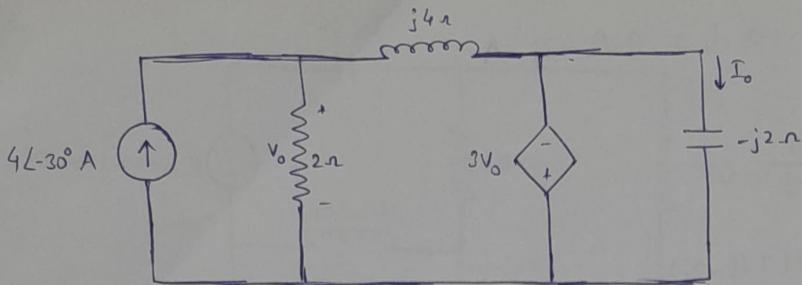
$$\boxed{\therefore I = 7.906 \angle 43.5^\circ} \text{ A}$$




To find:
I_o and V_o

Process:

Mesh Analysis

A2) Let us consider 3 loops

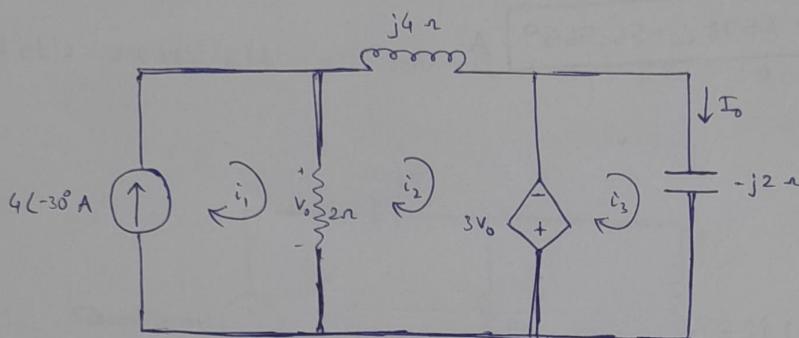

Now in Loop 1:

$-4L-30^\circ A$ is a Current source, \therefore in the loop itself. $i_1 = 4L-30^\circ A$

In Loop 2:

$$2(i_2 - i_1) + j4(i_2) - 3V_o = 0 \quad \text{--- (1)}$$

~~But $V_o = 2(i_1 - i_2)$~~

But from Loop 1, $V_{2n} = i_{2n} \times 2$

$$\Rightarrow V_{2n} = 2(i_1 - i_2)$$

$$\therefore V_o = 2(i_1 - i_2) \quad \text{--- (2)}$$

Put (2) in (1):

$$2(i_2 - i_1) + j4(i_2) + 6(i_2 - i_1) = 0$$

$$\Rightarrow 8(i_2 - i_1) + j4(i_2) = 0$$

$$\Rightarrow 2(i_2 - i_1) + j i_2 = 0$$

$$\Rightarrow 2i_1 - (2+j)i_2 = 0 \quad \text{--- (3)}$$

$$\text{But } i_1 = 4 \angle -30^\circ \text{ A} \Rightarrow i_1 = 2\sqrt{3} - 2j \text{ A}$$

$$\Rightarrow i_2 = \frac{2i_1}{2+j}$$

$$\therefore i_2 = \frac{2(2\sqrt{3} - 2j)}{2+j}$$

$$\boxed{\therefore i_2 = 1.97 - 2.9856j} \text{ A}$$

$$(\text{OR}) \quad \boxed{i_2 = 3.578 \angle -56.565^\circ} \text{ A}$$

In Loop 3:

$$\boxed{i_3 = I_0}$$

$$3V_0 + (-j2) i_3 = 0$$

But we know from ② that

$$V_0 = 2(i_1 - i_2)$$

$$= 2(2\sqrt{3} - 2j - 1.97 + 2.9856j)$$

$$= 2(1.494 + 0.9856j)$$

$$\Rightarrow \boxed{V_0 = 2.988 + 1.971j} \text{ Volts}$$

$$(\text{OR}) \quad \boxed{V_0 = 3.58 \angle 33.41^\circ} \text{ Volts}$$


$$\Rightarrow i_3 = \frac{3V_0}{2j} = \frac{10.74 \angle 33.41^\circ}{2 \angle 90^\circ} = 5.22 \angle -56.59^\circ \text{ A}$$

$$\boxed{\therefore I_0 = 5.22 \angle -56.59^\circ} \text{ A}$$

$$\boxed{\therefore I_0 = 2.874 - 4.357j} \text{ A}$$

$$\boxed{\therefore I_0 = 5.22 \angle -56.59^\circ \text{ A}}$$
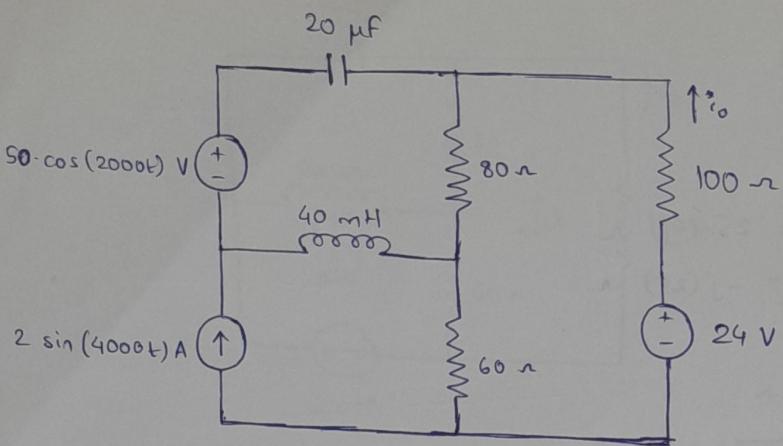
$$V_0 = 3.58 \angle 33.41^\circ \text{ A}$$




To find:

$$i_o$$


Process:

Superposition Theorem

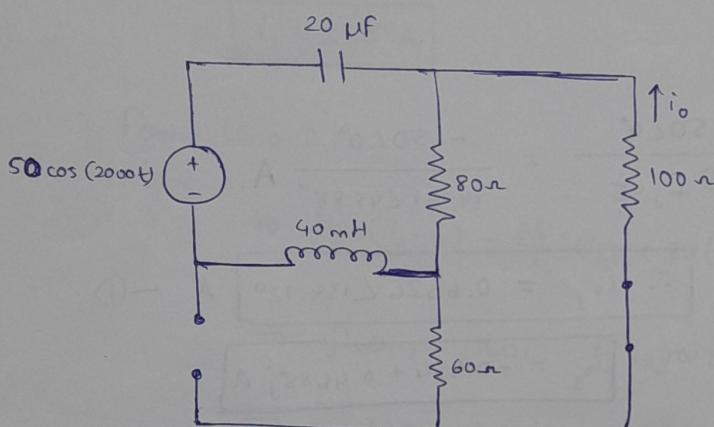
A3) Let's switch off all sources except $V_1 = 50 \cos(2000t)$ V



\downarrow

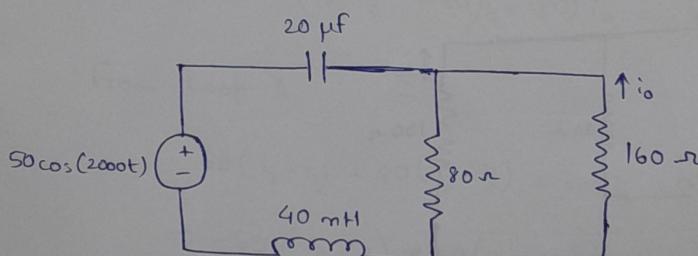

\downarrow

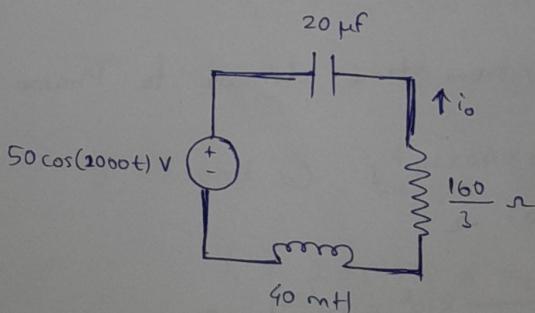


Quantities are given in time domain. Let us convert them to Phasor Domain, with $\omega = 2000 \text{ s}^{-1}$

$$X_L = j\omega L = j(2000)(40 \times 10^{-3})$$

$$= j(80) \Omega$$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{2000 \times 20} \times 10^6 = 25(j) \Omega$$

$$= -j(25) \Omega$$

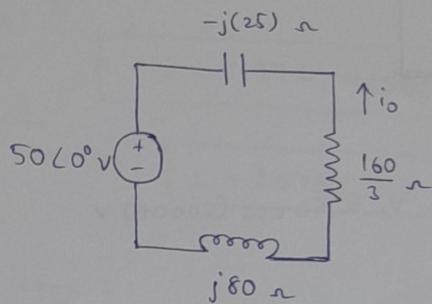


$$\therefore i_{o_L} = \frac{-50∠0^\circ}{\frac{160}{3} + j55} = \frac{-50∠0^\circ}{76.61∠45.88^\circ} A$$

$$\boxed{\therefore i_{o_1} = 0.6526∠134.12^\circ A} \quad \text{--- (1)}$$

(OR)

$$\boxed{i_{o_1} = -0.454 + 0.4685j A}$$

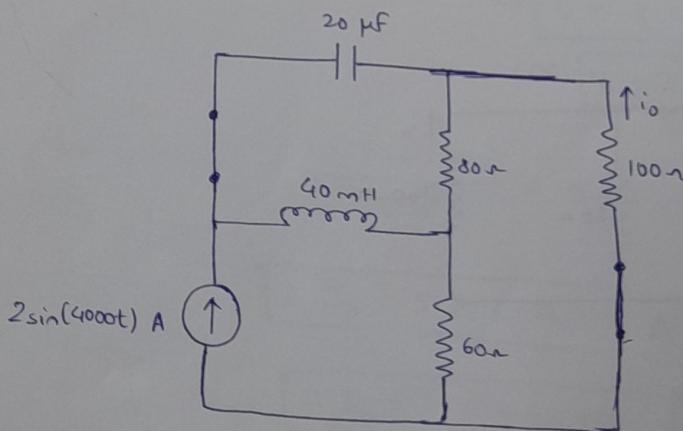Now, Let's switch off all sources except $V_2 = 2 \sin(4000t) A$




Let's convert quantities from time domain to Phasor Domain

$$X_L = j\omega L = 4000 \times 40 \times 10^{-3} j$$

$$= j(160) \Omega$$
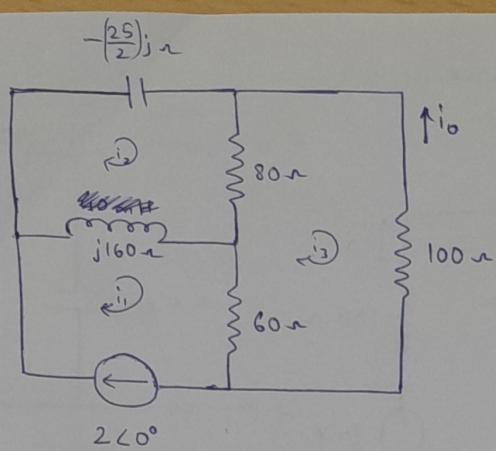
$$X_C = \frac{-j}{\omega C} = \frac{-j}{4000 \times 20} \times 10^6 = -\left(\frac{25}{2}\right)j \Omega$$



We can solve for i_{o_2} using Mesh Analysis.

From Loop 1:

$$i_1 = 2\angle 0^\circ \text{ A}$$

From Loop 2:

$$\begin{aligned}
 & \text{#} j160(i_2 - i_1) - \frac{25}{2}j(i_2) + 80(i_2 - i_3) = 0 \quad [i_3 = -i_{o_2}] \\
 \Rightarrow & j160i_2 - j160i_1 - \frac{25}{2}i_2j + 80i_2 + 80i_{o_2} = 0 \\
 \Rightarrow & -j320 + i_2(j160 - j\frac{25}{2}) + 80i_2 + 80i_{o_2} = 0 \\
 \Rightarrow & i_2(j160 - j\frac{25}{2} + 80) + i_{o_2}(80) = j320 \\
 \Rightarrow & \left(j\frac{295}{2} + 80\right)i_2 + (80)i_{o_2} = j320 \quad \text{--- (2)}
 \end{aligned}$$

From Loop 3:


$$\begin{aligned}
 & 60(i_3 - i_1) + 80(i_3 - i_2) + 100i_3 = 0 \\
 \Rightarrow & -60(i_{o_2} + 2) + 80(i_{o_2} + i_2) - 100i_{o_2} = 0 \\
 \Rightarrow & 60i_{o_2} + 120 + 80i_{o_2} + 80i_2 + 100i_{o_2} = 0 \\
 \Rightarrow & 240i_{o_2} + 80i_2 + 120 = 0 \\
 \Rightarrow & 6i_{o_2} + 2i_2 + 3 = 0 \quad \text{--- (3)}
 \end{aligned}$$

Solving (2) and (3), we get

$$i_2 = 2 + 0.45j \text{ A} = 2.056 \angle 12.754^\circ \text{ A}$$

$$i_{o_2} = -1.168 - 0.15j \text{ A} = 1.178 \angle -172.62^\circ \text{ A} \quad \text{--- (4)}$$


Finally, Let's short 24V source.

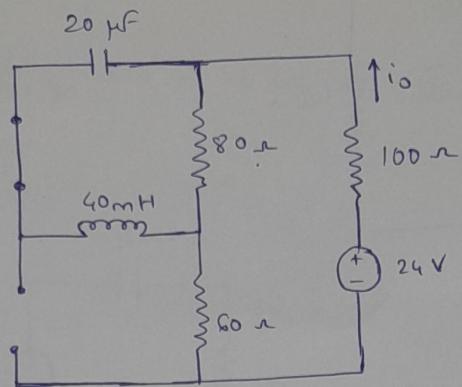

In DC conditions,

Capacitors act as Open Circuit

Inductors act as Close Circuit (Short)

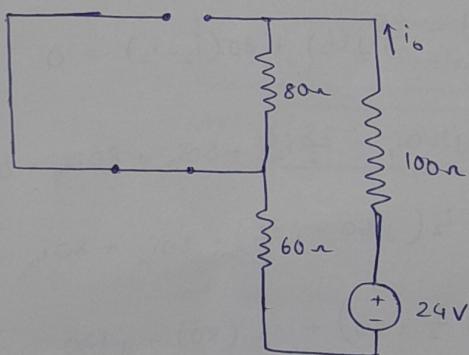


$$\therefore i_{o_2} = \frac{24}{240} = \frac{1}{10} \text{ A}$$

Now finally,


$$i_o = i_{o_1} + i_{o_2} + i_{o_3}$$

$$\therefore i_o = 0.6526 \cos(2000t + 134.12^\circ) + 1.178 \sin(4000t - 172.62^\circ) + \frac{1}{10} \text{ A}$$

We cannot Simplify further.

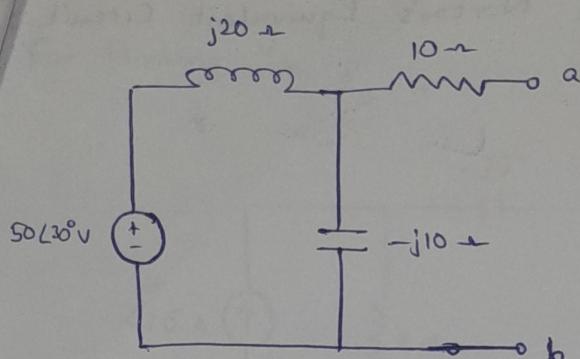

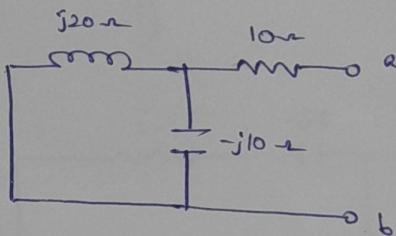Let's find Z_{Th} by turning off the sources.



$$(j20 \parallel -j10) + 10 = Z_{Th}$$

$$\Rightarrow Z_{Th} = 10 + \frac{j20 \times (-j10)}{j10} = j(-20) + 10$$

$$\therefore Z_{Th} = 10 - j20 \Omega$$

$$\therefore Z_N = 10 - j20 \Omega \Rightarrow Z_N = 22.36 \angle -63.435^\circ \Omega$$

①

For finding $V_{Th} = V_{ab}$:

$V_{ab} = V$ across $-j10 \Omega$ capacitor.

$$\Rightarrow V_{Th} = (50 \angle 30^\circ) \left(\frac{-j10}{j20 - j10} \right)$$

$$= 50 \angle 30^\circ (-1)$$

$$= (50 \angle 30^\circ) (1 \angle 180^\circ)$$

$$= 50 \angle 210^\circ$$


$$(OR) \boxed{V_{Th} = 50 \angle -150^\circ V}$$

∴


$$\therefore I_N = \frac{V_{Th}}{Z_{Th}} = \frac{50 \angle -150^\circ}{22.36 \angle -63.435^\circ} = 2.236 \angle -86.565^\circ A$$

$$\therefore I_N = 2.236 \angle -86.565^\circ A \quad -②$$

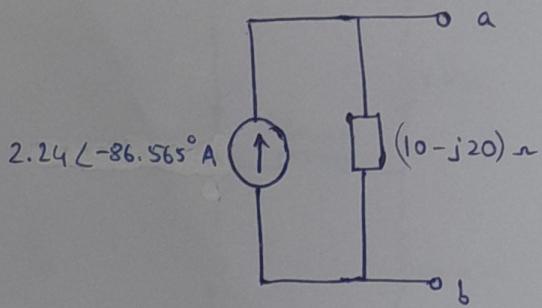
from ① and ②, we can draw the Norton's Equivalent Circuit



(b)

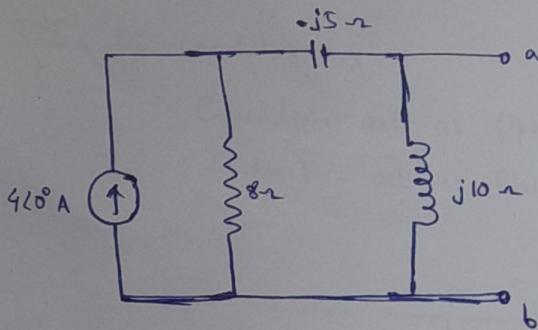

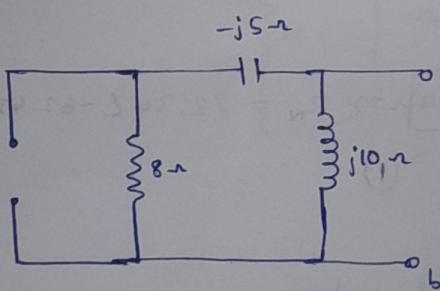for finding Z_{Th} , let's switch off the sources



$$Z_{Th} = (j10) \parallel (8 - j5)$$

$$= \frac{(j10)(8 - j5)}{8 + j5}$$



$$\Rightarrow Z_{Th} = \frac{800}{89} + j \frac{390}{89} \Omega$$

$$\therefore Z_{Th} = Z_N = (8.989 + 4.38j) \Omega$$

$$Z_N = 10 \angle 26^\circ \Omega$$

$$(OR) Z_N = 9 + 4.38j \Omega \quad - ①$$

for finding V_{Th} ,

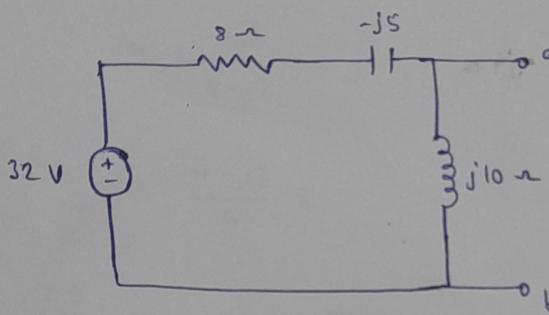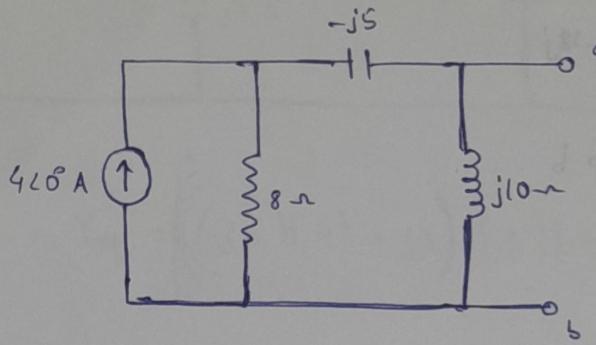

$$V_{ab} = V_{j10\Omega}$$

$$\therefore V_{Th} = (32 \angle 0^\circ) \left(\frac{j10}{8-j5+j10} \right)$$

$$= (32 \angle 0^\circ) (1.06 \angle 58^\circ) V$$

$$\boxed{\therefore V_{Th} = 33.92 \angle 58^\circ V}$$


$$\therefore I_N = \frac{V_{Th}}{Z_{Th}} = \frac{33.92 \angle 58^\circ}{10 \angle 26^\circ} A$$

$$= 3.392 \angle 32^\circ A$$

$$\boxed{\therefore I_N = 3.392 \angle 32^\circ A} \quad -②$$


$$(OR) \boxed{I_{Nr} = 2.88 + 1.8j} A$$

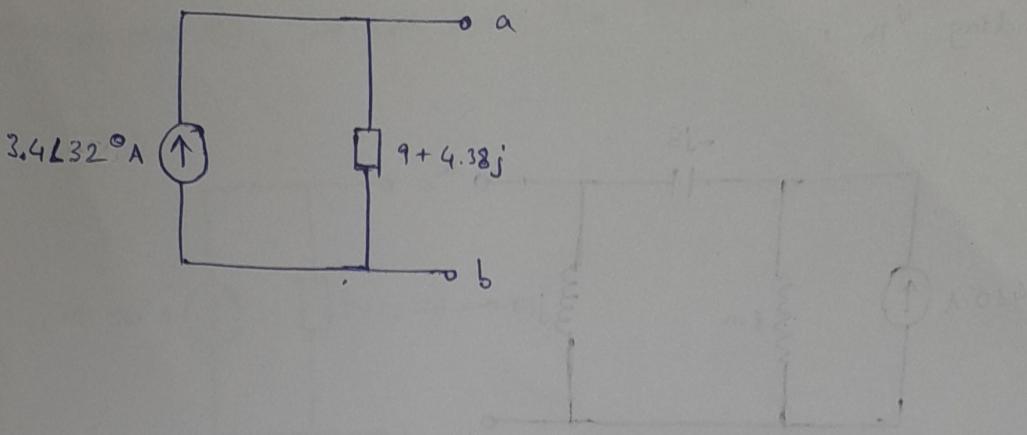Let's draw Norton's Equivalent Circuit: [from ① and ②]



Q5) (a)

(i)

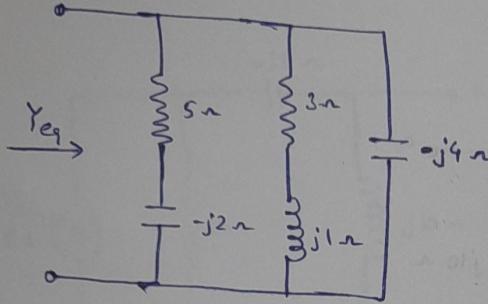

$$\text{Equivalent Admittance} = \frac{1}{\text{Eq. Impedance}}$$

$$Z_{eq} = (5-j2) \parallel (3+j) \parallel (-j4)$$

$$= \frac{(5-j2)(3+j)}{(8-j)} \parallel (-j4)$$

$$= \frac{\frac{(5-j2)(3+j)}{(8-j)} (-j4)}{\frac{(5-j2)(3+j)}{(8-j)} - j4} = \frac{(5-j2)(3+j)(-j4)}{(5-j2)(3+j) - j4(8-j)}$$


$$= 1.92 \angle -24.87^\circ = 1.74 - j0.8 \text{ ohms}$$

$$\therefore Y_{eq} = \frac{1}{Z_{eq}} = \frac{(5-j2)(3+j) - j4(8-j)}{(5-j2)(3+j)(-j4)} = \frac{13 - j33}{-4 - j68} \text{ S}$$

$$= \frac{35.4683 \angle -1.2^\circ}{68.1175 \angle -1.63^\circ}$$

$$Y_{eq} = 0.52 \angle 0.434^\circ \text{ S}$$
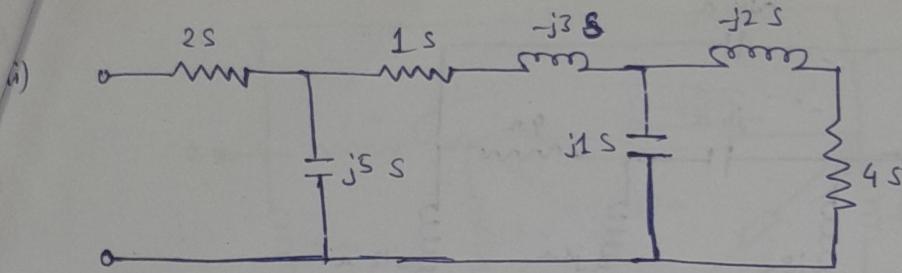
$$(\text{OR}) \quad Y_{eq} = 0.472 + 0.22j \text{ S}$$



$$Y_{eq} = \left[\left((-j2 \parallel 4) + j1 \right) \parallel 1 \parallel -j3 \right] \parallel 2$$

$$\Rightarrow Y_{eq_1} = \left(\frac{-j2 \times 4}{4-j2} \right) + j1$$


$$= \frac{-j8}{4-j2} + j$$

$$= \frac{4-j3}{5} s$$

1 and $-j3 \rightarrow$ series

$$\frac{1(-j3)}{1-j3} = \frac{-j3}{1-j3}$$

$$= \frac{9-j3}{10} s$$

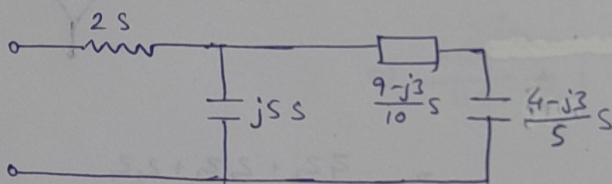

Now $\frac{9-j3}{10} s$ is in series with $\frac{4-j3}{5} s$

$$\Rightarrow \frac{(9-j3)(4-j3)}{50(9-j3+8-6j)} = \frac{81-j42}{185} s$$

$$\text{Now } \frac{81-j42}{185} + js = \frac{81+j883}{185} s$$


And $\frac{81+j883}{185}$ is in series with 2

$$\therefore Y_{eq} = \frac{\left(\frac{81+j883}{185} \right)_2}{\frac{81+j883}{185} + 2} = \frac{2(81+j883)}{451+j(883)} = (1.66 + 0.66j) s$$


$$\therefore Y_{eq} = 1.66 + 0.66j s$$

$$(\text{OR}) \quad Y_{eq} = 1.79 \angle 21.8^\circ s$$

5) (b)
(i)

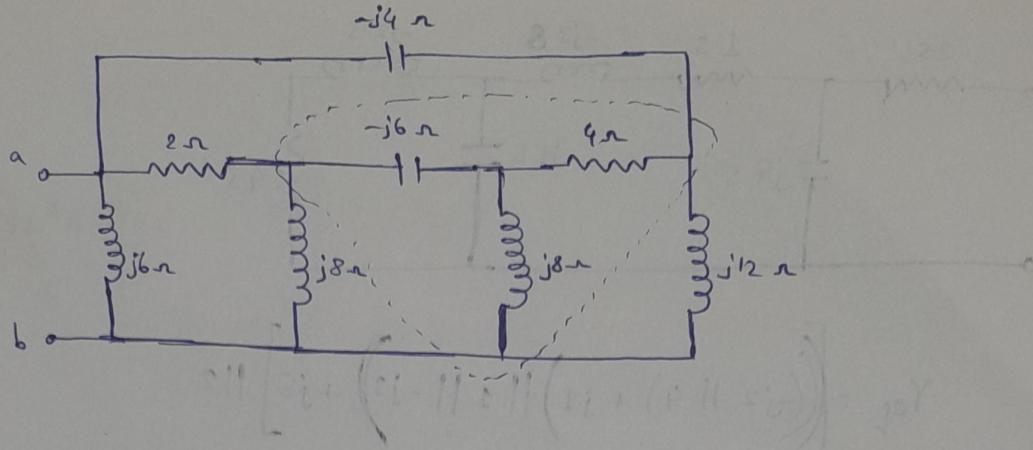

As we know,

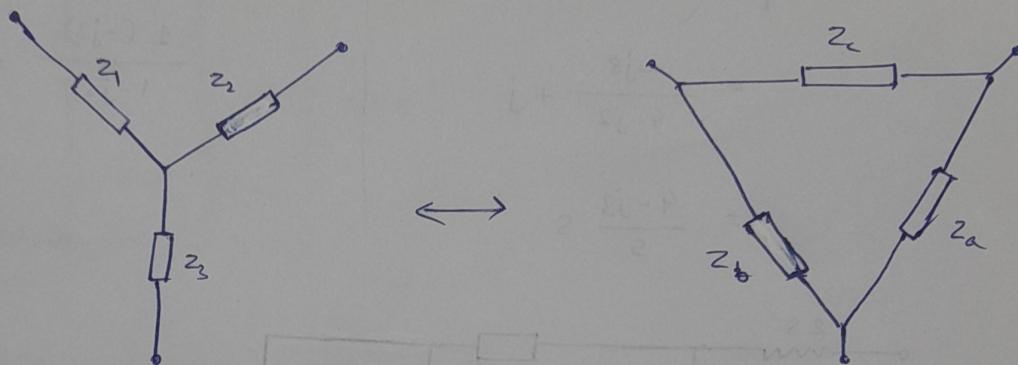

$$z_1 z_2 + z_2 z_3 + z_3 z_1$$

$$= (-j6)(4) + 4(j8) + (j8)(-j6)$$

$$= -j24 + j32 + 48$$

$$= 48 + j8$$

$$z_a = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_1}$$

$$z_b = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_2}$$


$$z_c = \frac{z_1 z_2 + z_2 z_3 + z_3 z_1}{z_3}$$

$$\therefore z_a = \frac{48 + j8}{-j6} = -\frac{4}{3} + j8 \text{ } \Omega$$

$$z_b = \frac{48 + j8}{4} = 12 + j2 \text{ } \Omega$$

$$z_c = \frac{48 + j8}{j8} = 1 - 6j \text{ } \Omega$$

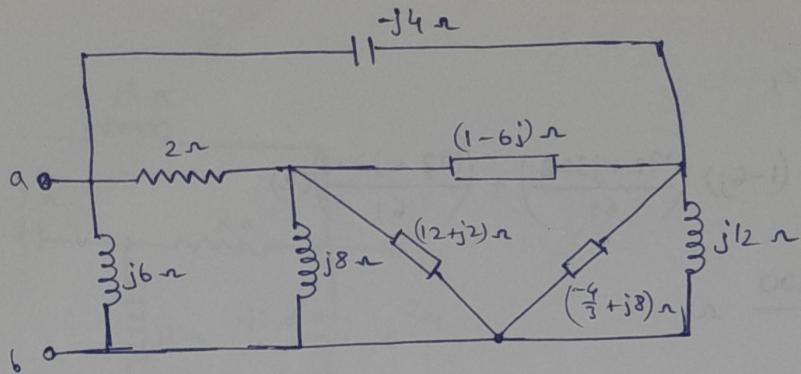We can redraw the circuit using this Δ to ∇ transformation.




$$(12+j2) \parallel j8 \Rightarrow \frac{(12+j2)(j8)}{12+j10} \text{ ohm}$$

$$\Rightarrow \frac{(6+j)(j8)}{6+j5} \text{ ohm}$$



$$\Rightarrow \frac{192 + j328}{61} \text{ ohm}$$

$$\left(-\frac{4}{3}+j8\right) \parallel j12 \Rightarrow \frac{\left(-\frac{4}{3}+j8\right)(j12)}{\left(-\frac{4}{3}+j20\right)} \text{ ohm}$$
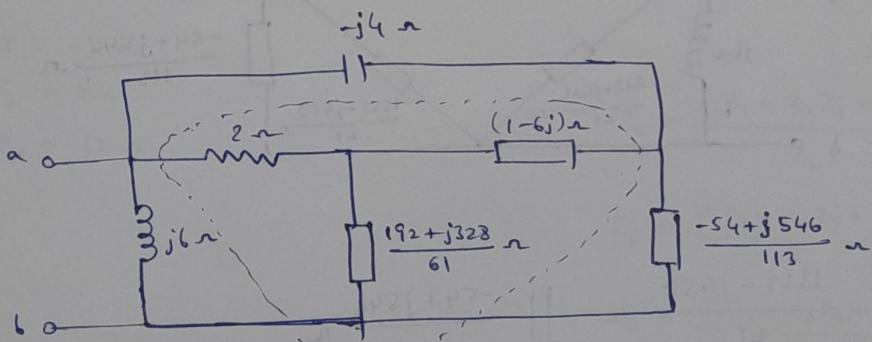
$$\Rightarrow \frac{-54}{113} + j \frac{546}{113} \text{ ohm}$$



Applying Δ to ∇ transformation again:

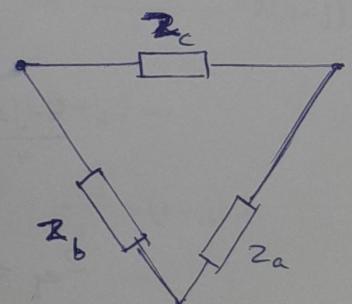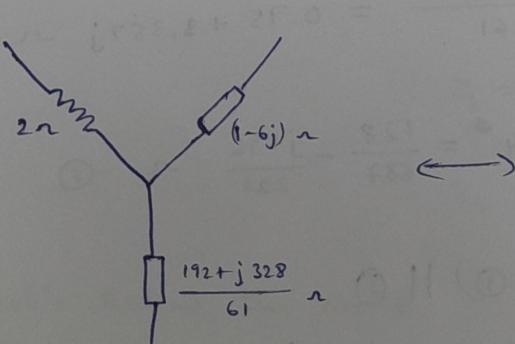

$$Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1$$


$$= 2(1-6j) + (1-6j) \left(\frac{192+j328}{61} \right) + \left(\frac{192+j328}{61} \right)(2)$$

$$= \frac{2666 - j900}{61} \Omega$$


$$Z_a = \frac{1333 - j450}{61} \Omega$$

$$Z_b = \frac{6 - j29}{4} \Omega$$

$$Z_b = \frac{218 + j403}{61} \Omega$$

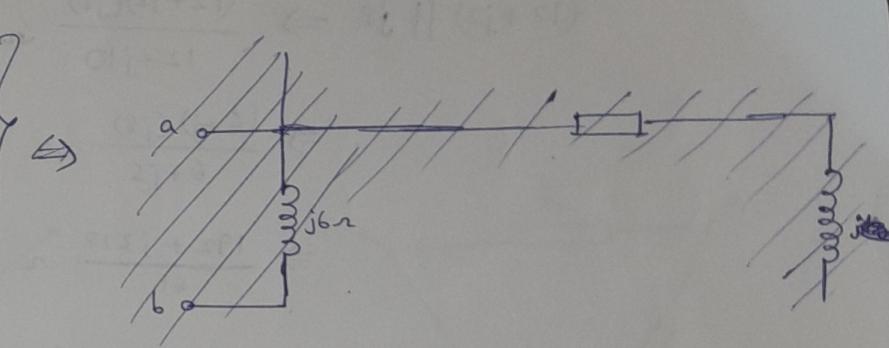

Let's draw the circuit now :

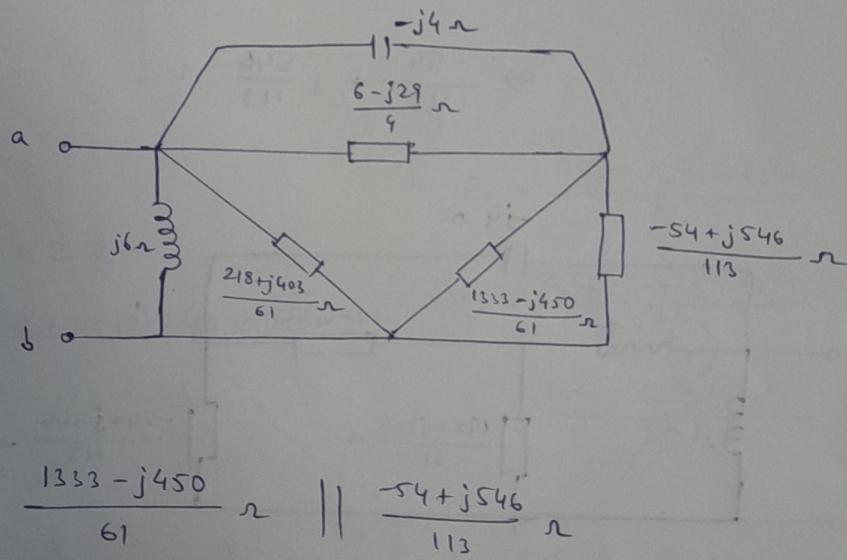

$$\frac{1333 - j450}{61} \Omega \parallel \frac{-54 + j546}{113} \Omega$$

$$= \frac{1314 + j12066}{2333} \Omega \quad \text{--- (1)}$$


$$j6 \parallel \frac{218 + j403}{61} = 0.75 + 3.357j \Omega \quad \text{--- (2)}$$

$$\frac{6 - j29}{4} \parallel -j4 = \frac{128}{687} - \frac{j596}{229} \Omega \quad \text{--- (3)}$$


$$Z_{eq} = (3) + (1) \parallel (2)$$

$$= (0.75 + 2.57j) \parallel (0.75 + 3.357j) \Omega$$
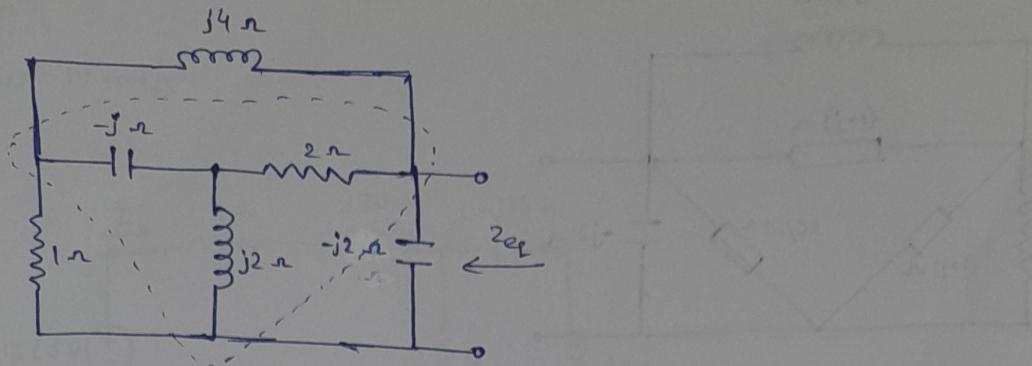
$$\therefore Z_{eq} = 0.33 + 1.457j \Omega \Rightarrow Z_{eq} = 1.575 \angle 75.34^\circ \Omega$$



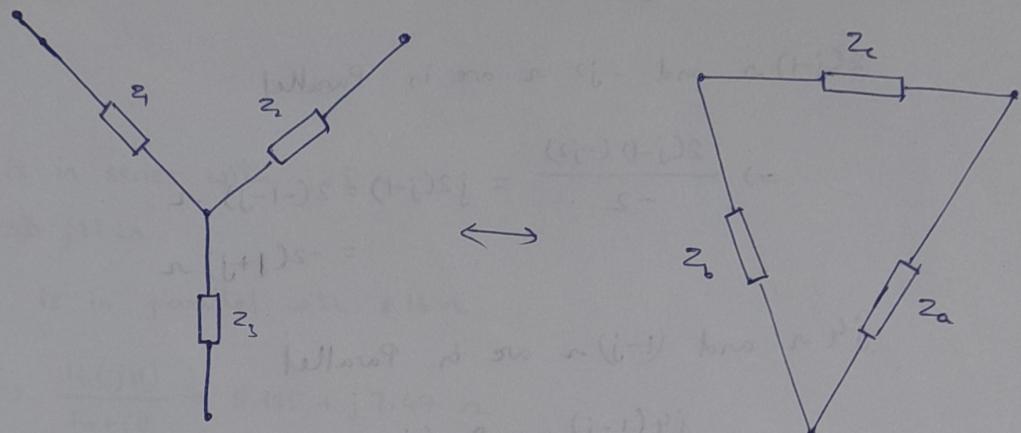As we know, Conversion from Δ to ∇ is as follows



$$Z_1 = -j1 \Omega$$

$$Z_2 = 2 \Omega$$

$$Z_3 = j2 \Omega$$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

$$\therefore Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1$$

$$= -j2 + j4 + 2$$


$$= 2 + j2 \Omega$$

$$\therefore Z_a = \frac{2(1+j)}{-j} = \frac{-2+2j}{1} = -2(1-j) \Omega$$

$$Z_b = \frac{2(1+j)}{2} = (1+j) \Omega$$

$$Z_c = \frac{2(1+j)}{j2} = \frac{1+j}{j} = (1-j) \Omega$$

Now let's Redraw the circuit.

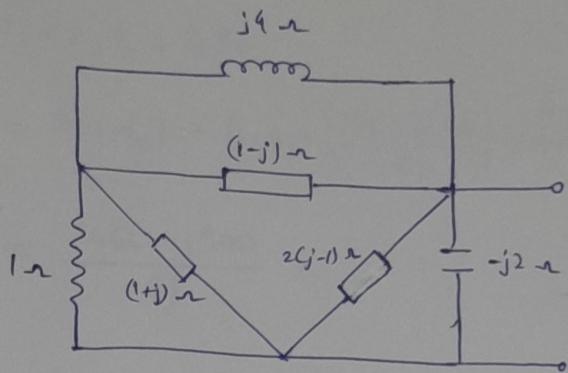

1Ω and $(1+j) \Omega$ are in Parallel

$$\Rightarrow \frac{1+j}{2+j} \Omega = \frac{3+j}{5} \Omega$$


$2(j-1) \Omega$ and $-j2 \Omega$ are in Parallel

$$\Rightarrow \frac{2(j-1)(-j2)}{-2} = j2(j-1) = 2(-1-j) \Omega$$

$$= -2(1+j) \Omega$$

$j4 \Omega$ and $(1-j) \Omega$ are in Parallel
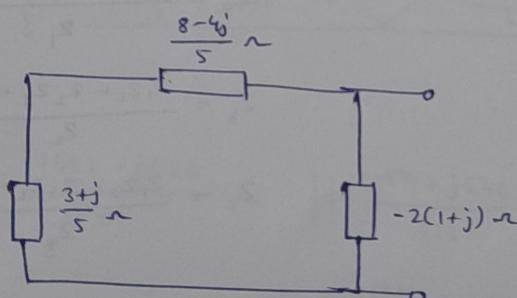
$$\Rightarrow \frac{j4(1-j)}{1+j3} = \frac{8-4j}{5} \Omega$$




$$Z_{\text{eff.}} = \left(\frac{8-4j+3+j}{5} \right) || (-2(1+j))$$

$$= \left(\frac{11-3j}{5} \right) || (2(-1-j))$$

$$Z_{\text{eff.}} = \frac{18-j38}{17} \Omega \Rightarrow \boxed{\therefore Z_{\text{eff.}} = 1.06-2.235j \Omega}$$

Given:

$$\omega = 10 \text{ rad/s}$$

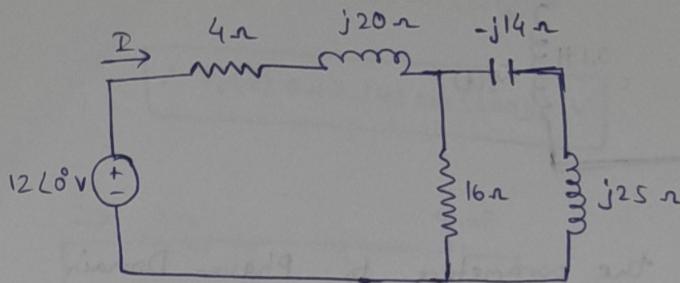

To find:

$$Z_{eq} \text{ and } I$$

Solution:

$-j14$ is in series with $j25\Omega$

$$\Rightarrow j11\Omega$$

$j11\Omega$ is in parallel with 16Ω

$$\Rightarrow \frac{16(j11)}{16+j11} = 5.135 + j7.47\Omega$$

4Ω and $j20\Omega$ are in series

$$\Rightarrow 4+j20\Omega$$

$$\begin{aligned} \text{Now } Z_{eq.} &= (4+j20) + (5.135 + j7.47) \Omega \\ &= (9.1353 + j27.47) \Omega \end{aligned}$$

$$\therefore Z_{eq} = 9.1353 + j27.47 \Omega$$


$$\text{OR } Z_{eq} = 28.95 \angle 71.6^\circ \Omega$$

$$\therefore I = \frac{V}{Z_{eq}} = \frac{12\angle 0^\circ}{28.95 \angle 71.6^\circ} \text{ A}$$

$$\therefore I = 0.131 - 0.4j \text{ A}$$

$$\text{OR } \therefore I = 0.4145 \angle -71.6^\circ \text{ A} \Rightarrow I = 0.4145 \cos(10t - 71.6^\circ) \text{ A}$$

7)

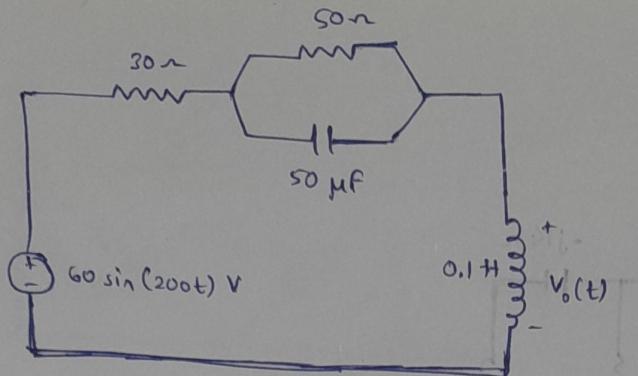

First let's convert all the parameters to Phasor Domain

$$\omega = 200 \text{ rad/s}$$



$$30 \Omega \rightarrow 30 \Omega$$

$$50 \mu F \rightarrow 50 \mu F$$

$$60 \sin(200t) \rightarrow 60 L - 90^\circ$$

$$50 \mu F \rightarrow \frac{1}{j \times 50 \times 10^{-6} \times 200} = \frac{-j}{10^{-2}} = -100j$$
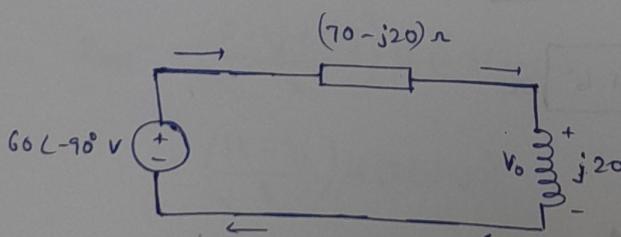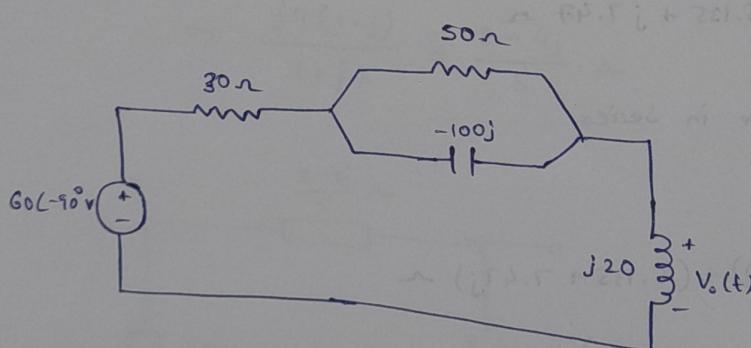
$$0.1 H \rightarrow j \times 200 \times 0.1 = 20j$$



$$[(50 \Omega) || (-100j) \Omega] + 30 \Omega$$

$$= \frac{(50)(-100j)}{50 - 100j} + 30$$

$$= \frac{-100j}{1 - 2j} + 30$$

$$= 70 - j 20 \Omega$$

$$\therefore V_o(t) = (60 L - 90^\circ V) \left(\frac{j 20}{70 - j 20 + j 20} \right)$$

$$= (60 L - 90^\circ) \left(\frac{2}{7} \angle 90^\circ \right) = \frac{120}{7} \angle 90^\circ V$$

$$\text{But opposite direction, } V_o = \frac{120}{7} \angle 180^\circ V$$


$$\therefore V_o(t) = \frac{120}{7} 480^\circ V$$

$$= 17.143 480^\circ V = 17.143 \cos(\omega t + 180^\circ)$$

$$\Rightarrow V_o(t) = -17.143 (\cos(\omega t)) V$$

$$\boxed{\therefore V_o(t) = -17.143 \cos(200t) V}$$

8)

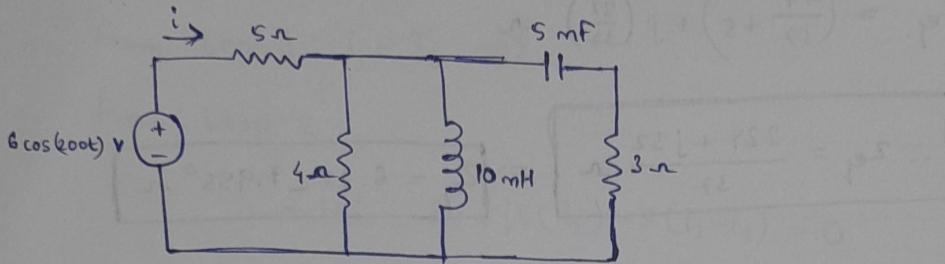

All the quantities are present in time domain,

let's convert to Phasor Domain with $\omega = 200 \text{ rad/s}$

$$6 \cos(200t) V \rightarrow 6 \angle 0^\circ V$$

$$5\Omega \rightarrow 5\Omega$$


$$4\Omega \rightarrow 4\Omega$$

$$10mH \rightarrow j \times 10^{-2} \times 200 = j2$$

$$3\mu F \rightarrow \frac{-j}{3 \times 10^{-6} \times 200} = -j$$

$$3\mu F \rightarrow \frac{-j}{3 \times 10^{-6} \times 200} = -j$$

Let's Redraw the circuit :

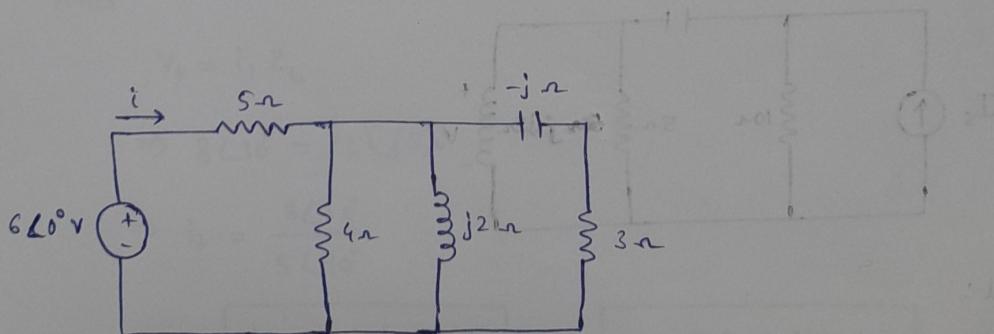

We can find Z_{eq} and then $i(t) = \frac{V(t)}{Z_{eq}}$.

$-j\Omega$ and 3Ω are in Series : $3-j\Omega$

$3-j\Omega$ and $j2\Omega$ are in Parallel :

$$\frac{(3-j)(j2)}{(3+j)} = \frac{6+j8}{5} \Omega$$

$\frac{6+j8}{5} \Omega$ and 4Ω are in Parallel :

$$\frac{(6+j8)(4)}{(26+j8)} = \frac{44}{37} + j \frac{32}{37} \Omega$$

Now, in series with 5Ω ,

$$\text{i.e. } Z_{eq} = \left(\frac{44}{37} + 5 \right) + j \left(\frac{32}{37} \right) \Omega$$

$$\therefore Z_{eq} = \frac{229 + j32}{37} \Omega \Rightarrow Z_{eq} = 6.25 \angle 7.955^\circ \Omega$$


Now, $I = \frac{(6 \angle 0^\circ)}{Z_{eq}} = \frac{6 \angle 0^\circ}{6.25 \angle 7.955^\circ} A$

$$\therefore I = 0.96 \angle -7.955^\circ A$$

$$\therefore i(t) = 0.96 (\cos(200t - 7.955^\circ)) A$$

9) Given :

$$V_0 = 8 \angle 30^\circ V$$

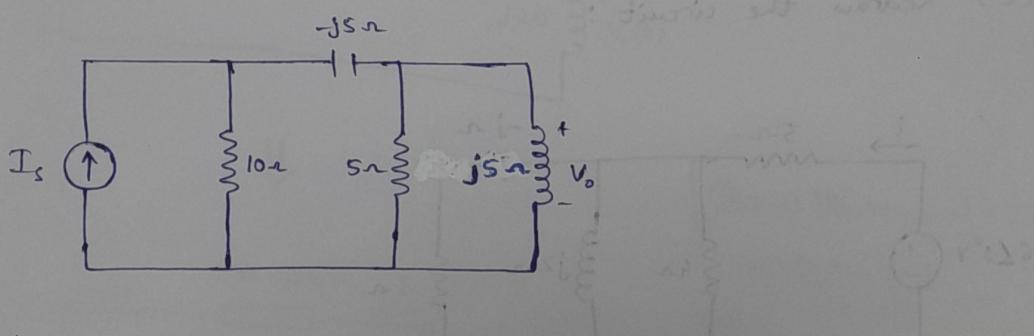


To find :

$$I_s$$

Solution :

Through Mesh Analysis, we can obtain I_s . Let's consider i_1 , i_2 and i_3 in first, second and third loop respectively.

$$\therefore i_1 = I_s$$

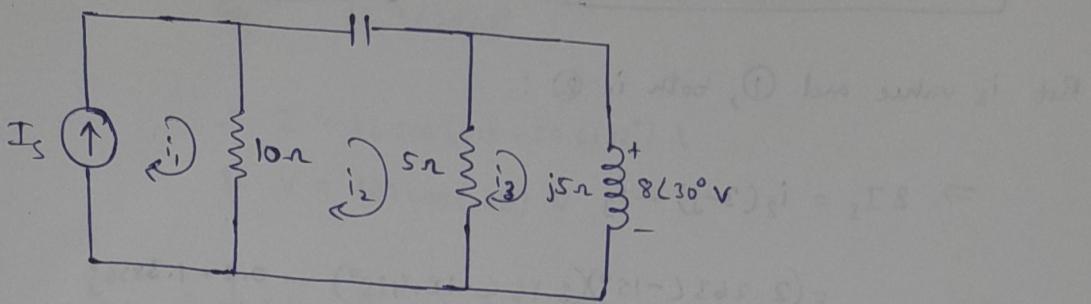

From Loop 1: $i_1 = I_s - ①$

From Loop 2:

$$-10(i_2 - i_1) + j5(i_2) - 5(i_2 - i_3) = 0$$

$$\Rightarrow -10i_2 + 10i_1 + j5i_2 - 5i_2 + 5i_3 = 0$$

$$\Rightarrow 10i_1 + i_2(-15 + j5) + 5i_3 = 0$$

$$\Rightarrow 2i_1 + i_2(-3 + j) + i_3 = 0 \quad -②$$

From Loop 3:

$$-5(i_3 - i_2) - V_o = 0$$

$$\Rightarrow V_o = 5(i_2 - i_3)$$

$$\Rightarrow 8\angle 30^\circ = 5(i_2 - i_3) \quad -③$$

And

$$V_o = i_3 Z_L$$

$$\Rightarrow 8\angle 30^\circ = i_3(j5) \quad \text{using } Z_L = j5 \text{ ohms}$$

$$\Rightarrow i_3 = \frac{8\angle 30^\circ}{j5} \quad \text{using } \frac{1}{j5} = -j0.2 \text{ A/V}$$

$$\therefore i_3 = 1.6\angle -60^\circ \text{ A} \Rightarrow i_3 = 0.8 - 1.3856j \text{ A} \quad -④$$

Put ④ in ①:

$$\Rightarrow 8\angle 30^\circ + 5i_3 = 5i_2$$

$$\Rightarrow 8\angle 30^\circ + 8\angle -60^\circ = 5i_2$$

$$\Rightarrow 6.93 + 4j + 4 - 6.93j = 5i_2$$

$$\Rightarrow 10.93 - 2.93j = 5i_2$$

$$\boxed{i_2 = 2.1856 - j0.5856 \text{ A}} \quad (\text{OR}) \quad \boxed{i_2 = 2.263 \angle -15^\circ}$$

Put i_2 value and ①, both in ② :


$$\Rightarrow 2I_s = i_2(3-j) - i_3 \\ = (2.263 \angle -15^\circ)(3.16 \angle -18.435^\circ) - 0.8 + 1.3856j$$

$$\therefore I_s = \frac{5.17 - 2.557j}{2} \text{ A}$$

$$\boxed{i_s = 2.5856 - j1.278 \text{ A}}$$

$$(\text{OR}) \quad \boxed{I_s = 2.88 \angle -26.31^\circ \text{ A}}$$

10)

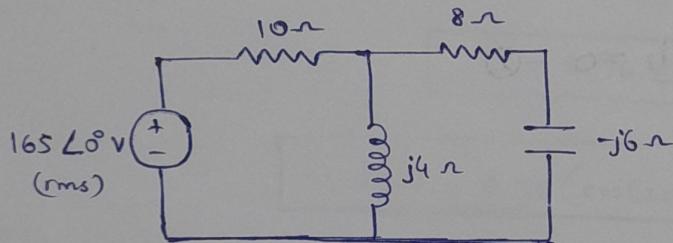

To Find:

Avg. Power supplied by the source and Power factor

Solution:

Let's find Z_{eq} :

8Ω in series with $-j6\Omega$ $\Rightarrow (8-j6)\Omega$

$$(8-j6)\Omega \parallel (j4)\Omega \Rightarrow \frac{(8-j6)(j4)}{(8-j2)} = \frac{32+j76}{17} \Omega$$

$$\frac{32+j76}{17} \Omega \text{ series with } 10\Omega \Rightarrow Z_{eq} = \frac{32+j76}{17} + 10$$

$$\therefore Z_{eq} = \frac{202+j76}{17} \Omega$$

$$\boxed{\therefore Z_{eq} = 11.88 + 4.47j \Omega}$$

$$(\text{OR}) \quad \boxed{Z_{eq} = 12.7 \angle 20.62^\circ \Omega}$$

Now

$$\text{Now, } I = \frac{V}{Z_{eq.}} = \frac{165 \angle 0^\circ}{12.7 \angle 20.62^\circ} A = 13 \angle -20.6182^\circ A$$

$$\therefore I = 13 \cos(\omega t - 20.6182^\circ) A$$

$$\& V = 165 \cos(\omega t) V$$

$$P_{avg.} = \frac{1}{2} \times V_m \times I_m \times \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \times V_{rms} \times \sqrt{2} \times I_{rms} \times \sqrt{2} \times \cos(\theta_v - \theta_i)$$

$$\Rightarrow P_{avg.} = V_{rms} \times I_{rms} \times \cos(\theta_v - \theta_i)$$

$$= 13 \times 165 \times \cos(0^\circ + 20.6182^\circ)$$

$$\therefore P_{avg.} = 2007.6 W$$

$$\text{And, } Pf = \frac{P}{S} = \frac{V_{rms} \cdot I_{rms} \cdot \cos(\theta_v - \theta_i)}{V_{rms} \cdot I_{rms}}$$

$$\therefore Pf = \cos(\theta_v - \theta_i)$$

$$\Rightarrow Pf = \cos(20.6182^\circ)$$

$$\left[\begin{array}{l} \theta_v = 0^\circ \\ \theta_i = -20.6182^\circ \end{array} \right]$$

$$\therefore Pf = 0.936$$

$\theta_v > \theta_i \Rightarrow \text{Lagging pf}$

$\therefore \text{Inductive,}$

which is proved
from the circuit.


11) Given:

60 n Resistor ~~not~~ absorbs 240 W ($P_{avg.}$)


To find:

Complex Power (S) of each branch in circuit & Overall Complex Power, V.

Solution:

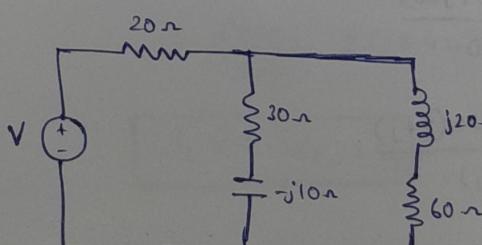

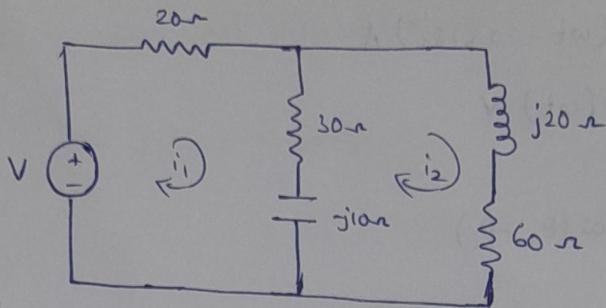ten let's consider i_1 flowing in loop 1 and i_2 flowing in loop 2.



In Loop 1:

$$V - 20i_1 - 30(i_1 - i_2) + j10(i_1 - i_2) = 0$$

$$\Rightarrow V - 20i_1 - 30i_1 + 30i_2 + j10i_1 - j10i_2 = 0$$

$$\Rightarrow V - i_1(50 - j10) + i_2(30 - j10) = 0$$

$$\Rightarrow \boxed{V = i_1(50 - j10) + i_2(30 - j10)} \quad \text{--- (1)}$$

In Loop 2:

$$-j20(i_2) - 60i_2 + j10(i_2 - i_1) - 30(i_2 - i_1) = 0$$

$$\Rightarrow i_1(30 - j10) - i_2(90 + j10) = 0$$

$$\Rightarrow i_1(30 - j10) = i_2(90 + j10)$$

$$\Rightarrow \boxed{i_1(3 - j) = i_2(9 + j)} \quad \text{--- (2)}$$

$$\boxed{V_{60\Omega} = i_2 \times 60} \quad \text{--- (3)}$$

Finding Z_{eq} :

$$\left[(30 - j10) || (j20 + 60) \right] + 20$$

$$\Rightarrow Z_{eq} = 20 + \frac{(30 - j10)(60 + j20)}{90 + j10}$$

$$= 20 + \frac{(10)(3 - j) * 20(3 + j)}{10(9 + j)}$$

$$= 20 \left(1 + \frac{10}{9 + j} \right)$$

$$\therefore Z_{eq} = 41.95 - 2.44j \Omega$$

$$\Rightarrow Z_{eq} = 42 \angle -3.33^\circ \Omega$$

(OR)

Ans

From ① and ② :

$$V = i_1(50 - j10) - i_1(8.05 - 7.56j)$$

$$\therefore V = i_1(41.95 - 2.44j)$$

$$[V = i_1 \times Z_{eq}]$$

$$\therefore Z_{eq} = 41.95 - j2.44 \Omega$$

From ③ ,

$$V_{60\Omega} = i_2 \times 60 \text{ V}$$

$$i_{60\Omega} = i_2$$

$\therefore \cos(\theta_V - \theta_i) = 0$ for the Resistor as both Voltage and Current are in phase for the Resistor.

$$P_{avg} = \frac{1}{2} \times V_m \times I_m = V_{rms} \times I_{rms}$$

$$= 60(i_2) \times i_2$$

$$\Rightarrow 60i_2^2 = 240 \text{ (given)}$$

$$\Rightarrow i_2^2 = 4 \text{ A}^2$$

$$\therefore i_2 = 2 \text{ A}$$

$$\Rightarrow i_2 = 2 \angle \tan^{-1}\left(\frac{20}{60}\right) \text{ A}$$

$$\Rightarrow i_1 = i_2 \times \frac{9+j}{3-j}$$

$$\therefore i_2 = 2 \angle 18.435^\circ \text{ A} \Rightarrow i_2 = 1.897 + j0.632 \text{ A}$$

$$= \frac{18+2j}{8-2j} \quad 2 \angle 18.435^\circ \times \frac{9.055 \angle 6.34^\circ}{3.162 \angle -18.435^\circ} \text{ A}$$

$$\therefore i_1 = 4.174 + j(3.92) \text{ A}$$

$$\Rightarrow i_1 = 5.727 \angle 43.21^\circ \text{ A}$$

$$\text{And } V = i_1 \cdot Z_{eq}$$

$$\begin{aligned} \therefore V &= (4.17 + j3.92)(41.95 - j2.44) \\ &= (5.727 \angle 43.21^\circ)(42 \angle -3.33^\circ) \\ &= 240.54 \angle 39.88^\circ \end{aligned}$$

$$\boxed{\therefore V = 240.54 \angle 39.88^\circ V}$$

$$\begin{aligned} \text{Overall Complex Power } (S) &= V_{rms} \cdot I_{rms} (\theta_v - \theta_i) \\ &= 240.54 \times 5.727 \angle 39.88^\circ - 43.21^\circ \\ &= 1377.573 \angle -3.33^\circ \text{ VA} \end{aligned}$$

$$\boxed{\therefore S = 1377.573 \angle -3.33^\circ \text{ VA}}$$

$$\Rightarrow \boxed{S = 1375.25 - 80j \text{ VA}}$$

$$\begin{aligned} S_{20_2} &= (i_{rms} \times R) \times i_{rms} \angle \theta_v - \theta_i \\ &= (5.727)^2 \times 20 \angle 0^\circ \end{aligned}$$

$$\Rightarrow \boxed{S_{20_2} = 655.97 \text{ VA}}$$

$$\begin{aligned} S_{30_2 - 70_2} &= (125.83)(4) \angle 36.85^\circ - 55.3^\circ \\ &= 503.32 \angle -18.45^\circ \text{ VA} \end{aligned}$$

$$\boxed{\therefore S_{30_2 - 70_2} = 503.32 \angle -18.45^\circ \text{ VA}}$$

$$\begin{aligned} S_{60 + j20_2} &= (125.83)(2) \angle 36.85^\circ - 18.45^\circ \\ &= 251.66 \angle 18.415^\circ \end{aligned}$$

$$\boxed{\therefore S_{60 + j20_2} = 251.66 \angle 18.415^\circ \text{ VA}}$$

$$S_{30 - j70_2} = 477.45 - 159.3j \text{ VA}$$

$$S_{60 + j20_2} = 238.77 + 79.5j \text{ VA}$$

$$S_{20_2} = 655.97 + 0j \text{ VA}$$

$$\begin{aligned} V - V_0 &= 20i_1 \\ \Rightarrow V_0 &= V - 20i_1 \\ &= 125.83 \angle 36.85^\circ \text{ V} \\ \therefore V_0 &= 100.7 + j(75.46) \text{ V} \end{aligned}$$

$$\begin{aligned} i_0 &= i_1 - i_2 = 2.277 + 3.289j \text{ A} \\ &= 4 \angle 55.3^\circ \text{ A} \end{aligned}$$


$$[V_0 = V_{30_2} \text{ and } i_0 = i_{30_2}]$$

Adding gives $S = 1375.2 - 80j \text{ VA}$
i.e. Overall Complex Power

Given:

$$Z_1 = 60 \angle -30^\circ \Omega$$

$$Z_2 = 40 \angle 45^\circ \Omega$$

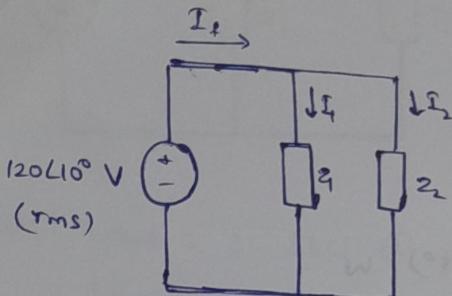

To find:

- (a) Apparent Power (c) Reactive Power
(b) Real Power (d) pf

Solution:

$$\text{Apparent Power (S)} = V_{\text{rms}} \times I_{\text{rms}}$$

$$\text{For } I_{\text{rms}}, \text{ we need to find } Z_{\text{eq}} \text{ and } I_{\text{rms}} = \frac{V_{\text{rms}}}{Z_{\text{eq}}}.$$

$$Z_{\text{eq}} = \frac{Z_1 \times Z_2}{Z_1 + Z_2} = \frac{(60 \angle -30^\circ)(40 \angle 45^\circ)}{60 \angle -30^\circ + 40 \angle 45^\circ} \Omega$$

$$\left[\begin{array}{l} 60 \angle -30^\circ = 51.96 - j 30 \\ 40 \angle 45^\circ = 28.284 + j 28.284 \end{array} \right] \rightarrow Z_1 + Z_2 = 80.264 - j 1.716 \Omega$$

$$\therefore Z_1 + Z_2 = 80.264 \angle -1.225^\circ \Omega$$

$$\Rightarrow Z_{\text{eq}} = \frac{2400 \angle 15^\circ}{80.264 \angle -1.225^\circ} \Omega$$

$$\therefore Z_{\text{eq}} = 29.9 \angle 16.225^\circ \Omega \Rightarrow Z_{\text{eq}} = 28.71 + j 8.355 \Omega$$

$$\therefore I_{\text{rms}} = \frac{V_{\text{rms}}}{Z_{\text{eq}}} = \frac{120 \angle 10^\circ}{29.9 \angle 16.225^\circ} A$$

$$\therefore I_{\text{rms}} = 3.9895 - j 0.435 A$$

$$\therefore I_{\text{rms}} = 4.0132 \angle -6.225^\circ A$$

$$(a) \text{ Apparent Power} = V_{rms} \times I_{rms}$$

$$\Rightarrow S = 120 \times 4.0132 \text{ VA}$$


$$\therefore S = 481.584 \text{ VA}$$

(b) Real Power (or) Avg. Power (P)

$$P = S \cos(\theta_v - \theta_i)$$

$$\Rightarrow P = 481.584 \times \cos(10^\circ + 6.225^\circ)$$

$$\therefore P = 462.4 \text{ W}$$

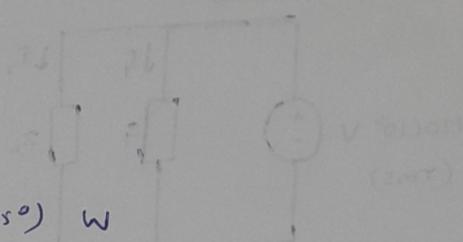

(c) pf Reactive Power (Q)

$$\text{Complex Power (S)} = V_{rms} \times I_{rms} \angle \theta_v - \theta_i$$

$$= 481.584 \angle 16.225^\circ$$

$$\Rightarrow S = 462.4 + 134.56j$$

$$\therefore Q = 134.56 \text{ VAR}$$

$$(\text{OR}) \quad Q = V_{rms} \times I_{rms} \times \sin(\theta_v - \theta_i)$$

$$= 481.584 \times \sin(16.225^\circ)$$

$$= 134.56 \text{ VAR}$$

(d) pf (Power factor)

$$pf = \frac{P}{S} = \cos(\theta_v - \theta_i)$$

$$= \cos(16.225^\circ)$$


$$= 0.96$$

$\theta_v - \theta_i > 0 \Rightarrow \text{Lagging pf}$

$$\therefore pf = 0.96$$

\downarrow
Inductive Load

Given:

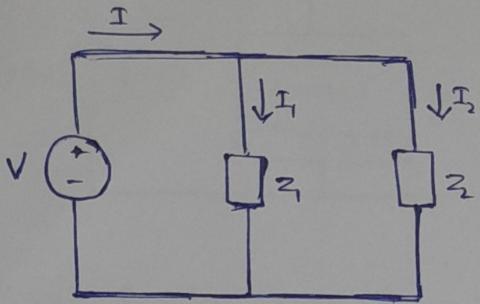

~~Load 1~~ Load 1 : 2kW @ pf = 0.75 leading

Load 2 : 4kW @ pf = 0.95 lagging

Solution :

$$P_1 = V \cdot I_1 \cdot \cos(\theta_V - \theta_{i_1})$$

$$P_2 = V \cdot I_2 \cdot \cos(\theta_V - \theta_{i_2})$$

$$Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$pf_1 = \cos(\theta_V - \theta_{i_1}) = 0.75$$

$$pf_2 = \cos(\theta_V - \theta_{i_2}) = 0.95$$

$$I_1 = I \cdot \frac{Z_2}{Z_1 + Z_2}$$

$$\Rightarrow 2000 = V \cdot I_1 \times 0.75$$

$$\Rightarrow \frac{8000}{3} = V \cdot I \cdot \frac{Z_2}{Z_1 + Z_2}$$

$$= V \times \frac{V}{Z_{eq}} \times \frac{(Z_1 + Z_2) Z_2}{(Z_1 + Z_2)}$$

$$= \frac{V^2 Z_2}{Z_1 Z_2} = \frac{V^2}{Z_1}$$

$$\Rightarrow \frac{8000}{3} = \frac{V_{rms}^2}{Z_1} - ①$$

$$\& 4000 = \frac{V^2}{Z_2} \times 0.95$$

$$\Rightarrow \frac{80000}{19} = \frac{V_{rms}^2}{Z_2} - ②$$

$$\therefore \frac{Z_1}{Z_2} = \frac{30}{19}$$

$$\begin{aligned} P &= P_1 + P_2 = V \cdot I / \cos(\theta_V - \theta_i) \\ \Rightarrow 6000 &= V \cdot I \cos(-\theta_i) \end{aligned}$$

$$\left(\text{where } I = \frac{V}{Z_{eq}} \right)$$

$$\theta_V - \theta_{i_1} < 0 \Rightarrow \theta_V - \theta_{i_1} = -41.41^\circ$$

$$\theta_V - \theta_{i_2} > 0 \Rightarrow \theta_V - \theta_{i_2} = 18.195^\circ$$

$$\begin{cases} \cos^{-1}(0.75) = -41.41^\circ \\ \cos^{-1}(0.95) = 18.195^\circ \end{cases}$$

Assume $\theta_V \neq 0$

$$\therefore \theta_{i_1} = 41.41^\circ$$

$$\theta_{i_2} = -18.195^\circ$$

$$\begin{aligned} I_1 &= I_1 L 41.41^\circ \\ &= 0.75 I_1 + 0.66 I_1 \end{aligned}$$

$$\begin{aligned} I_2 &= I_2 L -18.195^\circ \\ &= 0.95 I_2 + j 0.3125 I_2 \end{aligned}$$

$$S_1 = P_1 - jQ_1$$

$$= 2000 - j \left(\frac{8000}{3} \right) \sin(\cos^{-1}(0.75))$$

$$\boxed{\therefore S_1 = 2000 - j(1763.83) \text{ VA}}$$

$$S_2 = P_2 + jQ_2$$

$$= 4000 + j \left(\frac{80000}{19} \right) \sin(\cos^{-1}(0.95))$$

$$\boxed{\therefore S_2 = 4000 + j(1314.74) \text{ VA}}$$

$$\therefore S_{\text{source}} = S_1 + S_2$$

$$= 6000 + j(-449.1) \text{ VA}$$

$$\boxed{\therefore S = 6000 - j(+449.1) \text{ VA}}$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cos(\theta_v - \theta_i)$$

$$Q = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \sin(\theta_v - \theta_i)$$

$$\tan(\theta_v - \theta_i) = \frac{Q}{P}$$


$$\Rightarrow \tan(\theta_v - \theta_i) = \frac{-449.1}{6000}$$

$$\Rightarrow \tan(\theta_v - \theta_i) = -0.07485$$

$$\Rightarrow \theta_v - \theta_i = \tan^{-1}(-0.07485)$$

$$PF = \cos(\theta_v - \theta_i) = \cos(\tan^{-1}(-0.07485))$$

$$\boxed{\therefore PF = 0.9972}$$

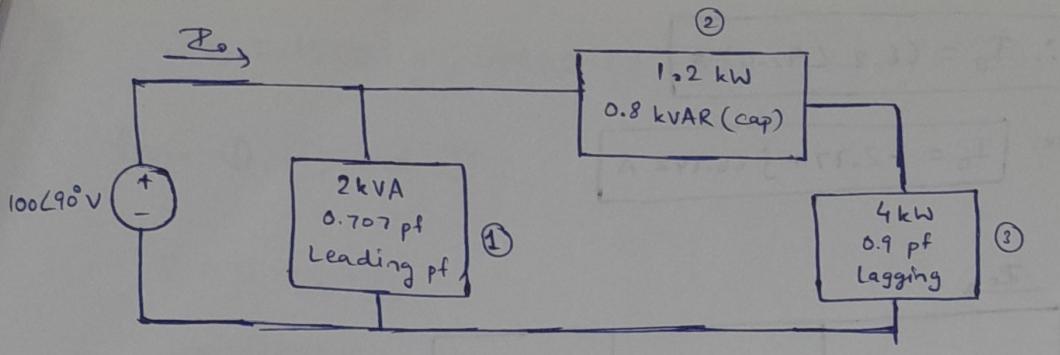

$$\text{Overall Complex Power } (S) = S_1 + S_2 + S_3$$

$$(i) S_2 = 1200 + j(-800) \text{ VA} - ② [\phi < 0 \text{ for Capacitive Loads}]$$

$$(ii) S_1 = 2000 \angle \theta_v - \theta_i - ①$$

$$\cos(\theta_v - \theta_i) = 0.707$$

$$\Rightarrow \theta_v - \theta_i = 45^\circ$$

$$\text{But } \theta_v - \theta_i = -45^\circ [\text{As } \theta_v - \theta_i < 0 \text{ for Leading pf}]$$

$$\therefore S_1 = 2000 \angle -45^\circ \text{ VA}$$

$$= 1414.2 - j(1414.2) \text{ VA}$$

$$(iii) S_3 = 4000 + j\phi$$

$$\tan(\theta_v - \theta_i) = \frac{\phi}{P}$$

$$\cos(\theta_v - \theta_i) = 0.9$$

$$\Rightarrow \tan(\cos^{-1}(0.9)) = \frac{\phi}{4000}$$

$$\Rightarrow \phi = 4000 \times 0.484$$

$$\therefore \phi = 1937.288 \text{ VAR}$$

$$\therefore S_3 = 4000 + j1937.288 \text{ VA} - ③$$

$$S = S_1 + S_2 + S_3$$

$$\Rightarrow S = 6614.21 - j276.925 \text{ VA}$$

$$\therefore S = 6620 \angle -2.4^\circ \text{ VA}$$

← Overall Complex Power Supplied


$$S = V_{rms} \cdot I_{rms}^*$$

$$\Rightarrow I_0^* = \frac{S}{V} = \frac{6620 \angle -2.4^\circ}{100 \angle 90^\circ} = 66.2 \angle -92.4^\circ \text{ A}$$

$$\therefore I_0 = 66.2 \angle 92.4^\circ A$$

(OR) $I_0 = -2.77 + j 66.142 A$

15)

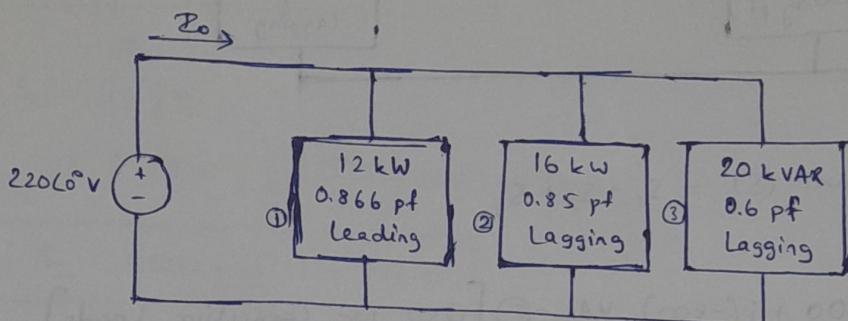

$$S = S_1 + S_2 + S_3$$

$$S = VI_0^* \Rightarrow \text{Then we can find } I_0$$

$$S_1 = 12000 + j\varnothing$$

($\varnothing < 0$ for Leading pf)

$$\tan(\vartheta_v - \vartheta_i) = \frac{\varnothing}{P} \quad \left[\because \vartheta_v - \vartheta_i < 0 \text{ for leading pf} \right]$$

$$\Rightarrow \tan(\cos^{-1}(0.866)) = \frac{\varnothing}{12000}$$

$$\Rightarrow \varnothing = 12000 \times (0.577)$$

$$\therefore \varnothing = -6928.2 \text{ VAR}$$

~~∴~~ $\boxed{\varnothing = -6928.2 \text{ VAR}}$

$$\therefore S_1 = 12000 - j(6928.2) \text{ VA} \quad -①$$

$$S_2 = 16000 + j(16000 \times \tan(\cos^{-1}(0.85)))$$

$$\therefore S_2 = 16000 + j(9915.91) \text{ VA} \quad -② \quad (\varnothing > 0 \text{ for lagging pf})$$

$$S_3 = P + j 20000$$

$$\tan(\vartheta_v - \vartheta_i) = \frac{\varnothing}{P}$$

$$\Rightarrow \tan(\cos^{-1}(0.6)) = \frac{20000}{P}$$

$$\Rightarrow P = \frac{20000}{4/3} = 15000 \text{ W}$$

$$\therefore S_3 = 15000 + j20000 \text{ VA} \quad \text{---(3)}$$

from ①, ② and ③ :

$$S = S_1 + S_2 + S_3$$

~~12000 + 16000 + 15000~~

$$\Rightarrow S = (12000 + 16000 + 15000) + j(-6928.2 + 9915.91 + 20000) \text{ VA}$$
$$= 43000 + j22987.71 \text{ VA}$$

$$\therefore S = 43 + j22987.71 \text{ kVA}$$

$$\therefore S = 43 + j23 \text{ kVA}$$

$$S = V_{rms} \cdot I_{rms}^*$$

$$\Rightarrow I_{rms}^* = \frac{S}{V_{rms}} = \frac{48758.944 \angle 28.13^\circ}{220 \angle 0^\circ} \text{ A}$$

$$\Rightarrow I_0^* = 221.63 \angle 28.13^\circ \text{ A}$$

$$\therefore I_0 = 221.63 \angle -28.13^\circ \text{ A}$$

(OR)

$$I_0 = 195.45 - j104.5 \text{ A}$$