

CEP181056

**Indian Institute of Information Technology, Design and
Manufacturing, Kar cheepuram**
End Semester Examination
Digital and Analogue Circuits Design (COM206T)



Total Marks: 50

Date: 19/11/2019


Time: 3 hours

1. A flip-flop has a 3ns delay from the time the clock edge occurs to the time the output is complemented. What is the maximum delay in a 10-bit binary ripple counter that uses these flip-flops? What is the maximum frequency at which the counter can operate reliably? (3)
2. An M-N flip-flop works as follows:
If MN = 00, the next state of the flip-flop is 0.
If MN = 01, the next state of the flip-flop is the same as the present state.
If MN = 10, the next state of the flip-flop is the complement of the present state.
If MN = 11, the next state of the flip-flop is 1.
(a) Complete the following table (use don't-cares when possible):

	Present State	Next State	M	N
00 / 01 no change / reset	0	0	0	X
11 / 10 set / toggle	0	1	1	X
00 / 10 reset / toggle	1	0	X	0
01 / 11 no change / set	1	1	X	1

- (b) Using this table and Karnaugh maps, derive and minimize the input equations for a counter composed of three M-N flip-flops which counts in the following sequence: ABC = 000, 001, 011, 111, 101, 100, (repeat) 000, ... (7)
- (c) Draw a logic diagram for the above mentioned counter. (7)

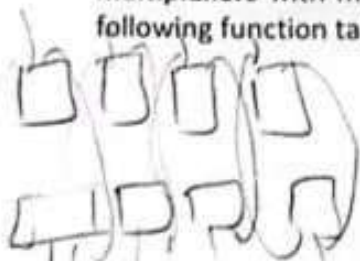4. Draw the logic (Block) diagram of a four-bit register with four D flip-flops and four 4 × 1 multiplexers with mode selection inputs s_1 and s_0 . The register operates according to the following function table. (5)




s_1	s_0	Register Operation
0	0	No Change
0	1	Compliment the four outputs
1	0	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data.

5. Show how two 2²-to-1 multiplexers (with no added gates) could be connected to form a 3-to-1 MUX (Block diagram). Input selection should be as follows: (3)

If AB = 00, select I_0

If AB = 01, select I_1

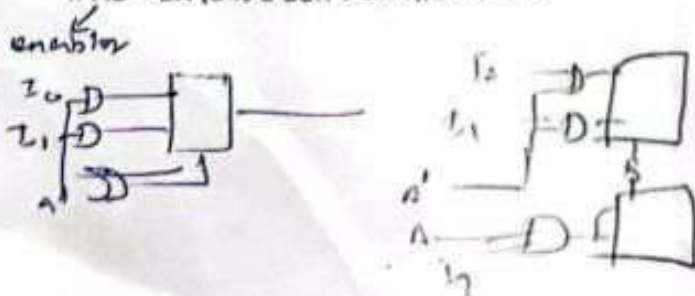If AB = 1X (B is a don't-care), select I_2 .



6. Find the complement of $F = wx + yz$; then show that $FF' = 0$ and $F + F' = 1$. (2)
7. Realize a full adder using a 3-to-8 line decoder and two NOR gates. (2)
8. Design a combinational circuit that generates the 9's complement of a BCD digit. (5)
9. Perform subtraction on the given unsigned binary numbers using the 2's complement of the subtrahend. Where the result should be negative, find its 2's complement and affix a minus sign.
 (a) $10011 - 10001$
 (b) $100010 - 100011$ (4)
10. What is the largest binary number that can be expressed with 14 bits? What are the equivalent decimal and hexadecimal numbers? (2)
11. The state of a 12-bit register is 100010010111 . What is its content, if it represents
 (a) Three decimal digits in BCD?
 (b) Three decimal digits in the excess-3 code? (2)
12. A sequential circuit has three flip-flops A, B, C; one input x -in; and one output y -out. The state diagram is shown in Fig.1. The circuit is to be designed by treating the in the design. (5)
13. Design a sequence detector that detects three or more consecutive 1's in a string of bits coming through the input lines. (5)
14. Represent the unsigned decimal numbers 842 and 537 in BCD, and form their sum. (2)
15. Draw a circuit for four bit Binary to Grey code conversion. (3)

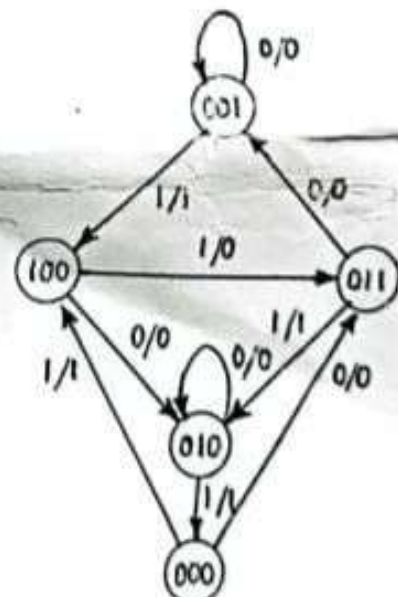


Fig. 1