



Electrical Circuits for Engineers (EC1000)

Lecture-9 (b) AC circuits

Sinusoidal Steady State Analysis (Ch. 10)
Network Theorems



Steps to Analyse AC circuits


1. Transform the circuit to the phasor or frequency domain.
2. Solve the problem using circuit techniques (nodal, Mesh, theorem etc.,)
3. Transform the resulting phasor to the time domain



3. Superposition Theorem

Since ac circuits are linear, superposition theorem applies to ac circuits.

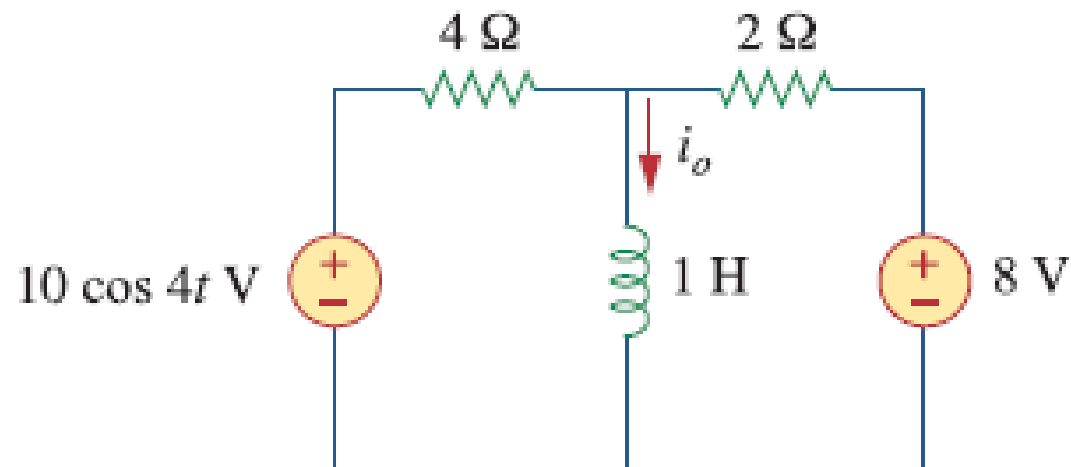1. Determine the current I_o in the circuit of figure below using Super Position Theorem.






3. Superposition Theorem

Let $I_o = I_{o1} + I_{o2}$, where I_{o1} is due to the dc source and I_{o2} is due to the ac source. For I_{o1} , consider the circuit in Fig. (a).


Clearly,

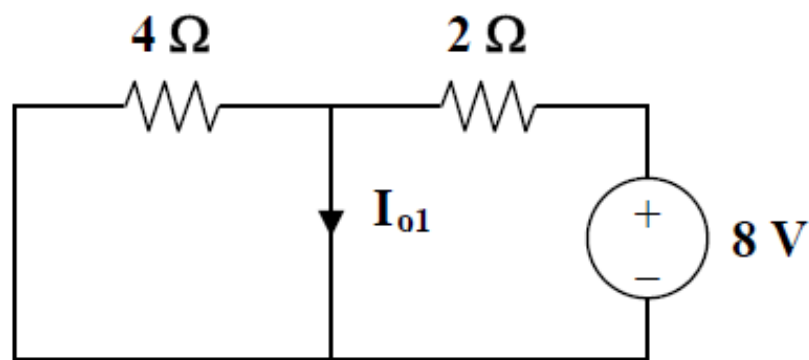

(a)

$$I_{o1} = 8/2 = 4 \text{ A}$$

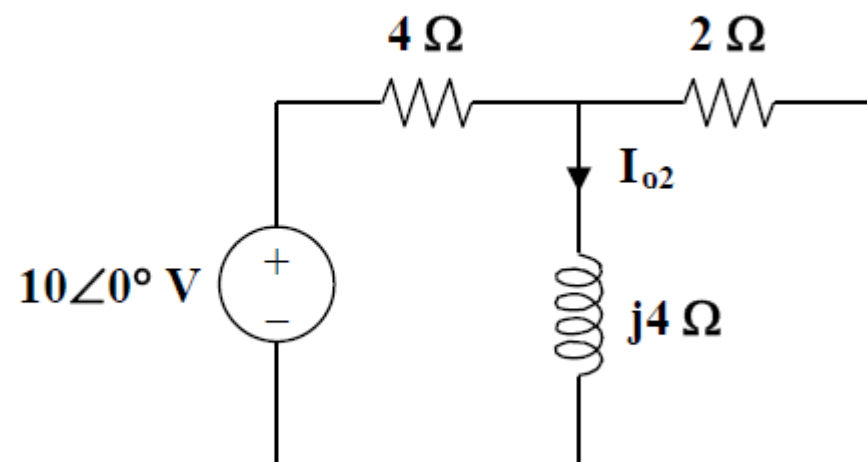
For I_{o2} , consider the circuit in Fig. (b).



(b)



3. Superposition Theorem

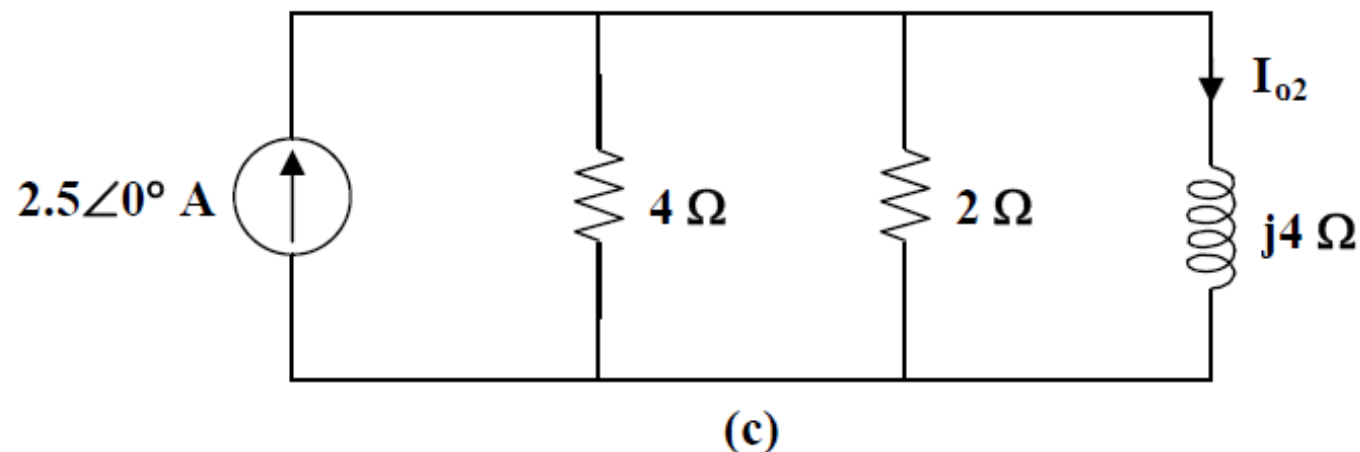

By the current division principle,

$$\mathbf{I}_{o2} = \frac{4/3}{4/3 + j4} (2.5 \angle 0^\circ)$$

$$\mathbf{I}_{o2} = 0.25 - j0.75 = 0.79 \angle -71.56^\circ$$

Thus,

$$I_{o2} = 0.79 \cos(4t - 71.56^\circ) \text{ A}$$

Therefore,


$$\mathbf{I}_o = \mathbf{I}_{o1} + \mathbf{I}_{o2} = [4 + 0.79 \cos(4t - 71.56^\circ)] \text{ A}$$



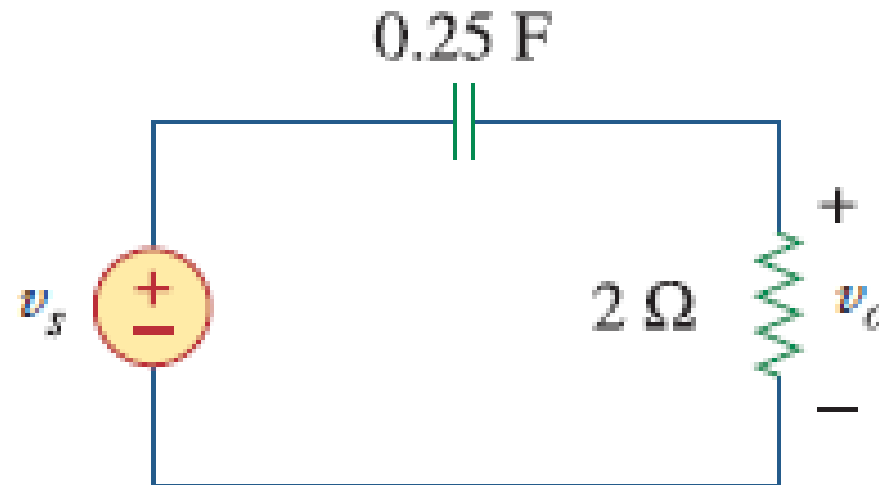Example Problem

Find v_o for the circuit in Fig


$$v_s = 6 \cos 2t + 4 \sin 4t \text{ V.}$$



We apply superposition principle. We let


$$v_o = v_1 + v_2$$

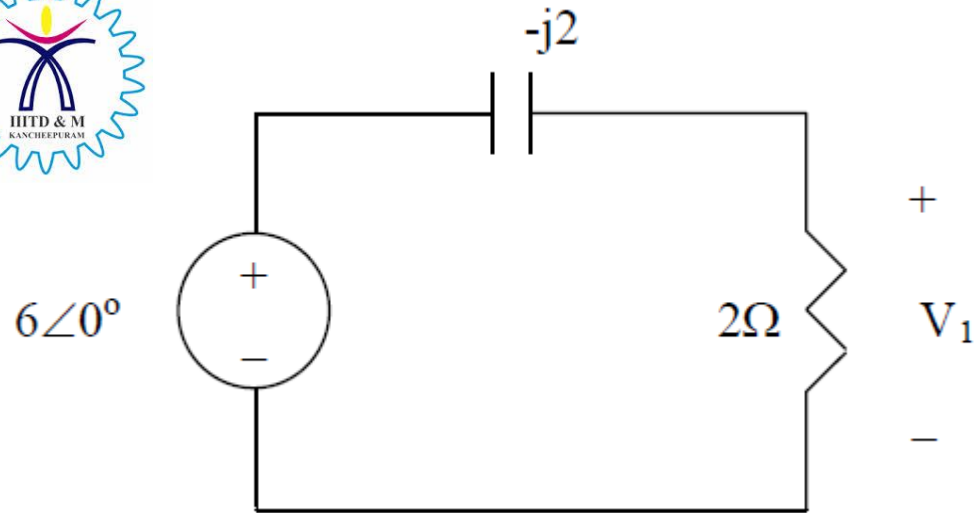where v_1 and v_2 are due to the sources $6\cos 2t$ and $4\sin 4t$ respectively.



$$V_1 = \frac{2}{2-j2} V (6) = 3+j3 = 4.243\angle 45^\circ$$
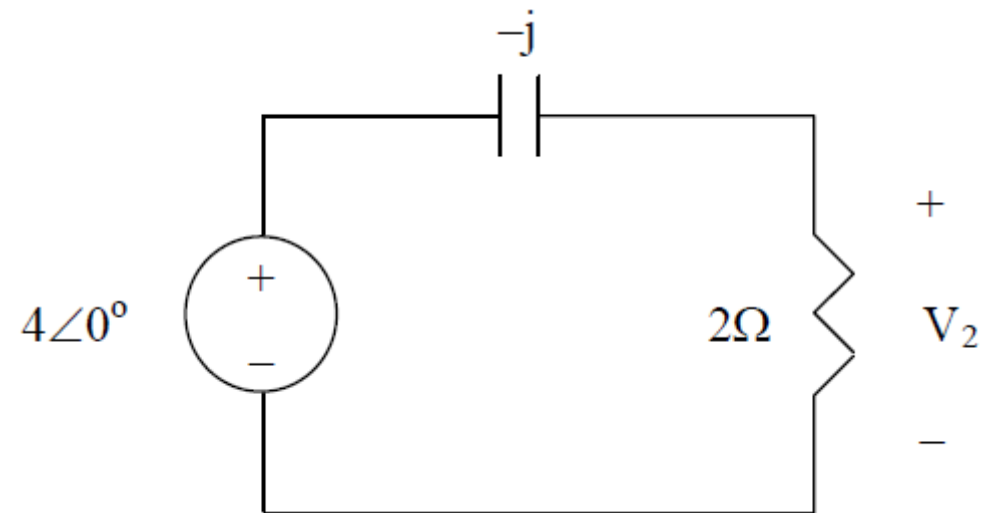
$$v_1(t) = 4.243\cos(2t+45^\circ) \text{ volts.}$$



$$V_2 = \frac{2}{2-j} (4) = 3.2 + j11.6 = 3.578\angle 26.56^\circ$$


$$v_2(t) = 3.578\sin(4t+25.56^\circ) \text{ volts.}$$

$$v_o = [4.243\cos(2t+45^\circ) + 3.578\sin(4t+25.56^\circ)] \text{ volts.}$$



Practice Problem

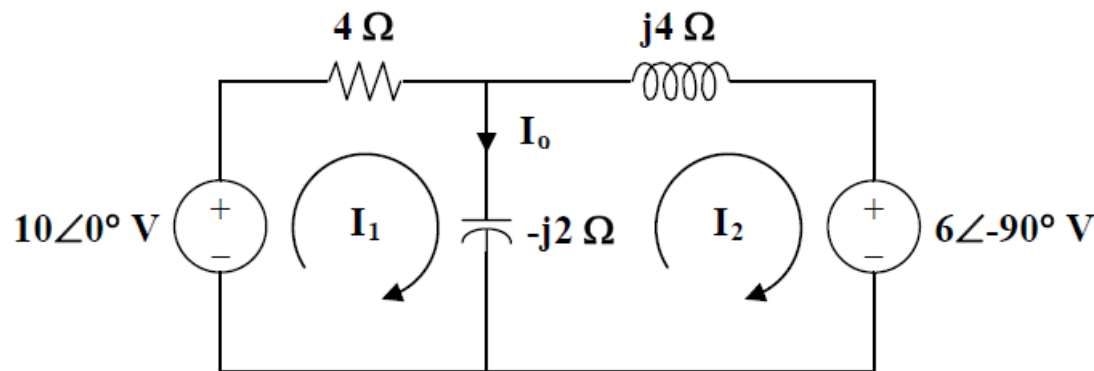
1. Find I_o in the circuit of figure below using Super Position Theorem




$$i_o(t) = 1.4142 \cos(2t + 45^\circ) \text{ A}$$



4. Thevenin & Norton Equivalent Circuit

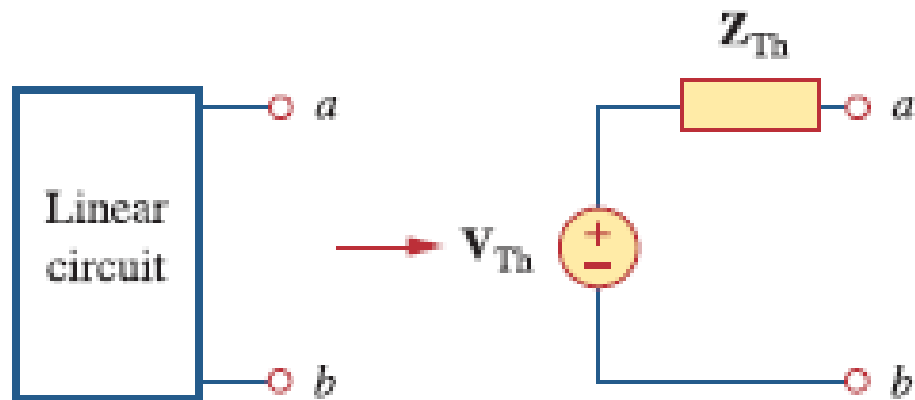

Thevenin Equivalent Circuit

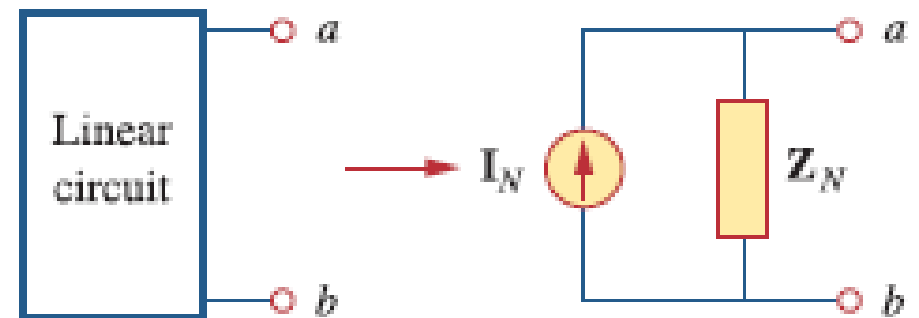


Norton Equivalent Circuit




Example Problem

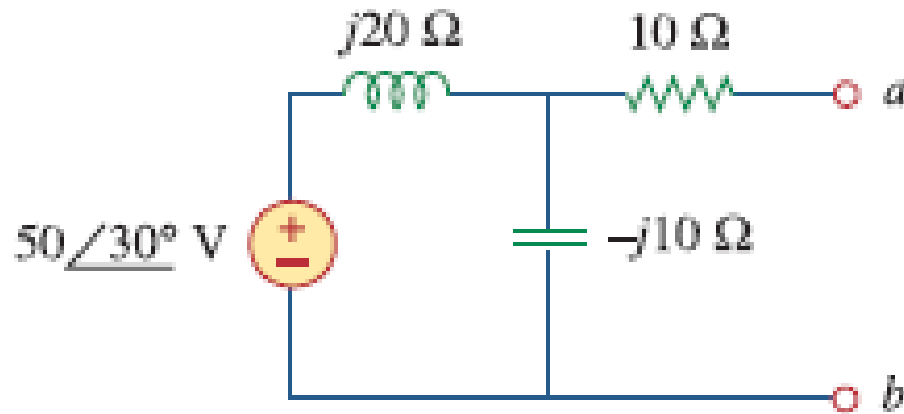1. Find Thevenin and Norton Equivalent Circuits at the terminals a-b




Solution:

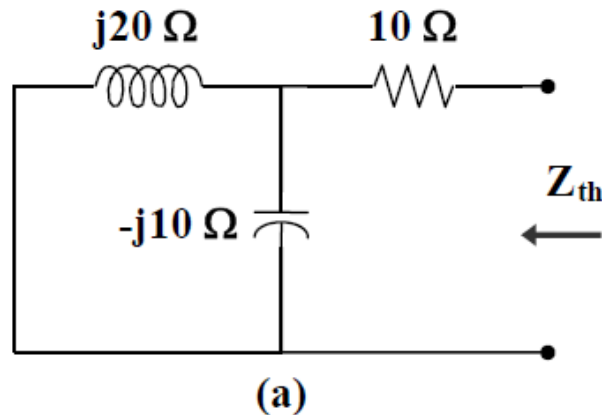(a) To find Z_{th} , consider the circuit in Fig. (a).



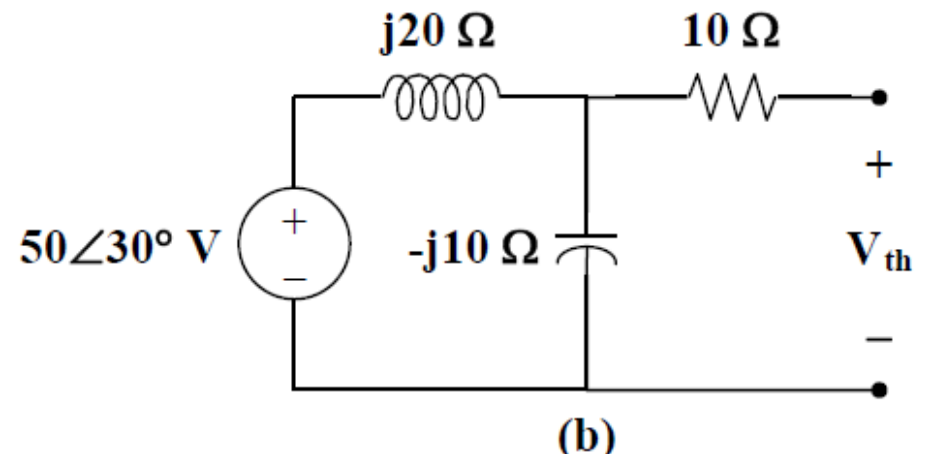To find V_{th} , consider the circuit in Fig. (b).



$$\begin{aligned} Z_N = Z_{th} &= 10 + j20 \parallel (-j10) = 10 + \frac{(j20)(-j10)}{j20 - j10} \\ &= 10 - j20 = 22.36 \angle -63.43^\circ \Omega \end{aligned}$$


$$V_{th} = \frac{-j10}{j20 - j10} (50 \angle 30^\circ) = -50 \angle 30^\circ \text{ V}$$

$$I_N = \frac{V_{th}}{Z_{th}} = \frac{-50 \angle 30^\circ}{22.36 \angle -63.43^\circ} = 2.236 \angle 273.4^\circ \text{ A}$$





Example Problem

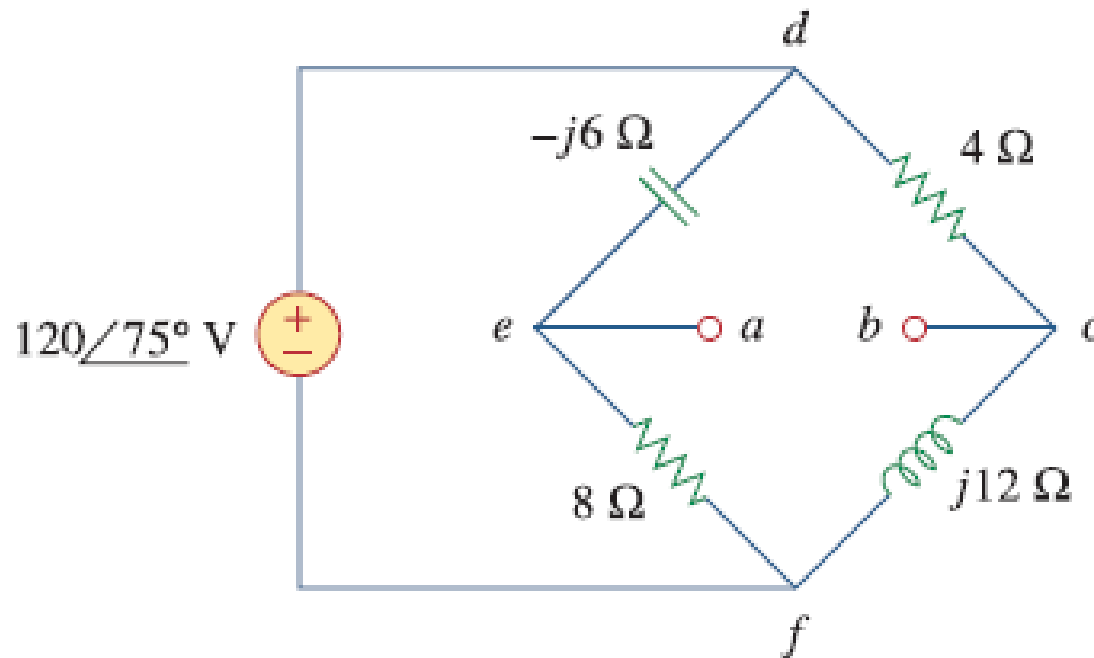2. Obtain the Thevenin Equivalent at terminals a-b for the below circuit



Solution

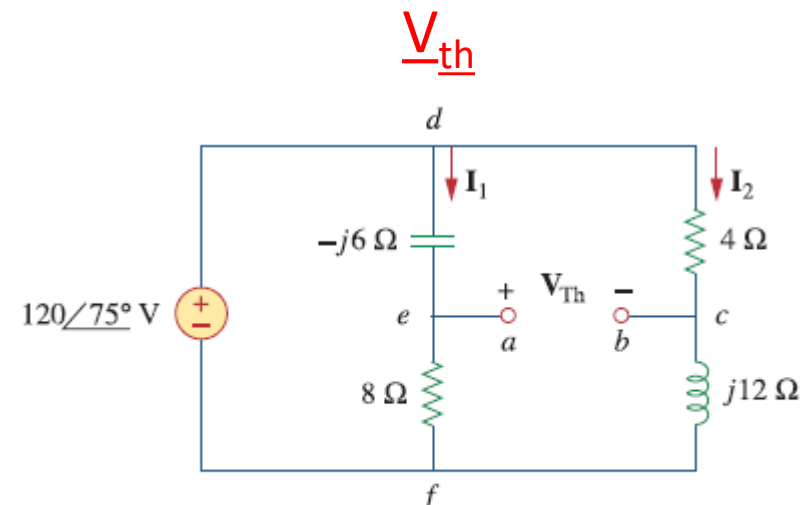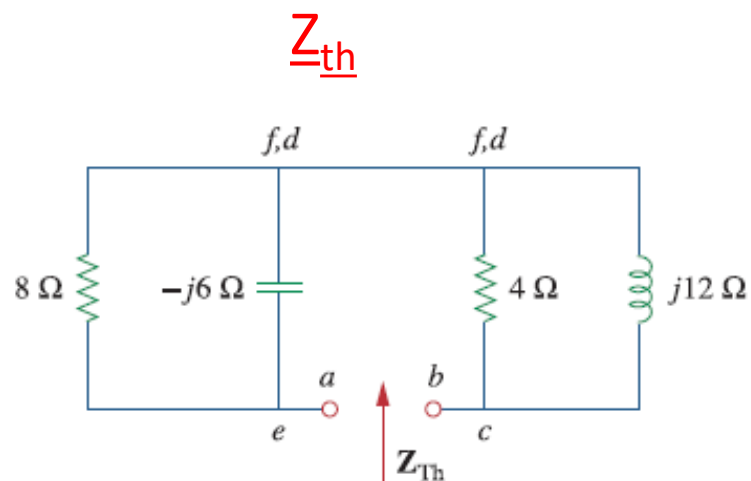



The Thevenin impedance is the series combination of \mathbf{Z}_1 and \mathbf{Z}_2 ; that is,

$$\mathbf{Z}_{\text{Th}} = \mathbf{Z}_1 + \mathbf{Z}_2 = 6.48 - j2.64 \Omega$$


To find \mathbf{V}_{Th} , consider the circuit in Fig. 10.23(b). Currents \mathbf{I}_1 and \mathbf{I}_2 are obtained as

$$\mathbf{I}_1 = \frac{120 \angle 75^\circ}{8 - j6} \text{ A}, \quad \mathbf{I}_2 = \frac{120 \angle 75^\circ}{4 + j12} \text{ A}$$

Applying KVL around loop $bcdeab$ in Fig. 10.23(b) gives

$$\mathbf{V}_{\text{Th}} - 4\mathbf{I}_2 + (-j6)\mathbf{I}_1 = 0$$

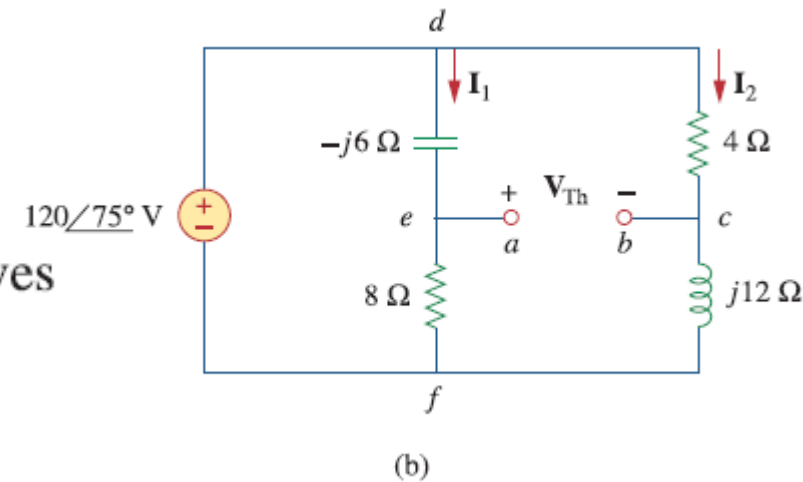
$$\begin{aligned} \mathbf{V}_{\text{Th}} = 4\mathbf{I}_2 + j6\mathbf{I}_1 &= \frac{480 \angle 75^\circ}{4 + j12} + \frac{720 \angle 75^\circ + 90^\circ}{8 - j6} \\ &= 37.95 \angle 3.43^\circ + 72 \angle 201.87^\circ \\ &= -28.936 - j24.55 = 37.95 \angle 220.31^\circ \text{ V} \end{aligned}$$





Practice Problem

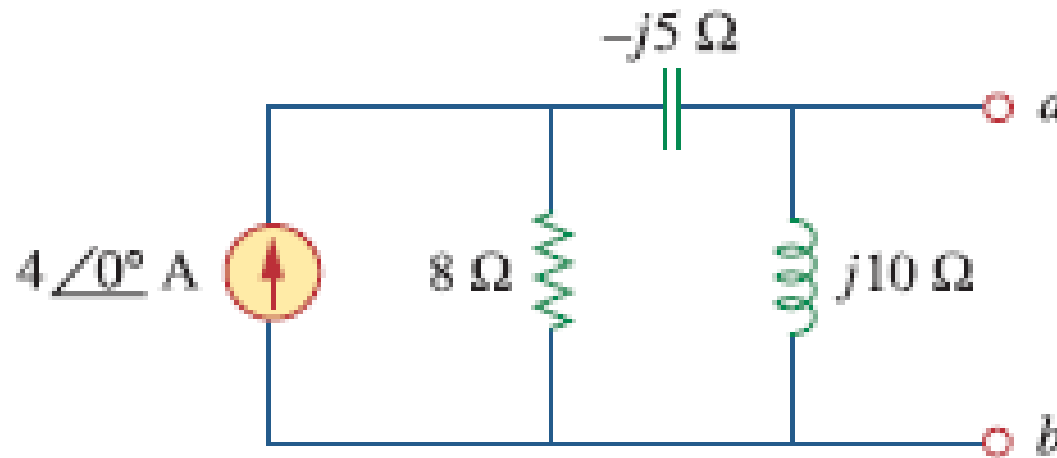1. Obtain the Thevenin Equivalent at terminals a-b for the below circuit



$$\mathbf{Z_N = Z_{th} = j10 \parallel (8 - j5) = \frac{(j10)(8 - j5)}{j10 + 8 - j5} = 10\angle 26^\circ\ \Omega}$$


$$\mathbf{V_{th} = j10\mathbf{I_o} = \frac{j320}{8 + j5} = 33.92\angle 58^\circ\ \text{V}}$$

$$\mathbf{I_N = \frac{V_{th}}{Z_{th}} = \frac{33.92\angle 58^\circ}{10\angle 26^\circ} = 3.392\angle 32^\circ\ \text{A}}$$



Practice Problem

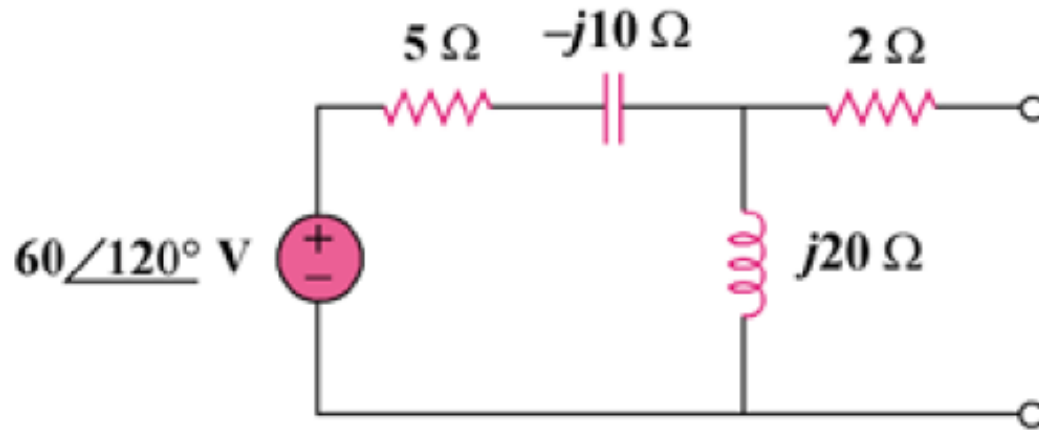2. Find the Thevenin and Norton equivalent circuits for the circuit shown in



$$\mathbf{Z_{th}} = 21.633 \angle -33.7^\circ \Omega$$


$$\begin{aligned} \mathbf{V_{th}} &= \frac{j20}{5 - j10 + j20} (60 \angle 120^\circ) = \frac{j4}{1 + j2} (60 \angle 120^\circ) \\ &= 107.3 \angle 146.56^\circ \text{ V} \end{aligned}$$

$$\mathbf{I_N} = \frac{\mathbf{V_{th}}}{\mathbf{Z_{th}}} = \frac{107.3 \angle 146.56^\circ}{21.633 \angle -33.7^\circ} = 4.961 \angle -179.7^\circ \text{ A}$$



Practice Problems

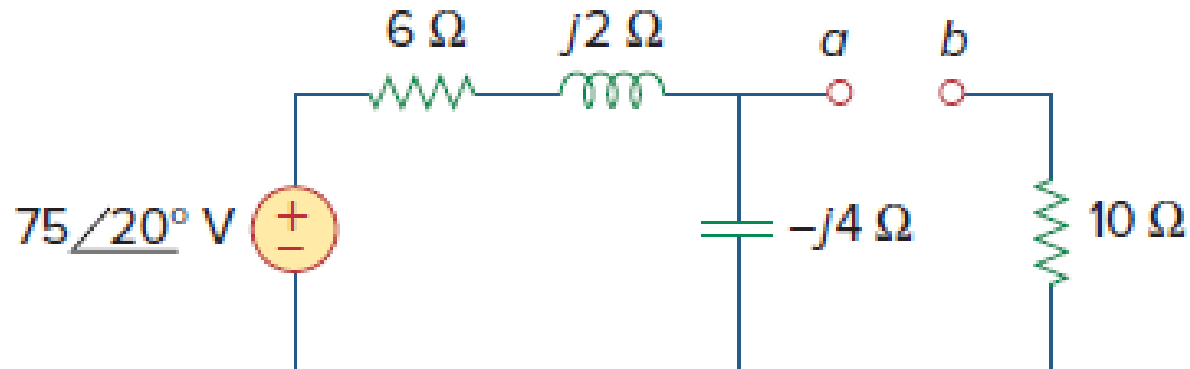1. Find the Thevenin's equivalent circuit for the circuit shown below.



Answer: $Z_{\text{Th}} = 12.4 - j3.2 \Omega$, $V_{\text{Th}} = 47.43 \angle -51.57^\circ \text{ V}$.

2. Find the Norton equivalent circuits for the circuit shown below.

