



# **Electrical Circuits for Engineers (EC1000)**


## **Lecture -4(C) Max. Power Transfer Theorem (Chapter 4)**




# 3. Maximum Power Transfer Theorem
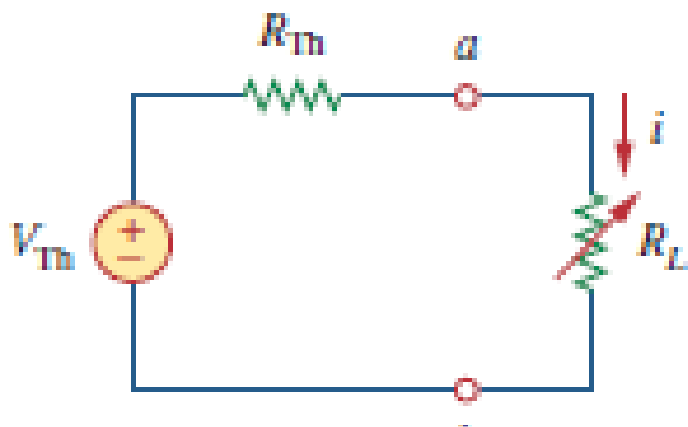
## Maximum Power Transfer Theorem

- In some applications it is required to transfer maximum power to the load.
- Maximum power is transferred to the load when the load resistance equals the Thevenin resistance  $R_L = R_{Th}$



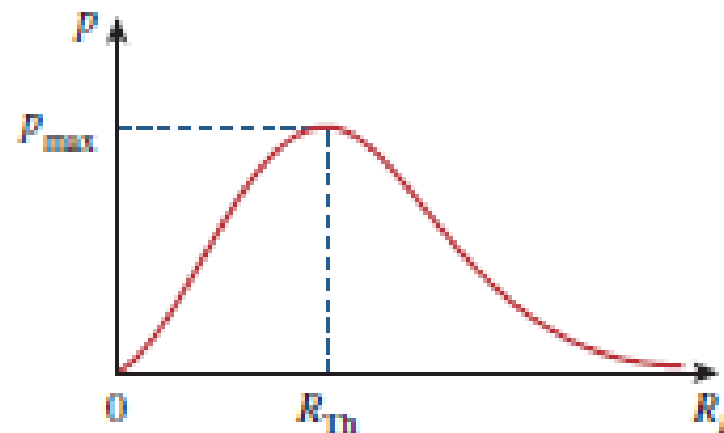
$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$





### 3. Maximum Power Transfer Theorem

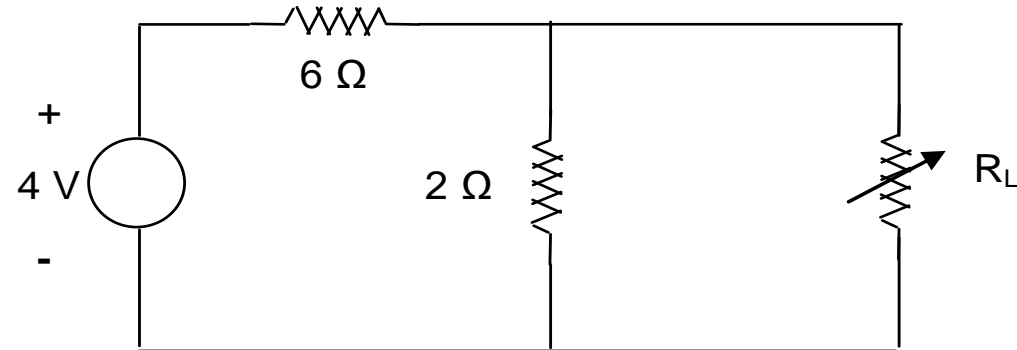
Example 1 Consider the circuit shown below. Determine the value of  $R_L$  when it is dissipating maximum power. Also find the value of maximum power dissipated.



Solution:

As a first step, Thevenin's equivalent across the load resistor is obtained.
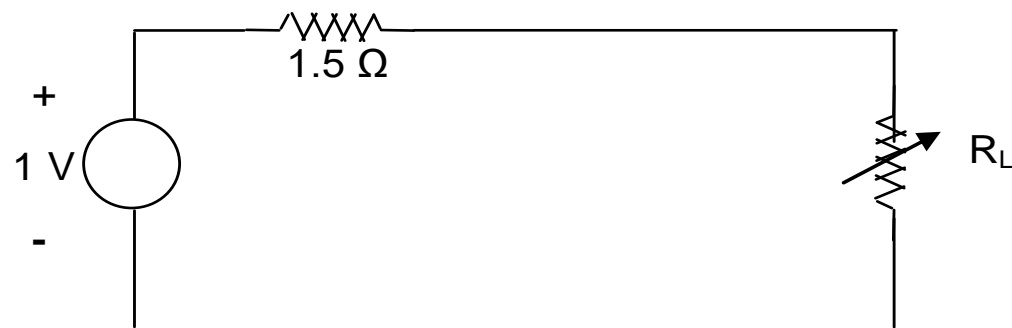
$$V_{Th} = \frac{2}{2 + 6} \times 4 = 1 \text{ V}; \quad R_{Th} = 6 \parallel 2 = 1.5 \Omega \quad \text{Resulting circuit is shown.}$$



For  $P_L$  to be maximum,  $R_L = 1.5 \Omega$ ; Then circuit current  $= 1/3 = 0.3333 \text{ A}$


Maximum power dissipated  $P_{max} = 0.3333^2 \times 1.5 = 0.16667 \text{ W}$




# Example Problems

**Example:2:** The variable resistor  $R_L$  in given figure is adjusted until it absorbs the maximum power from the circuit.

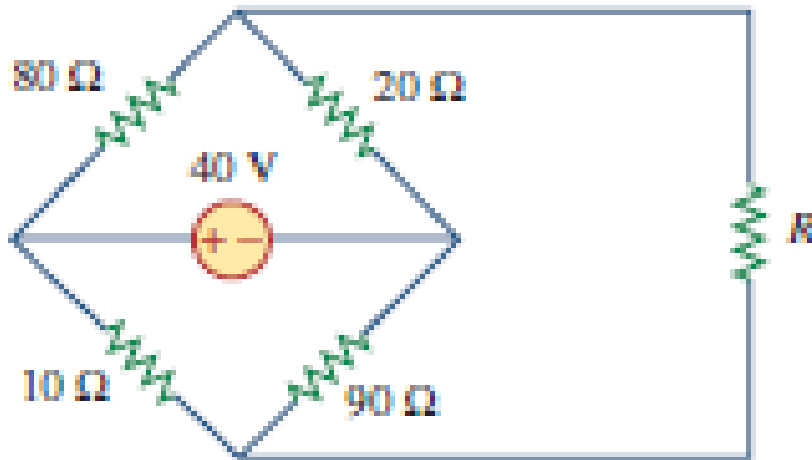- (a) Calculate the value of  $R$  for maximum power.
- (b) Determine the maximum power absorbed by  $R$ .




**To find  $R_{th}$**

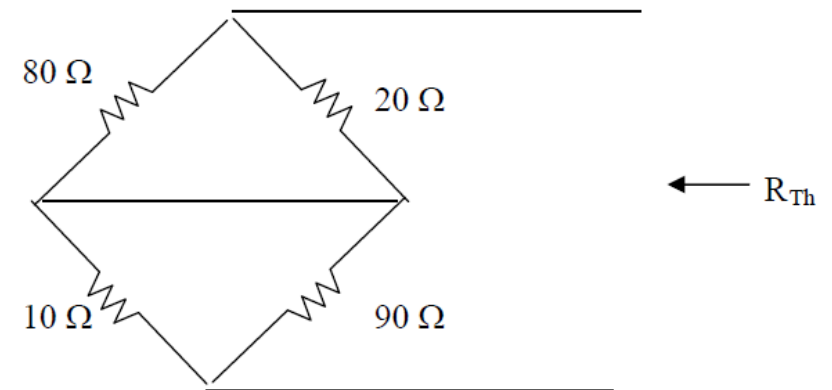

$$R_{Th} = 20 // 80 + 90 // 10 = 16 + 9 = 25 \Omega$$

Contd.,

To find  $V_{th}$

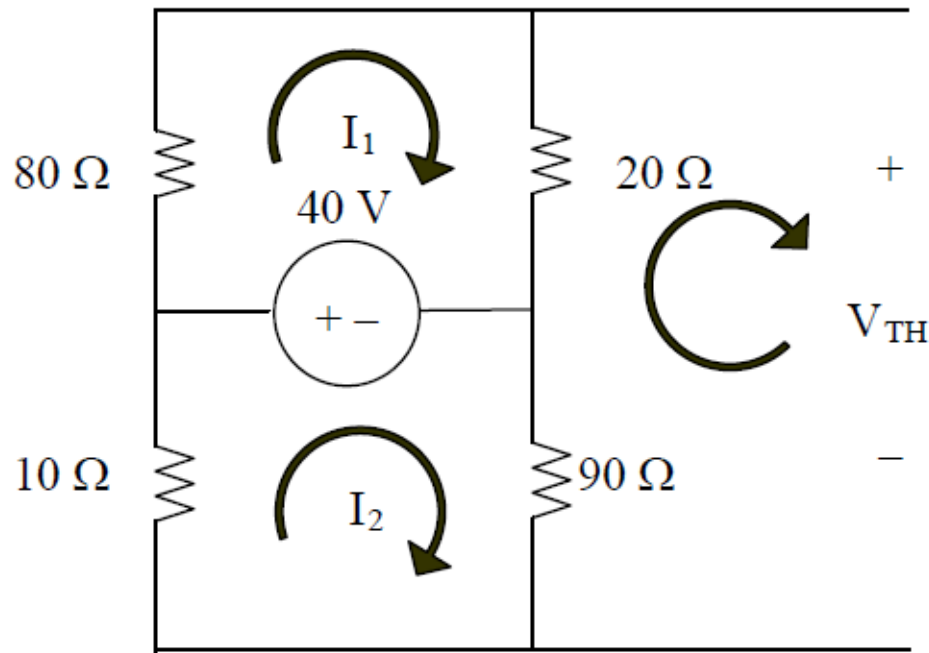

$$(80 + 20)i_1 - 40 = 0 \quad \longrightarrow \quad i_1 = 0.4$$

$$(10 + 90)i_2 + 40 = 0 \quad \longrightarrow \quad i_2 = -0.4$$

$$-90i_2 - 20i_1 + V_{th} = 0 \quad \longrightarrow \quad V_{th} = -28 \text{ V}$$


$$(a) \quad R = R_{th} = \mathbf{25 \, \Omega}$$

$$(b) \quad P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(28)^2}{100} = \underline{7.84 \text{ W}}$$




# Example Problems

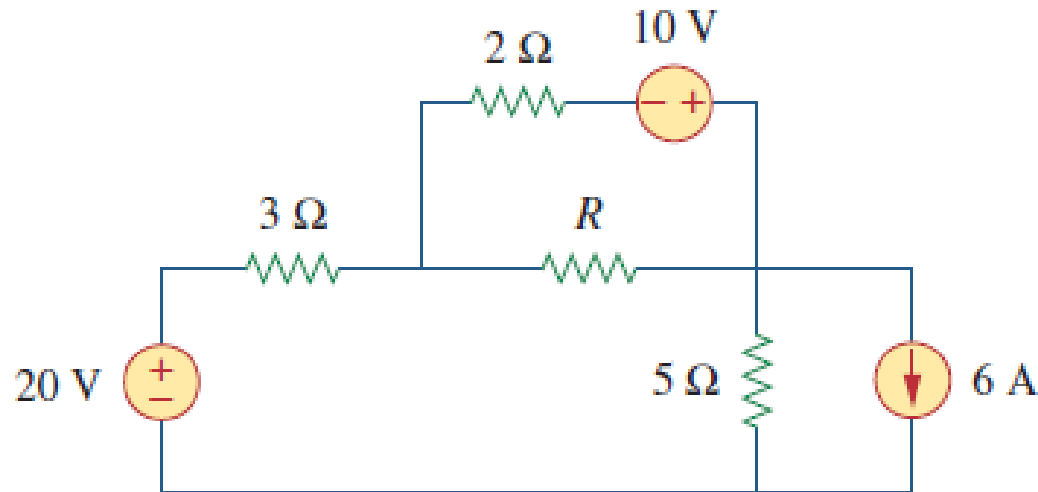
**Example:3:** Find the maximum power that can be delivered to the resistor  $R$  in the circuit of Figure below.



**To find  $R_{th}$**

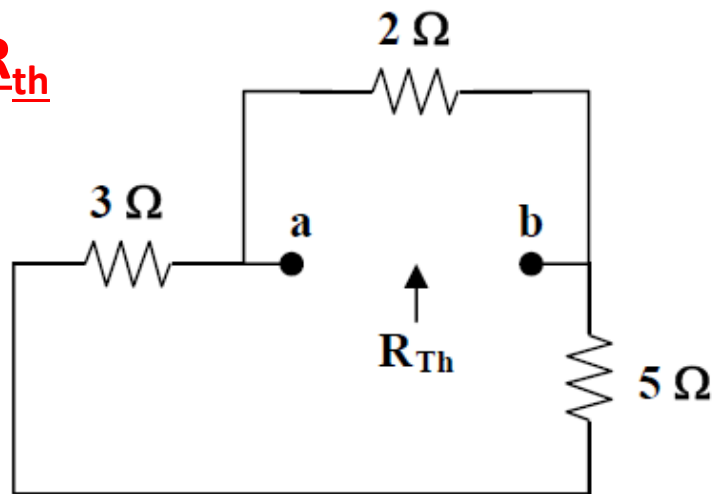

**To find  $V_{th}$**

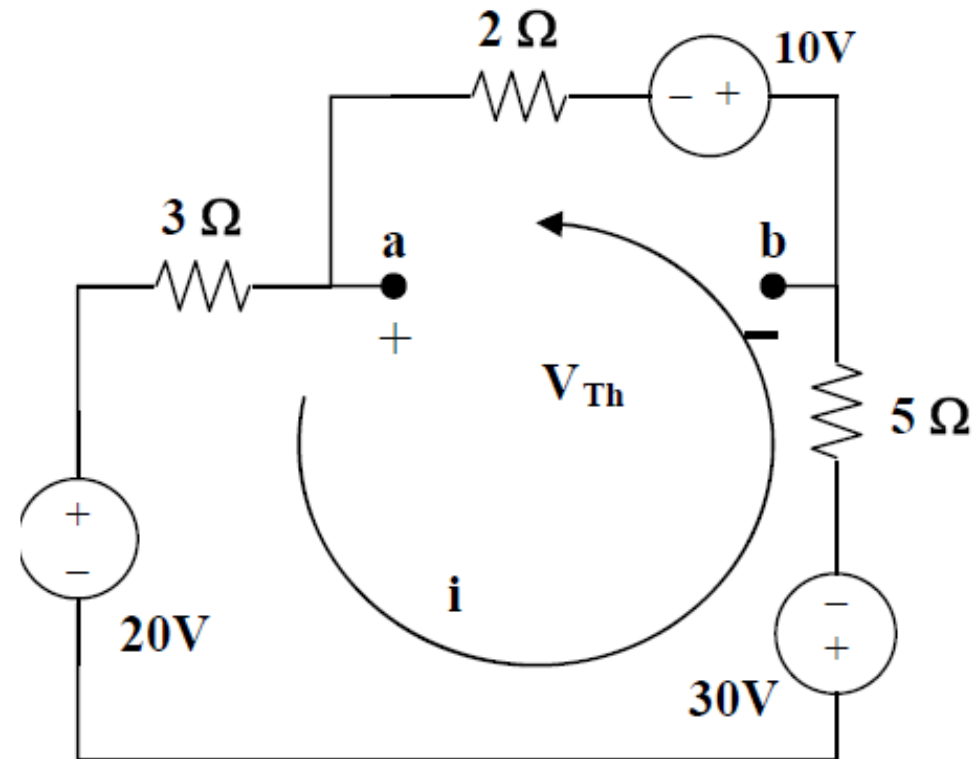

$$10i + 30 + 20 + 10 = 0, \text{ or } i = -6$$

$$V_{Th} + 10 + 2i = 0, \text{ or } V_{Th} = 2 \text{ V}$$

$$R_{Th} = 2 \parallel (3 + 5) = 2 \parallel 8 = 1.6 \text{ ohms} \quad p = V_{Th}^2 / (4R_{Th}) = (2)^2 / [4(1.6)] = 625 \text{ m watts}$$




# Practical Problems

1. (a) For the circuit in Figure, obtain the Thevenin equivalent at terminals a-b

(b) Calculate the current in  $R_L = 10 \text{ Ohm}$


(c) Find  $R_L$  for maximum power deliverable.

(d) Determine that maximum power.

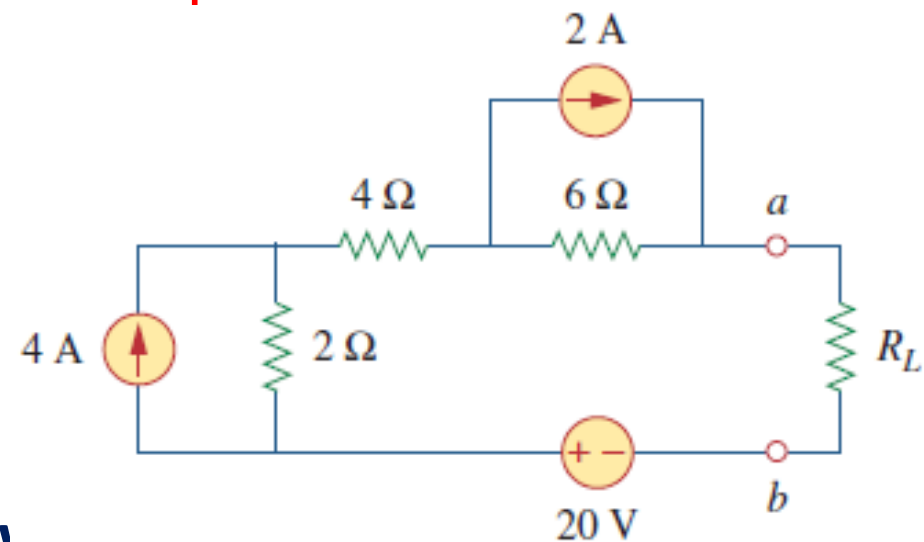

**Ans: 12 Ohm, 40 V, 33.33 V.**

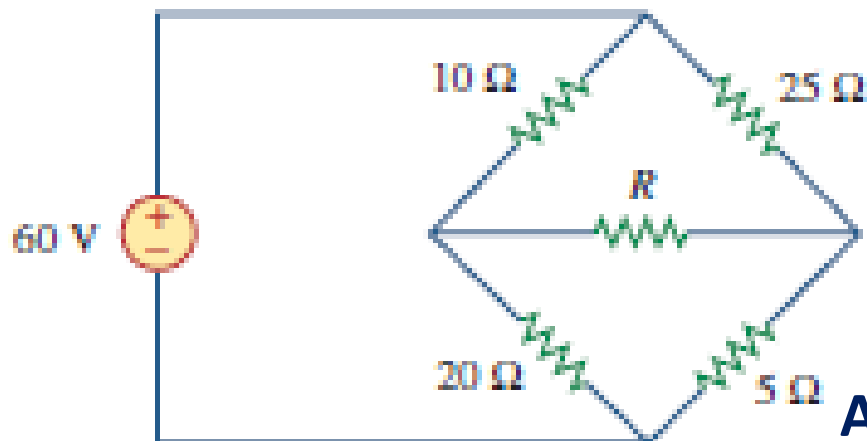2. Determine the maximum power that can be delivered to the variable resistor R in the circuit.



**Ans: 10.83 Ohm, 20.77 W**