



# **Electrical Circuits for Engineers (EC1000)**

## **Lecture-10 AC Power Analysis (Chapter 11)**



# AC Power Analysis

- 11.1 Instantaneous and Average Power
- 11.2 Maximum Average Power Transfer
- 11.3 Effective or RMS Value
- 11.4 Apparent Power and Power Factor
- 11.5 Complex Power





# 11.1 Instantaneous and Average Power (1)

The instantaneous power,  $p(t)$

We can also think of the instantaneous power as the power absorbed by the element at a specific instant of time. Instantaneous quantities are denoted by lowercase letters.
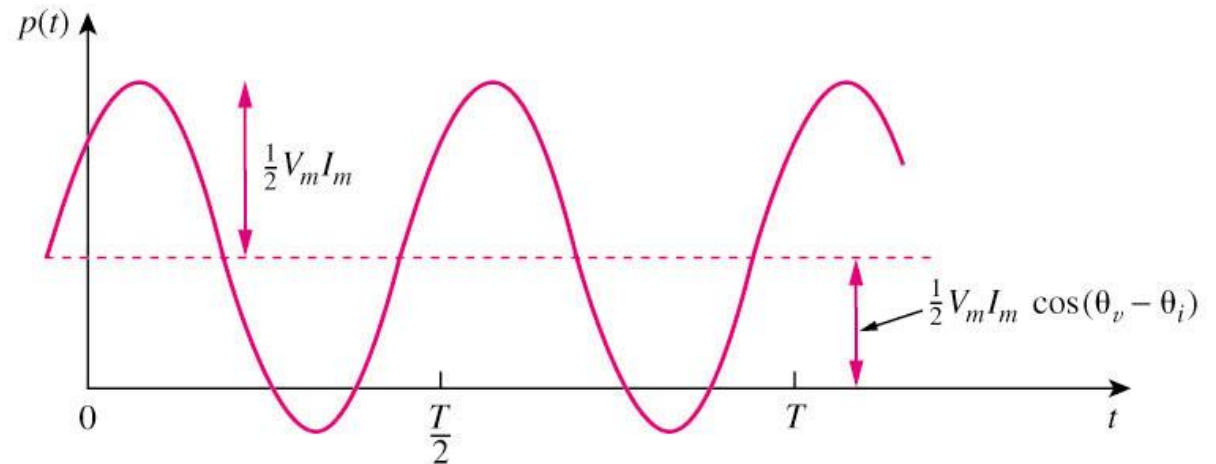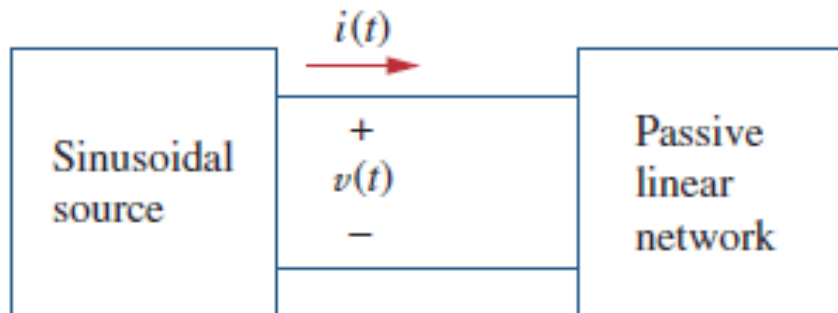
$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$
$$= \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\text{Constant power}} + \underbrace{\frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)}_{\text{Sinusoidal power at } 2\omega t}$$




$p(t) > 0$ : power is absorbed by the circuit;  $p(t) < 0$ : power is absorbed by the source.


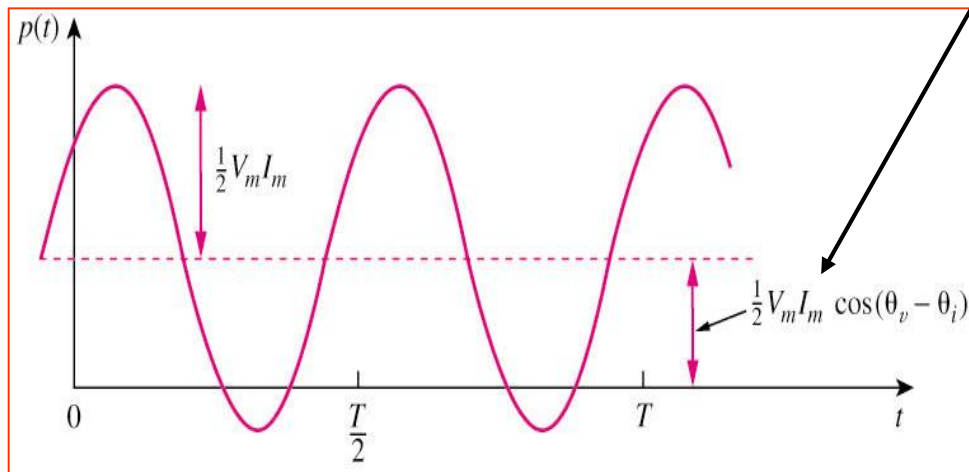
# 11.1 Instantaneous and Average Power (2)

The average power,  $P$ , is the average of the instantaneous power over one period.

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



1.  $P$  is not time dependent.
2. When  $\theta_v = \theta_i$ , it is a purely resistive load case.
3. When  $\theta_v - \theta_i = \pm 90^\circ$ , it is a purely reactive load case.
4.  $P = 0$  means that the circuit absorbs no average power.



# 11.1 Instantaneous and Average Power (3)

**Example 1** Calculate the instantaneous power and average power absorbed by a passive linear network if:

$$\begin{aligned} V(t) &= 120 \cos(377t + 45^\circ) \\ i(t) &= 10 \cos(377t - 10^\circ) \end{aligned}$$

**Solution:**

The instantaneous power is given by

$$p = vi = 1200 \cos(377t + 45^\circ) \cos(377t - 10^\circ)$$

Applying the trigonometric identity

$$\cos A \cos B = \frac{1}{2} [\cos(A + B) + \cos(A - B)]$$

$$p = 600 [\cos(754t + 35^\circ) + \cos 55^\circ]$$

The average power is

$$p(t) = 344.2 + 600 \cos(754t + 35^\circ) \text{ W}$$

$$\begin{aligned} P &= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} 120(10) \cos[45^\circ - (-10^\circ)] \\ &= 600 \cos 55^\circ = 344.2 \text{ W} \end{aligned}$$

which is the constant part of  $p(t)$  above.



## 11.1 Instantaneous and Average Power (4)

2. Calculate the instantaneous power and average power absorbed by a passive linear network if:

$$v(t) = 330 \cos(10t + 20^\circ) \text{ V} \quad \text{and} \quad i(t) = 33 \sin(10t + 60^\circ) \text{ A}$$

**Answer:**  $3.5 + 5.445 \cos(20t - 10^\circ) \text{ kW}$ ,  $3.5 \text{ kW}$ .



## 11.1 Instantaneous and Average Power (4)

Example 3. Find the average power delivered to the impedance  $Z=30-j70\Omega$  when a voltage  $V=120\text{ V}$  is applied across it.

**Solution:**

The current through the impedance is

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{120\angle 0^\circ}{30 - j70} = \frac{120\angle 0^\circ}{76.16\angle -66.8^\circ} = 1.576\angle 66.8^\circ \text{ A}$$

The average power is

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} (120)(1.576) \cos(0 - 66.8^\circ) = 37.24 \text{ W}$$

**Example 4.** A current  $\mathbf{I} = 33\angle 30^\circ \text{ A}$  flows through an impedance  $\mathbf{Z} = 40\angle -22^\circ \Omega$ . Find the average power delivered to the impedance.


**Answer:** 20.19 kW.



# 11.1 Instantaneous and Average Power (4)
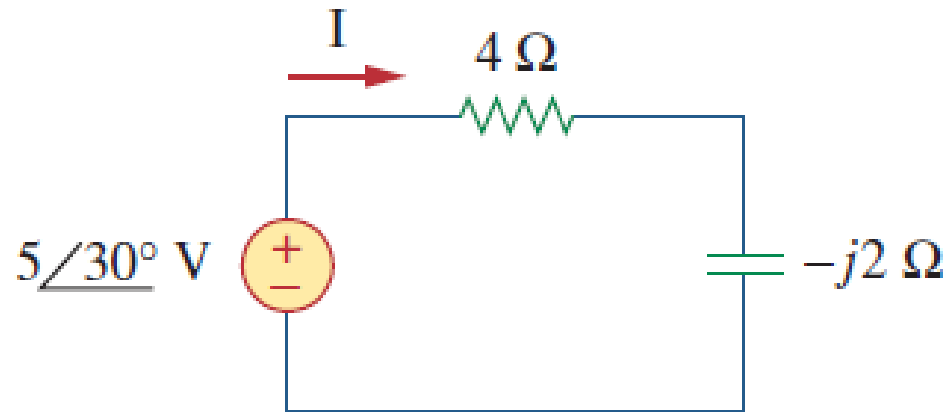
## Example 5

For the circuit shown in Figure, find the average power supplied by the source and the average power absorbed by the resistor.



### **Solution:**

The current  $I$  is given by

$$I = \frac{5\angle 30^\circ}{4 - j2} = \frac{5\angle 30^\circ}{4.472\angle -26.57^\circ} = 1.118\angle 56.57^\circ \text{ A}$$

The average power supplied by the voltage source is

$$P = \frac{1}{2}(5)(1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$





The current through the resistor is

$$\mathbf{I}_R = \mathbf{I} = 1.118 \underline{\underline{56.57^\circ}} \text{ A}$$

and the voltage across it is

$$\mathbf{V}_R = 4\mathbf{I}_R = 4.472 \underline{\underline{56.57^\circ}} \text{ V}$$

The average power absorbed by the resistor is

$$P = \frac{1}{2}(4.472)(1.118) = 2.5 \text{ W}$$


which is the same as the average power supplied. Zero average power is absorbed by the capacitor.



# 11.1 Instantaneous and Average Power (4)
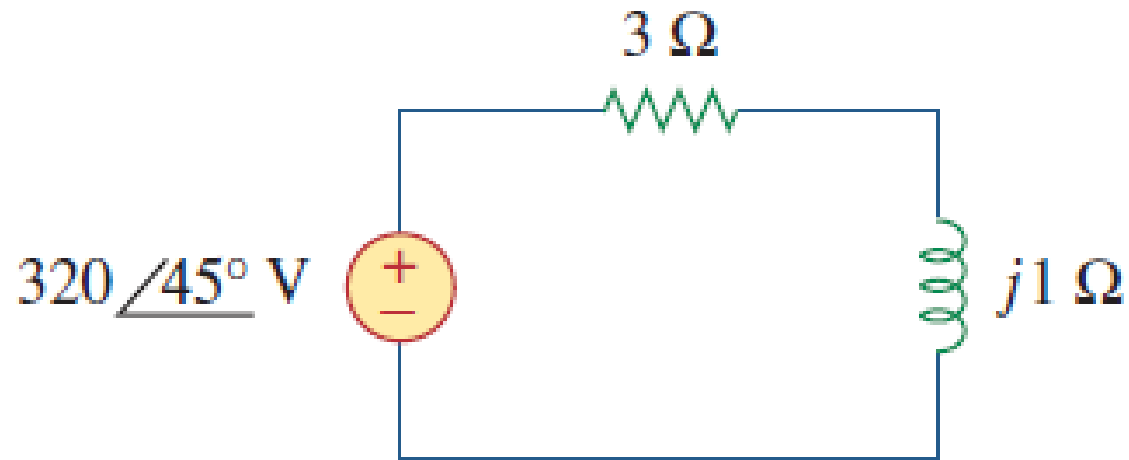
## Example 6


For the circuit shown in Figure, find the average power observed by the resistor and inductor. Find the average power supplied by the source.



**Answer:** 15.361 kW, 0 W, 15.361 kW.



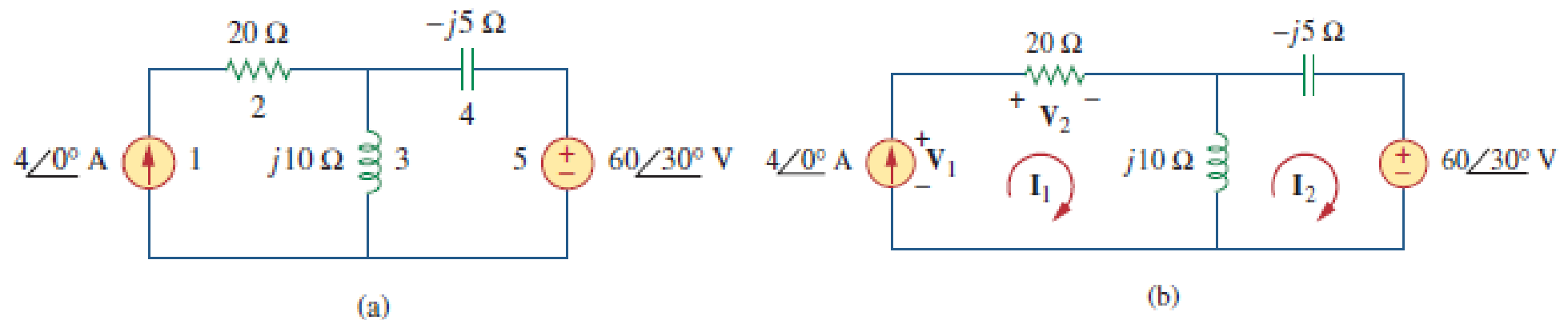**Example 7:** Determine the average power generated by each source and the average power absorbed by each passive element in the circuit of Figure.



**Solution:**

We apply mesh analysis as shown in Fig. 11.5(b). For mesh 1,

$$I_1 = 4\text{ A}$$

For mesh 2,

$$(j10 - j5)I_2 - j10I_1 + 60\angle 30^\circ = 0, \quad I_1 = 4\text{ A}$$

or

$$j5I_2 = -60\angle 30^\circ + j40 \Rightarrow I_2 = -12\angle -60^\circ + 8 \\ = 10.58\angle 79.1^\circ\text{ A}$$



$$P_5 = \frac{1}{2}(60)(10.58) \cos(30^\circ - 79.1^\circ) = 207.8 \text{ W}$$

$$\begin{aligned} V_1 &= 20I_1 + j10(I_1 - I_2) = 80 + j10(4 - 2 - j10.39) \\ &= 183.9 + j20 = 184.984 \angle 6.21^\circ \text{ V} \end{aligned}$$

The average power supplied by the current source is


$$P_1 = -\frac{1}{2}(184.984)(4) \cos(6.21^\circ - 0) = -367.8 \text{ W}$$

$$P_2 = \frac{1}{2}(80)(4) = 160 \text{ W}$$

$$P_4 = \frac{1}{2}(52.9)(10.58) \cos(-90^\circ) = 0$$

$$P_3 = \frac{1}{2}(105.8)(10.58) \cos 90^\circ = 0$$

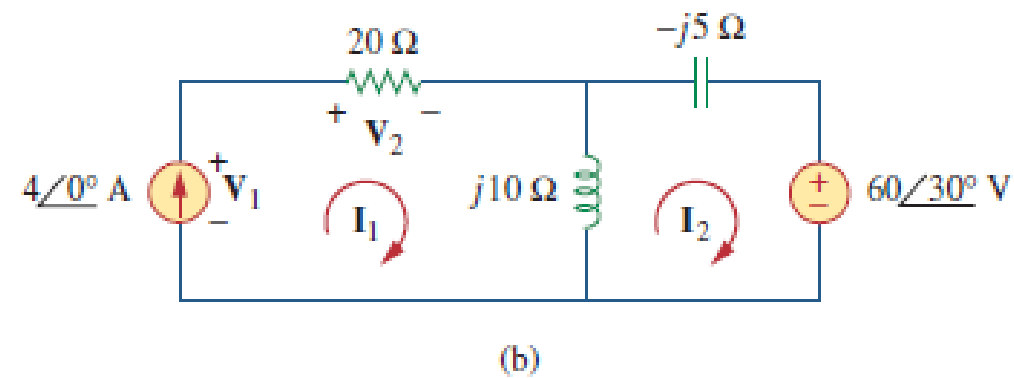
$$P_1 + P_2 + P_3 + P_4 + P_5 = -367.8 + 160 + 0 + 0 + 207.8 = 0$$




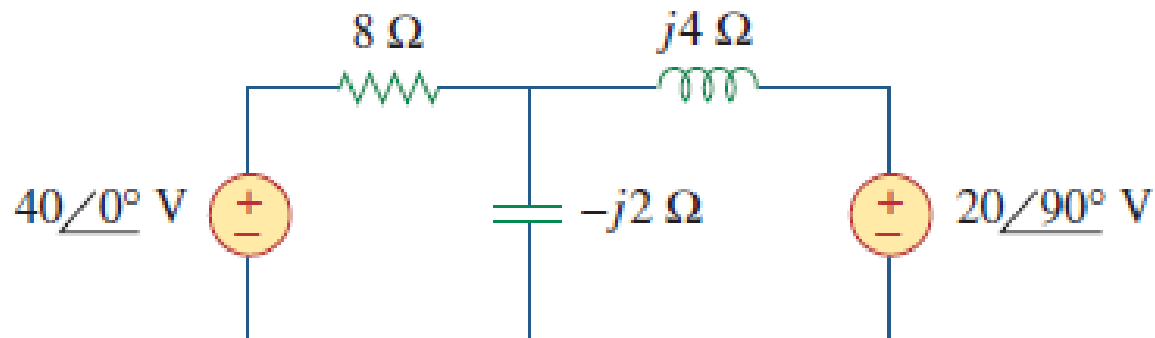
# Practice Problem


Determine the average power generated by each source and the average power absorbed by each passive element in the circuit of Figure.




**Answer:** 40-V Voltage source:  $-60$  W;  $j20$ -V Voltage source:  $-40$  W; resistor:  $100$  W; others:  $0$  W.


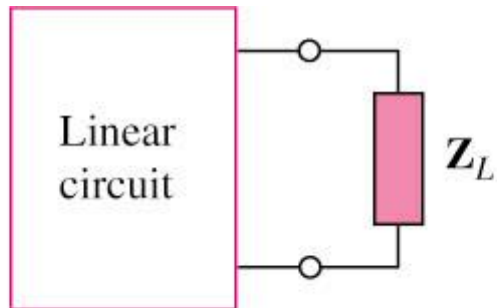
## 11.2 Maximum Average Power Transfer (1)



(a)

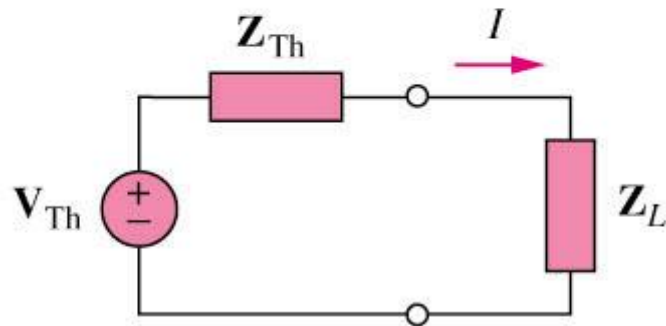

(b)

$$Z_{TH} = R_{TH} + jX_{TH}$$

$$Z_L = R_L + jX_L$$

The maximum average power can be transferred to the load if

$$X_L = -X_{TH} \text{ and } R_L = R_{TH}$$

$$P_{\max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$



If the load is purely real, then  $R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$



## 11.2 Maximum Average Power Transfer (2)
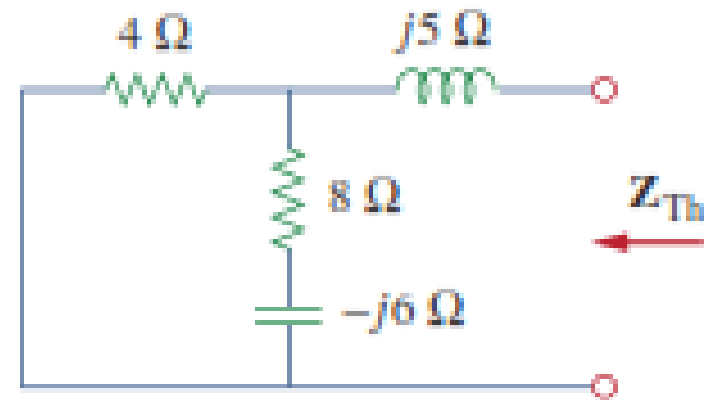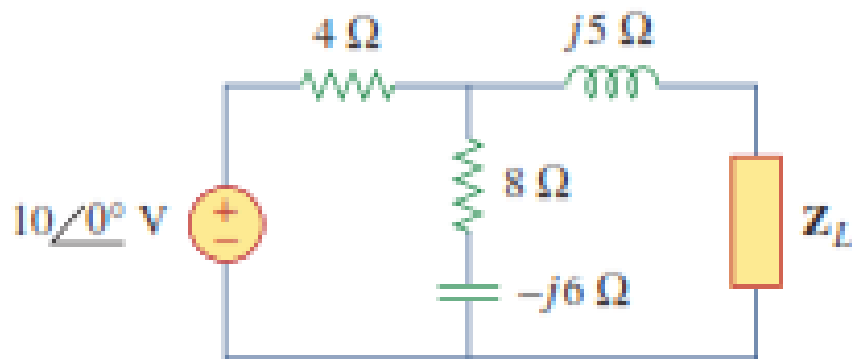
### Example 11.5

For the circuit shown below, find the load impedance  $Z_L$  that absorbs the maximum average power. Calculate that maximum average power.




(a)

$$Z_{Th} = j5 + 4 \parallel (8 - j6) = j5 + \frac{4(8 - j6)}{4 + 8 - j6} = 2.933 + j4.467 \, \Omega$$


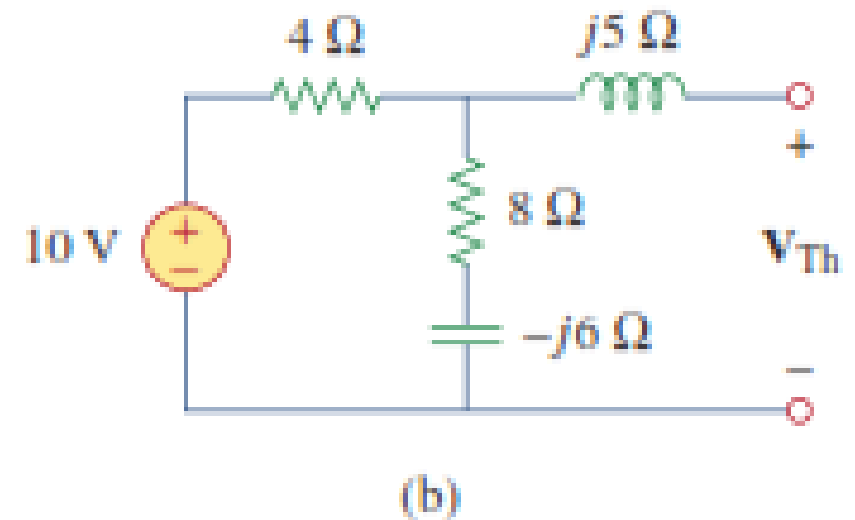
## 11.2 Maximum Average Power Transfer (2)



To find  $V_{Th}$ , consider the circuit in Fig. 11.8(b). By voltage division,

$$V_{Th} = \frac{8 - j6}{4 + 8 - j6}(10) = 7.454 \angle -10.3^\circ \text{ V}$$

The load impedance draws the maximum power from the circuit when

$$Z_L = Z_{Th}^* = 2.933 - j4.467 \Omega$$

$$P_{max} = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{(7.454)^2}{8(2.933)} = 2.368 \text{ W}$$






## 11.2 Maximum Average Power Transfer (2)


**Example: 11.6:** In the circuit in Figure, find the value of  $R_L$  that will absorb the maximum average power. Calculate that power.

**Ans:** 39.29 watts

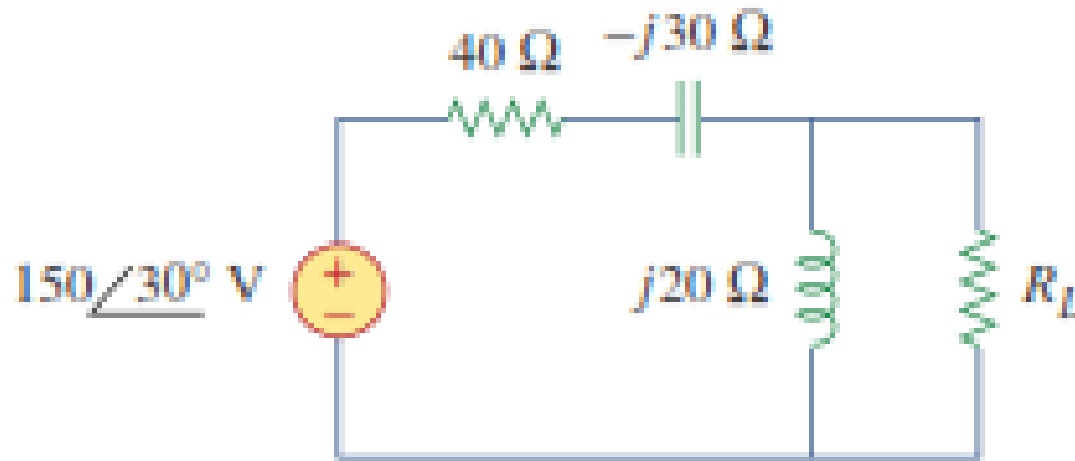




## 11.3 Effective or RMS Value (1)

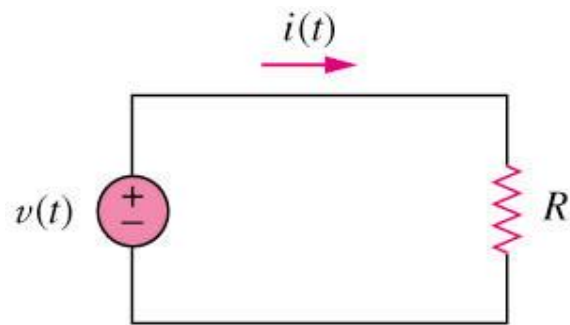

(a)

The total power dissipated by R is given by:
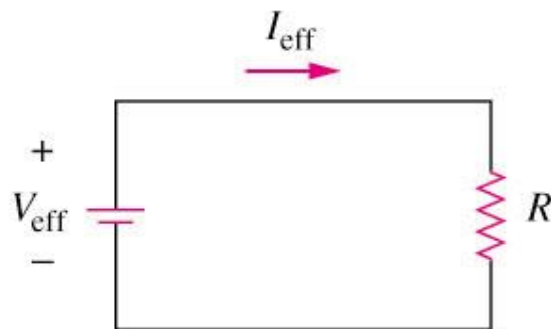
$$P = \frac{1}{T} \int_0^T i^2 R dt = \frac{R}{T} \int_0^T i^2 dt = I_{rms}^2 R$$



(b)

Hence,  $I_{eff}$  is equal to:


$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

The rms value is a constant itself which depending on the shape of the function  $i(t)$ .

The effective of a periodic current is the dc current that delivers the same average power to a resistor as the periodic current.<sup>18</sup>




## 11.3 Effective or RMS Value (2)

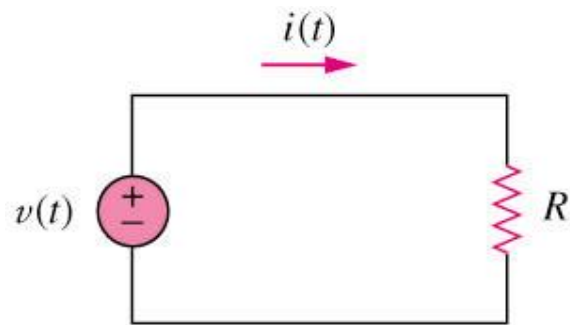

(a)

The rms value of a sinusoid  $i(t) = I_m \cos(\omega t)$  is given by:

$$I_{\text{rms}}^2 = \frac{I_m^2}{2}$$

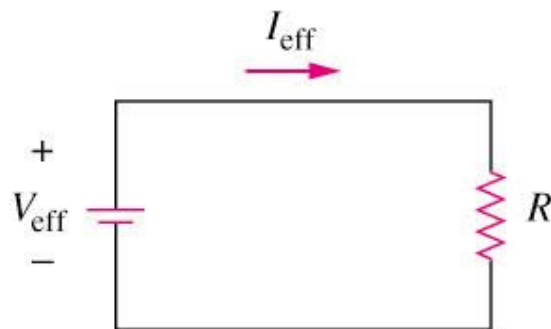

(b)

The average power can be written in terms of the rms values:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

Note: If you express amplitude of a phasor source(s) in rms, then all the answer as a result of this phasor source(s) must also be in rms value.



## 11.3 Effective or RMS Value (2)

The waveform shown in Figure is a half-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a 10-Ohm resistor.

### Solution:

The period of the voltage waveform is  $T = 2\pi$ , and

$$v(t) = \begin{cases} 10 \sin t, & 0 < t < \pi \\ 0, & \pi < t < 2\pi \end{cases}$$

The rms value is obtained as


$$V_{\text{rms}}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2\pi} \left[ \int_0^{\pi} (10 \sin t)^2 dt + \int_{\pi}^{2\pi} 0^2 dt \right]$$

But  $\sin^2 t = \frac{1}{2}(1 - \cos 2t)$ . Hence,

$$\begin{aligned} V_{\text{rms}}^2 &= \frac{1}{2\pi} \int_0^{\pi} \frac{100}{2} (1 - \cos 2t) dt = \frac{50}{2\pi} \left( t - \frac{\sin 2t}{2} \right) \Big|_0^{\pi} \\ &= \frac{50}{2\pi} \left( \pi - \frac{1}{2} \sin 2\pi - 0 \right) = 25, \quad V_{\text{rms}} = 5 \text{ V} \end{aligned}$$

The average power absorbed is

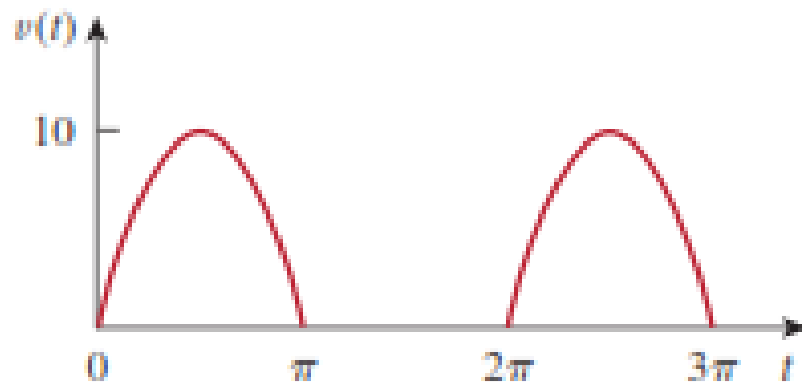
$$P = \frac{V_{\text{rms}}^2}{R} = \frac{5^2}{10} = 2.5 \text{ W}$$




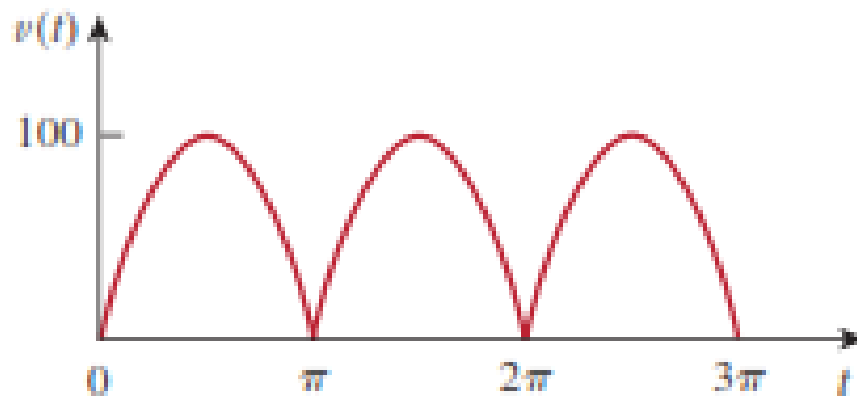
## 11.3 Effective or RMS Value (2)

The waveform shown in Figure is a full-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a 6-Ohm resistor.



Answer: 70.71 V, 833.3 W.



## 11.4 Apparent Power and Power Factor (1)

Apparent Power,  $S$ , is the product of the r.m.s. values of voltage and current.

It is measured in volt-amperes or VA to distinguish it from the average or real power which is measured in watts.

$$P = V_{\text{rms}} I_{\text{rms}} \cos (\theta_v - \theta_i) = S \cos (\theta_v - \theta_i)$$

Apparent Power,  $S$

Power Factor,  $\text{pf}$

Power factor is the cosine of the phase difference between the voltage and current. It is also the cosine of the angle of the load impedance.




## 11.4 Apparent Power and Power Factor (2)

Purely resistive load (R)	$\theta_v - \theta_i = 0, \quad \text{Pf} = 1$	$P/S = 1$ , all power are consumed
Purely reactive load (L or C)	$\theta_v - \theta_i = \pm 90^\circ,$ $\text{pf} = 0$	$P = 0$ , no real power consumption
Resistive and reactive load (R and L/C)	$\theta_v - \theta_i > 0$ $\theta_v - \theta_i < 0$	<ul style="list-style-type: none"><li>• <u>Lagging</u> - inductive load</li><li>• <u>Leading</u> - capacitive load</li></ul>


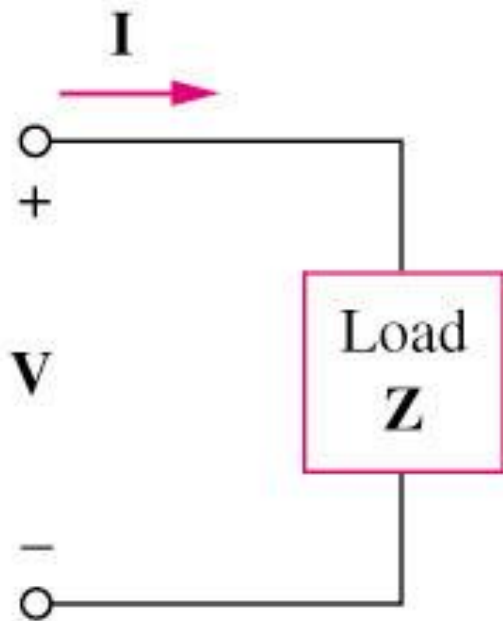
## 11.5 Complex Power (1)

Complex power **S** is the product of the voltage and the complex conjugate of the current:



$$\mathbf{V} = V_m \angle \theta_v$$


$$\mathbf{I} = I_m \angle \theta_i$$

$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$





## 11.5 Complex Power (2)

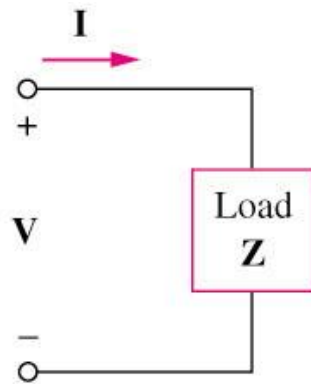

$$S = \frac{1}{2} V I^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos (\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin (\theta_v - \theta_i)$$

$$S = \mathbf{P} + j \mathbf{Q}$$


P: is the average power in watts delivered to a load and it is the only useful power.

Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- Q = 0 for *resistive loads* (unity pf).
- Q < 0 for *capacitive loads* (leading pf).
- Q > 0 for *inductive loads* (lagging pf).



## 11.5 Complex Power (3)

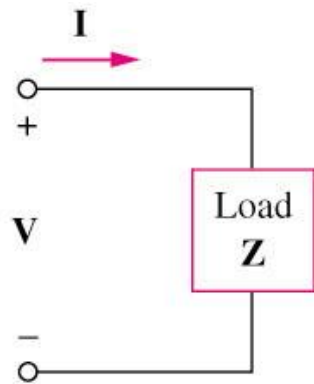

$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$$
$$\mathbf{S} = \mathbf{P} + j \mathbf{Q}$$

Apparent Power,  $S = |\mathbf{S}| = V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2}$


Real power,  $P = \text{Re}(\mathbf{S}) = S \cos(\theta_v - \theta_i)$

Reactive Power,  $Q = \text{Im}(\mathbf{S}) = S \sin(\theta_v - \theta_i)$

Power factor,  $\text{pf} = P/S = \cos(\theta_v - \theta_i)$




# 11.5 Complex Power (4)

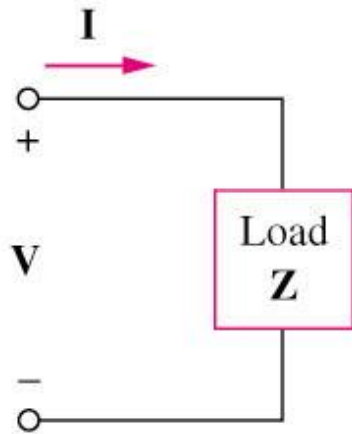


$$\Rightarrow S = V_{\text{rms}} I_{\text{rms}} \cos (\theta_v - \theta_i) + j V_{\text{rms}} I_{\text{rms}} \sin (\theta_v - \theta_i)$$

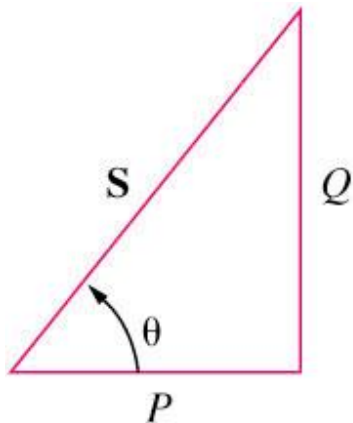
$$\mathbf{S} = \mathbf{P} + j \mathbf{Q}$$



Power Triangle

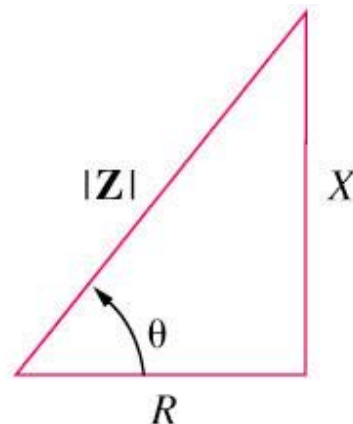

Impedance Triangle

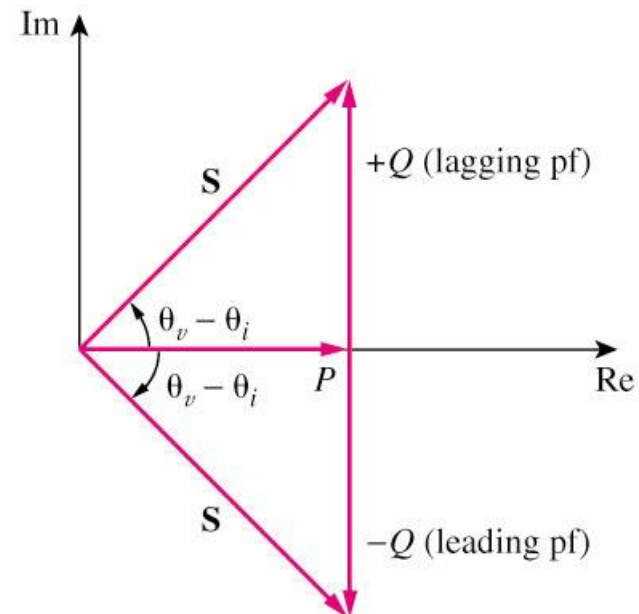

Power Factor



# Example Problem.1

A series-connected load draws a current  $i(t) = 4 \cos(100\pi t + 10^\circ)$  A when the applied voltage is  $v(t) = 120 \cos(100\pi t - 20^\circ)$  V. Find the apparent power and the power factor of the load. Determine the element values that form the series-connected load.

## Solution:

The apparent power is

$$S = V_{\text{rms}} I_{\text{rms}} = \frac{120}{\sqrt{2}} \frac{4}{\sqrt{2}} = 240 \text{ VA}$$

The power factor is

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(-20^\circ - 10^\circ) = 0.866 \quad (\text{leading})$$

The pf is leading because the current leads the voltage. The pf may also be obtained from the load impedance.

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = 25.98 - j15 \, \Omega$$

$$\text{pf} = \cos(-30^\circ) = 0.866 \quad (\text{leading})$$

The load impedance  $\mathbf{Z}$  can be modeled by a 25.98- $\Omega$  resistor in series with a capacitor with

$$X_C = -15 = -\frac{1}{\omega C} \quad \longrightarrow \quad C = \frac{1}{15\omega} = \frac{1}{15 \times 100\pi} = 212.2 \, \mu\text{F}$$



## Practice Problem.1


Obtain the power factor and the apparent power of a load whose impedance is  $\mathbf{Z} = 60 + j40 \, \Omega$  when the applied voltage is  $v(t) = 320 \cos(377t + 10^\circ) \text{ V}$ .

**Answer:** 0.8321 lagging,  $710 \angle 33.69^\circ \text{ VA}$

## Practice Problem.2

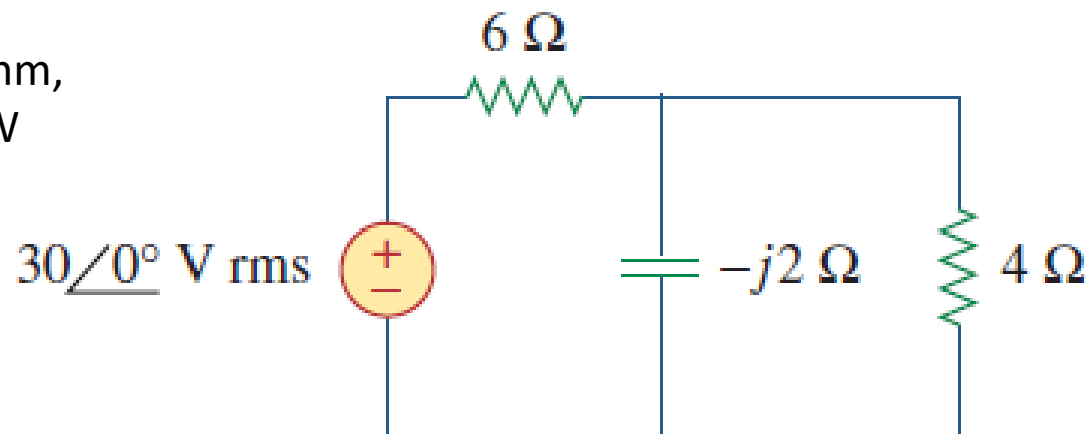2. Determine the power factor of the entire circuit of Figure as seen by the source. Calculate the average power delivered by the source.


**Ans:**  $\mathbf{Z} = 7 \angle -13.24 \, \Omega$ ,  
0.9734 leading, 125 W





## Practice Problem.3

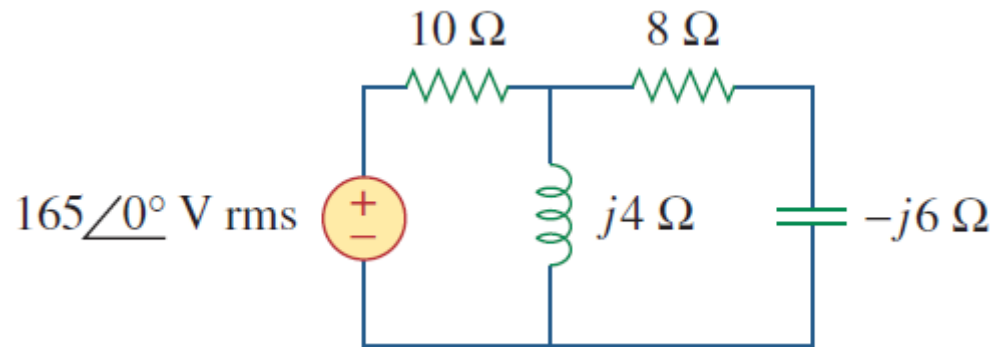3. Determine the power factor of the entire circuit of Figure as seen by the source. Calculate the average power delivered by the source.



**Answer:** 0.936 lagging, 2.008 kW



# Example Problem on Complex Power

The voltage across a load is  $v(t) = 60 \cos(\omega t - 10^\circ)$  V and the current through the element in the direction of the voltage drop is  $i(t) = 1.5 \cos(\omega t + 50^\circ)$  A. Find: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

## Solution:

(a) For the rms values of the voltage and current, we write

$$\mathbf{V}_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -10^\circ, \quad \mathbf{I}_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle +50^\circ$$

The complex power is

$$\mathbf{S} = \mathbf{V}_{\text{rms}} \mathbf{I}_{\text{rms}}^* = \left( \frac{60}{\sqrt{2}} \angle -10^\circ \right) \left( \frac{1.5}{\sqrt{2}} \angle -50^\circ \right) = 45 \angle -60^\circ \text{ VA}$$

The apparent power is

$$S = |\mathbf{S}| = 45 \text{ VA}$$



(b) We can express the complex power in rectangular form as

$$\mathbf{S} = 45 \angle -60^\circ = 45[\cos(-60^\circ) + j \sin(-60^\circ)] = 22.5 - j38.97$$

Since  $\mathbf{S} = P + jQ$ , the real power is

$$P = 22.5 \text{ W}$$

while the reactive power is

$$Q = -38.97 \text{ VAR}$$

(c) The power factor is

$$\text{pf} = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

It is leading, because the reactive power is negative. The load impedance is

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{60 \angle -10^\circ}{1.5 \angle +50^\circ} = 40 \angle -60^\circ \Omega$$

which is a capacitive impedance.





# Practice Problem on Complex Power

For a load,  $\mathbf{V}_{\text{rms}} = 110 \angle 85^\circ \text{ V}$ ,  $\mathbf{I}_{\text{rms}} = 0.4 \angle 15^\circ \text{ A}$ . Determine: (a) the complex and apparent powers, (b) the real and reactive powers, and (c) the power factor and the load impedance.

**Answer:** (a)  $44 \angle 70^\circ \text{ VA}$ ,  $44 \text{ VA}$ , (b)  $15.05 \text{ W}$ ,  $41.35 \text{ VAR}$ , (c)  $0.342$  lagging,  $94.06 + j258.4 \Omega$ .