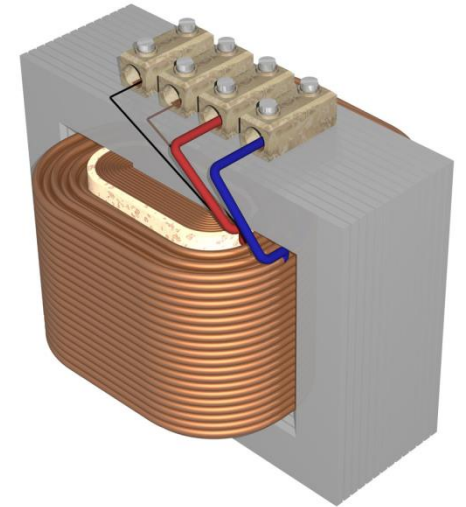




# Electrical Circuits for Engineers (EC1000)



## Lecture-11 Transformers





# Introduction



**William Stanley invented the transformer during 1885**

Transformer is a Static device, used to transfer electrical energy from one circuit to another circuit without change in frequency


Use to change the AC voltage level from one to another.

Works under Faraday's law of Electro Magnetic Induction


It contains

- 1) **Winding** (Primary & Secondary)- **Electrical Circuit**  
(Copper/Aluminium conductor)
- 2) **Magnetic Core** (Iron Core)— **Magnetic circuit**

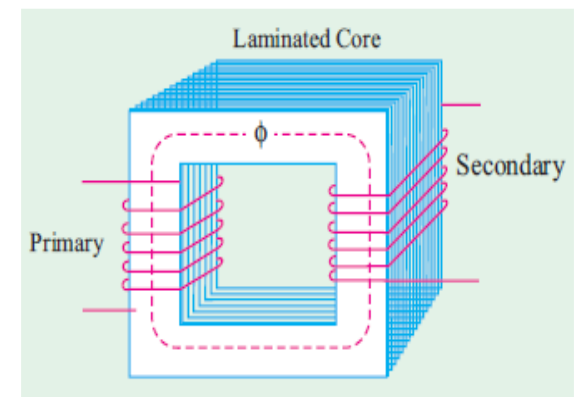**Both windings are magnetically coupled and Electrically Isolated**



# ***Transmission of Power***

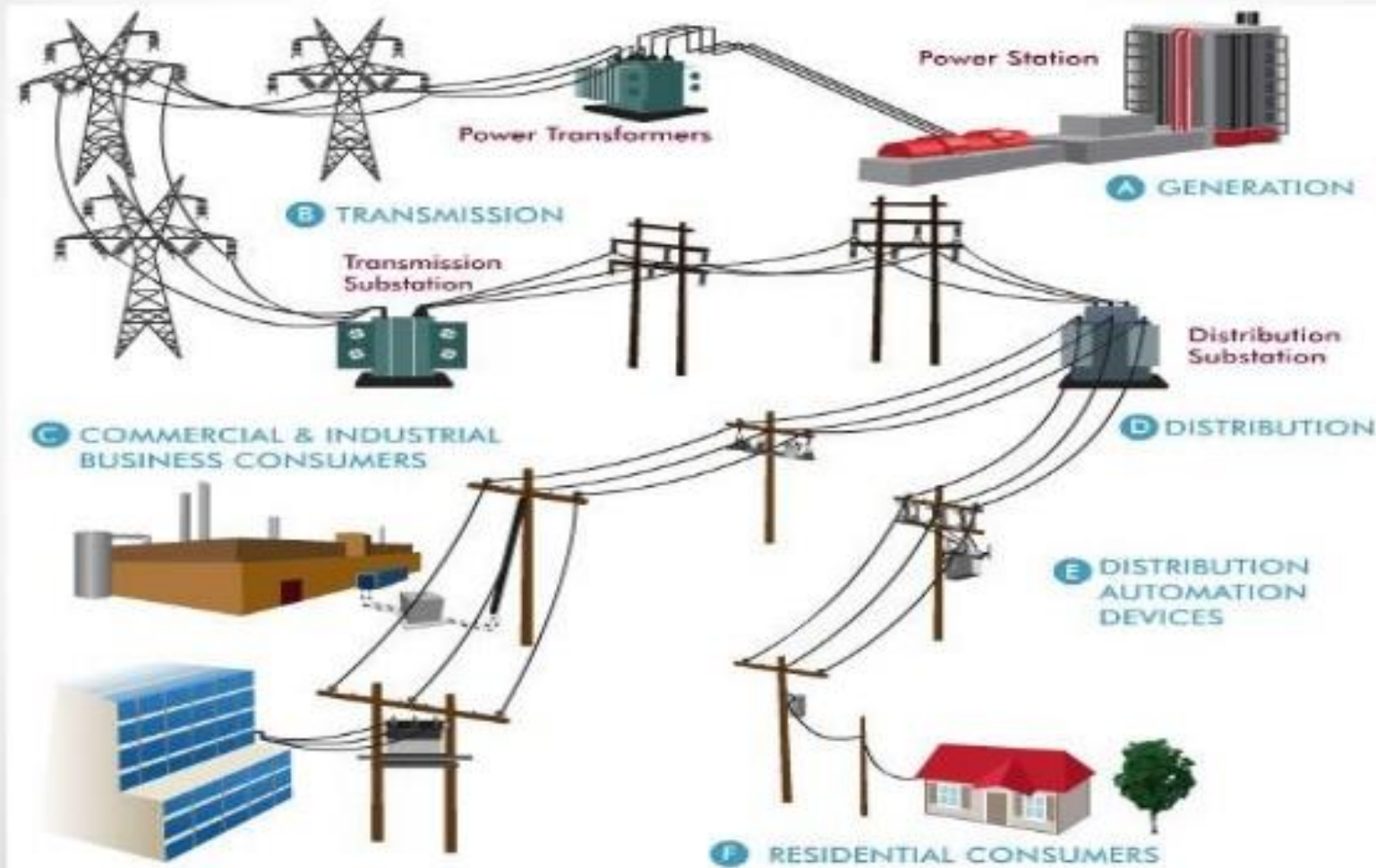



# Transformer

The essential components of the transformer are:



1. Magnetic core
2. Two windings, namely primary and secondary windings
3. A time varying magnetic flux

## Magnetic circuit

The core of the transformer is made of high-grade silicon steel or sheet steel lamination, which has low hysteresis loss and provides a continuous magnetic path.

The main functions of the magnetic circuit are:

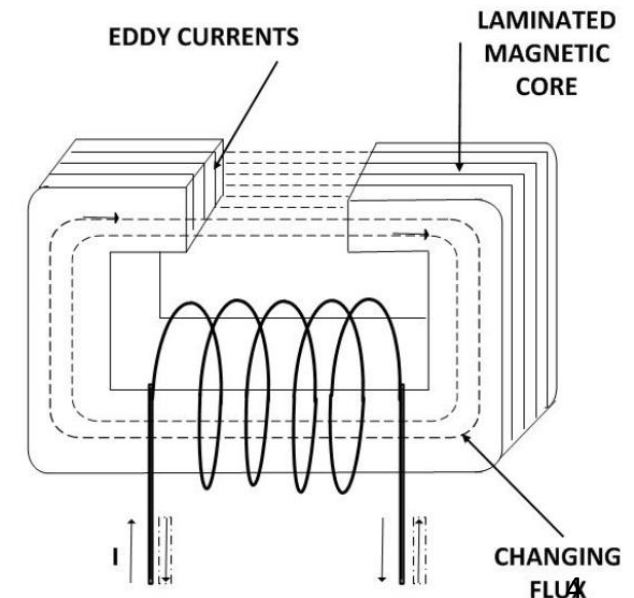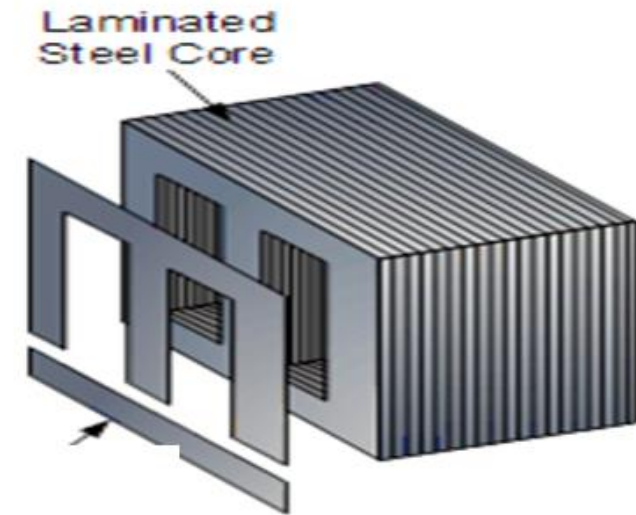- Provides low reluctance path for carrying the flux.
- Carries the windings required for electric power transfer.






# Transformer
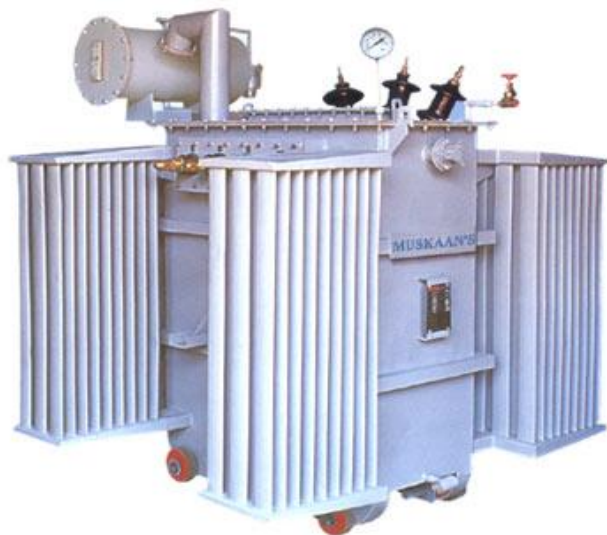
## Electric circuit



- In the transformer, there are two windings, namely primary and secondary windings.
- The winding connected to the input side is called the *primary winding*,
- The winding connected to the output side is called the *secondary winding*.
- These windings are made of copper







# Transformer

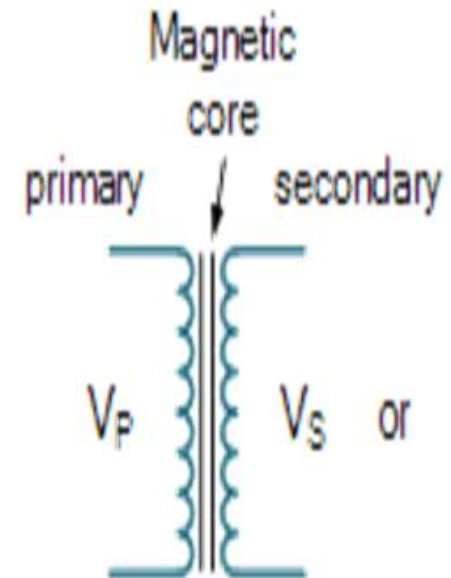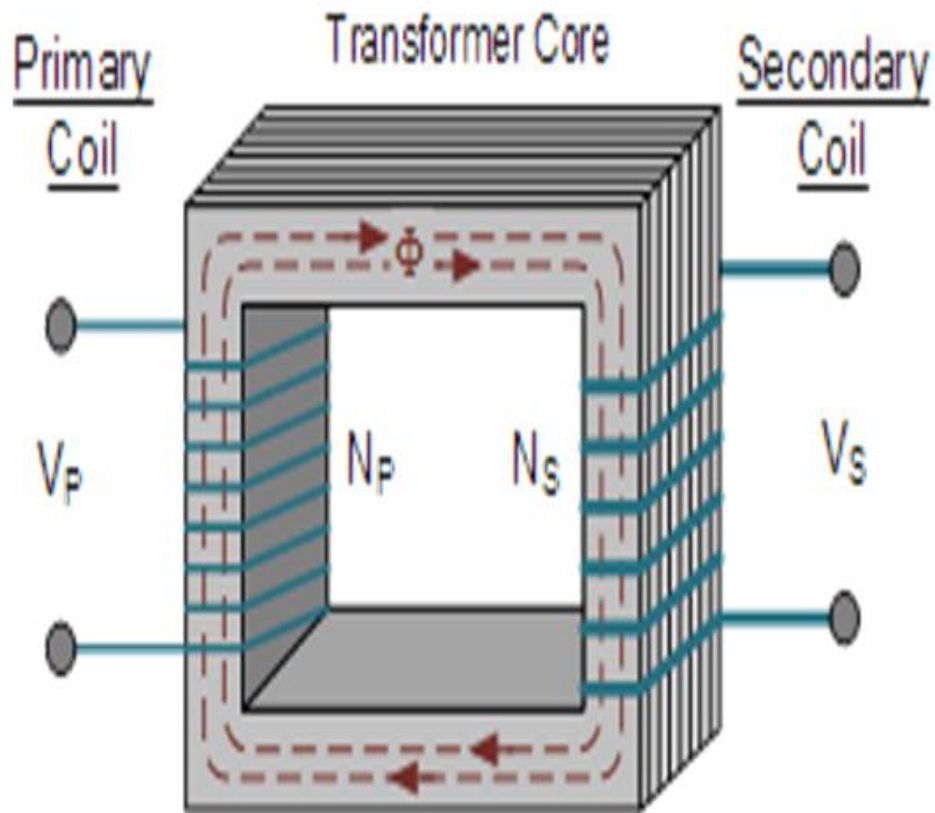

Transformer  
Symbol



# Types of Transformer



According to the core construction and the manner in which the windings are wound, transformers are classified as

- **core-type**
- **shell-type**



In the core-type transformer, the windings surround the core.

In the shell-type transformer, the core surrounds the windings.

## core-type

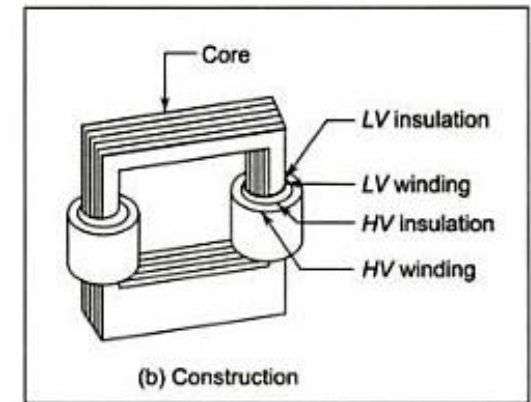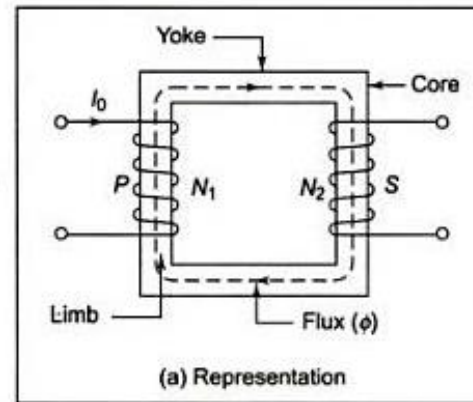

## shell-type

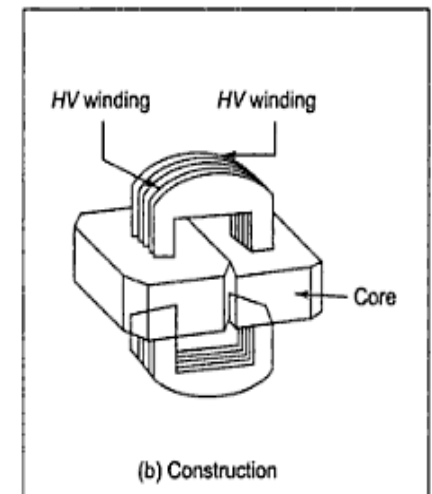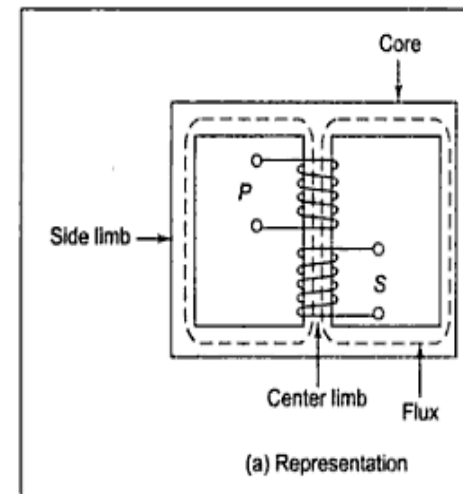



# EMF Equation of a transformer

$$\Phi = \Phi_{\max} \sin \omega t$$


$$E = N \frac{d\Phi}{dt}$$

$$E = N \times \omega \times \Phi_{\max} \times \cos(\omega t)$$

$$E_{\max} = N \omega \Phi_{\max}$$

$$E_{\text{rms}} = \frac{N\omega}{\sqrt{2}} \times \Phi_{\max} = \frac{2\pi}{\sqrt{2}} \times f \times N \times \Phi_{\max}$$
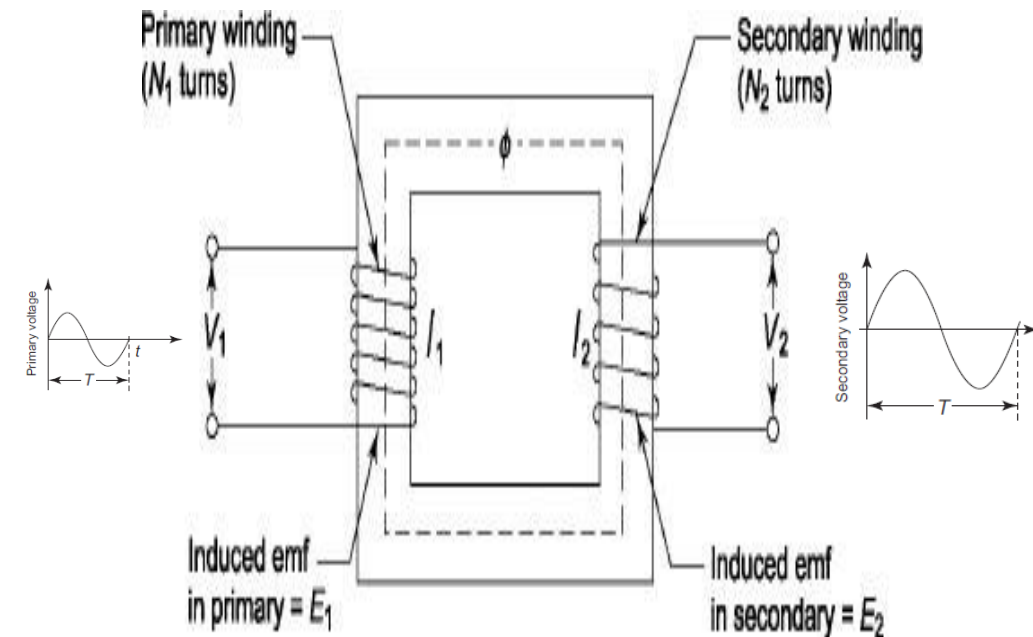
$$\therefore E_{\text{rms}} = 4.44 f N \Phi_{\max}$$



•Where:

- $f$  - is the flux frequency in Hertz,  $= \omega/2\pi$
- $N$  - is the number of coil windings.
- $\Phi$  - is the amount of flux in webers





# Transformation Ratio

$$E_1 = 4.44 f \Phi_m N_1 \quad E_2 = 4.44 f \Phi_m N_2$$

$$K = \frac{E_2}{E_1}$$


$$K = \frac{4.44 f \Phi_m N_2}{4.44 f \Phi_m N_1} \Rightarrow K = \frac{N_2}{N_1}$$

- Primary side power is same as secondary power

$$E_1 \cdot I_1 = E_2 \cdot I_2 \Rightarrow \frac{E_2}{E_1} = \frac{I_1}{I_2} \Rightarrow K = \frac{I_1}{I_2}$$

$$K = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2}$$

## Transformer Regulation

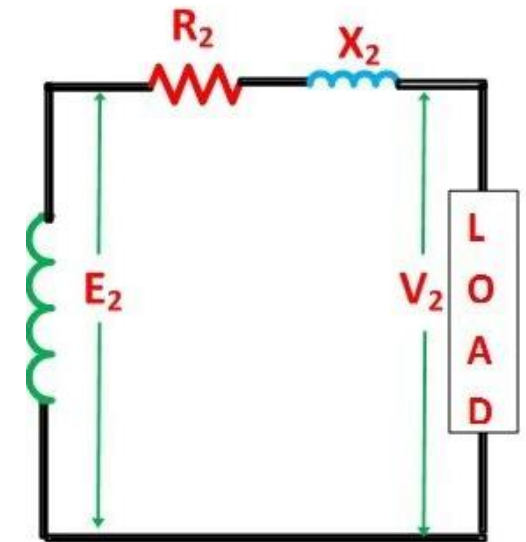

The measure of how well a power transformer maintains constant secondary voltage over a range of load currents is called the transformer's voltage regulation

$$\text{Regulation Percentage} = \frac{E_{\text{no-load}} - E_{\text{full-load}}}{E_{\text{full-load}}} (100\%)$$

If  $E_2 > E_1$ , Then The Transformer is called as Step up Transformer.

If  $E_2 < E_1$ , Then The Transformer is called as Step down Transformer.

$E_2 = E_1$ , Isolation Transformer





# Example Problems

1. The maximum flux density in the core of a 250/3000-volts, 50-Hz single-phase transformer is  $1.2 \text{ Wb/m}^2$ . If the e.m.f. per turn is 8 volt, determine (i) primary and secondary turns (ii) area of the core.

**Solution. (i)**

$$E_1 = N_1 \times \text{e.m.f. induced/turn}$$

$$N_1 = 250/8 = \mathbf{32}; N_2 = 3000/8 = \mathbf{375}$$

**(ii)** We may use

$$E_2 = -4.44 f N_2 B_m A$$

$$\therefore 3000 = 4.44 \times 50 \times 375 \times 1.2 \times A; \mathbf{A = 0.03m^2}.$$



# Example Problems

2. A single-phase transformer has 400 primary and 1000 secondary turns. The net cross-sectional area of the core is 60 cm<sup>2</sup>. If the primary winding be connected to a 50-Hz supply at 520 V, calculate (i) the peak value of flux density in the core (ii) the voltage induced in the secondary winding.

**Solution.**

$$K = N_2/N_1 = 1000/400 = 2.5$$

(i)  $E_2/E_1 = K \therefore E_2 = KE_1 = 2.5 \times 520 = \mathbf{1300 \text{ V}}$

(ii)  $E_1 = 4.44 f N_1 B_m A$

or  $520 = 4.44 \times 50 \times 400 \times B_m \times (60 \times 10^{-4}) \therefore B_m = \mathbf{0.976 \text{ Wb/m}^2}$



# Example Problems

3. A 25-kVA transformer has 500 turns on the primary and 50 turns on the secondary winding. The primary is connected to 3000-V, 50-Hz supply. Find the full-load primary and secondary currents, the secondary e.m.f. and the maximum flux in the core. Neglect leakage drops and no-load primary current.

**Solution.**

$$K = N_2/N_1 = 50/500 = 1/10$$

Now, full-load  $I_1 = 25,000/3000 = \mathbf{8.33\text{ A}}$ . F.L.  $I_2 = I_1/K = 10 \times 8.33 = \mathbf{83.3\text{ A}}$   
e.m.f. per turn on primary side  $= 3000/500 = 6\text{ V}$

$\therefore$  secondary e.m.f.  $= 6 \times 50 = \mathbf{300\text{ V}}$  (or  $E_2 = KE_1 = 3000 \times 1/10 = 300\text{ V}$ )

Also,  $E_1 = 4.44 f N_1 \Phi_m$ ;  $3000 = 4.44 \times 50 \times 500 \times \Phi_m \therefore \Phi_m = \mathbf{27\text{ mWb}}$





# Practice Problem

1. The required no-load ratio in a 1 -phase 50 Hz core type transformer is 6000/250 V. Find the no. of turns in each winding if the flux is to be about 0.06 wb. (Ans: 480, 20 turns).
2. A 25 kVA, single-phase transformer has 250 turns on the primary and 40 turns on the secondary winding. The primary is connected to 1500-volt, 50 Hz mains. Calculate (i) Primary and Secondary currents on full-load, (ii) Secondary e.m.f., (iii) maximum flux in the core.  
(Ans: 25 mWb, 240V, 16.67 A, 104.2 A)




# Ideal Transformer
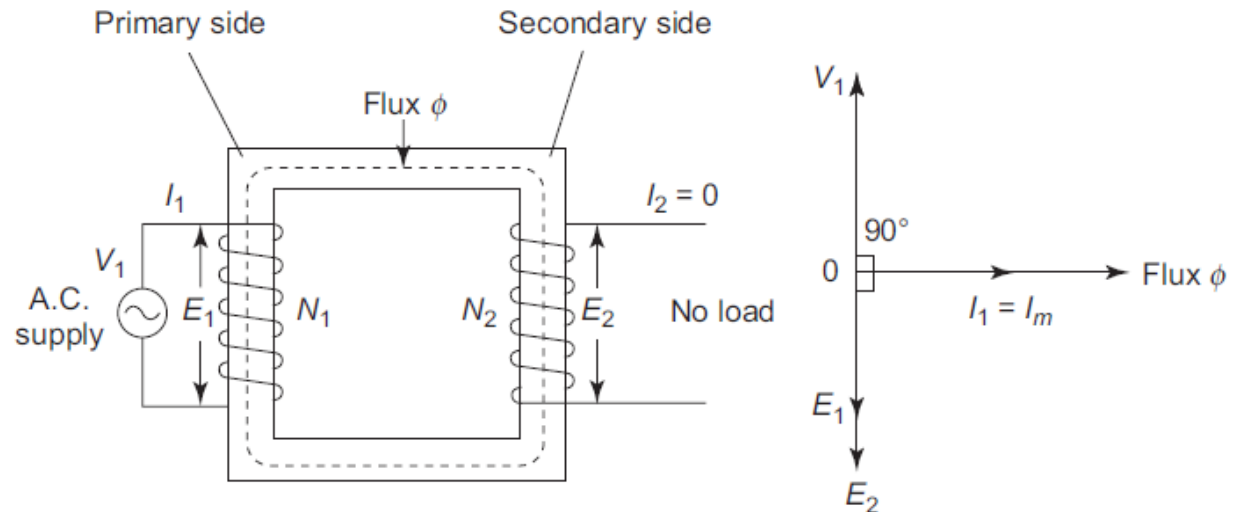
## Ideal transformer

An ideal transformer has the following properties:

- Absence of winding resistance
- Infinite permeability of the core
- No leakage flux
- 100% efficiency



## Ideal Transformer on No-load



- The current drawn from the source is used to produce the magnetic flux.
- Hence, the current drawn from the primary winding is called magnetizing current.
- As the winding is purely inductive, the magnetizing current  $I_m$  lags the supply voltage by  $90^\circ$ .
- The alternating flux  $\Phi$  is in phase with  $I_m$ .
- This alternating flux induces an emf in the primary winding,  $E_1$ , which opposes the supply voltage i.e., the phase angle between  $E_1$  and  $V_1$  is  $180^\circ$ .
- Since an alternating flux links the secondary winding, an emf,  $E_2$ , is induced in the secondary winding.
- Induced emf in secondary winding,  $E_2$ , depends on the number of turns,  $N_2$ , in the secondary winding.
- Since the secondary circuit is not closed, the secondary current,  $I_2 = 0$



# Practical Transformer
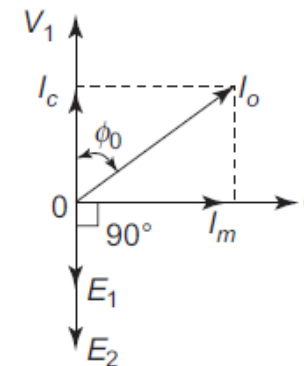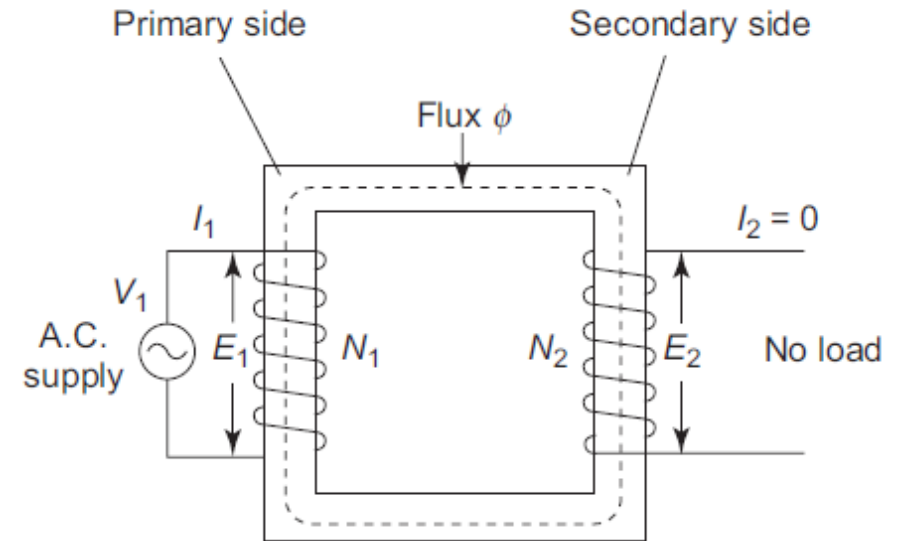
## On No-load

- The primary current drawn from the source has two components
  - Magnetising component: The magnetizing current,  $I_m$ , which is a purely reactive component of  $I_o$  that lags  $V_1$  by  $90^\circ$ , is required to magnetise the core and to produce the magnetic flux.
  - Loss component: The core loss component  $I_c$ , supplies the total losses of the transformer under no load condition.
- Hence, the total no-load current of a transformer,  $I_o$  is the vector addition of  $I_m$  and  $I_c$ .
- Since  $I_c$  is very small, approximately 0.04 times the full-load rated current, it contributes more to core loss or iron loss when compared to primary copper loss.
- Hence, the no load input power,  $W_o$ , supplies the iron loss of the transformer, which is constant for different load conditions.
- Since the secondary circuit is not closed, the secondary current,  $I_2 = 0$ .




$I_o$  = No load current  
 $I_m$  = Magnetizing current  
 $I_c$  = Core loss component  
 $E_1$  = Induced emf in primary side winding  
 $E_2$  = Induced emf in secondary side winding  
 $V_1$  = Source voltage

$$\bar{I}_o = \bar{I}_m + \bar{I}_c$$

$$I_c = I_o \cos \phi_0 \text{ and } I_m = I_o \sin \phi_0$$



$$W_o = V_1 I_o \cos \phi_0$$

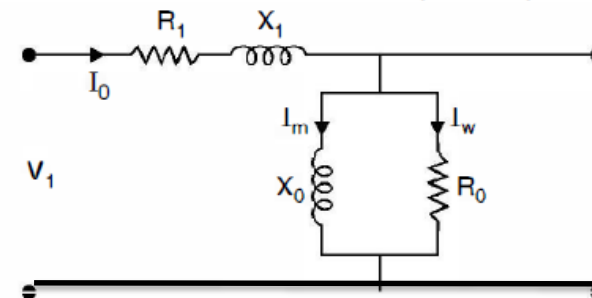


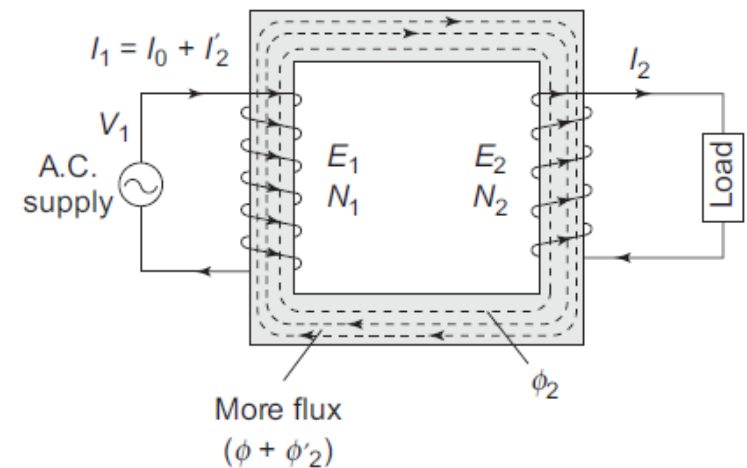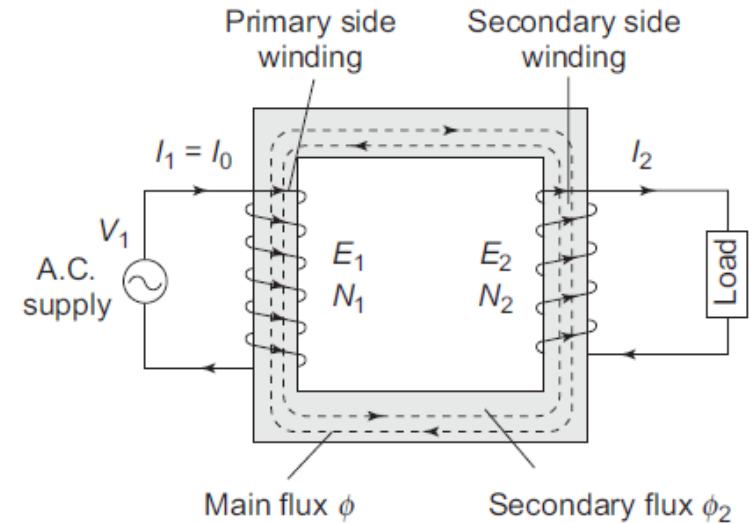
# Transformer on Load


- Since the load is connected to the secondary winding, the current  $I_2$  flows through the winding and an output voltage  $V_2$  is obtained across the load.
- The phase difference between the output voltage  $V_2$  and  $I_2$  depends on the load
  - If load is inductive,  $I_2$  lags  $V_2$ ,
  - If load is capacitive,  $I_2$  leads  $V_2$
  - If load is resistive,  $I_2$  is in phase with  $V_2$ .
- The current  $I_2$  flowing through secondary winding produces its own magnetic flux  $\Phi_2$ , which opposes the magnetic flux  $\Phi$ . Since  $\Phi_2$  opposes  $\Phi$ , there is a momentary reduction in the magnetic flux  $\Phi$ , which further decreases the induced emf  $E_1$ .
- This decrease in  $E_1$  increases the difference between  $V_1$  and  $E_1$  that causes the primary winding to draw extra current  $I_2'$ , thereby producing an additional flux  $\Phi_2'$  opposite to  $\Phi_2$ .
- Since this current  $I_2'$  neutralizes  $\Phi_2$ , the flux is maintained constant in the transformer and hence, it is also known as constant flux machine.





# Transformer on Load

## Equivalent Circuit

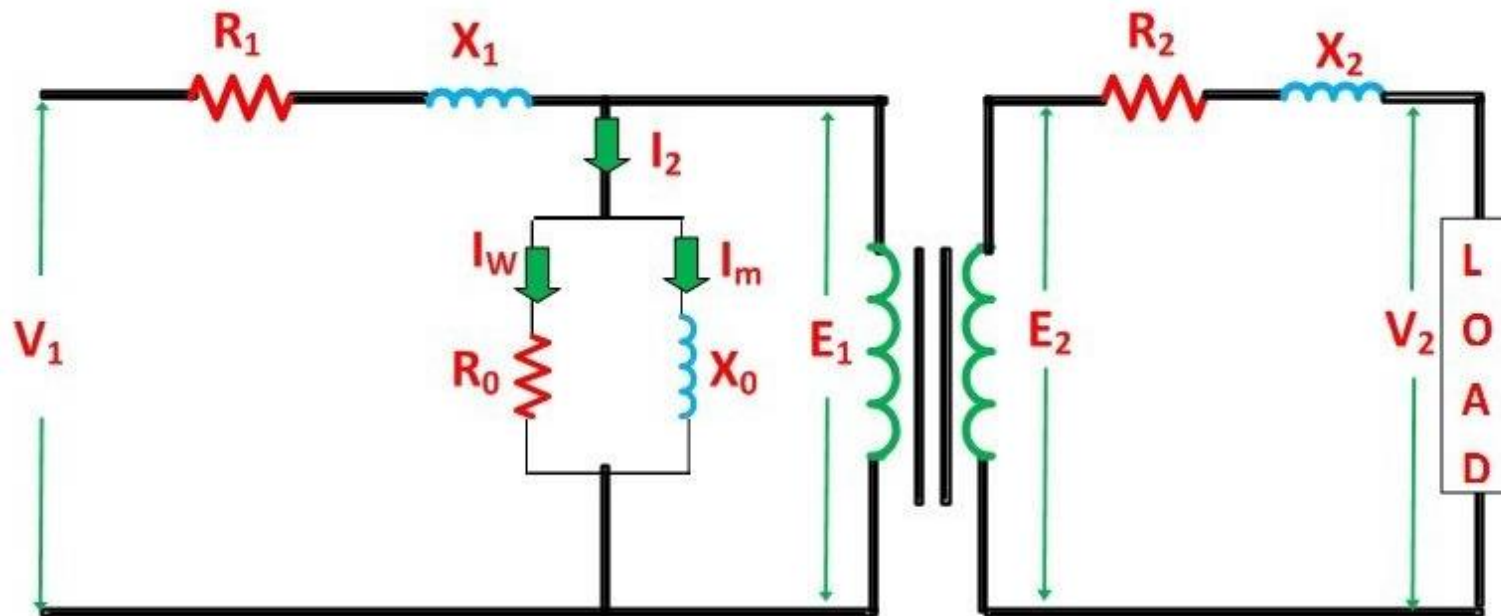






# Losses in transformer

Two types of losses occur in a transformer:

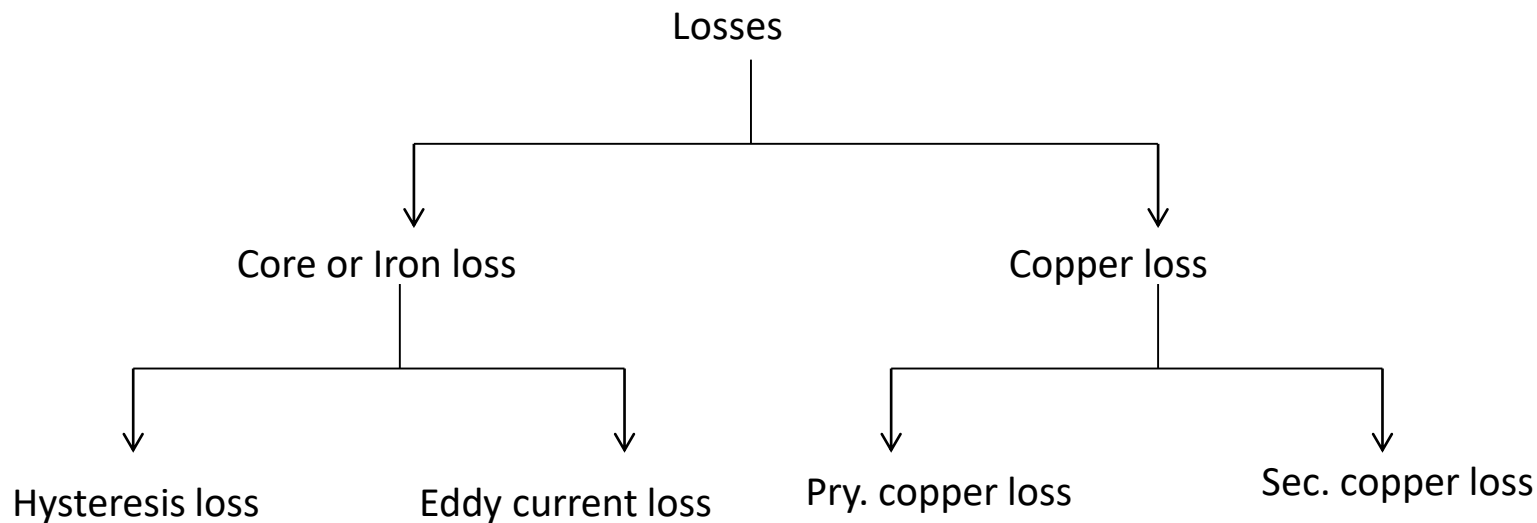1. **Core loss** or iron loss occurs in a transformer because it is subjected to an alternating flux.
2. The windings carry current due to loading and hence **copper losses** occur.





# Efficiency of transformer

the efficiency of the transformer is defined as the ratio of the power output to power input

$$\eta = \frac{\text{Power output}}{\text{Power input}}$$

$$\text{Power input} = \text{Power output} + \text{Total losses}$$

$$\eta = \frac{\text{Power output}}{\text{Power output} + \text{total losses}} = \frac{\text{Power output}}{\text{Power output} + P_i + P_c}$$

The **transformer efficiency is maximum** when the copper loss is equal to the core loss



# Applications of transformer


**Transformers are used in the following applications:**

- (i) Power transformers located in Power Plants are used to step-up the generated voltage to a high transmission voltage.**
- (ii) Transformers are used in distribution circuit to step-down voltages to the desired level.**
- (iii) Almost all electronic circuits use transformers.**
- (iv) Potential transformers are used to measure high voltages and current transformers are used to measure high currents.**
- (v) Furnace transformers and welding transformers are some special applications of transformers.**


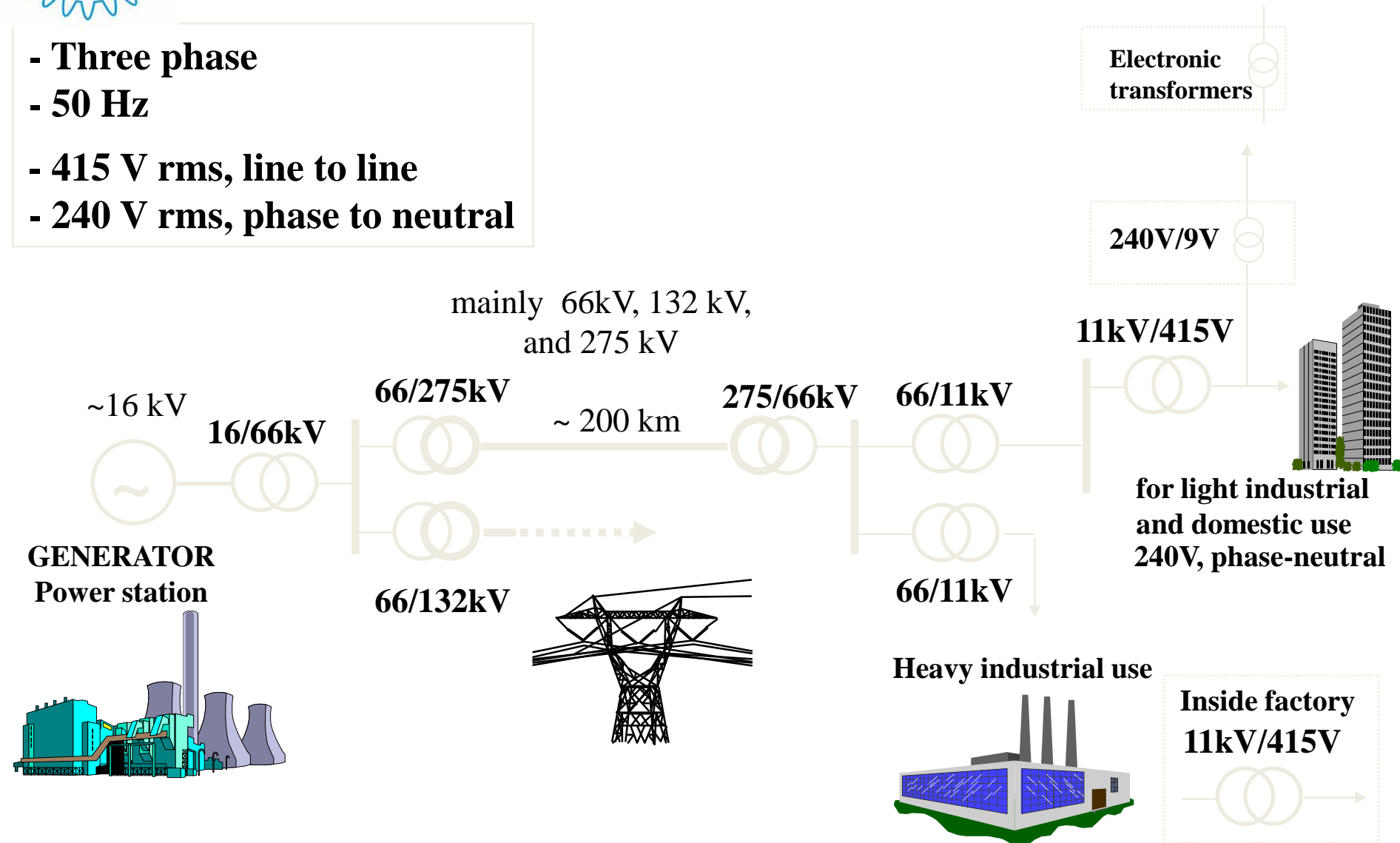
# POWER DISTRIBUTION


- Three phase
- 50 Hz
- 415 V rms, line to line
- 240 V rms, phase to neutral




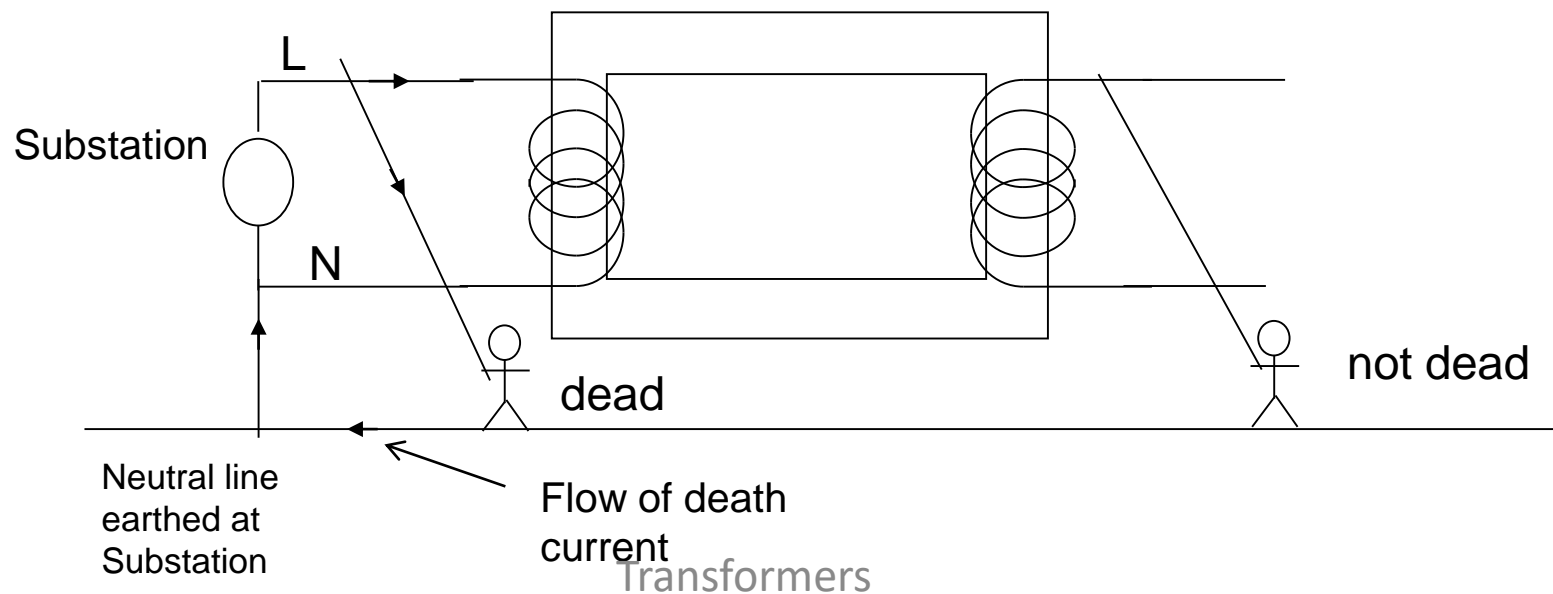
## *Isolation and Safety*

- There is no electrical connection between the primary circuit and the secondary circuit
- The secondary circuit is "electrically isolated" from the primary
- Study the following in which someone makes contact with the conductors:







## *Ratings*

**Rating:** Maximum power delivered by the transformer without exceeding permissible Temperature Rise.

In a name plate, or on a website, a Transformer is typically described as: 240/15V, 150 VA, 20%, 50 Hz. This means:

240 V: Rated input voltage



15 V: Full load output voltage  $V_2$

50 Hz: The frequency that the TF is designed for

150 VA: Volt-Amp rating =  $V_2 I_2$  (values rms)

Note: Power is  $|\tilde{V}_2| |\tilde{I}_2| \cos \theta_2$  and if TF supplying inductive load then  $\theta = 90^\circ$  and  $P = 0$ , even though  $|\tilde{I}_2|$  could be at rated value of 10A rms

# Name Plate Details

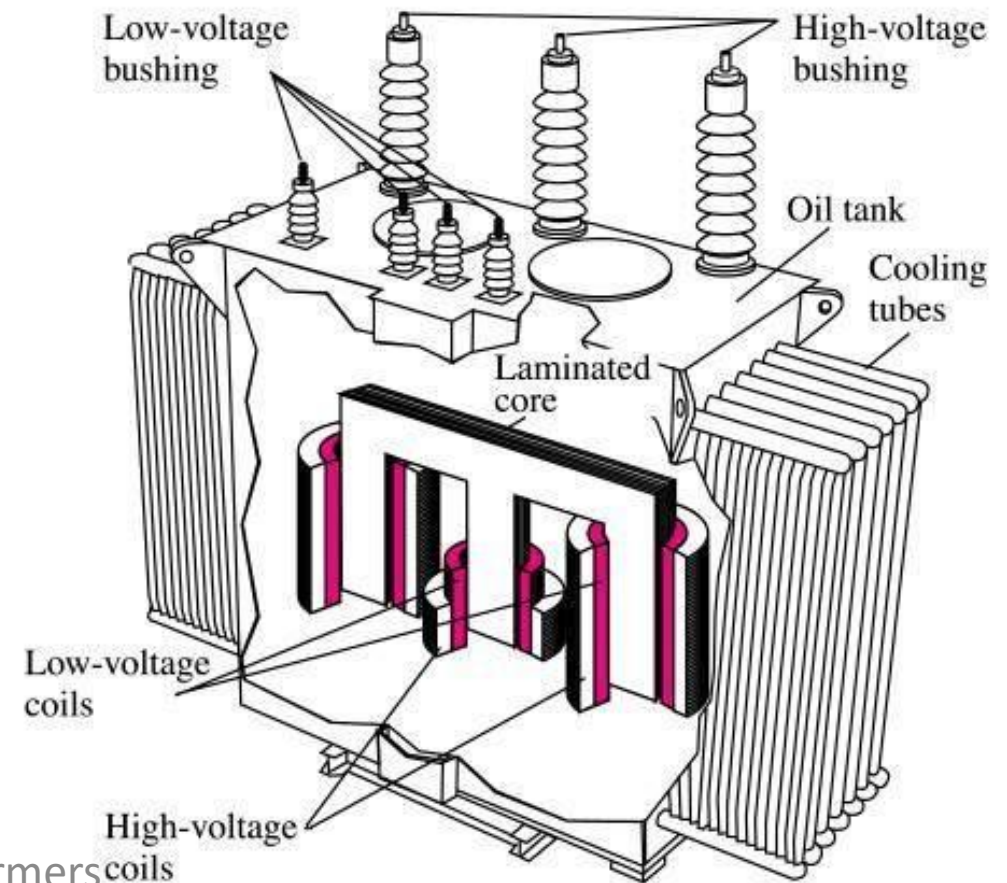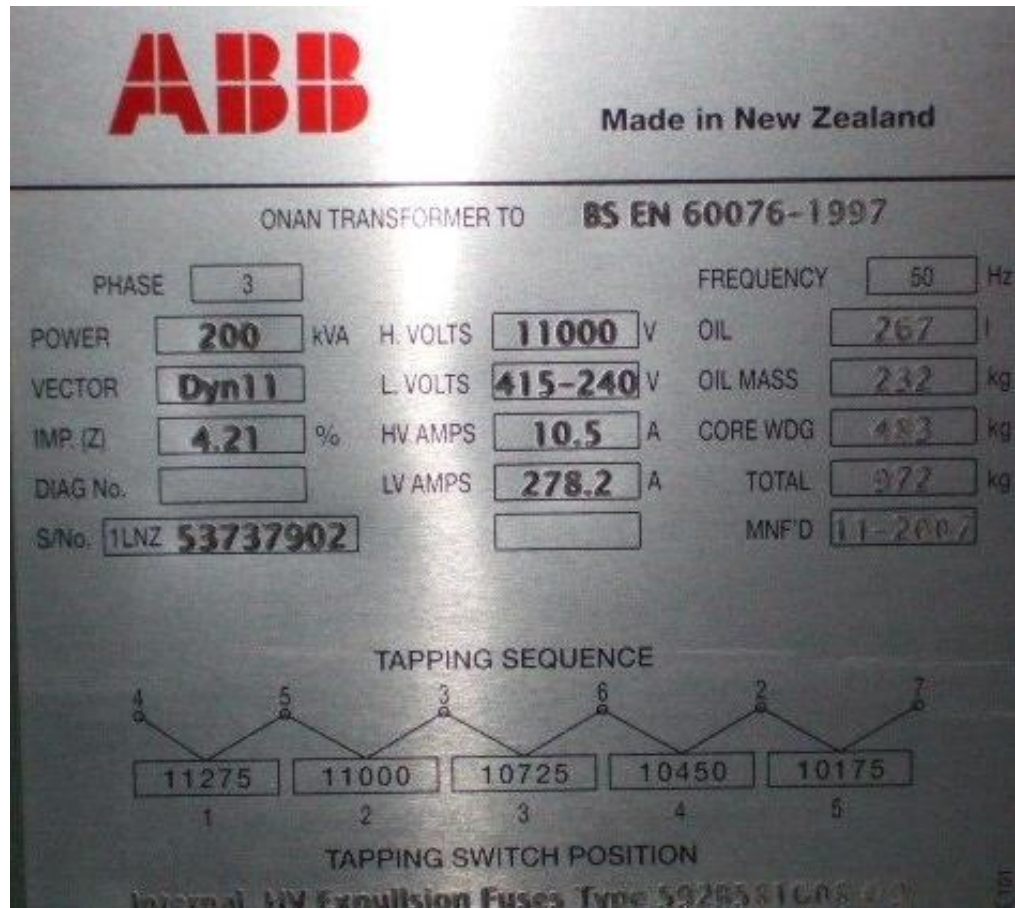



## A good transformer should have:

- ✓ **high permeability:**  
the core is made of iron, and therefore small magnetising current
- ✓ **low iron losses:**  
core is laminated (high resistivity silicon steel or soft ferrite)
- ✓ **small leakage reactance:**  
the primary and secondary coils on top of each other
- ✓ **low winding resistances:**  
reduced  $I^2 R$  loss (heat), and  $\rightarrow$  higher efficiency
- ✓ **conductors:**  
aluminium, copper, and heavier insulation