

At Supernode 1-2,

KCL  $i_3 + 10 = i_1 + i_2$

or node voltages;  $\frac{V_3 - V_2}{6} + 10 = \frac{V_1 - V_4}{3} + \frac{V_1}{2}$



$$\Rightarrow 5V_1 + V_2 - V_3 - 2V_4 = 60 \quad \text{--- ①}$$

At Supernode 3-4,

$$i_1 = i_3 + i_4 + i_5$$

$$\Rightarrow \frac{V_1 - V_4}{3} = \frac{V_3 - V_2}{6} + \frac{V_4}{1} + \frac{V_3}{4} \quad \text{--- ②}$$
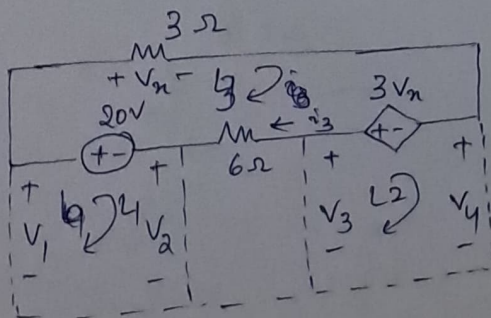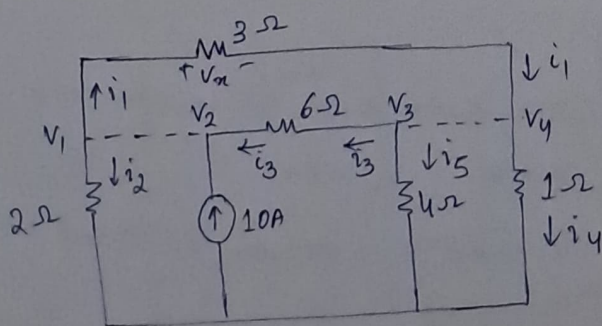
$$\Rightarrow 4V_1 + 2V_2 - 5V_3 - 16V_4 = 0 \quad \text{--- ②}$$



For LOOP 1  $-V_1 + 20 + V_2 = 0 \Rightarrow V_1 - V_2 = 20 \quad \text{--- ③}$

L2  $-V_3 + 3V_x + V_4 = 0 \quad (\because V_x = V_1 - V_4)$

$$\Rightarrow 3V_1 - V_3 - 2V_4 = 0 \quad \text{--- ④}$$

L3  $V_x - 3V_x + 6i_3 - 20 = 0 \quad (\because 6i_3 = V_3 - V_2; V_x = V_1 - V_4)$

$$\Rightarrow -2V_1 - V_2 + V_3 + 2V_4 = 20 \quad \text{--- ⑤}$$

→ So, total '5' equations but '4' unknowns

$$(V_1, V_2, V_3, V_4)$$

Substituting '3' in '1' & '2'.

$$6V_1 - V_3 - 2V_4 = 80 \quad \text{--- (6)}$$

$$\text{and } 6V_1 - 5V_3 - 16V_4 = 40 \quad \text{--- (7)}$$

eqn (4), (6) & (7) in matrix form

$$\begin{bmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{bmatrix} \begin{bmatrix} V_1 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 80 \\ 40 \end{bmatrix}$$


By Solving it  $\Rightarrow V_1 = 26.67 \text{ V}$

$$V_3 = 173.33 \text{ V}$$

$$V_4 = -46.67 \text{ V.}$$

Then  $V_2 = V_1 - 20 = 6.667 \text{ V.}$

Q2

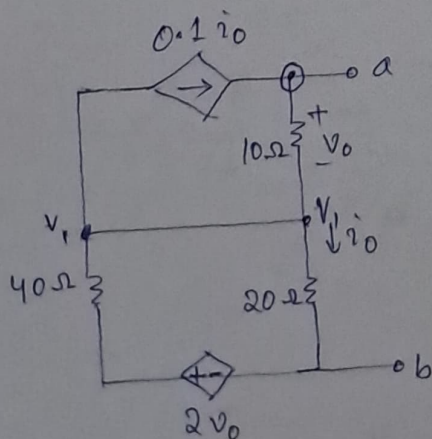


\* Since there are no independent sources,  $V_{th} = 0 \text{ V.}$

\* To obtain  $R_{th}$ , consider the circuit below.

This is doubt.  
How 1V??

→

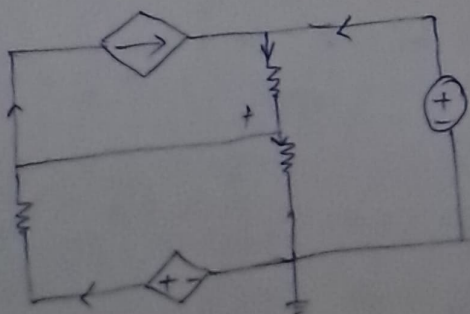

At node 2

$$i_o + 0.1i_o = (1 - V_1)/10$$

$$\text{or } 10i_o + i_o = 1 - V_1 \quad \text{--- (1)}$$

node 1

$$V_1/20 + 0.1i_o = \frac{(2v_o - V_1)}{40} + \frac{(1 - V_1)}{10}$$

--- (2)



(2)

$$i_o = \frac{V_1}{20} \quad \text{and} \quad V_o = 1 - V_1$$

eqn (2)  $1 \cdot 1 \cdot V_1/20 = [(2 - 3V_1)/40] + [(1 - V_1)/10]$

$$\Rightarrow 2 \cdot 2 V_1 = 2 - 3V_1 + 4 - 4V_1 = 6 - 7V_1$$

$$\Rightarrow V_1 = 6/9.2, \quad \text{--- (3)}$$




eqn (1) &amp; (3)

$$10 i_x + \frac{V_1}{20} = 1 - V_1$$

$$\Rightarrow 10 i_x = 1 - V_1 - \frac{V_1}{20} = 1 - \left(\frac{21}{20}\right) V_1 = 1 - \left(\frac{21}{20}\right) (6/9.2)$$

$$\Rightarrow i_x = 31.52 \text{ mA}; \quad R_{th} = \frac{1}{i_x} = 31.73 \text{ Ohms}$$

(3) (4)

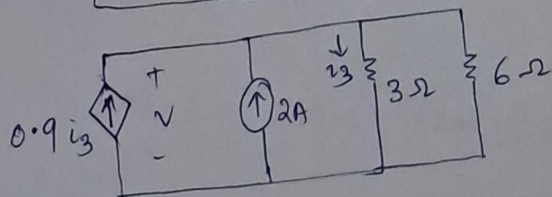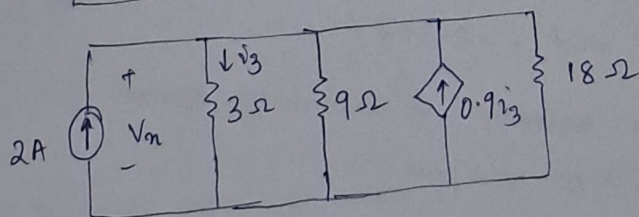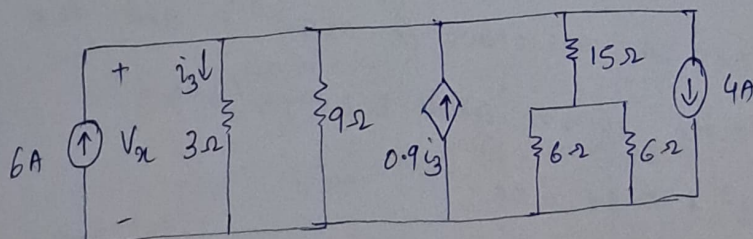

$$-0.9i_3 - 2 + i_3 + \frac{V}{6} = 0 \quad ; \quad V = 3i_3$$

$$\Rightarrow i_3 \neq 0$$

$$\Rightarrow i_3 = \frac{10}{3} \text{ A}$$

$$V = 3i_3 = 10 \text{ V}$$


$$\text{Power} = V \times 0.9i_3 \Rightarrow 10 (0.9) \left(\frac{10}{3}\right)$$

Dependent Source

$$= 30 \text{ W}$$

Then Tellegen Theorem

Q5

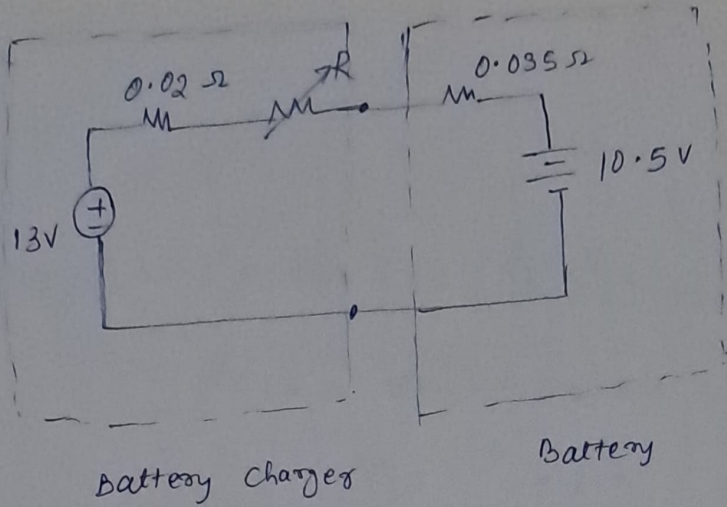

'R' = ? (a) Charging current of 4A flows

$$-13 + 0.02i + Ri + 0.035i + 10.5 = 0$$

required  $i = 4A$  ;  $R = 570m\Omega$ .

(b) The total power delivered to the battery consists of the power absorbed by the  $0.035\Omega$  resistance ( $0.035i^2$ ) and the power absorbed by the  $10.5V$  ideal battery ( $10.5i$ ).

$$0.035i^2 + 10.5i = 25$$

$$i = -302.4A \text{ and } i = 2.362A$$

idea is to charge the battery  $\Rightarrow$  absorbing power  $\Rightarrow$  'i' is positive

$$i = 2.362A$$

$$R = [13 - 10.5 - 0.055(2.362)] / 2.362 = 1.003\Omega$$

(c) To obtain a voltage of 11V across the battery, we apply KVL


$$0.035i + 10.5 = 11 \text{ so that } i = 14.29A$$

$$R = [13 - 10.5 - 0.055(14.29)] / 14.29 = 119.9m\Omega$$



③

Q6

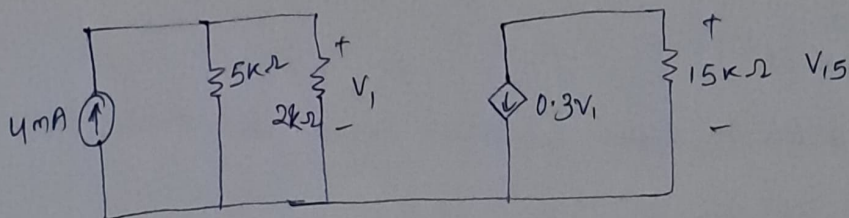

$$P_{15\Omega} = \frac{(V_{15})^2}{15 \times 10^3}$$


$$V_{15} = 15 \times 10^3 (-0.3V_1)$$

$$\text{where } V_1 = \left[ \frac{4 \times 5}{5+2} \right] \cdot 2 = 5.714 \text{ V}$$

$$\text{Therefore } V_{15} = -25714 \text{ V}$$



$$\text{and } P_{15} = 44.08 \text{ kW}$$

Q7

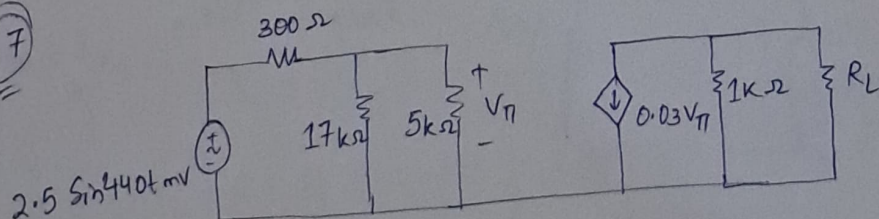

MPT for  $R_L$

→ Thevenin eq<sup>n</sup> → since it is asked ' $R_L$ '

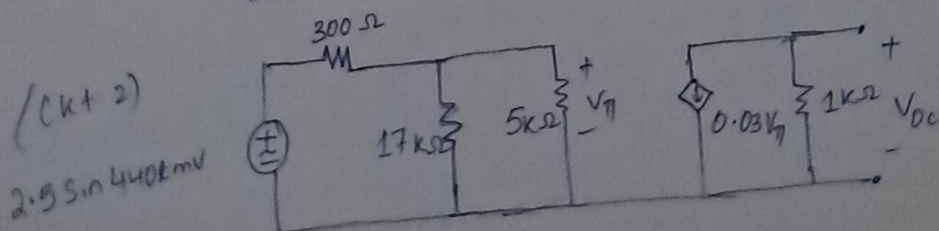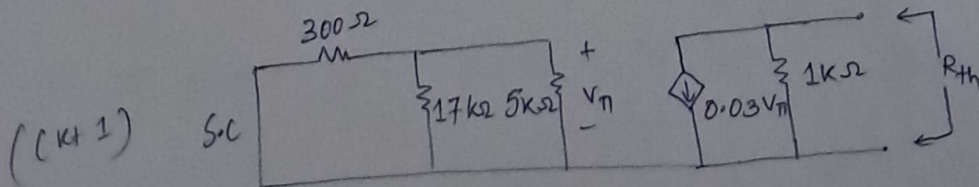

(Ckt 1)

Since  $V_{\pi} = 0$ , the dependent current source is an open circuit

$$R_{th} = 1k\Omega$$

So, in order to obtain maximum power delivered into the load

$R_L$  should be set to  $R_{th} = 1k\Omega$


(Ckt 2)

$$V_{oc} = -0.03 V_{\pi} (1000) = -30 V_{\pi}$$

$V_{\pi}$  can be found from voltage division

$$V_{\pi} = (2.5 \times 10^{-3} \sin 440t) \left( \frac{3864}{300 + 3864} \right)$$

$$V_{oc} = -69.6 \sin 440t \text{ mV}$$

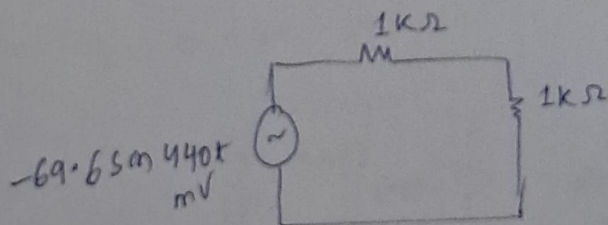

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = 1.211 \sin^2 440t \text{ mW}$$


⑨

$$\text{No. of loops} = 6 - 7 + 1$$

$$= 8 - 5 + 1 = 4 \quad (\text{minimum no. of eqs})$$



Q2

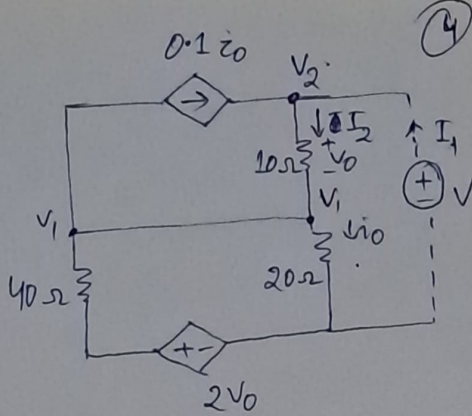

$$R_{th} = \frac{V}{I_1}$$

$$I_2 = I_1 + 0.1 i_0 \quad \text{--- (1)}$$

$$V_0 = I_2 \times 10 \Omega = (I_1 + 0.1 i_0) 10 \quad \text{--- (2)}$$

$$V_2 - V_0 = V_1 \quad \text{--- (3)}$$

$$V = V_2 - V_0 - V_1 - 20 i_0 \quad \text{--- (4)}$$

$$I_1 + 0.1 i_0 = \frac{V_2 - V_1}{10} \quad \text{--- (5)}$$

$$\Rightarrow 10 I_1 + 0.1 i_0 = V_2 - V_1 \quad \text{--- (6)}$$

$$\frac{V_1}{20} + 0.1 i_0 = \frac{2V_0 - V_1}{40} + \frac{V_2 - V_1}{10}$$

$$\frac{i_0}{20} = \frac{V_1}{20} ; V_0 = V_2 - V_1$$

$$10 I_1 + 0.1 i_0 = V_2 - \frac{i_0}{20}$$

$$\Rightarrow 200 I_1 + 2 i_0 = 20 V_2 - i_0 \Rightarrow 200 I_1 + 3 i_0 = 20 V_2$$

$$\frac{20 i_0}{20} + 0.1 i_0 = \frac{2V_0 - 20 i_0}{40} + \frac{V_0}{10}$$

$$\Rightarrow 1.1 i_0 = \frac{2V_0 - 20 i_0 + 4V_0}{40} \Rightarrow 1.1 i_0 \times 40 = 6V_0 - 20 i_0$$

$$\frac{V_0}{i_0} = \frac{64}{6}$$

$$200 I_1 + 3 i_0 = 20 V - 400 i_0 + 20 V_1$$

$$\Rightarrow 200 I_1 + 403 i_0 = 20 V + 20 V_1$$

$$\Rightarrow 200 I_1 + 403 i_0 = 20 V + 400 i_0$$

$$\Rightarrow 200 I_1 + 3 i_0 = 20 V$$

$$\Rightarrow 200 + 3 \frac{i_0}{I_1} = 20 R_{th}$$

$$i_0 = \frac{V_1}{20}$$

$$\Rightarrow R_{th} = 10 + 3 \frac{i_0}{I_1}$$

$$V = V_0 + 20 i_0$$

$$R_{th} = 10 + 3 \frac{i_0}{0.1 i_0 + I_2}$$

$$R_{th} = 10 + \frac{3 i_0}{0.1 i_0 + \frac{V_0}{10}} = 10 + \frac{30 i_0}{i_0 + V_0}$$

$$\text{--- (7)}$$

$$= \frac{40 i_0 + 10 V_0}{i_0 + V_0}$$

$$\Rightarrow R_{th} = \frac{40 + 10 V_0 / i_0}{1 + V_0 / i_0} = 20 \frac{(V_0 + V_1)}{(V - 20 i_0 + V_1)}$$

$$\Rightarrow 200 I_1 + 3 i_0 = 20 (V - 20 i_0 + V_1)$$

$$\Rightarrow 44 i_0 + 20 i_0 = 6 V_0$$

$$\Rightarrow \frac{64}{6} i_0 = V_0$$

$$R_{th} = \frac{40 + 10 \left( \frac{64}{6} \right)}{1 + \left( \frac{64}{6} \right)}$$

$$= \frac{40 + \frac{640}{6}}{1 + \frac{64}{6}} = \frac{\frac{240 + 640}{6}}{\frac{69}{6}} = \frac{880}{69} = \underline{12.75 \text{ ohms}}$$