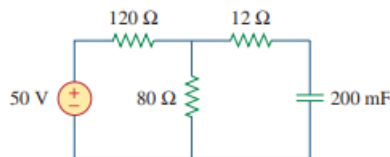


(Chapter-07) First order circuits


Practice Problems

The Source-Free RC Circuit

Q1. Find the time constant for the RC circuit in Fig given below.



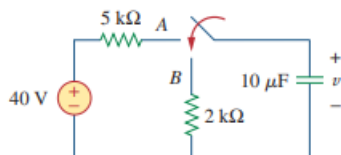
Q2. The switch in Fig. below has been in position A for a long time. Assume the switch moves instantaneously from A to B at $t=0$. Find V for $t>0$.




Q3. For the given circuit, if:

$$v = 10e^{-4t} \text{ V} \quad \text{and} \quad i = 0.2 e^{-4t} \text{ A}, \quad t > 0$$

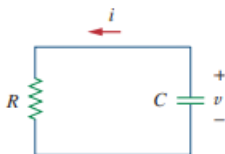- (a) Find R and C .
- (b) Determine the time constant.
- (c) Calculate the initial energy in the capacitor.
- (d) Obtain the time it takes to dissipate 50 percent of the initial energy.




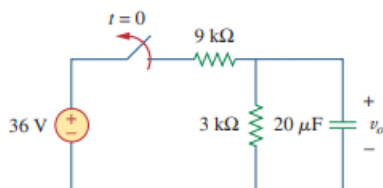Q4. For the given circuit, find $V_o(t)$ for $t>0$. Determine the time necessary for the capacitor voltage to decay to one-third of its value at $t = 0$.




The Source-Free RL Circuit

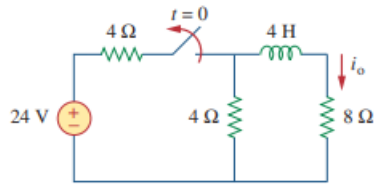Q1. For the circuit given, find i_o for $t > 0$.



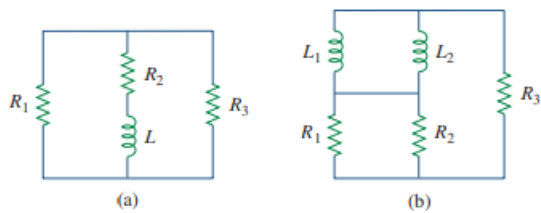Q2. Determine the time constant for each of the circuits.




Q3. In the circuit of Fig given below:

$$v(t) = 80e^{-10^3 t} \text{ V}, \quad t > 0$$


$$i(t) = 5e^{-10^3 t} \text{ mA}, \quad t > 0$$

(a) Find R , L , and τ .

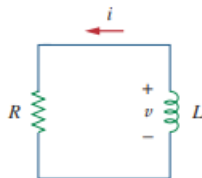(b) Calculate the energy dissipated in the resistance for $0 < t < 0.5 \text{ ms}$.





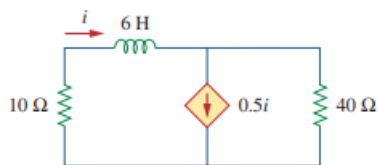Q4. In the given circuit, find $i(t)$ for $t > 0$ if $i(0) = 6 \text{ A}$.




Step Response of an RC Circuit

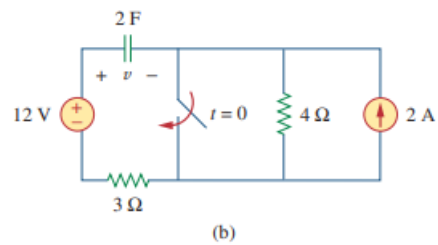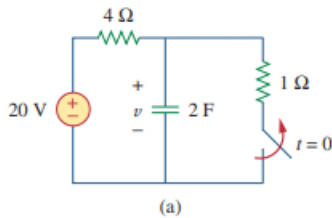Q1. Calculate the capacitor voltage for $t < 0$ and $t > 0$ for each of the circuits given below:




Q2. (a) If the switch in Fig has been open for a long time and is closed at $t = 0$, find $V_o(t)$


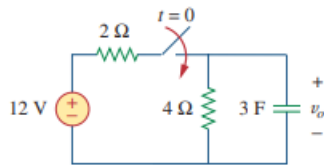
(b) Suppose that the switch has been closed for a long time and is opened at $t = 0$, Find $V_o(t)$.



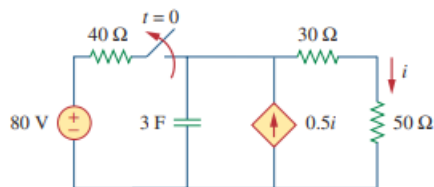Q3. Consider the circuit in Fig given below, Find $i(t)$ for $t < 0$ and $t > 0$.




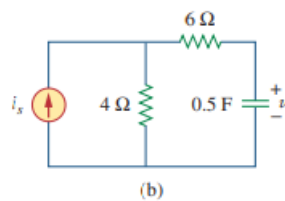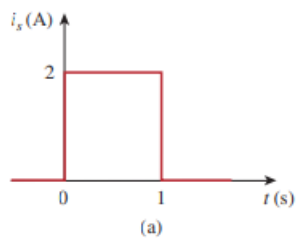Q4. If the waveform in Fig(a) is applied to the circuit of Fig(b), find $V(t)$. Assume $V(0) = 0$.




Step Response of an RL Circuit

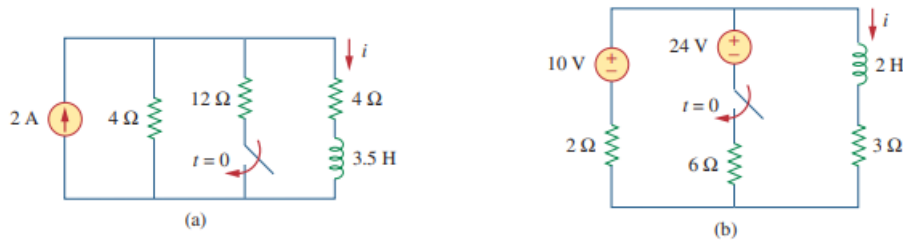
Q1. Obtain the inductor current for both $t < 0$ and $t > 0$ in each of the circuits given below.



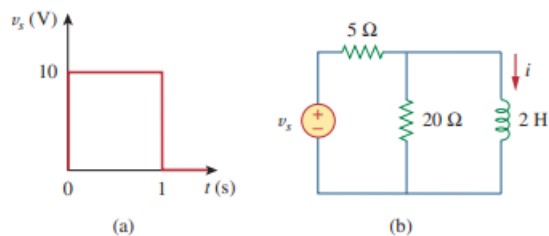Q2. If the input pulse in Fig(a) is applied to the circuit in Fig(b), determine the response $i(t)$



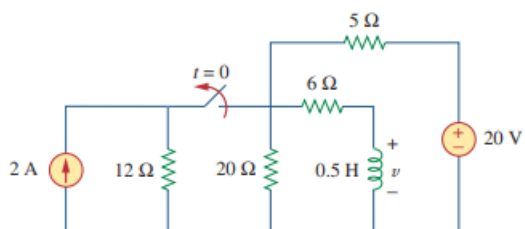Q3. For the network shown in Fig, find $V(t)$ for $t > 0$.



Q4. Switch S_1 in fig is closed at $t = 0$, and switch S_2 is closed at $t = 2$ s. Calculate $i(t)$ for all t .

Also find $i(1)$ and $i(3)$.

