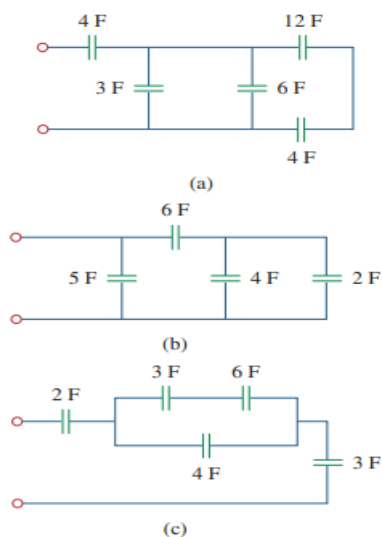


(Chapter-06) CAPACITORS

Practice Problems


Q1. Determine the equivalent capacitance for each of the circuits given below.



(Ans: 3F, 8F, 1F)

Q2. A voltage of $30e^{-2000t}$ appears across a parallel combination of a 100-mF capacitor and a 12Ω resistor. Calculate the power absorbed by the parallel combination. **(Ans: $-179.925e^{-4000t}$ W)**

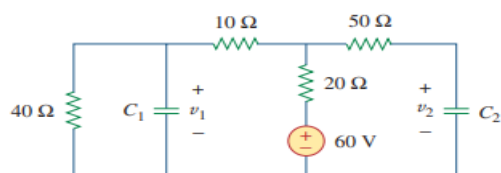
Q3. Find the voltage across the capacitors in the circuit of Fig given below under dc conditions.




(Ans: $v_1=42V$, $v_2=48V$)

Q4. For the given circuit, determine:

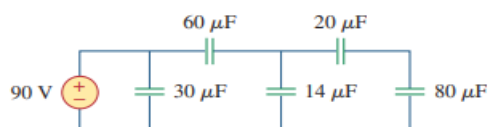- (a) the voltage across each capacitor and
- (b) the energy stored in each capacitor.



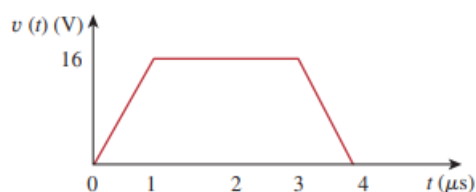Q5. A 4-mF capacitor has the current waveform shown in Fig. Assuming that $V(0)=10V$, sketch the





voltage waveform $V(t)$.

(Chapter-05) INDUCTOR

Practice Problems

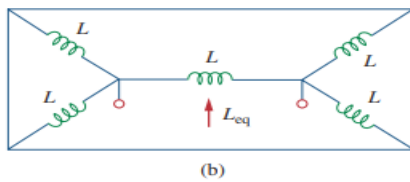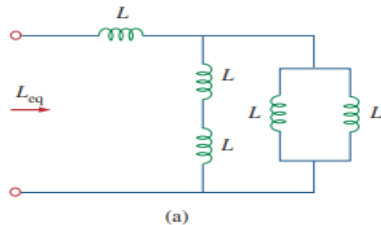Q1. Find L_{eq} in each of the circuits given below:




(Ans: 1.4L, 500mL)

Q2. The current $i(t)$ through a 20-mH inductor is equal in magnitude, to the voltage across it for all values of time. If $i(0)=2A$, find $i(t)$.


(Ans: $25e^{50t}A$)

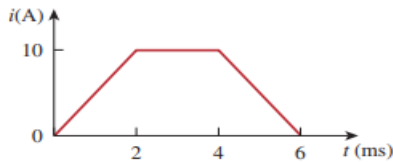Q3. The current through a 5-mH inductor is shown in Fig. 6.66. Determine the voltage across the inductor at $t=1, 3$ and $5ms$.




(Ans: 25V, 0V, -25V)

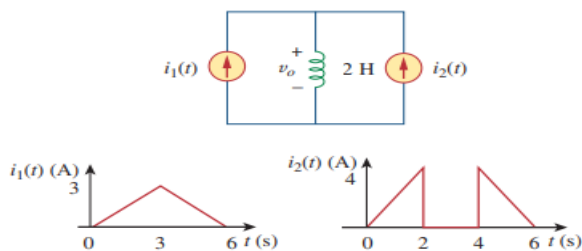Q4. In the circuit of given Fig, sketch v_o .



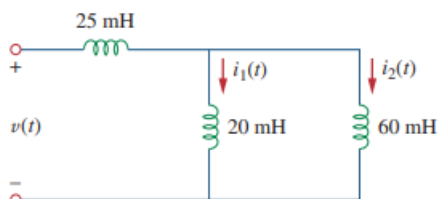Q5. Consider the circuit in Fig. given below. Given that $V(t)=12e^{-3t}$ mV for $t>0$ and $i_1(0) = -10mA$, find: (a) $i_2(0)$, (b) $i_1(t)$ and (c) $i_2(t)$.




(Ans: (-3.33) mA), $(-75e^{-3t}+65) A$, $(-25 e^{-3t}+21.67) A$)

(Chapter-04) Max. Power Transfer


Practice Problems

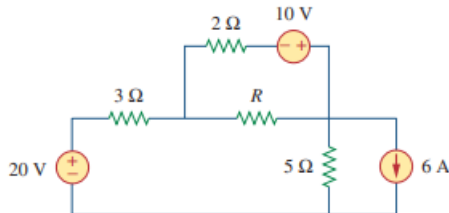Q1. Find the maximum power that can be delivered to the resistor R in the circuit.



(Ans: 625mW)

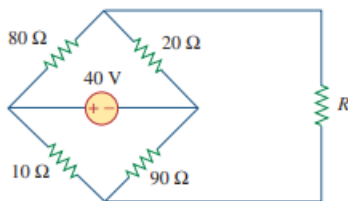Q2. The variable resistor R in Fig. given is adjusted until it absorbs the maximum power from the circuit.



(a) Calculate the value of R for maximum power.

(Ans: 25Ω)

(b) Determine the maximum power absorbed by R .

(Ans: 7.84W)

Q3. (a) For the circuit below, obtain the Thevenin equivalent at terminals a-b. (Ans: 12Ω)

(b) Calculate the current in load resistance $R_L=8Ω$ (Ans: 2V)

(c) Find R_L for maximum power deliverable to R_L (Ans: 12Ω)

(d) Determine that maximum power. (Ans: 33.33W)

