

Assignment - 1 EC23B1066

Given, $v = 10 \sin(4\pi t) \text{ V}$
 $v = 2 \cos(4\pi t) \text{ V}$

To find : a) power delivered to the element at
 $t = 0.35$
 b) calculate the energy delivered to the element b/w 0 & 0.6s

Solⁿ

a) $P(t) = v(t) \times i(t)$

$$P(t) = 2 \cos(4\pi t) \times 10 \sin(4\pi t) \text{ (as } 4\pi t)$$

$$P(t) = 80 \pi \cos^2(4\pi t)$$

$$P(t) = 80\pi \left(\frac{\cos(8\pi t) + 1}{2} \right)$$

$$P(0.3) = 80\pi \left(\frac{\cos(2.4\pi) + 1}{2} \right)$$

$$P(0.3) = 80\pi \times 0.6545 = 164.4759 \text{ mW}$$

b) $\Delta E = \int_0^{0.6} 80\pi \left(\frac{\cos(8\pi t) + 1}{2} \right) dt$

$$= 40\pi \int_0^{0.6} (\cos(8\pi t) + 1) dt$$

$$= 40\pi \times \left[\frac{\sin(8\pi t)}{8\pi} + t \right]_0^{0.6}$$

$$= 40\pi \times \left(\frac{0.5878}{8\pi} + 0.6 \right)$$

$$= 40\pi \times 0.6234$$

$$= 78.3372 \text{ mJ}$$

Given : Burner 1 : 20 minutes

Burner 2 : 40 minutes

Burner 3 : 15 minutes

Burner 4 : 45 minutes

Oven : 30 minutes

Solⁿ

Burner-1 $H = 1.2 \times \frac{20}{60} = 0.4 \text{ kwh}$

Burner-2 $H = 1.2 \times \frac{40}{60} = 0.8 \text{ kwh}$

$$\text{Burner 3} \quad H = 1.2 \times \frac{15}{60} = 0.3 \text{ kWh}$$

$$\text{Burner 4} \quad H = 1.2 \times \frac{45}{60} = 0.9 \text{ kWh}$$

$$\text{Oven} \quad H = 1.8 \times \frac{30}{60} = 0.9 \text{ kWh}$$

$$\text{Total Energy Used} = (0.4 + 0.8 + 0.3 + 0.9 + 0.9) \\ = 3.3 \text{ kWh}$$

$$\text{Total Cost} = 3.3 \times (0.12) \\ = \text{£} 0.396$$



(3) a) Total Energy Consumed in kWh

$$= 200 \times 18 + 800 \times 2 + 1200 \times 4 \\ = 3600 + 1600 + 4800 \\ = 10000 \text{ Wh} \\ = 10 \text{ kWh}$$

b) Average power per hours

$$= \frac{10}{24} \text{ kW} = 0.4167 \text{ kW}$$

(4) To find i_1 and i_4

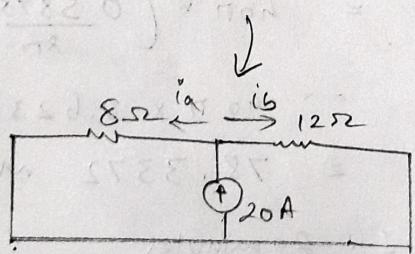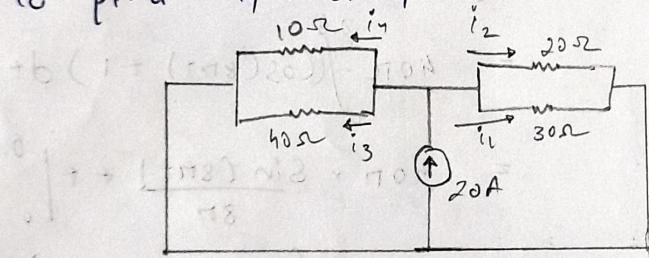

Applying Current division


$$i_a = \frac{12}{20} \times 20 = 12$$

$$i_b = \frac{8}{20} \times 20 = 8$$

$$\text{So } i_4 = \frac{40 \times 12}{50} = 9.6 \text{ A}$$

$$i_1 = \frac{20 \times 8}{50} = 3.2 \text{ A}$$


(5)

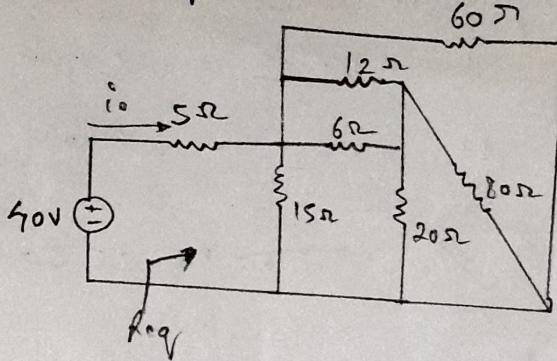To find R_{eq} & I_o in the circuit

Sol


$$\Rightarrow 20//80$$

$$R_{eq} = 16\Omega$$

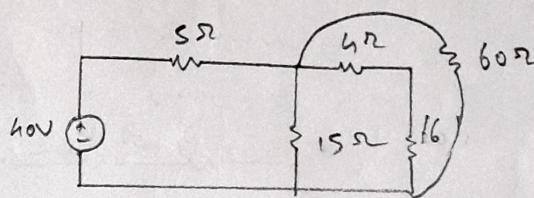


$$\Rightarrow 6//12$$

$$R_{eq} = 4$$

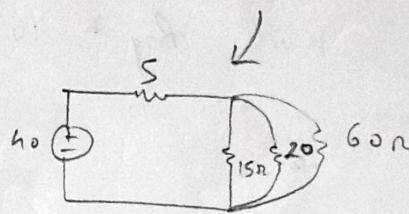


$$\Rightarrow 20//60$$

$$R_{eq} = 15$$

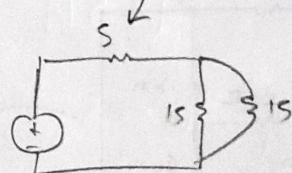

$$\Rightarrow 15//15$$

$$R_{eq} = 15/2$$

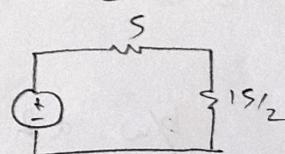 \rightarrow 5 series with $15/2$

$$R_{eq} = 12.5$$



$$R_{eq} = 12.5$$

$$I_o = \frac{40}{25/2} = \frac{16}{5}$$


6

Find the equivalent resistance in the Circuit

a>

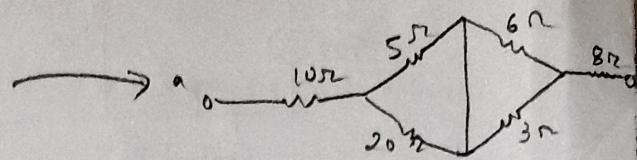
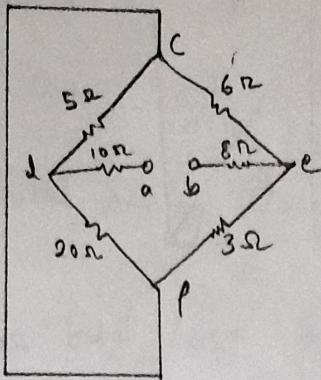

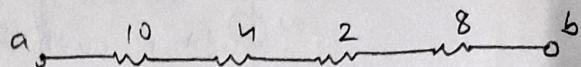
$$\Rightarrow 20//5 \text{ & } 6//3 \\ R_{eq} = 4\Omega \quad R_{eq} = 2\Omega$$



$$R_{eq} = 10 + 4 + 2 + 8 = 24\Omega$$


b>

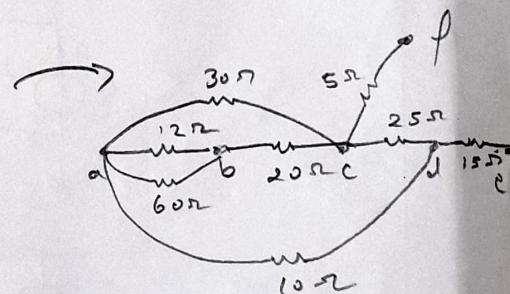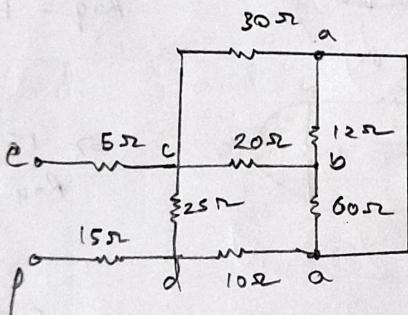

b/w a & b



$$\Rightarrow 12 // 60$$

$$R_{eq} = 10$$

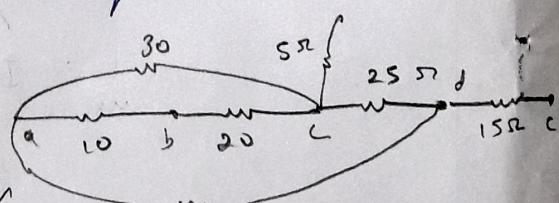

10Ω & 20Ω in series

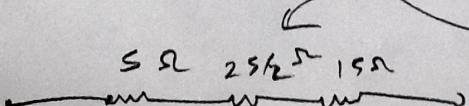
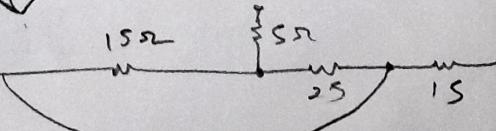
$$\text{then } 30\Omega // 30\Omega \\ = 15\Omega$$




$$R_{eq} = \frac{65}{2}$$

7

To obtain equivalent resistance

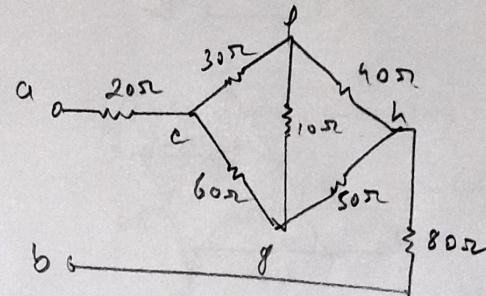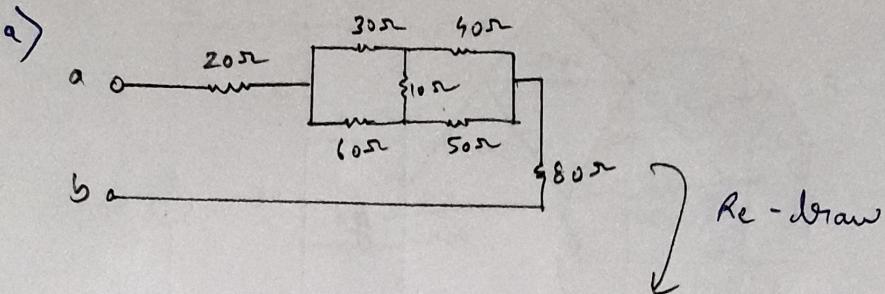


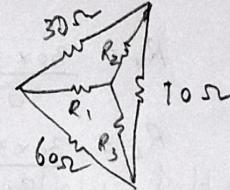
Using ~~Star~~ Delta \rightarrow Star on c/f/g



$$R_1 = \frac{30 \times 60}{30 + 60 + 10} = 18 \Omega$$



$$R_2 = \frac{30 \times 10}{100} = 3 \Omega$$
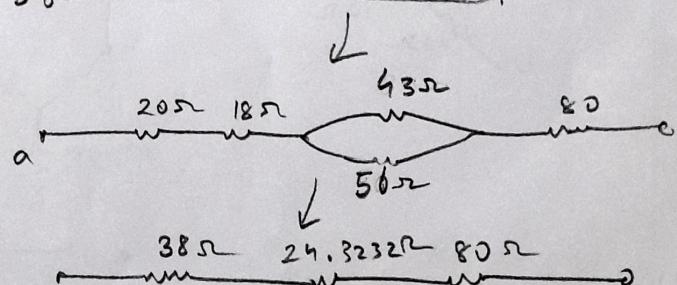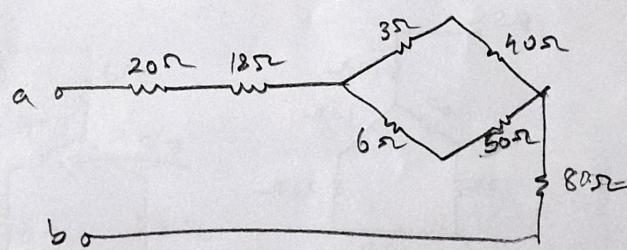
$$R_3 = \frac{60 \times 10}{100} = 6 \Omega$$



$$142.3232$$

$$R_{eq} = 142.3232$$

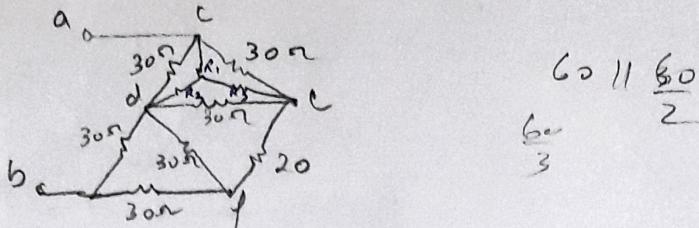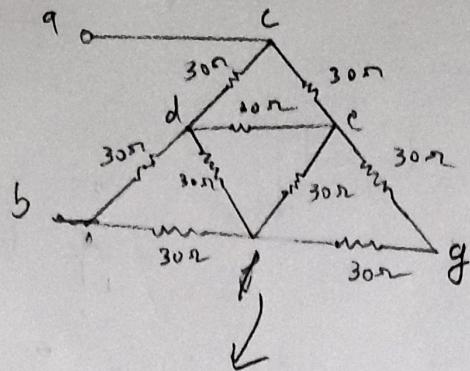

Delta \rightarrow Star on cde


$$R_1 = \frac{30 \times 30}{90} = 10 \Omega$$

$$R_2 = \frac{30 \times 30}{90} = 10 \Omega$$

$$R_3 = \frac{30 \times 30}{90} = 10 \Omega$$


Delta \rightarrow Star on dbf
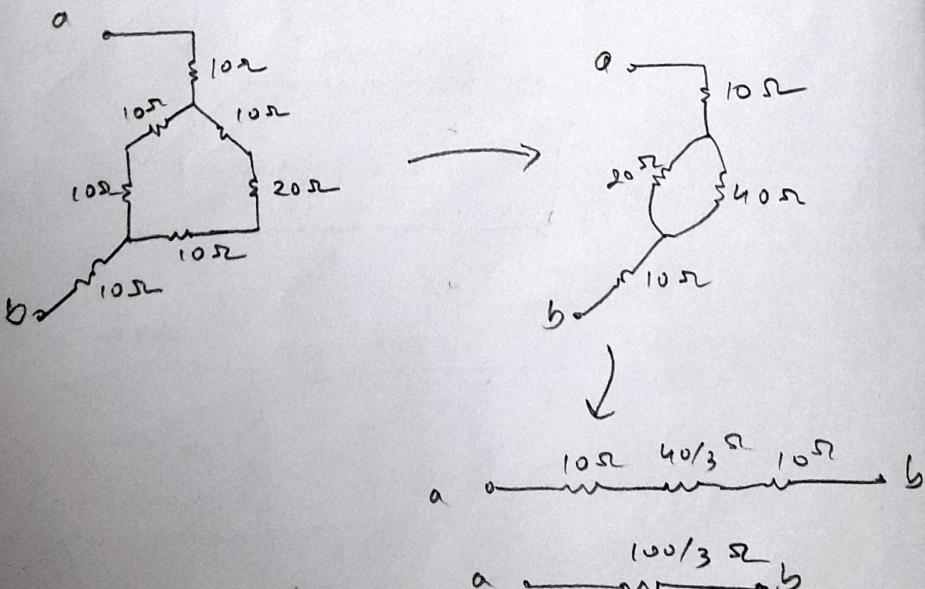
$$R_1 = R_2 = R_3 = \frac{30 \times 30}{90} = 10 \Omega$$



$$R_{eq} = 100/3 \Omega$$

(8)

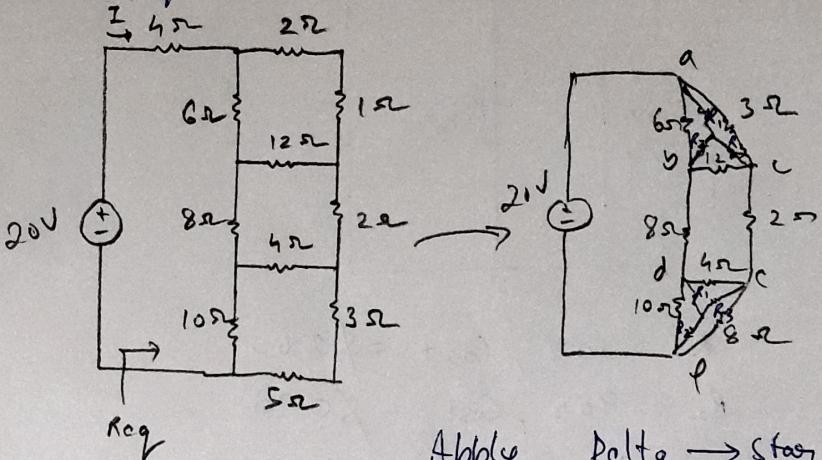To find R_{eq} & I in the circuitApply Delta \rightarrow Star on abc

$$R_1 = \frac{6 \times 3}{21} = 6/7$$

$$R_2 = \frac{26 \times 12}{21} = 24/7$$


$$R_3 = \frac{12 \times 3}{21} = 12/7$$

Apply Delta \rightarrow Star on dcf

$$R_1 = \frac{4 \times 10}{22/11} = \frac{20}{11}$$

$$R_2 = \frac{10 \times 8}{22/11} = \frac{40}{11}$$

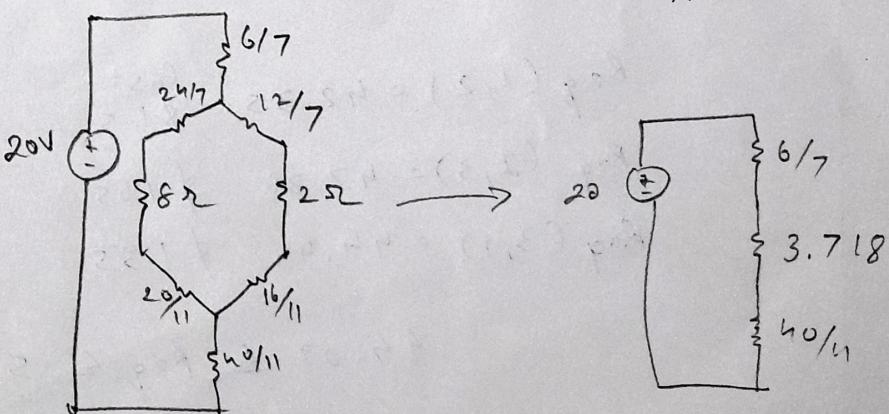
$$R_3 = \frac{4 \times 8}{22/11} = \frac{16}{11}$$



$$R_{eq} = 8.2115$$

$$I = \frac{V}{R_{eq}} = \frac{20}{8.2115} = 2.4356A$$

(9)

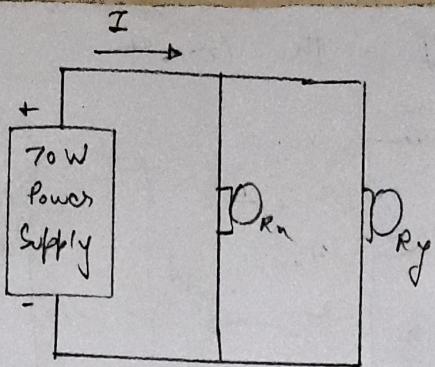

$$R_1 = 80\Omega, \text{ Cost} = \$0.60$$

$$R_2 = 90\Omega, \text{ Cost} = \$0.90$$

$$R_3 = 100\Omega, \text{ Cost} = \$0.75$$

$I = 1.2 A \pm 5$ [System should be designed for minimum cost such that lies within the range]

i> Let

$$I = 1.2 + \frac{5}{100} \Rightarrow \frac{95}{100} I = 1.2 \Rightarrow I = 1.263 A$$

$$P = I^2 R_{eq}, \quad R_{eq} = \frac{70}{(1.263)^2} = 44.1 \Omega$$

ii> Let $I = 1.2 - \frac{5I}{100}, \quad I = 1.14 A$

$$R_{eq} = \frac{70}{(1.14)^2} = 53.86 \Omega \quad R_1 = 80 \\ R_2 = 90$$

$$R_{eq}(1,2) = 42.35 \quad \text{Cost} \quad \$1.5 \quad R_3 = 100$$


$$R_{eq}(2,3) = 47.36 \quad \$1.65$$

$$R_{eq}(3,1) = 44.44 \quad \$1.35$$

$$44.09 \leq R_{eq} \leq 53.86 \Omega$$

Since R_1 & R_3 cost is minimum and it lies in range, we should use that.

x 10

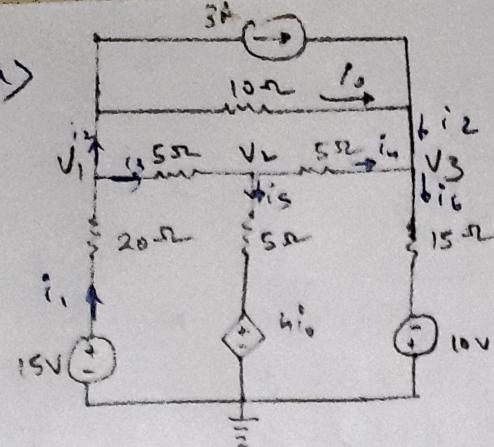

$$i_0 = \frac{V_1 - V_3}{10}$$

$$i_1 = \frac{15 - V_1}{20}$$

$$i_2 = 3 + \frac{V_1 - V_3}{10}$$

$$i_3 = \frac{V_1 - V_2}{5}$$

$$i_4 = \frac{V_2 - V_3}{5}$$

$$i_5 = \frac{V_2 - 4i_6}{5}$$

$$i_6 = \frac{V_3 + 10}{15}$$

$$i_5 = \frac{V_2 - 4(V_1 - V_3)}{5}$$

Using KCL at node 1

$$i_1 = i_2 + i_3$$

$$\frac{15 - V_1}{20} = 3 + \frac{V_1 - V_3}{10} + \frac{V_1 - V_2}{5}$$

$$\frac{15 - V_1}{20} - \frac{V_1 + V_3}{10} - \frac{V_2 + V_1}{5} = 3$$

$$-V_1 + 15 + 2V_3 - 2V_1 + 4V_3 - 6V_1 = 60$$

$$-7V_1 + 4V_2 + 2V_3 = 45$$

Using KCL at node 2

$$i_3 = i_4 + i_5$$

$$\frac{V_1 - V_2}{5} = \frac{V_2 - V_3}{5} + \frac{5V_2 - 2V_1 + 2V_3}{25}$$

$$5V_1 - 5V_2 = 5V_2 - 5V_3 + 5V_2 - 2V_1 + 2V_3$$

$$7V_1 - 15V_2 + 3V_3 = 0$$

Using KCL at node 3

$$i_6 = i_4 + i_2$$

$$\frac{V_3 + 10}{15} = \frac{V_2 - V_3}{5} + 3 + \frac{V_1 - V_3}{10}$$


$$2V_3 + 20 + 6V_3 - 6V_2 + 3V_3 - 3V_1 = 90$$

$$-3V_1 - 6V_2 + 11V_3 = 70$$

$$\therefore V_1 = -7.2$$

$$V_2 = -2.77, V_3 = 2.88$$

b>

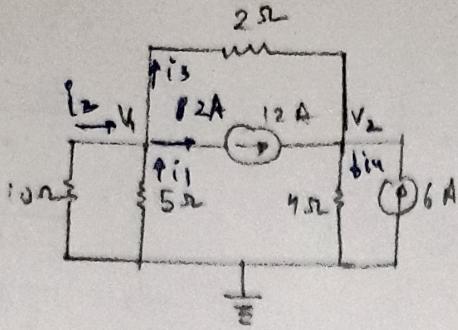

at node 1

$$i_1 + i_2 = 12 + i_3$$

$$-\frac{v_1}{5} - \frac{v_1}{10} = 12 + \frac{v_1 - v_2}{2}$$

$$-\frac{v_1}{5} - \frac{v_1}{10} + \frac{v_2 - v_1}{2} = 12$$

$$-2v_1 - v_1 + 5v_2 - 5v_1 = 120$$

$$-8v_1 + 5v_2 = 120$$

at node 2

$$12 + i_3 + 6 = i_4$$


$$12 + \frac{v_1 - v_2}{2} + 6 = \frac{v_2}{4}$$

$$\frac{2v_1 - 2v_2}{4} - \frac{v_2}{4} = -18$$

$$2v_1 - 3v_2 = -72$$

$$v_1 = 0V, v_2 = 24V$$

c>

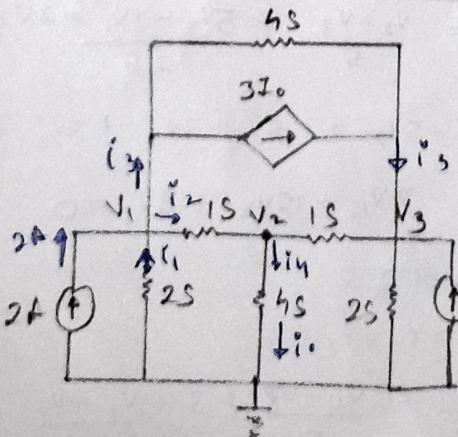

at node 1

$$2 - \frac{v_1 - v_2}{2} + 3(\frac{v_2}{2}) + (v_1 - v_3) = 0$$

$$2 - \frac{v_1 - v_2}{2} + v_1 + v_2 - 12v_2 - 4v_1 + 4v_3 = 0$$

$$-7v_1 - 11v_2 + 4v_3 = -2$$

at node 2

$$v_1 - v_2 = v_2 - v_3 + 4v_2$$

$$v_1 - 6v_2 + v_3 = 0$$

At node 3

$$3(v_2) + 4(v_1 - v_3) + v_2 - v_3 + 4 = 2v_3$$

$$12v_2 + 4v_1 - 4v_3 + v_2 - v_3 - 2v_3 = -4$$


$$4v_1 + 13v_2 - 7v_3 = -4$$

$$v_1 = 0.625$$

$$v_2 = 0.375$$

$$v_3 = 1.625$$

⑪ Find Φ_0 using nodal Analysis

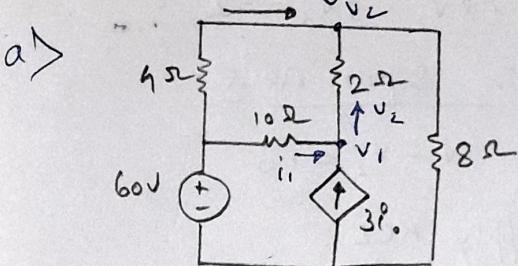

at node 1

$$\frac{60 - v_1}{10} + 3 \left(\frac{60 - v_2}{4} \right) = \frac{v_1 - v_2}{2}$$

$$\frac{60 - v_1}{10} + \frac{180 - 3v_2}{4} + \frac{v_2 - v_1}{2} = 0$$

$$120 - 2v_1 + 900 - 15v_2 + 10v_2 - 10v_1 = 0$$

$$-12v_1 - 5v_2 = -1020$$

$$12v_1 + 5v_2 = 1020$$

at node 2

$$\frac{60 - v_2}{4} + \frac{v_1 - v_2}{2} = \frac{v_2}{8}$$

$$\frac{60 - v_2}{4} + \frac{v_1 - v_2}{2} - \frac{v_2}{8} = 0$$


$$120 - 2v_2 + 4v_1 - 4v_2 - v_2 = 0$$

$$4v_1 - 7v_2 = -120$$

$$v_1 = 62.88$$

$$v_2 = 53.07$$

$$i_0 = \frac{60 - 53.07}{4} = 1.733 A$$

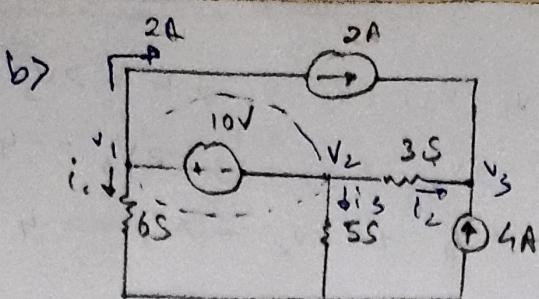

at Supernode

$$\begin{aligned} i_0 &= 6V_1 \\ i_2 &= (V_2 - V_3) \\ i_3 &= 5V_2 \end{aligned}$$

$$2 + i_0 + i_2 + i_3 = 0$$

$$2 + 6V_1 + 3(V_2 - V_3) + 5V_2 = 0$$

$$6V_1 + 8V_2 - 3V_3 = -2$$

KVL in Super node

$$V_1 - V_2 = 10$$

at node 3 Apply KCL

$$2 + i_2 + 4 = 0$$


$$2 + 3V_2 - 3V_3 + 4 = 0$$

$$3V_2 - 3V_3 = -6$$

$$V_1 = 4.9V, V_2 = -5.1V, V_3 = -3.1V$$

$$i_0 = 29.4A$$

(12)

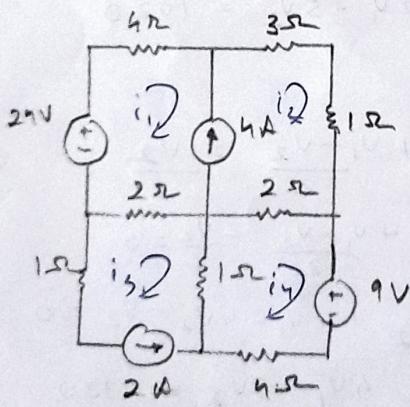

Using KVL in mesh -1

$$-2V + 4i_1 - 4 + 2(i_2 - i_3) = 0$$

$$6i_1 - 2i_3 = 28$$

$$3i_1 - i_3 = 14$$

In Mesh -2

$$3i_2 + 1i_2 + 2(i_2 - i_4) + 4 = 0$$

$$-2 + i_3 + 2(i_3 - i_1) + 1(i_3 - i_4) = 0$$

$$-2i_1 + 4i_3 - i_4 = 2$$

$$6i_2 - 2i_4 + 4 = 0$$

$$3i_2 - i_4 + 2 = 0$$

• In mesh - 4

$$9 + 4i_4 + (i_4 - i_3) + 2(i_4 - i_2) = 0$$

$$\boxed{1 - 2i_2 - i_3 + 7i_4 = -9}$$


~~Now~~ $\therefore i_1 = 5.68 \text{ A}, i_2 = -1.05 \text{ A}$

$$i_3 = 3.055 \text{ A}, i_4 = -1.15 \text{ A}$$

$$i_o = i_3 - i_4$$

$$i_o = 4.2 \text{ A}$$

b)

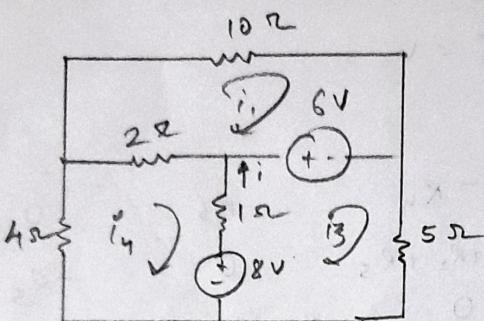

• in loop - 1

$$-6 + 2(i_1 - i_2) + 10i_1 = 0$$

$$12i_1 - 2i_2 = 6$$

• in loop - 2

$$8 + 4(i_2) + 2(i_2 - i_1) + i_2 - i_3 = 0$$

$$8 - 2i_1 + 7i_2 - i_3 = 0$$

• in loop - 3

$$5i_3 - 8 + (i_3 - i_2) + 6 = 0$$

$$-i_2 + 6i_3 = 2$$


$$i_1 = 0.35 \text{ A}, i_2 = -1.025, i_3 = 0.162$$

$$i_o = i_3 - i_2 = 0.162 + 1.025$$

$$\boxed{i_o = 1.187 \text{ A}}$$

13

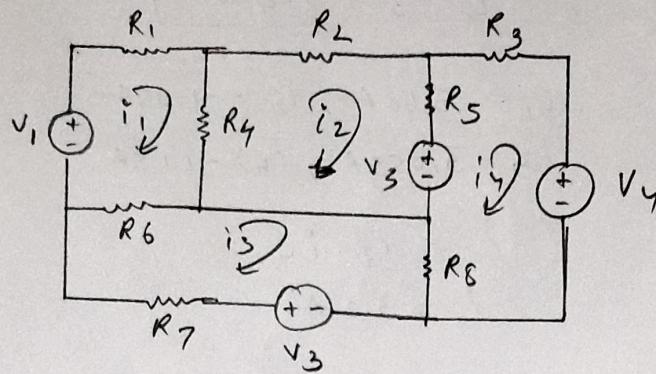By Inspection, obtain the mesh-current for the circuit in Fig.




$$RI = V$$

$$R = Z \times \frac{1}{3}$$

$$\left[\begin{array}{cccc} R_1 + R_2 + R_6 & -R_4 & -R_6 & 0 \\ -R_4 & R_3 + R_2 + R_5 & 0 & -R_5 \\ -R_6 & 0 & R_6 + R_8 + R_7 & -R_8 \\ 0 & -R_5 & -R_8 & R_5 + R_3 + R_8 \end{array} \right] \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \\ i_7 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ -V_4 + V_2 \end{bmatrix}$$

$$z = \begin{bmatrix} V_1 \\ -V_2 \\ V_3 \\ -V_4 + V_2 \end{bmatrix}$$

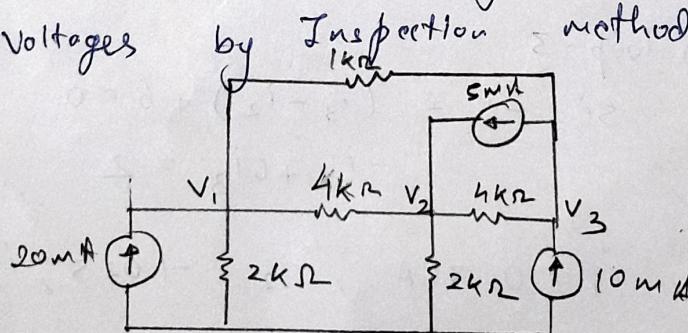for the circuit shown in fig, find the node voltages by Inspection method.



$$GIV = I$$

$$\left[\begin{array}{ccc} \frac{1}{4} & -\frac{1}{4} & -1 \\ -\frac{1}{4} & 2 & -\frac{1}{4} \\ -1 & -\frac{1}{4} & \frac{5}{4} \end{array} \right] \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \\ 5 \end{bmatrix}$$


$$\begin{bmatrix} 1.75 & -0.25 & -1 \\ -0.25 & 1 & -0.25 \\ -1 & -0.25 & 1.25 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \\ 5 \end{bmatrix}$$

$$v_1 = 36.43 \text{ V}$$

$$v_2 = 23.59 \text{ V}$$

$$v_3 = 37.85 \text{ V}$$

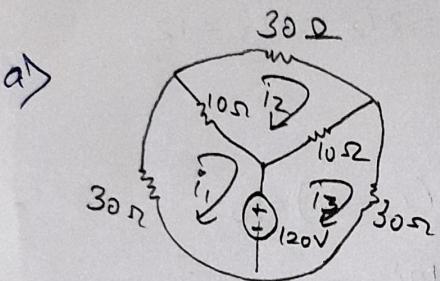(15) For the circuit shown in fig, find the mesh currents $i_1, i_2, \& i_3$.



$$RI = V$$

$$\begin{bmatrix} 40 & -10 & 0 \\ -10 & 50 & -10 \\ 0 & -10 & 40 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -120 \\ 0 \\ 120 \end{bmatrix}$$


By Solving this

$$i_1 = -3 \text{ A}$$

$$i_2 = 0$$

$$i_3 = 3 \text{ A}$$

6)

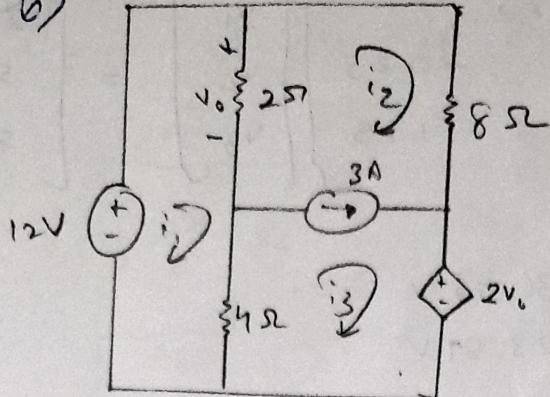

$$\begin{aligned} V_o &= -2(i_2 - i_1) \\ &= 2(i_1 - i_2) \end{aligned}$$

in Mesh loop - 1

$$-12 + 2(i_1 - i_2) + 4(i_1 - i_3) = 0$$

$$6i_1 - 2i_2 - 4i_3 = 12$$

in mesh loop - 2

$$8i_2 - 3 + 2(i_2 - i_1) = 0$$

$$-2i_1 + 10i_2 = 3$$

in mesh loop 3

$$4(i_3 - i_1) + 3 + 4(i_1 - i_2) = 0$$

$$-4i_2 + 4i_3 = -3$$

$$i_1 = 2.25A$$

$$i_2 = 0.75A$$

$$i_3 = 0A$$