



# **Electrical Circuits for Engineers (EC1000)**

## **Lecture -4 Network Theorems (Chapter 4)**

# Overview

- Thevenin's Theorem
- Norton's Theorem
- Superposition Theorem
- Maximum Power Transfer Theorem



## 2. Linear Circuits

- **Linearity** is the property of an element describing a **linear** relationship between **cause** and **effect**.
- we shall limit its applicability to **resistors** in this chapter.
- The property is a combination of both the **homogeneity** (scaling) property and the **additivity** property.

### Homogeneity:


If the input (i.e the excitation) is multiplied by a constant, then the output (i.e response) is multiplied by the same constant.

For a **resistor**, for example,  
Ohm's law relates the input  $i$  to the output  $v$ ,

$$V \propto i$$
$$V = iR$$

If the **current** is increased by a **constant**  $k$ , then the **voltage** increases correspondingly by  $k$ ; that is,

$$kiR = kV$$

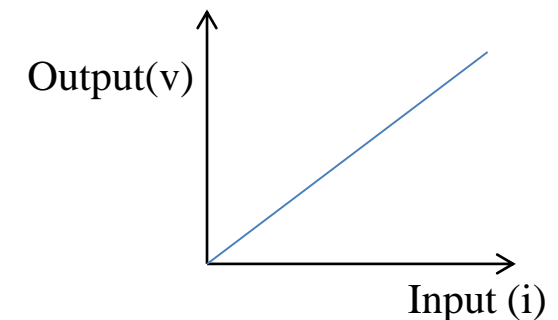



# Network Theorem

## Additivity property

Response to a **sum of inputs** is the **sum of the responses to each input** applied separately.

Using the voltage-current relationship of a resistor,


$$\text{If, } V_1 = i_1 R, V_2 = i_2 R$$

Then,

$$V = i_1 R + i_2 R = V_1 + V_2$$

A **linear circuit** is one whose output is linearly related (or directly proportional) to its input.

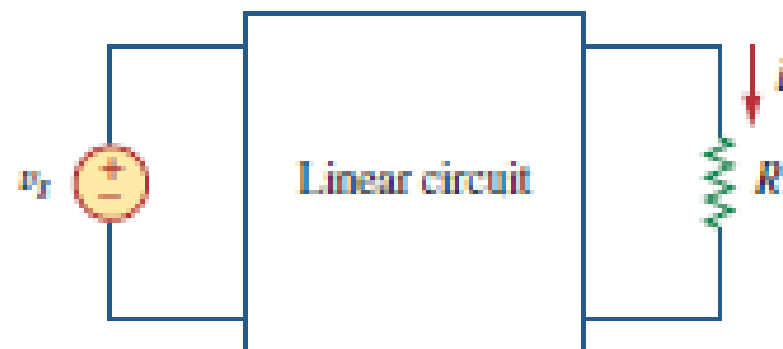
**Note** that since  $P = i^2/R$  or  $V^2/R$  (making it a quadratic function rather than a linear one), the **relationship between power and voltage (or current) is Nonlinear**. Therefore, the theorems covered in this chapter are not applicable to **power**.






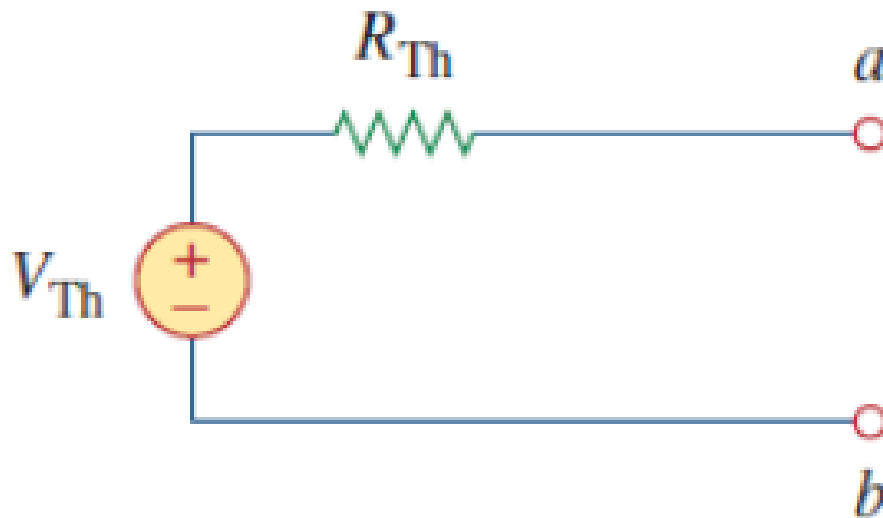
# 1. Thevenin's theorem

“A linear *BILATERAL* electric circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{Th}$  in series with a resistor  $R_{Th}$ , where  $V_{Th}$  is the open-circuit voltage at the terminals and  $R_{Th}$  is the input or equivalent resistance at the terminals when the independent sources are turned off”.






# 1. Thevenin's theorem

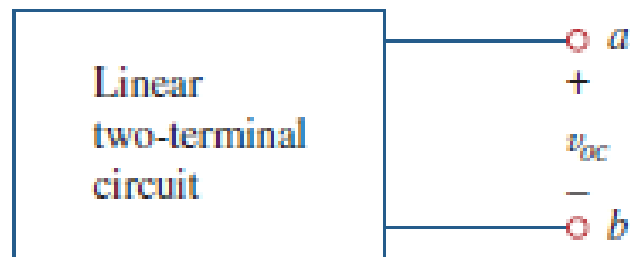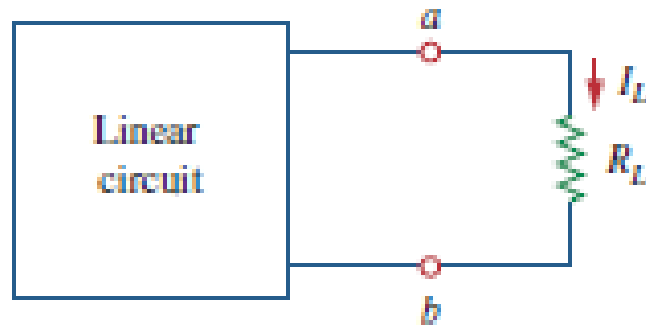


$$V_{Th} = v_{oc}$$

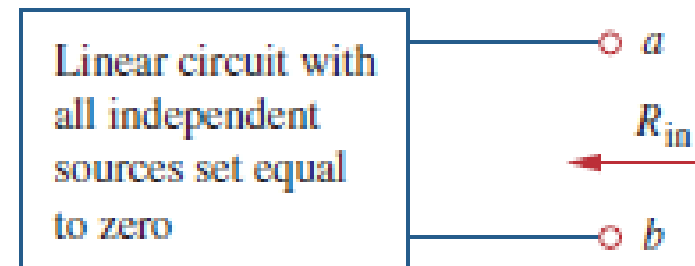

$$R_{Th} = R_{in}$$

Set independent sources zero and use reduction techniques to find  $R_{Th}$

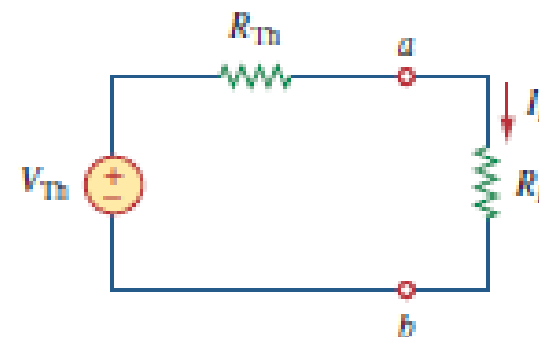- Open circuit the terminals 'a' and 'b' by removing the load  $R_L$  connected to it.
- Find the voltage across the terminals 'a' and 'b'.



Thevenin equivalent

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$



# Thevenin's theorem

## Example 1

Find the Thevenin's voltage with respect to the load resistor  $R_L$  in circuit shown in Fig.


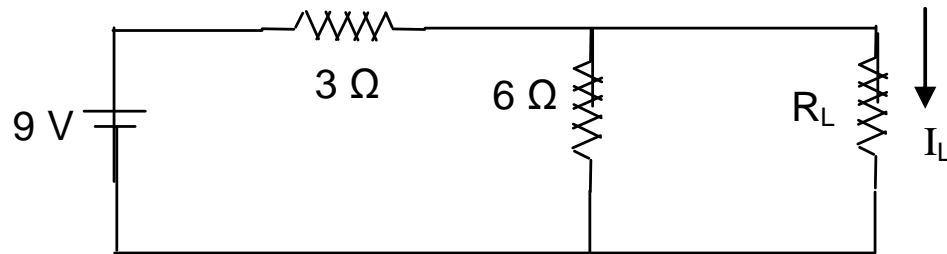


Fig. Circuit for Example1
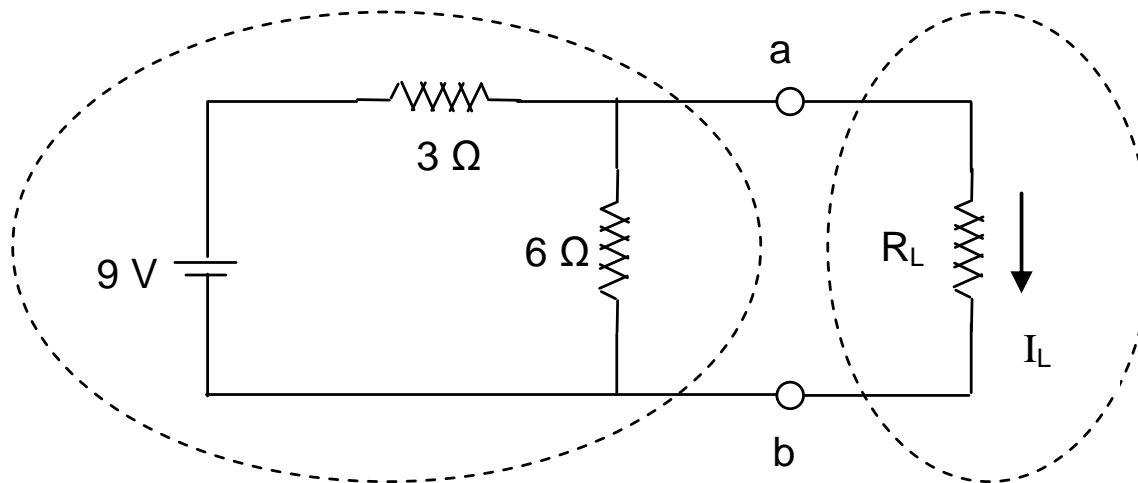
## Solution

The given circuit can be divided into two circuits as shown in Fig.




Circuit A

Circuit B



# Contd.,

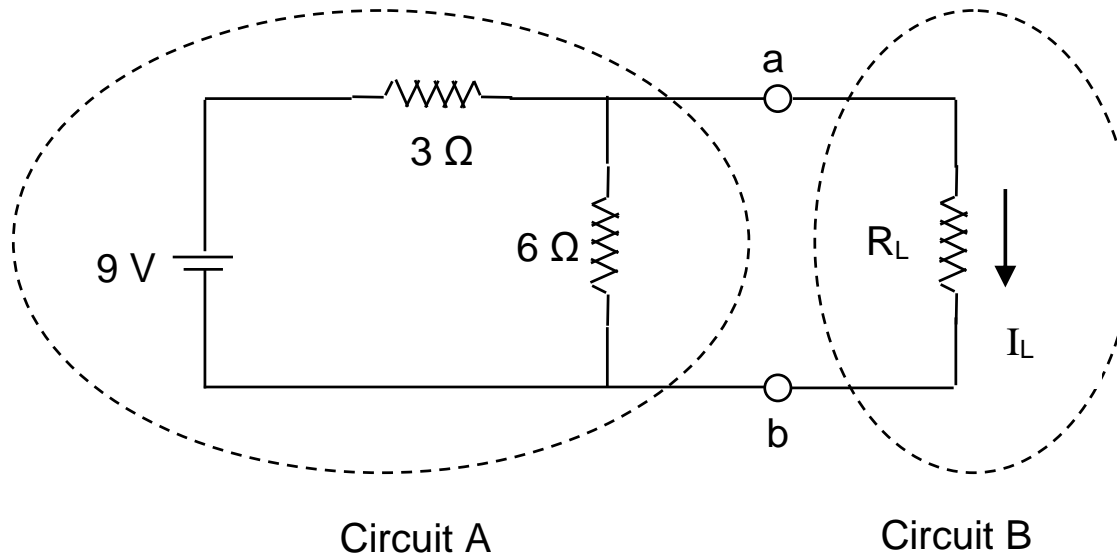

Thevenin's voltage of circuit A can be obtained from the circuit shown in Fig.

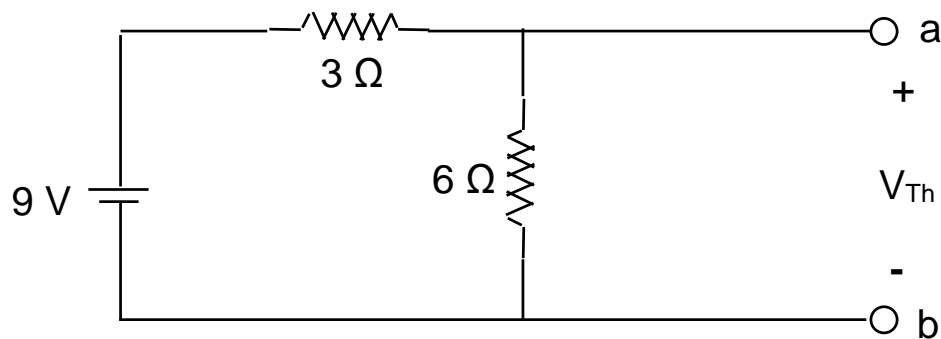


Fig. Circuit.


Using voltage division rule  $V_{Th} = V_{6\Omega} = \frac{6}{9} \times 9 = 6V$




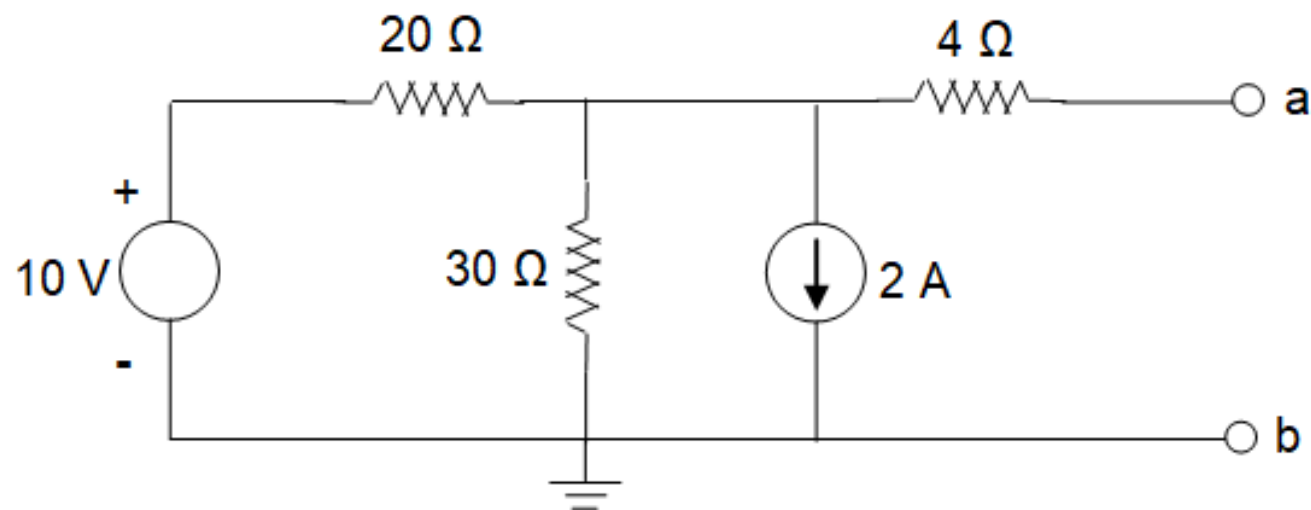
## Example 2

Obtain the Thevenin's equivalent for the circuit shown in Fig.



Solution:

$$\frac{V_{Th} - 10}{20} + \frac{V_{Th}}{30} + 2 = 0$$

Open circuit voltage  $V_{ab}$  is the Thevenin's voltage  $V_{Th}$ .



To find Thevenin's voltage:

Note that there is no current flow in resistor of  $4\ \Omega$ . Therefore, voltage  $V_{Th}$  is same as the voltage across  $30\ \Omega$  resistor. Then, the node voltage equation is

$$V_{Th} = -18\text{ V}$$




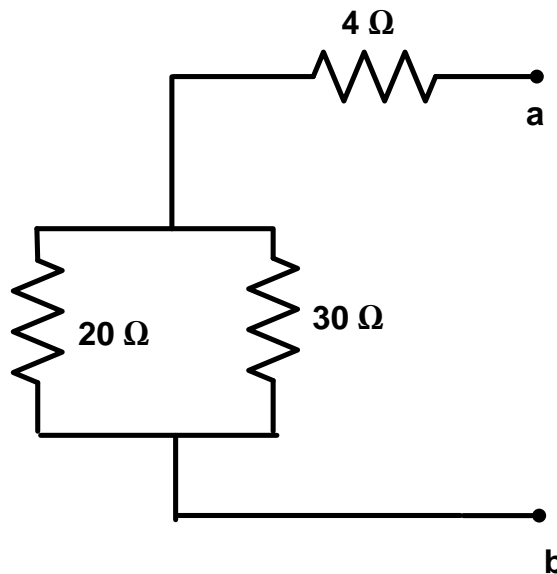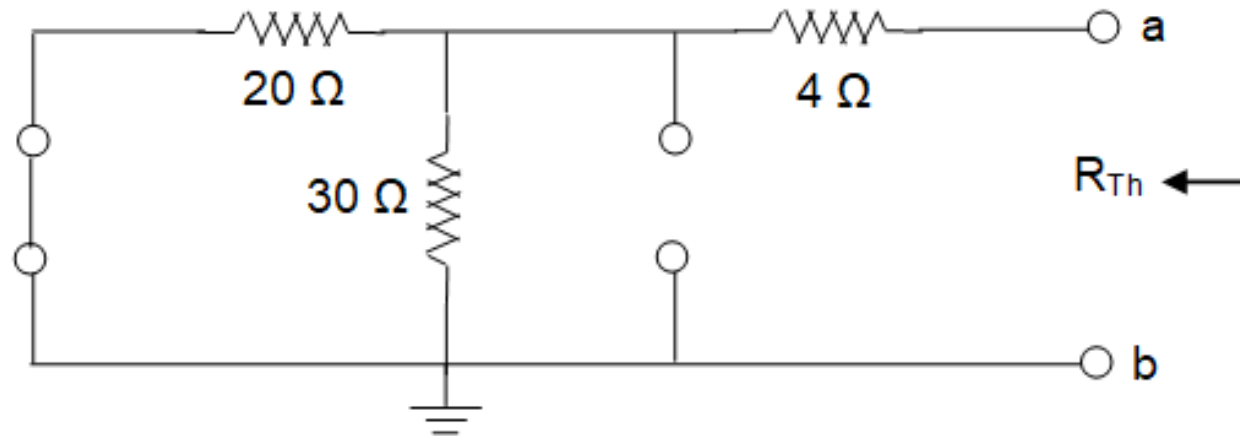Reducing the sources to zero, the resulting circuit is shown in Fig.




$$R_{Th} = 4 + 20 \parallel 30 = 16 \Omega$$

Thevenin's equivalent circuit

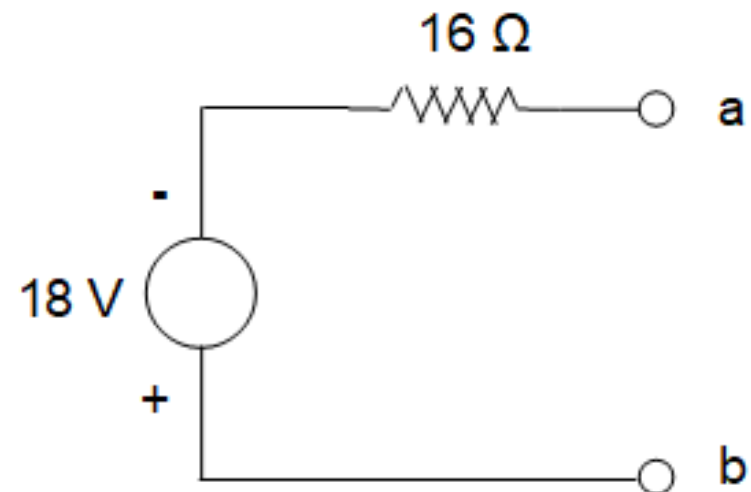



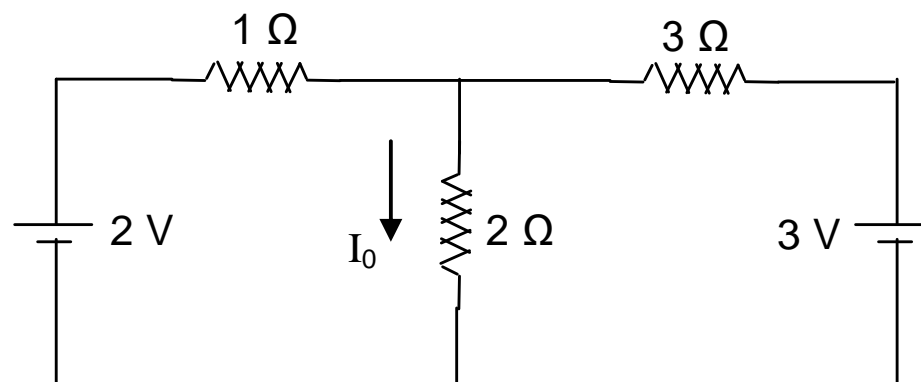**Example 3** Using Thevenin's equivalent circuit, calculate the current  $I_0$  through the  $2\ \Omega$  resistor in the circuit shown below.



**Solution:** Circuit by which  $V_{Th}$  and  $R_{Th}$  can be calculated are shown in Fig.


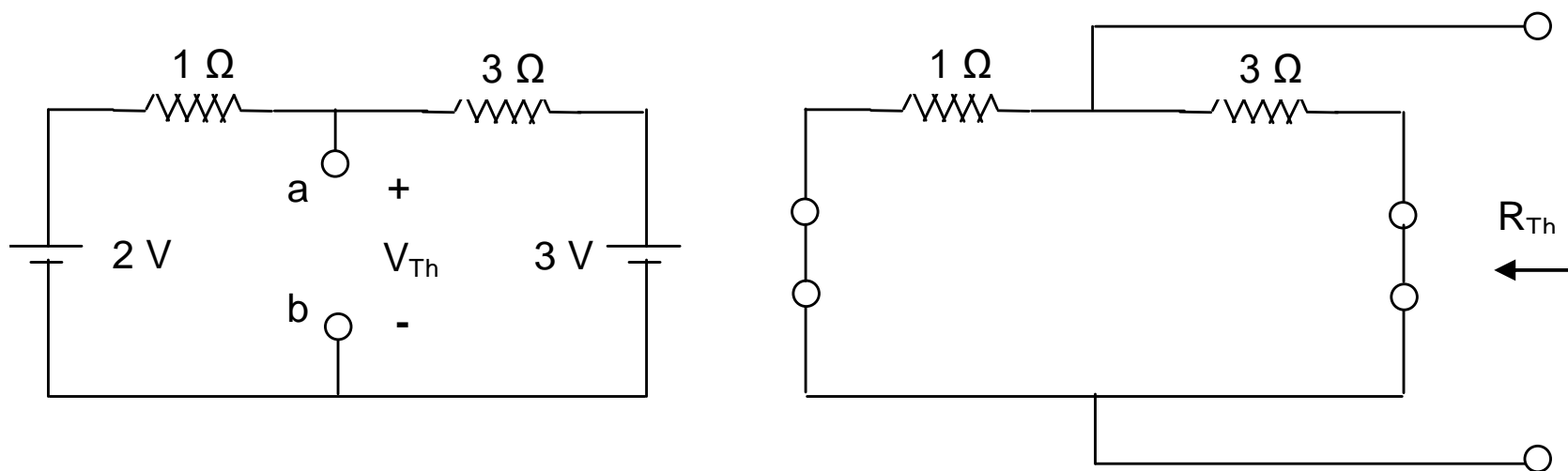


Fig. Circuits for  $V_{Th}$  and  $R_{Th}$  - Example 3.

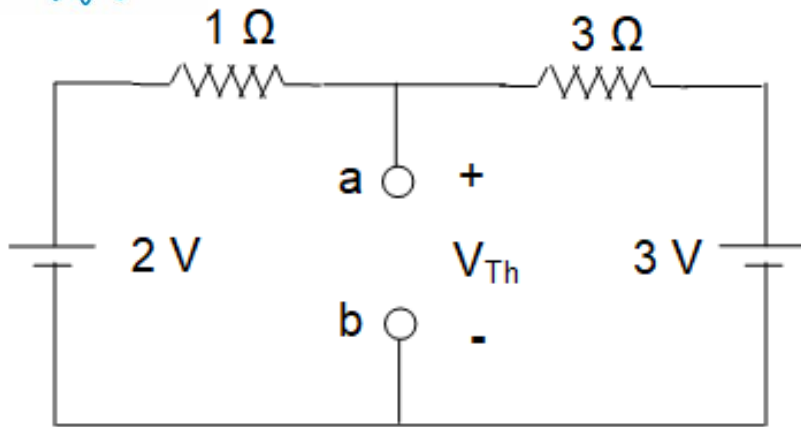


# Contd.,



$$\frac{V_{Th} - 2}{1} + \frac{V_{Th} - 3}{3} = 0$$


$$4V_{Th} = 9$$

$$V_{Th} = 2.25$$

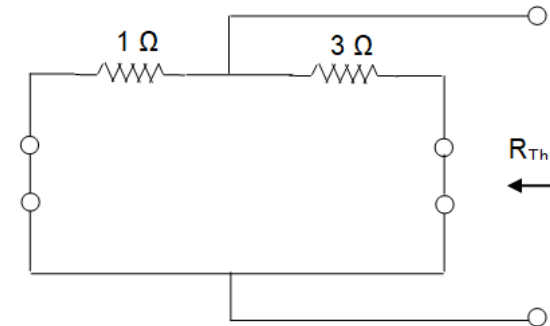

$$R_{Th} = 1 \parallel 3 = 0.75 \Omega$$

Thevenin's equivalent circuit becomes

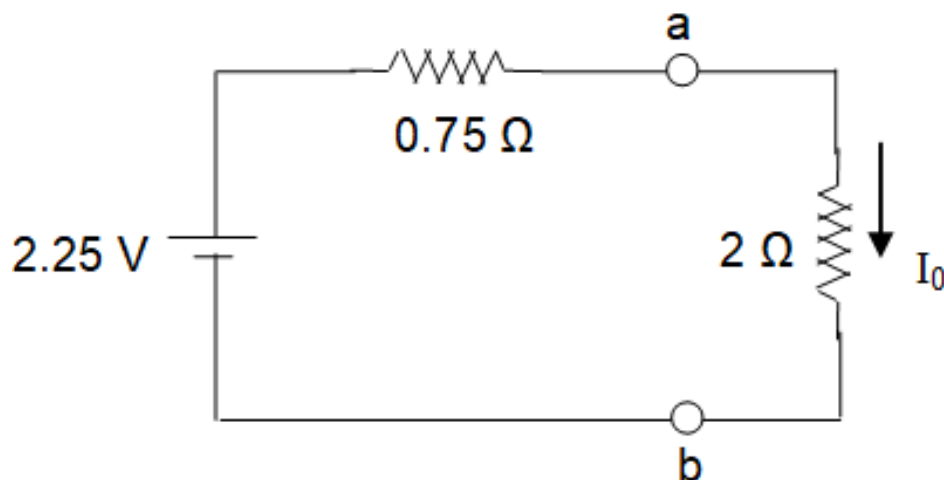


$$\text{Current } I_0 = 2.25 / 2.75 = 0.8182 \text{ A}$$




# Practice Problems

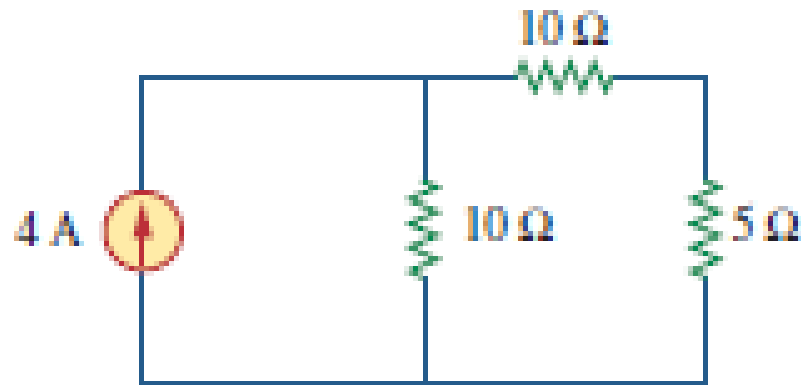1. Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit of Figure. Then find  $I$ .



**Ans:** 40 V, 20 Ohm

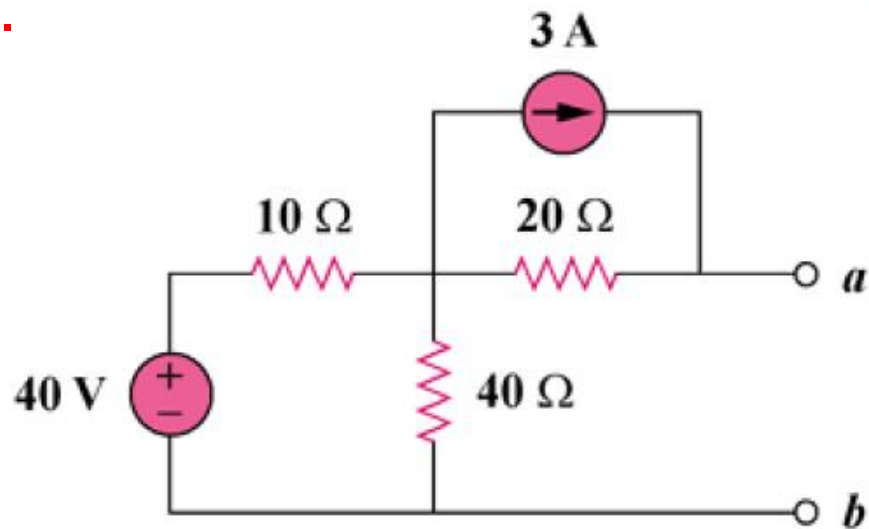2. Find the Thevenin equivalent at terminals a-b of the circuit in Figure.




**Ans:** 92 V, 28 Ohm



## 2. Norton's Theorem
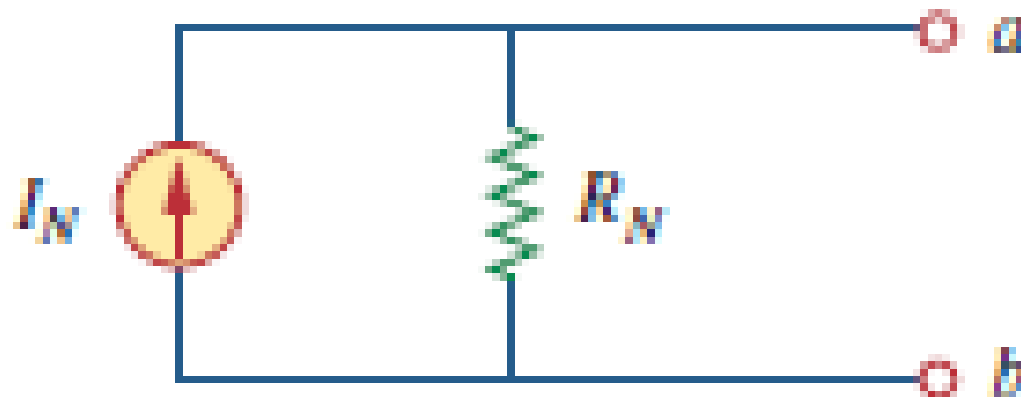
### Statement:



*“A linear BILATERAL circuit can be replaced by an equivalent circuit consisting of a current source  $I_N$  in parallel with a resistor  $R_N$ , where  $I_N$  is the short-circuit current through the terminals and  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off”.*




Norton's Equivalent Circuit



## 2. Norton's Theorem

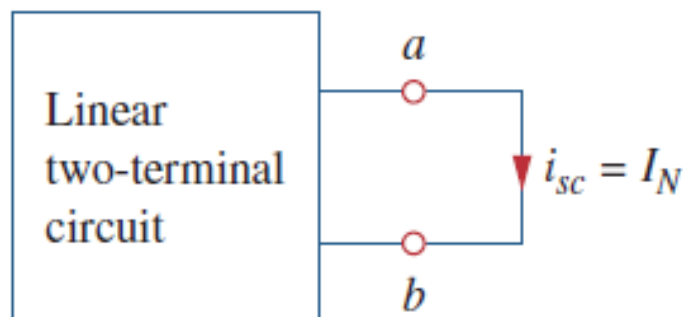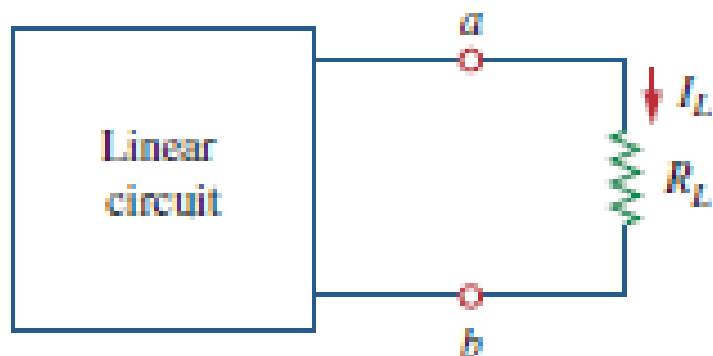

$$I_N = \frac{V_{Th}}{R_{Th}}$$

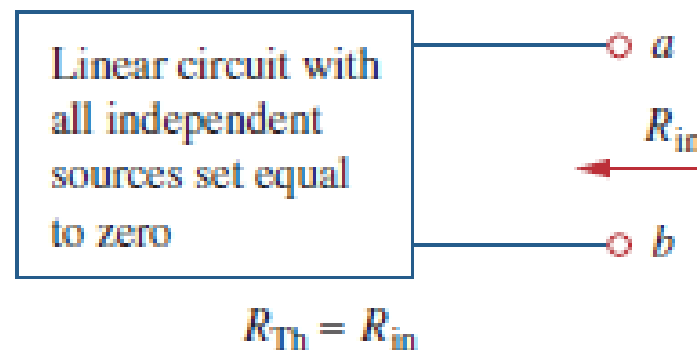


Set independent sources zero and use reduction techniques to find  $R_{Th}$

$$R_{Th} = \frac{V_{oc}}{i_{sc}} = R_N$$

$$V_{oc} = V_{Th}$$

$$I_N = i_{sc}$$

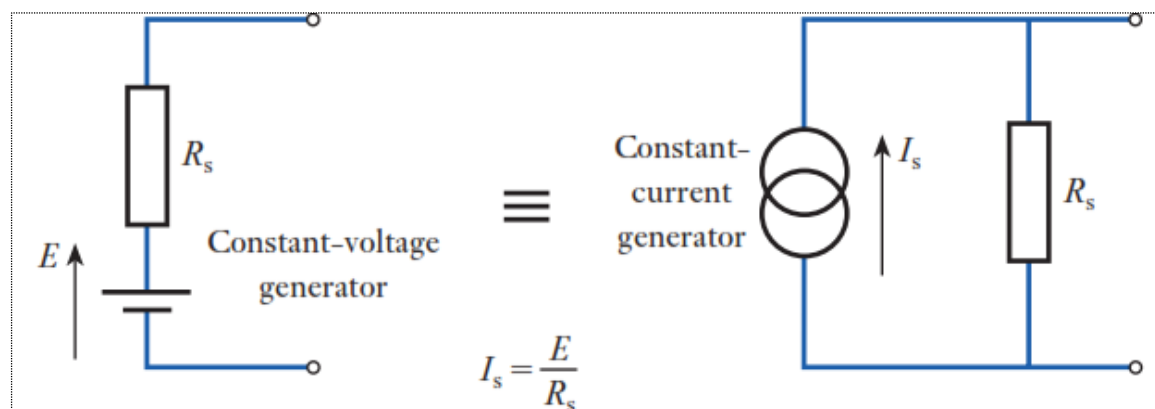- Short circuit the terminals 'a' and 'b' by removing the load  $R_L$  connected to it.
- Find the current through the terminals 'a' and 'b'.



Equivalence of constant-voltage generator and constant-current generator forms of representation



## 2. Norton's Theorem (Examples)

### Example 1

Using Norton's theorem, determine the current through the resistor  $R_L$  when  $R_L = 0.7$ ,  $1.2$  and  $1.6 \Omega$  in the circuit shown in Fig.


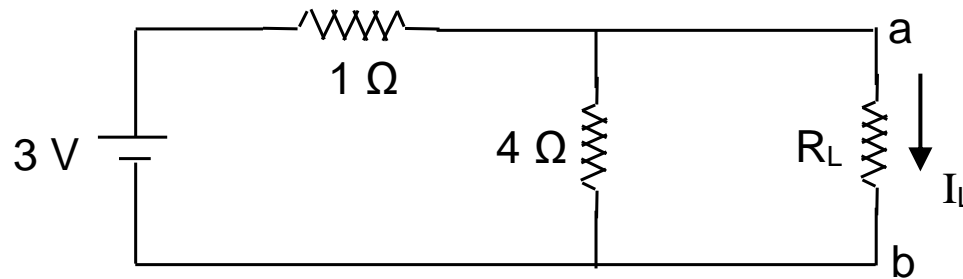



Fig. Circuit for Example 1.
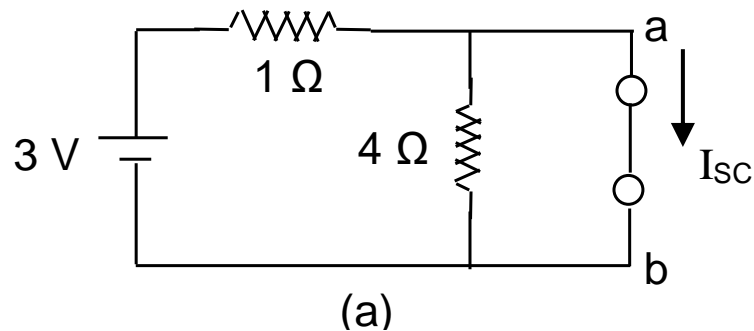
### Solution:

Circuits to determine  $I_{sc}$  and  $R_N$  are shown in Fig. (a) and (b).



(a)

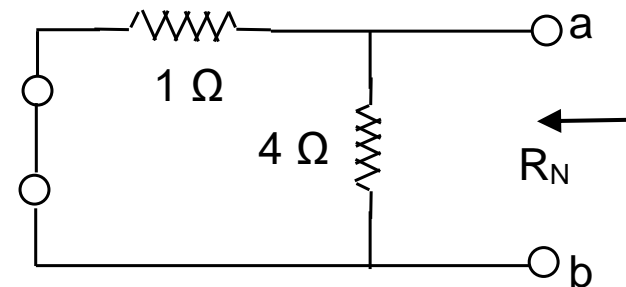



(b)

Fig. Short circuit current and Norton's resistance.






Contd.,

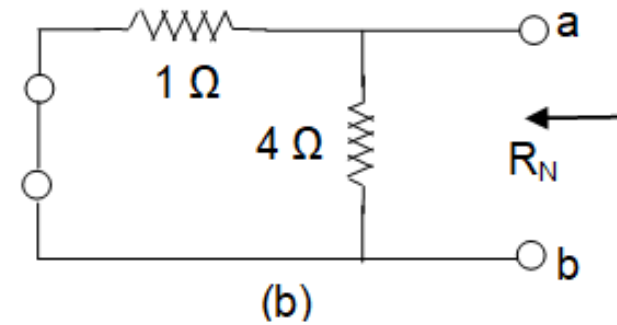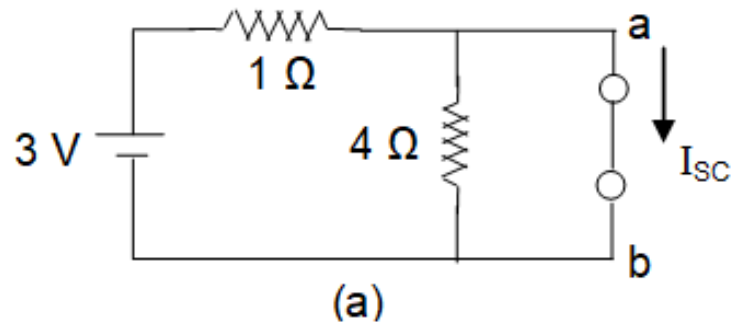

It is to be noted that since there is a short circuit parallel to  $4\ \Omega$  no current flows in it.

Norton's current  $I_N = 3\text{ A}$ ; Norton's resistance  $R_N = 1 \parallel 4 = 0.8\ \Omega$

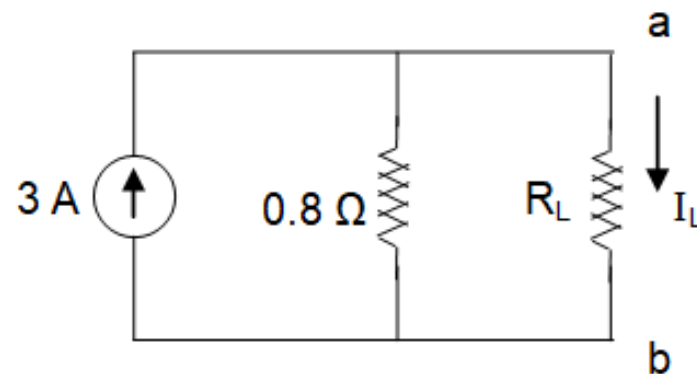Norton's equivalent circuit is shown in Fig.





When  $R_L = 0.7\ \Omega$ ,  $I_L = (0.8 / 1.5) \times 3 = 1.6\text{ A}$ ; When  $R_L = 1.2\ \Omega$ ,  $I_L = (0.8 / 2) \times 3 = 1.2\text{ A}$

When  $R_L = 1.6\ \Omega$ ,  $I_L = (0.8 / 2.4) \times 3 = 1.0\text{ A}$



# Example Problems

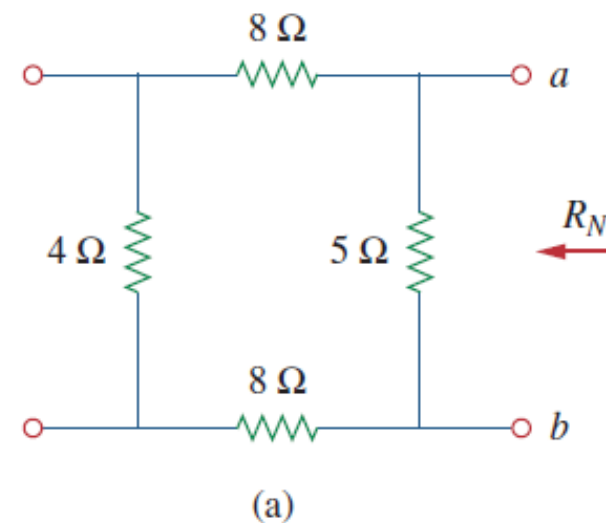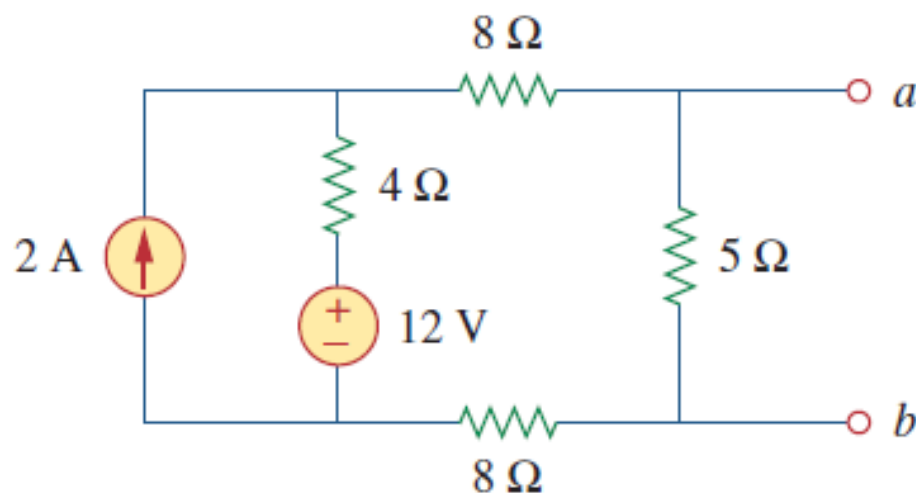2. Obtain the Norton's equivalent circuit for the below circuit.




## Solution

a) Find  $R_N$

$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$



## b) $V_N$

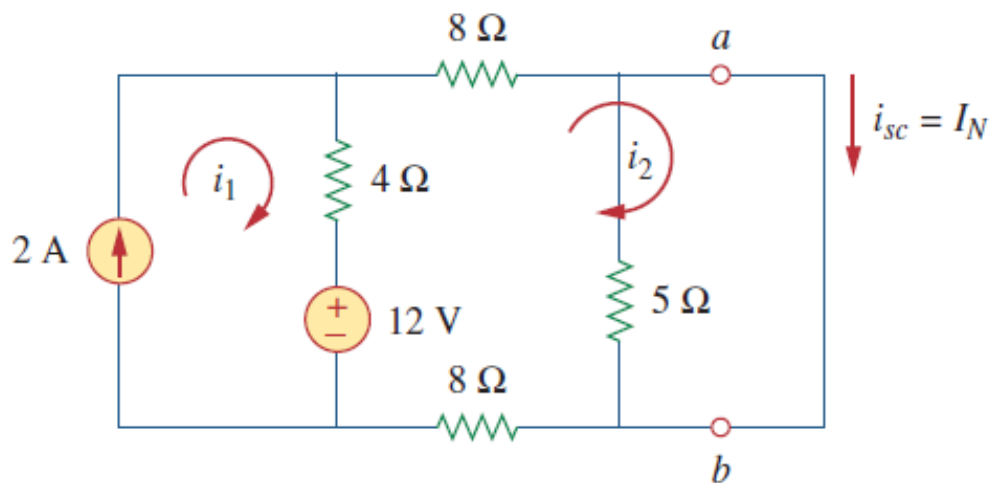


(b)

We ignore the 5-Ω resistor because it has been short-circuited. Applying mesh analysis, we obtain


$$i_1 = 2 \text{ A}, \quad 20i_2 - 4i_1 - 12 = 0$$

$$i_2 = 1 \text{ A} = i_{sc} = I_N$$

## Norton's equivalent circuit

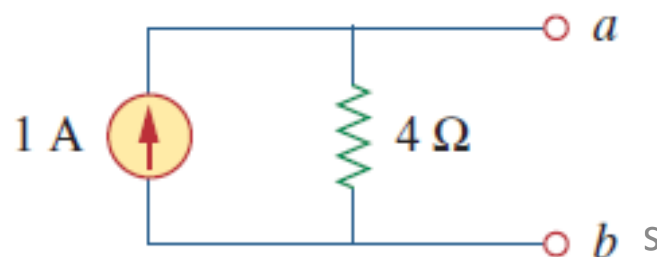

## Alternate Method (Thevenin's Voltage)

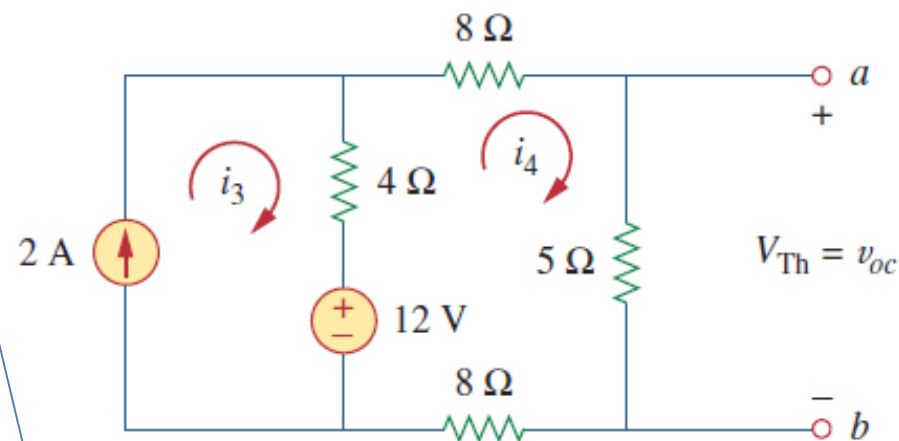

(c)

$$i_3 = 2 \text{ A}$$

$$25i_4 - 4i_3 - 12 = 0 \Rightarrow i_4 = 0.8 \text{ A}$$


$$v_{oc} = V_{Th} = 5i_4 = 4 \text{ V}$$

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{4}{4} = 1 \text{ A}$$




# Practical Problems

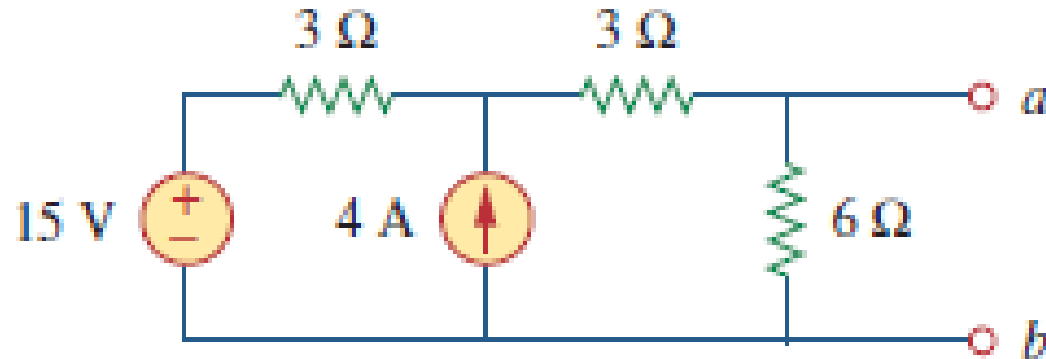1. Obtain the Norton's equivalent circuit for the below circuit.




Answer:  $R_N = 3\ \Omega$ ,  $I_N = 4.5\ \text{A}$ .

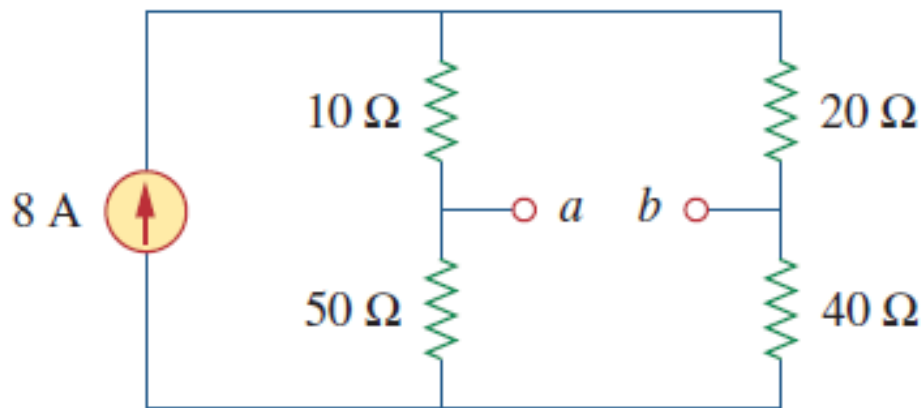2. Determine Thevenin's and Norton's equivalent across a-b circuit for the below circuit


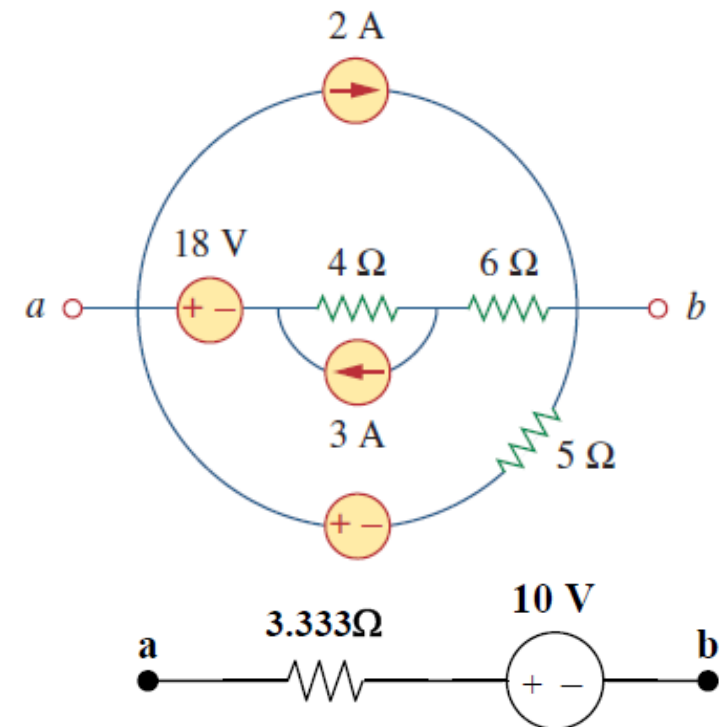
$$V_{Th} = 40\text{V}, \text{ and } I_N = V_{Th}/R_{Th} = 40/22.5 = 1.7778\ \text{A}$$





## 4. Superposition Theorem

### **Statement:**

The superposition principle states that the voltage across (or current through) an element in a **linear** circuit is the **algebraic sum** of the voltages across (or currents through) that element due to **each independent** source acting alone.


- Superposition theorem is applicable to linear circuits having two or more independent sources.

**Note:** When one source is acting alone, another source should be turned off (i.e. **Current source** should be **open circuited** and **Voltage sources** should be **short circuited**)




# Example Problems

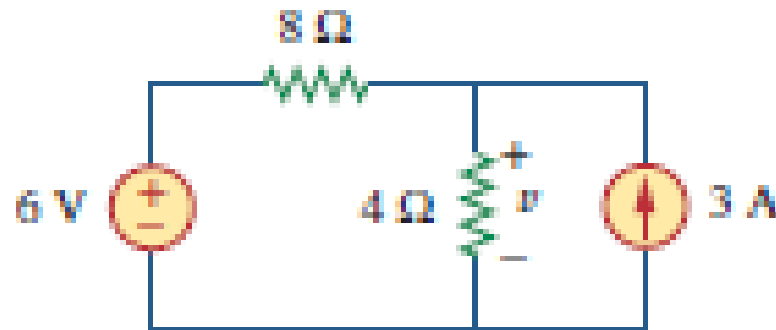**Example 1.** Use the superposition theorem to find  $v$  in the circuit of Figure.




1. When 6 V source is acting

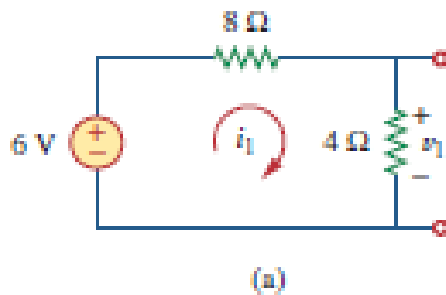

$$v_1 = \frac{4}{4 + 8}(6) = 2 \text{ V}$$

2. When 3 A source is acting

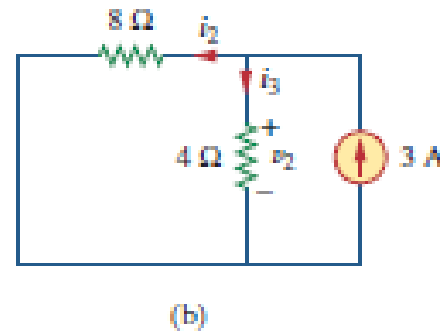

$$i_3 = \frac{8}{4 + 8}(3) = 2 \text{ A}$$


$$v_2 = 4i_3 = 8 \text{ V}$$

$$V = v_1 + v_2 = 2 \text{ V} + 8 \text{ V} = 10 \text{ V}$$




# Example Problems

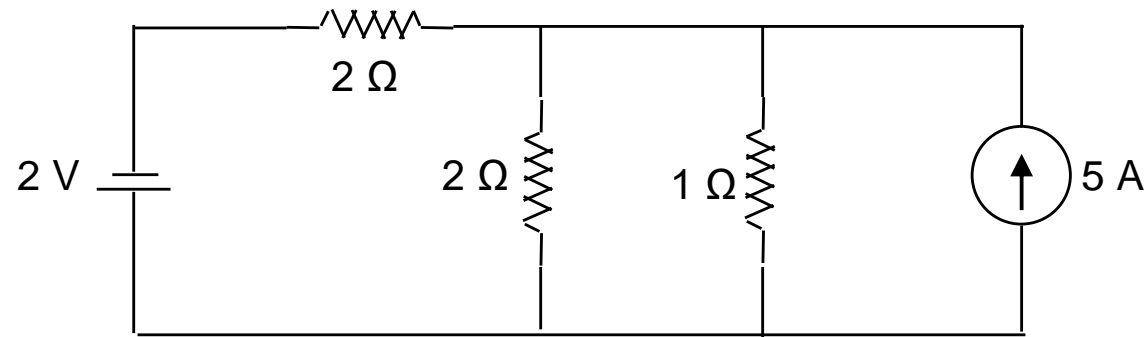**Example 2** Calculate the current through the  $1\ \Omega$  resistor in the circuit shown below.



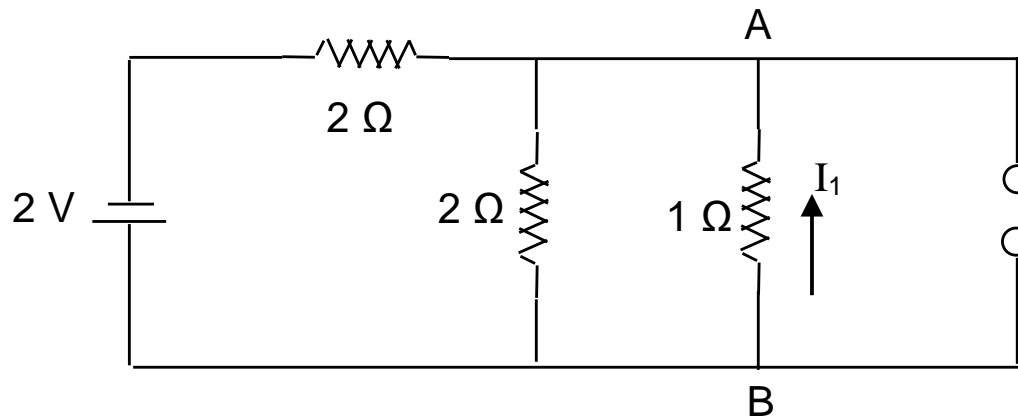**Solution:** First calculate current  $I_1$  due to voltage source alone. The current source is open circuited. The resulting circuit is shown below.




Total circuit resistance  $R_T = 2.6667\ \Omega$ . Circuit current  $I_T = \frac{2}{2.6667} = 0.75\ \text{A}$

Current  $I_1 = \frac{2}{3} \times 0.75 = 0.5\ \text{A}$  from B to A



Contd.,

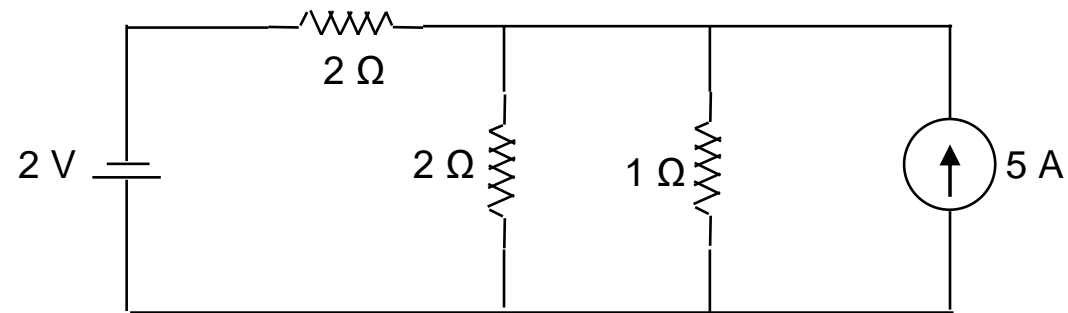

Now calculate current  $I_2$  due to current source alone. The voltage source is short circuited as shown in Fig.

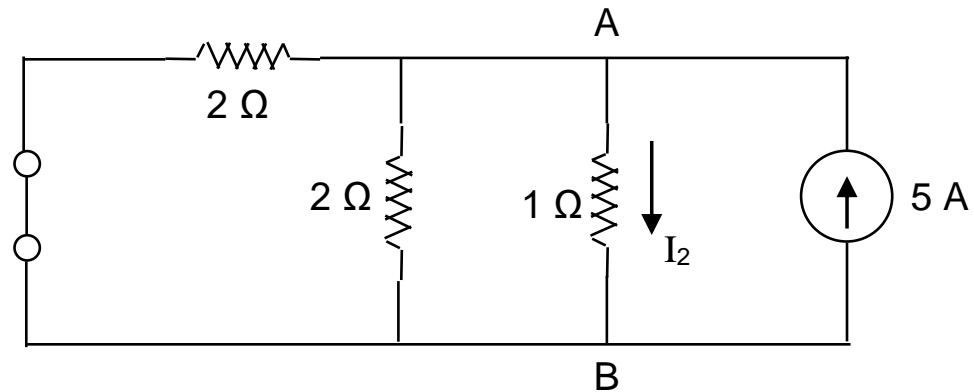


Fig. Circuit - Example 1

Noting that two  $2\ \Omega$  resistors are in parallel, current  $I_2 = 2.5\text{ A}$  from A to B.


When both the sources are simultaneously present:

Current through  $1\ \Omega$  resistor =  $2.5 - 0.5 = 2\text{ A}$  from A to B.






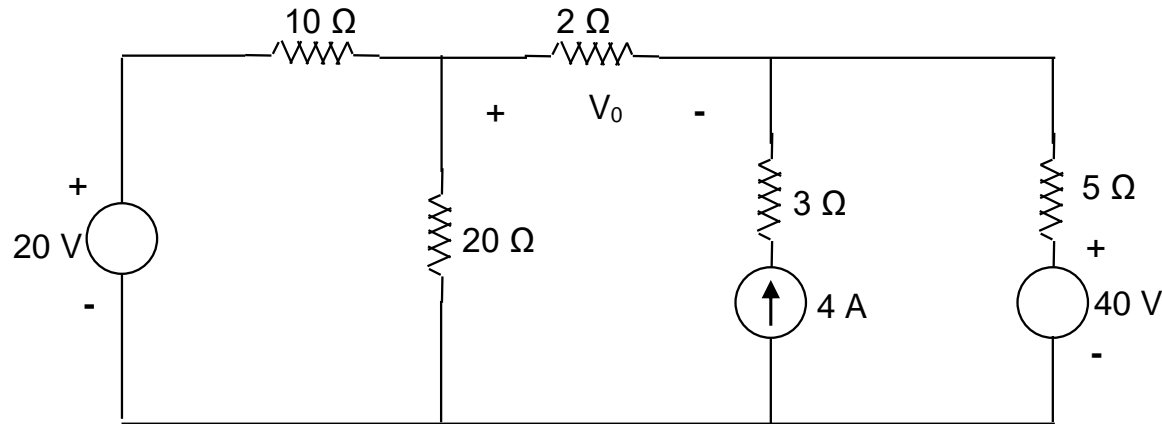**Example 3** In the circuit shown, find the voltage drop,  $V_0$  across the  $2\ \Omega$  resistor using Superposition theorem.



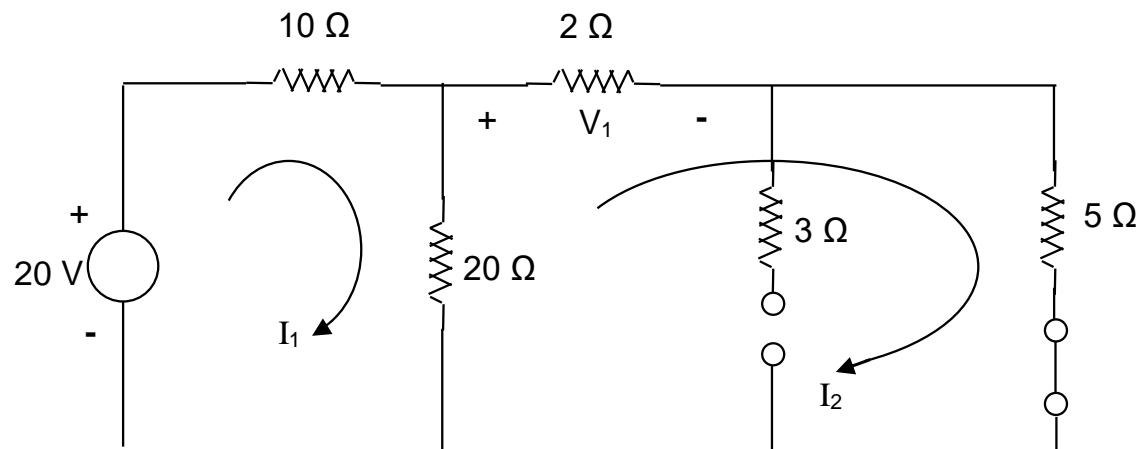**Solution:** 20 V source alone present: The circuit will be as shown below.




Mesh current equations : 
$$\begin{bmatrix} 30 & -20 \\ -20 & 27 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$
 On solving,  $I_2 = 0.9756\text{ A}$

Thus voltage  $V_1 = 2 \times 0.9756 = 1.9512\text{ V}$

**4 A source alone present:**

The circuit will be as shown below.

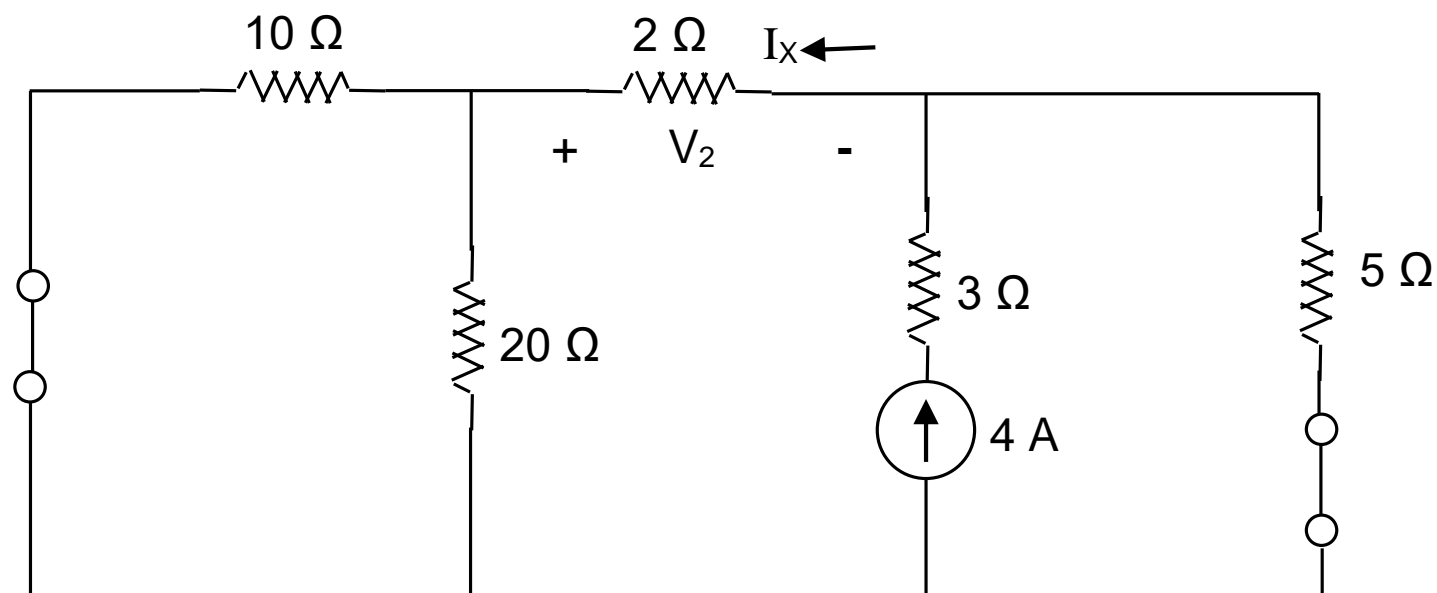

$$2 + 10 \parallel 20 = 8.6667 \Omega$$


$$\text{Therefore current } I_x = \frac{5}{13.6667} \times 4 = 1.4634 \text{ A}$$

$$\text{Thus voltage } V_2 = - 2 \times 1.4634 = - 2.9268 \text{ V}$$



40 V source alone present:

Resulting circuit is shown below.

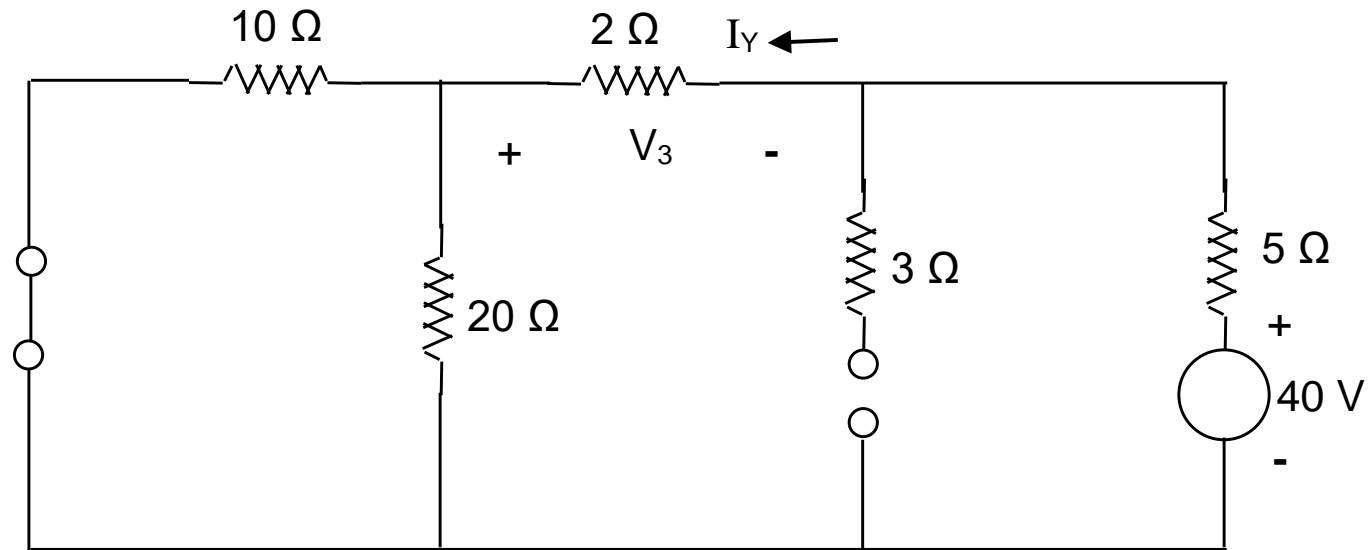

Circuit resistance  $R_T = 5 + 2 + (10 \parallel 20) = 13.6667 \Omega$

Current  $I_Y = 40 / 13.6667 = 2.9268 \text{ A}$ ; Thus voltage  $V_3 = - 2 \times 2.9268 = - 5.8537 \text{ V}$

When all the three sources are simultaneously present,


voltage across  $2 \Omega$ , i.e.  $V_0 = V_1 + V_2 + V_3 = 1.9512 - 2.9268 - 5.8537 = - 6.8293 \text{ V}$



# Practice Problems


1. Using superposition, find  $V_o$  in the circuit of below Figure.

Ans: 7.4 V

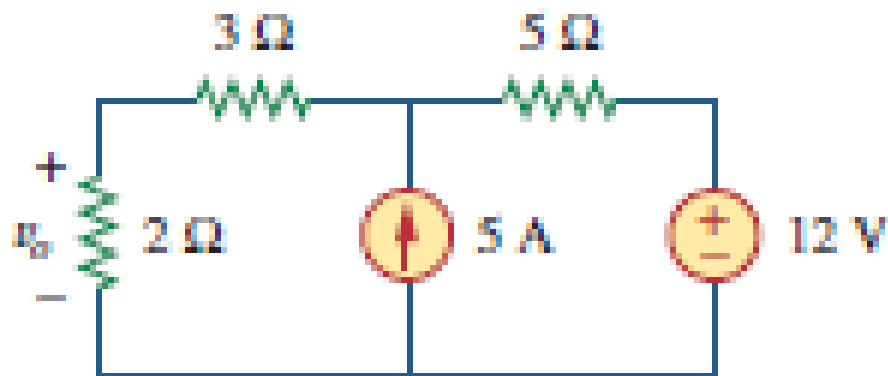

2. Using superposition, find  $i$  in the circuit of below Figure.

Ans: 2 A

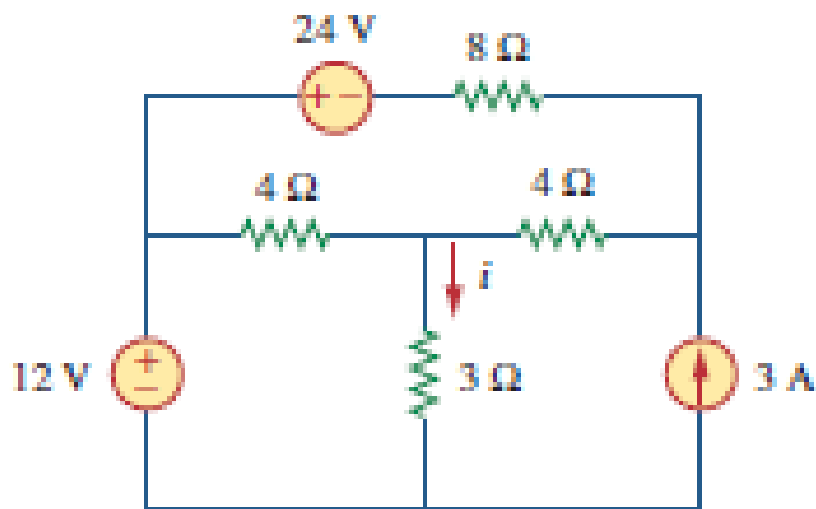



**All the materials extracted from Fundamentals of Electric Circuits by Charles K. Alexander, Matthew N.O. Sadiku, 5<sup>th</sup> Edition, McGraw Hill, for the purpose of Teaching and Learning only.**