



# **Electrical Circuits for Engineers (EC1000)**

## **Lecture - 4(a) Source Transformation (Chapter 4)**


# Overview

- Source Transformation
- Thevenin's Theorem
- Norton's Theorem
- Maximum Power Transfer Theorem
- Superposition Theorem



# 1. Source Transformation (Chapter-4.4)

## Source Transformation

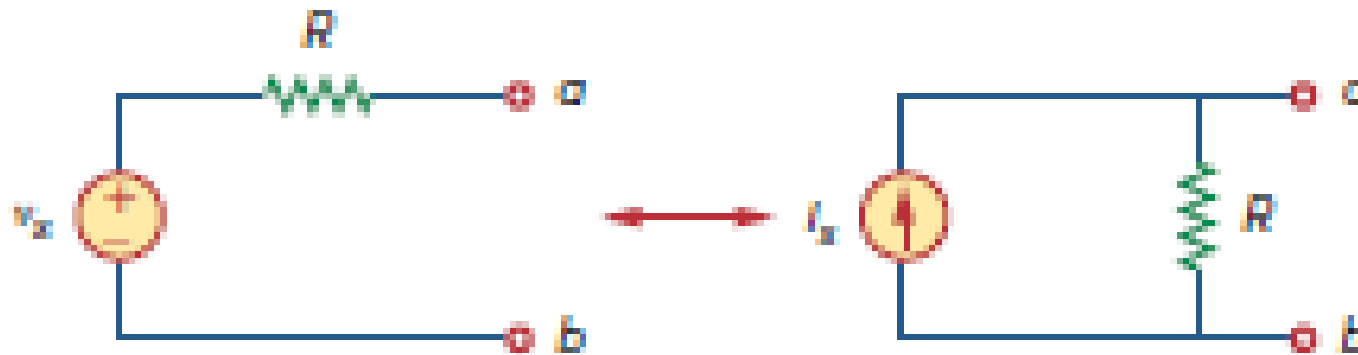


A **source transformation** is the process of replacing a voltage source  $V_s$  in series with a resistor  $R$  by a current source  $i_s$  in parallel with a resistor  $R$ , or vice versa.






# Source Transformation

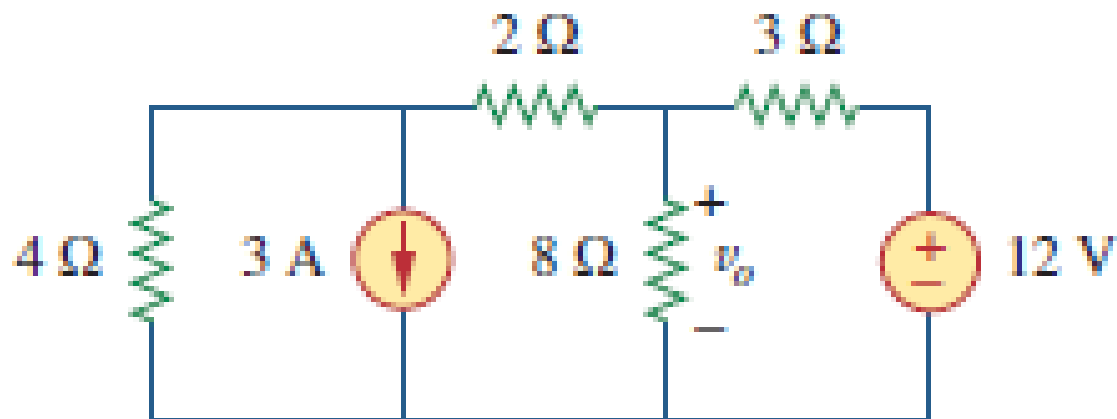1. Use source transformation to find  $V_o$





Contd.,

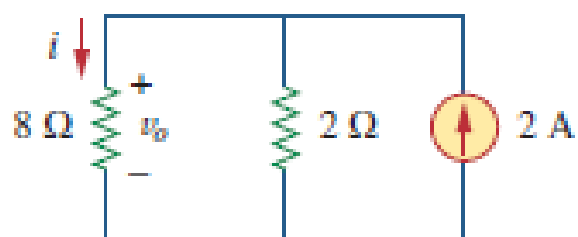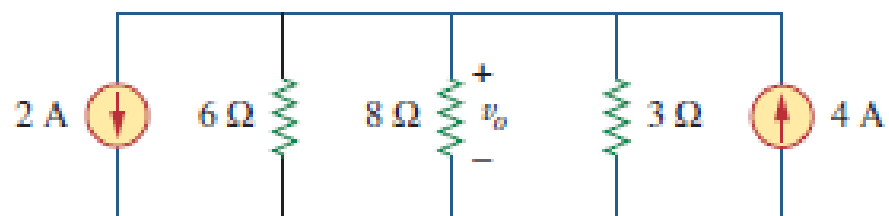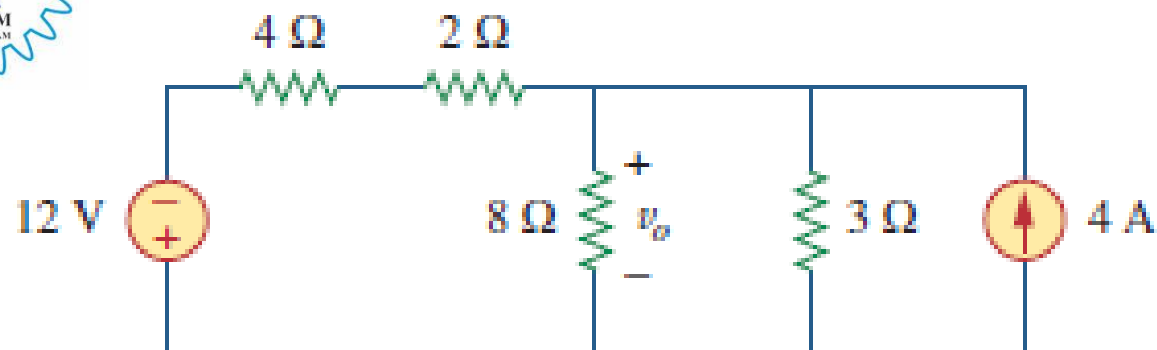


$$i = \frac{2}{2 + 8}(2) = 0.4 \text{ A}$$

$$v_o = 8i = 8(0.4) = 3.2 \text{ V}$$




# Source Transformation

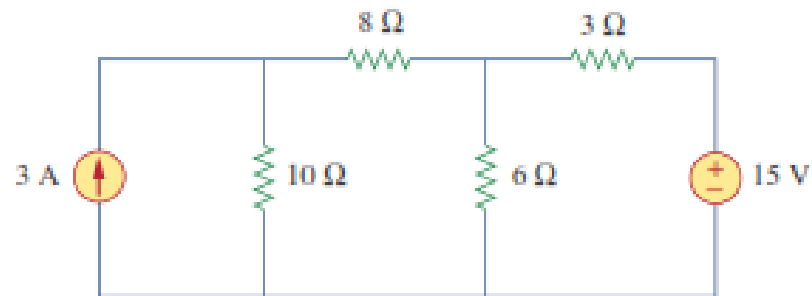2. Referring to below figure, use source transformation to determine the current and power absorbed by the 8 Ohm resistor.



## Solution

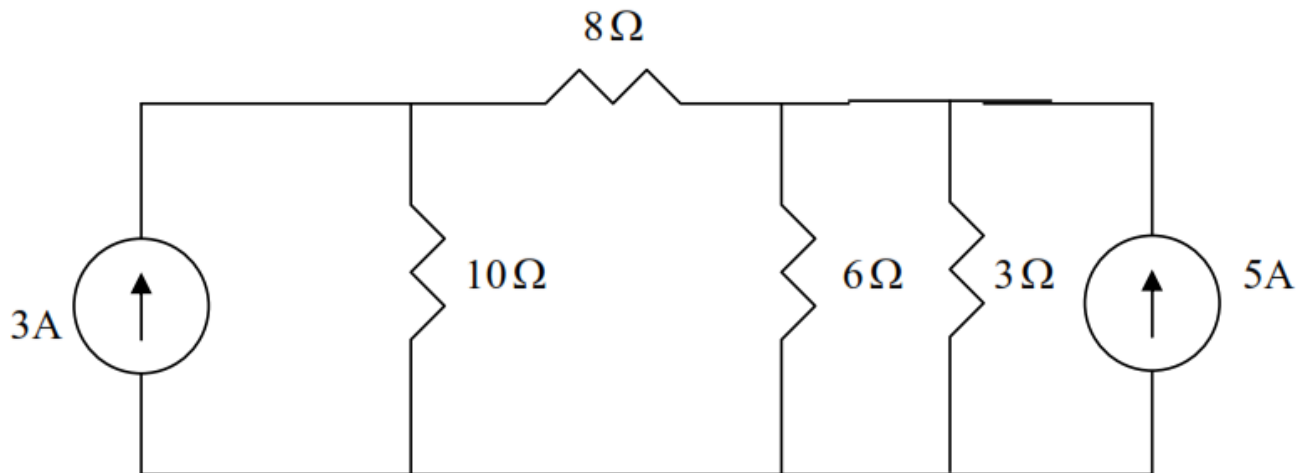



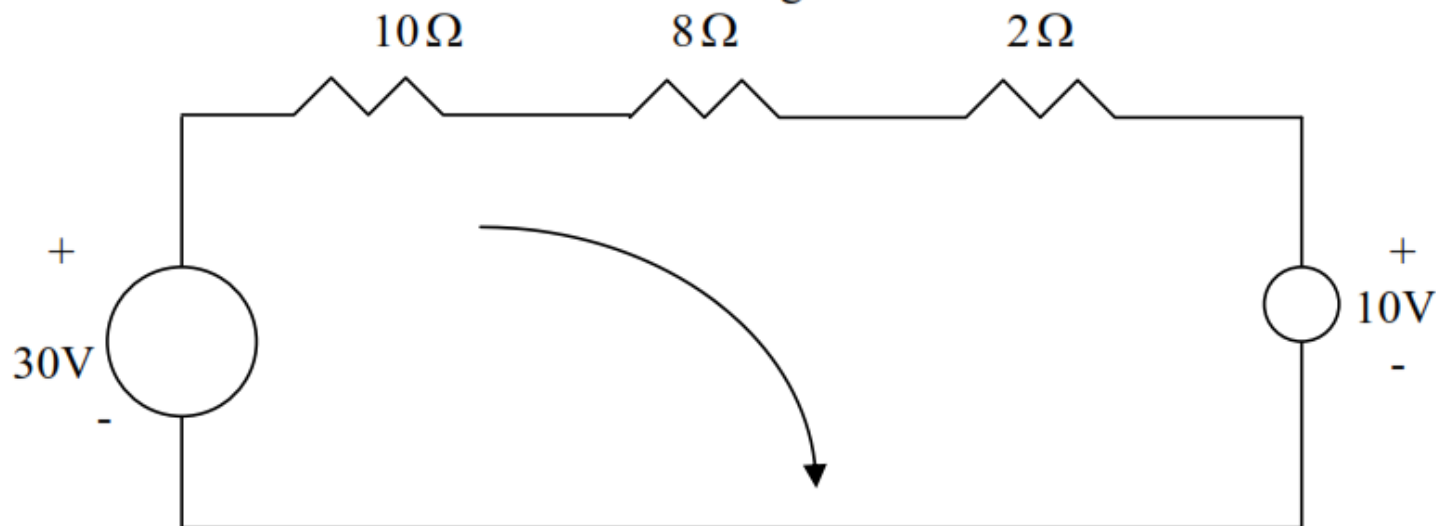
# Source Transformation

Contd.,

$3//6 = 2\text{-ohm}$ . Convert the current sources to voltages sources as shown below.



Applying KVL to the loop gives



$$-30 + 10 + I(10 + 8 + 2) = 0 \quad \longrightarrow \quad I = 1 \text{ A}$$

$$p = VI = I^2 R = 8 \text{ W}$$



# Source Transformation

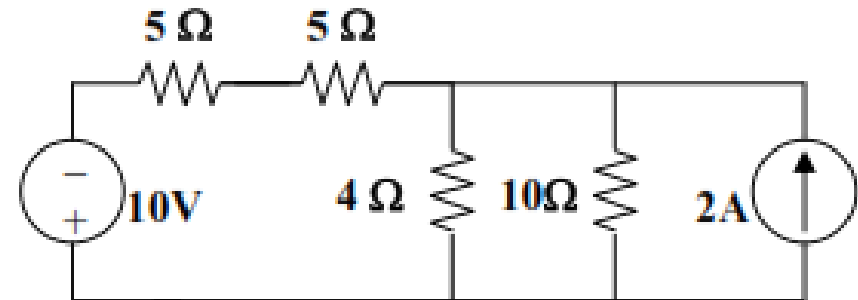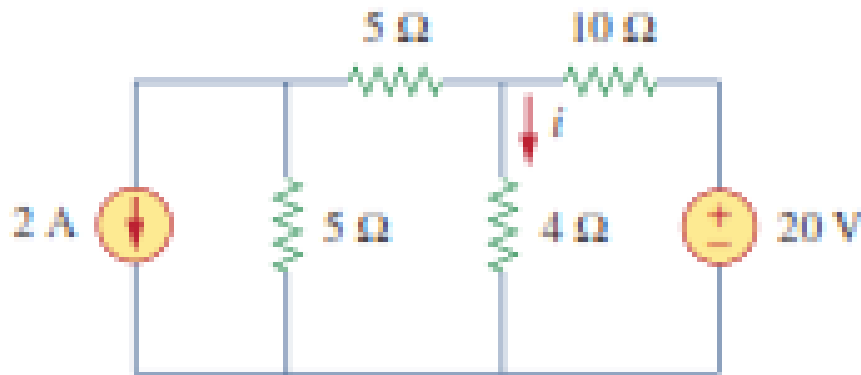
3. For the circuit in shown below, use source transformation to find  $i$ .



(a)
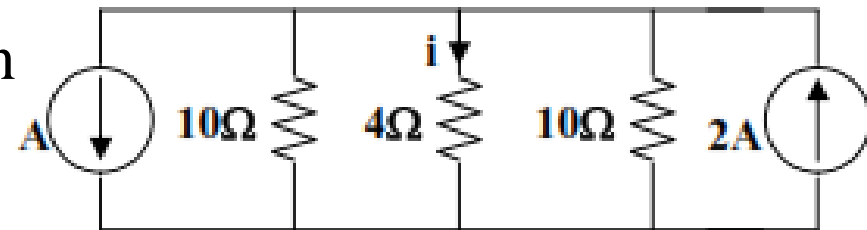
## Solution

We now transform only the voltage source to obtain the circuit in Fig. (b).



(b)


$$10 \parallel 10 = 5 \Omega, \quad i = [5 / (5 + 4)](2 - 1) = 5/9 = \mathbf{555.5 \text{ mA}}$$






# Problems

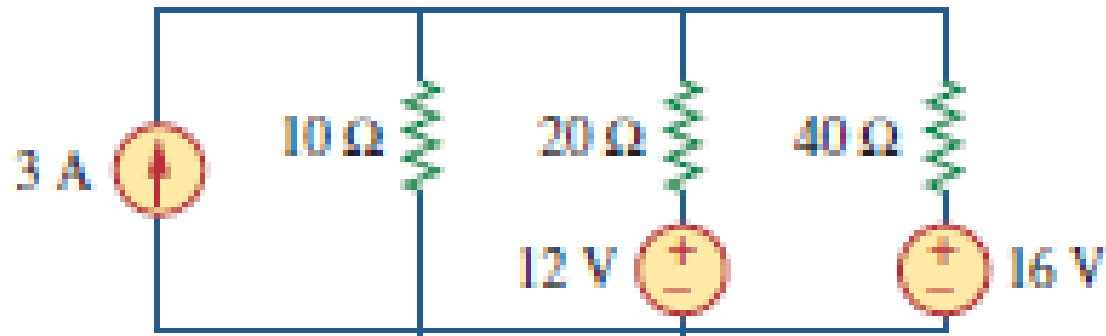
1. Use source transformation to reduce the circuit in Figure to a single voltage source in series with a single resistor.



**Ans:**

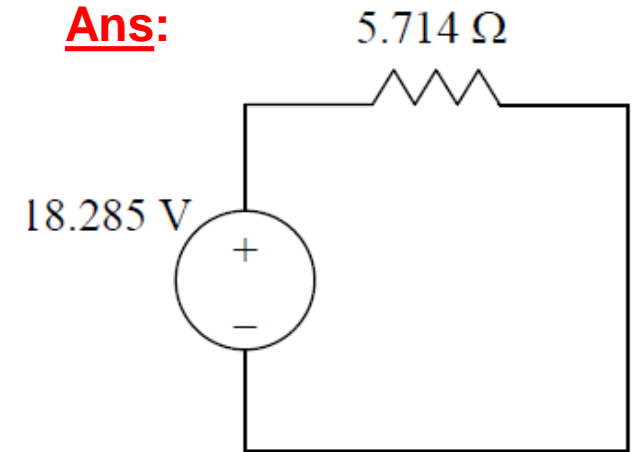

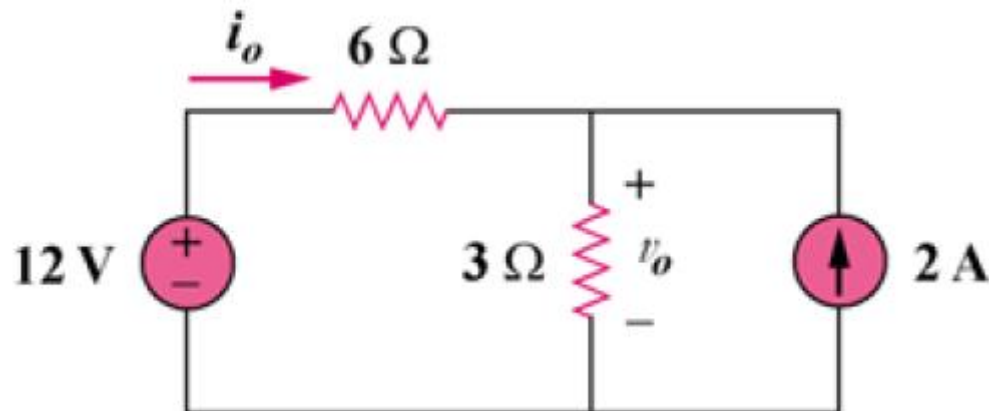2. Apply source transformation to find  $V_o$  and  $i_o$  in the circuit of below Figure.




**Ans: 666.7 mA, 8 V**




# Problems

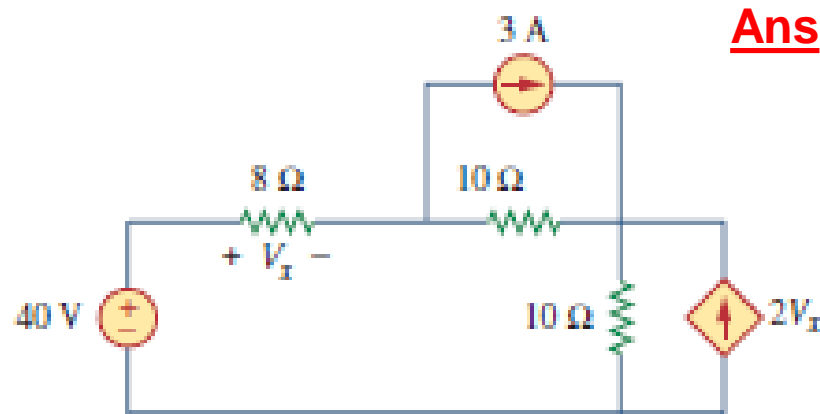3. Use source transformation to find  $v_x$  the voltage in the circuit of Figure.



**Ans: 2.978 V**

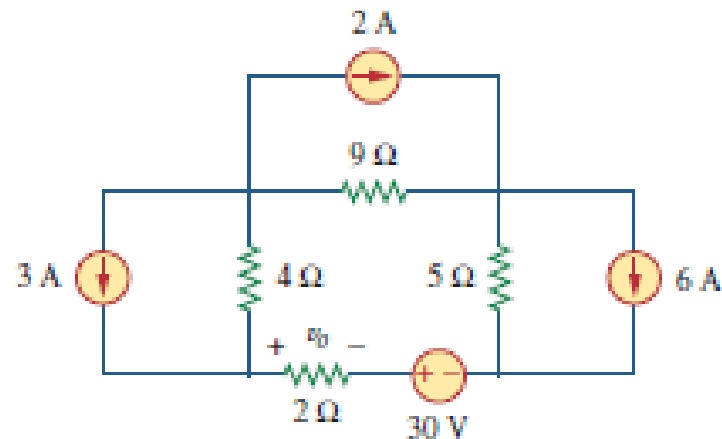4. Use source transformation to find  $v_o$  in the circuit of Figure.



**Ans: -6.6 V**