



EC1001: Digital Circuits
Solutions: Assignment-3_Chapter3&4

1. Simplify the following Boolean functions, using three-variable maps:

(a) $F(x, y, z) = \Sigma(0, 1, 2, 3, 5, 7)$

(b) $F(x, y, z) = x'yz + xy' + yz'$

Solution:

$$F(x, y, z) = \Sigma(0, 1, 2, 3, 5, 7)$$

		y			
		00	01	11	10
x	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4	m_5 1	m_7 1	m_6

$$F = x' + z$$

$$F(x, y, z) = x'yz + xy' + yz'$$

		y			
		00	01	11	10
x	0	m_0	m_1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7	m_6 1

$$F = xy' + x'y + yz'$$

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4


2. Simplify the following Boolean functions, using four-variable maps:

(a) $F(w, x, y, z) = \Sigma(1, 3, 5, 6, 7, 9, 11)$

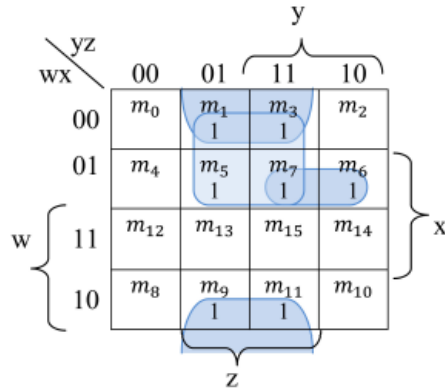(b) $F(w, x, y, z) = wxyz + wx' + wx'y + wxy + w'yz'$


Solution:

$$F(w, x, y, z) = \Sigma(1, 3, 5, 6, 7, 9, 11)$$



$$F = w'z + x'z + w'xy$$

$$wxyz + wx' + wx'y + wxy + w'yz'$$

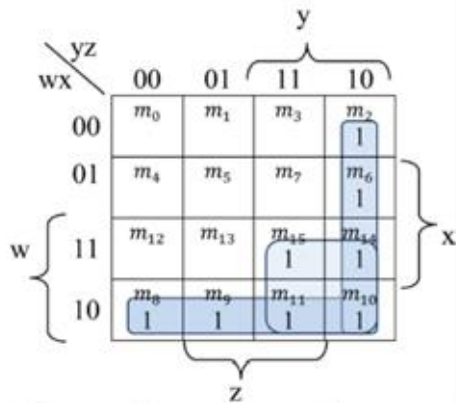


$$F = wx' + wy + yz'$$

EC1001: Digital Circuits
Solutions: Assignment-3_Chapter3&4


3. Simplify the following expression to (1) sum-of-products and (2) products-of-sums.
 $F = A'B + A'B'C + CD$

Solution:

$$A'B + A'B'C + CD$$

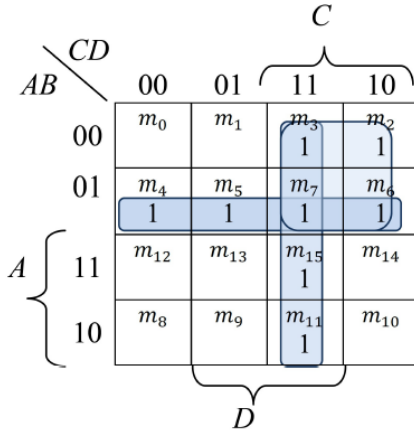

$$F = A'B + A'C + CD$$

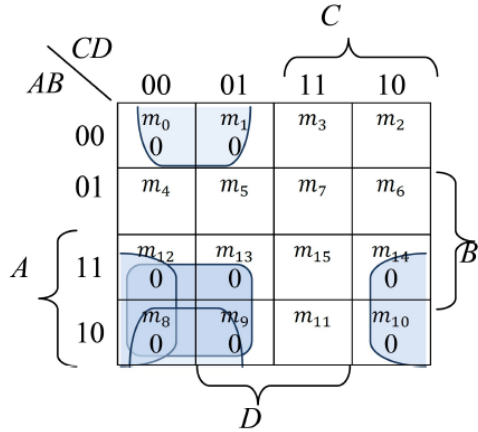

$$F' = B'C' + AC' + AD'$$


$$F = (B + C)(A' + C)(A' + D)$$

4. Draw a NAND logic diagram that implements the complement of the following function:
 $F(A, B, C, D) = \Sigma(0, 2, 4, 5, 8, 9, 10, 11)$

Solution:


$$F(A, B, C, D) = \Sigma(0, 2, 4, 5, 8, 9, 10, 11)$$
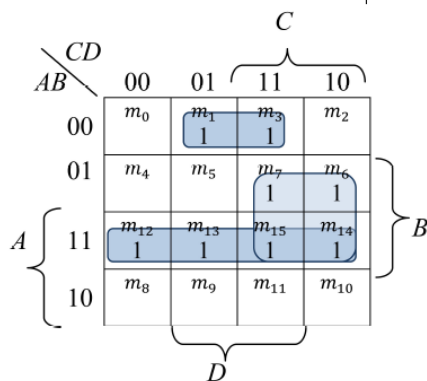
$$F' = \Sigma(1, 3, 6, 7, 12, 13, 14, 15)$$



$$F = A'B'D + BC + AB$$

$$= ((A'B'D + BC + AB)')' = ((A'B'D)'(BC)'(AB)')'$$

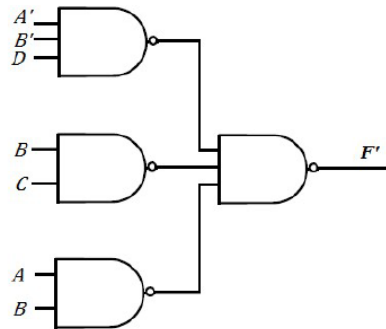

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4



5. Implement the following Boolean function F, together with the don't-care conditions d, using no more than two NOR gates:

$$F(A, B, C, D) = \Sigma(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \Sigma(0, 1, 5, 8)$$

Assume that both the normal and complement inputs are available.

Solution:

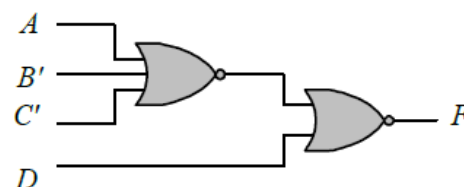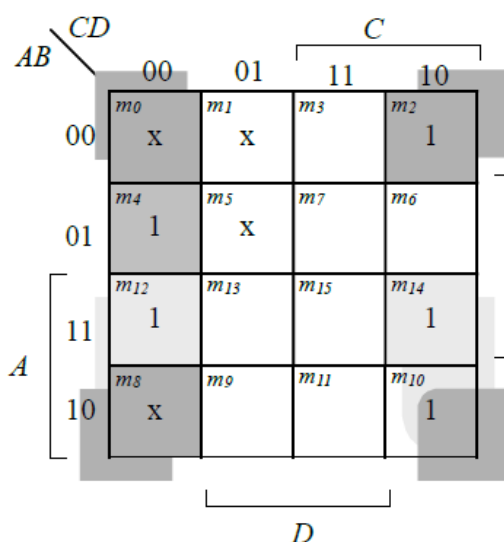

$$F = B'D' + AD' + C'D'$$

$$F' = D + A'BC$$


$$F = [D + A'BC]' = [D + (A + B' + C')]'$$

6. Implement the following Boolean expression with exclusive-NOR and AND gates.

$$F = A'B'C'D' + ABC'D' + A'B'CD + ABCD$$

Solution:

$$\begin{aligned} F &= A'B'C'D' + ABC'D' + A'B'CD + ABCD \\ &= C'D'(\overline{A \oplus B}) + CD(A \oplus B) \\ &= (\overline{A \oplus B})(C \oplus D) \end{aligned}$$

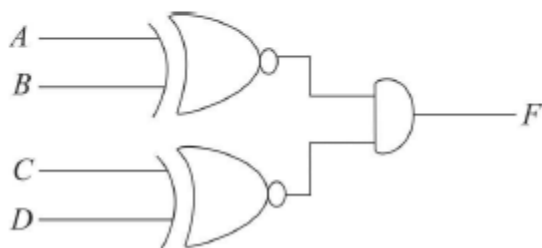

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4

7. Design a combinational circuit with three inputs, x , y , and z , and three outputs, A , B , and C . When the binary input is 0, 1, 2, or 3, the binary output is two greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is one less than the input.

Solution:

x	y	z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

$$A = \sum(2,3,5,6,7)$$

$x \backslash yz$	00	01	11	10
0	0	0	1	1
1	0	1	1	1

$$A = y + xz$$

$$B = \sum(0,1,4,7)$$

$x \backslash yz$	00	01	11	10
0	1	1	0	0
1	1	0	1	0

$$B = x'y' + y'z' + xyz$$

$$C = \sum(1,3,4,6)$$

$x \backslash yz$	00	01	11	10
0	0	1	1	0
1	1	0	0	1

$$C = x'z + xz' = x \oplus z$$

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4

8. Design a combinational circuit that generates the 9's complement of a decimal digit represented by a gray code.

Solution:

Decimal	Gray code				9's complement			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	1	1	0	1
1	0	0	0	1	1	1	0	0
2	0	0	1	1	0	1	0	0
3	0	0	1	0	0	1	0	1
4	0	1	1	0	0	1	1	1
5	0	1	1	1	0	1	1	0
6	0	1	0	1	0	0	1	0
7	0	1	0	0	0	0	1	1
8	1	1	0	0	0	0	0	1
9	1	1	0	1	0	0	0	0

Don't care terms: 8, 9, 10, 11, 14, 15

Simplified expressions (K-map):

AB \ CD	00	01	11	10
00	1	1		
01				
11			x	x
10	x	x	x	x

$$W = B'C'$$

AB \ CD	00	01	11	10
00	1	1	1	1
01			1	1
11			x	x
10	x	x	x	x

$$X = C + B'$$


AB \ CD	00	01	11	10
00				
01	1	1	1	1
11			x	x
10	x	x	x	x

$$Y = A'B$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	1		x	x
10	x	x	x	x

$$Z = D'$$

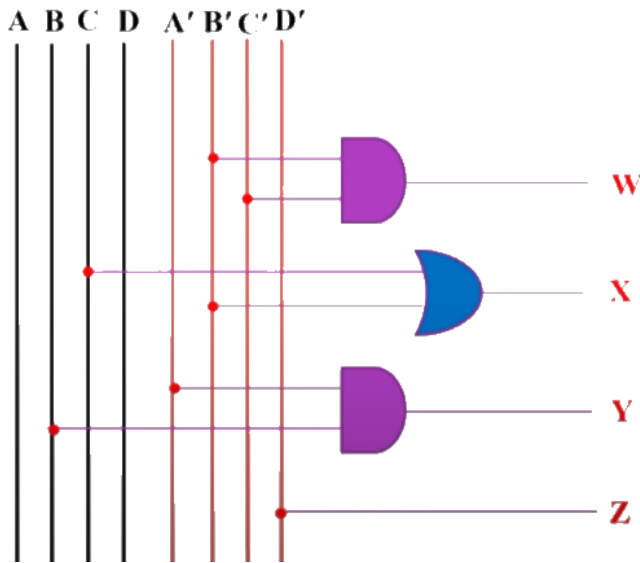EC1001: Digital Circuits
Solutions: Assignment-3_Chapter3&4



9. (a) Design a half-subtractor circuit with inputs x and y and outputs $Diff$ and B_{out} . The circuit subtracts the bits $y-x$ and places the difference in D and the borrow in B_{out} .
- (b) Design a full-subtractor circuit with three inputs x , y , B_{in} and two outputs $Diff$ and B_{out} . The circuit subtracts $y-x-B_{in}$, where B_{in} is the input borrow, B_{out} is the output borrow, and $Diff$ is the difference.


Solution:

x	y	$Diff.$	B_{out}
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	0

$$Diff. = x'y + xy'$$

$$= x \oplus y$$

$$B_{out} = xy'$$

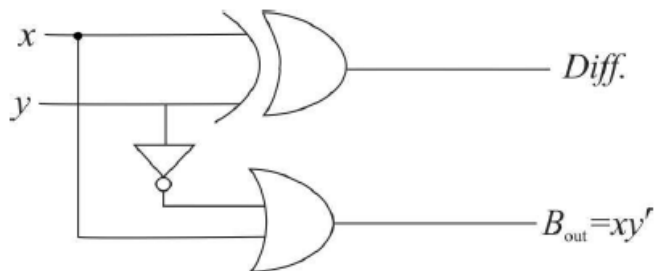

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4


x	y	Bin	$Diff.$	$Bout$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

$x \backslash y$	00	01	11	10
0	0	1	0	0
1	1	1	1	0

$$Bout = xy' + y' Bin + xBin$$

$$Diff. = x' (y \oplus Bin) + x (y \oplus Bin)'$$

$$= x \oplus y \oplus Bin$$

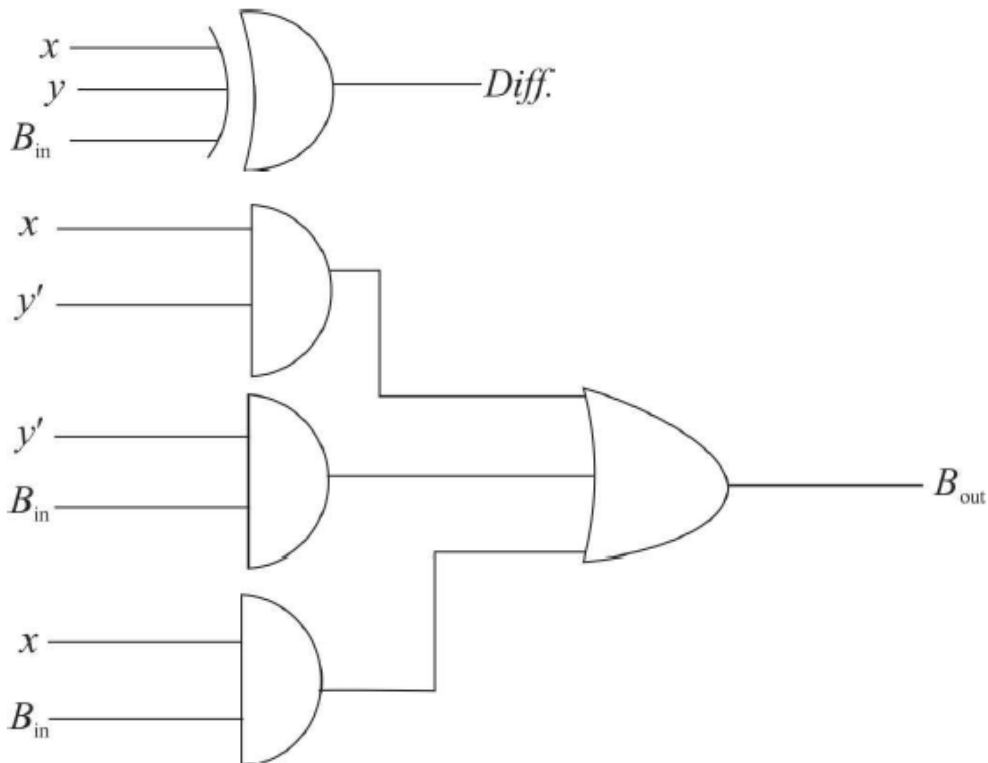

EC1001: Digital Circuits

Solutions: Assignment-3_Chapter3&4

10. Derive the two-level Boolean expression for the output carry C_4 shown in the lookahead carry generator of Fig. 4.12.

Solution:

$$C_4 = G_3 + P_3C_3 = G_3 + P_3(G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0)$$

$$= G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0$$