



Electrical Circuits for Engineers (EC1000)

Lecture-2 (a) (Chapter-2) Basic Laws



Overview

- Ohm's law
- Kirchoff's law
- Network topology
- Series and Parallel connection
- Verification of Ohm's law and Kirchoff's law
- Practice problems



Basic Laws

Ohm's law

Ohm's law states that “*The voltage ‘V’ across a resistor is directly proportional to the current ‘I’ flowing through the resistor*”.

$$V \propto I$$

$$V = I R$$

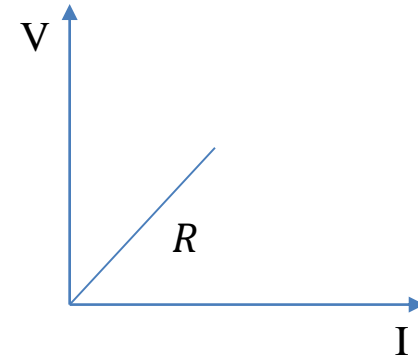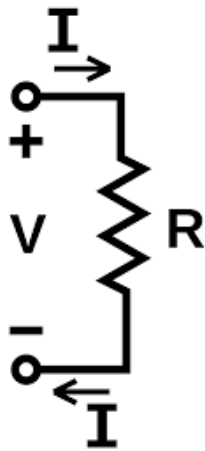

Some expressions for power

$$P = \frac{V^2}{R}$$


$$P = I^2 R$$

$$P = VI$$



Basic Laws


Open circuit

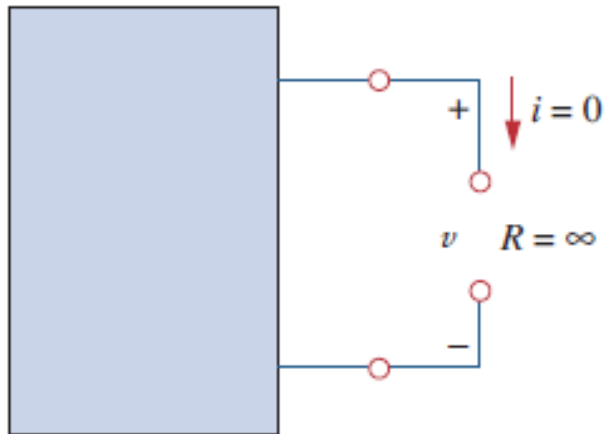

An **open circuit** is a circuit element with resistance approaching infinity.

$$R = \frac{V}{I}$$

Short circuit

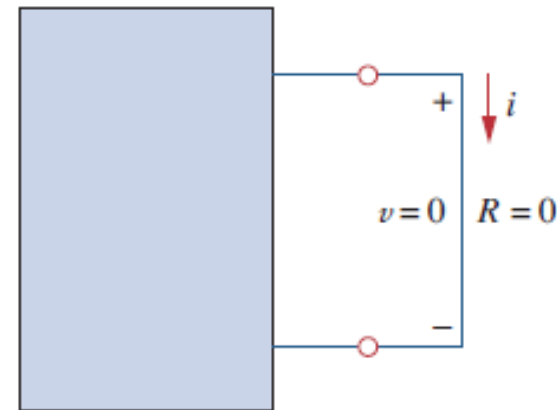

A **short circuit** is a circuit element with resistance approaching zero.



Basic Laws


Network topology

Node

A node is the point of connection between two or more branches.

Branch


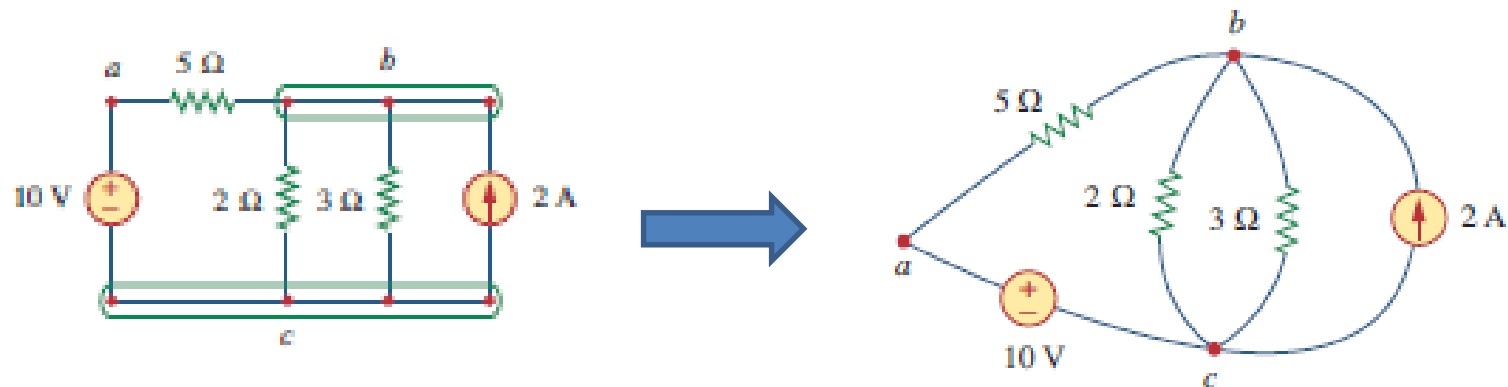
A branch represents a single element such as a voltage source or a resistor.





Basic Laws

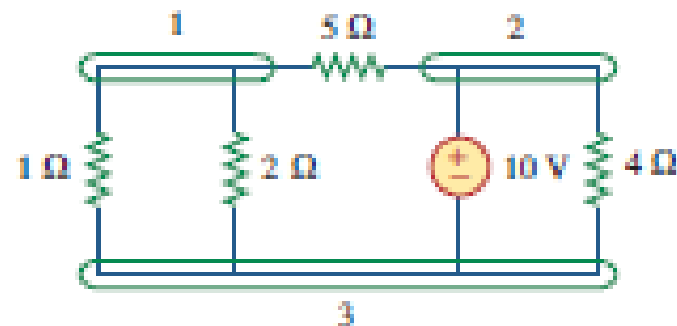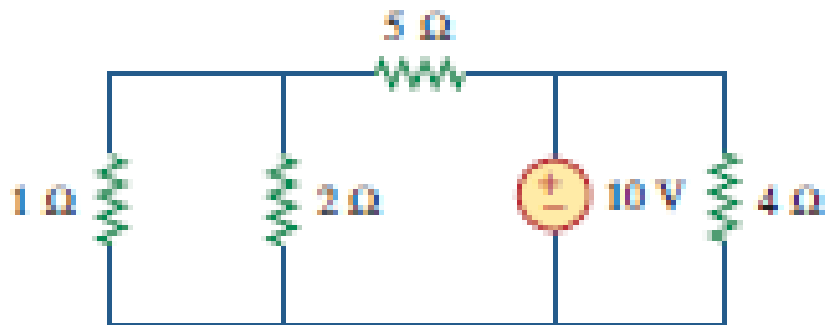1. How many nodes and branches does the below circuit have?








Basic Laws

Loop

A loop is any closed path in a circuit.

Mesh

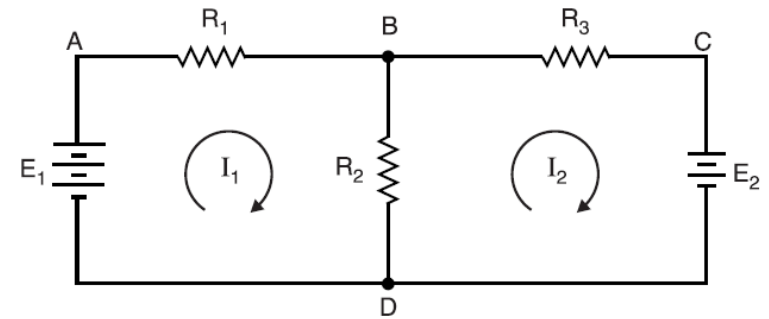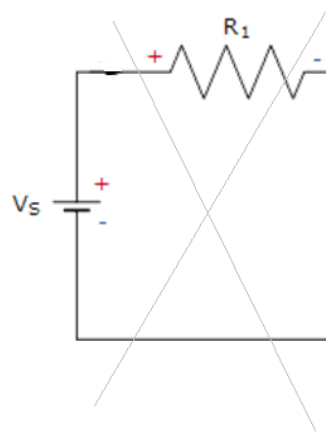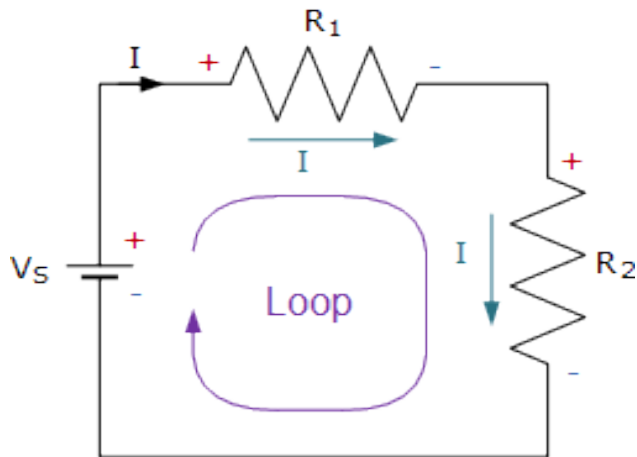A mesh is the most elementary form of a loop and cannot be further divided into other loops.






Basic Laws


Kirchhoff's current law (KCL)

Current law states that the “*Algebraic sum of currents entering a node (a closed bath) is zero*”.

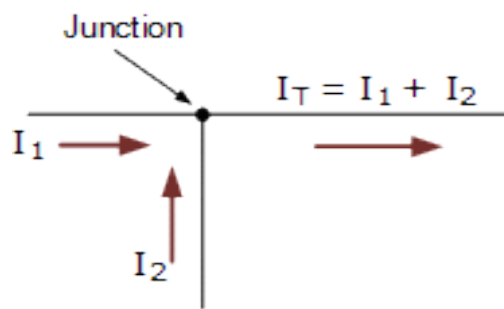i.e Total current entering a node is exactly equal to the total current leaving the same node.


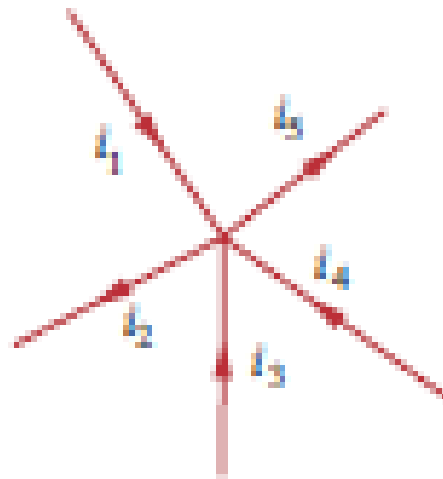
$$\Sigma I_{\text{in}} = \Sigma I_{\text{out}}$$
$$\Sigma I = 0$$



$$i_1 + i_3 + i_4 = i_2 + i_5$$




Basic Laws

Kirchoff voltage law

It states that the “Algebraic sum of all voltages around a closed path (loop) is zero”.

$$\sum v = 0$$

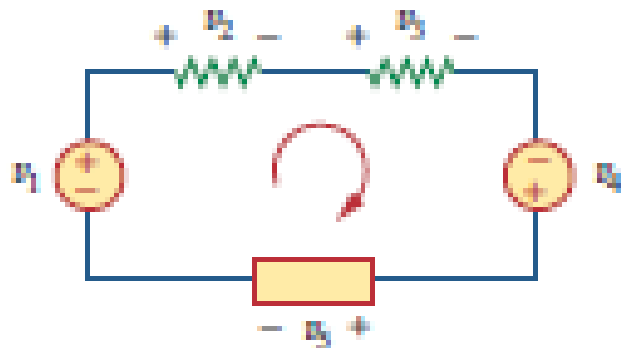


$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

i.e. Sum of voltage drops = Sum of voltage rises




Basic Laws

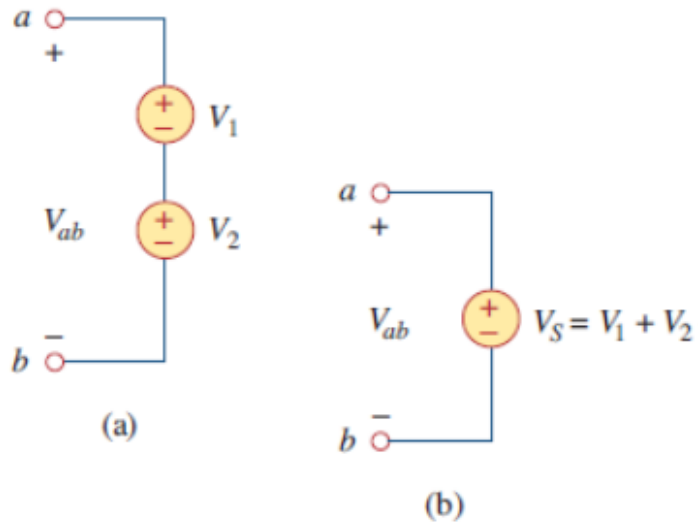


$$-V_{ab} + V_1 + V_2 = 0$$

$$V_{ab} = V_1 + V_2$$

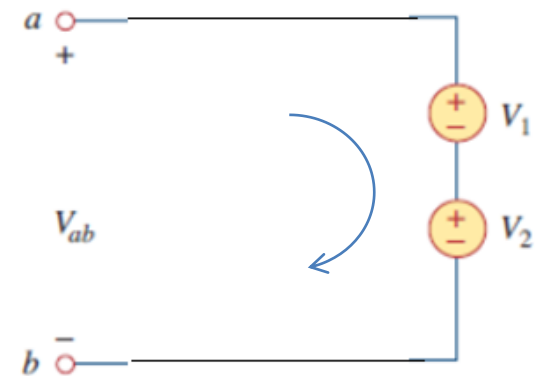



Basic Laws


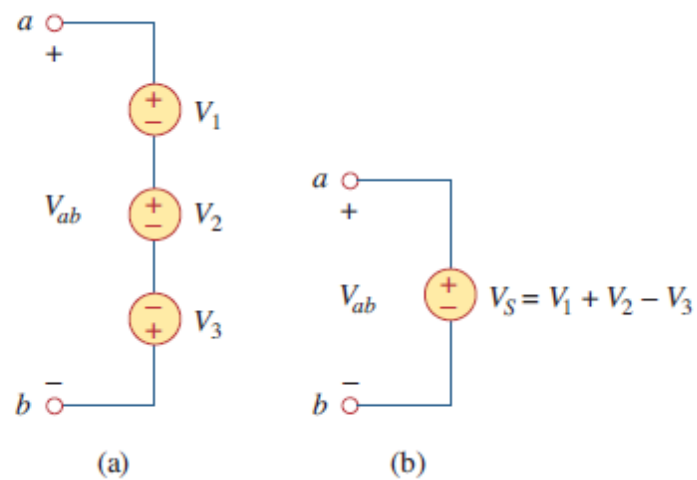


$$-V_{ab} + V_1 + V_2 - V_3 = 0$$


$$V_{ab} = V_1 + V_2 - V_3$$



Basic Laws

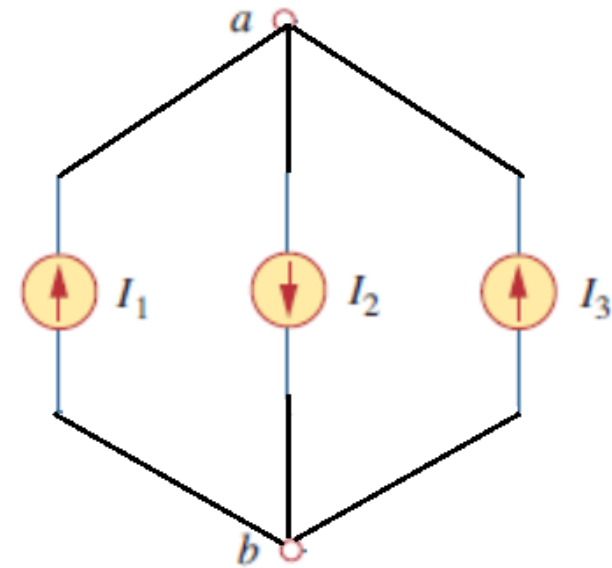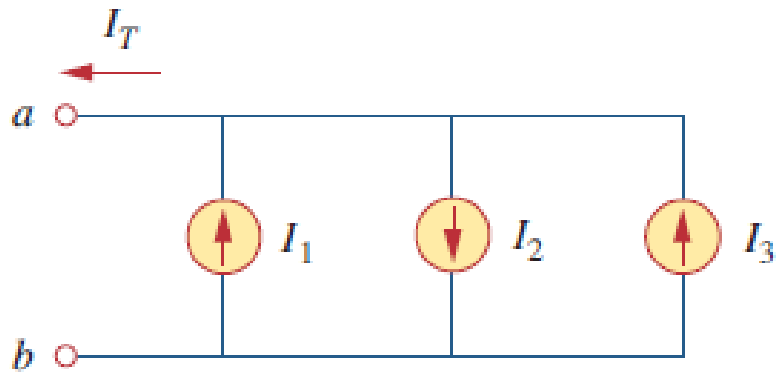



$$I_T = I_1 - I_2 + I_3$$

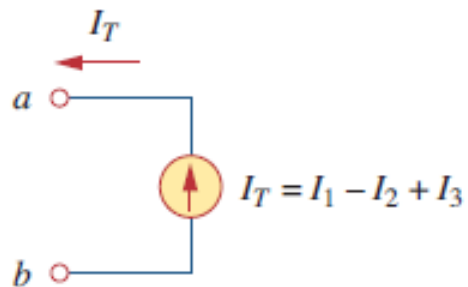



Problems

Find voltages v_1 and v_2 using KVL

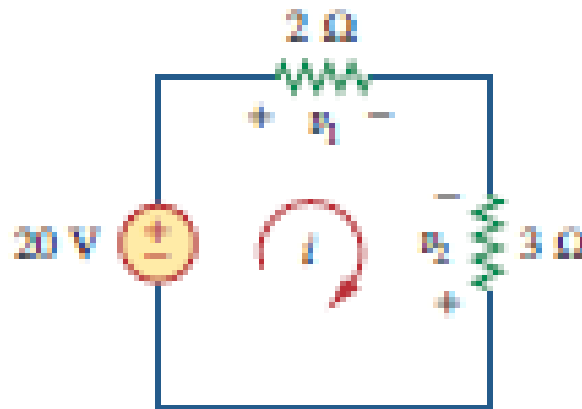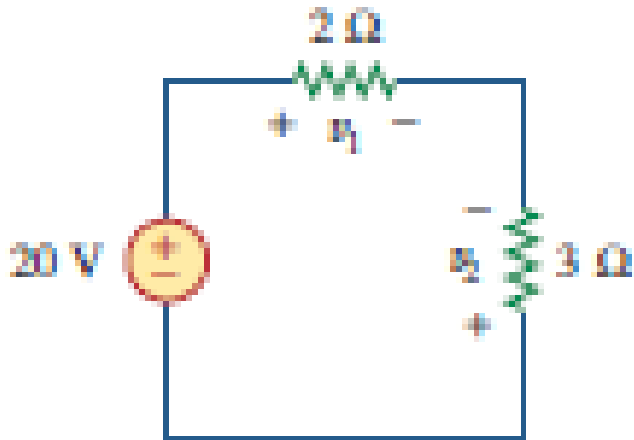


$$v_1 = 2i, \quad v_2 = -3i$$

$$-20 + v_1 - v_2 = 0$$

Ans: $v_1 = 8 \text{ V}$, $v_2 = -12 \text{ V}$

Find V_0 for the below circuit



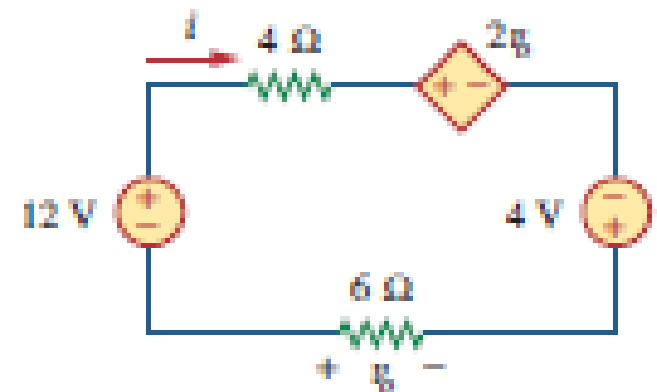


Ans: $v_0 = 48 \text{ V}$




Basic Laws

Parallel connection

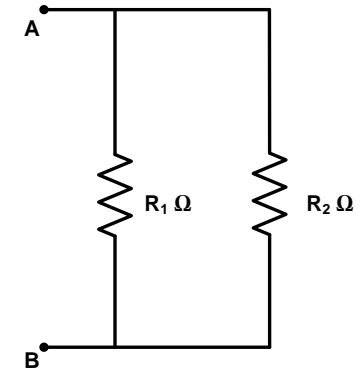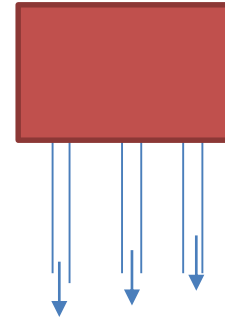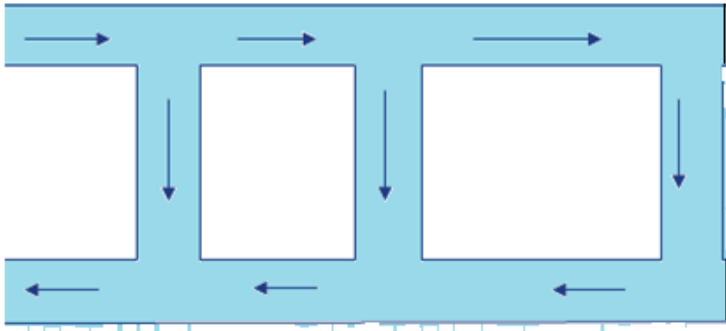


Series connection

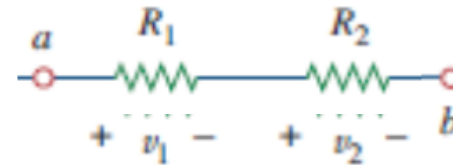



Basic Laws

Resistance in Series

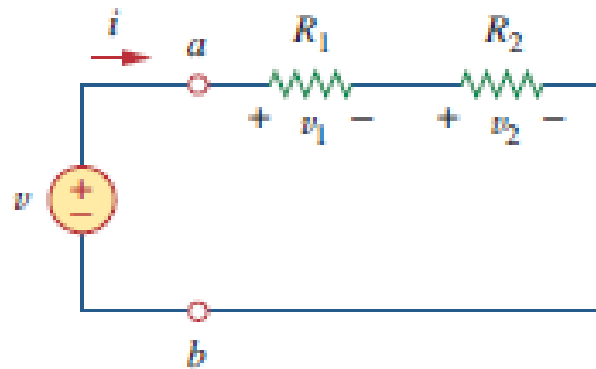

$$v_1 = iR_1, \quad v_2 = iR_2$$

$$\frac{i}{v} = \frac{1}{R_1 + R_2}$$

$$-v + v_1 + v_2 = 0$$

$$\frac{1}{R} = \frac{1}{R_1 + R_2}$$


$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$i = \frac{v}{R_1 + R_2}$$

$$R_{\text{eq}} = R_1 + R_2$$



Voltage division rule

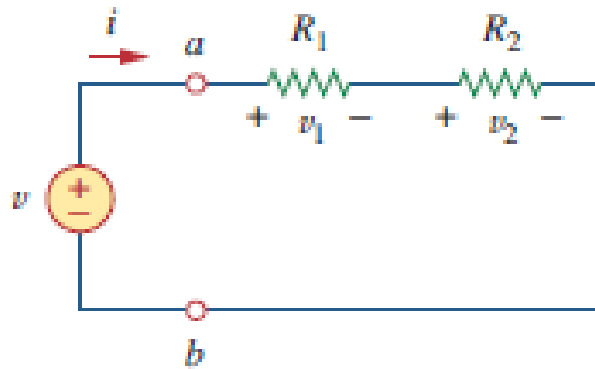


$$i = \frac{v}{R_1 + R_2}$$

$$v_1 = iR_1, \quad V_1 = \frac{R_1}{R_1 + R_2} V$$

$$v_2 = iR_2, \quad V_2 = \frac{R_2}{R_1 + R_2} V$$



Parallel Connection & Current Division

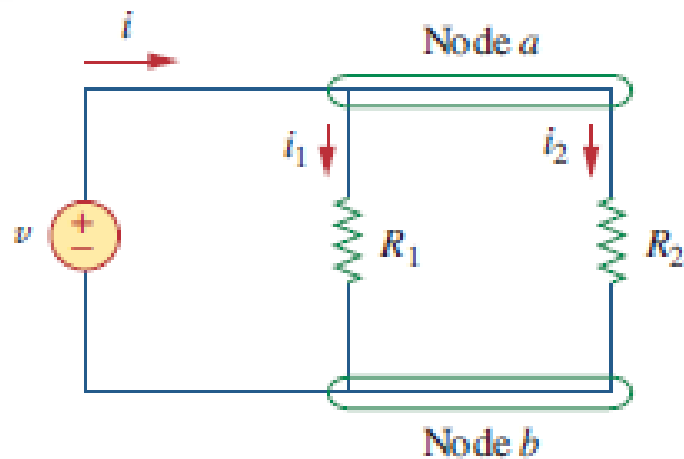

$$v = i_1 R_1 = i_2 R_2$$

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

Applying KCL at node a gives the total current i as

$$i = i_1 + i_2$$

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


$$i_1 = \frac{R_2 i}{R_1 + R_2}, \quad i_2 = \frac{R_1 i}{R_1 + R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$




Problems

Find R_{eq}

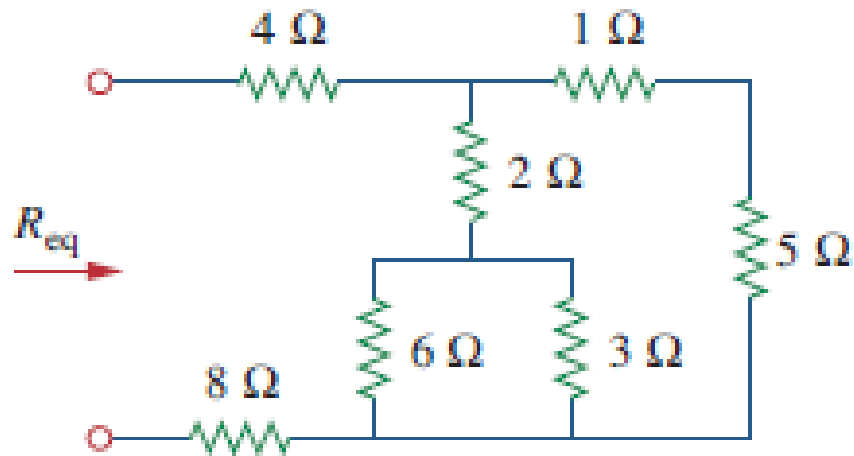


$$6\ \Omega \parallel 3\ \Omega = \frac{6 \times 3}{6 + 3} = 2\ \Omega$$

$$1\ \Omega + 5\ \Omega = 6\ \Omega$$

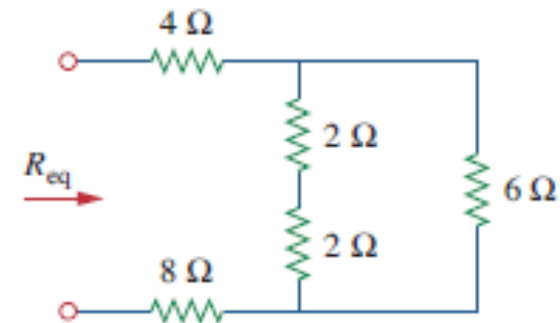

(a)

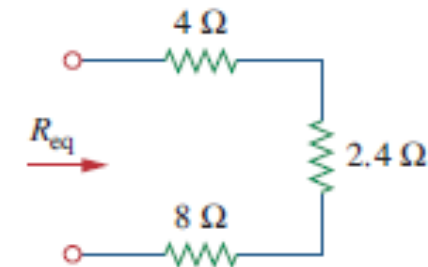


$$R_{eq} = 4\ \Omega + 2.4\ \Omega + 8\ \Omega = 14.4\ \Omega$$




Problems

1. Find R_{eq}

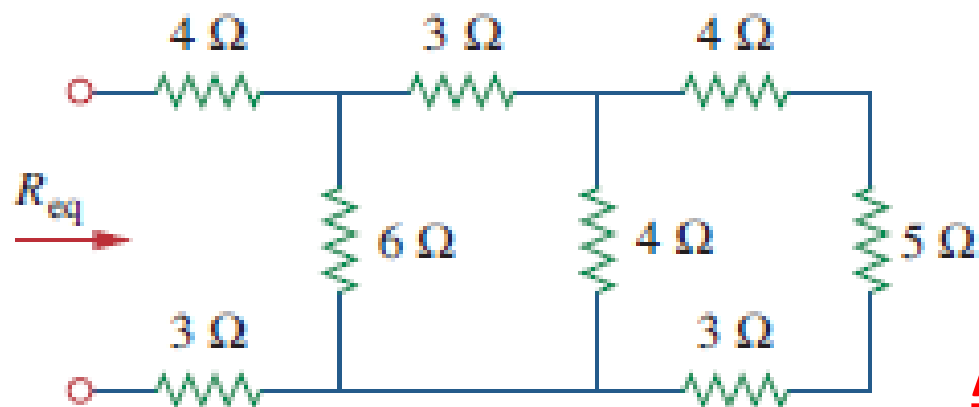

Ans: $10\ \Omega$

2. Find R_{eq}

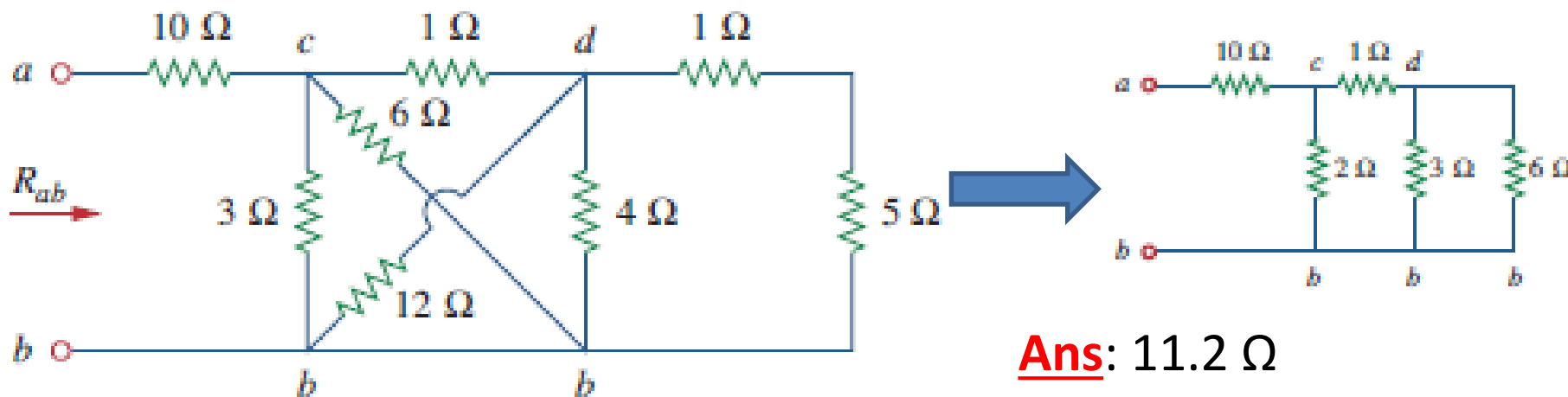


Ans: $11.2\ \Omega$




Problems

3. Find R_{ab}

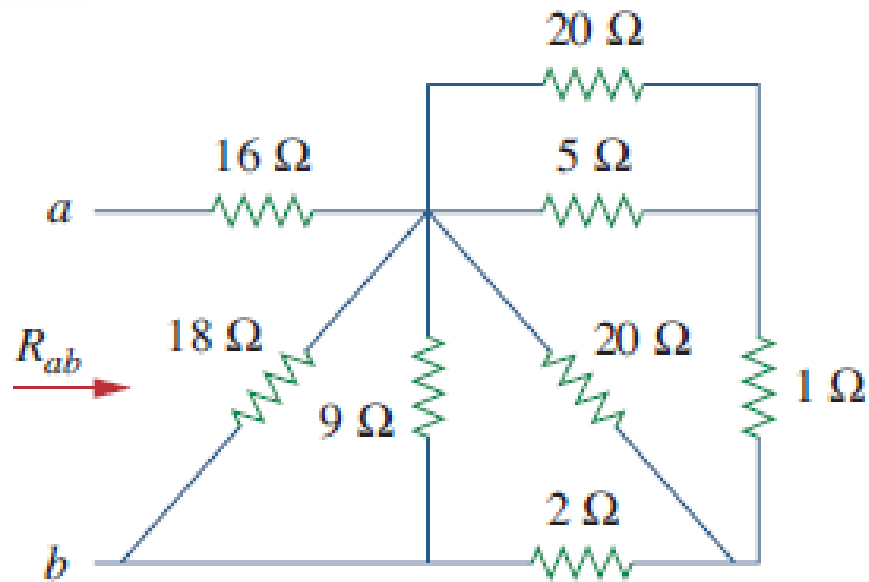

Ans: 10 Ω

4. Find G_{eq}

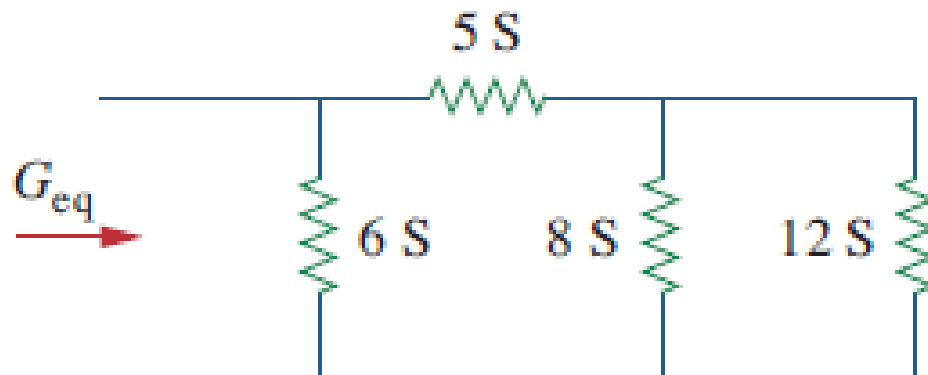


Ans: 10 S



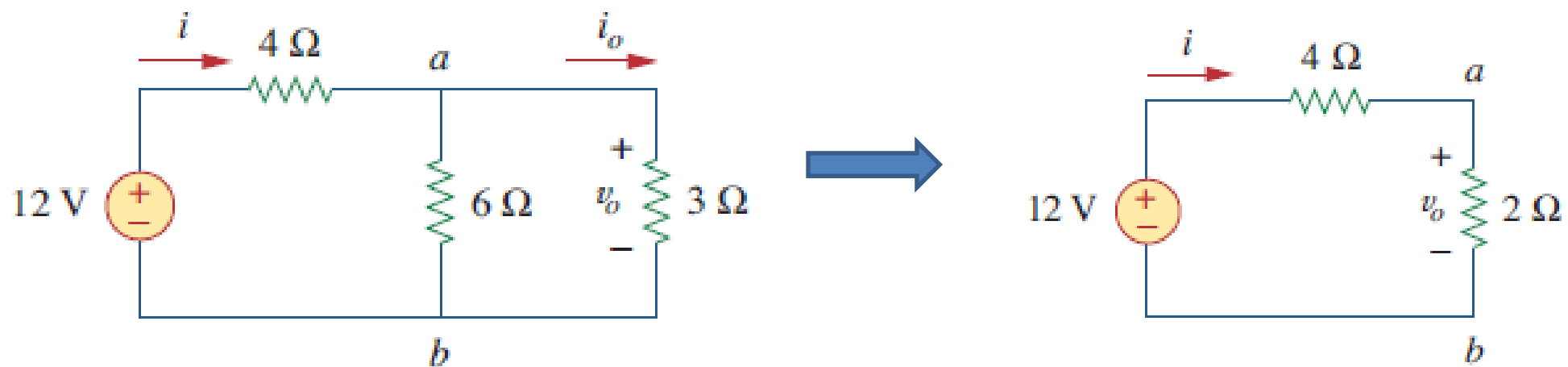Problems

Find i_o and v_o in the circuit shown here. Calculate the power dissipated in the $3\ \Omega$ resistor.




Ans: $4/3\ \text{A}$, $4\ \text{V}$, and $5.33\ \text{W}$



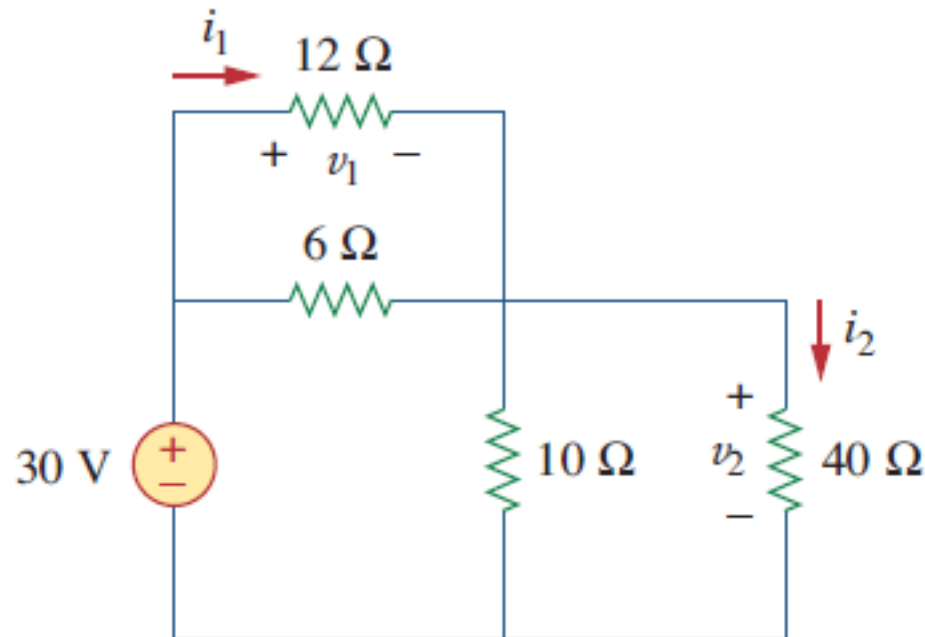Problems

Find v_1 and v_2 in the circuit shown here. Also calculate i_1 and i_2 , and power dissipated in $12\ \Omega$ and $40\ \Omega$ resistors.




Answer: $v_1 = 10\text{ V}$, $i_1 = 833.3\text{ mA}$, $p_1 = 8.333\text{ W}$, $v_2 = 20\text{ V}$, $i_2 = 500\text{ mA}$, $p_2 = 10\text{ W}$.




Practical Problems

Find the voltage V_{AB}

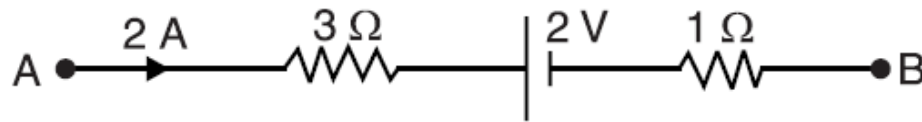

Find the current I

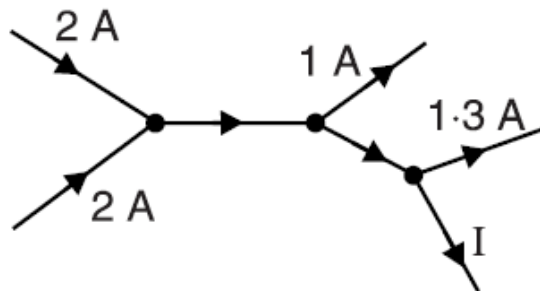



Thank You