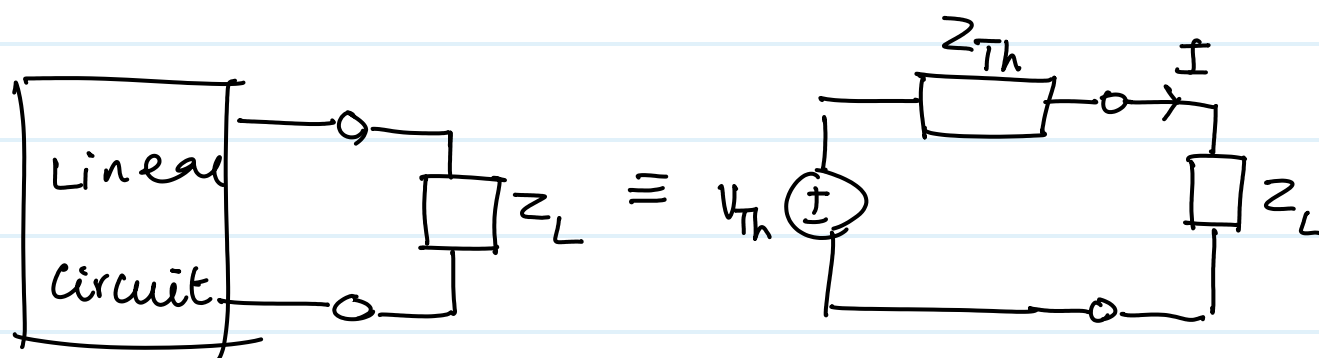


08/11/2023

MAXIMUM AVERAGE POWER TRANSFER



$$Z_{Th} = R_{Th} + jX_{Th}$$

$$Z_L = R_L + jX_L$$

Power is max if $R_L = R_{Th}$
equivalently, $\boxed{Z_L = \bar{Z}_{Th}}$

$$\frac{dP}{dR_L} = 0$$

$$\frac{dP}{dX_L} = 0$$

$$\boxed{Z_L = \bar{Z}_{Th}}$$


gives this.

$$P_{max} = \frac{V_{Th}^2}{8R_{Th}}$$

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = |Z_L|$$

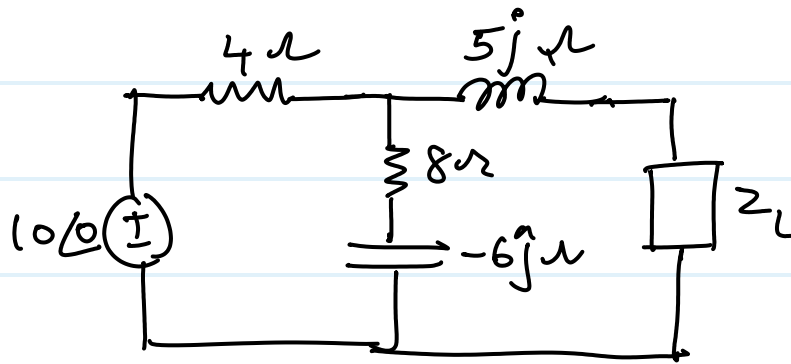EXAMPLE


find load impedance (Z_L) that gets max Power. Calculate P_{max}



$$P_{max} \Rightarrow \boxed{Z_L = \overline{Z_{Th}}}$$

$$P_{max} = \frac{|V_{Th}|^2}{8 R_{Th}}$$

find Z_{Th} :

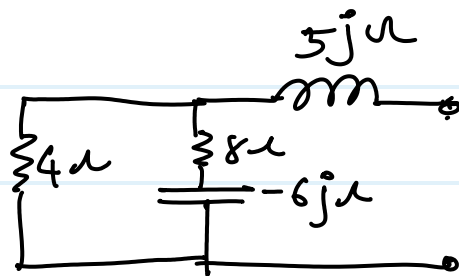

$$Z_{Th} = (4\Omega) \parallel (8 - 6j) + 5j$$

$$= \frac{4(8 - 6j)}{12 - 6j} + 5j$$


$$= \frac{44}{15} - \frac{8}{15}j + 5j$$

$$Z_{Th} = \frac{44}{15} + \frac{67}{15}j$$

$$Z_L = \overline{Z_{Th}} = \frac{44}{15} - \frac{67}{15}j$$

$$P_{\max} = \frac{V_{Th}^2}{8R_{Th}}$$

find V_{Th} :

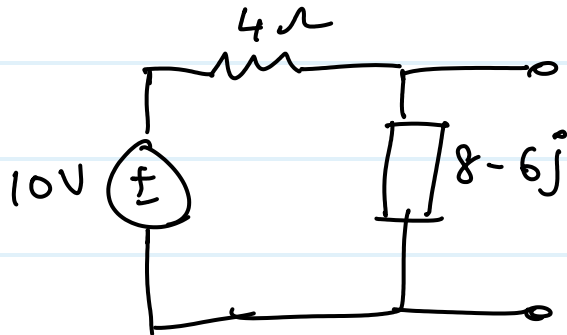

$$10 = 4\bar{i} + (8 - 6j)\bar{i}$$

$$10 = \bar{i}(12 - 6j)$$

$$\frac{10}{12 - 6j} = \bar{i}$$

$$\bar{i} = \left(\frac{2}{3} + \frac{1}{3}j \right) A$$


$$\left(\frac{2}{3} + \frac{1}{3}j \right) (8 - 6j)$$

$$V_{Th} = \frac{22}{3} - \frac{4}{3}j$$



R_{Th}

$$= 7.33 - 1.33j = 7.45 \angle -10^\circ$$

$$Z_{Th} = 2.93 + 4.47j$$

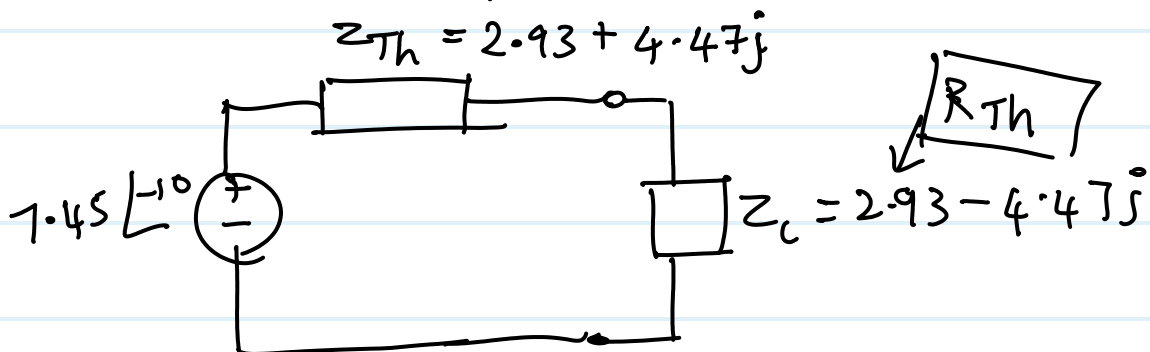


$$P_{\max} = \frac{(7.45)^2}{8(2.93)} = 2.368 W$$

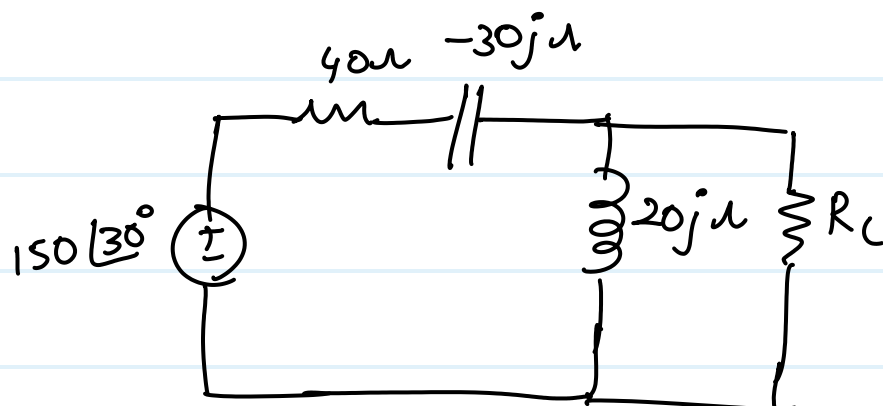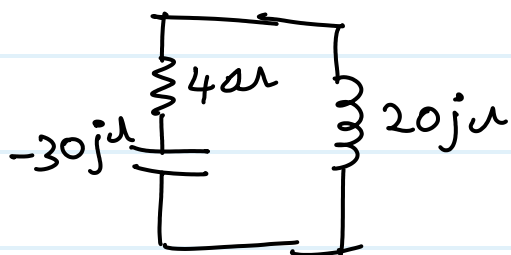EXAMPLE : Z_{Th} :

$$\begin{aligned}
 Z_{Th} &= (40 - 30j) \parallel 20j \\
 &= \frac{(40 - 30j)(20j)}{40 - 10j} \\
 &= \frac{160}{17} + \frac{380}{17}j
 \end{aligned}$$

$$R_L = |Z_{Th}| = 24.25$$

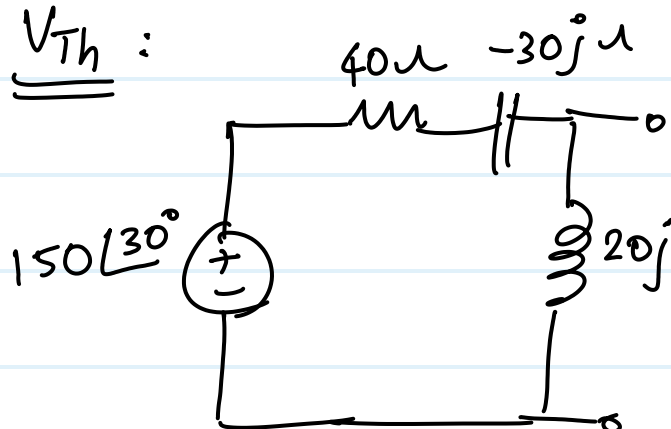 V_{Th} :

$$\begin{aligned}
 150\angle 30^\circ &= (40 - 30j + 20j)i \\
 \frac{150\angle 30^\circ}{40 - 10j} &= i \\
 &= 2.615 + 2.53j
 \end{aligned}$$

$$V_{Th} = -50.577 + 52.3j$$

$$= 72.76 \angle 134^\circ$$



$$P_{max} = \frac{V_{Th}^2}{8R_{Th}} \leftarrow \underline{\underline{Re(Z_{Th})}}$$

$$\frac{(72.76)^2}{8 \times \left(\frac{160}{17}\right)} = \underline{\underline{70.311 \text{ V}}}$$

Effective (or) RMS Value

$$P = \frac{1}{T} \int_0^T i^2 R dt = R \frac{1}{T} \int_0^T i^2 dt = I_{RMS}^2 R$$
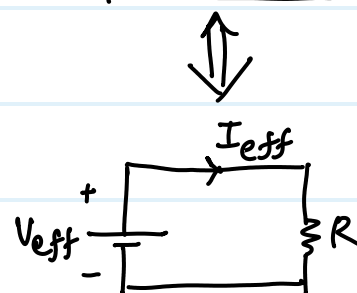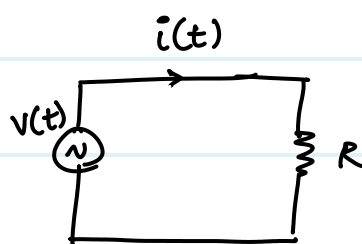
$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{RMS}$$



$$i(t) = I_m \cos \omega t$$

$$i^2(t) = I_m^2 \cos^2 \omega t$$

$$i^2(t) dt = I_m^2 \left(\frac{1 + \cos 2\omega t}{2} \right) dt$$

$$\int i^2(t) dt = I_m^2 \left(\int_0^T \frac{dt}{2} + \int_0^T \frac{\cos 2\omega t}{4\omega} d(2\omega t) \right)$$


$$\int i^2(t) dt = I_m^2 \left[\frac{T}{2} + \left[\frac{\sin 2\omega t}{4\omega} \right]_0^T \right] = \frac{I_m^2 T}{2}$$

$$\frac{\int i^2(t) dt}{T} = \frac{I_m^2}{2} \Rightarrow \sqrt{\frac{\int i^2(t) dt}{T}} = \frac{I_m}{\sqrt{2}} = I_{RMS} //$$

Avg. Power using RMS:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos(\theta_v - \theta_i) \\ = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

EXAMPLE : find RMS , $R = 10\Omega$

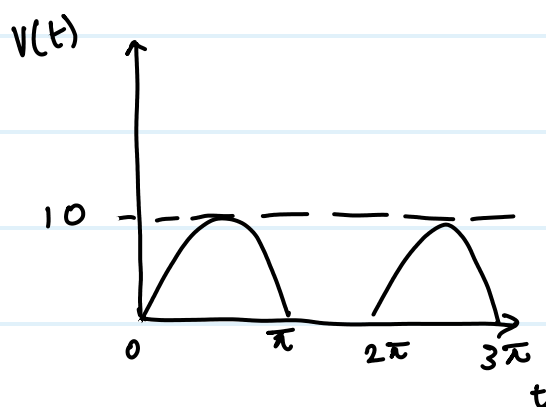


$$v(t) = \begin{cases} 10 \sin t & 0 < t < \pi \\ 0 & \pi < t < 2\pi \end{cases}$$

$$V_{RMS}^2 = \frac{1}{T} \int_0^T v^2(t) dt \\ = \frac{1}{T} \left[\int_0^{\pi} 100 \sin^2 t dt + \int_{\pi}^{2\pi} 0^2 dt \right] \\ = \frac{100}{T} \int_0^{\pi} \left(\frac{1 - \cos 2t}{2} \right) dt \\ = \frac{100}{2T} \left[t \right]_0^{\pi} = \frac{100}{2\pi} \pi \\ = 25$$

$$P = \frac{V_{RMS}^2}{R} = \frac{25}{10} = 2.5 \text{ W}$$

$$V_{RMS} = \sqrt{25} = 5 \text{ V}$$

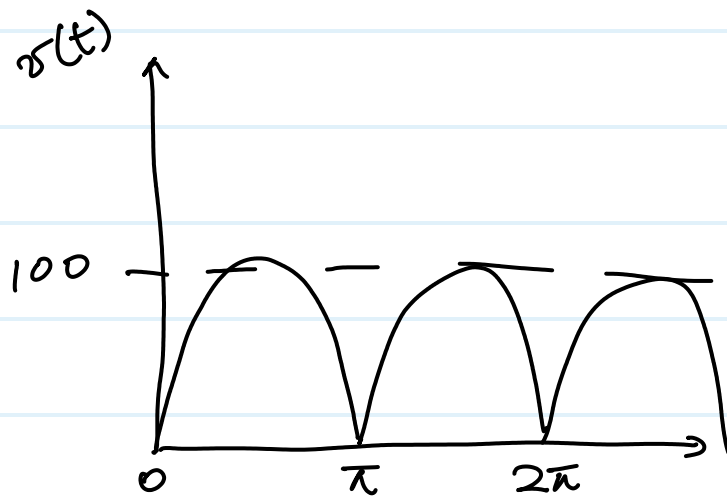

find RMS

find P_{avg}

$R = 6\Omega$

find $P_{6\Omega}$

$$0 < t < \pi : v(t) = 10 \sin t \text{ V}$$

$$\pi < t < 2\pi : v(t) = 10 \sin t \text{ V}$$

$$v_{RMS} = \sqrt{\frac{\int_0^T v^2(t) dt}{T}} = \sqrt{\frac{\int_0^{\pi} 100 \sin^2 t dt + \int_{\pi}^{2\pi} 100 \sin^2 t dt}{T}}$$

09/11/2023

APPARENT POWER (S)

↳ "S" is the product of rms. values of Voltage and current. Its the "Rating" of equipments.

$$\hookrightarrow P_{avg} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \underbrace{V_{RMS} I_{RMS}}_{\text{"S"}} \underbrace{\cos(\theta_v - \theta_i)}_{\text{power factor ("pf")}}$$

$$\Rightarrow P_{avg} = S \cdot pf$$

pf : cosine of phase diff. b/w
voltage & current
(or) cosine of \angle of load
impedence.

↳ S \rightarrow has units as Volt-Ampere (VA)

\rightarrow we specifically say VA & not W to distinguish

S from P_{avg} ($P_{avg}/P \rightarrow$ active power - useful/real power)

↳ $pf = \frac{P}{S}$; P \rightarrow active power , S \rightarrow Apparent power

Purely Resistive (only R)	$\theta_v - \theta_i = 0, P_f = 1$	$P/S = 1$, all P_{avg} consumed
Purely reactive (only L or C)	$\theta_v - \theta_i = \pm 90^\circ$ $P_f = 0$	$P = 0$, no P_{avg} consumed
Resistive & Reactive (R and L or C)	<ul style="list-style-type: none"> $\theta_v - \theta_i > 0$ $\theta_v - \theta_i < 0$ 	<ul style="list-style-type: none"> Lagging-inductive Leading-capacitive


* bill = actual power + pf.penalty * lagging / leading
↪ wrt current.

to make $P_f \rightarrow 1$, L & C are used together.

Capacitors are used as condensers in order to improve P_f .

COMPLEX POWER (S)

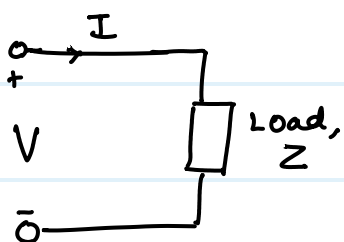↳ "S" is the product of the voltage and the complex conjugate of the current



$$V = V_m \angle \theta_v$$

$$I = I_m \angle \theta_i$$

$$I^* = I_m \angle -\theta_i$$

$$S = \frac{1}{2} V I^* = V_{RMS} I_{RMS} \angle \theta_v - \theta_i$$

$$= V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

$$+ (V_{RMS} I_{RMS} \sin(\theta_v - \theta_i))j$$

reactive power

↓
Allows work to happen (to create \vec{B} field)

active → actual work done by source

measured in VAR

$$S = P + Qj$$

↙
active power

↓
reactive power

(exchanged b/w source & reactive load)

$Q = 0 \rightarrow$ resistive, $pf = 1$


$Q < 0 \rightarrow$ capacitive, leading pf

$Q > 0 \rightarrow$ inductive, lagging pf

Q is reqd.,


but in low levels..

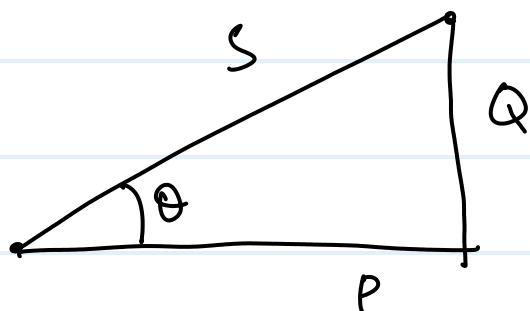else, more power will be drawn by reactive load...



$$S = P + Qj \therefore |S| = \sqrt{P^2 + Q^2}$$
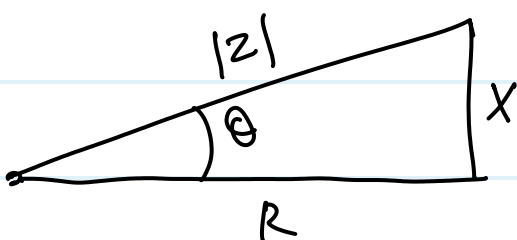
$$\cos \theta = \frac{P}{S} \quad ; \quad \sin \theta = \frac{Q}{S}$$



$$Z = R + jX = \sqrt{R^2 + X^2} = |Z|$$

$$\cos \theta = \frac{R}{|Z|}$$

$$\theta = \tan^{-1} \left(\frac{X}{R} \right)$$

$$\cos \theta = \cos \left[\tan^{-1} \left(\frac{X}{R} \right) \right]$$

Apparent Power $\rightarrow V_{RMS} \cdot I_{RMS} = \sqrt{P^2 + Q^2}$ (S)

Real Power $\rightarrow S \cos(\theta_v - \theta_i)$ ($\text{Re}(S)$) \rightarrow (P)

Reactive Power $\rightarrow S \sin(\theta_v - \theta_i)$ ($\text{Im}(S)$)

Power factor $\rightarrow \cos(\theta_v - \theta_i)$ ($P/S \rightarrow pf$)

14/11/2023

EXAMPLE :

$$i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$$

$$v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$$

find \rightarrow Apparent Power, power factor
(S) (P/S)


$$S = V_{\text{RMS}} I_{\text{RMS}} = \frac{V_0 I_0}{2} = \frac{4 \times 120}{2} = 240 \text{ VA}$$

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(-20 - 10) = +\cos 30 = \frac{\sqrt{3}}{2} = 0.867$$

$\theta_i > \theta_v \Rightarrow \text{pf: leading}$
capacitive

$$\begin{aligned} \text{pf} = R/Z &= \frac{\text{Re}(Z)}{Z} = \frac{30 \cos 30^\circ}{30 \angle -30^\circ} & Z &= \frac{V(t)}{i(t)} \\ &= \cos 30^\circ / 30^\circ \leftarrow \text{leading} & &= \frac{V_m \angle \theta_v}{I_m \angle \theta_i} \\ &= 0.867 \angle 30^\circ & &= Z_m \angle \theta_v - \theta_i \\ & & &= 30 \angle -30^\circ \end{aligned}$$

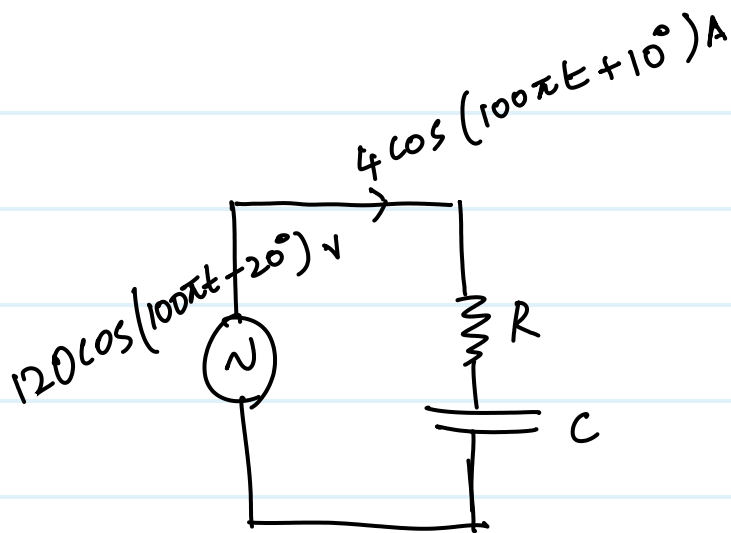$30 \angle -30^\circ \rightarrow 30 \cos(-30^\circ) + j 30 \sin(-30^\circ)$



$$R = \operatorname{Re}(Z)$$

$$= 30 \cos 30$$

$$= 30 \times 0.867 = 25.98 \Omega$$

$$I_m(Z) = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

$$-15j = -\frac{j}{\omega C} \Rightarrow \omega C = \frac{1}{15}$$

$$\Rightarrow C = \frac{1}{15 \times 100\pi}$$


$$= \frac{1}{1500\pi}$$

$$= 2.12 \times 10^{-6} \text{ F}$$

$$= 2.12 \mu\text{F}$$

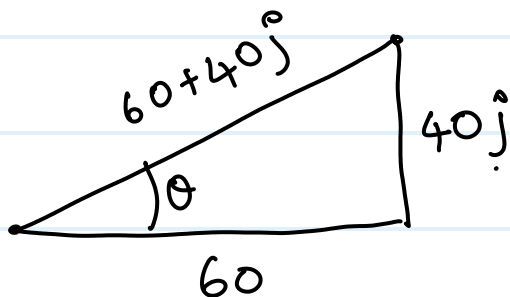EXAMPLE:

$$Z = (60 + 40j) \Omega; v(t) = 320 \cos(377t + 10^\circ) \text{ V}$$



$$\cos \theta = \frac{60}{|60 + 40j|} = 0.832$$

$$Z = R + jX, \quad X \rightarrow +ve \Rightarrow \theta_v - \theta_i > 0$$


$$\Rightarrow |\theta_v > \theta_i| \rightarrow \text{lagging (inductive)}$$

$$\frac{1}{2} \times \left(\frac{320 \angle 10^\circ \cdot 320 \angle 10^\circ}{72.111 \angle 33.7^\circ} \right) = \frac{320^2}{2 \times 72.111} \angle -13.7^\circ = \frac{1420}{2} \angle -13.7^\circ \text{ Check}$$

$$= 710 \angle -13.7^\circ \text{ VA}$$

find pf, P_{avg} .

EXAMPLE

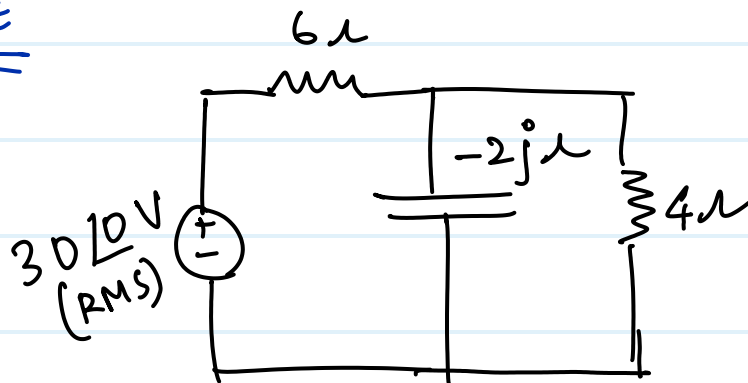


$$\frac{-8j}{4-2j} = \frac{4}{5} - \frac{8j}{5}$$

$$\frac{4}{5} + 6 = \frac{34}{5}$$

$$Z = 6.98 \angle -13.24^\circ \Omega$$
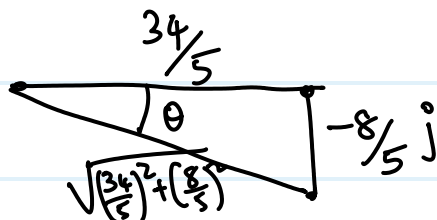
$$Z_{eq} = \left(\frac{34}{5} - \frac{8j}{5} \right) \Omega$$



$$\cos \theta = \frac{\left(\frac{34}{5} \right)}{6.98} = \frac{6.8}{6.98} = 0.9734 \quad (\text{leading})$$

↓
capacitive

$$\begin{aligned} \text{Average } P &= V_{RMS} \cdot I_{RMS} \cos(\theta_v - \theta_i) \\ &= 30 \times 4.29 \times 0.9734 \\ &= 125.5 \end{aligned}$$

$$\begin{aligned} i_{RMS} &= \frac{V_{RMS}}{Z} \\ &= \frac{30 \angle 0}{6.98 \angle -13.24} \\ &= 4.29 \angle 13.24 \end{aligned}$$

EXAMPLE

$$v(t) = 60 \cos(\omega t - 10^\circ) \text{ V}$$

$$i(t) = 1.5 \cos(\omega t + 50^\circ) \text{ V}$$

- (a) complex & apparent power, (b) real & reactive power
(c) pf & impedance.

$$(a) \quad V = 60 \angle -10^\circ ; V_{\text{RMS}} = \frac{60}{\sqrt{2}} \angle -10^\circ \quad \& \quad I = 1.5 \angle 50^\circ ;$$

$$I_{\text{RMS}} = \frac{1.5 \angle 50^\circ}{\sqrt{2}}$$

$$\text{Complex } P = V_{\text{RMS}} \cdot \overline{I_{\text{RMS}}}$$

$$= \frac{60}{\sqrt{2}} \angle -10^\circ \cdot \frac{1.5}{\sqrt{2}} \angle -50^\circ = 45 \angle -60^\circ \text{ VA}$$

$$\text{Apparent: } V_{\text{RMS}} \cdot I_{\text{RMS}} = \frac{60}{\sqrt{2}} \times \frac{1.5}{\sqrt{2}} = 45 \text{ VA.}$$

$$(b) \quad \text{Real} = \text{Re}(\text{Complex } P) = 45 \cos(-60^\circ) = 22.5 \text{ VA}$$

$$\text{Reactive} = \text{Im}(\text{Complex } P) = 45 \sin(-60^\circ) = -45 \times 0.867$$

$$= -38.97 \text{ VAR}$$

(leading)

↓
capacitive

$$(c) \quad \text{pf} = \cos(\theta_v - \theta_i) = \cos(-60^\circ) = 0.5 \text{ (leading)}$$

$$Z = \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ} = 40 \angle -60^\circ \Omega$$

EXAMPLE

$$V_{\text{RMS}} = 110 \angle 85^\circ \text{ V}, \quad I_{\text{RMS}} = 0.4 \angle 15^\circ \text{ A}$$

- (a) complex & apparent powers. (b) real and reactive powers (c) the power factor & load impedance.

