
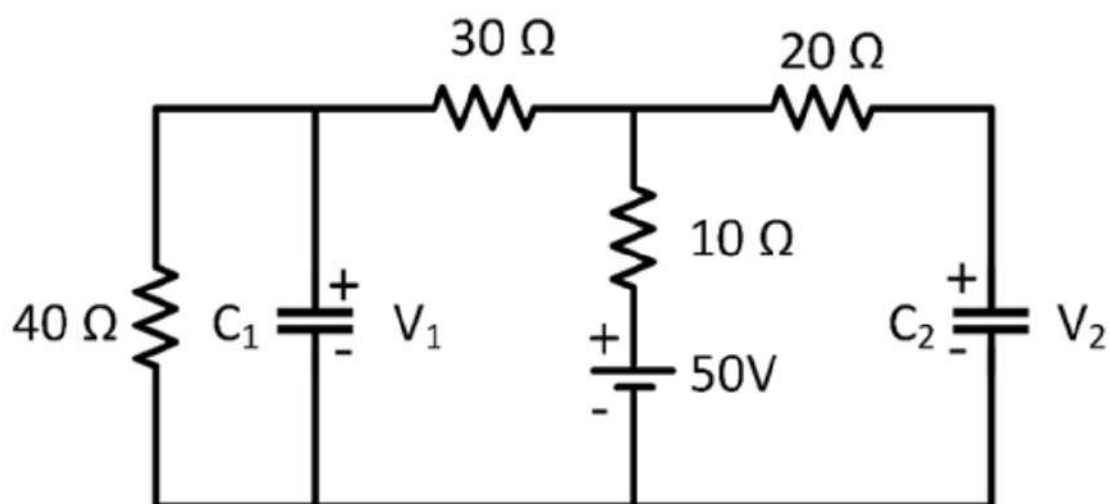


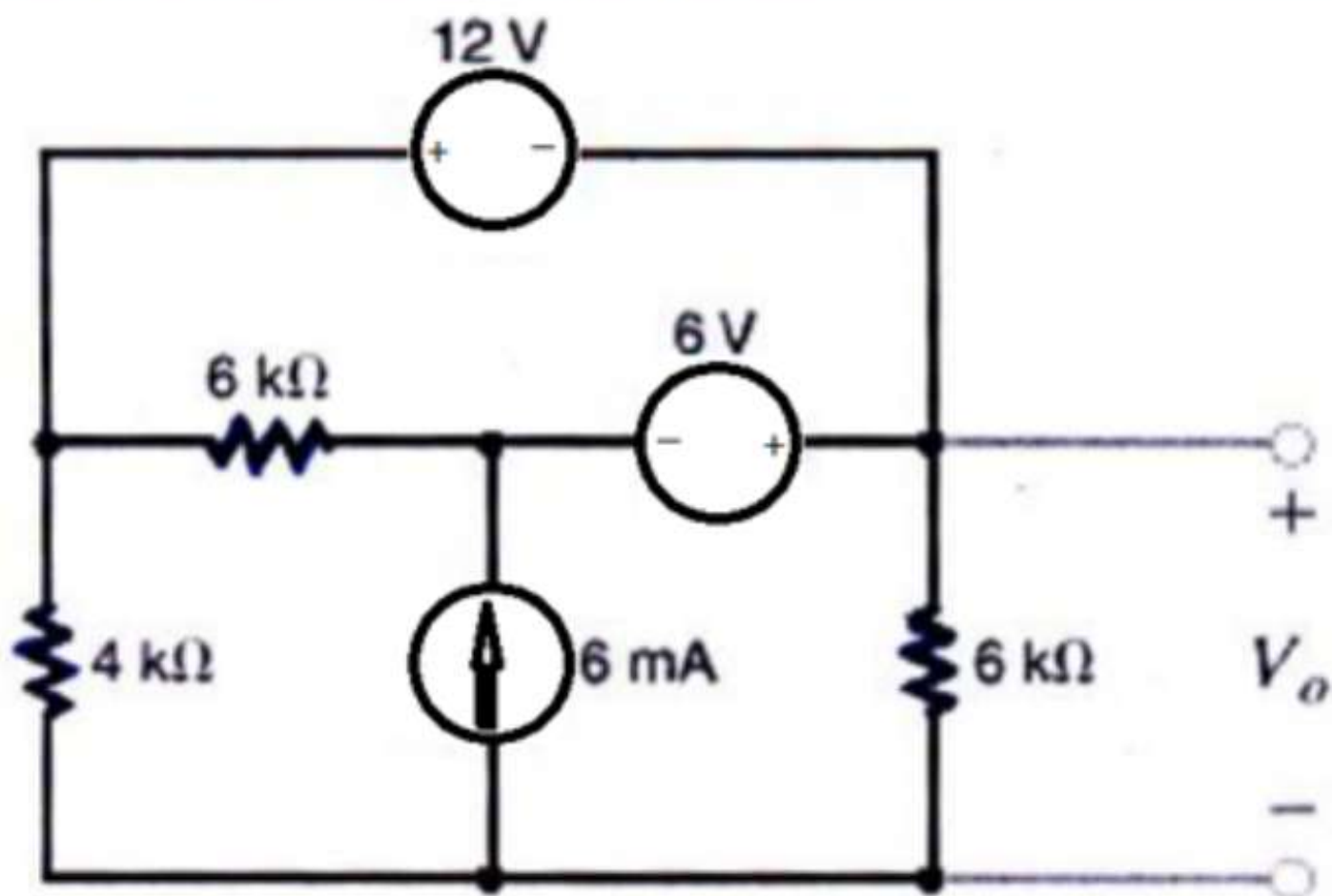
Find the voltage across the capacitors (V_1 & V_2) in the below circuit under dc conditions.




Find V_o for the circuit shown.



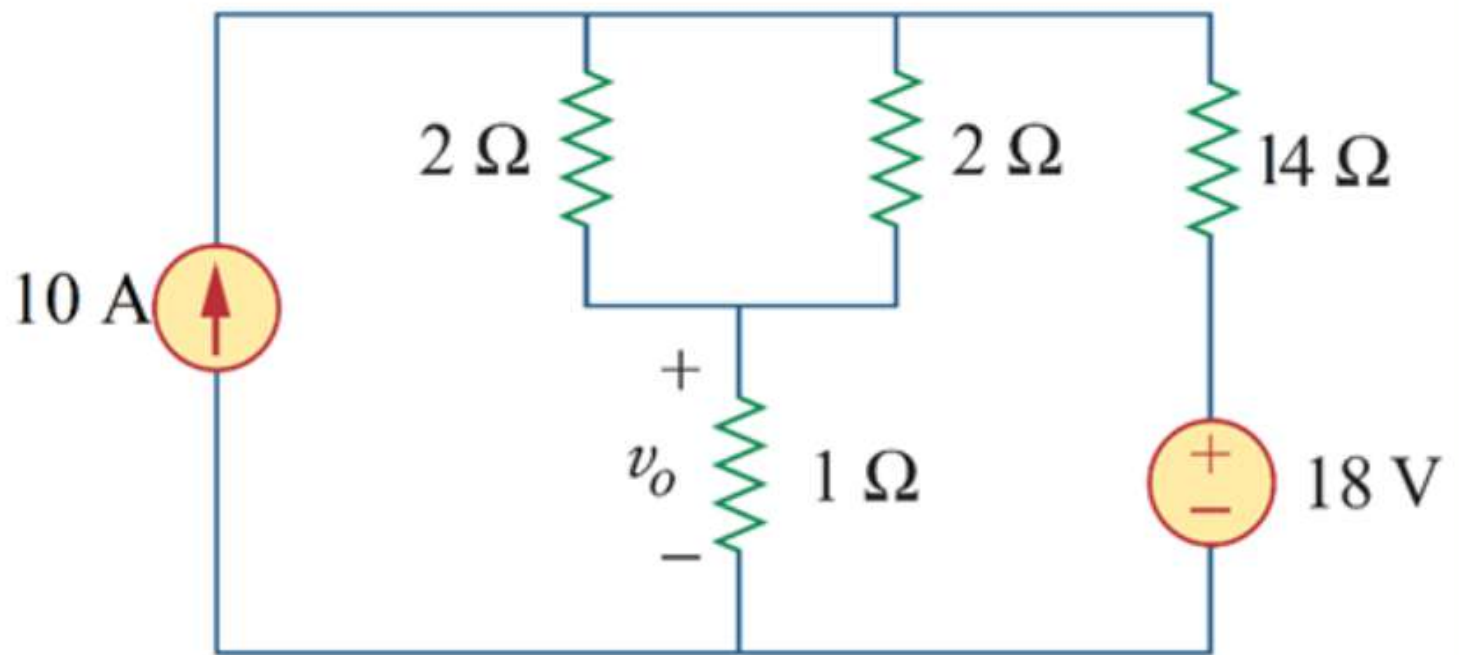
Find the V_o in the circuit by using superposition principle.



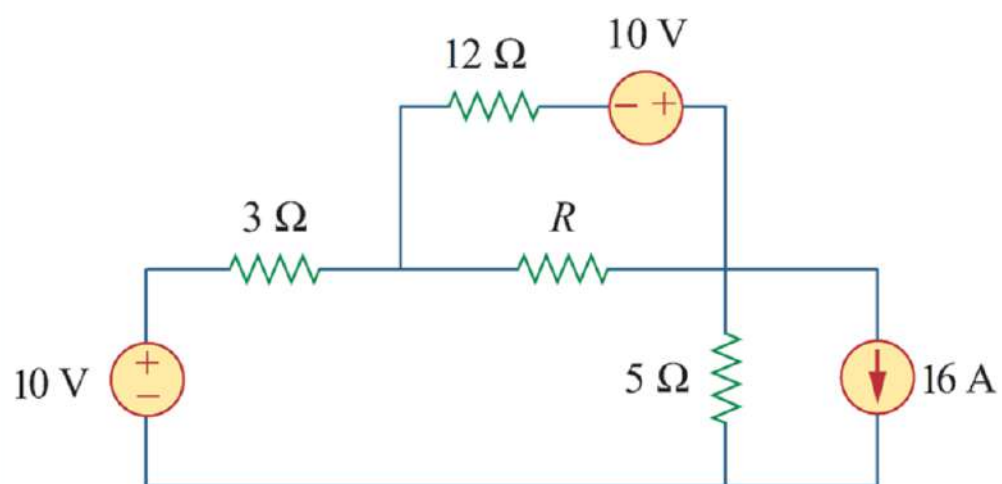Calculate the maximum power delivered to the variable resistor R shown in the circuit. Also find the value of R .



Calculate I_o in the circuit.

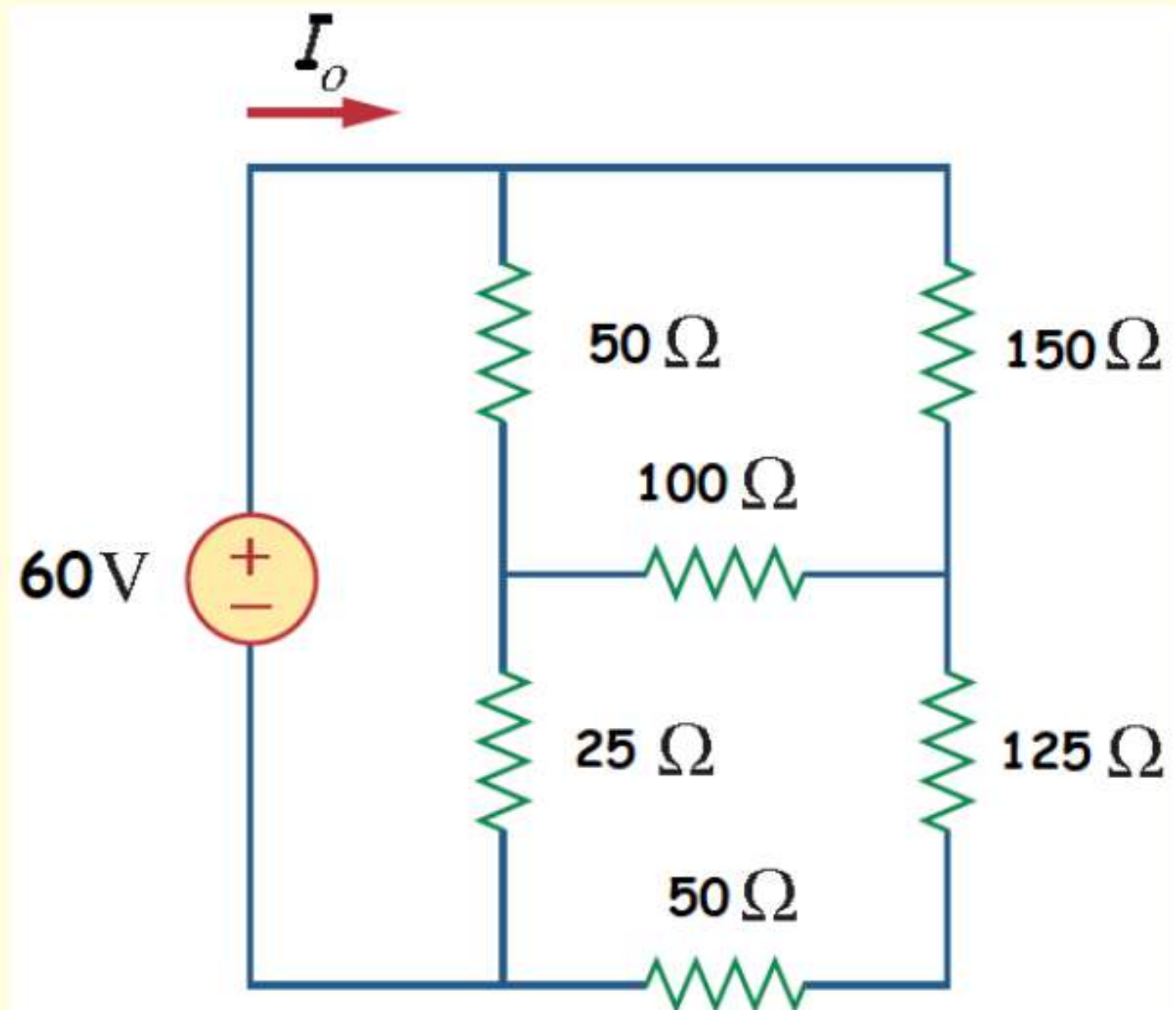

8. a) A 50 mH inductor is connected in parallel with a 2.5 k Ω resistor. The current through the inductor is $i(t) = 50 e^{-100t}$ mA.


(i) Find the voltage across the inductor (V_L).

(ii) Find the voltage across the resistor (V_R).


(iii) Calculate the energy in the inductor at $t=0$.

(3 marks)

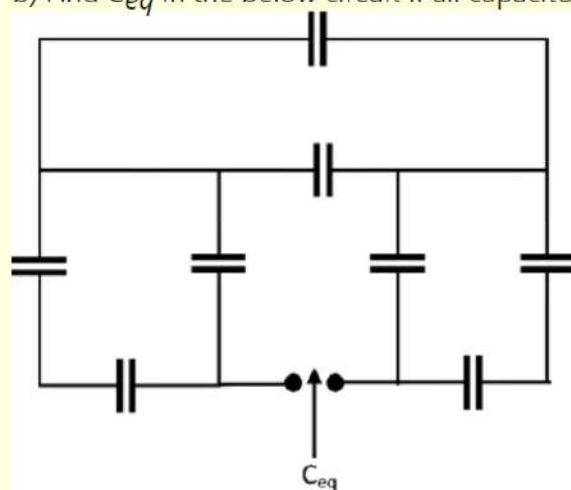b) Find C_{eq} in the below circuit if all capacitors are 10 μ F. (2 marks)



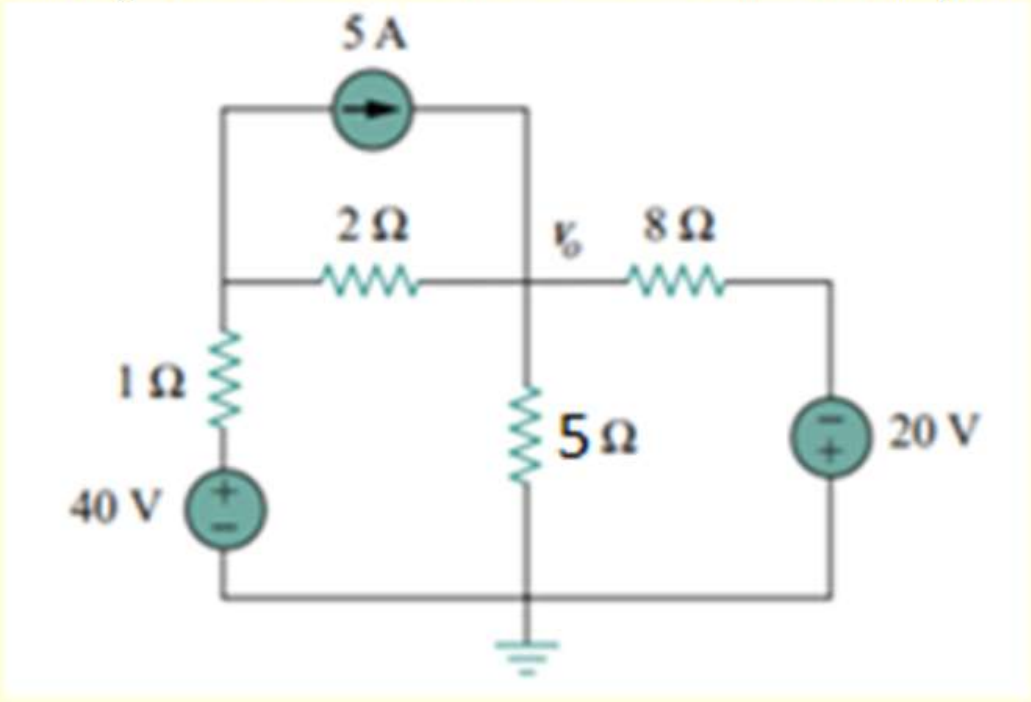Find V_O in the circuit shown below. Also calculate the power dissipated in the $5\ \Omega$ resistor.



Find equivalent resistance R_{ab} in the circuit.

