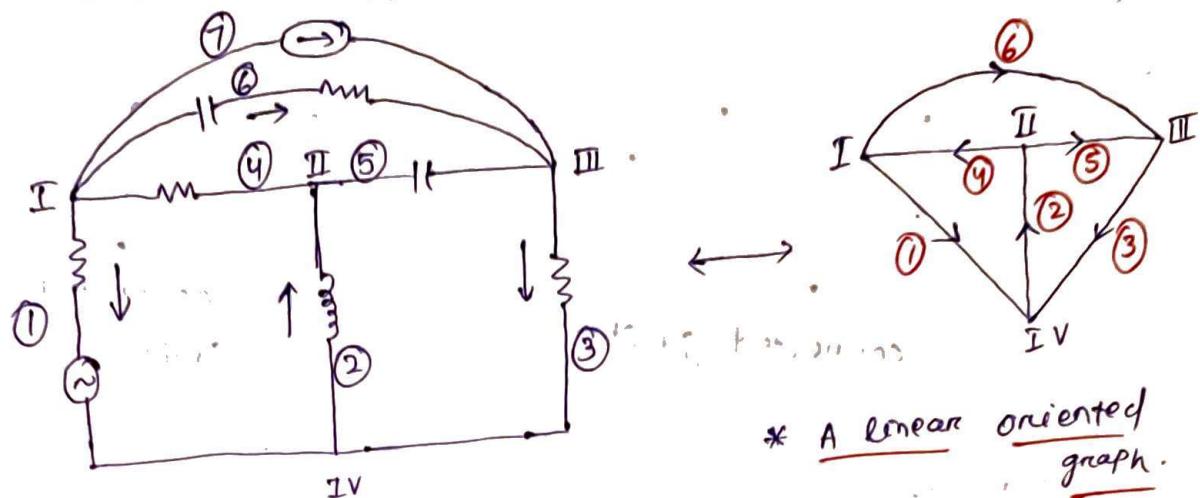


The Graph Theory.

14.11.10

while constructing a graph from a given n/w, all the passive elements, ideal voltage sources are replaced by short ckt's and all the ideal current sources are replaced by open ckt's



i.e. the graph branches \leq the n/w branches

- The no. of nodes or vertices = $n = 4$
 - The no. of branches or edges = $b = 6$
 - complete graph :- or the standard graph :-
Btw any pair of nodes, only one branch is connected for all the combinations.
- Q1. Det. the no. of edges of a complete graph with 'n' nodes

if

- (a) n^2 (b) $n-1$ (c) $n(n-1)$ (d) $\frac{n(n-1)}{2}$

$$b = {}^n C_2 = \frac{n(n-1)}{2}$$

gt is a way of selecting two nodes from a given set of n -nodes

→ For the present complete graph there are $\frac{4(4-1)}{2} = 6$ branches.

Connected Graph :-

In a connected graph all the nodes are connected by at least one branch, otherwise it is said to be un-connected.



connected graph



un-connected graph

(.) → free node

or isolated node.

Sub-graph :-

It is a graph with less no. of branches as compared with the original graph.

Tree of a graph :-

→ Tree is a connected sub graph which connects all the nodes without any closed loop.

→ Tree branches are called twigs.

→ The no. of twigs of any graph $= n-1$

→ The no. of possible trees of a complete graph with n nodes $= \underline{\underline{n^{n-2}}}$


→ For the present complete graph there are $4^{(4-2)} = 16$ possible trees.

Co-tree / the complemented tree :-

It is a tree formed with all the removed branches from the original graph in order to construct a tree.

→ Co-tree branches are called "links" or "chords".

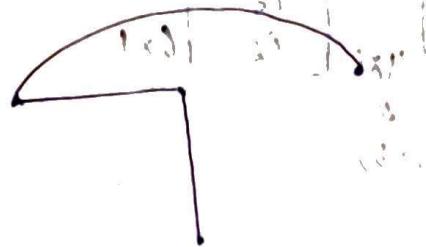→ The no. of links of any graph = $b - (n - 1)$
 $= b - n + 1$



∴ $T(2, 4, 6)$, $L(1, 3, 5)$, $T(1, 2, 3)$, $L(4, 5, 6)$
(tree) (links) (tree) (links)


→ The co-tree may consist of a loop in its representation.

→ Tree + Co-Tree = original graph.

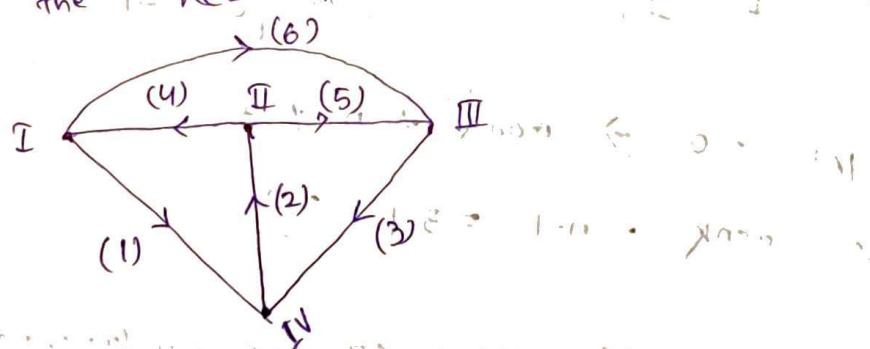1. The incidence matrix $\rightarrow (AI)$

Let the branch currents be i_1, i_2, \dots, i_6 .

By writing the KCL equations at every node



$$I \Rightarrow i_1 - i_4 + i_6 = 0$$

$$II \Rightarrow -i_2 + i_4 + i_5 = 0$$

$$III \Rightarrow i_3 - i_5 - i_6 = 0$$


$$IV \Rightarrow -i_1 + i_2 - i_3 = 0$$

$$\begin{array}{c}
 \text{I} \quad \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 0 & 0 & -1 & 0 & 1 \end{bmatrix} \\
 \text{II} \quad \begin{bmatrix} 0 & -1 & 0 & 1 & 1 & 0 \end{bmatrix} \\
 \text{III} \quad \begin{bmatrix} 0 & 0 & 1 & 0 & -1 & -1 \end{bmatrix} \\
 \text{IV} \quad \begin{bmatrix} -1 & 1 & -1 & 0 & 0 & 0 \end{bmatrix}
 \end{array}
 \begin{array}{l}
 4 \times 6 \\
 \downarrow \\
 A_I
 \end{array}
 \begin{array}{c}
 \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} \\
 6 \times 1
 \end{array}
 = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}
 \begin{array}{l}
 (n \times b) \\
 \text{rank } n
 \end{array}$$

Properties

- (i) For a given graph the incidence matrix is unique of order $(n \times b)$
- (ii) The rank of the incidence matrix = rank of the graph = $n-1$.
- (iii) The determinant of the incidence matrix of a closed loop is always equal to zero.

e.g.

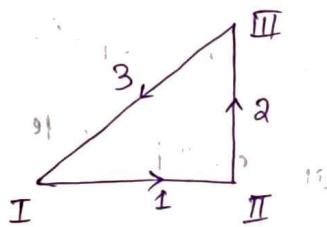

$$A = \begin{array}{c}
 \text{I} \quad \begin{bmatrix} 1 & 2 & 3 \\ 1 & 0 & -1 \end{bmatrix} \\
 \text{II} \quad \begin{bmatrix} -1 & 1 & 0 \end{bmatrix} \\
 \text{III} \quad \begin{bmatrix} 0 & -1 & 1 \end{bmatrix}
 \end{array}
 \begin{array}{l}
 3 \times 3
 \end{array}$$

$$|A| = 0 \rightarrow \text{rank } \neq n \neq 3$$

$$\text{So, rank } = n-1 = 3-1 = 2.$$


2. The Fundamental Loop matrix or the fundamental cut matrix or the Tie-set matrix. :-

Let the branch voltages v_1, v_2, \dots, v_b .

f-loops or f-CKts on Tie-sets :-

These are the minimum no. of loop or mesh eqns required to solve the corresponding w/w.

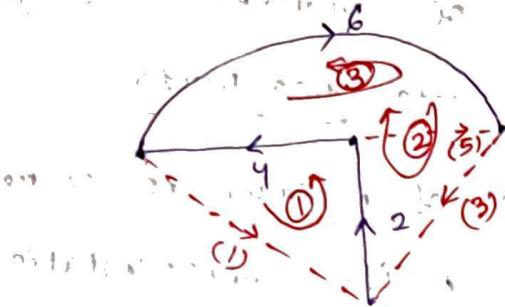- Step 1 To form loop equations first we have to find the links.
- Select a tree.
 - By adding one link at a time to the existing tree will result in one f-loop at a time.
 - Select the f-loop current direction as on-the link current direction.



$$f_{l_1} \Rightarrow v_1 + v_2 + v_4 = 0$$

$$f_{l_2} \Rightarrow v_3 + v_2 + v_4 + v_6 = 0$$

$$f_{l_3} \Rightarrow v_5 - v_6 - v_4 = 0$$

$$\begin{array}{l}
 f_{l_1} \left[\begin{array}{cccccc} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 0 & 1 & 0 & 0 \end{array} \right] \quad \left[\begin{array}{c} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \end{array} \right] \\
 f_{l_2} \left[\begin{array}{cccccc} 0 & 1 & 1 & 1 & 0 & 1 \\ 0 & 0 & 0 & -1 & 1 & -1 \end{array} \right] \quad 3 \times 6 \quad 3 \times 1 \\
 f_{l_3} \left[\begin{array}{cccccc} 0 & 0 & 0 & -1 & 1 & -1 \end{array} \right] \quad 3 \times 6 \quad 3 \times 1
 \end{array}$$

\Downarrow \Downarrow
 (B_f) $(b-n+1) \times b$

Properties :-

- The rank of the f-loop matrix equal to $b-n+1$.
- Since every link will result one f-loop at a time for any graph the no. of links $= b-n+1$.
- Every f-loop consists of only one link in its representation.

→(v) Since every tree will result one f-loop matrix at a time
for any graph, the no. of f-loop matrices are always equal
to the no. of trees

→(vi) For a complete graph there are n^{n-2} f-loop matrices.

3. Cut-set


The cut-set is a minimal set of branches of a graph,
removal of each divides the graph into two parts.

i.e. the cut-set always consists of minimum no. of removed
branches from the original graph in its representation

c (1, 2, 3)



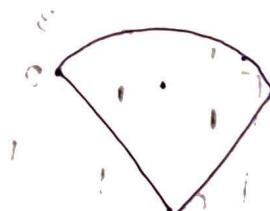The graph of the cut-set
i.e. the remaining branches




f-Cut sets

These are the minimum no. of loop modal eqn required
to solve the corresponding flow.


Step - 1

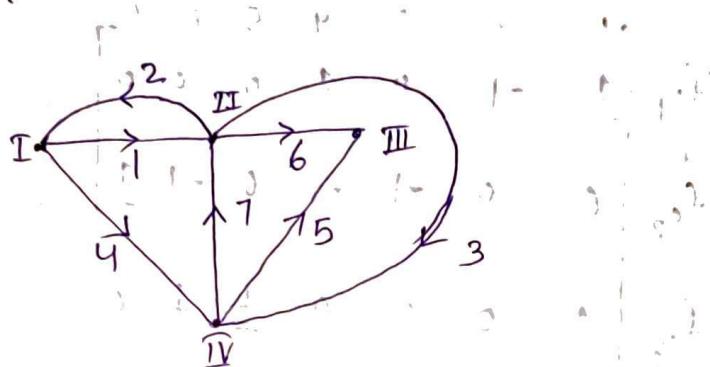- (i) Select a tree
- (ii) By removing one tree branch at a time will result one f-cut set at a time.
- (iii) select the f-cut set direction as in the tree branch direction.




Obs :- gt is not a complete graph.

Step 2

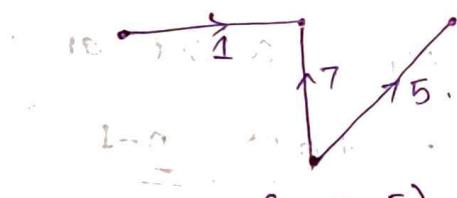

$$T(1, 7, 5)$$

$$fc_1 : C(1, 2, 4)$$

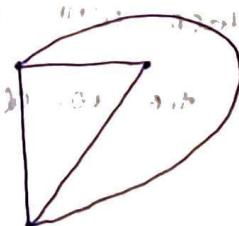


The graph after f-cut set i.e. the remaining branched.

$$fc_2 : C(7, 6, 4, 3)$$



$$f_{C_3} : C(5, 6)$$

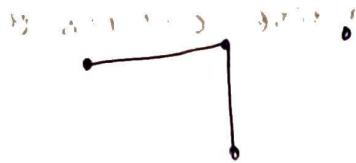

The f-cut set matrix (Q_C) :-

$$Q_C = \begin{bmatrix} f_{C_1} & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ f_{C_2} & 0 & 0 & -1 & -1 & 0 & -1 & 1 \\ f_{C_3} & 0 & 0 & 0 & 0 & 1 & 1 & 0 \end{bmatrix}$$

Properties :-

- (i) The rank of the Q_C matrix = $n-1$
- (ii) Since every tree branch will result one f-cutset at a time, for the graph no. of f-cutsets = twigs = $n-1$
- (iii) Every f-cutset consists of only one tree branch in its representation.
- (iv) Since every tree will result one f-cutset matrix at a time, for any graph the no. of Q_C matrices are always equal to the no. of trees
→ For a complete graph, there are n^{n-2} Q_C matrices.

Q1 A complete graph consists of 66 branches. Determine the no. of f-loops, f-cut sets and their respective matrices.

(A) $b = nC_2 = \frac{n(n-1)}{2} = 66$

$$\Rightarrow n = 12.$$

$$f\text{-loops} = b - n + 1 = 66 - 12 + 1 = 55.$$

$$f\text{-cut sets} = n-1 = 12-1 = 11$$

$f\text{-loop matrices} = f\text{-cut-set matrices} = \text{no. of trees}$

$$= \underline{\underline{n^{n-2}}} = \underline{\underline{12^{10}}}$$

Q2 A n/w graph consists of 17 branched and 10 nodes. Det. the no. of equations required to solve the corresponding


n/w.

(A) nodal eqn = f-cut sets = $n-1 = \underline{\underline{9}}$

mesh eqn = f-loops = $b - n + 1 = \underline{\underline{8}}$

so, the no. of eqns required = minimum of nodal, mesh eqns.

$$= \underline{\underline{8}}$$

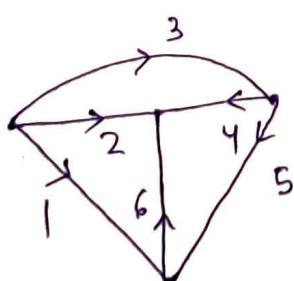

Q3

The valid cut sets

(a) 1, 2, 3, 4 X


(b) 3, 4, 5, 6 X

(c) 5, 6, 1, 2 X

Ans 1, 3, 4, 6



Q11

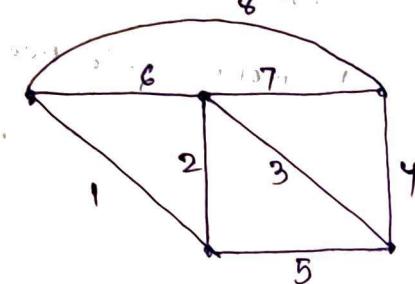

LIST I

A) 1, 2, 3, 4

B) 1, 4, 5, 6, 7

C) 4, 5, 6, 7

D) 2, 1, 3, 8


LIST II

1. Twigs


2. Links

3. f-cutsets

4. f-loop

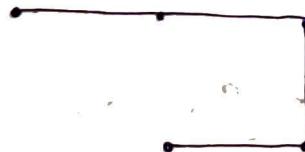

A Tree.

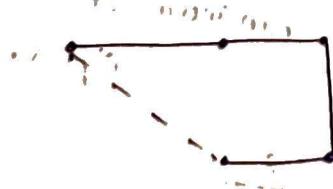

f-loop

(The graph after f-cutset)
e.g. the remaining
branches

The Avg. and r.m.s values of the Periodic Signals

Let $n(t)$ be the periodic signal of period T , then

$$x_{avg} = x_{d.c} = \frac{1}{T} \int_0^T n(t) dt = \frac{\text{Area over one period}}{\text{period}}$$

$$n_{rms} = \sqrt{\frac{1}{T} \int_0^T n^2(t) dt}$$

Sinusoidal signals - I

→ The Avg. and r.m.s values of some or co-sine function of any phase and frequency are.

$$\rightarrow 0 \text{ & } \frac{\text{mean value}}{\sqrt{2}}$$

Q11) $i(t) = 3 + 4\sqrt{2} \cos(100t + 10^\circ) + 5\sqrt{2} \cos(200t + 10^\circ) A$

$$I_{d.c} = I_{avg} = \frac{1}{T} \int_0^T i(t) dt = 3 + 0 + 0 = 3A$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{3^2 + \left(\frac{4\sqrt{2}}{\sqrt{2}}\right)^2 + \left(\frac{5\sqrt{2}}{\sqrt{2}}\right)^2} = \sqrt{3 + 16 + 25} = \sqrt{44} = 6.62A$$

Q11) $v(t) = 2 - 3\sqrt{2} \cos(10t + 45^\circ) + 3 \cos 10t V$

$$v_{avg} = v_{d.c} = \frac{1}{T} \int_0^T v(t) dt = 2 + 0 + 0 = 2V$$

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \sqrt{2^2 + \left(\frac{-3\sqrt{2}}{\sqrt{2}}\right)^2 + \left(\frac{3}{\sqrt{2}}\right)^2 + 0 + (\text{non-zero term}) + 0}$$

$$= \sqrt{8.5} V$$

Another method.

when same frequencies are present then do the sum of all the frequencies first


$$v(t) = 2 - 3\sqrt{2} \cos(10t + 45^\circ) + 3 \cos 10t \text{ v.}$$

$$\Rightarrow v(t) = 2 - 3\sqrt{2} \left(\cos 10t \cdot \frac{1}{\sqrt{2}} - \sin 10t \cdot \frac{1}{\sqrt{2}} \right) + 3 \cos 10t$$
$$= \underline{2 - 3 \sin 10t} \text{ v.}$$

$$v_{rms} = \sqrt{2^2 + \left(\frac{-3}{\sqrt{2}}\right)^2 + 0}$$
$$= \sqrt{8.5} \text{ v.}$$

Non-sinusoidal signals of periodic nature -

Q11

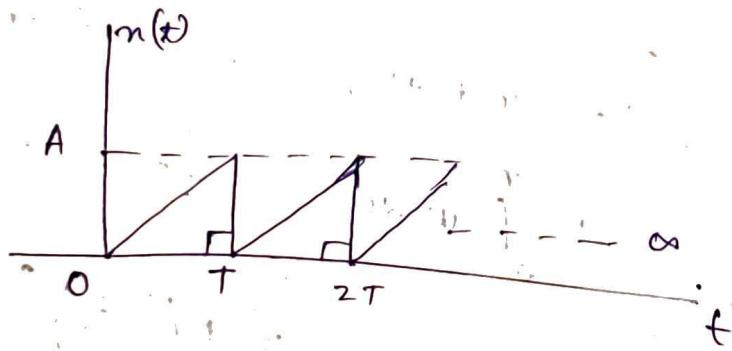


$$n(t) = \frac{A}{T} t \quad \text{for } 0 \leq t \leq T$$

$$x_{avg.} = \frac{\frac{1}{2} \cdot T \cdot A}{T} = \frac{A}{2}$$

$$v_{rms} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{A}{T} t\right)^2 dt} = \frac{A}{\sqrt{3}}$$

Q11

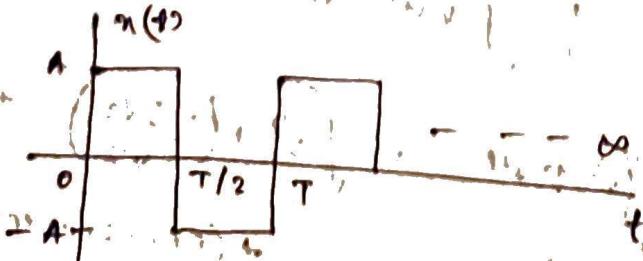


$$m_{avg} = x_{d.c.} = \frac{AT}{2} - \frac{AT}{2} \cdot \text{percentage} = 0$$

$$x_{rms} = \sqrt{\frac{1}{T} \left(\int_0^{T/2} A^2 dt + \int_{T/2}^T (-A)^2 dt \right)} = A$$

(9) ~~תְּמִימָה וְתַבְדֵּל בְּמִזְבֵּחַ וְבְמִזְבֵּחַ~~ (5)

α_1/α_0

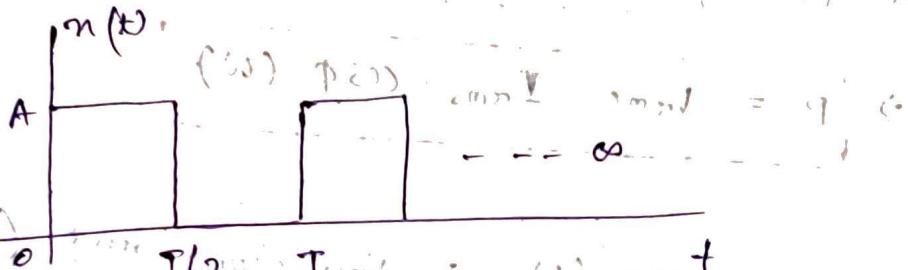

(Half rectified sq. wave)

$$n_{avg} = n_{d.c} \cdot \frac{\frac{AT}{2} + 0}{T} = A/2$$

$$m_{rms} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} A^2 dt + \int_{T/2}^T (0)^2 dt \right]} = \frac{A}{\sqrt{2}}$$

\rightarrow full rectified

For d.c = Avg. value = r.m.s value = max. value.

100% 100% 100% 100% 100% 100% 100% 100% 100% 100%

giant *shrub* *or* *tree*

Philip Morris Inc.

• Although not the standard name, "Ampfer" is also used.

as well as now (4)

The power calculation -1

case (i). Let $v(t) = V_m \cos(\omega t + \alpha) V$.
 $i(t) = I_m \cos(\omega t + \beta) A$.

(i) The true power / The Active Power (P)

$$\Rightarrow P = V_{rms} \cdot I_{rms} \cdot \cos \phi (W)$$

(ii) The reactive power $(Q) = V_{rms} \cdot I_{rms} \cdot \sin \phi (VAR)$

(iii) The complex power or The Apparent Power (S)

$$S = V_{rms} \cdot I_{rms} (VA)$$

$$S = \sqrt{P^2 + Q^2} (VA)$$

(*) Let $v(t) = 160 \cos(\omega t + 10^\circ) V$

$i(t) = 5 \cos(\omega t - 20^\circ) A$ calculate all the

powers.

$$\begin{aligned} V_{rms} &= \frac{160}{\sqrt{2}} V & Z &= \frac{V}{I} = \frac{160 \underbrace{[10^\circ - 90^\circ]}_{[-20^\circ - 90^\circ}}{5} \\ I_{rms} &= \frac{5}{\sqrt{2}} A & &= 32 \underbrace{[30^\circ]}_{[-20^\circ]} \end{aligned}$$

$\phi = 30^\circ \Rightarrow$ inductive.

Q1) $V = 4 \underbrace{[10^\circ]}_{[-20^\circ]} V$.

$I = 2 \underbrace{[20^\circ]}_{[-20^\circ]} A$, then calculate all the powers.

A) $V_{rms} = 4V$, $I_{rms} = 2A$

$$V = \frac{V}{I} = \frac{V}{I_{rms}} = 2 \angle 30^\circ$$

Note: when directly phasors are given then the magnitudes are taken as r.m.s values, since they are measured by using the r.m.s. meters.

case(ii)

$$\text{Let } Z = R + jX$$

$$i(t) = I_{rms} \cos(\omega t + \beta) A$$

$$I_{rms}^2 \cdot Z = I_{rms}^2 \cdot R \pm j I_{rms}^2 \cdot X$$

$$\begin{aligned} S &= P \pm jQ \\ |S| &= \sqrt{P^2 + Q^2} \\ \angle S &= \pm \tan^{-1} \left(\frac{Q}{P} \right) \end{aligned}$$

$$\begin{aligned} P &= I_{rms}^2 \cdot R(w) = P_{avg} \\ Q &= I_{rms}^2 \cdot X \quad (\underline{\text{VAR}}) \end{aligned}$$

Q11

$$i = 5\sqrt{2} \cos 2t A$$

$$Z = \left(3 + \frac{j}{3} \right) \Omega$$

$$I_{rms} = \frac{5\sqrt{2}}{\sqrt{2}} = 5 A$$

$$P = 5^2 \times 3 = 75 W$$

$$Q = 5^2 \times \frac{1}{3} = \frac{25}{3} \text{ VAR}$$

$$S = \sqrt{P^2 + Q^2} \quad \text{VA}$$

case (ii)

$$Y = \frac{1}{Z} = G + jB.$$

$$Z = R + jX$$

$$V(t) = V_m \cos(\omega t + \alpha) V$$

$$V_{rms}^2 \cdot Y = V_{rms}^2 \cdot G + j \cdot V_{rms}^2 \cdot B$$

$$S = P + Q$$

$$|S| = \sqrt{P^2 + Q^2}$$

$$\angle S = \pm \tan^{-1}(Q/P)$$

$$P = V_{rms}^2 \cdot G (\omega)^{\text{avg}} = P_{\text{avg}},$$

$$Q = V_{rms}^2 \cdot B \text{ VAR},$$

The n/w synthesis

Theory : Refer L.T

Realizations : $\left\{ \begin{array}{l} \text{FF - I} \xrightarrow{\text{Partial fraction expansion of } z(s)} \\ \text{FF - II} \rightarrow " " " " " " y(s) . \\ \text{C - I} \rightarrow \text{polynomial division by descending order} \\ \text{C - II} \rightarrow " " " " \text{ by ascending order} \end{array} \right.$

All The Driving point impedance function of a one port network is


$$n/w \text{ } \text{ } \text{ } \text{ } \text{ } \text{ } z(s) = \frac{2s}{s^2 + 3}$$

$$\text{A) } Z(s) = \frac{2s}{s^2 + 3} \quad Y = \frac{1}{s/2 + 3/2s} = \frac{1}{Y(s)}$$

$$y(s) = s \cdot \frac{1}{2} + \frac{1}{s+2}$$

$$Y(5) = SC + \frac{1}{SL}$$

(v) (v) (v)

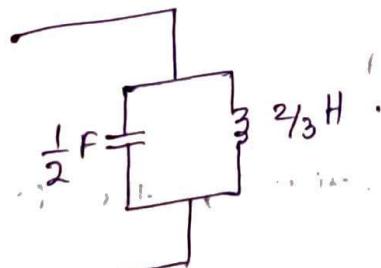

$$Y(s) = \frac{2s}{s^2 + 3} = \frac{1}{\frac{s^2}{2} + \frac{3}{2s}} = \frac{1}{Z(s)}$$


$$z(s) = s \cdot \frac{1}{2} + \frac{1}{s \cdot \frac{2}{3}}$$

$$Z(s) = S \cdot L + \frac{1}{S \cdot C}$$

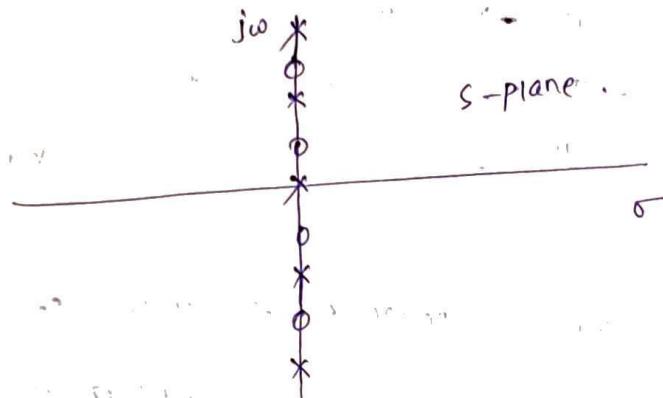
(i) For the LC impedance funcn the poles and zeros are alternate and lies only on the -ve real axis.

eg.

$$Z(s) = \frac{(s^2+1)(s^2+3)}{s(s^2+2)(s^2+4)}$$



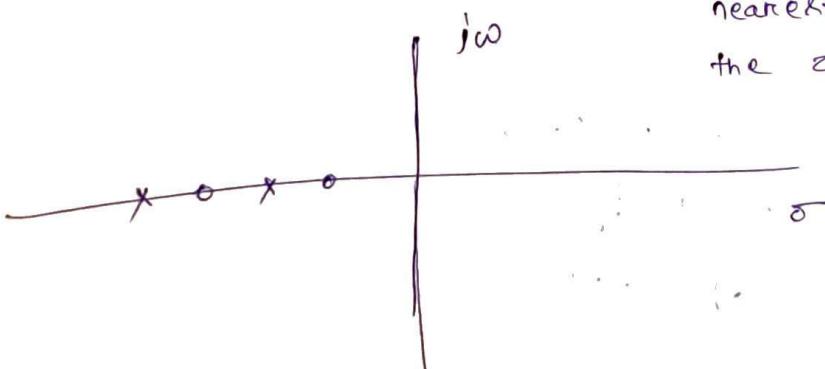
(ii) For the RL impedance funcn, the poles and zeros are alternate, lies only on the +ve real axis and nearest to the origin if the zero the (zero can be at the origin)



$$Z(s) = \frac{(s+1)(s+3)}{(s+2)(s+4)}$$

(iii) For the RC impedance function, the poles and zeros are alternate, lies only on the -ve real axis and nearest to the origin is the pole (the pole can be at the origin)

$$Z(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$$

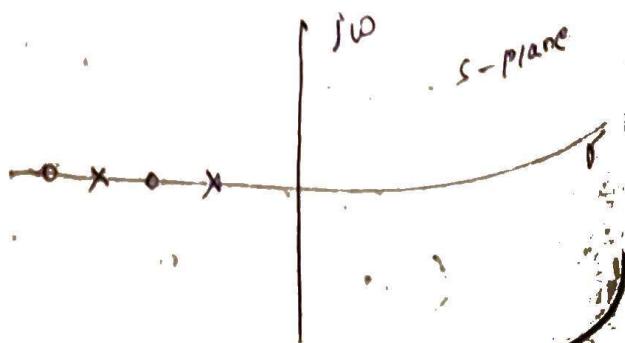

(iv) For the RLC impedance funcn, the poles and zeroes are complex conjugate phase and they are symmetric w.r.t the +ve real axis.

Note: In the above case instead of impedance function if admittance functions are given then they are converted into the impedances function first and later the above steps are performed.

- RL-imp. funcn \equiv RC-Admittance funcn and vice versa.
- Impedance = Impedance or Admittance.

Q1 The driving point imittance funcn of a one port n/w

ex. $f(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$ then the choice is.

- (i) R-L impedance funcn.
- (ii) R-C admittance funcn.
- (iii) L-C imp. funcn
- (iv) R-L admittance funcn.


Soln → If $f(s) = Z(s)$, then it is an R-C funcn.

→ If $f(s) = Y(s)$, then it is an R-L funcn

Conclusion - i.e. if it is on RC funcn and on admittance domain, it is an R-L funcn.



The Locus Diagrams.. -

16.11.10

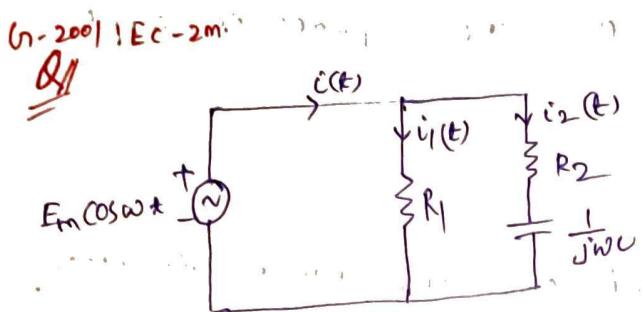


N.W. ip on S.S.

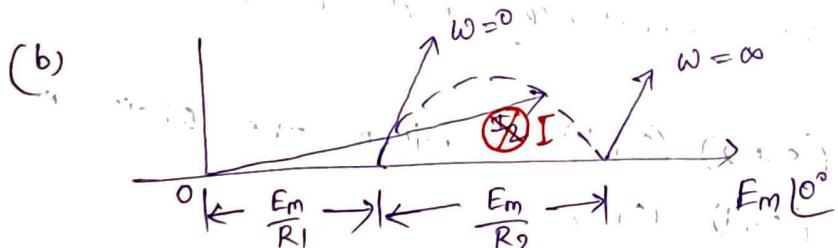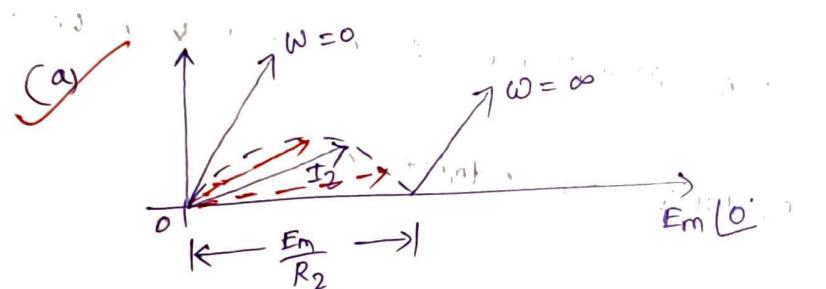In the ckt shown, the freq. of the source ω varied from 0 to ∞ . Then the locus of the current phasor I_2 is



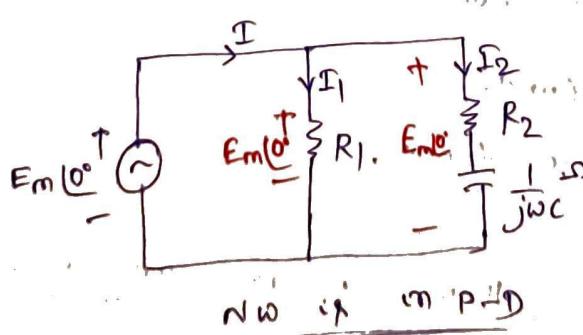Transform the above N.W. in to the phasor domain.



$$\text{By KCL in P-D} \Rightarrow I = I_1 + I_2$$

$$\text{In p-d, } I_1 = \frac{E_m [0]}{R_1}$$

$$I_2 = \frac{E_m [0]}{R_2 + \frac{1}{j\omega C}}$$

$$I_2 = \frac{E_m [0^\circ]}{R_2 + \frac{1}{j\omega C}} = \frac{E_m [0^\circ]}{R_2 - \frac{j}{\omega C}} = \frac{E_m \left[\tan^{-1} \frac{1}{\omega C R_2} \right]}{\sqrt{R_2^2 + \left(\frac{1}{\omega C} \right)^2}}$$

$$\omega = 0 \Rightarrow I_2 = 0$$



$$\omega = \infty \Rightarrow I_2 = \frac{E_m [0^\circ]}{R_2}$$

\Rightarrow $0 < \omega < \infty$, the current phasor I_2 always lead the voltage $E_m [0^\circ]$

~~Q1~~ In the above case instead of ' ω ' if ' R_2 ' is varied from 0 to ∞ then the locus of the current phasor I_2

(A) $R_2 = 0 \Rightarrow I_2 = \frac{E_m [0^\circ]}{0 + \frac{1}{j\omega C}} = E_m \omega C [90^\circ]$

$$R_2 = \infty \Rightarrow I_2 = 0 A$$

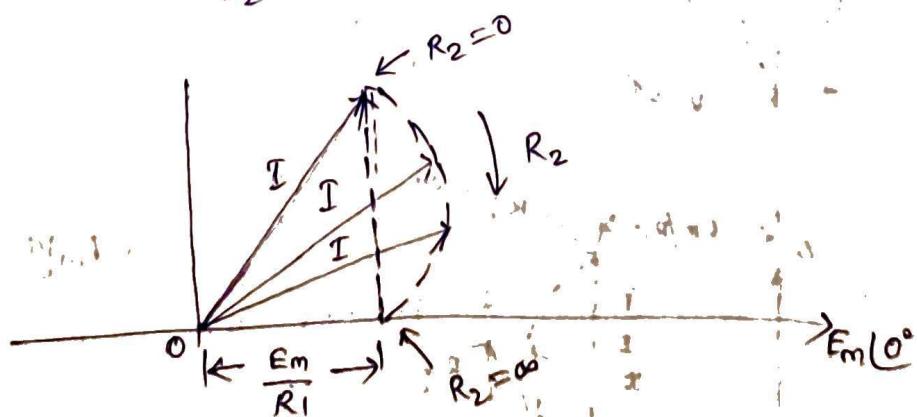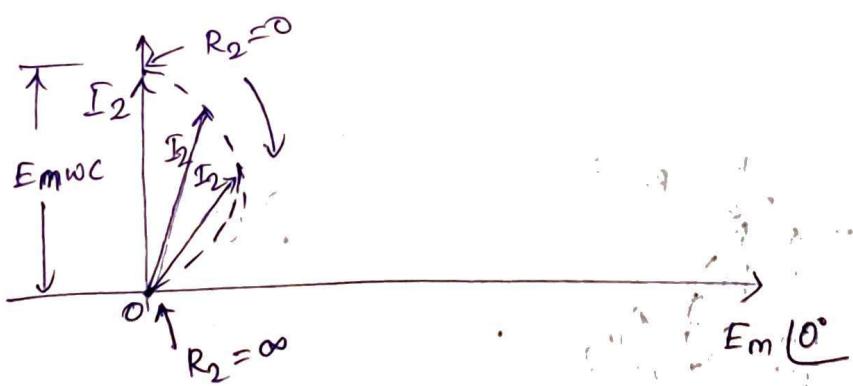

Q// In the above case, instead of capacitor if conductor is present



then

$$I = I_1 + I_2$$



$$I_1 = \frac{E_m |0^\circ|}{R_1}$$

$$I_2 = \frac{E_m |0^\circ|}{R + j\omega L} = \frac{E_m \left[-\tan^{-1} \frac{\omega L}{R_2} \right]}{\sqrt{R_2^2 + (\omega L)^2}}$$

'w' varied

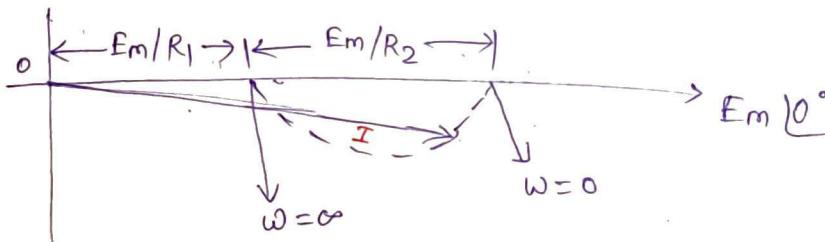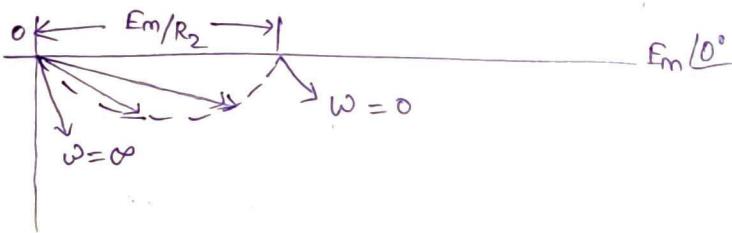

R_2 varied

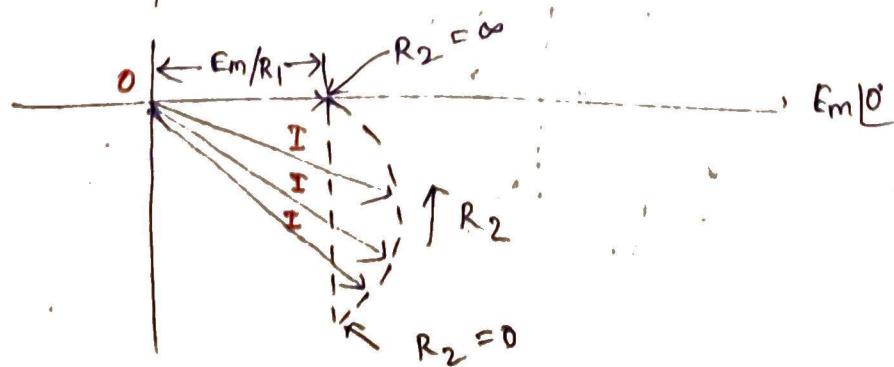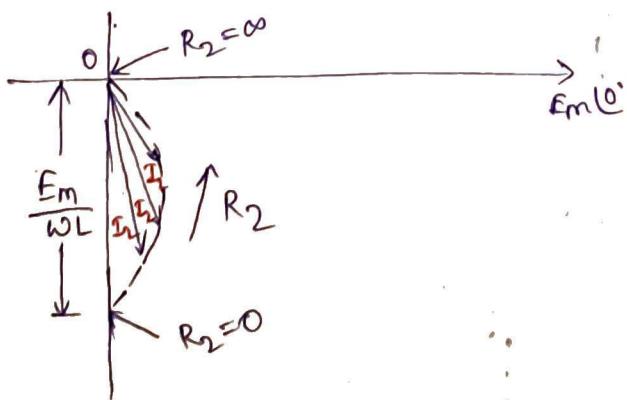

FILTERS →

$$Z_R = R \omega^2$$

$$Z_L = j\omega L \omega$$

$$Z_C = \frac{1}{j\omega C} \omega$$


$$\omega = 0 \Rightarrow Z_L = 0 \Rightarrow L \rightarrow S \cdot C$$

$$Z_C = \infty \Rightarrow C \rightarrow 0 \cdot C$$

$$\omega = \infty \Rightarrow Z_L = \infty \Rightarrow L \rightarrow 0 \cdot C$$

$$Z_C = 0 \Rightarrow C \rightarrow S \cdot C$$

Q1) The CKT shown in fig. represents

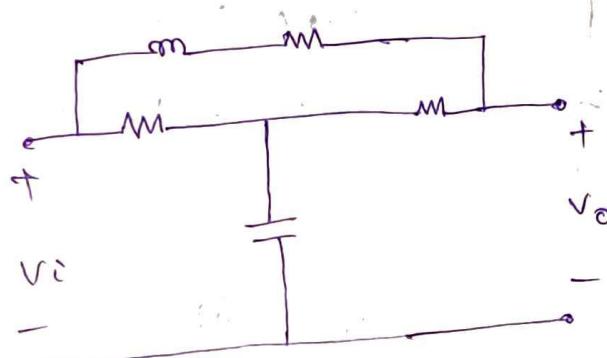

(a) LPF

(b) HPF


(c) BPF

(d) BSF.

$$\omega = 0 \Rightarrow V_0 = V_i$$

$$\omega = \infty \Rightarrow V_0 = 0$$

Q1

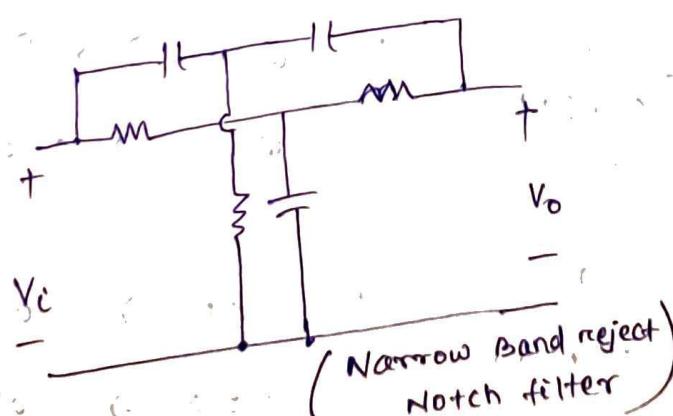

(a) LPF

(b) HPF


(c) BPF

(d) BSF

$$\omega = 0 \Rightarrow V_0 = V_i$$

$$\omega = \infty \Rightarrow V_0 = V_i$$

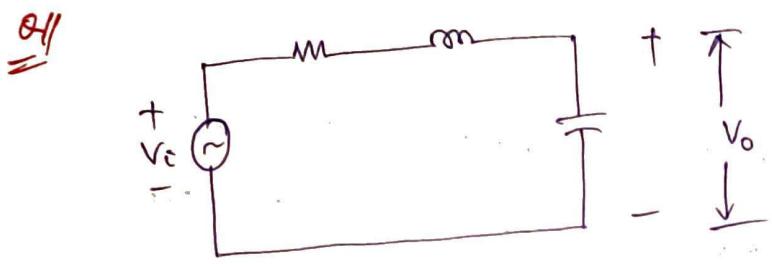
The series and parallel RLC CKT at resonance are called as BPF



$$\omega = 0 \Rightarrow V_0 = V_i$$

LPF


$$\omega = \infty \Rightarrow V_0 = 0$$

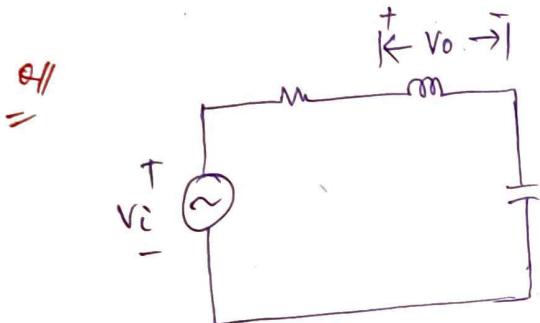

$$\omega = 0 \Rightarrow V_0 = 0$$

HPF
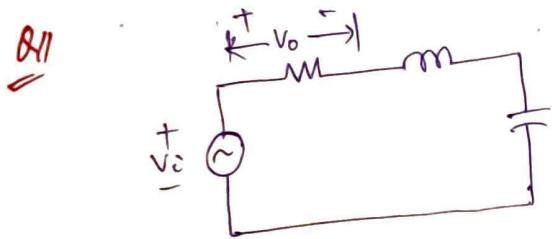
$$\omega = \infty \Rightarrow V_0 = V_i$$



$$V_0 = R \cdot i(t)$$

$$\omega = 0 \Rightarrow V_0 = 0$$

BPF

$$\omega = \infty \Rightarrow V_0 = 0$$

2nd order Filter →

LPF : $H(s) = \frac{1}{s^2 + s + 1}$; $\omega = 0 \Rightarrow s = 0 \Rightarrow H(s) = 1 \checkmark$

$$\omega = \infty \Rightarrow s = \infty \Rightarrow H(s) = 0 \times$$

HPF : $H(s) = \frac{s^2}{s^2 + s + 1}$; $\omega = 0 \Rightarrow s = 0 \Rightarrow H(s) = 0 \checkmark$

$$\omega = \infty \Rightarrow s = \infty \Rightarrow H(s) = 1 \checkmark$$

BPF : $H(s) = \frac{s}{s^2 + s + 1}$; $\omega = 0 \Rightarrow s = 0 \Rightarrow H(s) = 0 \times$

$$\omega = \infty \Rightarrow s = \infty \Rightarrow H(s) = 0 \times$$

BSF : $H(s) = \frac{s^2 + 1}{s^2 + s + 1}$; $\omega = 0 \Rightarrow s = 0 \Rightarrow H(s) = 1 \checkmark$

$$\omega = \infty \Rightarrow s = \infty \Rightarrow H(s) = 1 \checkmark$$

$|H(j\omega)|$ a function of ω

APP : $H(s) = \frac{1-s}{1+s}$ $\therefore \omega=0 \Rightarrow s=0 \Rightarrow H(s)=1$
 $\omega=\infty \Rightarrow s=\infty \Rightarrow H(s)=-1$
 $= 1 \text{ } [180^\circ]$

$\Re \{H(j\omega)\}$ is independent of ' ω '

All The main phase shift added the All pass filter to the CIP signal.


(A)

$$H(s) = \frac{1-s}{1+s}$$

$$H(j\omega) = \frac{1-j\omega}{1+j\omega}$$

$$|H(j\omega)| = 1$$

$$\underline{|H(j\omega)|} = \phi = -\tan^{-1}\omega - \tan^{-1}\omega = -2\tan^{-1}\omega$$

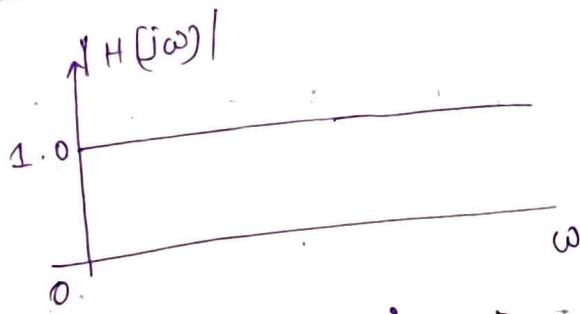


$$\omega=0 \Rightarrow \phi=0^\circ = \Phi_{min}$$

$$\omega=\infty \Rightarrow \phi=-2\tan^{-1}\infty = -2 \times 90^\circ = -180^\circ$$

$$= +180^\circ = \Phi_{max}$$

All The main phase shift added by the first order LPF to the CIP signal.

(A)

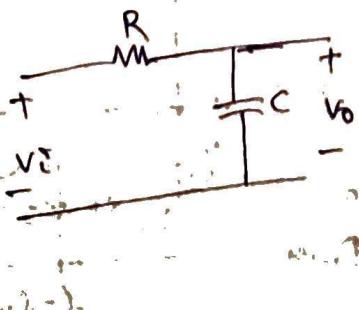

$$\omega=0 \rightarrow V_o \approx V_i$$

$$\omega=\infty \rightarrow V_o=0$$


$$\rightarrow V_o(s) = \left(\frac{V_i(s)}{R + \frac{1}{sC}} \right) \cdot \frac{1}{sC}$$

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = H(s) = \frac{1}{1 + sCR}$$

$$|H(j\omega)| = \frac{1}{1 + j\omega CR} = \frac{1}{1 + j\frac{f}{f_L}} \quad \text{where } f_L = \frac{1}{2\pi RC},$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}}$$

$$\underline{|H(j\omega)|} = \phi = -\tan^{-1}\left(\frac{f}{f_L}\right)$$

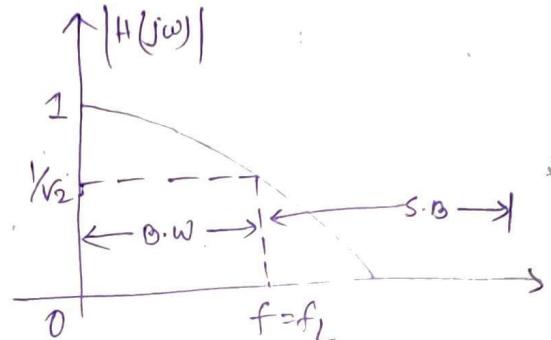


$$f=0 \Rightarrow \phi = 0^\circ = \phi_{\min}$$

$$f=\infty \Rightarrow \phi = -45^\circ = \phi_{\max}$$

\rightarrow gt can delay the signal max. -45° .

QII HPF

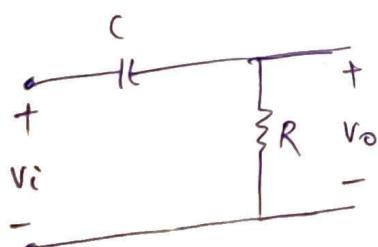

$$\rightarrow V_o(s) = \left(\frac{V_i(s)}{R + \frac{1}{sC}} \right) R$$

$$\Rightarrow \frac{V_o(s)}{V_i(s)} = H(s) = \frac{sCR}{1 + sCR} = \frac{1}{1 - \frac{j}{\omega CR}} = \frac{1}{1 - j \frac{f_H}{f}}$$

$$\omega_0 = 0 \Rightarrow V_o = 0$$

$$\omega = \infty \rightarrow V_o = V_i \rightarrow H(j\omega) = \frac{1}{1 - j \frac{f_H}{f}} = \frac{1}{1 - j \frac{f_H}{f}}$$


where $f_H = \frac{1}{2\pi RC}$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{f_H}{f}\right)^2}}$$

$$\underline{|H(j\omega)|} = \phi = +\tan^{-1}\left(\frac{f_H}{f}\right)$$

$$f = \infty \Rightarrow \phi = 0^\circ = \phi_{\min}$$

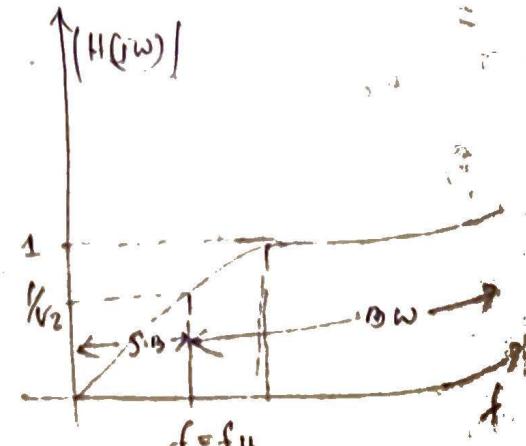
$$f = f_H \rightarrow \phi = 45^\circ = \phi_{\max}$$



Coupled Ckt \Rightarrow (M)

→ These are the ckt's in the presence of mutual inductance (M). This is due to the mutual flux betn the coils. The mutual flux ~~is~~ ^{and} ~~need~~ ^{can} ~~are~~ may oppose the self fluxes based on the dot convention, if the current enters the dots or leaves the dots simultaneously then the mutual flux will aid to the self fluxes otherwise it will oppose.

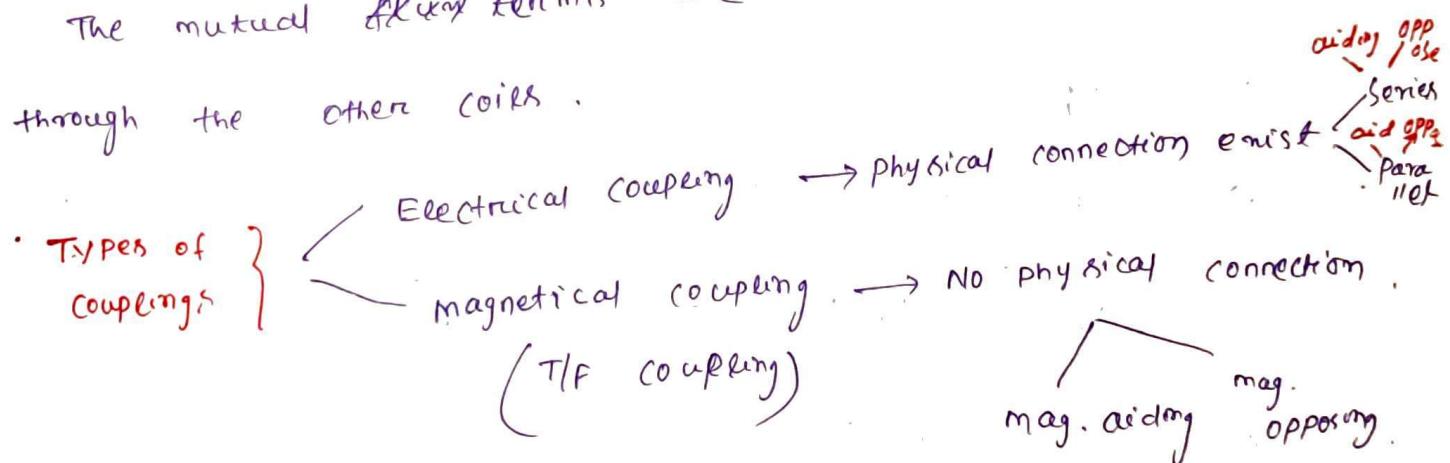→ The mutual flux terms are because of the currents flowing through the other coils.



Magnetic aiding →

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \text{--- (1)}$$

$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \quad \text{--- (2)}$$


$$v_1 = (L_1 - M) \frac{di_1}{dt} + M \frac{d}{dt} (i_1 + i_2) \quad \text{--- (3)}$$

$$v_2 = (L_2 - M) \frac{di_2}{dt} + M \frac{d}{dt} (i_1 + i_2) \quad \text{--- (4)}$$

$$(1) = (3)$$

$$(2) = (4)$$

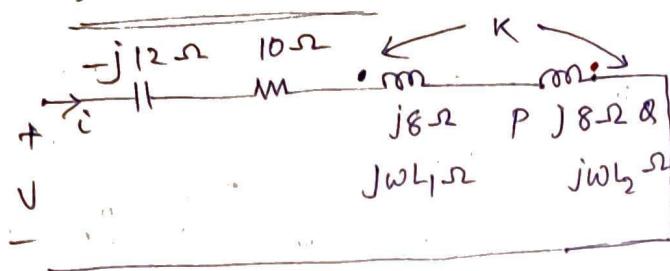Q11 For the series resonance det. the value of 'K'.



N.W.C. in S.S.

$$X_C = X_L$$

(A) $X_C = 12$ (given.)

$X_{L_{eq}} = 12$ must be series resonance.

So, the dot in the 2nd coil is at 'Q'.

$$\Rightarrow L_{eq} = L_1 + L_2 - 2M$$


$$\Rightarrow L_{eq} = L_1 + L_2 - 2K\sqrt{L_1 L_2}$$

$$\Rightarrow \omega L_{eq} = \omega L_1 + \omega L_2 - 2K\sqrt{\omega L_1 \omega L_2}$$

$$\Rightarrow 12 = 8 + 8 - 2K\sqrt{8 \cdot 8}$$

$$\Rightarrow 12 = 16 - 2K \cdot 8 \Rightarrow K = \frac{1}{4} = 0.25$$

Q11

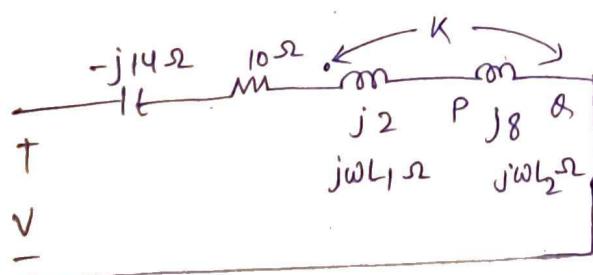

$$X_C = 14 \text{ (given)}$$

$\Rightarrow X_{L_{eq}} = 14$ must form series resonance

So, the dot in the 2nd coil is at 'P'.

$$\Rightarrow L_{eq} = L_1 + L_2 + 2M$$

$$\Rightarrow L_{eq} = L_1 + L_2 + 2K\sqrt{L_1 L_2}$$


$$\Rightarrow \omega_{\text{eq}} = \omega L_1 + \omega L_2 + 2K\sqrt{\omega L_1 \cdot \omega L_2}$$

$$\Rightarrow 14 = 2 + 8 + 2K\sqrt{2 \cdot 8}$$

$$\Rightarrow K = \frac{1}{2} = 0.5$$


Q11

Dek. Lab.

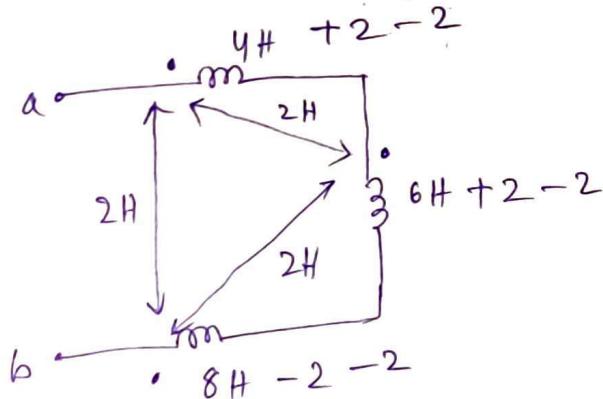

$$L_{\text{ab}} = 4 + 6 + 8 + 2 - 2 - 2 - 2 = 16 \text{ H}$$

Q12

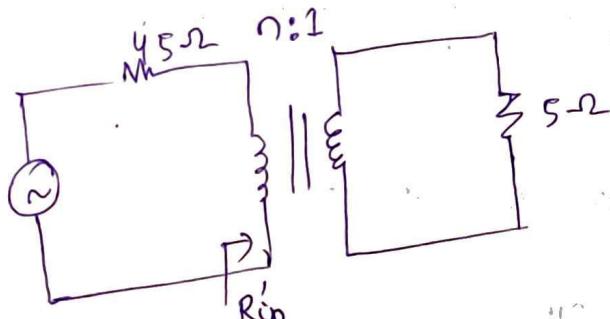


for the max. power transfer to the 5 ohm resistor,

the value of 'n' is

$$Z_m = \left(\frac{n_1}{n_2}\right)^2 \cdot Z_L$$

$$\Rightarrow R_m = n^2 \cdot 5 \Omega$$

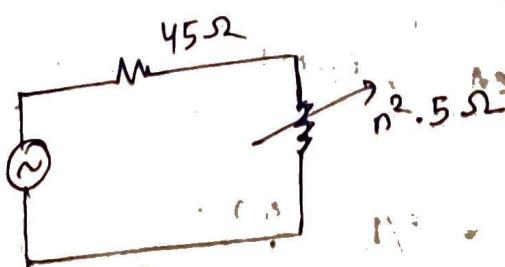


For MPT, $R_L = R_S$

$$\Rightarrow n^2 \cdot 5 = 45 \Rightarrow n = \underline{\underline{3}}$$

Q1

Det. I_1 & I_2

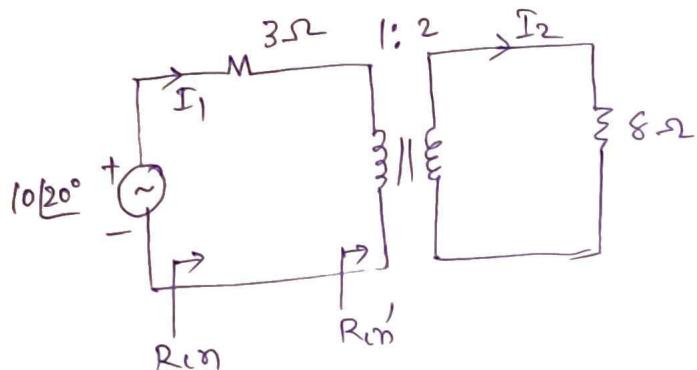

$$R_{in}' = \frac{8}{2^2} = 2\Omega$$


$$R_{in} = 3 + R_{in}' = 5\Omega$$

$$I_1 = \frac{10/20^\circ}{5} = 2/20^\circ A$$

$$\frac{I_1}{I_2} = n = 2 \Rightarrow I_2 = \frac{I_1}{2} = 1/20^\circ A$$

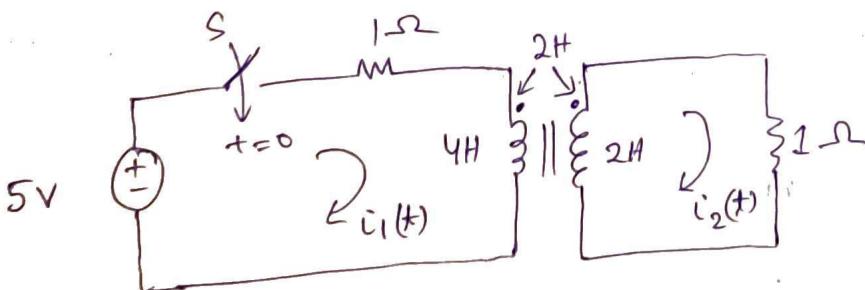Q1

Det. $i_1(t)$ and $i_2(t)$ for $t \geq 0$.



(1)

Initial condn.

$$i_1(0^-) = 0A = i_1(0^+)$$

$$i_2(0^-) = 0A = i_2(0^+)$$

Final condn.

$$i_1(\infty) = 5/1 = 5A$$

$$i_2(\infty) = 0A$$

$$5 = 1 \cdot i_1 + 4 \frac{di_1}{dt} - i_2 \frac{di_2}{dt}$$

$$\Rightarrow \frac{5}{s} = 1 \cdot I_1(s) + 4 \left[s I_1(s) - i_1(0^+) \right] - 2 \left[s I_2(s) - i_2(0^+) \right]$$

$$\textcircled{2} \quad 0 \neq 1/42 \quad \text{#}$$

$$0 = 1 \cdot i_2 + 2 \frac{di_2}{dt} - 2 \frac{di_1}{dt}$$

$$\Rightarrow 0 = 1 \cdot I_2(s) + 2 \left[s I_2(s) - i_2(0^+) \right] - 2 \left[s I_1(s) - i_1(0^+) \right]$$


$$I_1(s) = \checkmark$$

$$I_2(s) = \checkmark$$


$$\Rightarrow i_1(t) = \checkmark$$

$$\Rightarrow i_2(t) = \checkmark$$

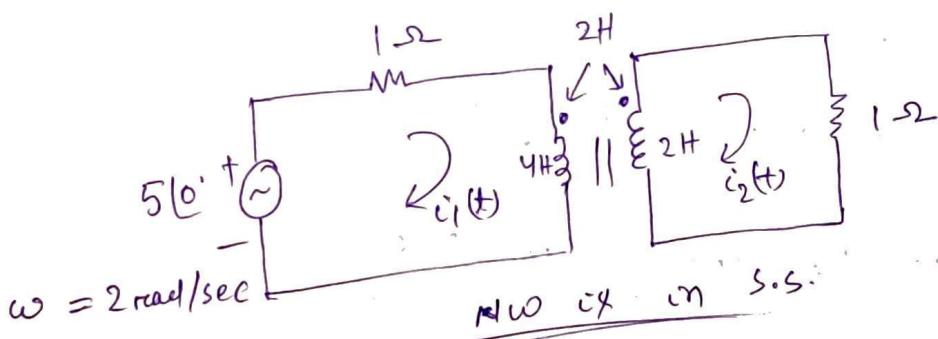BII Det. the S.S. current $i_1(t)$ & $i_2(t)$



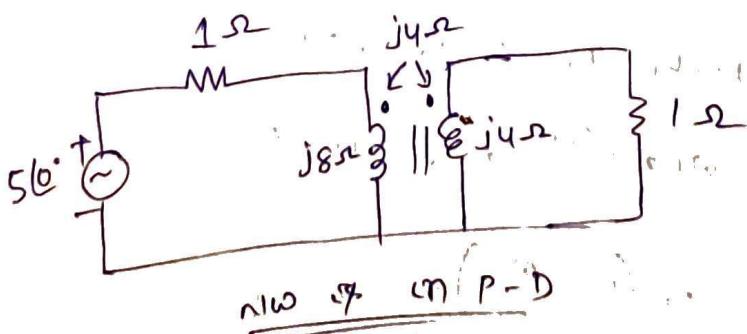(A) Transform the above N/W onto the phasor domain.



$$V = Z \cdot I$$

By KVL in P-D \Rightarrow

$$5 \angle 0^\circ = 1 \cdot I_1 + j8 \cdot I_1 - j4 \cdot I_2$$


$$0 = 1 \cdot I_2 + j4 \cdot I_2 - j4 \cdot I_1$$

$$I_1 = \frac{\Delta_1}{\Delta}, \quad I_2 = \frac{\Delta_2}{\Delta}$$

$$\rightarrow i_1(t) = R \cdot P [I_1 \cdot e^{j2t}] A$$

$$i_2(t) = R \cdot P [I_2 \cdot e^{j2t}] A$$

Q11

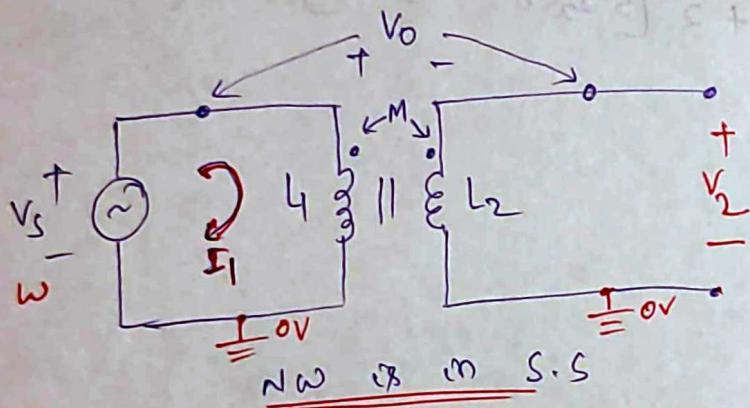

Express V_0 in terms of V_s .

(A)

By KVL in P-D \Rightarrow

$$V_s - V_0 - V_2 = 0$$

$$\Rightarrow V_0 = V_s - V_2 = V_s \left(1 - \frac{V_2}{V_s}\right)$$

$I_2 = 0A$, AS the secondary is open.


$$V_s = Z \cdot I$$

By KVL in P-D \Rightarrow

$$V_s = j\omega L_1 \cdot I_1 + j\omega M \cdot (0)$$

$$V_2 = j\omega L_2 \cdot (0) + j\omega m \cdot (I_1)$$

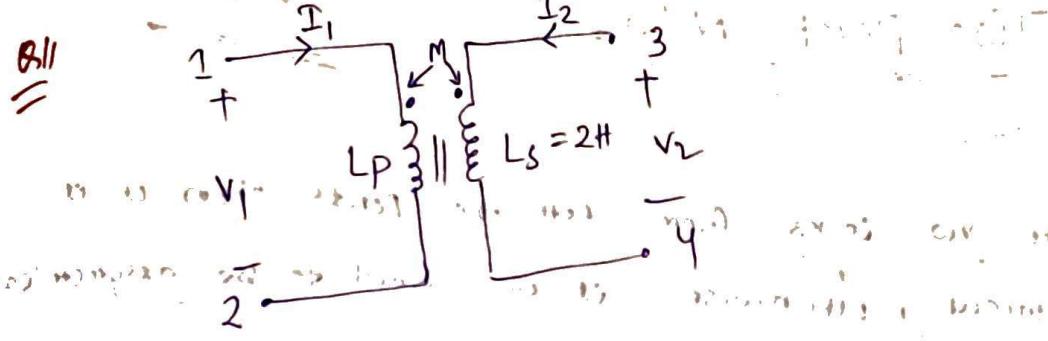
$$\Rightarrow V_0 = V_s \left(1 - \frac{m}{L_1}\right)$$



with 3 & 4 open.

$$L_{12} = 4H \quad \text{with } 3 \& 4 \text{ short.} \quad \text{Det. } K$$
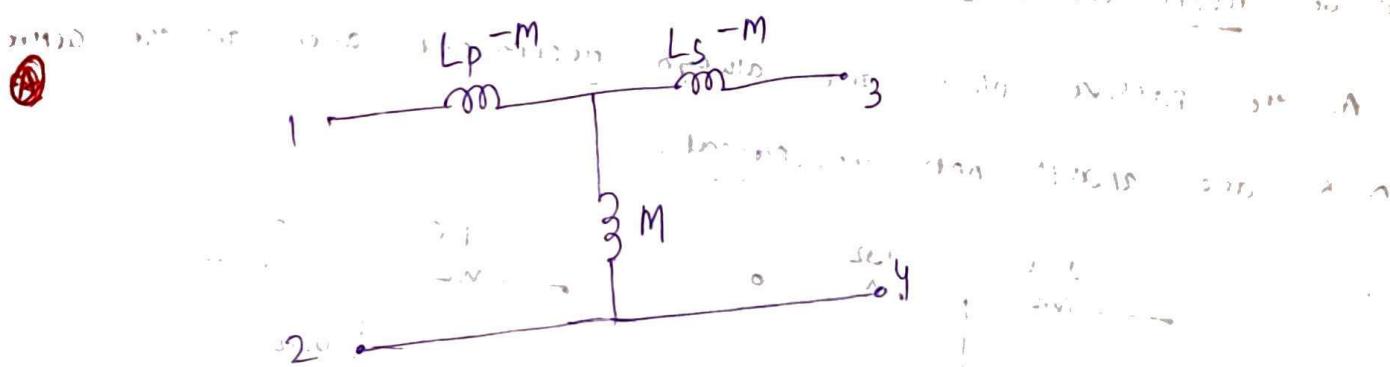
$$L_{12} = 3H \quad \text{with } 3 \& 4 \text{ open.}$$



$$L_{12} = 4 = L_p - M + M \parallel (L_s - M)$$

$$\begin{aligned} L_{12} = 3 &= L_p - M + M \parallel (L_s - M) \\ &= L_p - M + \frac{M \cdot (L_s - M)}{L_s} = L_p - M + M - \frac{M^2}{L_s} \end{aligned}$$

$$\Rightarrow 3 = 4 - \frac{M^2}{2} \Rightarrow M = \sqrt{2}$$

$$K = \frac{2M}{\sqrt{4pLs}} \approx \frac{\sqrt{2}}{\sqrt{4 \cdot 2}} = \frac{1}{2} = 0.5$$

$$\left(\begin{array}{c} \sigma' \\ \sigma'' \end{array} \right) \left(\begin{array}{c} \sigma' + \sigma'' \\ \sigma' - \sigma'' \end{array} \right) = \left(\begin{array}{c} 1 \\ 0 \end{array} \right) \left(\begin{array}{c} 0 \\ 1 \end{array} \right)$$

Two Port N/Ws.

18.11.10

Symmetrical N/W :-


When the N/W looks from both the ports then it is said to be symmetrical, otherwise it is said to be asymmetrical.

Reciprocal N/W :-


When the N/W obeys the reciprocity then it is said to be reciprocal, otherwise it is said to be non-reciprocal.

→ All the passive N/Ws are always reciprocal and all the active N/Ws are always not reciprocal.

e.g.

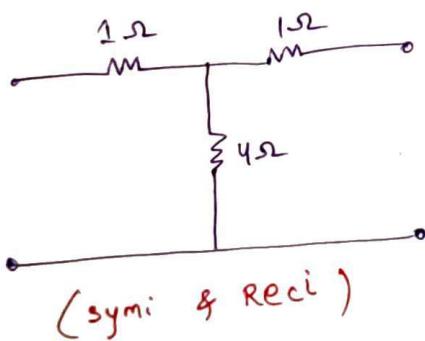

(sym & Reci)

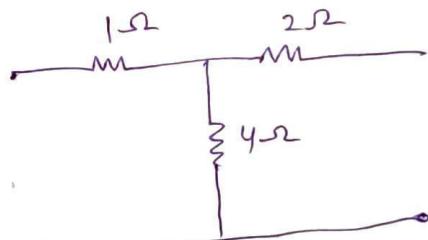

(Asym & Reci)

$$\rightarrow V_1 \quad V_2$$

$$I_1 \quad I_2$$

From the four variables, we can select two variables as independent variable in $Y_{C_2} = 6$ different ways and hence 6 sides of parameters for a given two port N/W.

$$\Rightarrow \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

Hence $-I_2$ is the leaving current from port '2' i.e. the current delivered to the load.

$$\Rightarrow \begin{pmatrix} V_{be} \\ i_c \end{pmatrix} = h \begin{pmatrix} i_b \\ -V_{ce} \end{pmatrix} \rightarrow \begin{matrix} \text{controlled} \\ \text{variables} \end{matrix}$$

$$\begin{pmatrix} v_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ v_2 \end{pmatrix}$$

Q1 The γ -parameters of a two port n/w

$$Y = \begin{pmatrix} 0 & -\frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} \end{pmatrix} \rightarrow \text{then the n/w is}$$

Q2 $\gamma_{11} \neq \gamma_{22} \Rightarrow$ Asym
 $\gamma_{12} \neq \gamma_{21} \Rightarrow$ Non reciprocal & Active, that too dependent sources with resistances.

$$T = \begin{pmatrix} 2 & 3 \\ 1 & 2 \end{pmatrix}$$

Q3 $A = D \Rightarrow$ Sym
 $AD - BC = 1 \Rightarrow$ reciprocal and passive, that too only resistances.

Q4 In a two port reciprocal n/w, the O/P open circled voltage divided by the input current eq equal to:

$$(a) h_{12} \quad (b) z_{12} \quad (c) \frac{1}{Y_{21}} \quad (d) B.$$

$$\rightarrow z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad (\text{reciprocal}) \quad (z_{12} = z_{21})$$


$$\stackrel{On}{\Rightarrow} y = z^{-1}$$

$$\begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix}^{-1} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix}^{-1}$$

$$\rightarrow y_{21} = \frac{-z_{21}}{z_{11}z_{22} - z_{21}z_{12}}$$

Q11

Det. h_{12}

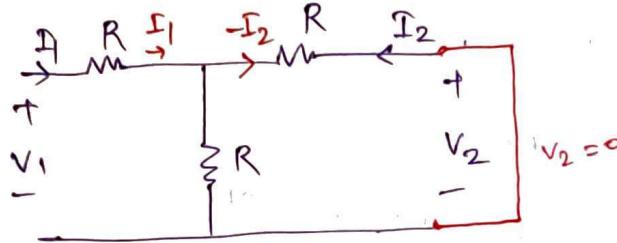

(A)

Since passive \Rightarrow Reciprocal $\Rightarrow h_{12} = -h_{21}$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = h_{fe}$$


$$-I_2 = \left. \frac{I_1 \cdot R}{R+R} \right|_{V_2=0}$$

$$\Rightarrow h_{21} = -1/2.$$

$$h_{12} = \frac{1}{2}$$

Q12

Det. Z_{in}

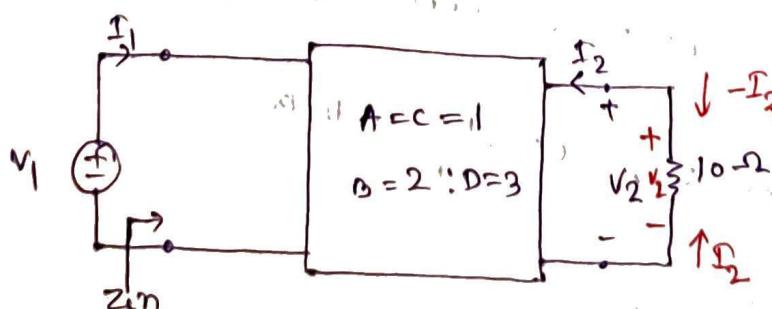

\Rightarrow

$$\frac{AD - BC}{1} = 1 \Rightarrow \text{Reci} \Rightarrow \text{only resistance.}$$

$$Z_{in} = R_{in} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2}$$

$$\Rightarrow (A + CV_2) I_2 + V_2 \cdot AV_2 = V_2 \cdot CV_2 + BI_2 \\ \Rightarrow V_2 = \frac{BI_2}{A + CV_2 + AV_2}$$


$V = R \cdot I$ | Ohm's Law

$$\Rightarrow V_2 = 10(-I_2)$$

$$Z_{in} = \frac{-10I_2 - 2I_2}{-10I_2 - 3I_2} = \frac{-12I_2}{-13I_2} = \frac{12}{13}$$

Q1

Det. $\cdot V_1$

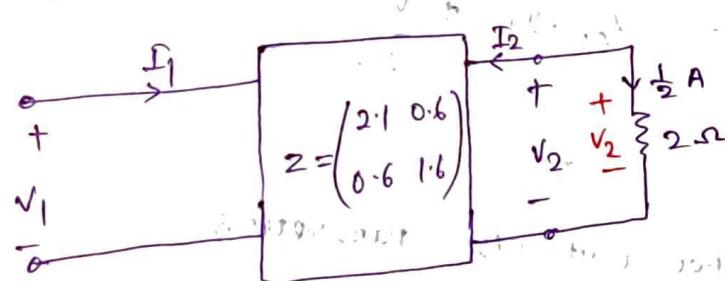

$$V_1 = 2.1 I_1 + 0.6 I_2$$

$$V_2 = 0.6 I_1 + 1.6 I_2$$

$$V_2 = 2 - \frac{1}{2} = 1 V$$

$$\text{By KCL} \Rightarrow I_2 - \frac{1}{2} = 0 \Rightarrow I_2 = 0.5 A.$$

$$\Rightarrow V_1 = 6 V$$

$$I = 0.6 \times I_1 + 1.6 \times -0.5$$

$$\frac{1.8}{0.6} = I_1 = 3 A$$

$$V_1 = 2.1 \times 3 + 0.6 (-0.5) = 6 V$$

fig-③

P-87

$$I = Y \cdot V$$

$$\text{nodal} \Rightarrow -I_1 + Y_A \cdot V_1 + Y_C (V_1 - V_2) = 0.$$

$$-I_2 + Y_B \cdot V_2 + Y_C (V_2 - V_1) = 0.$$

fig-④

$$\text{By KVL} \Rightarrow V_1 = Z_A \cdot I_1 + Z_C (I_1 + I_2)$$


$$V_2 = Z_B \cdot I_2 + Z_C (I_1 + I_2)$$

fig-⑤

$$\text{By KVL} \Rightarrow V_1 = (n_b + n_c) I_1 + n_{bc} \cdot V_2$$

$$\text{By KCL} \Rightarrow I_2 = Z_{cb} \cdot I_1 + \frac{V_2}{n_c + n_d}$$

Q1 Det. all the two port n/w parameters

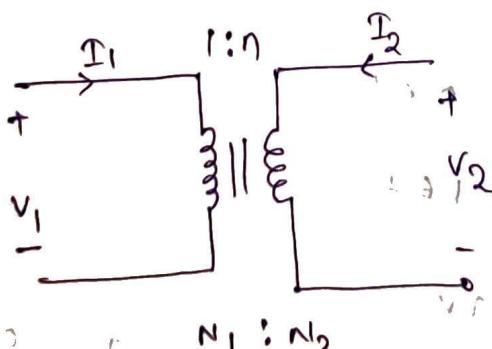

$$\kappa = 1 \Rightarrow m = \sqrt{L_1 L_2}$$

(A)

$$\frac{V_2}{V_1} = \frac{n_2}{n_1} = n = \frac{I_1}{-I_2} \quad (\text{From Coupled CKts})$$

$$\Rightarrow \frac{V_2}{V_1} = n ; \quad \frac{I_1}{-I_2} = n .$$

$\rightarrow \underline{\underline{T}}$:

$$V_1 = \frac{1}{n} V_2 - (0) I_2.$$

$$I_1 = (0) V_2 - n I_2.$$

$$T = \begin{pmatrix} 1/n & 0 \\ 0 & n \end{pmatrix} \quad AD - BC = 1$$

$$T' = T^{-1} = \begin{pmatrix} n & 0 \\ 0 & 1/n \end{pmatrix}$$

$\rightarrow \underline{\underline{h}}$:

$$V_1 = (0) I_1 + \frac{1}{n} V_2,$$

$$I_2 = -\frac{I_1}{n} + (0) V_2.$$

$$\Rightarrow h = \begin{pmatrix} 0 & \frac{1}{n} \\ -\frac{1}{n} & 0 \end{pmatrix} \quad h_{12} = -h_{21} \Rightarrow \text{reciprocal. } T$$

$$g = h^{-1} = \begin{pmatrix} 0 & n \\ n & 0 \end{pmatrix} \quad g_{12} = -g_{21}.$$

$\rightarrow \underline{\underline{Y \& Z}}$

$$v_2 = nv_1$$

$$I_1 = -n I_2.$$

Note:

in an ideal transformer [it is] impossible to express V_1, V_2 in terms of I_1 and I_2 simultaneously, hence the 2-parameter does not exist, similarly the Y-parameters.

Q1 In the above case if the ~~polarities~~ of the sources ~~is~~

turns ratio is $n:1$ then:

(a)

$$\frac{V_2}{V_1} = \frac{nI_2}{nI_1} = \frac{1}{n} = \frac{I_1}{-I_2}$$

$$\Rightarrow T = \begin{pmatrix} n & 0 \\ 0 & \frac{1}{n} \end{pmatrix} \quad \text{&} \quad h = \begin{pmatrix} 0 & n \\ -n & 0 \end{pmatrix}$$

etc.

fig-17

BY KVL in L-D \Rightarrow ~~V₁(s) = 4 I₂(s) + 100/s [I₁(s) + I₂(s)]~~

$$V_2(s) = 3 I_2(s) + \frac{10}{s} [I_1(s) + I_2(s)]$$

fig-19


$$\text{T.A.: } Z_1 = 0.5s = \frac{s}{2} \Omega$$

$$Z_2 = 2 \Omega$$

$$T_A = \begin{pmatrix} 1 + \frac{Z_1}{Z_2} & Z_1 \\ \frac{1}{Z_2} & 1 \end{pmatrix} = \begin{pmatrix} 1 + \frac{s}{4} & \frac{s}{2} \\ \frac{1}{2} & 1 \end{pmatrix}$$

$$T = (T_A)(T_{N_1})$$

fig (18a)

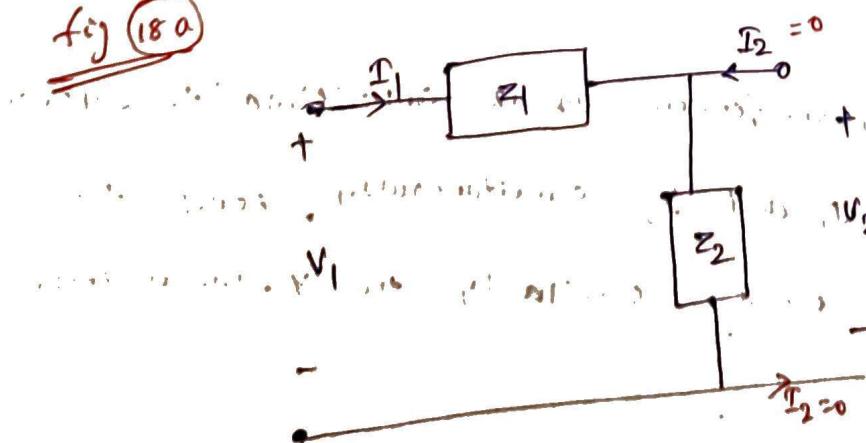

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$



$$V_1 = (z_1 + z_2) \cdot I_1$$

$$V_2 = z_2 \cdot I_1$$

$$\Rightarrow A = 1 + \frac{z_1}{z_2}$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

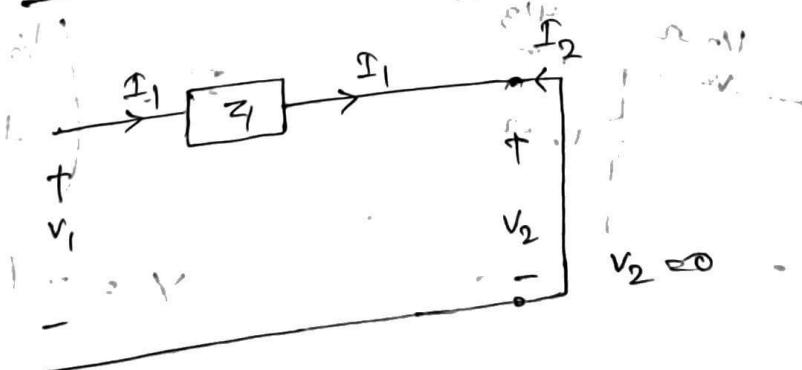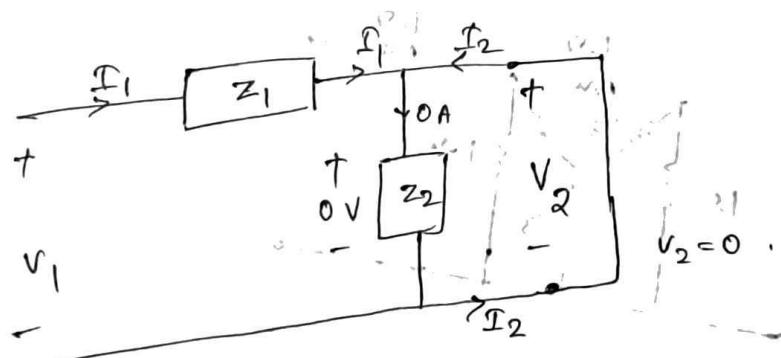


$$\text{By KCL} \Rightarrow -I_1 - I_2 = 0$$

$$\Rightarrow I_1 = -I_2 \Rightarrow D = 1$$

$$\text{By KVL} \Rightarrow V_1 = z_1 I_1 = z_1 (-I_2) \Rightarrow B = z_1$$

$$T_a = \begin{pmatrix} 1 + \frac{z_1}{z_2} & z_1 \\ \frac{1}{z_2} & 1 \end{pmatrix}; \quad \underline{AD - BC = 1}$$

QII Det. Y_{12}

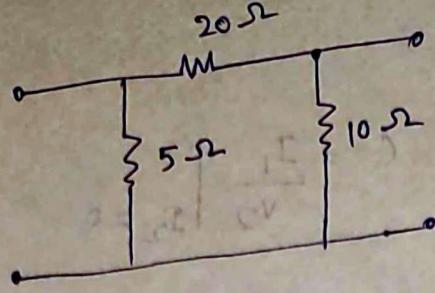

(A)

$$Y_{12} = Y_{21} = -Y_C$$



$$= -\frac{1}{2C} = -\frac{1}{20}$$

$$I = \frac{V}{R} = \frac{V}{20} = 0.05 V$$

$$Y_{11} = Y_A + Y_C = \left(\frac{1}{5} + \frac{1}{20}\right) \text{ } \Omega$$

$$Y_{22} = Y_B + Y_C = \left(\frac{1}{10} + \frac{1}{20}\right) \text{ } \Omega$$


QI Det. Z

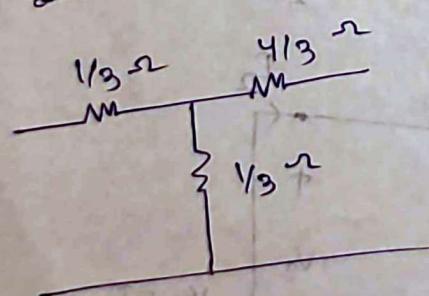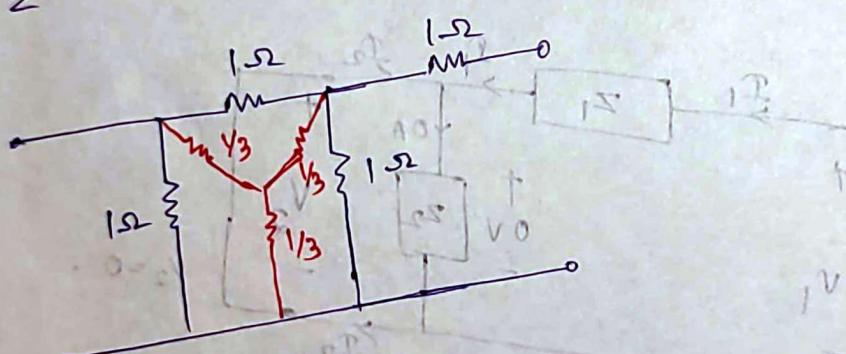

$$\begin{pmatrix} \frac{1}{3} + \frac{1}{3} & \frac{1}{3} \\ \frac{1}{3} & \frac{4}{3} + \frac{1}{3} \end{pmatrix}$$

$$Y = Z^{-1}$$


QI Det. Z .

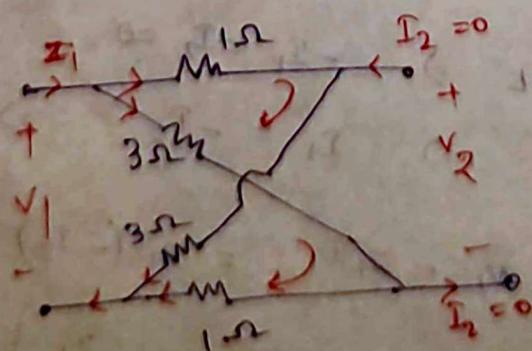

$$z_{11} = \frac{n}{I_1} \Big|_{I_2=0}$$

$$v_1 = (4 \parallel 4) \cdot I_1 \mid_{I_2=0} \quad \text{... (1)}$$

$$\text{similarly } \therefore v_2 = (4 \mid 4) \cdot I_2 \Big|_{I_1=0} \quad \text{passive & reciprocal}$$

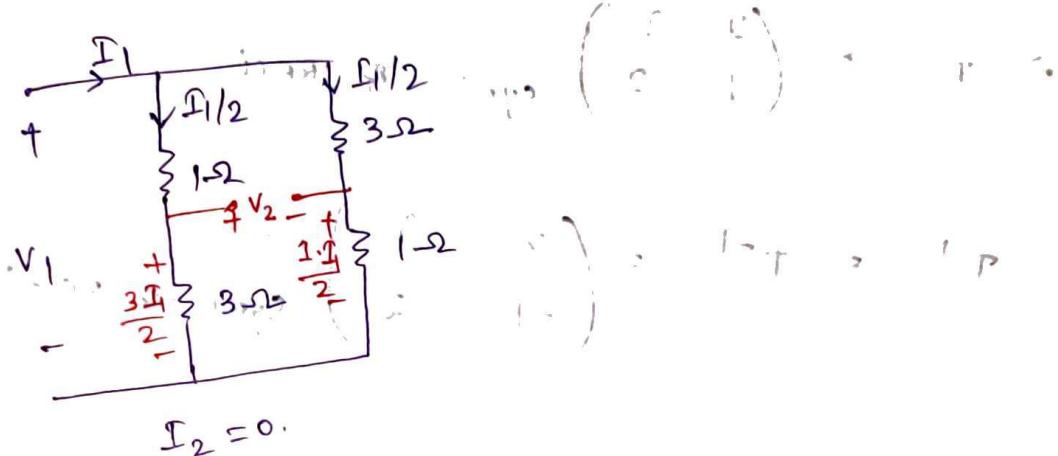

Obs: Hence V_2 is the open circled voltage.

$$By \text{ KVL} \Rightarrow \frac{3 \cdot I_1}{2} - V_2 - \frac{1 \cdot I_1}{2} = 0$$

$$\Rightarrow v_2 = I_1$$

$$\Rightarrow z_2 \cdot z_1 = z_{12}.$$

$$Z = \begin{pmatrix} 2 & \begin{pmatrix} 1 \\ 2 \end{pmatrix} \\ 0 & 1 \end{pmatrix} \quad \text{symi \& Reci}$$

$$Y = Z^{-1} = \begin{pmatrix} \frac{2}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{pmatrix}, \text{ sym & Reci}$$

T:

$$v_1 = 2I_1 + I_2 \quad \rightarrow ①$$

$$v_2 = I_1 + 2I_2 \quad \rightarrow ②$$

$$② \Rightarrow I_1 = v_2 - 2I_2 \quad \rightarrow ③$$

$$③ \text{ in } ① \Rightarrow v_1 = 2(v_2 - 2I_2) + I_2$$

$$= 2v_2 - 3I_2 \quad \rightarrow ④$$

$$\Rightarrow T = \begin{pmatrix} 2 & 3 \\ 1 & 2 \end{pmatrix} \text{ symi & Reci}$$

$$T^1 = T^{-1} = \begin{pmatrix} 2 & -3 \\ -1 & 2 \end{pmatrix} \text{ symi & Reci.}$$

h:

$$② \Rightarrow 2I_2 = T I_1 + v_2$$

$$\Rightarrow I_2 = -\frac{I_1}{2} + \frac{v_2}{2} \quad \rightarrow ⑤$$

$$⑤ \text{ in } ① \Rightarrow v_{Q1} = 2I_1 - \frac{I_1}{2} + \frac{v_2}{2}$$


$$= \frac{3}{2} I_1 + \frac{v_2}{2} \quad \rightarrow ⑥$$

$$\Rightarrow h = \begin{pmatrix} \frac{3}{2} & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{pmatrix} \text{ symi & Reci.}$$

$$g = h^{-1} = \begin{pmatrix} \frac{1}{2} & -\frac{1}{2} \\ \frac{1}{2} & \frac{3}{2} \end{pmatrix} \text{ symi & Reci}$$

Q1

Def. cell the two port N/W parameters

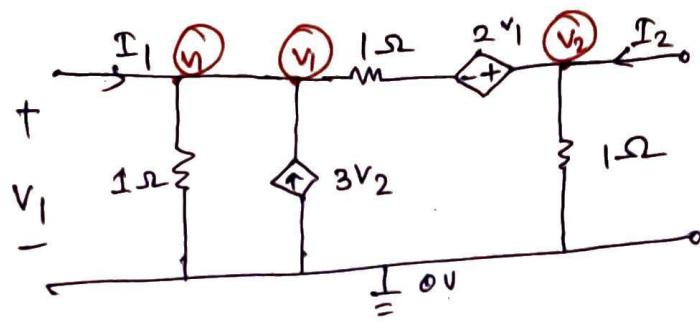

A

NODAL \Rightarrow

$$-I_1 + \frac{V_1}{1} - 3V_2 + \frac{V_1 + 2V_1 - V_2}{1} = 0$$

$$\Rightarrow I_1 = 4V_1 - 4V_2 \quad \text{--- (1)}$$

Nodal \Rightarrow

$$-I_2 + \frac{V_2}{1} + \frac{V_2 - 2V_1 - V_1}{1} = 0$$

$$\Rightarrow I_2 = -3V_1 + 2V_2 \quad \text{--- (2)}$$

$$\Rightarrow Y = \begin{pmatrix} 4 & -4 \\ -3 & 2 \end{pmatrix}$$

Any mi & non-reci
and active that too
dependent sources with only resi

$Z = Y^{-1}, g, h, T, T'$ by re-writing the eqn.

Q2

The Z-Parameter of two two port networks are :-


(1) & $\begin{pmatrix} 1 & 2 \\ 3 & 4 \end{pmatrix}$ if there two networks are connected in series, then the Z-parameter of the overall two port network.

$$\textcircled{A} \quad Z = (Z_A) + (Z_B) = \begin{pmatrix} 2 & 2 \\ 4 & 5 \end{pmatrix} \Omega$$

$Y = Z^{-1}$, g, h, T, T^{ad} by re-writing the eqns.

All

Det. - T

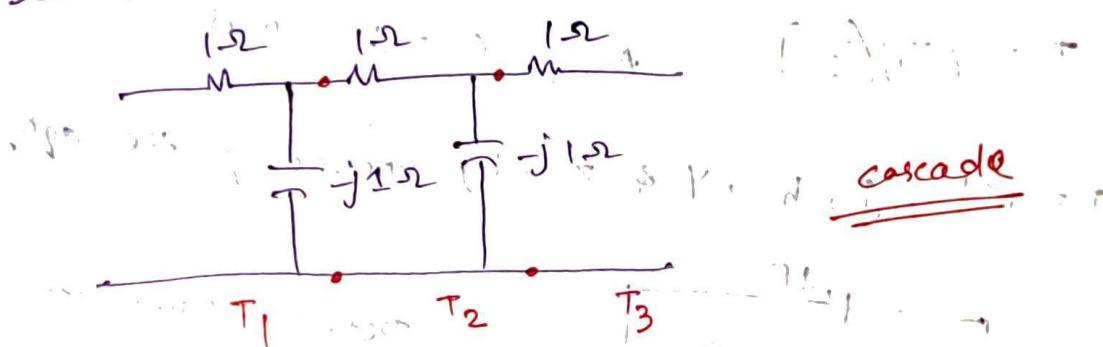

$$T_1 = T_2 : z_1 = 1 \Omega$$

$$z_2 = -j1 \Omega$$

$$T_1 = T_2 = \begin{pmatrix} 1 + \frac{1}{-j1} & 1 \\ 1 & 1 \end{pmatrix}$$

$$= \begin{pmatrix} 1+j & 1 \\ j & 1 \end{pmatrix}$$

$$AD - BC = 1$$

$$T_3 : z_1 = 1 \Omega$$

$$z_2 = \infty$$


$$\Rightarrow T_3 =$$

$$\begin{pmatrix} 1 & 1 \\ 0 & -1 \end{pmatrix}$$

$$\boxed{T = (T_1)(T_2)(T_3)}$$

$$AD - BC = 1 \text{ must}$$
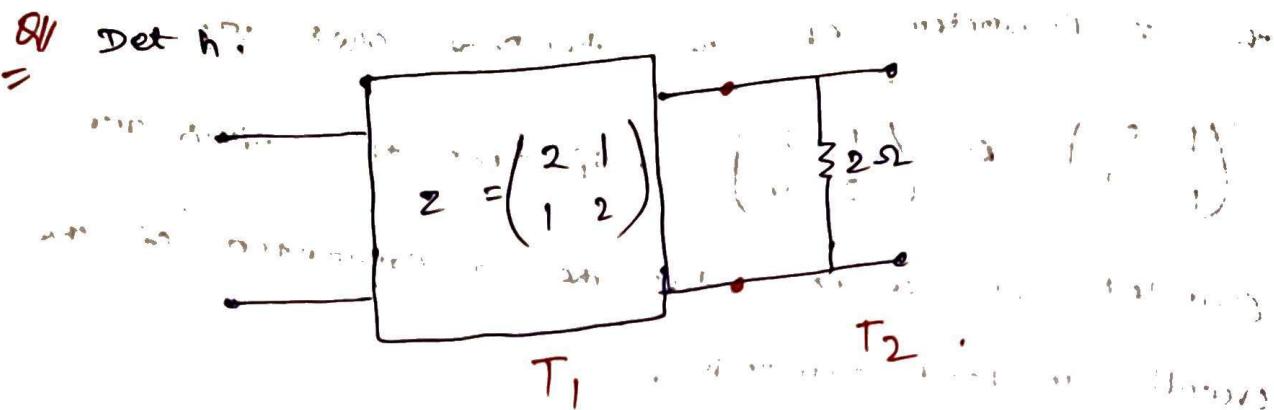
$$T^{\text{ad}} = T^{-1}, g, h, Y \text{ & } Z \text{ by re-writing the eqns.}$$




$$T_1 : z = \begin{pmatrix} 2 & 1 \\ 1 & 2 \end{pmatrix} \Rightarrow T_1 = \begin{pmatrix} 2 & 3 \\ 1 & -2 \end{pmatrix}$$

$$T_2 : z_1 = 0 \Rightarrow T_2 = \begin{pmatrix} 1 & 0 \\ \frac{1}{2} & 1 \end{pmatrix}$$

$$T = (T_1)(T_2) \quad AD - BC = 1 \text{ must}$$

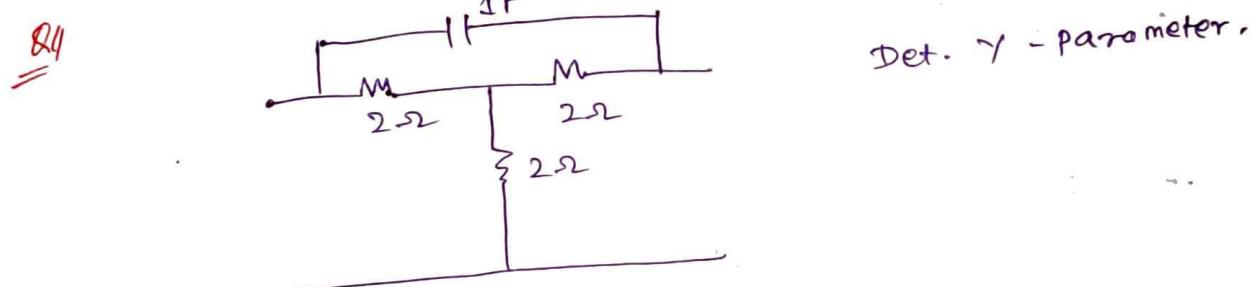$T = T^{-1}, g, h, Y$ & z by reworking the eqns.




Det. γ - parameter.

(A)

$$z_A = \begin{pmatrix} 4 & 2 \\ 12 & 4 \end{pmatrix}$$
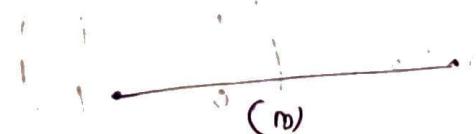
$$Y_A = \begin{pmatrix} \frac{1}{3} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{1}{3} \end{pmatrix} \text{ v.}$$



$$z' = \frac{1}{s} \cdot \omega \Rightarrow Y_A = \frac{s}{3} \cdot \omega$$


$$Y_B = \frac{1}{4} \begin{pmatrix} Y & -Y \\ -Y & Y \end{pmatrix} = \begin{pmatrix} s & -s \\ -s & s \end{pmatrix} \text{ or } \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$$

$$|Y| = |Y_A| + |Y_B|$$

symi & Reci.

$$z = Y^{-1}, T, T', g, h \quad \text{by rewriting the eqn.}$$

Q11

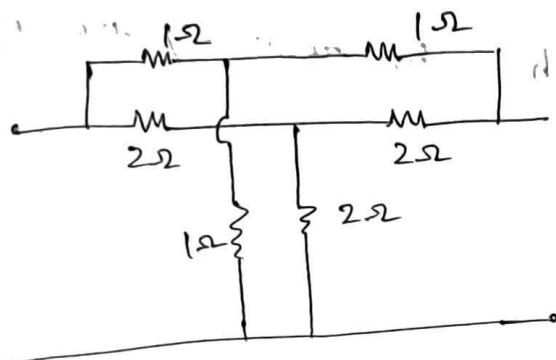

Det. Y .

$$Z_A = \begin{pmatrix} 4 & 2 \\ 2 & 4 \end{pmatrix} \Omega$$

$$Z_B = \begin{pmatrix} 2 & 1 \\ 1 & 2 \end{pmatrix} \Omega$$

$$Y_A = \begin{pmatrix} \frac{1}{3} & -\frac{1}{6} \\ -\frac{1}{6} & \frac{1}{3} \end{pmatrix} \text{ or}$$

$$\Rightarrow Y_B = \begin{pmatrix} \frac{2}{3} & -\frac{1}{3} \\ -\frac{1}{3} & \frac{2}{3} \end{pmatrix} \text{ or}$$


$$Y = (Y) + (Y_B) = \begin{pmatrix} 1 & -\frac{1}{2} \\ -\frac{1}{2} & 1 \end{pmatrix} \text{ or}$$

Symi & Reci

$$z = Y^{-1}, T, T', g, h \quad \text{by rewriting the eqn.}$$

Q11

Det. Y .

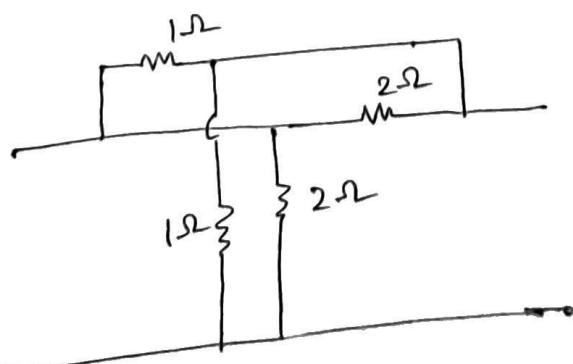

$$Z_A = \begin{pmatrix} 2 & 2 \\ 2 & 4 \end{pmatrix} \Omega$$

$$Y_A = \begin{pmatrix} 1 & -\frac{1}{2} \\ \frac{-1}{2} & \frac{1}{2} \end{pmatrix} \text{ or}$$

$$z = \begin{pmatrix} 1 & 2 \\ 2 & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} v = \begin{pmatrix} 1 & 2 \\ 2 & 1 \end{pmatrix} v$$

$$\Rightarrow y_B = \begin{pmatrix} 1 & -1 \\ -1 & 2 \end{pmatrix} v$$

$$(Y)_B = (Y_A) + (Y_B)$$

Asym & Reci

$z = y^{-1}, T, T^1, g, h$ by rewriting the eqns.

$$z = \begin{pmatrix} 1 & 2 \\ 2 & 1 \end{pmatrix} v$$

$$z = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} v$$

A =

$$z = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} v$$

$$z = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} v$$

A'

$$\therefore z = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} v + (ev) + (fv) = v$$

Eqn 2: v satisfies $A'v = 0$, i.e., $T^1 v = 0$