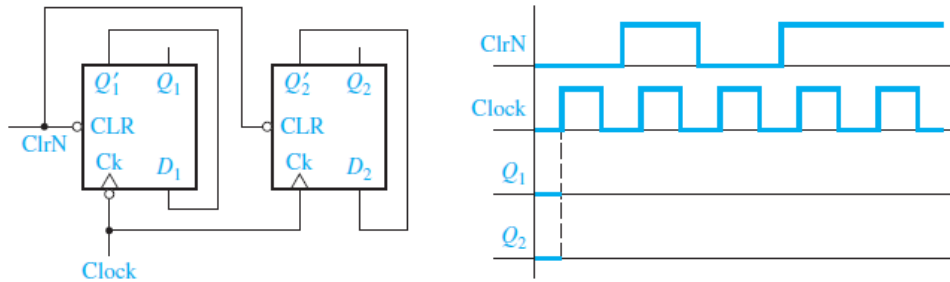



1. An  $AB$  latch operates as follows: If  $A = 0$  and  $B = 0$ , the latch state is  $Q = 0$ ; if either  $A = 1$  or  $B = 1$  (but not both), the latch output does not change; and when both  $A = 1$  and  $B = 1$ , the latch state is  $Q = 1$ .

- (a) Construct the truth table and derive the characteristic equation for this  $AB$  latch.
- (b) Derive a circuit for the  $AB$  latch that has four two-input NAND gates and two inverters.

2. Complete the timing diagram for the following circuit. Note that the Ck inputs on the two flip-flops are different.



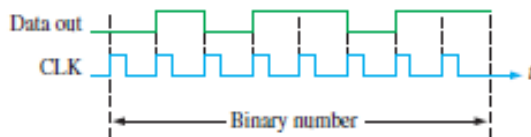3. The sequence 1011 is applied to the input of a 4-bit serial shift register that is initially cleared. What is the state of the shift register after three clock pulses?
4. A leading-edge clocked serial in/serial out shift register has a data-output waveform as shown in figure. What binary number is stored in the 8-bit register if the first data bit out (leftmost) is the LSB?



5. If a 10-bit ring counter similar has the initial state 1010000000, determine the waveform for each of the  $Q$  outputs.