

HARDWARE DESCRIPTION LANGUAGE

Digital Design (with an introduction to the Verilog HDL) 6th Edition,
M. Morris Mano, Michael D. Ciletti



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY,
DESIGN AND MANUFACTURING,
KANCHEEPURAM

- Dr. Kalpana Settu
Assistant Professor
ECE, IIITDM Kancheepuram

HDL

- A hardware description language (HDL) is a computer-based language that describes the hardware of digital systems in a textual form. It resembles an ordinary computer programming language, such as C, but is specifically oriented to describing hardware structures and the behavior of logic circuits.
 - It can be used to represent logic diagrams, truth tables, Boolean expressions, and complex abstractions of the behavior of a digital system.
 - One way to view an HDL is to observe that it describes a relationship between signals that are the inputs to a circuit and the signals that are the outputs of the circuit.
- There are two standard HDLs that are supported by the IEEE: VHDL and Verilog (IEEE: Institute of Electrical and Electronics Engineers).
 - Why Verilog, not VHDL? Easier!!

Very High Speed Integrated Circuit (VHSIC) Hardware Description Language (VHDL)


Three Modeling Styles in Verilog

- Gate-level Modeling (also known as **Structural modeling**) describes a circuit by specifying its gates and how they are connected with each other.
- Dataflow Modeling is used mostly for describing the Boolean equations of combinational logic and uses continuous assignment statements with the keyword **“assign”**.
- Behavioral Modeling uses procedural assignment statements with the keyword **“always”**. It is used mostly to describe sequential circuits.

Gate-level Modeling

Module Description

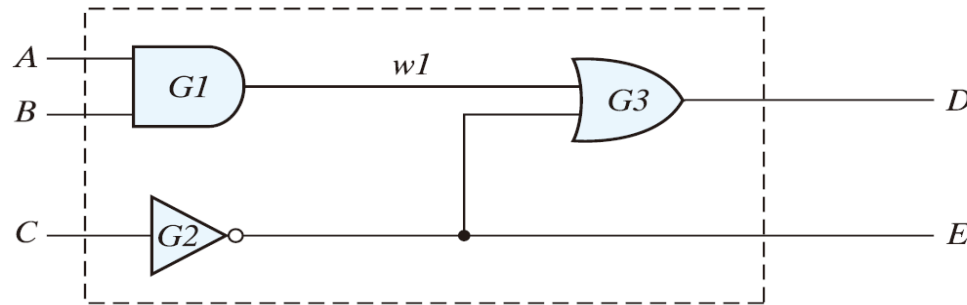- **Keywords:** module, endmodule, input, output, wire, and, or, not



// Verilog model of circuit of Figure 3.35. IEEE 1364–1995 Syntax

```
module Simple_Circuit (A, B, C, D, E);  
  output D, E;  
  input A, B, C;  
  wire w1;  
  
  and G1 (w1, A, B); // Optional gate instance name  
  not G2 (E, C);  
  or G3 (D, w1, E);  
endmodule
```


input and output specify which of the ports are inputs and which are outputs

module and endmodule → start and end of the declaration (description) of the module



wire → internal connection

and, or, not → primitive gates (basic functional block used in Verilog HDL)

Create Verilog Script

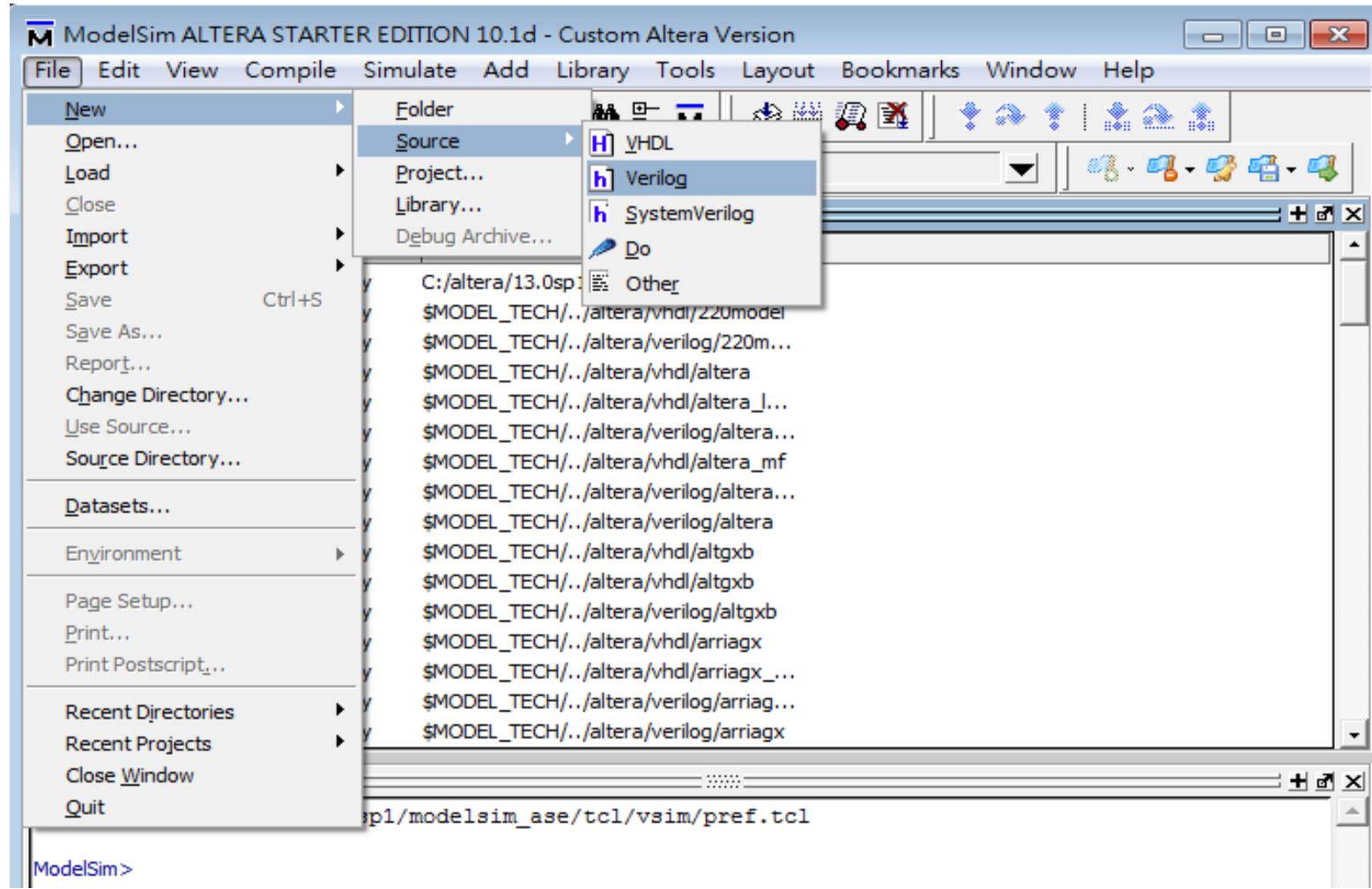


Verilog Script

 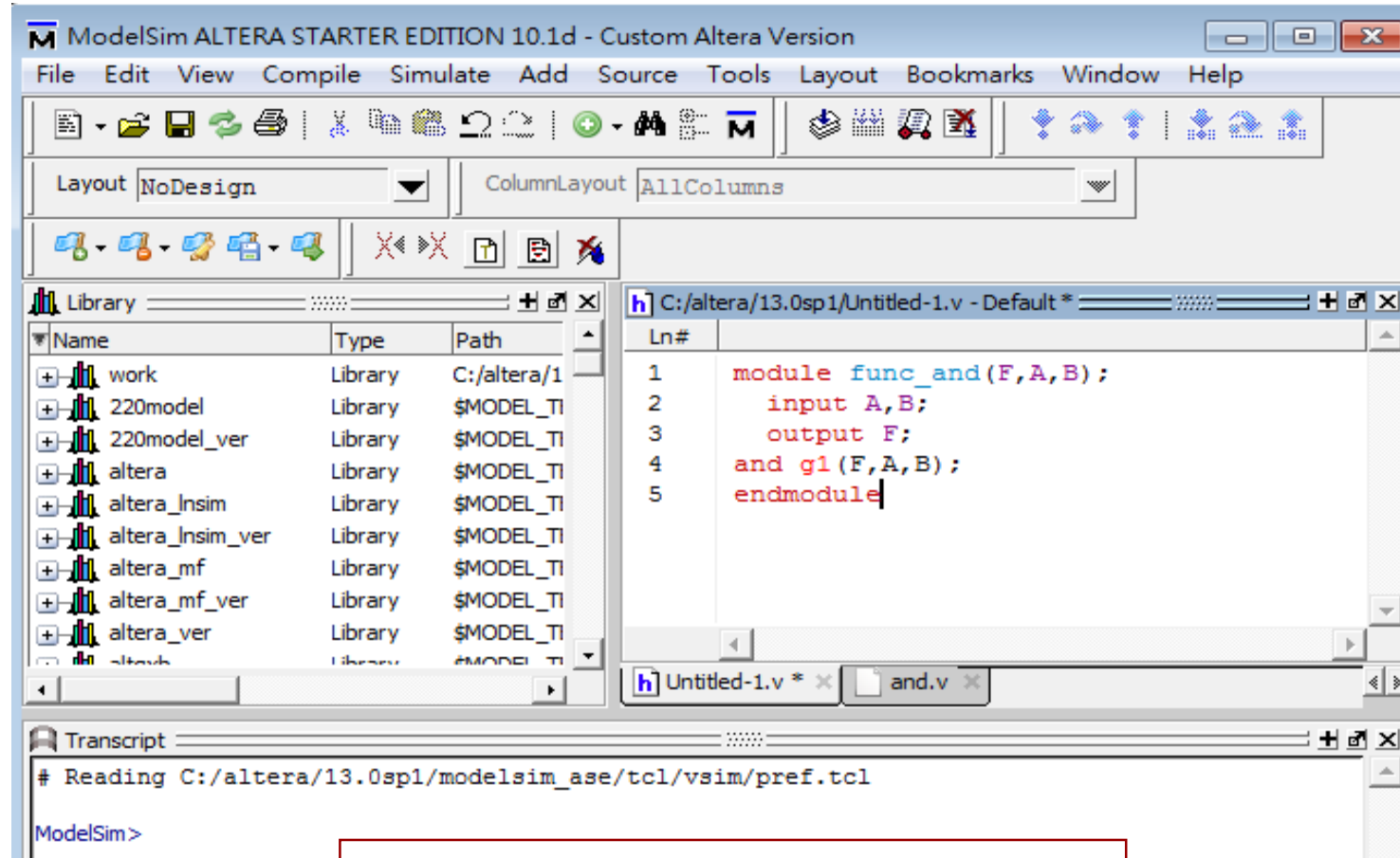


Try to understand the script

Save Your Script

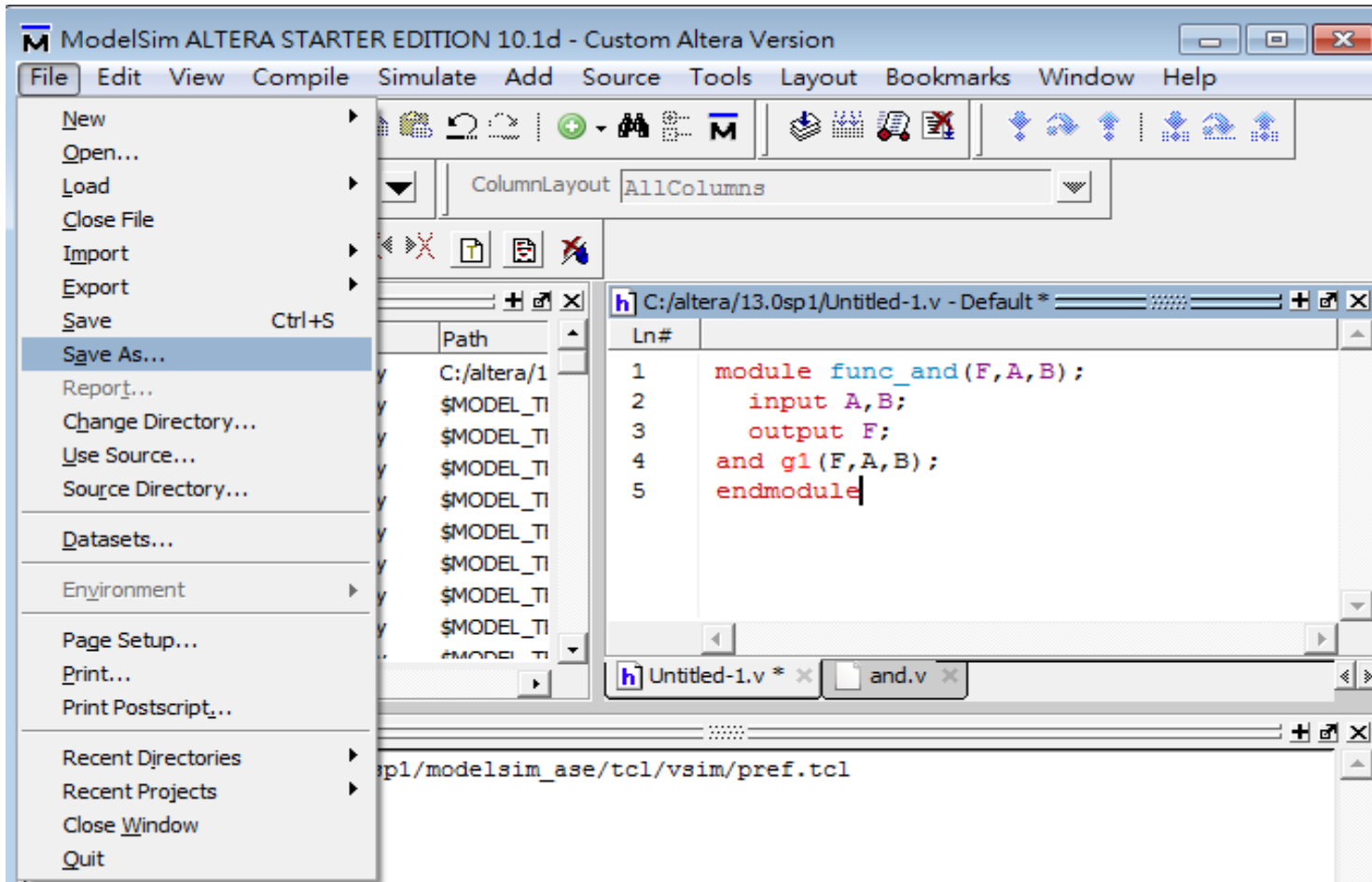


You can create a folder called “Data” and save the file named “and.v” in the folder

Compile Your Script

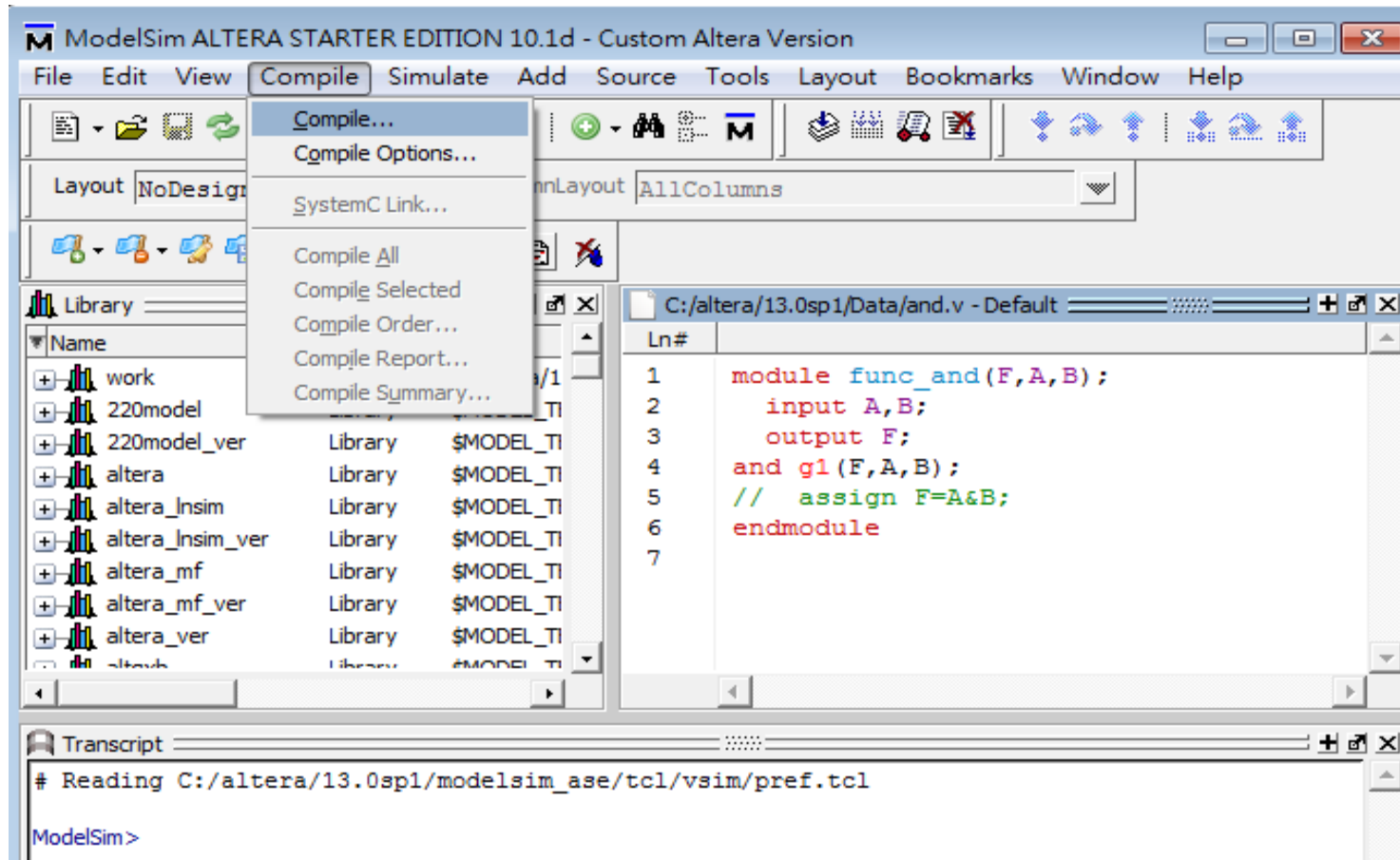

Compile Your Script

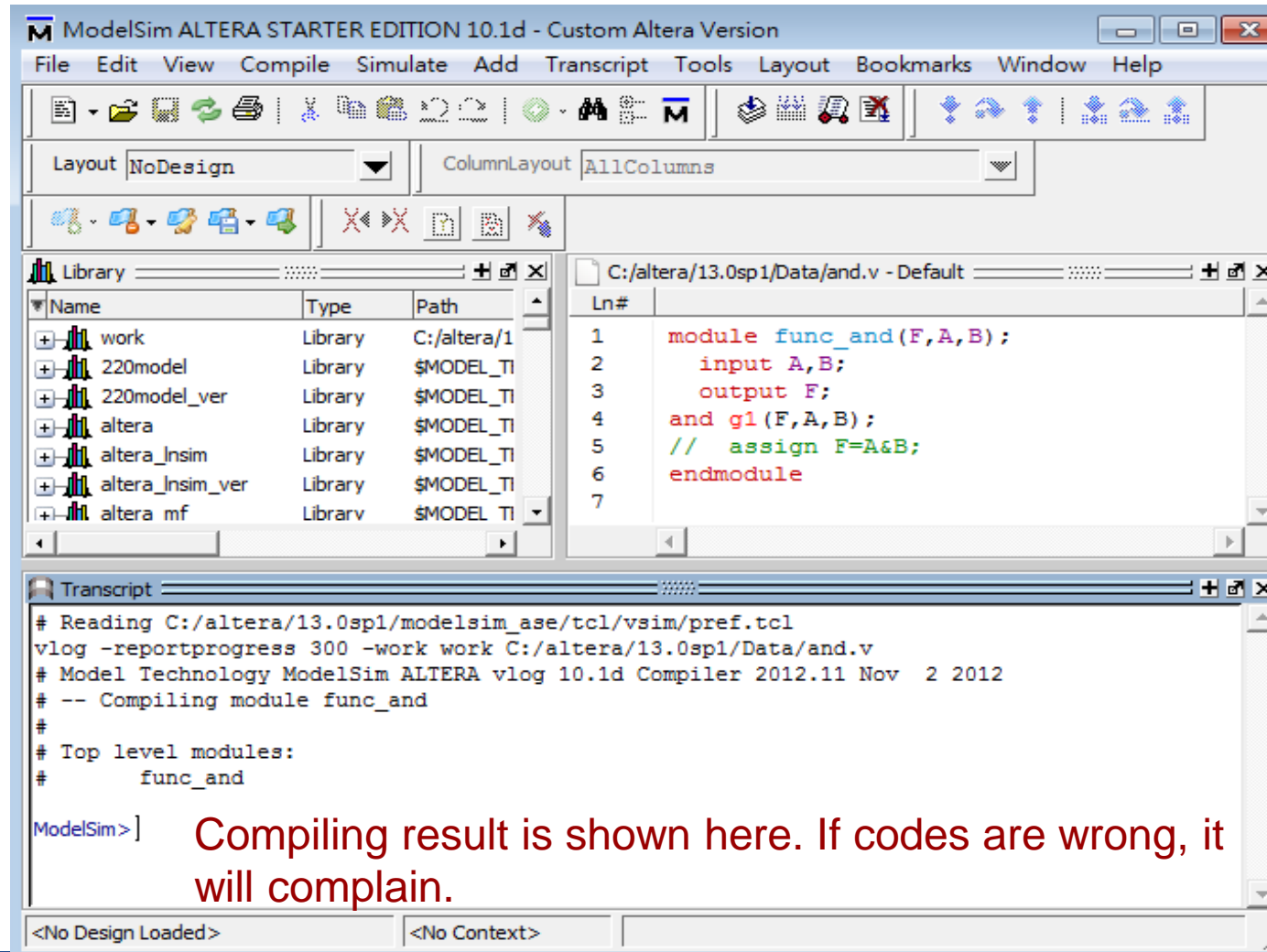

Test Bench

- In order to simulate a circuit with an HDL, it is necessary to apply inputs to the circuit so that the simulator will generate an output response.
- An HDL description that provides the stimulus to a design is called a *test bench*.
- In its simplest form, a test bench is a module containing a signal generator and an instantiation of the model that is to be verified.

Create a Test Bench

```
C:/intelFPGA_pro/17.0/data/test_bench_2var.v - Default
Ln#
1  `include "C:/intelFPGA_pro/17.0/data/and.v"
2  module tb_func;
3      reg A = 1'b0;
4      reg B = 1'b0;
5      wire F;
6      func_and M1 (F,A,B);
7
8  initial
9      begin
10         #2000;
11         $stop;
12     end
13
14     initial
15         begin
16             #250 A = 1'b0; B = 1'b1;
17             #250 A = 1'b1; B = 1'b0;
18             #250 A = 1'b1; B = 1'b1;
19         end
20     endmodule
```


reg → register

1'b0 → 1 bit, binary code, value 0
 
#2000 means run 2000 time units and then stop (total simulation generates waveforms over an interval of 2000 ps)



After 250 time units A is 0 and B is 1

- Understand the script
- Save it as "test_bench_2var.v"




Simulate the Test Bench

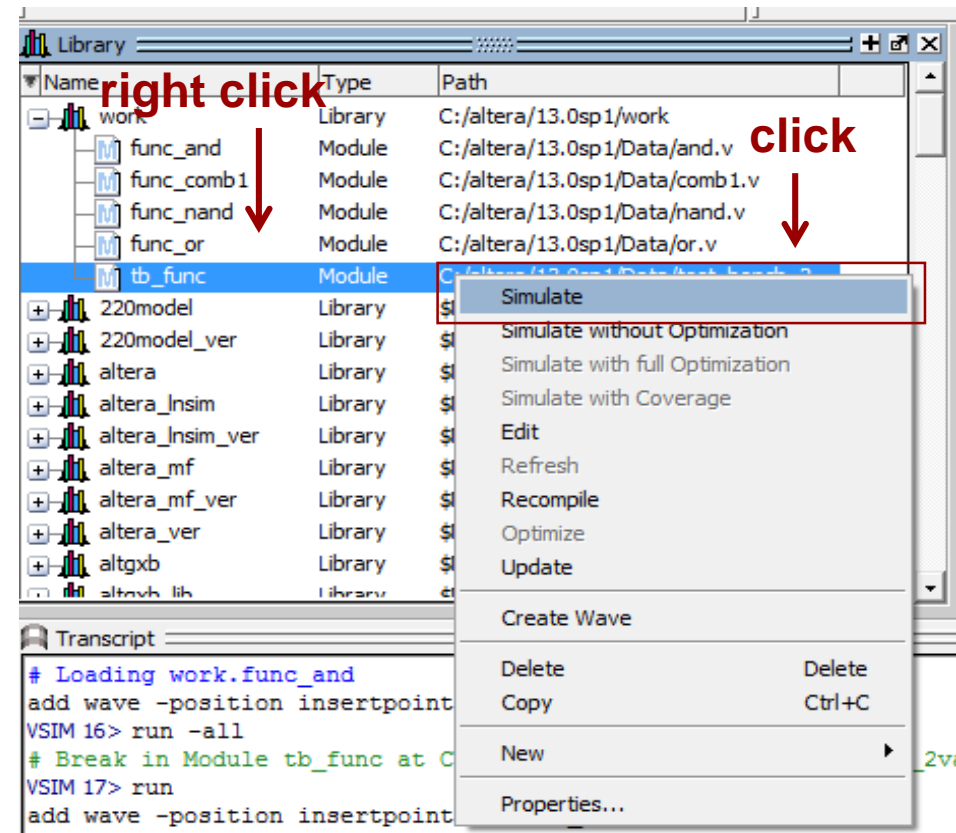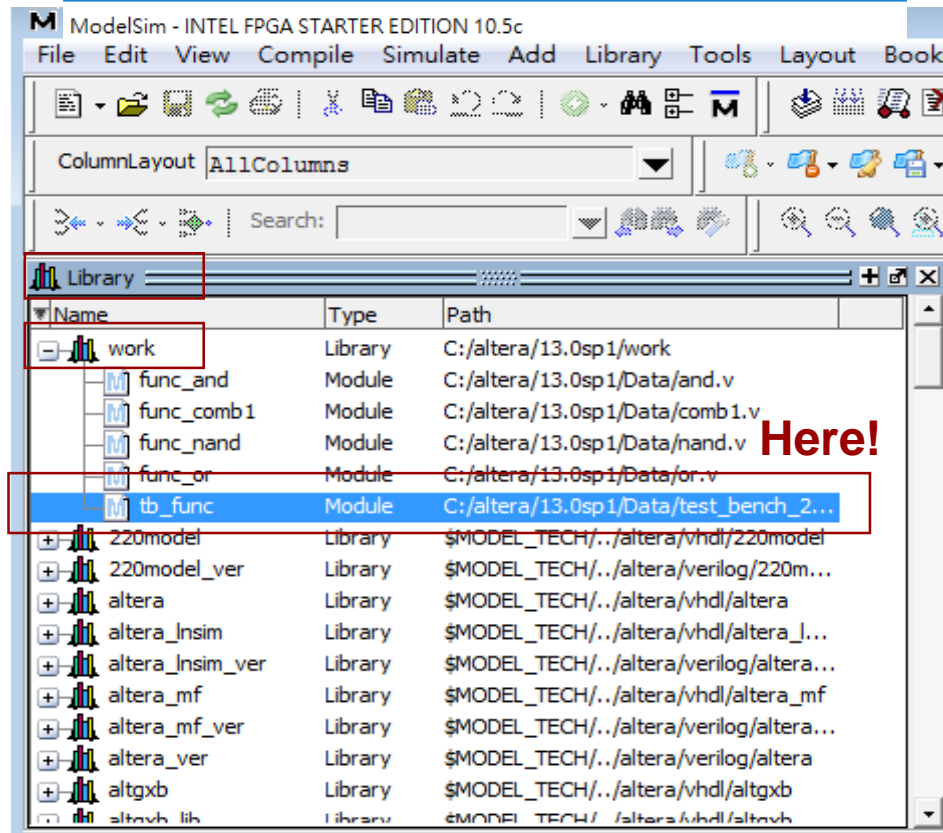- After compiling, go to Library “work” and find the module called “tb_func”, which you defined in your test bench.
- Right click tb_func and click on “simulate”.



Waveforms

 

Data Flow Modeling

- A Boolean function can be directly described in Verilog. You do not need to care about gate-level logic.
- Here is an example of how do you write an “AND” operation in Verilog using the command “**assign**”.

Ln#	
1	<code>module func_and(F,A,B);</code>
2	<code>input A,B;</code>
3	<code>output F;</code>
4	<code>assign F=A&B;</code>
5	<code>endmodule</code>
6	

- The operator “&” means “AND” operation.

Example:

$$F = B'C + BC'A' + (A \oplus C)$$

```
assign F = (~B&C) | (B&~C&~A) | (A^C);
```

Behavioral Modeling

- Behavioral Modeling uses procedural assignment statements with the keyword “**always**”. It is used mostly to describe sequential circuits.



always @(A or B or select)

The procedural assignment statements inside the always block are executed every time there is a change in any of the variables listed after the @ symbol.

➤ DFF Module

```
1 module DFF(Q,D,CLK);
2   input D,CLK;
3   output Q;
4   reg Q;
5   always @(posedge CLK)
6     Q<=D;
7 endmodule
```

  always @(posedge CLK) → This statement will initiate execution of the procedural statements in the associated always block if a change occurs in posedge CLK



Verilog simulation

- To complete a verilog simulation, we need to do following steps:
 1. Create a file for a main logic **Verilog script**, named “xxx.v”.
 2. Create **a test bench** file, also named “zzz.v”, to test your script.
 3. **Compile** each script → check if scripts are correct.
 4. **Simulate** the test bench.
 5. **Add Wave** and **Run** to evaluate timing signals.
 6. Use **wave function** to check the results.

The End

Reference:

1. Digital Design (with an introduction to the Verilog HDL) 6th Edition, M. Morris Mano, Michael D. Ciletti

Note: The slides are supporting materials for the course “Digital Circuits” at IIITDM Kancheepuram. Distribution without permission is prohibited.