

23/08/23

Reference Books:

Hughes - Electrical and Electronic Technology

- Edward Hughes,
- Ian McKenzie Smith
- John Hiley
- Keith Brown

(Charles Alexander)

→ Tenth Edition, Pearson, 2010

→ Electrical Energy

- Flexible
- Efficiency
- Clean

Electrical	→ W, kW, MW
Electronic	→ μW , mW

Electrical	Electronic
1) Fan, Light, Powerplant, etc	2) Video call, Voice call, etc
2) W, kW, MW	2) μW , mW
3) V, kV, MV	3) mV, V
4) A, kA	4) μA , mA
5) Power Frequency 50 Hz, 60 Hz	5) kHz, MHz, GHz

Sources of DC → Battery, Solar Cells, DC Generator, Fuel Cells

Sources of AC → AC Generator

Generation



Transmission



Distribution → Consumers

24/09/23

Generated Power : 100 MW

Voltage : 10 kV

$$i = \frac{P}{V} = \frac{100 \times 10^6}{10 \times 10^3}$$

$$= 10 \text{ kA} \Rightarrow \boxed{I_v = 10 \text{ kA}}$$

~~10 kA~~

$I \uparrow \Rightarrow \text{Size} \uparrow \Rightarrow \text{Volume} \uparrow \Rightarrow \text{Cost} \uparrow$

distance $\uparrow \Rightarrow$ Resistance (Internal) $\uparrow \Rightarrow$ Voltage drop \uparrow
($i^2 R$ loss) \uparrow



Efficiency \downarrow

$P = i \cdot V \uparrow$

$V : 10 \text{ kV} \rightarrow 100 \text{ kV}$ (Transformer)

~~VA~~

$\Rightarrow i : 10 \text{ kA} \rightarrow 1 \text{ kA}$

Efficiency of Transformer : 99.5%


- (i) Voltage
- (ii) Current
- (iii) Power
- (iv) Work
- (v) Resistance
- (vi) Inductance
- (vii) Capacitance

Primary Consumer \rightarrow Bulk ~~con~~
Secondary Consumer \rightarrow Domestic

Electricity Fundamentals

CHAPTER-I

Materials

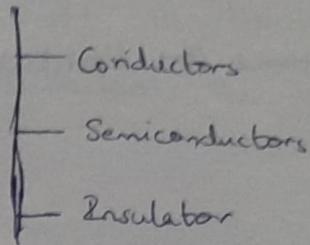

Air gets ionized \rightarrow 30 kV per cm

$$\text{Electric Potential, } V = \frac{\text{Work done}}{\text{Charge}} = \frac{dW}{dq} \quad \left[\text{Volt (or) Joule/Coulomb} \right]$$

EMF : Difference in potentials ~~of~~ of two charged bodies
is called Potential difference. It develops EMF.

$$i = \frac{dq}{dt}$$

$$\text{Energy} = \text{Work} = Vq = Vit$$

$$V = \frac{\text{Work}}{q}$$

$$P = \frac{dF}{dt} \quad \& \quad \text{Power} = \frac{\text{Work}}{t}$$

$$\Rightarrow \frac{Vit}{t} = \underline{\underline{iV}}$$

25/8/23

Law of Conservation of Energy

$$P_{\text{supplied}} = VI = P_{\text{output}}$$

Active Element \rightarrow Produces Energy
Passive Element \rightarrow Receives Energy

Bilateral Elements \rightarrow Resistors

Unilateral Elements \rightarrow Diodes

$$R = \rho \frac{l}{a} \quad \begin{matrix} \text{specific Resistance (or) Resistivity} \\ \downarrow \\ \text{ohms (R)} \end{matrix}$$

$$G = \frac{1}{R} \quad \begin{matrix} \downarrow \\ \text{Siemens (or) Mho (or) } \\ (S) \end{matrix}$$



For study, we assume sources are independent.
But in Reality, the sources are dependent.

○ \rightarrow Independent

(\sim) \rightarrow Independent AC source

($+$) \rightarrow Independent DC source

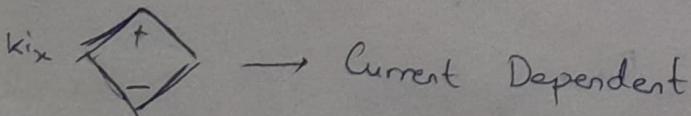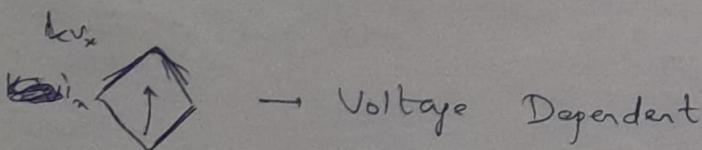(\uparrow) \rightarrow Independent Current source



Q) An energy source forces a constant current of 2A for 10s to flow through a light bulb. If 2.3 kJ is given off in the form of light and heat energy. Calculate the voltage drop across the bulb.

~~Wattage~~

Sol: Given :

$$i = 2 \text{ A}$$


$$t = 10 \text{ s}$$

$$H = i^2 R t$$

$$= Vit$$

$$\Rightarrow 2300 = V \times 2 \times 10$$
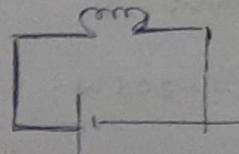
$$\Rightarrow \boxed{V = 115 \text{ V}}$$



$$(OR) \quad \Delta Q = i \Delta t = 20 \text{ C}$$

$$V = \frac{\Delta Q}{\Delta t} = 115 \text{ V}$$

Q) How much energy does a ~~100~~ 100 W electric bulb consume in 2 hours?

$$\begin{aligned} \text{Ans: } P \cdot E &= 2 \times 100 = 200 \text{ Watt hrs} \\ &= 200 \times 3600 = 720 \text{ kJ} \end{aligned}$$

$$(W = P \cdot t)$$


Q) A 100 v lamp has a hot resistance of 250 Ω. Find the current taken by the lamp and its Power rating in watts. Calculate also the energy it will consume in 24 hours.

Sol: Given :

$$V = 100 \text{ V}$$

$$R = 250 \Omega$$
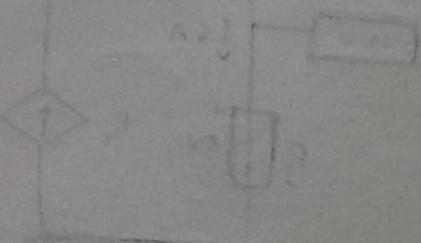
$$P = V^2/R = \frac{100 \times 100}{250} = 40 \text{ W}$$



$$\begin{aligned} P &= iV \\ &= i^2 R \end{aligned}$$

$$W = Pt$$


$$= 40 \times 24 = 960 \text{ Watt-hours}$$

$$i = \frac{V}{R} = \frac{100}{250} = 0.4 \text{ A}$$

Q) Figure shows a circuit with five elements.

~~Q~~ Calculate the Power P_3 received or Delivered by element 3.

$$P_1 = -205 \text{ W}$$

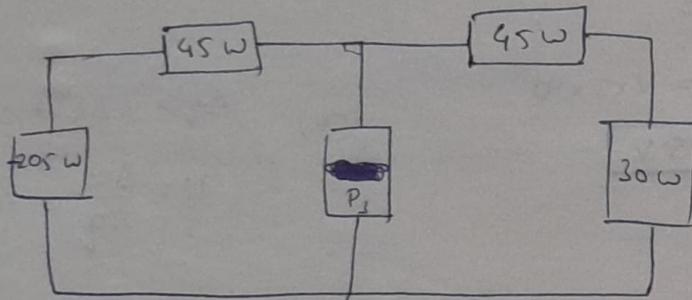


$$\sum_{i=1}^5 P_i = 0 \Rightarrow P_3 = 85 \text{ W}$$

Received

According to Law of Conservation of Energy

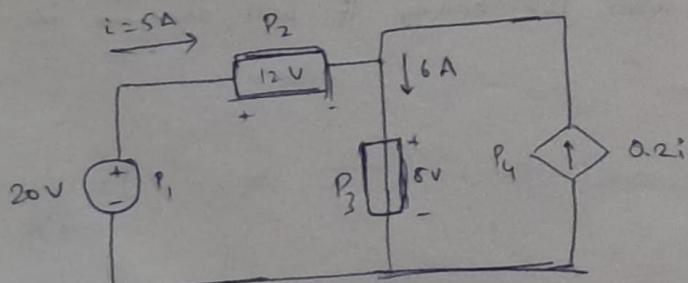Q) Calculate the power absorbed or supplied by each element.



$$\sum P = 0$$

$$P_1 + P_2 + P_3 + P_4 = 0$$

$$P_3 = 48 \text{ W}$$



$$P_1 = -100 \text{ W}$$

$$P_2 = 60 \text{ W}$$

$$P_4 = 8 \text{ W}$$

(Supplied :-ve)

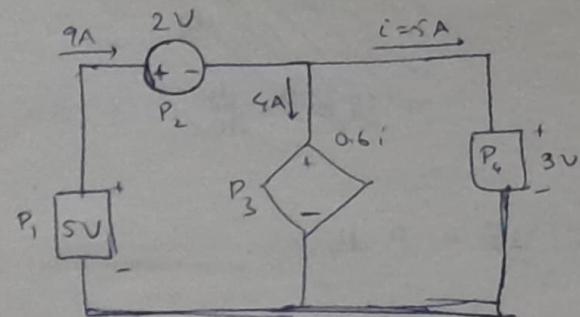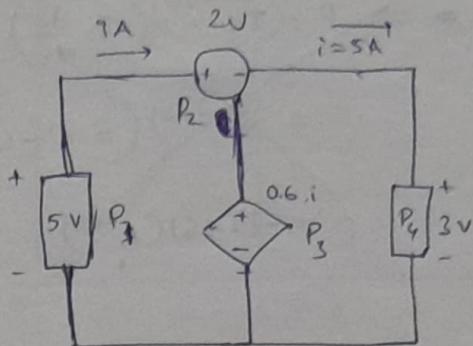Q) Find the power absorbed or supplied by each component.



$$P_1 = 45 \text{ W}$$

$$P_4 = 15 \text{ W}$$

$$P_2 = 18 \text{ W}$$

$$\rightarrow P_3 = 9 \text{ W}$$

27/8/23

Practice Problems :

Q3) $i = 85 \text{ mA}$
 $t = 12 \text{ h}$

$$q = it$$

$$= 85 \times 10^{-3} \times 12 \times 3600$$

$$= 3672 \text{ C}$$

$$\boxed{q = 3.672 \text{ kC}}$$

$$E = (iV)t$$

$$(P = E/t)$$

$$\Rightarrow E = 85 \times 10^{-3} \times 1.2 \times 12 \times 3600$$

$$= 4406.4 \text{ J}$$

$$= 4.4064 \text{ kJ}$$

Q4) $i(t) = 3e^{-2t} \text{ A}$

$$V(t) = 5 \frac{di}{dt} \text{ V}$$

(a) $dq = i \cdot dt$

$$\Rightarrow \int_0^t dq = \int_0^t 3e^{-2t} dt$$

$$\Rightarrow q = \left[-\frac{3}{2} e^{-2t} \right]_0^t$$


$$= \left[\frac{3}{2} e^{-2t} \right]_0^t = \left(\frac{3}{2} - \frac{3}{2} e^{-4} \right) = 1.4725 \text{ C}$$

$$= \int_0^3 15 \times e^{-2t} dt.$$


Q5)

$$i(t) = \begin{cases} 3t, & 0 \leq t \leq 6 \\ 18, & 6 \leq t < 10 \\ -12, & 10 \leq t < 15 \\ 0, & 15 \leq t \end{cases}$$

$0 < t < 20$

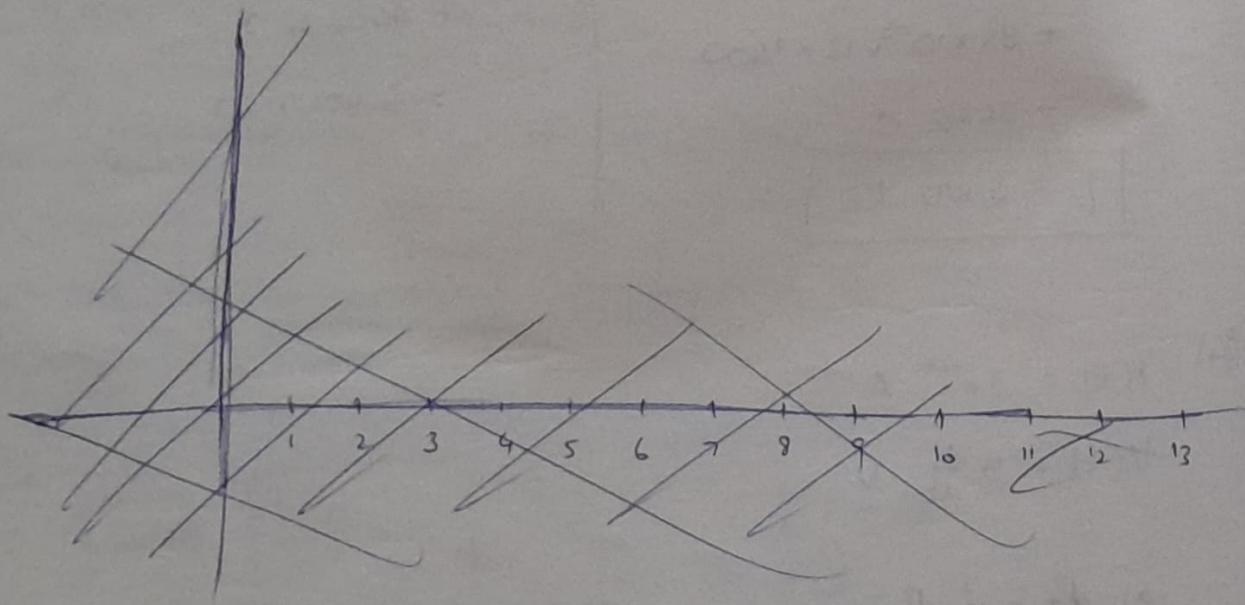

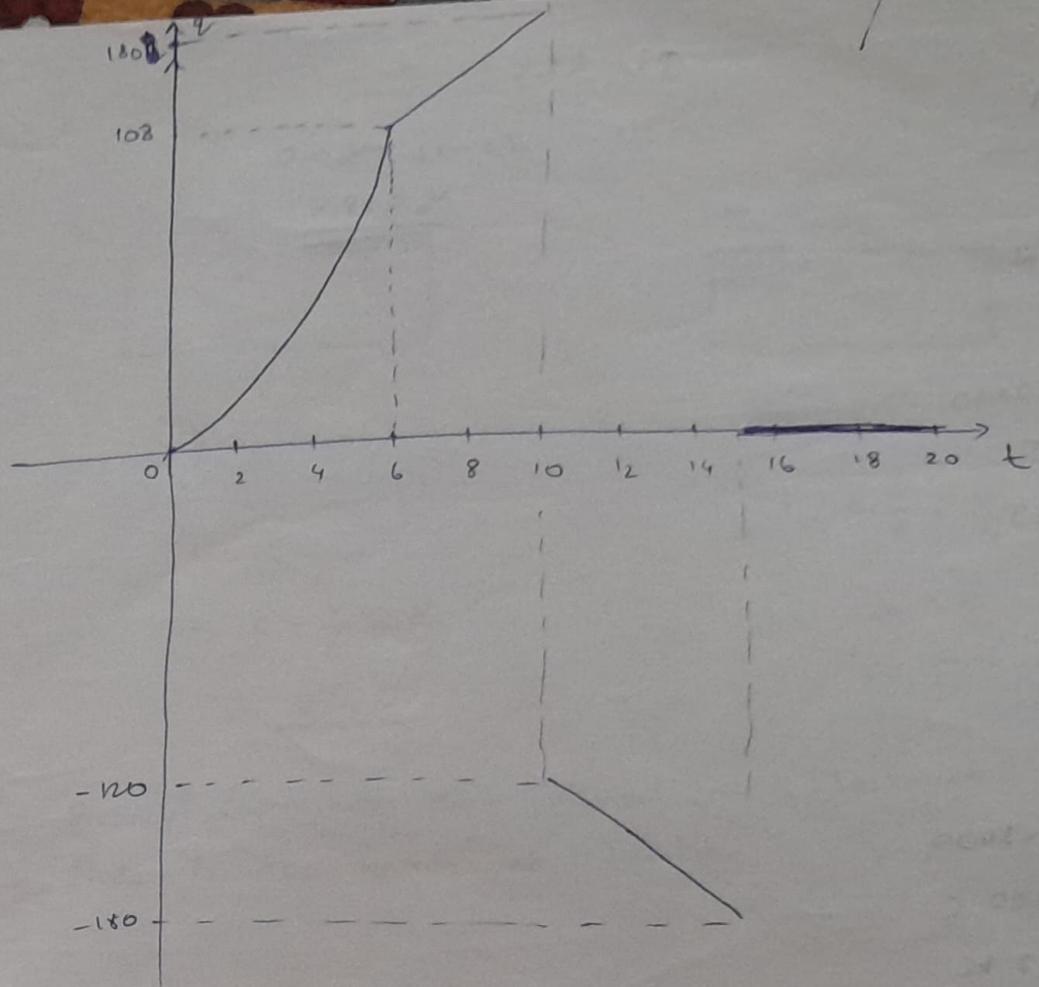
$$q(t) = \begin{cases} 3t^2, & 0 \leq t < 6 \\ 18t, & 6 \leq t < 10 \\ -12t, & 10 \leq t < 15 \\ 0, & t \geq 15 \end{cases}$$



Q6)

(a)

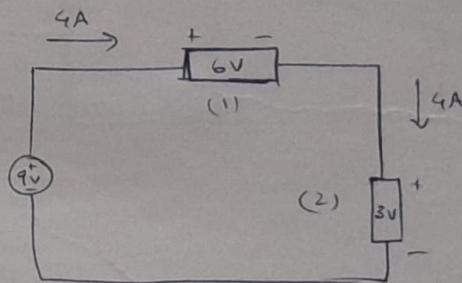


$$P = iV$$

$$(1) \rightarrow P = 4 \times 6 = 24 \text{ W}$$

$$(2) \rightarrow P = 4 \times 3 = 12 \text{ W}$$

(b)

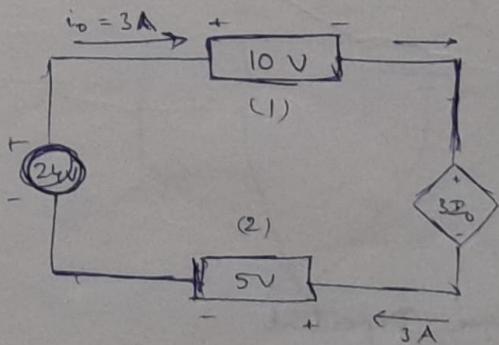

$$P = iV$$

$$(1) P = 3 \times 10 = 30 \text{ V}$$

$$(2) P = 3 \times 5 = 15 \text{ V}$$

Q8) $V = 12 \text{ V}$

$$i = 150 \times 10^{-3} \text{ A}$$

(a) $P = iV$

$$= 1.8 \text{ W}$$

(b) $E = Pt$

$$= 1.8 \times 20 \times 60$$

$$= 2160 \text{ J}$$

$$= 2.16 \text{ kJ}$$

Q9) $i = 3 \text{ A}$

$t = 4 \text{ hr}$

(a) $q = it$

$$\Rightarrow q = 3 \times 4 \times 3600$$

$$= 43200 \text{ C}$$

$$= 43.2 \text{ kC}$$

~~ANSWER~~

28/8/23

CHAPTER - 2

→ Ohm's Law

→ Kirchoff's Law

→ Network ~~and~~ Topology

→ Series and Parallel Connections

~~CHAPTER - 2~~

→ Ohm's Law :

$$V = RI$$


Resistance : Temperature Dependent

Resistor

Linear
Resistor

Non-Linear
Resistor
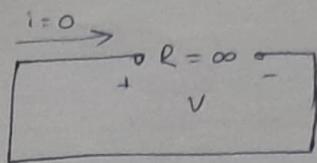
$$P_R = I^2 R \longrightarrow \text{Ohmic Loss}$$




(Open Circuit)

$$V = iR$$

$$\Rightarrow R = \frac{V}{i} = \frac{V}{0}$$

$$\underline{R \rightarrow \infty}$$

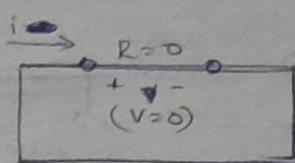


(Short Circuit)

$$i_{sc} = \frac{V}{R} = \frac{V}{0}$$


$$i_{sc} \propto V$$

$$i_{sc} \rightarrow \infty$$

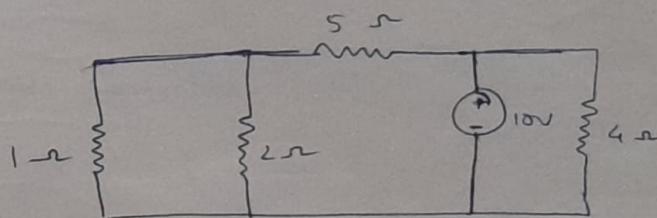Branch Represents each element in Electrical Circuit.
Node is also known as Junction.



III

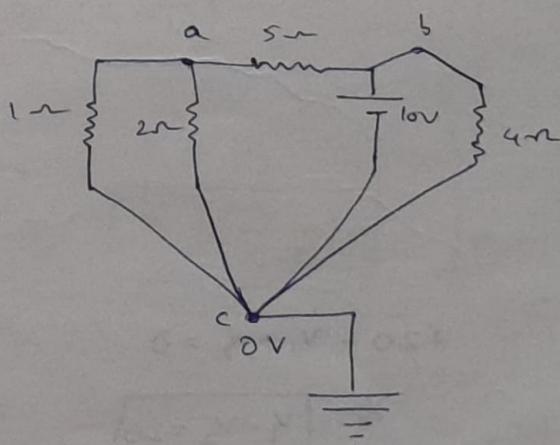

3 nodes

no. of branches = 6

no. of nodes = 3

no. of 2 independent loops = 2

$$b = l + n - 1$$


$$l = 3$$

$$n = 3$$


$$b = 5$$

$$b = 3 + 3 - 1 = 5$$

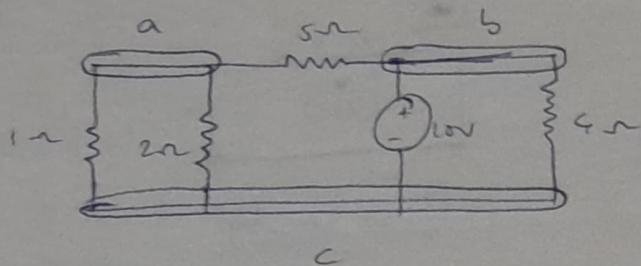Ground \rightarrow Common Node / Reference Node



Q)

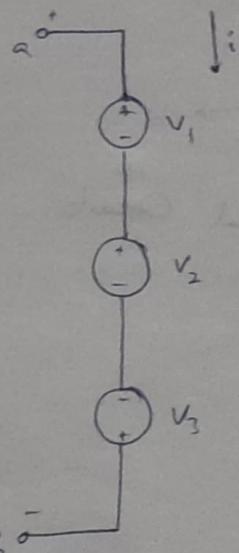


$$V_a - V_1 - V_2 + V_3 = V_b$$

$$V_a - V_b = V_1 + V_2 - V_3$$


$$\boxed{V_{ab} = V_1 + V_2 - V_3}$$

Q)

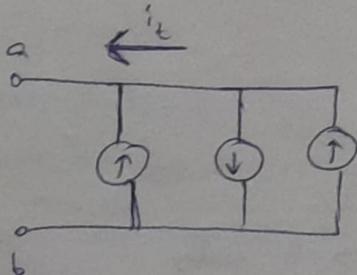

$$i_t = i_1 - i_2 + i_3$$

Q) Find V_1 and V_2 using KVL

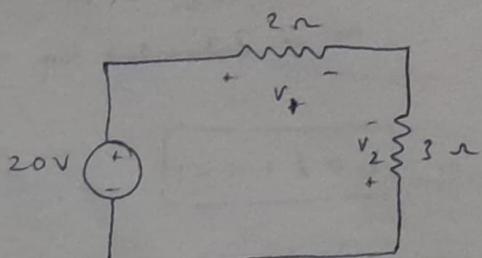


$$+20 - V_1 + V_2 = 0$$

$$\Rightarrow \boxed{V_1 - V_2 = 20}$$

$$\begin{aligned} V_1 &= 2i \\ V_2 &= 3i \end{aligned} \quad \left\{ \Rightarrow \boxed{i = 20 \text{ A}} \right. \text{ ACW}$$
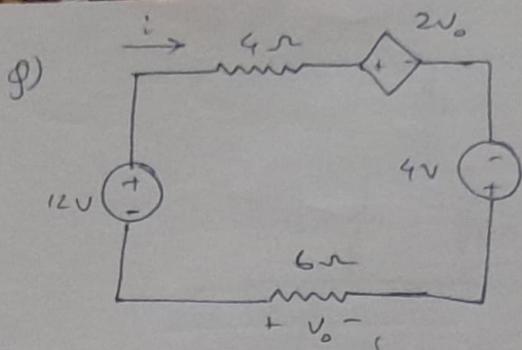
$$\begin{aligned} V_1 &= 40 \text{ V} \\ V_2 &= 60 \text{ V} \end{aligned}$$



$$-4i - 2V_o + 4 + 6i + 12 = 0$$

$$6i = V_o$$

$$\Rightarrow 2i - 2V_o + 16 = 0$$

$$\Rightarrow 2i - 12i + 16 = 0$$

$$\Rightarrow 10i = 16$$

$$i = 1.6 \Rightarrow V_o = 9.6 \text{ V}$$

30/8/25:

→ Series Connection :


$$V = V_1 + V_2$$

$$V_1 = iR_1$$

$$V_2 = iR_2$$

$$R_{\text{eq.}} = R_1 + R_2$$

$$[V = i(R_1 + R_2)]$$

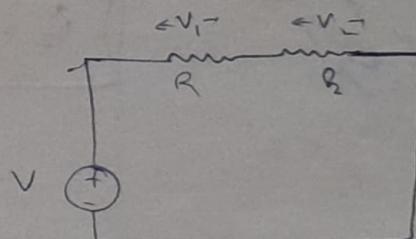


$$V_1 = iR_1$$

$$V_1 = \left(\frac{V}{R_1 + R_2} \right) R_1$$

$$V_2 = iR_2$$

$$V_2 = \left(\frac{V}{R_1 + R_2} \right) R_2$$

Parallel Connection

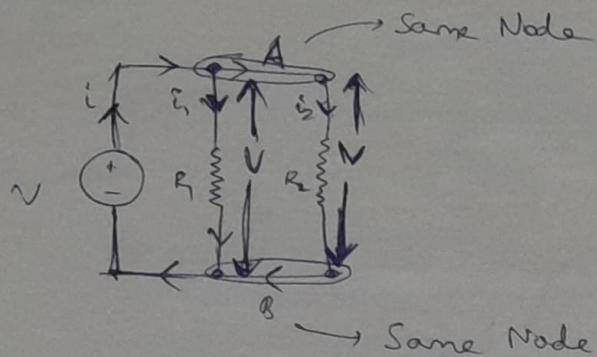

$$\boxed{i = i_1 + i_2}$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow \boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}}$$

~~R_{eq}~~

$$\boxed{R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2}}$$

~~$$i_1 = \frac{V}{R_1}$$

$$i_2 = V \left(\frac{1}{R_1} - \frac{1}{R_2} \right)$$~~


$$\boxed{i_1 = i \left(\frac{R_2}{R_1 + R_2} \right)}$$

$$\boxed{i_2 = i \left(\frac{R_1}{R_1 + R_2} \right)}$$

$\frac{1}{R_{eq}}$

$\frac{1}{R_{eq}}$


Q)

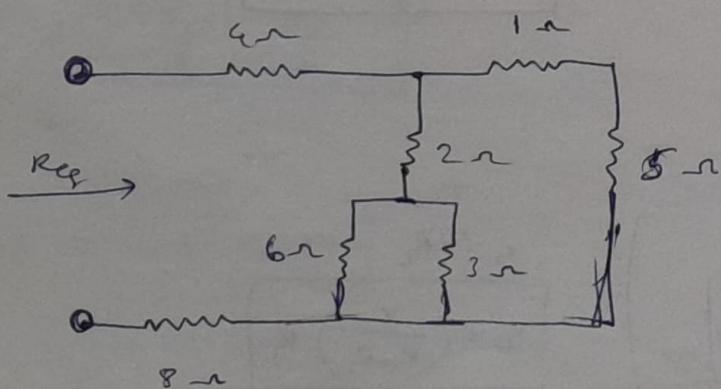

find R_{eq} .

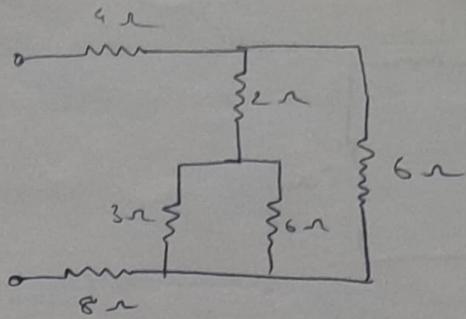
A) Starts with Extreme Right side

1 ohm series with 5 ohm
 $\Rightarrow 6 \text{ ohm}$




3 ohm parallel with 6 ohm

$$\Rightarrow 2 \text{ ohm}$$

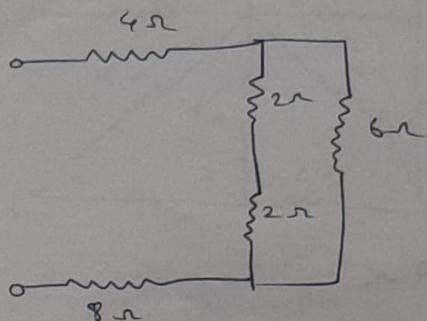


2 ohm series with 2 ohm

$$\Rightarrow 4 \text{ ohm}$$

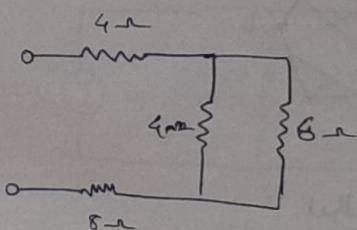

4 ohm parallel with 6 ohm


$$\Rightarrow 12/5 \text{ ohm}$$

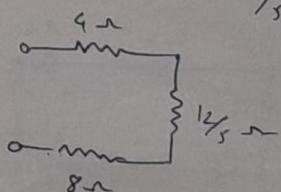

4 ohm, 8 ohm and $12/5$ ohm in series


~~$$= 14.4 \text{ ohm}$$~~

$$\Rightarrow 14.4 \text{ ohm}$$

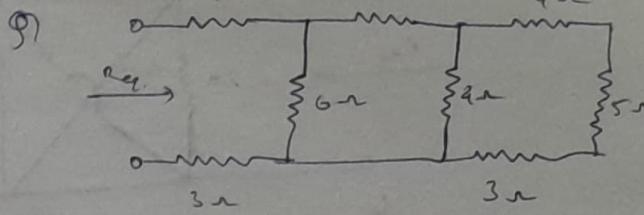

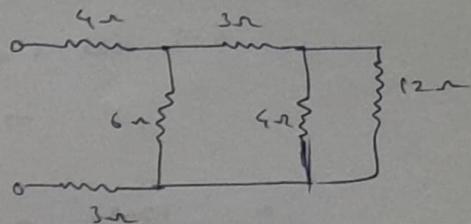9)

4 ohm, 5 ohm, 3 ohm in Series
 $\Rightarrow 12 \text{ ohm}$



4 ohm and 12 ohm in parallel

$$\Rightarrow 3 \text{ ohm}$$

3 ohm and 3 ohm in Series


$$\Rightarrow 6 \text{ ohm}$$

6 ohm and 6 ohm in parallel

$$\Rightarrow 3 \text{ ohm}$$

4 ohm, 3 ohm, 3 ohm in Series


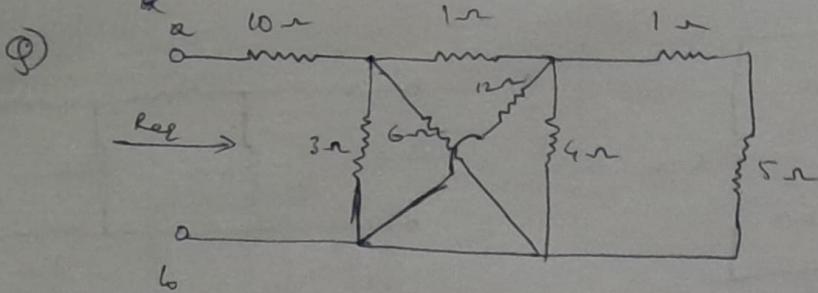
$$\Rightarrow \underline{10 \text{ ohm}}$$




$$\frac{2}{12} + \frac{3}{12}$$

1 ohm and $5\text{ ohm} \rightarrow$ series
 $\Rightarrow 6\text{ ohm}$

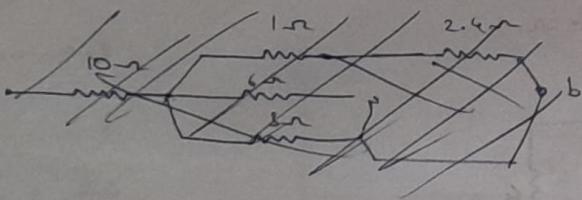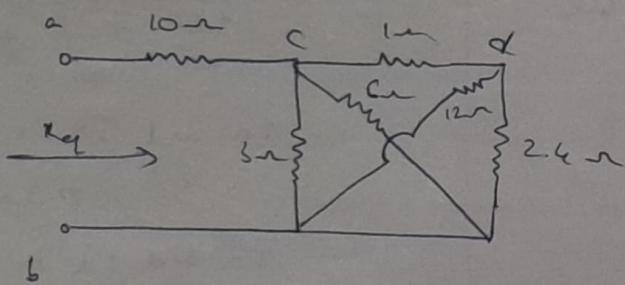6 ohm and $4\text{ ohm} \rightarrow$ parallel
 $\Rightarrow 2.4\text{ ohm}$



12 ohm and 2.4 ohm in parallel

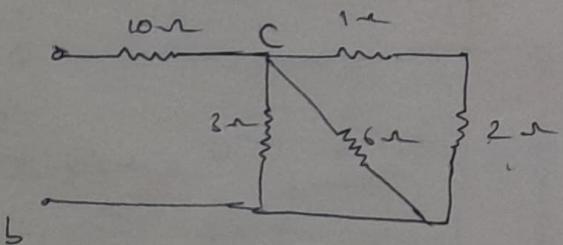

~~$$\frac{5}{12} + \frac{1}{12} = 2$$~~

1 ohm and 2 ohm series $\Rightarrow 3\text{ ohm}$


$3\text{ ohm}, 3\text{ ohm}, 6\text{ ohm} \rightarrow$ parallel
 $\Rightarrow 1.2$

Note: If the given Problem is relevant to Conductance 'g', The following Assumptions are made.


$$(i) \text{ Series} : \frac{1}{g_{\text{eq}}} = \frac{1}{g_1} + \frac{1}{g_2}$$

$$(ii) \text{ Parallel} : g_{\text{eq}} = g_1 + g_2$$

(Q3)

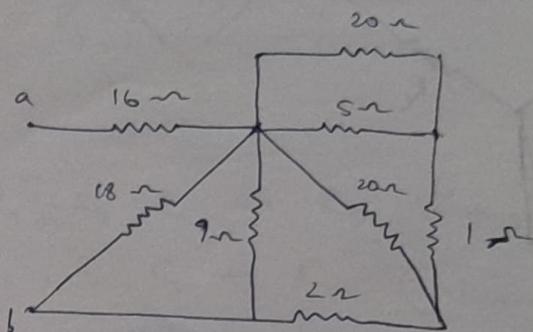

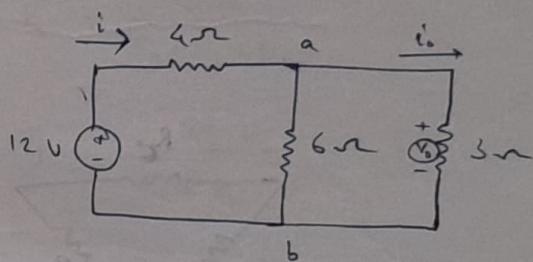Q) Find i_o and V_o . Calculate Power Dissipated in the 3Ω Resistor




$$R_{\text{eff}} = 6$$

$$i = \frac{12}{6} = 2 \text{ A}$$

$$\frac{i}{2} = \frac{4}{8+3} = \frac{4}{11}$$
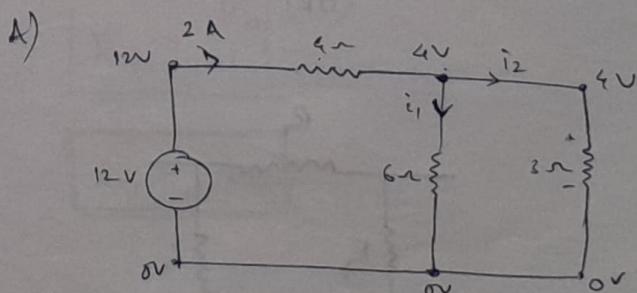
$$\frac{i}{2} = \frac{4}{8+3} = \frac{4}{11}$$



$$i_1 = i \left(\frac{R_2}{R_1 + R_2} \right)$$

$$= 2 \times \frac{3}{9}$$

$$i_1 = \frac{6}{9} = \frac{2}{3}$$

$$i_2 = \frac{4}{3}$$


$$i_2 = i_0 = 1.33 \text{ A}$$

$$V_o = 4 \text{ V}$$

$$P = i^2 R = \left(\frac{4}{3} \right)^2 \times 3 = \frac{16}{9}$$

$$P = 5.33 \text{ W}$$


→ Wye - Delta Transformations

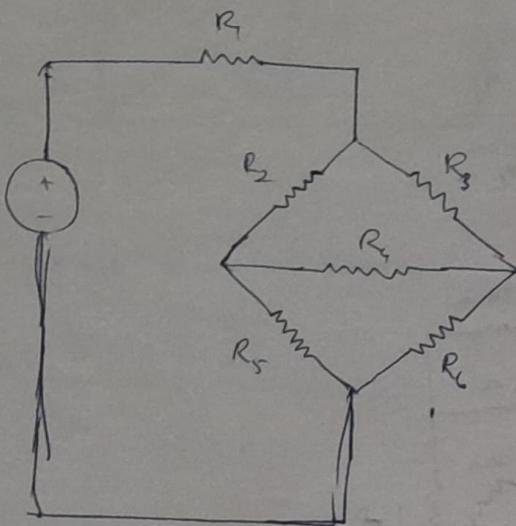


Δ - T - Star

∇ - Mesh - Π


~~Representation:~~ Representation:

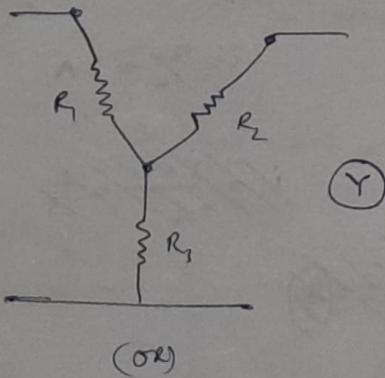


(Y)

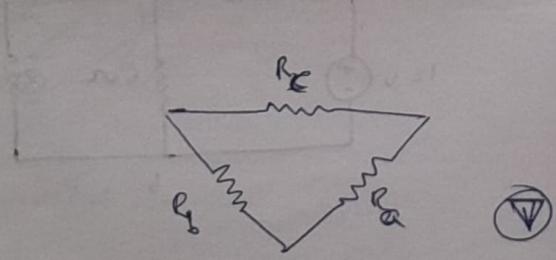

(Δ)

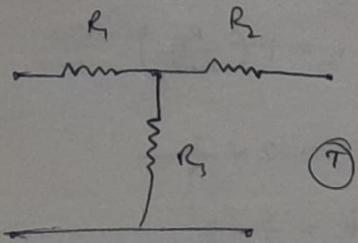


(T)

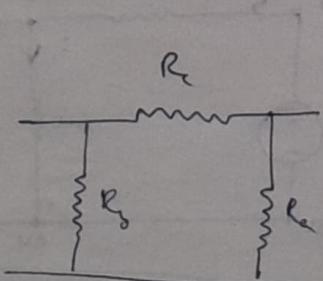

Conversion :

① ∇ to γ conversion

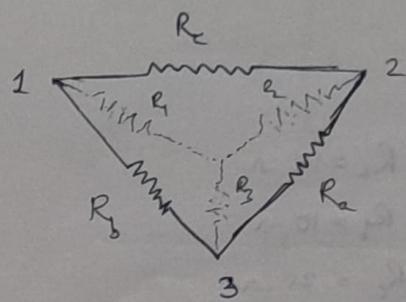

$$R_a, R_b, R_c \rightarrow R_\nabla \text{ (Known)}$$

$$R_1, R_2, R_3 \rightarrow R_\gamma \text{ (Unknown)}$$

$$R_1 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

If $R_1 = R_2 = R_3 = R_\gamma$


$$R_a = R_b = R_c = R_\nabla$$

$$R_\gamma = \frac{R_\nabla}{3}$$

$$R_\nabla = 3R_\gamma$$

Proof : HW

② γ to ∇ conversion

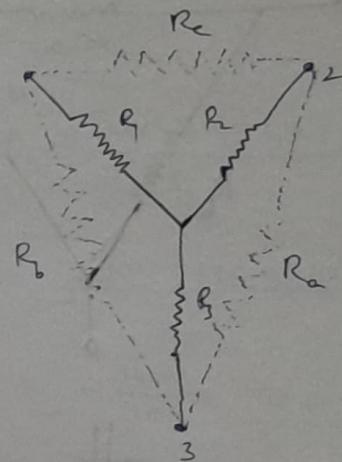

$$R_1, R_2, R_3 \rightarrow R_\gamma \text{ (Known)}$$

$$R_a, R_b, R_c \rightarrow R_\nabla \text{ (Unknown)}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

If


$$R_a = R_b = R_c = R_\nabla$$

$$R_1 = R_2 = R_3 = R_\gamma$$

$$R_\nabla = 3R_\gamma$$

$$R_\gamma = \frac{R_\nabla}{3}$$


Q) Convert Δ to γ

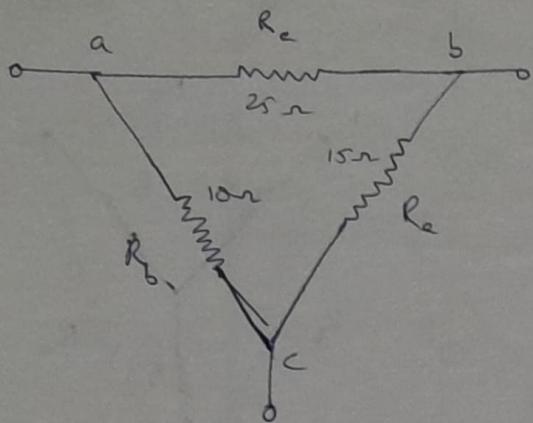

$$R_a = 15 \text{ ohms}$$

$$R_b = 10 \text{ ohms}$$

$$R_c = 25 \text{ ohms}$$

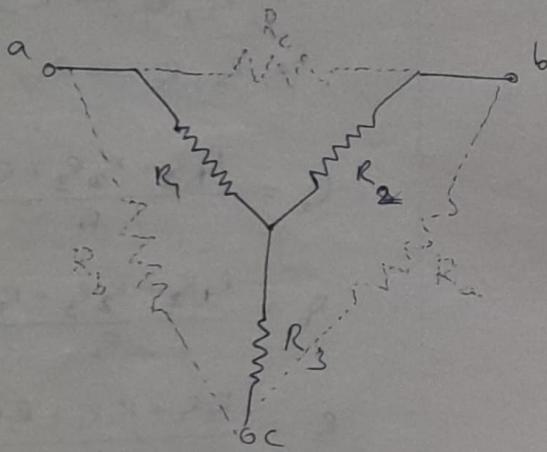

$$R_1 = \frac{R_b \cdot R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a \cdot R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$

$$R_1 = \frac{25 \times 10}{50} = 5 \text{ ohms}$$

$$R_2 = \frac{25 \times 15}{50} = \frac{7}{2} \text{ ohms}$$

$$R_3 = \frac{10 \times 15}{50} = 3 \text{ ohms}$$

g) Transform Δ to ∇

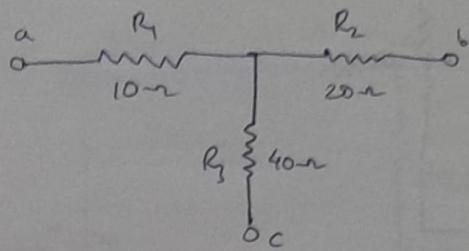

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$= \frac{400 + 800 + 200}{10}$$

$$\Rightarrow \frac{1400}{10} = 140 \text{ ohms}$$



~~RE~~

$$R_b = \frac{1400}{20} = 70 \text{ ohms}$$
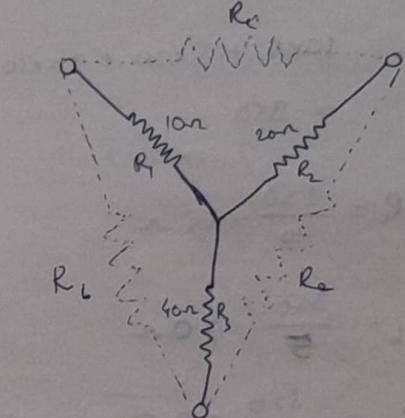
$$R_c = \frac{1400}{40} = 35 \text{ ohms}$$




g)

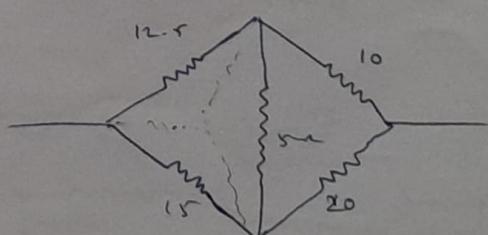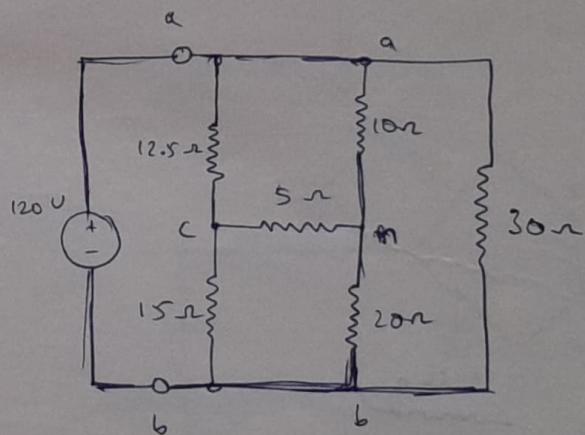


$$\frac{12.5 \times 5}{42.5}$$

$$\frac{12.5 \times 15}{42.5}$$

$$\frac{15 \times 5}{42.5}$$

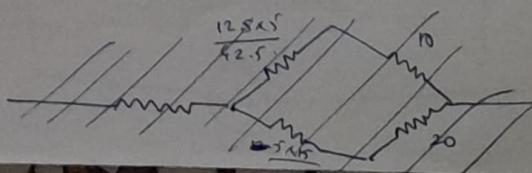

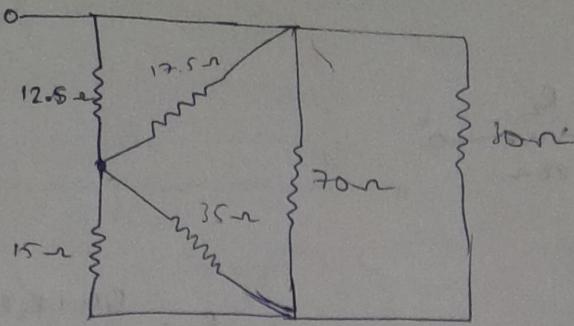

Elements a, b, c are in star



$$10 \times 5 + 5 \times 20 + 20 \times 10 \\ = 350$$

(OR)


$$R_c = \frac{350}{10} = 35 \text{ ohms}$$

$$R_b = \frac{350}{5} = 70 \text{ ohms}$$

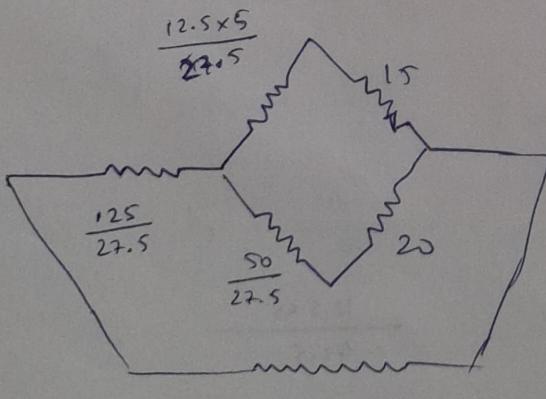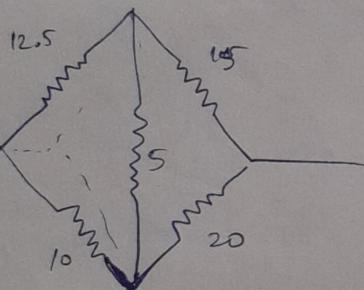
$$R_a = \frac{350}{20} = 17.5 \text{ ohms}$$




30V

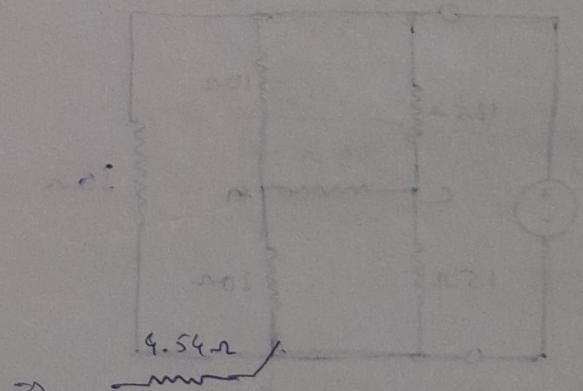



\Rightarrow

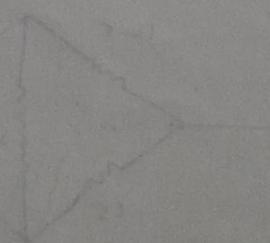

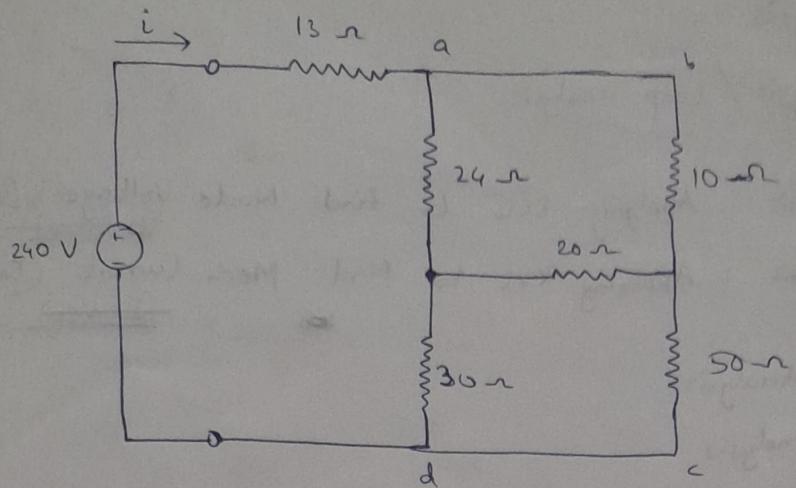Q) For the given network in Figure, find R_{ab} and i



$abcd \rightarrow \Delta$

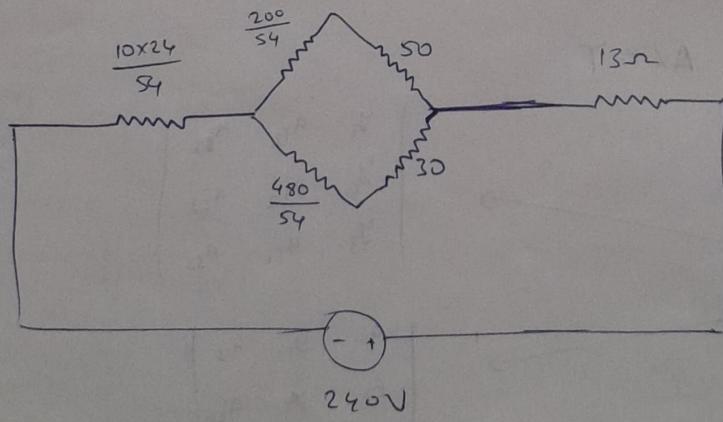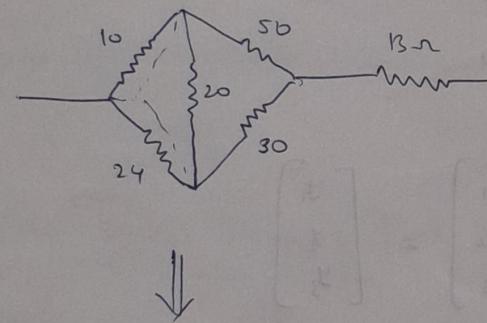

$$\frac{100}{27} + 50$$


$$50 \left(1 + \frac{8}{27}\right)$$

$$\frac{50 \times 29}{27}$$

$$\frac{240}{27} + 30$$

$$30 \left(1 + \frac{9}{27}\right)$$

$$\frac{30 \times 35}{27}$$

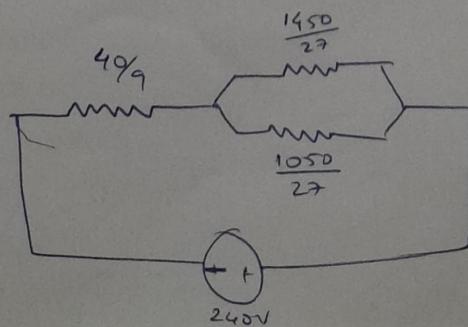

4/9/23

Chapter : 3 : Methods of Analysis

(1) Nodal Analysis

(2) Mesh Analysis / Loop analysis

Nodal Analysis : Applying KCL to find Node Voltages ($[V] \cdot [q] = [I]$)
~~(P = V)~~

Mesh Analysis : Applying KVL to find Mesh Current ($[R] \cdot [I] = [V]$)
~~(P = V)~~

(3) Super Node Analysis

(4) Super Mesh Analysis

Cramer's Rule :

$$a_{11}x_1 + a_{12}x_2 + a_{13}x_3 = y_1$$

$$a_{21}x_1 + a_{22}x_2 + a_{23}x_3 = y_2$$

$$a_{31}x_1 + a_{32}x_2 + a_{33}x_3 = y_3$$

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} y_1 \\ y_2 \\ y_3 \end{bmatrix}$$

$$AX = Y$$

$$|A_1|$$

$$|A_1|$$

$$|A_2|$$

$$|A_2|$$

$$\begin{vmatrix} y_1 & a_{12} & a_{13} \\ y_2 & a_{22} & a_{23} \\ y_3 & a_{32} & a_{33} \end{vmatrix}$$

$$\begin{vmatrix} a_{11} & y_1 & a_{13} \\ a_{21} & y_2 & a_{23} \\ a_{31} & y_3 & a_{33} \end{vmatrix}$$

$$x_1 = \frac{|A_1|}{|A|}$$

$$x_2 = \frac{|A_2|}{|A|}$$

$$x_3 = \frac{|A_3|}{|A|}$$


$$A \cdot X = Y$$

$$R \cdot I = V$$

$$I = V \left(\frac{1}{R} \right)$$

$$I = V \cdot G$$

\rightarrow Mesh Current Analysis :

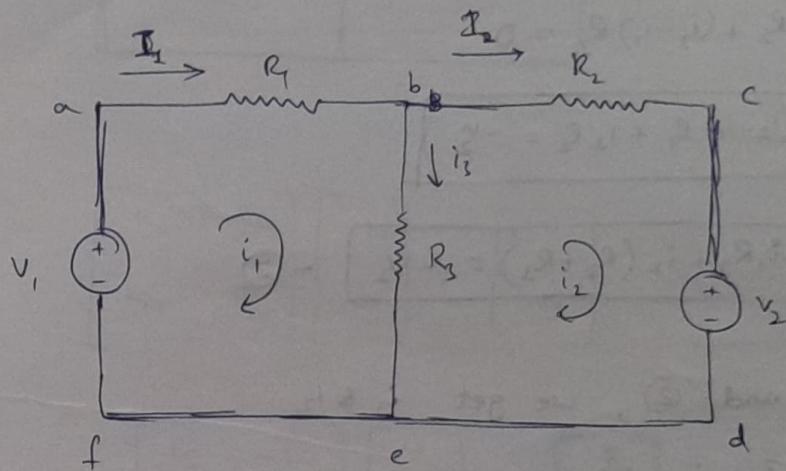


I_1, I_2 : Branch currents

i_1, i_2 : Loop currents

In the given Circuit, find i_1 and i_2 .

Mess Analysis using KVL

Loop - I Apply KVL :

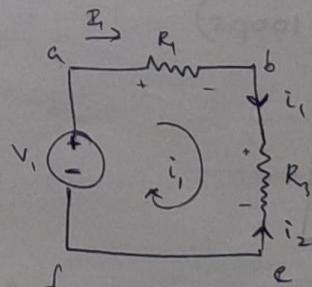

$i_1 > i_2$ (Because loop of i_1)

$$V_1 - i_1 R_1 - (i_1 - i_2) R_3 = 0$$

~~∴ $i_1 = i_2 + (i_1 - i_2) R_3 / R_1$~~


$$\Rightarrow V_1 = i_1 R_1 + (i_1 - i_2) R_3$$

$$V_1 = i_1 R_1 + i_1 R_3 - i_2 R_3$$

$$V_1 = i_1 (R_1 + R_3) - i_2 R_3$$

- ①

Loop - 2: Apply KVL:

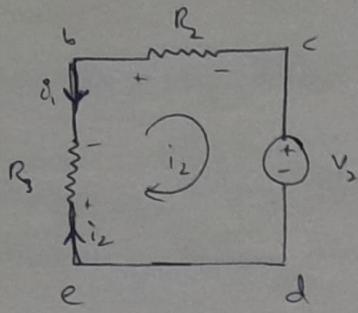

$i_2 > i_1$ (Because of loop)

$$V_2 + i_2 R_2 + (i_2 - i_1) R_1 = 0 \quad \text{--- (1)}$$

$$\Rightarrow [(i_2 - i_1) R_1 + i_2 R_2] = -V_2$$

$$\Rightarrow [-i_1 R_1 + i_2 (R_2 + R_1)] = -V_2 \quad \text{--- (2)}$$

Solving (1) and (2), we get i_1 & i_2

$$I_1 = i_1$$

$$I_2 = i_2$$

$$I_3 = (i_1 - i_2)$$

Cramer Rule:

$$[R] \cdot [I] = [v]$$

Size $\Rightarrow 2 \times 2$ (2 loops)

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$\begin{bmatrix} R_{11} + R_3 & -R_3 \\ -R_3 & R_{22} + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} +V_1 \\ -V_2 \end{bmatrix}$$

$R_{11} \rightarrow$ Resistance in 1st loop

$R_{12} \rightarrow$ Resistance b/w 1st and 2nd loops

$R_{22} \rightarrow$ Resistance in 2nd loop

Q) Find I_1 , I_2 and I_3

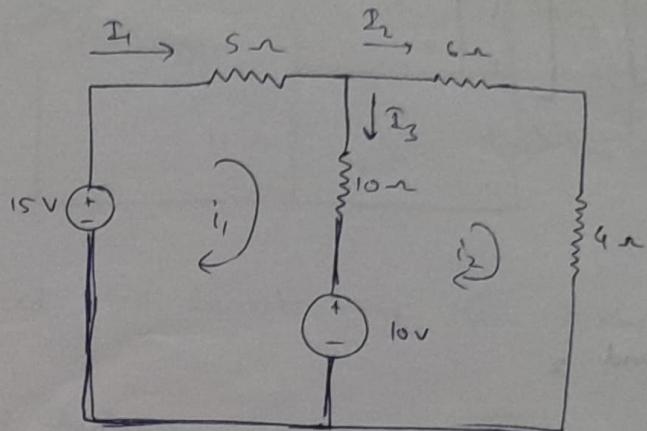

M-II

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 15 & -10 \\ -10 & 20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

M-I

From Loop - I :

$$15 - 5i_1 - 10(i_1 - i_2) - 10 = 0 \Rightarrow -15i_1 + 10i_2 + 5 = 0$$

$$\Rightarrow 15i_1 - 10i_2 = 5 \quad \text{--- (1)}$$

From Loop - II :

$$-6i_2 - 4i_2 + 10 - 10(i_2 - i_1) = 0 \Rightarrow 10i_1 - 20i_2 + 10 = 0$$

$$\Rightarrow 20i_2 - 10i_1 = 10 \quad \text{--- (2)}$$

$$30i_1 - 20i_2 = 10$$

$$-10i_1 + 20i_2 = 10$$

$$\boxed{i_1 = 1A} \Rightarrow \boxed{i_2 = 1A}$$

$$i_3 = i_1 - i_2 = 0A$$


(OR)

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$\Rightarrow i_1 = 1 \text{ A}$$

$$i_2 = 1 \text{ A}$$

Q) Find Mesh Currents i_1 and i_2

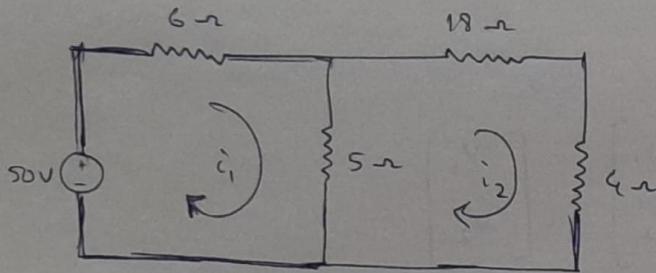

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 11 & -5 \\ -5 & 27 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$

$$\Rightarrow \boxed{11i_1 - 5i_2 = 50}$$

$$-5i_1 + 27i_2 = 0 \Rightarrow \boxed{27i_2 = 5i_1}$$

(OR) :

$$\text{Loop I : } 50 - 6i_1 - 5(i_1 - i_2) = 0$$

$$\Rightarrow \boxed{50 = 11i_1 - 5i_2}$$


$$\text{Loop II : } -18i_2 - 4i_2 - 5(i_2 - i_1) = 0$$

$$\Rightarrow \boxed{5i_1 = 27i_2}$$

$$\begin{array}{l} i_2 = 0.9025 \\ i_1 = 4.8735 \end{array}$$

$$\boxed{\begin{array}{l} i_1 = 4.8735 \\ i_2 = 0.9025 \end{array}}$$

Q)

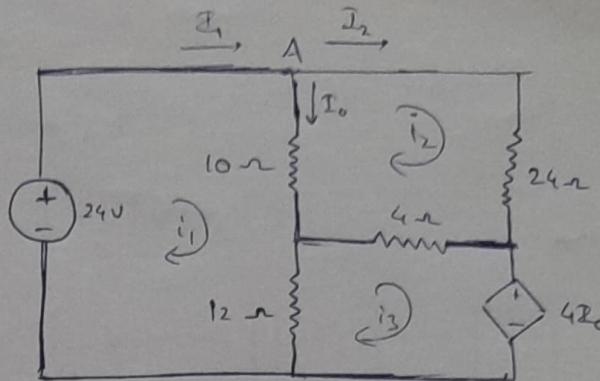

Find Mesh Currents using Mesh Analysis

→ Nodal Analysis:

Assumption:


Actual Node
• a (+)


Reference Node (0V)
• b (-)



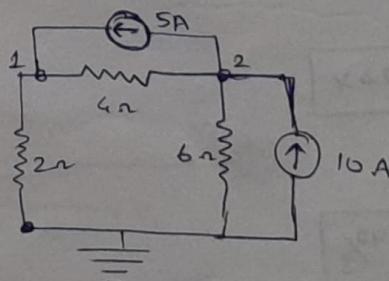
- (i) Write the equations for "n-1" nodes.
- (ii) i → Always flows from higher Potential to lower Potential
- (iii) Apply KCL for each Node to obtain branch currents
in terms of Node voltages using Ohm's Law.
- (iv) Find Node Voltage by solving Simultaneous equations.

Q) Find Node Voltages at 1 and 2. for the given Circuit.



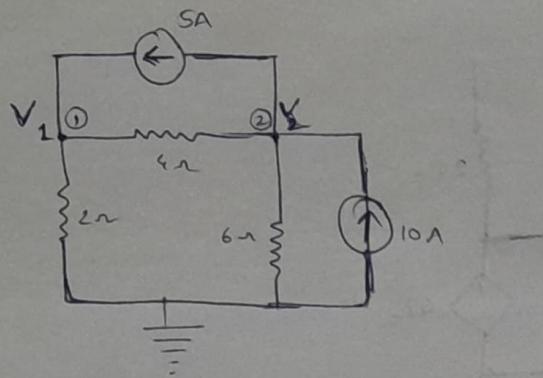

Step-I:

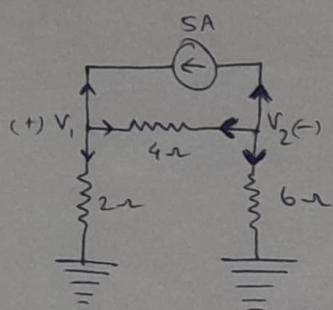

KCL at V_1 Node


$$\frac{V_1}{2} + \frac{V_1 - V_2}{4} - 5 = 0$$

$$\Rightarrow 2V_1 + V_1 - V_2 - 20 = 0$$

$$\Rightarrow \boxed{3V_1 - V_2 = 20} \quad -\textcircled{1}$$

KCL at Node V_2 :
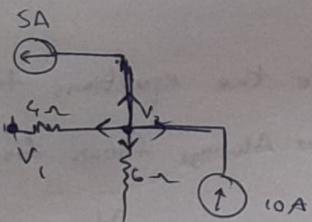
$$\frac{V_2}{6} + 5 - 10 + \frac{V_2 - V_1}{4} = 0$$



$$\Rightarrow \frac{V_2}{6} + \frac{V_2 - V_1}{4} + 5 = 10$$

$$\Rightarrow \frac{V_2}{6} + \frac{V_2 - V_1}{4} = 5$$

$$\Rightarrow 2V_2 + 3V_2 - 3V_1 = 60$$

$$\Rightarrow \boxed{-3V_1 + 5V_2 = 60} \quad -\textcircled{2}$$

$\textcircled{1} + \textcircled{2}$,

$$4V_2 = 80 \Rightarrow \boxed{V_2 = 20 \text{ V}}$$

$$3V_1 = 40$$

$$\Rightarrow \boxed{V_1 = \frac{40}{3}}$$

(OR)

Cramer's Rule :

$$[G] \cdot [V] = [I]$$

$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

$$|G| = 12$$

$$V_1 = \frac{\nabla v_1}{\nabla}$$

$$\nabla v_1 = \begin{bmatrix} 20 & -1 \\ 60 & 5 \end{bmatrix}$$

$$V_2 = \frac{\nabla v_2}{\nabla}$$

$$|\nabla v_1| = 160$$



$$\Rightarrow V_1 = \frac{160}{12} = 13.33 \text{ V}$$

$$\nabla v_2 = \begin{bmatrix} 3 & 20 \\ -3 & 60 \end{bmatrix}$$

$$V_2 = \frac{240}{12} = 20 \text{ V}$$

$$|\nabla v_2| = 240$$

Q) Obtain Node Voltages

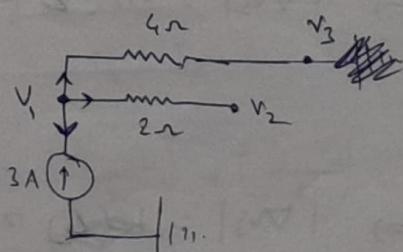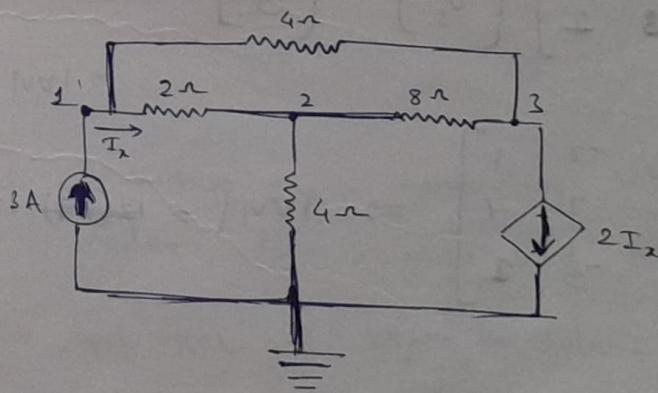


KCL for Node 1

$$\frac{V_1 - V_2}{4} + \frac{V_1 - V_2}{2} - 3 = 0$$

$$\Rightarrow V_1 + 2V_1 - 2V_2 - 12 = 0 - V_3$$

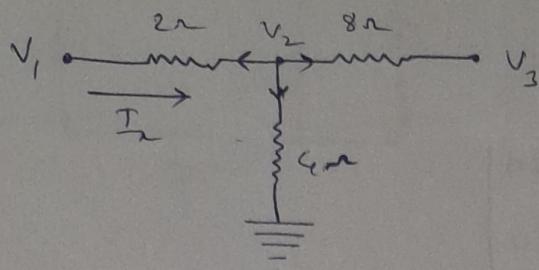
$$\Rightarrow 3V_1 - 2V_2 = 12 - V_3 \quad \text{---(1)}$$



$$\frac{v_2}{4} + \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{8} = 0$$

$$\Rightarrow 2v_2 + 4v_2 - 4v_1 + v_2 - v_3 = 0$$
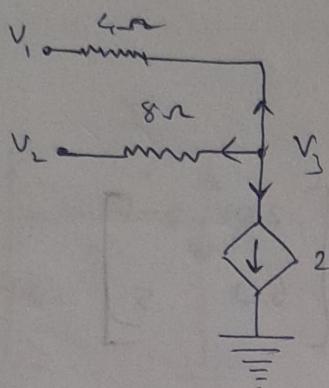
$$\Rightarrow \boxed{-4v_1 + 7v_2 - v_3 = 0}$$



$$\frac{v_3 - v_1}{4} + \frac{v_3 - v_2}{8} + 2I_x = 0$$

$$2v_3 - 2v_1 + v_3 - v_2 + 2v_1 - 8v_2 = 0$$

$$\Rightarrow \boxed{6v_1 - 8v_2 + 3v_3 = 0}$$

$$\Rightarrow \boxed{2v_1 - 3v_2 + v_3 = 0}$$

$$\boxed{I_x = \frac{v_1 - v_2}{2}}$$

$$\begin{bmatrix} 3 & -2 & 1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \Rightarrow |\nabla v| = 12(3)(4) + 2(-2) + 0$$

$$|\nabla v| = 48$$

$$\nabla v_1 = \begin{bmatrix} 12 & -2 & 1 \\ 0 & 7 & -1 \\ 0 & -3 & 1 \end{bmatrix} \Rightarrow |\nabla v_1| = 12(-2) 12 \times 4 = 48$$

$$\nabla v_2 = \begin{bmatrix} 3 & -2 & 1 \\ -4 & 0 & -1 \\ 2 & 0 & 1 \end{bmatrix} \Rightarrow |\nabla v_2| = -12(-2) = 24$$

$$\nabla v_3 = \begin{bmatrix} 3 & -2 & 12 \\ -4 & 7 & 0 \\ 2 & -3 & 0 \end{bmatrix} \Rightarrow |\nabla v_3| = 12(-2) = -24$$


$$V_1 = \frac{48}{10} = 4.8V$$

$$V_2 = \frac{24}{10} = 2.4V$$

$$V_3 = \frac{-24}{10} = -2.4V$$

8/9/23

→ Supernode:

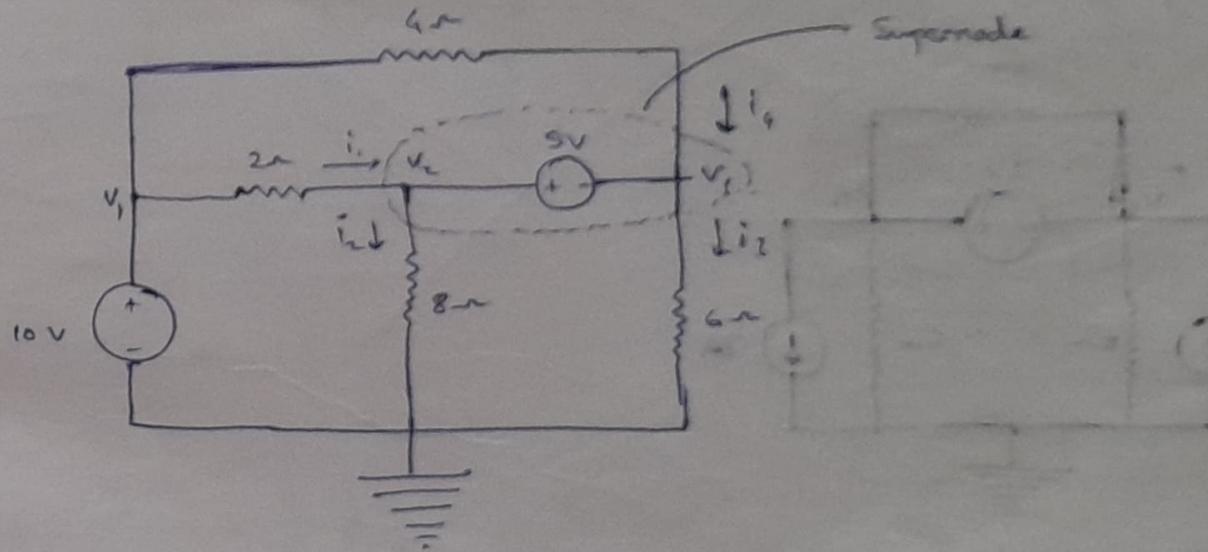

If a Voltage source connecting between 2 non-referencing nodes, form a generalised node (or) Supernode.

We apply KCL and KVLR to determine the node voltages.

Apply KCL:


$$i_1 + i_4 = i_2 + i_3$$

$$\Rightarrow \left(\frac{V_1 - V_2}{2} \right) + \left(\frac{V_1 - V_3}{4} \right) = \frac{V_2}{8} + \frac{V_3}{6}$$

$$\Rightarrow 12V_1 - 12V_2 + 6V_1 - 6V_3 = 3V_2 + 4V_3$$

$$\Rightarrow 18V_1 - 15V_2 - 10V_3 = 0 \quad \text{---(1)}$$

Apply KVL for supernode :

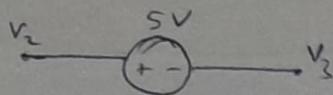



~~Supernode~~

$$-V_2 + 5 + V_3 = 0$$

$$\Rightarrow V_2 - V_3 = 5 \quad \text{---(2)}$$

A supernode has no voltage of its own.

(Q)

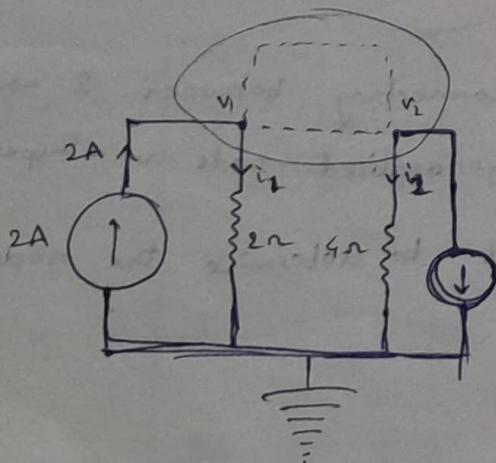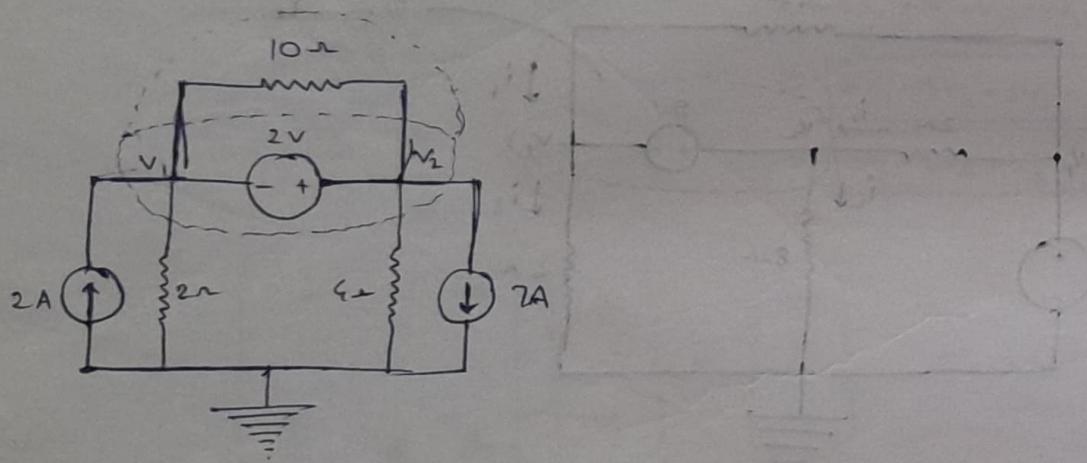

$$2 = i_1 + i_2 + 7$$

$$\Rightarrow 2 = \frac{V_1}{2} + \frac{V_2}{4} + 7$$

$$\Rightarrow \boxed{2V_1 + V_2 = -20} \quad \text{---(1)}$$

$$V_2 = 2 - \frac{2V_1}{3}$$



$$\boxed{V_2 = -\frac{16}{3}}$$

$$\boxed{V_1 + 2 = V_2} \quad \text{---(2)}$$

$$\Rightarrow \cancel{2V_1} \Rightarrow 3V_1 = -22$$

$$\Rightarrow \boxed{V_1 = -22/3}$$

(8)

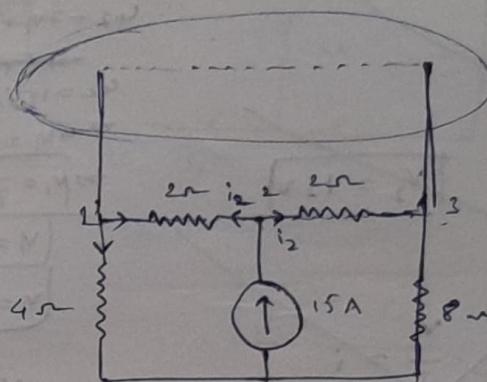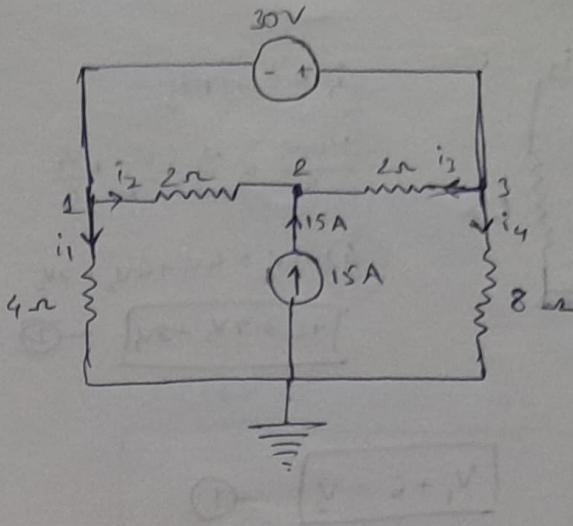

$$i_2 + i_3 = 15$$

$$\Rightarrow \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{2} = 15$$

~~$$v_2 - v_1 = 30$$~~

$$v_1 + 30 = v_3 \quad \text{---(2)}$$

$$\Rightarrow [2v_2 - v_1 - v_3 = 30] \quad \text{---(1)}$$

$$\Downarrow 2v_2 - 2v_1 - 30 = 30$$

$$\Rightarrow v_2 - v_1 = 30 \quad \text{---(3)}$$

from (2) and (3),

$$v_2 = v_3$$

$$i_2 = i_1 + i_3 + i_4$$

$$15 = \frac{v_2 - v_1}{2} + \frac{v_1}{4} + \frac{v_2}{8} + \frac{v_2 - v_3}{2}$$

$$= \frac{4v_2 - 4v_1 - 2v_1 + v_3 + 4v_2 - 4v_3}{8}$$

$$= \frac{-6v_1 + 8v_2 - 8v_3}{8}$$

$$\Rightarrow -6v_1 + 8v_2 - 8v_3 = 120$$

$$\Rightarrow [-6v_1 + 5v_2 = 120] \quad \text{---(4)} \quad [v_2 = v_3]$$

~~$$2v_2 - 2v_1 - 30 = 30$$~~

$$v_1 = 30$$

&


$$v_2 = 60 \text{ V}$$

$$v_3 = 60 \text{ V}$$

from (3), (4)



~~v_1 = 30~~ & ~~v_2 = 60~~

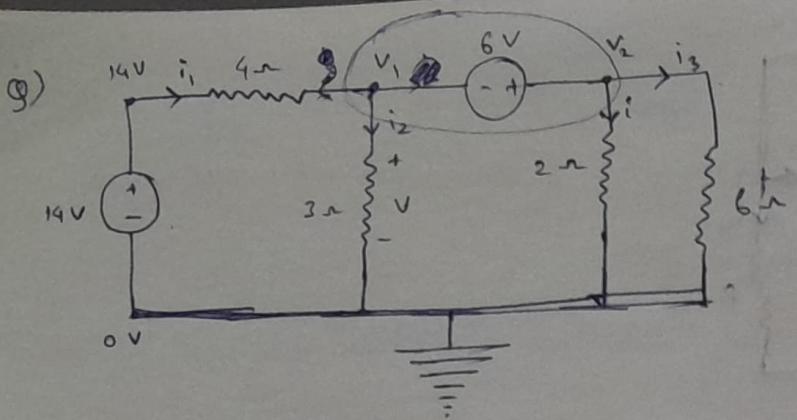

$$i_1 = i_2 + i_3$$

$$\frac{14 - V_1}{4} = \frac{V_1}{3} + \frac{V_2}{2} + \frac{V_2}{6}$$

$$42 - 3V_1 = 4V_1 + 6V_2 + 2V_2$$

$$742 = 7V_1 + 8V_2 \quad \text{--- (2)}$$

$$V_1 + 6 = V_2 \quad \text{--- (1)}$$

$$i_1 = i_2$$

$$\Rightarrow \frac{14 - V_1}{4} = \frac{V_1}{3}$$

$$\Rightarrow 42 - 3V_1 = 4V_1$$

$$\Rightarrow V_1 = 7V$$

$$V = 7V$$

$$V_2 = 13V$$

$$\frac{V_2}{2} = i$$

$$\Rightarrow i = 6.5A$$

$$42 = 7V_1 + 8(V_1 + 6)$$

~~= 7V1 + 8V1 + 48~~

$$42 = 15V_1 + 48$$

$$\Rightarrow 15V_1 = -6$$

$$\Rightarrow V_1 = -\frac{6}{15}V$$

$$V_1 = -0.4V$$

$$V_1 = -400mV$$


$$i = \frac{V_2}{2}$$


$$i = \frac{5.6}{2} = 2.8A$$

~~Supermesh~~
11/9/23
Supernode: When a current source connected between two loops, it is encircled.

If a Resistance is connected in series with it, it also should be encircled.

Ex.

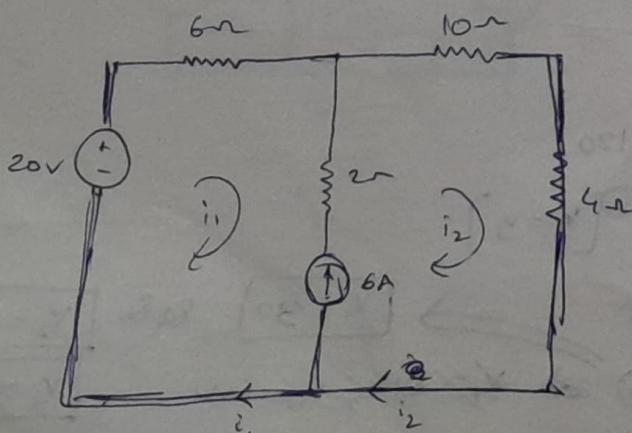

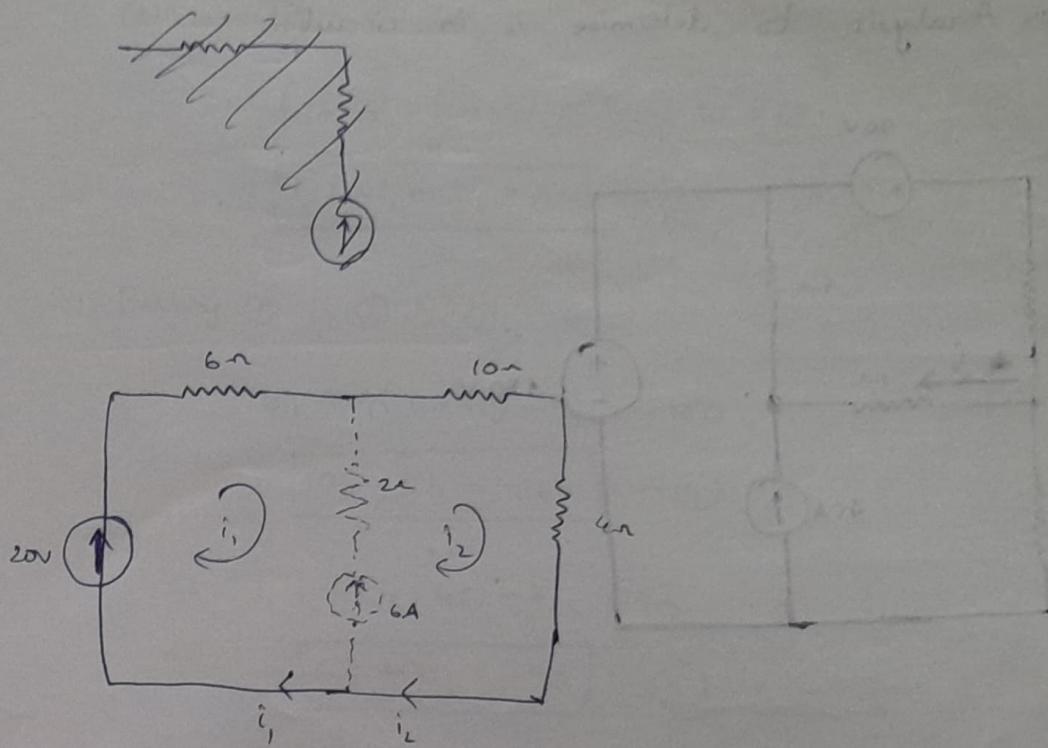

$$i_2 = i_1 + 6 \quad (\text{Super Mesh} - \text{KCL})$$

Apply KVL for loop :

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$

$$\Rightarrow 6i_1 + 14i_2 = 20 \quad (2)$$

Solving ① and ② ,


$$i_1 = -3.2 \text{ A}$$

$$i_2 = 2.8 \text{ A}$$


→ Supermesh does not have its own current.



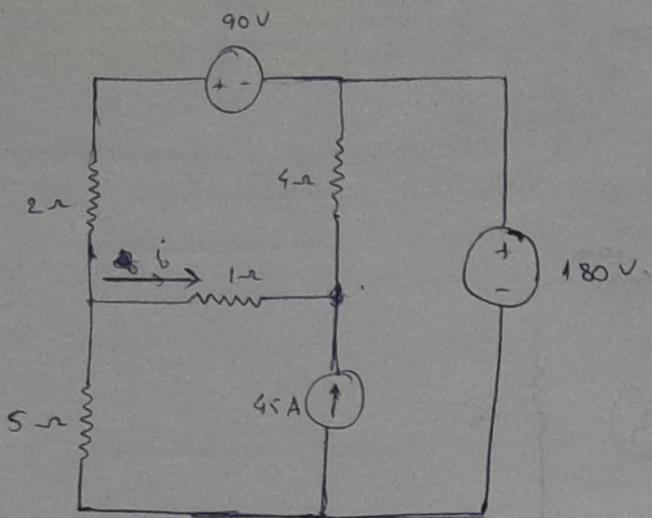Q) Use Mesh Analysis to determine i_o in circuit.



Sol:

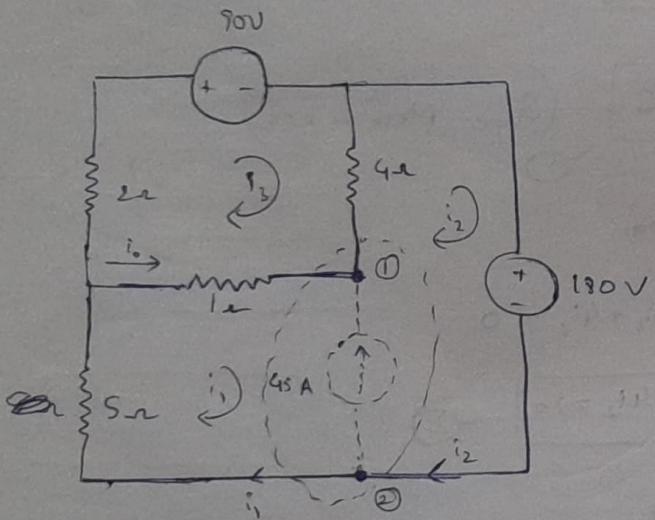

45A current source
Connected b/w 1 & 2.
& Hence it forms
~~supermesh~~ Supermesh.

$$i_1 + 45 = i_2 \quad \text{--- (1)}$$

By Applying KCL in Supermesh

Applying KVL in loops:

@ Loop - I and II :

$$-5i_1 + i_3 = 9 \quad \cancel{5i_1 = 5i_1}$$

$$-5i_1 + (i_1 - i_3) - 4(i_2 - i_3) - 180 = 0$$

$$\Rightarrow [6i_1 + 4i_2 - 5i_3 = -180] \quad \text{--- (2)}$$

@ Loop - III :

$$-4(i_3 - i_2) - (i_3 - i_1) - 2i_2 - 90 = 0$$

$$\Rightarrow [i_1 + 4i_2 + 7i_3 = 90] \quad - \textcircled{3}$$

Putting ① in ② & ③,

$$6i_1 + 4(i_1 + 45) - 5i_3 = -180$$

$$\Rightarrow [10i_1 - 5i_3 = -360] \quad - \textcircled{4}$$

$$i_1 + 4(i_1 + 45) + 7i_3 = 90$$

$$\Rightarrow [5i_1 + 7i_3 = -90] \quad - \textcircled{5}$$

$$\begin{bmatrix} 10 & -5 \\ 5 & -7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_3 \end{bmatrix} = \begin{bmatrix} -360 \\ -90 \end{bmatrix}$$

$$|R_1| = 45$$

$$R_1 = \begin{bmatrix} -360 & -5 \\ -90 & -7 \end{bmatrix}$$

$$|R_1| = 2070$$

$$|R_3| = 900$$


$$|R_1| = 2520 - 450 \\ = 2070$$

$$i_1 = \frac{2070}{45} = -46 \text{ A}$$

$$R_3 = \begin{bmatrix} 10 & -360 \\ 5 & -90 \end{bmatrix}$$

$$i_3 = \frac{900}{45} = 20 \text{ A}$$


$$|R_1| = -900 + 1800 \\ = 900$$

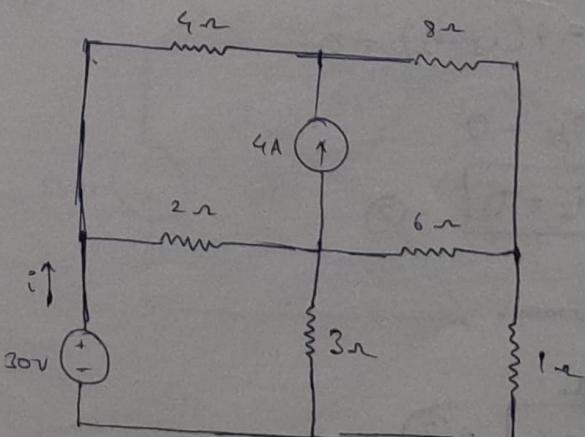


Find i

(H.W)
✓ 8)

(Q)

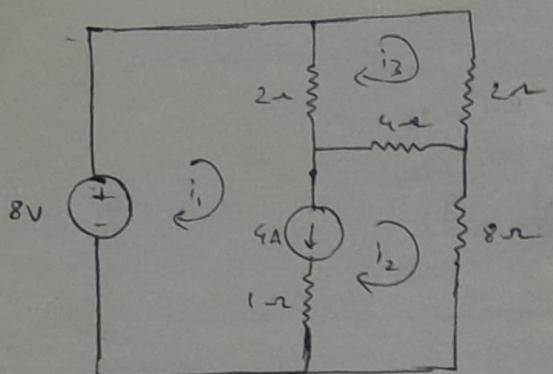

Sol:

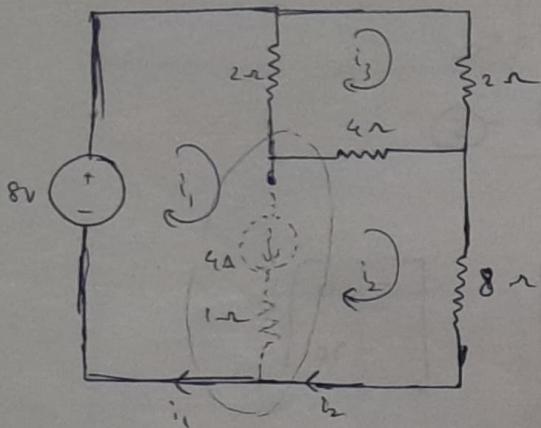

Applying KVL for Loop ① and ② :

$$8 - 2(i_1 - i_3) - 4(i_2 - i_3) - 8i_2 = 0$$

$$\Rightarrow 8 - 2i_1 - 12i_2 + 6i_3 = 0$$

$$\Rightarrow \boxed{2i_1 + 12i_2 - 6i_3 = 8} \quad - \textcircled{1}$$

Applying KVL for Loop ③ :

$$-2(i_3 - i_1) - 2i_3 - 4(i_3 - i_2) = 0$$

$$\Rightarrow 2i_1 + 4i_2 - 8i_3 = 0$$

$$\Rightarrow \boxed{i_1 + 2i_2 + 4i_3 = 0} \quad - \textcircled{2}$$

Applying KCL in Supermesh,

~~$i_1 = i_2 + 4$~~

$$\boxed{i_1 = i_2 + 4} \quad - \textcircled{3}$$

Sub ① in ① and ② :

$$3i_2 + 4 - 4i_3 = 0$$

$$\boxed{3i_2 - 4i_3 = -4} \quad -\textcircled{4}$$

D₁

$$\boxed{14i_2 - 6i_3 = 0} \quad \cancel{\textcircled{5}}$$

$$\boxed{7i_2 = 3i_3} \quad -\textcircled{5}$$

$$3\left(\frac{3i_3}{7}\right) - 4i_3 = -4$$

$$\Rightarrow \frac{9i_3}{7} - 4i_3 = -4$$

$$\Rightarrow 9i_3 - 28i_3 = -28$$

$$\Rightarrow 19i_3 = 28$$

$$\boxed{i_3 = \frac{28}{19} = 1.473 \text{ A}}$$

$$i_2 = \left(\frac{3}{7}\right)i_3$$

$$\boxed{i_2 = 0.63158 \text{ A}}$$

$$\boxed{i_1 = 4.6316 \text{ A}}$$


$$\begin{bmatrix} 2 & 12 & -6 \\ 1 & 2 & -4 \\ 1 & -1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \\ 4 \end{bmatrix}$$

$$i_2 = \frac{12}{19}$$

$$i_1 = \frac{88}{19}$$

~~Q~~

→ Practice Problems :

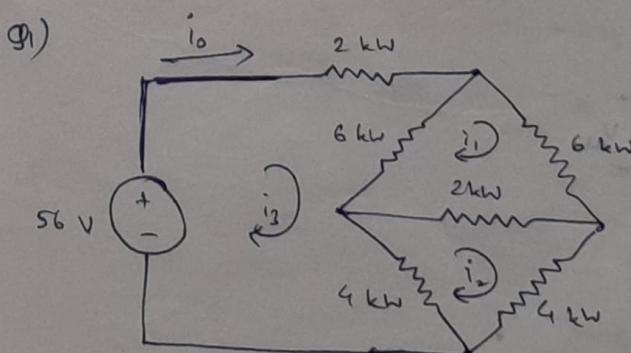

Mesh Analysis
Find ~~i_o~~ i_o.

$$-6i_1 - 2(i_1 - i_2) - 6(i_1 - i_3) = 0$$

[KVL in Loop I]

$$\Rightarrow 14i_1 - 2i_2 - 6i_3 = 0 \quad \text{---} \textcircled{1}$$

$$\Rightarrow 7i_1 - i_2 - 3i_3 = 0 \quad \text{---} \textcircled{1}$$

$$-4i_2 - 4(i_2 - i_1) - 2(i_2 - i_3) = 0$$

[KVL in Loop 2]

$$\Rightarrow 2i_1 - 10i_2 + 4i_3 = 0$$

$$\Rightarrow i_1 - 5i_2 + 2i_3 = 0 \quad \text{---} \textcircled{2}$$

$$56 - 2i_3 - 6(i_3 - i_1) - 4(i_3 - i_2) = 0$$

$$\Rightarrow 56 + 6i_1 + 4i_2 - 12i_3 = 0 \quad \text{---} \textcircled{3}$$


$$\begin{bmatrix} 7 & -1 & -3 \\ 1 & -5 & 2 \\ 6 & 4 & -12 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -56 \end{bmatrix}$$

$$i_1 = 4A$$

$$i_2 = 4A$$

$$i_3 = 8A = i_o \quad \checkmark$$

(g)

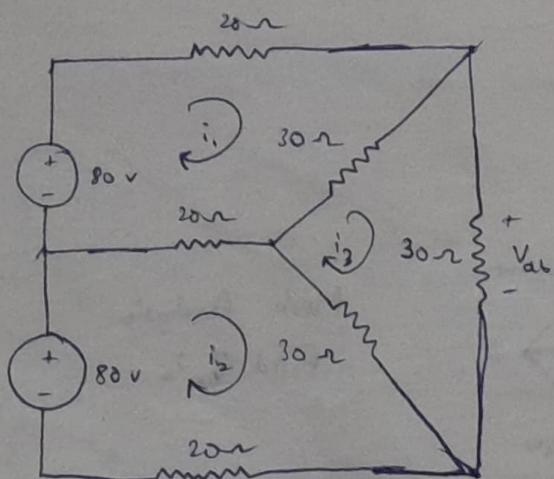



$$80 - 20i_1 - 30(i_1 - i_2) - 20(i_1 - i_2) = 0 \quad \text{---(1)}$$

$$80 - 20(i_2 - i_1) - 30(i_2 - i_3) - 20(i_2) = 0$$

$$-30(i_3 - i_1) - 30(i_2 - i_3) - 20i_3 = 0$$

$$V_{ab} = 30i_3$$

H.W
Sol :

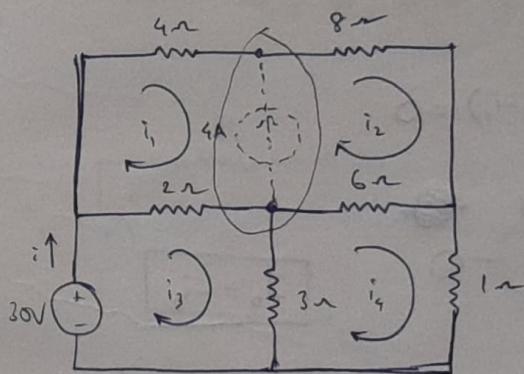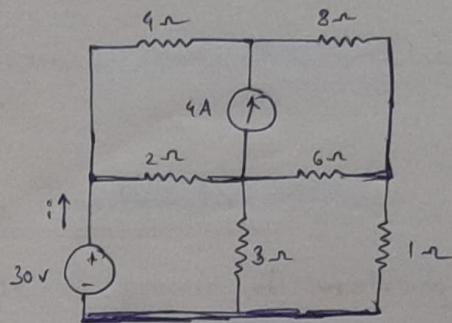

Loop ③ :

$$30 - 2(i_3 - i_1) - 3(i_2 - i_4) = 0$$

$$\Rightarrow 30 = -2i_1 + 5i_3 - 3i_4 \quad \text{---(1)}$$

Loop ④ :

$$-3(i_4 - i_3) - 6(i_4 - i_2) - i_4 = 0$$

$$\Rightarrow 6i_2 + 3i_3 - 10i_4 = 0 \quad \text{---(2)}$$

Now loop ① and ② :

$$-2(i_1 - i_3) - 4(i_1) - 8(i_2) - 6(i_2 - i_4) = 0$$

$$\Rightarrow -6i_1 - 14i_2 + 2i_3 + 6i_4 = 0$$

$$\Rightarrow -2i_1 + 7i_2 - 2i_3 - 3i_4 = 0 \quad \text{---(3)}$$


$$i_1 = \frac{-73}{132} = -0.553 \text{ A}$$

$$i_2 = \frac{455}{132} = 3.447 \text{ A}$$

$$i_3 = \frac{565}{66} = \underline{8.561 \text{ A}}$$

$$i_4 = \frac{51}{11} = 4.636 \text{ A}$$

HW
Sol:

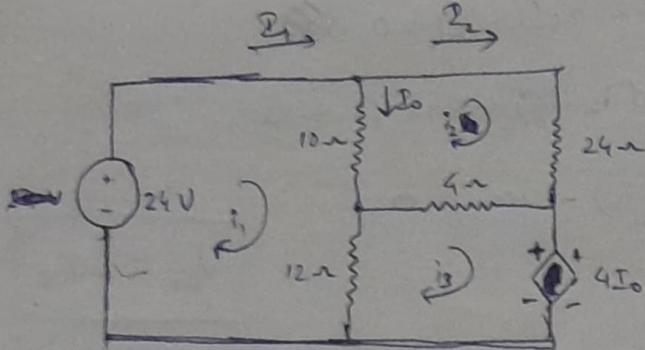

Mesh Analysis

Loop ① :

$$24 - 10(i_1 - i_2) - 12(i_1 - i_3) = 0$$

$$\Rightarrow 24 = 22i_1 - 10i_2 - 12i_3$$

$$\Rightarrow 12 = 11i_1 - 5i_2 - 6i_3 \quad -\textcircled{1}$$

Loop ② :

$$-24i_2 - 4(i_2 - i_3) - 10(i_2 - i_1) = 0$$

$$\Rightarrow 10i_1 - 38i_2 + 4i_3 = 0$$

$$5i_1 - 19i_2 + 2i_3 = 0 \quad -\textcircled{2}$$

Loop ③ :

$$\boxed{I_0 = -i_2}$$

$$-12(i_3 - i_1) = 4(i_3 - i_2) + 4i_2 = 0$$

$$\Rightarrow 12i_1 + 8i_2 - 16i_3 = 0$$

$$\Rightarrow 3i_1 + 2i_2 - 4i_3 = 0$$

$$i_1 = \frac{216}{65}$$

$$i_2 = \frac{6}{5}$$

$$i_3 = \frac{201}{65}$$


12/9/23

Chapter 4 :




- Source Transformation
- Norton's Theorem
- Thevenin's Theorem
- Superposition Theorem
- Maximum Power Transformation Theorem





Source Transformation :

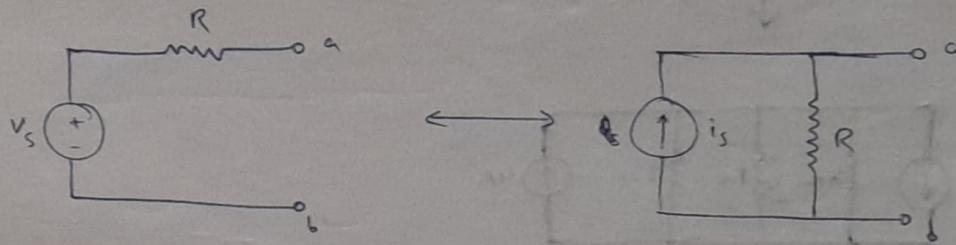Is a process of replacing voltage source (V_s) in series with a Resistor R by a current source (i_s) in parallel with a Resistor R , or vice versa.



Q) Use Source Transformation to find V_o

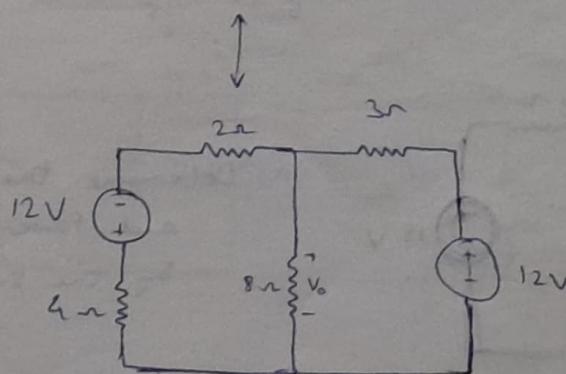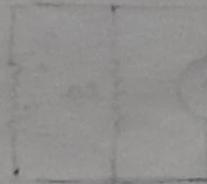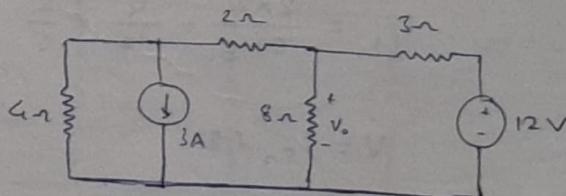

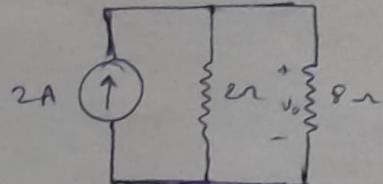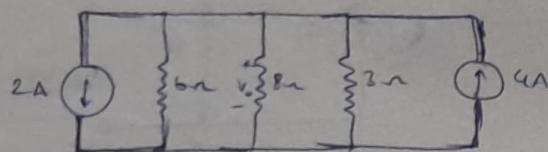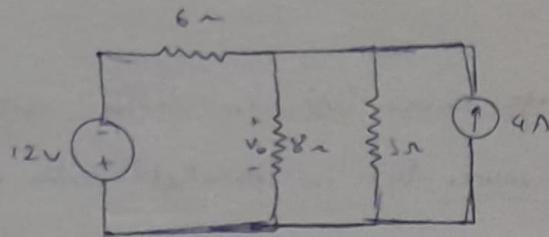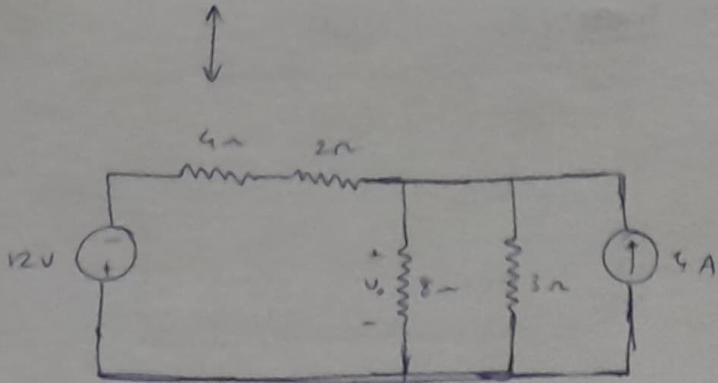


$$i_{8\Omega} = \frac{2 \times 2}{2+8} = \frac{4}{10} = \frac{2}{5}$$





$$V = i_{8\Omega} \times 8$$

$$= \frac{2}{5} \times 8 = \frac{16}{5} = 3.2 V$$

(b)

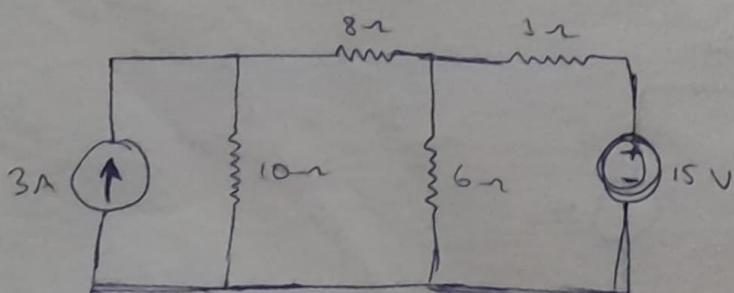

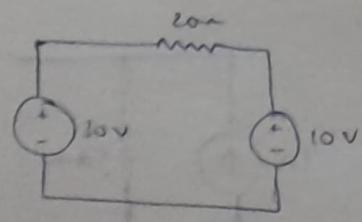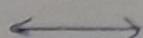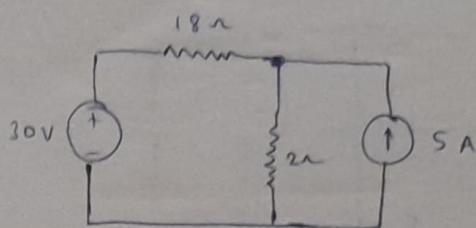
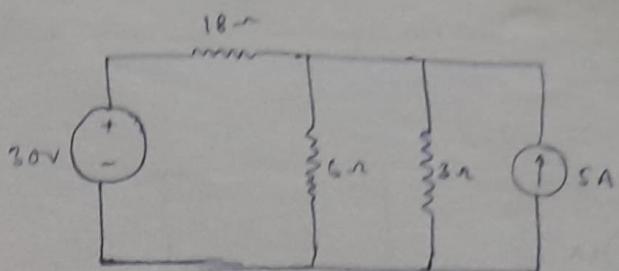
Determine the current and Power absorbed by the 8Ω resistor.




$$i = \frac{20}{20} = 1 \text{ A}$$

$$i = 1 \text{ A}$$



$$P = i^2 R = 8 \text{ W}$$

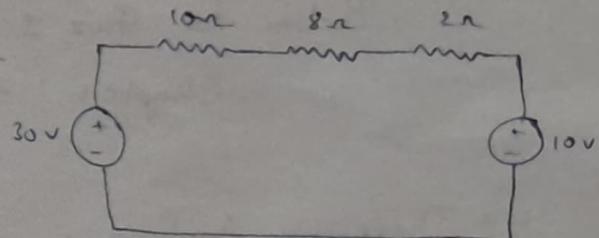
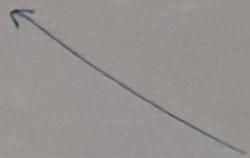


Q)

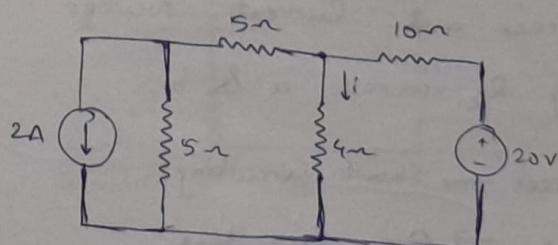

Find "i"

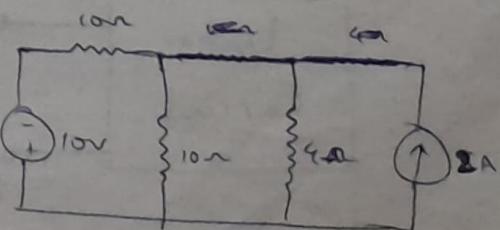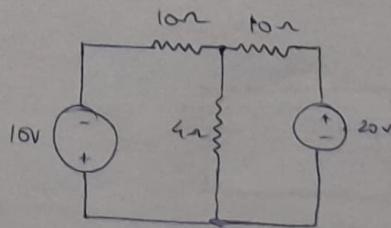

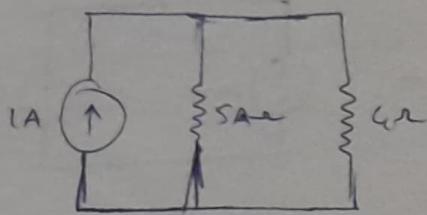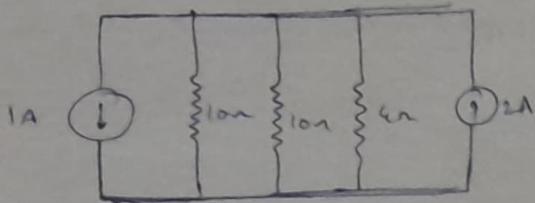

$$i = \frac{5 \times 1}{9} = \frac{5}{9} A$$

13/9/23

LINEAR CIRCUITS:

~~Portion for Quiz 1, Chapter 4~~

Portion for Quiz 1:


Chapters 1, 2, 3, 4

→ Thermin's Analysis:


Turn off Voltage sources and Current sources while calculating R_{Th} across a & b.

Voltage sources → short circuiting


Current sources → Open circuiting

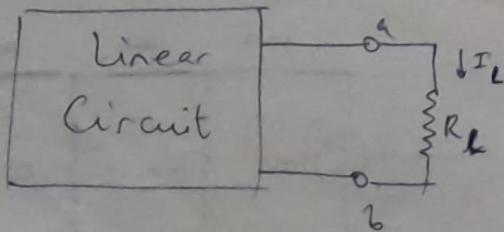

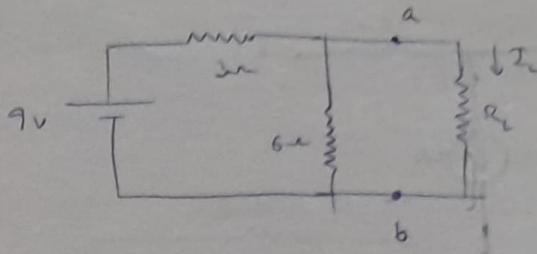Q) Find Thvenin's Voltage w.r.t R_L (load resistor)



Sol:

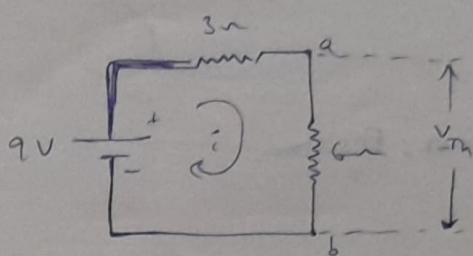


$$V_{Th} = V_{6\Omega}$$


$$\Rightarrow V_{6\Omega} = \frac{9 \times 6}{6+3} = \frac{54}{9} = 6 \text{ V}$$

$$\therefore V_{Th} = 6 \text{ V}$$


Finding R_{Th} :

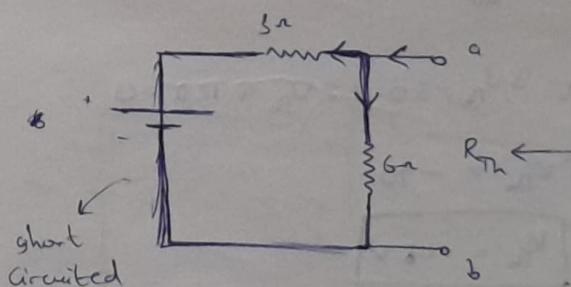

$$R_{Th} = 3 \parallel 6 = 2 \Omega$$

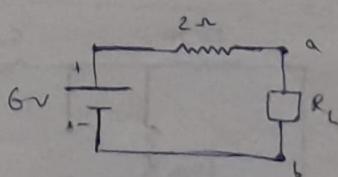


Q) Obtain Thvenin's Equivalent Circuit:

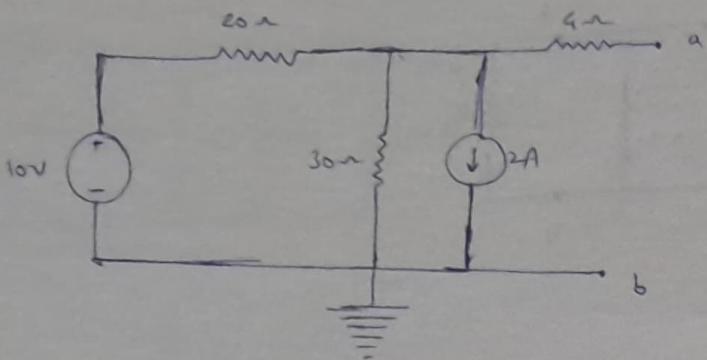

Soln:

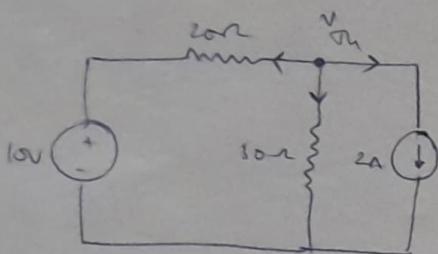No current flowing through 4 ohm Resistor



Apply KCL @ V_{Th} ,



$$\frac{V_{Th} - 10}{20} + \frac{V_{Th}}{30} + 2 = 0$$

$$\Rightarrow V_{Th} - 30 + 2V_{Th} + 120 = 0$$

$$\Rightarrow 5V_{Th} = -90$$

$$V_{Th} = -18 \text{ V}$$


For R_{Th} ,

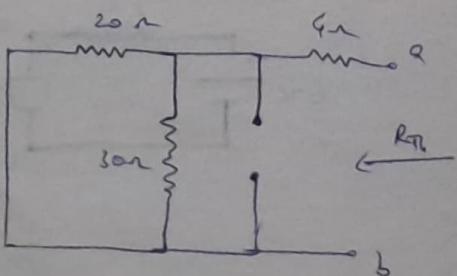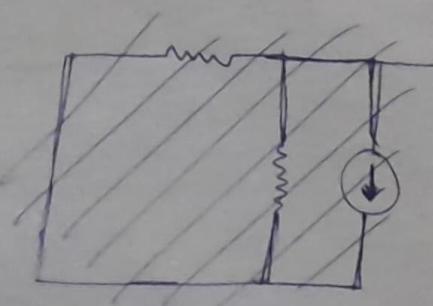

$$R_{Th} = 20 \parallel 30 + 4$$

$$= 12 + 4$$


$$\Rightarrow R_{Th} = 16 \Omega$$

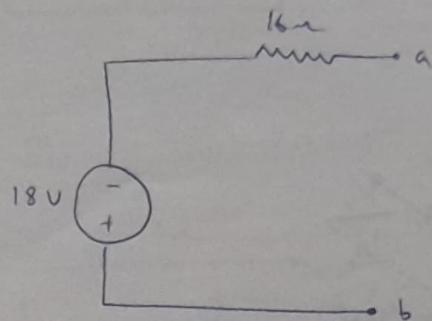

Thevenin's Equivalent Circuit


Q) Using Thevenin's Equivalent Circuit.

Calculate i_o through 2Ω Resistor.

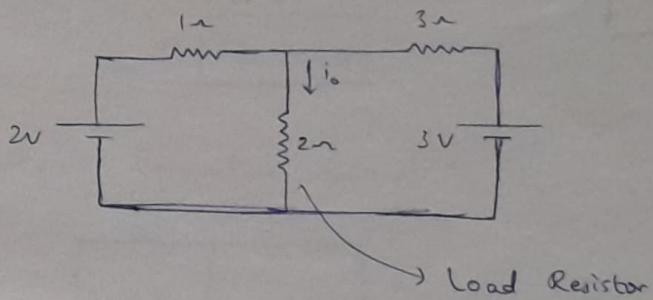

Load Resistor

Sol:

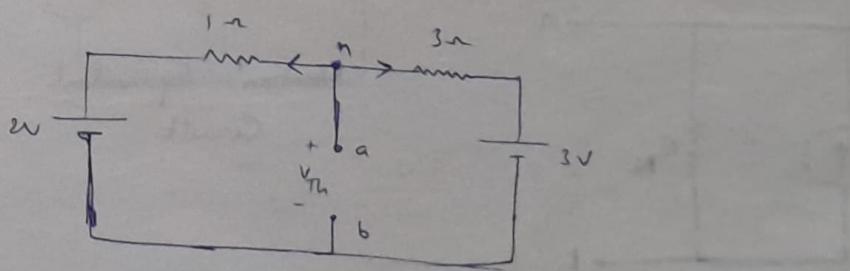


$$\frac{V_{Th}-2}{1} + \frac{V_{Th}-3}{3} = 0$$

(Applying KCL @ 'n' node)

$$\Rightarrow 3V_{Th} - 6 + V_{Th} - 3 = 0$$

~~KCL~~

$$\Rightarrow V_{Th} = 2.25 V$$

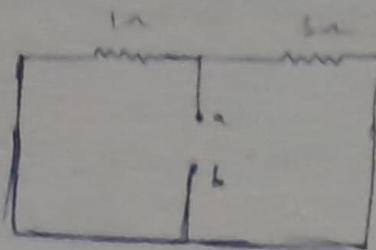


$$1 + \frac{1}{3} \Rightarrow \left(\frac{3}{4} \right)$$

$$R_{Th} = \frac{3}{4} \Omega = 0.75 \Omega$$

$$\therefore i_o = \frac{V_{Th}}{R_L} = \frac{2.25}{0.75} = \frac{3}{4} A$$


Thevenin's Equivalent Circuit:

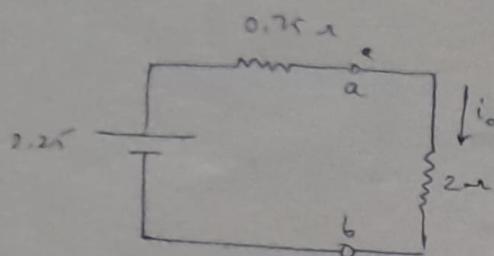

$$i_o = \frac{2.25}{2.75} = 0.8182 \text{ A}$$




→ Norton's Theorem:

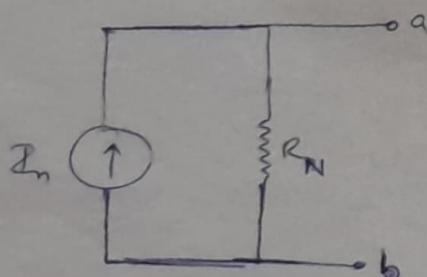


Norton's Equivalent Circuit

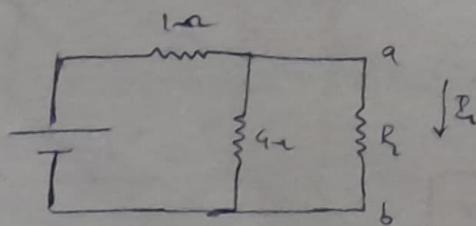
g) Use Norton's Theorem to find current through R_L , $R_L = 0.7 \Omega$



Sol.

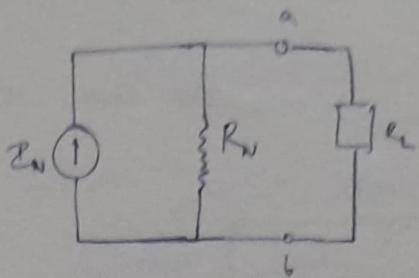

(i) Z_N

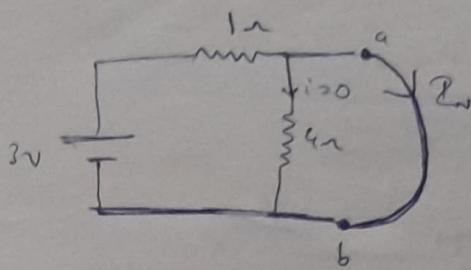


$$Z_N = \frac{3}{1} = 3\Omega$$

∴

$$\boxed{Z_N = 3\Omega}$$


(ii) R_N

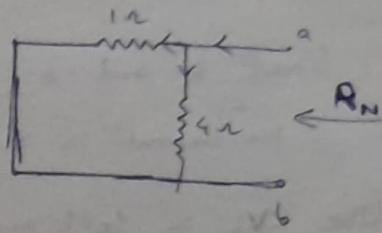

$$R_N = \frac{1 \times 4}{1+4} \Rightarrow \boxed{R_N = \frac{4}{5}\Omega}$$



~~R_N~~

Norton's Equivalent Circuit:

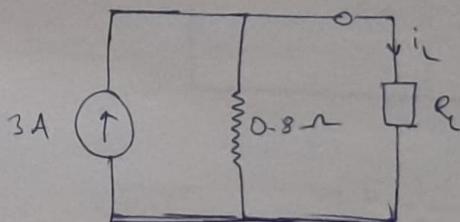

$$I_L = \frac{3 \times 0.8}{0.8 + 0.7} = \frac{2.4}{1.5} = 1.6\text{ A}$$

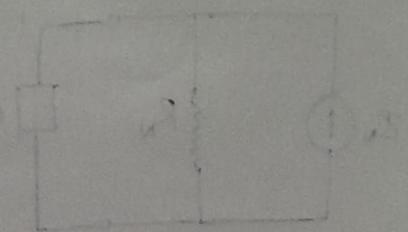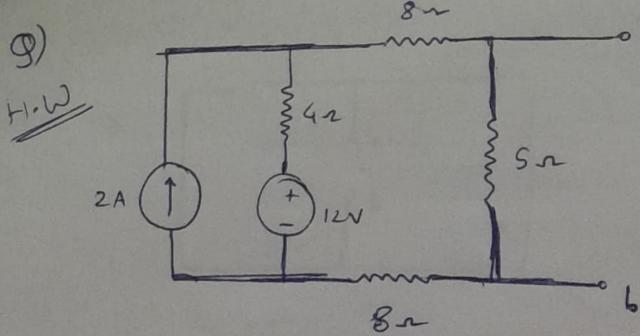
$$\boxed{\therefore I_L = 1.6\text{ A}}$$



Obtain Norton's Equivalent Circuit
i.e. Find R_N and I_N

R_N : Short a and b

∴ No current in 5Ω resistor

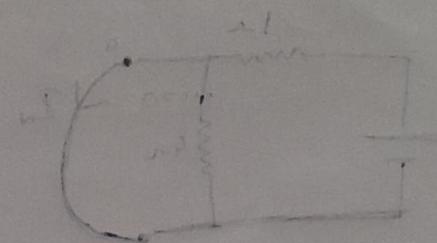

Use KVL in left and right loops

$$i_1 = 2 \text{ A}$$

i_2 (I_N) \rightarrow KVL

$$\text{Ans} : i_2 = 1 \text{ A} = I_N$$

$$R_N = 4 \Omega$$


R_N : Short 12V voltage source

Open 2A current source

$$5\Omega \parallel (8\Omega + 4\Omega + 8\Omega) \rightarrow R_N$$

$$[AE = 4.5]$$

Q) Solve using Thevenin's Theorem

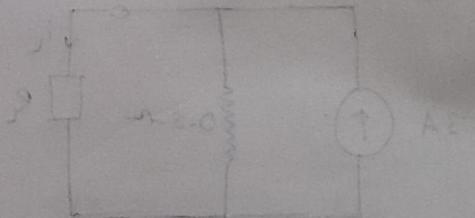


→ Superposition Theorem:

It can be only used if Linear Circuit has 2 or more independent sources.

When 1 source is acting alone, the other sources should be shut off.


Q) Use Superposition Theorem to find V

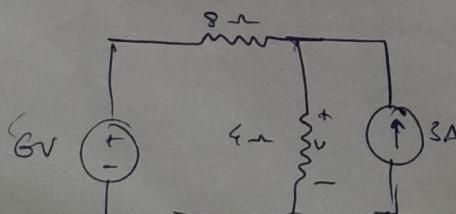

Current Source \rightarrow Open Circuit

Voltage Source \rightarrow Close Circuit

(i) When 6V source is Acting :

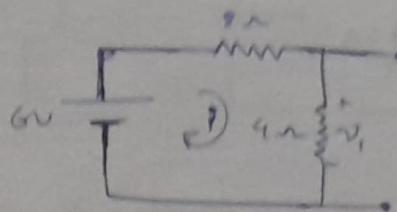

$$i = \frac{6}{12} = \frac{1}{2} \text{ A}$$


$$\boxed{i = 0.5 \text{ A}}$$

$$\left[V_1 = \frac{6 \times 4}{12} = 2 \text{ V} \right]$$

$$V_{4\text{m}} = 0.5 \times 4 = 2 \text{ V}$$

$$\boxed{V_{4\text{m}} = 2 \text{ V}} \Rightarrow \underline{V_1 = 2 \text{ V}}$$

(ii) When 3A source is Acting :

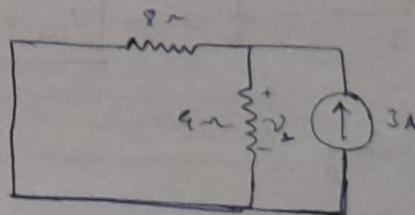


$$i = \frac{3 \times 8}{8 + 4} = 2 \text{ A}$$

$$\boxed{i = 2 \text{ A}}$$


$$\Rightarrow \boxed{V_2 = 8 \text{ V}}$$

$$V_{2\text{m}} = V_1 + V_2 = 2 + 8 = 10 \text{ V}$$

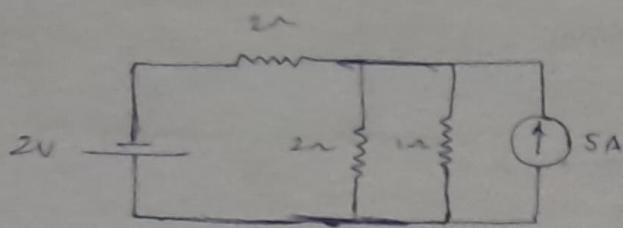Q) Calculate current through 1 Ω Resistor in the circuit




(i) When 2V source is acting

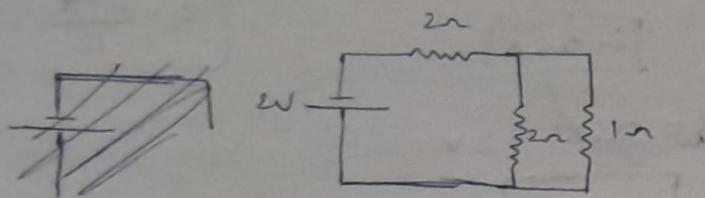

$$i = \frac{2}{\frac{2}{3} + 2} = \frac{1}{\frac{1}{3} + 1} = \frac{3}{4} \text{ A}$$

$$V_{1n} = \frac{\frac{2}{3} \times 2}{3} = \frac{1}{2} \text{ V} \Rightarrow \boxed{V_{1n} = \frac{1}{2} \text{ V}}$$

(ii) When SA source is acting

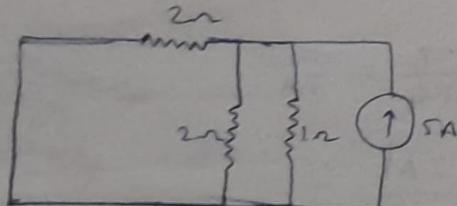


$$i_2 = \frac{5 \times 1}{1+1} = \frac{5}{2} \text{ A}$$


$$\boxed{V_{1n} = \frac{5}{2} \text{ V}}$$

$$\boxed{V_{1n} (\text{Total}) = 2\Omega}$$

(Q) Find V_o across 2Ω

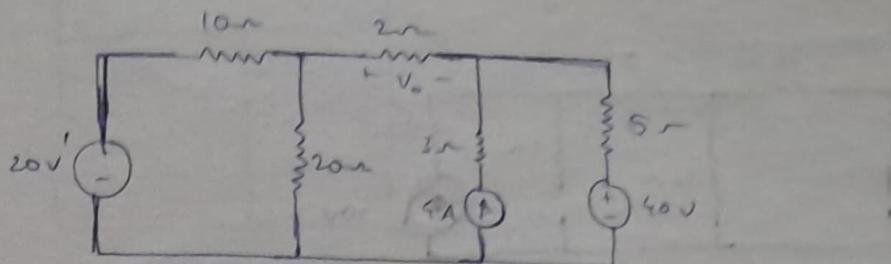

(i) When 20V source is acting

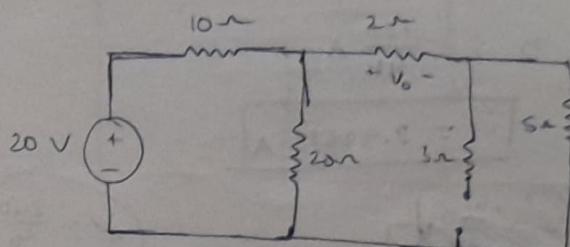

$$R_{eff} = \frac{20 \times 7}{20 + 7} + 10$$

$$R_{eff} = \frac{140}{27} + \frac{270}{27} = \frac{410}{27}$$

$$i = \frac{20}{410} \times 27$$

$$i = \frac{54}{41} A$$

$$i = \frac{\frac{54}{41} \times 20}{27}$$


$$= \frac{40}{41} A$$

$$i = 0.9756 A$$

$$\Rightarrow V = 1.9512 V$$

$$V = \frac{80}{41}$$


(ii) When 4A source is acting

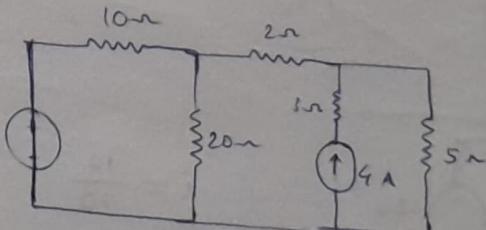

$$\frac{10 \times 20}{30} = \frac{20}{3}$$

$$\frac{20}{3} + \frac{6}{7} = \frac{26}{3}$$
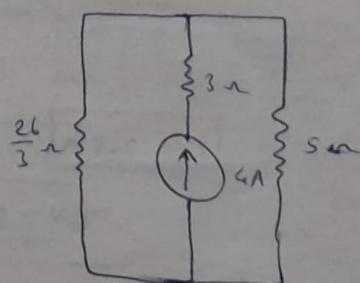
$$\frac{\frac{26}{3} \times 5}{\frac{41}{3}} = \frac{26 \times 5}{41}$$




$$\frac{4 \times 5}{\frac{26}{3} + 5} = \frac{60}{41} A \Rightarrow i = 1.4634 A$$

$$V = 2.9268 V$$

$$V = \frac{120}{41}$$

(iii) When 40V source is Acting

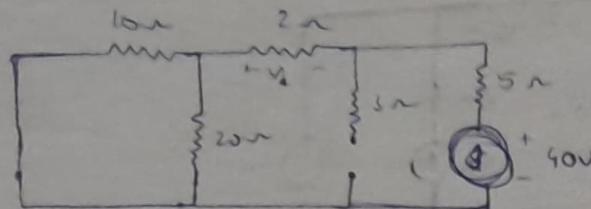

$$\frac{20}{3} \Omega + 7 \Omega$$

$$V = i = \frac{40}{\frac{20}{3} + 7}$$

$$\Rightarrow i = \frac{120}{41} \text{ A}$$

$$i = 2.92683 \text{ A}$$


~~$$V = \frac{240}{41}$$~~

$$V = \frac{240}{41}$$


$$V = 5.85 \text{ V}$$

Total $V = \frac{440}{41} \text{ V}$

Q)

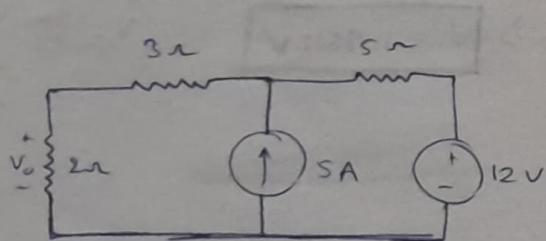

(i)

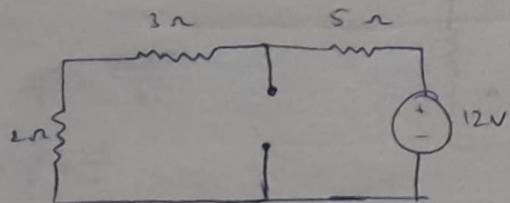


$$i = \frac{12}{10}$$

$$i = 1.2 \text{ A}$$

$$\Rightarrow V = 2.4 \text{ V}$$

(ii)

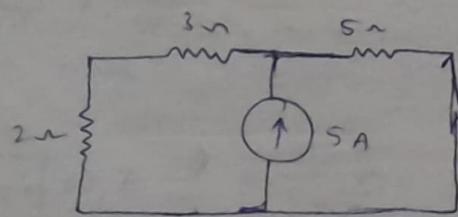


$$i = 2.5 \text{ A}$$

$$\Rightarrow V = 5 \text{ V}$$


$$\text{Total } V = 7.4 \text{ V}$$

(Q)
H.W

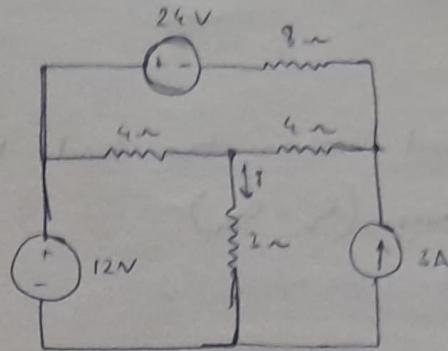

Find i in the circuit using
Superposition principle and
verify using Thévenin's Analysis.

(i)

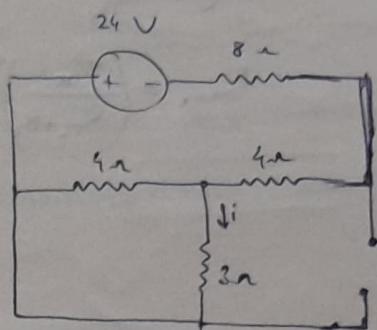

$$R_{\text{eff}} = 12 + \frac{4 \times 3}{7}$$

$$= 12 + \frac{12}{7}$$



$$i = \frac{24}{12 + \frac{12}{7}} = \frac{24}{\frac{96}{7}} = \frac{7}{4} \text{ A}$$

$$\boxed{i = 1.75 \text{ A}}$$

$$i_{3n} = \frac{\frac{7}{4} \times 4}{7}$$

$$\boxed{i_{3n} = 1 \text{ A}} \quad -①$$

(ii)

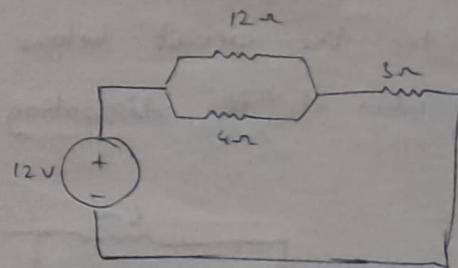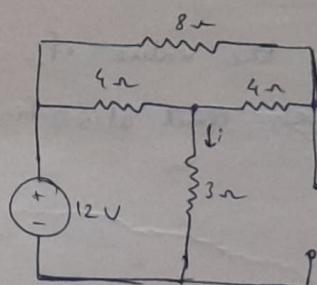


$$i = \frac{12}{6} = 2 \text{ A}$$

$$\frac{12}{12+4} = 2$$

$$\boxed{i_{3n} = 2 \text{ A}} \quad -②$$

(iii)

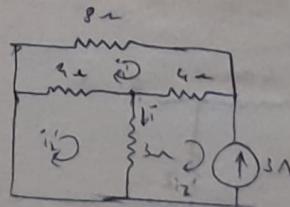

$$i = i_2' - i_1'$$

$$= \frac{-1}{5} + \frac{9}{10}$$

$$\Rightarrow i = \frac{3}{10}$$

$$-3(i_2' - i_1') - 4(i_2' - i_1') - 3 = 0$$

$$\Rightarrow 4i_1' + 3i_2' - 7i_3' = 3 \quad -①$$

$$-4(i_2' - i_1') - 3(i_2' - i_3') = 0$$

$$\Rightarrow -4i_1' - 7i_2' + 3i_3' = 0 \quad -②$$

$$-8i_1' - 4(i_1' - i_2') - 4(i_1' - i_2') = 0$$

$$\Rightarrow -16i_1' + 4i_2' + 4i_3' = 0 \quad -③$$


$$\boxed{i_{3n} = \frac{3}{10} \text{ A}}$$

$$\text{Total } i = \frac{81}{20} \text{ A}$$

$$\boxed{i = 4.05 \text{ A}}$$

→ Maximum Power Transfer Theorem :

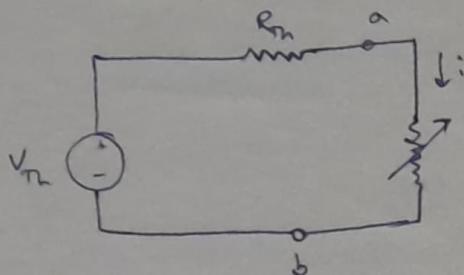
Max. power is transferred to load, when the load Resistance equals to Thevenin's Resistance ($R_L = R_{Th}$)



$$R_{max.} = i^2 R_L$$


$$R_L = R_{Th}$$
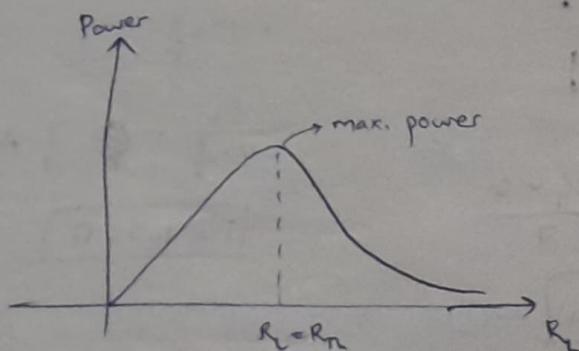
$$P_{max.} = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$




$$P_{max.} = \frac{V_{Th}^2}{4 R_{Th}}$$

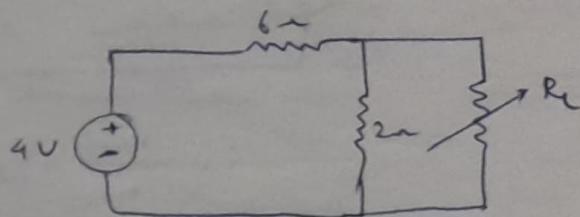Ex. Consider the circuit below. Determine the value of R_L when it is dissipating max. power and also find $P_{max.}$




$V_{Th}:$

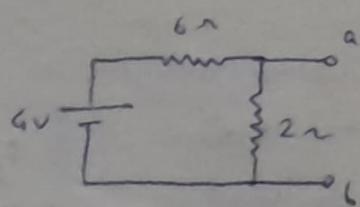

$$V_{Th} = V_{2\Omega}$$

$$= \frac{4(2)}{8} = 1V$$

$R_{Th}:$

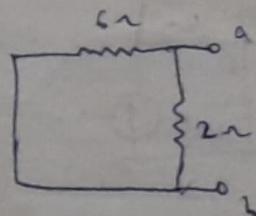

$$R_{Th} = \frac{6 \times 2}{8} = \frac{3}{2} = 1.5 \Omega$$

For max. power,


$$R_{Th} = R_L = 1.5 \Omega$$

Q

$$P_{max.} = \frac{V_{Th}^2}{4R_{Th}} = \frac{1^2}{4 \times 1.5} = \frac{1}{6} W$$


Q) The variable Resistor R_L in given figure is adjusted until it absorbs the max. power from the circuit.

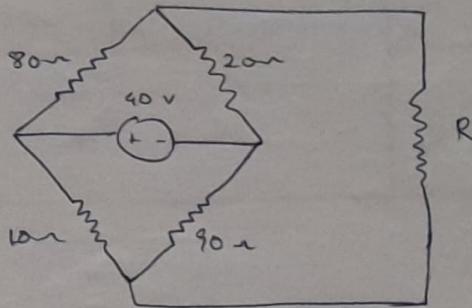- Calculate the value of R for max. power.
- Determine max. power absorbed by R .



As R is adjusted, $\therefore R = R_{Th}$

for finding R_{Th} :

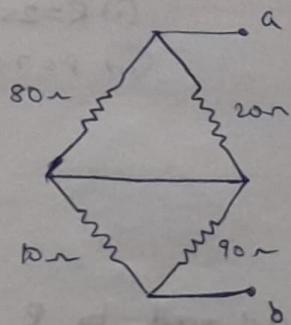

$$20 \parallel 80 + 90 \parallel 10 = R_{Th}$$

$$\frac{20 \times 80}{100} + \frac{90 \times 10}{100} = R_{Th}$$


$$16 + 9 = 25$$

$$\boxed{R_{Th} = 25 \Omega}$$

During max power absorption, $R = R_{Th} = 25 \Omega$

→ Maximum Power Transfer Theorem :

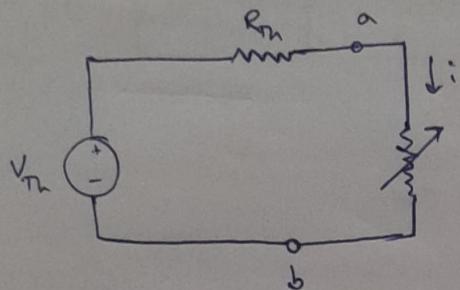
Max. power is transferred to load when the load Resistance equals to Thevenin's Resistance ($R_L = R_{Th}$)



$$R_{max.} = i^2 R_L$$


$$R_L = R_{Th}$$
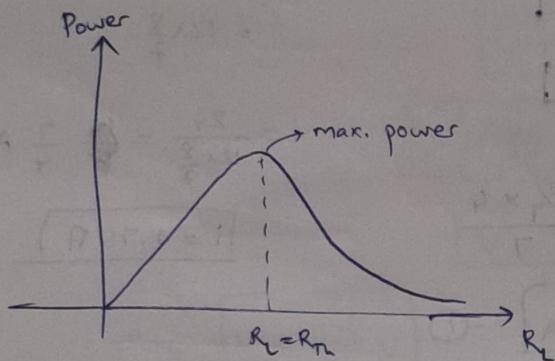
$$P_{max.} = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$




$$P_{max.} = \frac{V_{Th}^2}{4 R_{Th}}$$

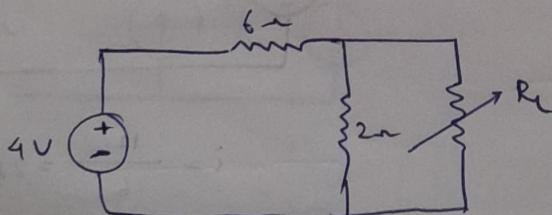Ex. Consider the circuit below. Determine the value of R_L when it is dissipating max. power and also find $P_{max.}$




$V_{Th.}$:

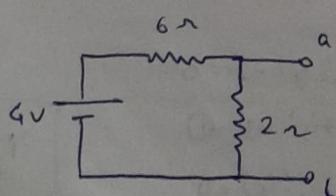

$$\begin{aligned} V_{Th.} &= V_{2\text{ ohm}} \\ &= \frac{4(2)}{8} = 1\text{ V} \end{aligned}$$

$R_{Th.}$:

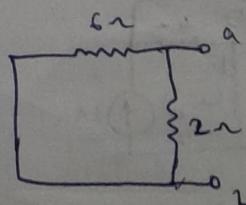

$$R_{Th.} = \frac{6 \times 2}{8} = \frac{3}{2} = 1.5\text{ ohm}$$

For max. power,


$$R_m = R_L = 1.5 \Omega$$

R

$$P_{\text{max.}} = \frac{V_m^2}{4R_m} = \frac{1^2}{4 \times 1.5} = \frac{1}{6} \text{ W}$$


Q) The variable Resistor R_L in given figure is adjusted until it absorbs the max. power from the circuit.

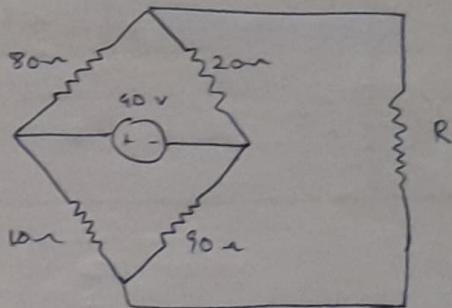- Calculate the value of R for max power.
- Determine max. power absorbed by R



As R is adjusted, $\therefore R = R_m$

For finding R_m :

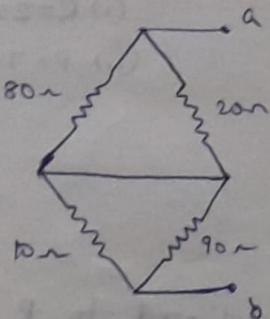

$$20 \parallel 80 + 90 \parallel 10 \Rightarrow R_m$$


$$\frac{20 \times 80}{100} + \frac{90 \times 10}{100} = R_m$$

$$16 + 9 = 25$$

$$R_m = 25 \Omega$$

During max power absorption, $R = R_m = 25 \Omega$

For finding V_{Th} :

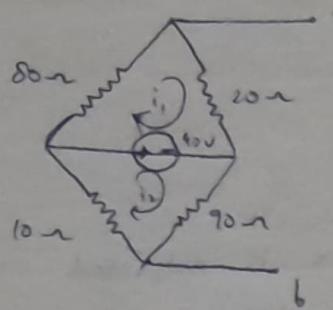

for ①:

$$-20i_1 + 40 - 80i_1 = 0$$

$$\Rightarrow 40 = 100i_1$$

$$\Rightarrow i_1 = 0.4 \text{ A}$$

for ②:

$$-90i_2 - 10i_2 - 40 = 0$$

$$\Rightarrow -100i_2 + 40 = 0$$

$$\Rightarrow i_2 = -0.4 \text{ A}$$

$$V_a - 20i_1 - 90i_2 = V_b$$


$$\Rightarrow V_a - V_b = 20i_1 + 90i_2$$

$$= -28 - 70i_1$$


$$= -70 \times \frac{4}{10}$$

$$= -28 \text{ V}$$

$$V_{Th} = -28 \text{ V}$$

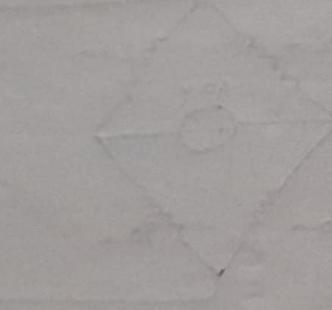

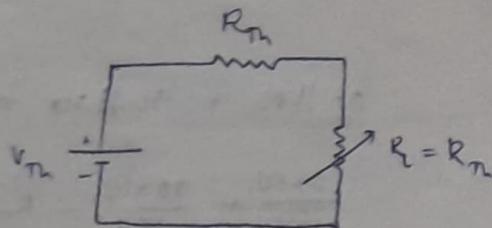
$$P_{max} = \frac{(V_{Th})^2}{4R_{Th}} = \frac{(28)^2}{4 \times 25} = \frac{(28)^2}{100} = 7.84 \text{ W}$$




$$(i) R = 25 \Omega$$

$$(ii) P = 7.84 \text{ W}$$

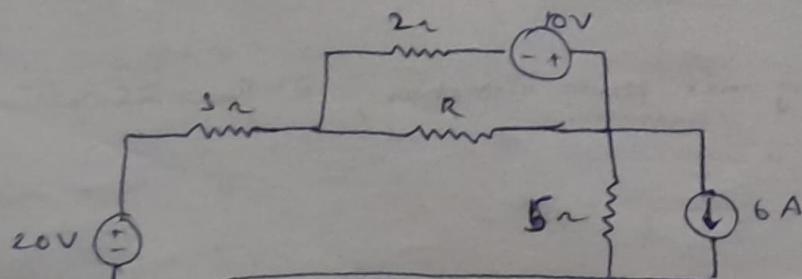Q) Find Max. Power that can be delivered to R



Finding R_{Th} :

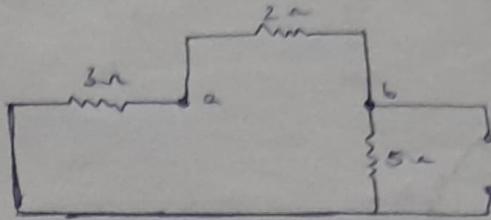


$$R_{Th} = 8 \parallel 2$$

$$\Rightarrow \frac{8 \times 2}{10} = 1.6 \text{ ohm}$$

$$R_{Th} = 1.6 \text{ ohm}$$

Finding V_{Th} :

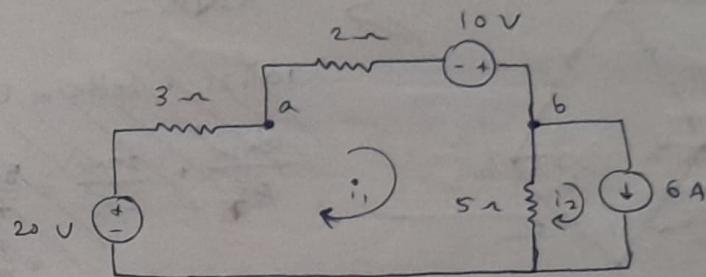

$$20 - 3i_1 - 2i_1 + 10 - 5(i_1 - i_2) = 0$$

$$\Rightarrow 30 - 10i_1 + 5i_2 = 0$$

$$\Rightarrow 10i_1 - 5i_2 = 30$$

$$\Rightarrow 2i_1 - i_2 = 6$$

$$i_2 = 6 \text{ A}$$

$$\Rightarrow 2i_1 - 6 = 6$$

$$i_1 = 6 \text{ A}$$

$$V_a - 2i_1 + 10 = V_b$$

$$\Rightarrow V_{Th} = 2i_1 - 10$$

$$= 12 - 10$$

$$= 2 \text{ V}$$


$$V_{Th} = 2 \text{ V}$$

$$P_{max} = \frac{(V_{Th})^2}{4R_{Th}} = \frac{4}{4 \times 1.6} = \frac{5}{8} \text{ W} \Rightarrow$$



$$P_{max} = 0.625 \text{ W}$$

$$P_{max} = 625 \text{ mW}$$

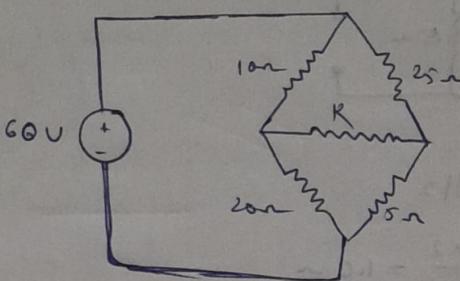Q) Determine max ~~max~~ power delivered to R.



For finding R_{Th} :

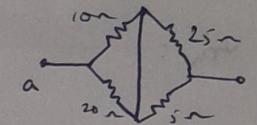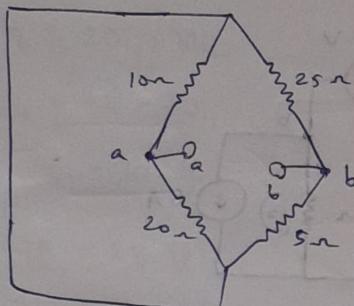


$$10 \parallel 25 + 20 \parallel 5 = R_{Th}$$

$$\frac{10 \times 25}{35} + \frac{20 \times 5}{25} = \frac{50}{7} + 4 = \frac{58}{7} \Omega$$

$$\frac{35 \times 25}{58} \Omega$$

For finding V_{Th} :

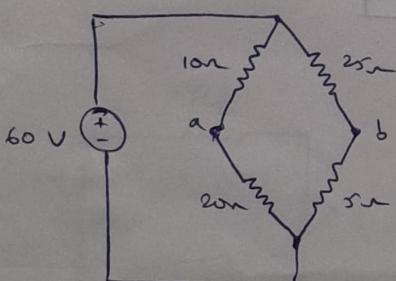


$$10 \parallel 20 + 25 \parallel 5 = R_{Th}$$

~~$$R_{Th} = \frac{20}{3} + \frac{25}{6} \Omega$$~~

$$R_{Th} = \frac{20}{3} + \frac{25}{6} = \frac{65}{6} \Omega$$

$$\Rightarrow R_{Th} = 10.833 \Omega$$

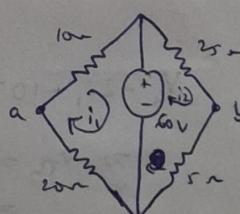

$$V_a - 10i_1 - 25i_2 = V_b$$

$$\Rightarrow V_a - V_b = V_{Th} = 10i_1 + 25i_2$$

$$= 15i_2$$

$$\Rightarrow V_{Th} = 30V$$

$$-10i_1 - 60 - 20i_2 = 0$$

$$-60 = 10i_1 + 20i_2$$

$$\underline{10i_1 = -60}$$

$$-25i_2 - 5i_2 + 60 = 0$$


$$\underline{i_2 = 2A}$$

$$P_{max} = \frac{(V_{Th})^2}{4R_{Th}} = \frac{900}{4 \times \frac{65}{6}} = \frac{270}{13} W$$



$$\therefore P_{max} = 20.769 W$$

$$\Rightarrow P_{max} = 20.77 W$$

Q)

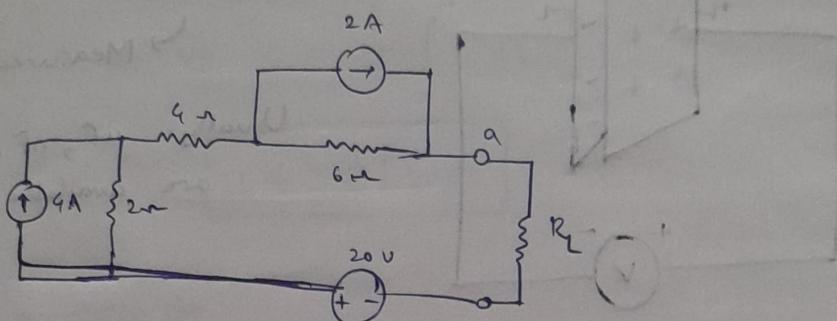

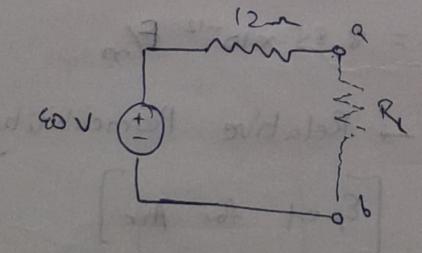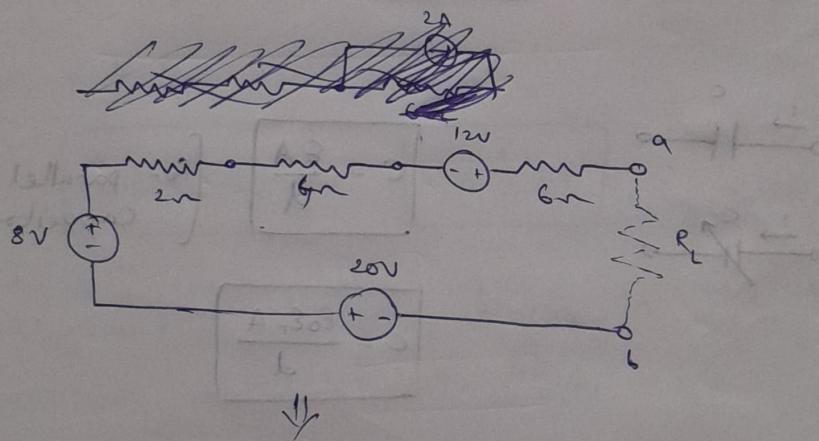- (i) Calculate ~~current through~~ R_L
- (ii) Find R_L for max power deliverable
- (iii) Determine that max power



$$\underline{\underline{R_{Th} = 12\Omega}}$$

Q.


$$\underline{\underline{V_{Th} = 40V}}$$

$$P = \frac{(V_{Th})^2}{4R_{Th}}$$

$$= \frac{40 \times 40}{4 \times 12} = \frac{400}{12} = 33.33 W$$

Chapter - 6 : Capacitors and Inductors :

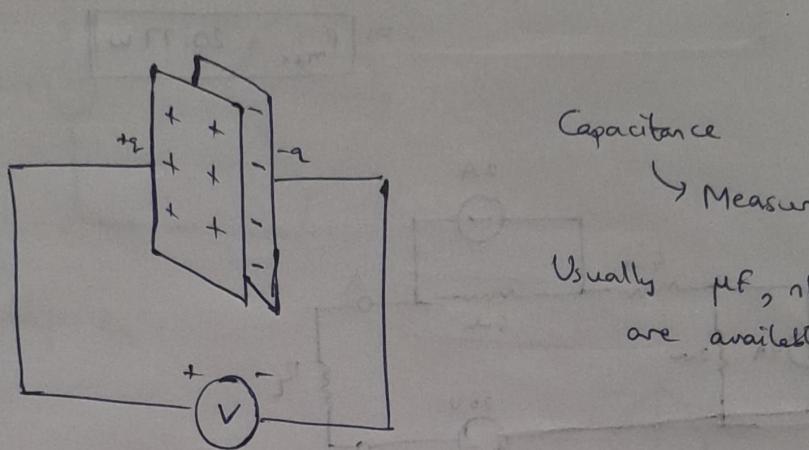
Capacitance and Inductor — Only store energy, No dissipation.



Capacitance

→ Measured in Farads
Usually μF , nF and pF
are available in market
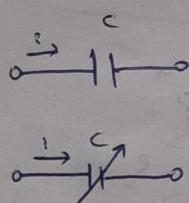
$$\begin{aligned} q &\propto V \\ \Rightarrow q = CV & \Rightarrow C = \frac{q}{V} \end{aligned}$$



$$C = \frac{\epsilon A}{d} \quad \left[\text{for parallel plate capacitors.} \right]$$

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

$$q = CV$$

$$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

$$i = \frac{dq}{dt} = C \frac{dV}{dt}$$

$\epsilon_r \rightarrow$ Relative Permeability

$$[\epsilon_r = 1 \text{ for Air}]$$

$$i = C \cdot \frac{dV}{dt}$$

No current flows in Capacitor as

$$\frac{dV}{dt} = 0 \text{ . Hence behaves like}$$

open circuited under DC conditions.

$$i_c = C \cdot \frac{dV}{dt}$$

$$\Rightarrow dV = \frac{i_c}{C} dt$$

$$\Rightarrow \int dV = \int \frac{i_c}{C} dt$$

$$\Rightarrow V_c = \frac{1}{C} \int i_c dt$$

$$\therefore V_c = \frac{1}{C} \int i_c dt$$

$$P = CV \cdot \frac{dV}{dt}$$

$$E = \int P dt$$

$$= C \int V dV$$


$$= \frac{1}{2} CV^2$$

$$\therefore E = \frac{1}{2} CV^2$$

$$\Rightarrow W = \frac{1}{2} CV^2$$

Capacitor stores Energy in the form of
Electrostatic field.

Real Capacitor:

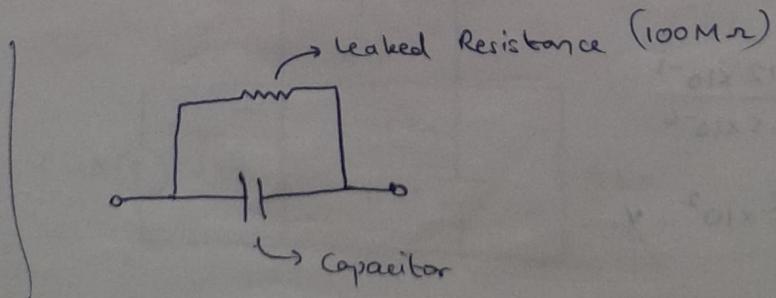

Non-linear Capacitor

Under DC, Capacitor behaves Open Circuited.

But Battery can charge Capacitor.

Q) (1) Calculate charge stored on a 3 pF capacitor with 20 V across it

$$\textcircled{A} \quad Q = CV$$

$$= 3 \times 10^{-12} \times 20$$

$$= 6 \times 10^{-11} \text{ C}$$

$$= 60 \text{ pC}$$

(2) Find the Energy stored in the Capacitor.

$$\textcircled{A} \quad W = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 3 \times 10^{-12} \times 20 \times 20$$

~~$$= 600 \times 10^{-12}$$~~

$$= 600 \times 10^{-12}$$

$$= 600 \text{ pJ}$$

$$= 0.6 \text{ nJ}$$

Q) What is Voltage across $4.5\text{ }\mu\text{F}$ capacitor if the charge on one plate is 0.12 mC ? How much energy is stored?

$$V = \frac{Q}{C}$$

$$Q = CV$$

$$= \frac{0.12 \times 10^{-3}}{4.5 \times 10^{-6}}$$

$$= \frac{12}{45} \times 10^2 \text{ V}$$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 4.5 \times 10^{-6} \times \frac{144}{(45)^2} \times 10^4$$

$$= \frac{1}{2} \times \frac{144}{45} \times 10^{-3} = \frac{72}{45} \times 10^{-1} \text{ J}$$

Q) Voltage across $5\ \mu F$ capacitor is

$$v(t) = 10 \cos(6000t) \text{ V}$$

Calculate the current through it.

$$i_C = C \cdot \frac{dv}{dt}$$

$$= 5 \times 10^{-6} \times 10 \times 6000 \times (-\sin(6000t))$$

$$\Rightarrow i_C = -0.3 \sin(6000t) \text{ A}$$

i.e. Capacitor responds to AC sources only.

Q) If a $10\ \mu F$ capacitor is connected to a voltage source


$$v(t) = 75 \sin(2000t) \text{ V}$$

Determine the current


Ans : $i_C = C \cdot \frac{dv}{dt}$

$$\Rightarrow i_C = 10 \times 10^{-6} \times \cos(2000t) \times 75 \times 2000$$

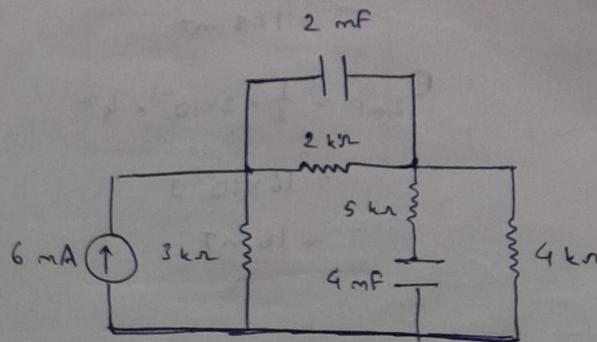Q) Obtain the Energy stored in each Capacitor under DC condition




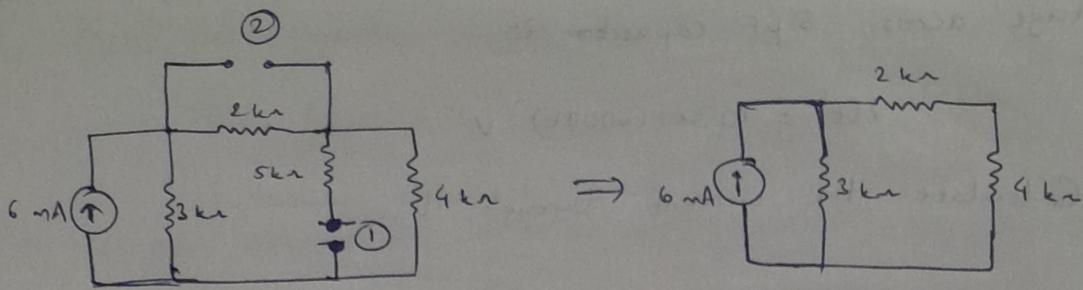Under DC \rightarrow Capacitor behaves as Open Circuit



$$V_{4\text{mF}} = V_{4\text{k}\Omega}$$

$$V_{2\text{mF}} = V_{2\text{k}\Omega}$$

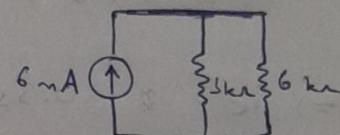

~~$$V_{4\text{k}\Omega} = 2 \text{ mA} \times 4 \text{ k}\Omega$$~~

$$= 8 \text{ V}$$

~~$$V_{2\text{k}\Omega} = 4 \times 2$$~~

$$= 8 \text{ V}$$

~~$$i_{4\text{k}\Omega} = \frac{3 \times 6}{9} = 2 \text{ mA}$$~~

$$i_{2\text{k}\Omega} = 2 \text{ mA}$$

$$V_{4\text{k}\Omega} = 2 \text{ mA} \times 4 \text{ k}\Omega$$

$$= 8 \text{ V}$$

$$i_{4\text{k}\Omega} = \frac{3 \times 6}{9} = 2 \text{ mA}$$

$$V_{2\text{k}\Omega} = 2 \text{ mA} \times 2 \text{ k}\Omega$$

$$= 4 \text{ V}$$

$$i_{2\text{k}\Omega} = 2 \text{ mA}$$

$$E = \frac{1}{2} CV^2 \Rightarrow E_{4\text{mF}} = \frac{1}{2} \times 4 \times 10^{-3} \times 8^2$$
~~$$E_{4\text{mF}} = \frac{1}{2} \times 4 \times 10^{-3} \times 8^2$$~~

$$= 128 \times 10^{-2} \text{ J}$$


$$= 128 \text{ mJ}$$

$$E_{2\text{mF}} = \frac{1}{2} \times 2 \times 10^{-3} \times 4^2$$

$$= 16 \times 10^{-3} \text{ J}$$


$$= 16 \text{ mJ}$$

(g)

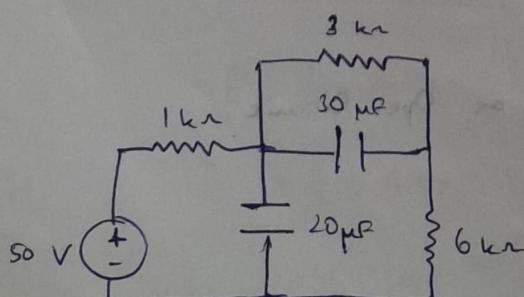

[Ans: 20.25 mJ, 3.375 mJ]

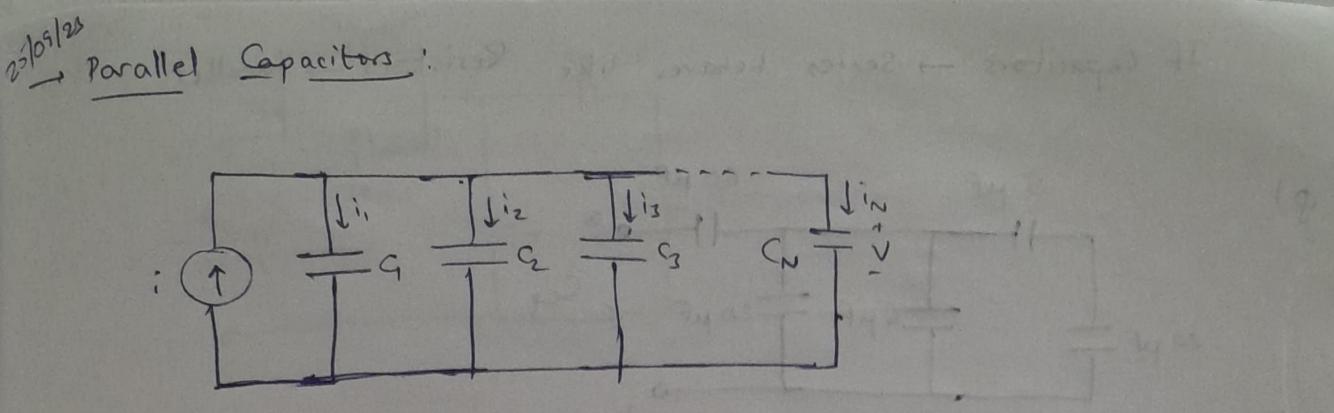Find Energy stored in the capacitors under DC conditions in the given figure.




$$i = i_1 + i_2 + i_3 + \dots + i_N$$



$$\Rightarrow i = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + \dots + C_N \frac{dV}{dt}$$

$$i = C_{eq} \cdot \frac{dV}{dt}$$
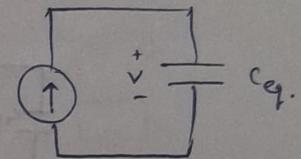
$$\Rightarrow \boxed{C_{eq} = C_1 + C_2 + C_3 + \dots + C_N}$$



→ Capacitors are in Series:

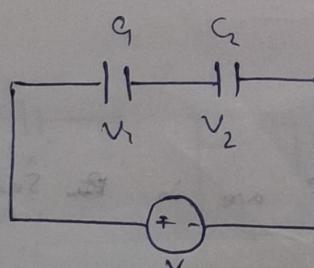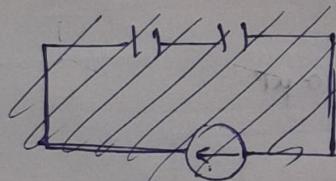

$$W_C = \frac{1}{2} C V^2$$

$$C = \frac{Q}{V}$$

$$\Rightarrow V = \frac{1}{C} \int i dt$$

$$i = C \frac{dV}{dt}$$

$$P = C V \cdot \frac{dV}{dt}$$

$$V = V_1 + V_2$$

$$\Rightarrow \frac{Q}{C_{eq}} = \frac{q_1}{C_1} + \frac{q_2}{C_2}$$


($q_1 = q_2 = q$)

$$[q_1 = q_2 = q]$$

$$\Rightarrow \boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$$


If Capacitors \rightarrow Series behaves like Resistors \rightarrow Parallel

Q)

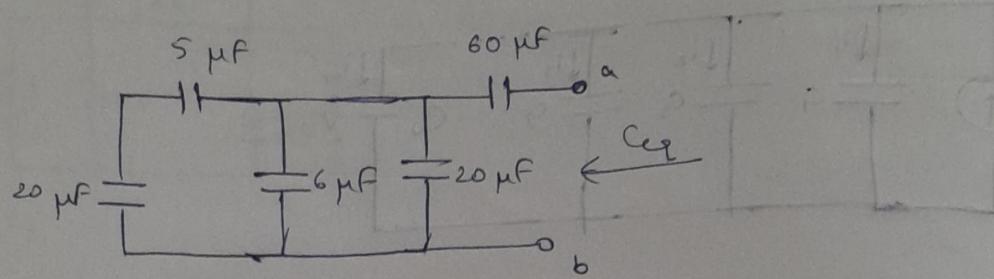


20 μF and 5 μF are in Series
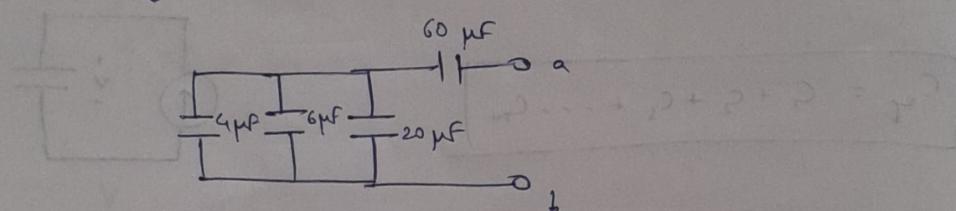
$$\frac{20 \times 5}{20 + 5} = \frac{100}{25} = 4 \mu\text{F}$$



4 μF , 6 μF and 20 μF \rightarrow Parallel

$$= 4 + 6 + 20 = 30 \mu\text{F}$$

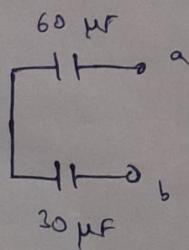


30 μF and 60 μF are in Series

$$\frac{30 \times 60}{30 + 60} = \frac{1800}{90} = 20 \mu\text{F}$$

$$C_{\text{eff}} = 20 \mu\text{F}$$

9)

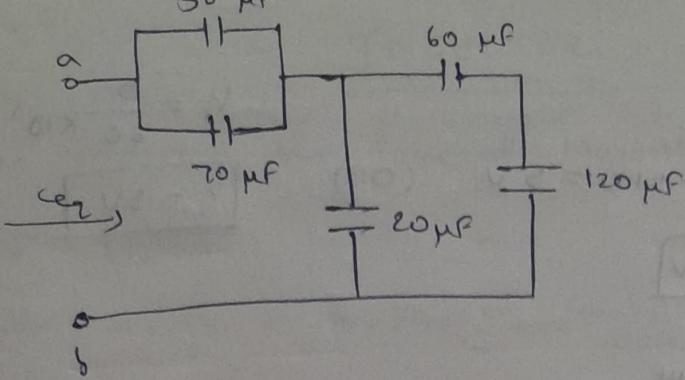


$$\boxed{V_2 = ?}$$

60 μF and 120 $\mu\text{F} \rightarrow$ Series

$$\frac{60 \times 120}{60+120} = \frac{7200}{180} = 40 \mu\text{F}$$

40 μF and 20 $\mu\text{F} \rightarrow$ Parallel

$$40 + 20 = 60 \mu\text{F}$$

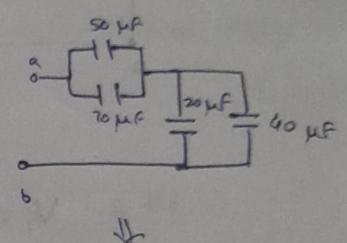


50 μF and 70 $\mu\text{F} \rightarrow$ Parallel

$$50 + 70 = 120 \mu\text{F}$$

Now 60 μF and 120 $\mu\text{F} \rightarrow$ Series

$$\frac{60 \times 120}{60+120} = 40 \mu\text{F}$$
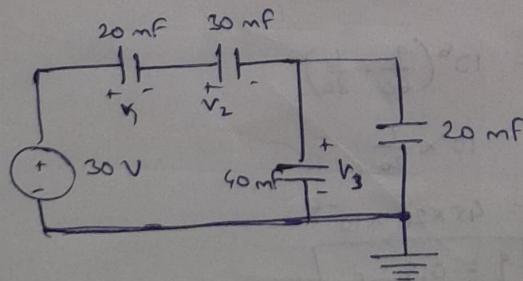
$$\boxed{\therefore C_{\text{eff}} = 40 \mu\text{F}}$$



$$\frac{20 \times 30}{50} = \frac{600}{50} = 12 \text{ mF}$$

20 mF and 40 mF \rightarrow Parallel

$$\Rightarrow 20 + 40 = 60 \text{ mF}$$

60 mF and $\frac{60}{5}$ mF \rightarrow Series
 $\Rightarrow 10 \text{ mF}$

$$\textcircled{1} \quad V_1 = \frac{q/C_1}{20} = \frac{0.3}{20} \times 10^3 \\ = 1.5 \times 10^2 = 15 \text{ V}$$

$$V_2 = \frac{q/C_2}{30} = \frac{0.3}{30} \times 10^3 = 10 \text{ V}$$

$$\textcircled{2} \quad q = CV \\ \Rightarrow q = 30 \times 10 \times 10^3 \\ = 0.3 \text{ C}$$

$$\boxed{\therefore q = 0.3 \text{ C}}$$

$$V = 20$$

$$V = V_1 + V_2 + V_3$$


$$\Rightarrow V_3 = 20 - (10 + 15) = 5 \text{ V} \quad (\text{OR})$$

$$V_1 = 5 \text{ V}$$

$$V_3 = \frac{0.3}{60} \times 10^3$$

$$V_3 = 5 \text{ V}$$

Q)

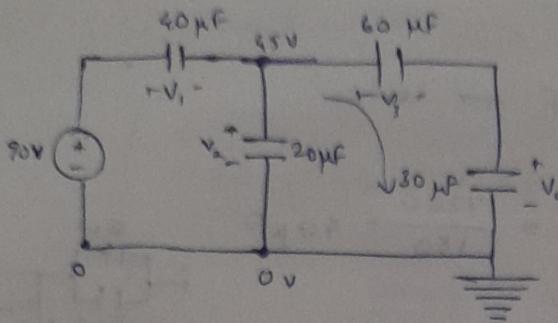

$$C_{\text{eff}} = 20 \mu\text{F}$$

$$q = CV$$

$$= 20 \times 90 \times 10^{-6}$$

$$\Rightarrow q = 1.8 \times 10^{-3} \text{ C}$$

$$q = 1.8 \text{ mC}$$

$$V_1 = \frac{1.8 \times 10^{-3}}{40 \times 10^{-6}}$$

$$= \frac{180}{40} \times 10^3$$


$$= \frac{180}{4} = 45 \text{ V}$$

$$\therefore V_1 = 45 \text{ V}$$

$$V_2 = 45 \text{ V}$$

$$V_3 = 15 \text{ V}$$

$$V_4 = 30 \text{ V}$$

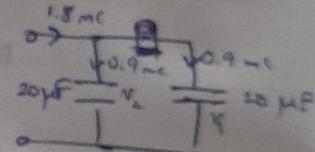

Using KVL:

$$45 - \frac{q}{60 \times 10^{-6}} - \frac{q}{30 \times 10^{-6}} = 0$$

$$45 = 10^6 \left(\frac{q}{60} + \frac{q}{30} \right)$$

$$= 10^6 \times \frac{q}{20}$$

$$q = 45 \times 20 \times 10^{-6}$$

$$q = 0.9 \text{ mC}$$

$$V_3 = \frac{0.9 \times 10^{-3}}{60 \times 10^{-6}} = 15 \text{ V}$$

$$V_4 = \frac{0.9 \times 10^{-3}}{30 \times 10^{-6}} = 30 \text{ V}$$

INDUCTORS :

→ Stores Energy in the form of Magnetic field.

~~Inductor consists~~

→ Inductor consists of a coil of conducting ~~wire~~-wire.

Conductor.

Measured in 'H'

$$V = L \frac{di}{dt}$$

Constant of proportionality called the Inductance of Inductor.

(length)

↔ l




A (Cross sectional Area)

No. of turns of a coil = N

$$L = \frac{N^2 \mu A}{l}$$

Inductance of any
Inductor

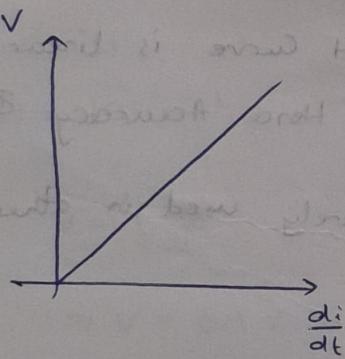

(Linear Inductor)

$\mu = \mu_0 \mu_r$
↓
Relative Permeability

Absolute Permeability

$$\left[\begin{array}{l} \mu_0 = 4\pi \times 10^{-7} \text{ Vs/A} \\ \mu_r = 1 \text{ for air} \end{array} \right]$$

If current does not change with time,

{ (V=∞) Capacitor → Open Circuited

(V=0) Inductor → Short Circuited

μH → Communication System

H → Power Systems

(Under DC situation,
V=0 for Inductor)

→ Inductor

→ Air Core Inductor

→ Iron core Inductor

26/09/21

Core → Made up of Ferromagnetic Material

Coil → Made up of Conducting material


Core is wounded over by the coil.

This system → Inductor.

Conductor

coil


Inductor:

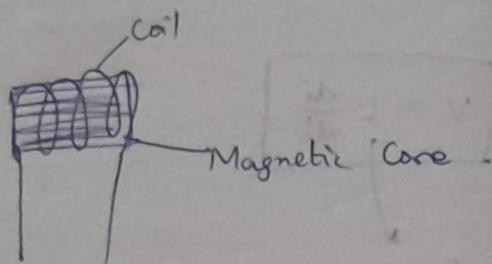

Air Core Inductors are used to make Ammeters and Voltmeters, so that BH Curve is linear and Saturation reduces and Hence Accuracy Increases.


But Air core Inductors are rarely used in other cases.

Symbol:

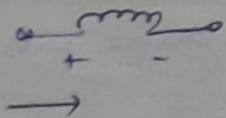

$$V = L \cdot \frac{di}{dt}$$

Voltage across the
~~coiled~~ Inductor

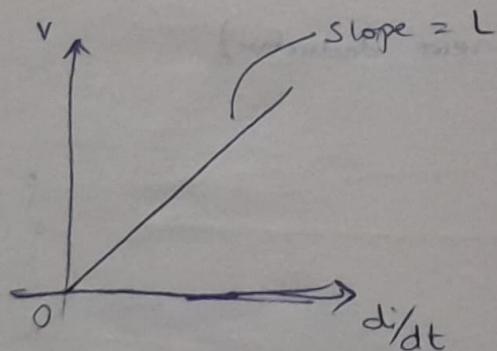

$$i = \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau$$

Current through
the Inductor

$$W = \frac{1}{2} L i^2$$

Energy stored in the
Inductor

$$V_L = L \frac{di}{dt}$$

$$\cdot i_L = \frac{1}{L} \int v dt$$

$$P = i_C \cdot V_L$$

$$\int P dt = W = \frac{1}{2} L i^2$$

Capacitors resist sudden change in Voltage.

Inductors resist sudden change in Current.

Resistors resist ~~sudden~~ flow of steady current.

Ideal Inductors do not dissipate power in form of heat. But it is otherwise in real Inductors.

Q) $L = 0.1 \text{ H}$

$$i(t) = 10t e^{-st} \text{ A}$$

Sol : $V = L \frac{di}{dt}$

$$\Rightarrow V = 0.1 \times 10 (se^{-st} - st e^{-st})$$

$$\cancel{\boxed{V = -4e^{-st} (1 - st) \text{ Volts}}}$$

$$\Rightarrow \boxed{V = e^{-st} (1 - st) \text{ Volts}}$$

$$W = \frac{1}{2} \times 0.1 \times (10t e^{-st})^2$$

~~Ans~~

$$\boxed{W = 5t^2 e^{-10t} \text{ J}}$$

g) Find i through 5H Inductor

$$V(t) = \begin{cases} 10t^2, & t > 0 \\ 0, & t < 0 \end{cases}$$

Find Energy stored at $t=5s$. Assume $i(v) > 0$

$$\begin{aligned} i &= \frac{1}{L} \int_{-\infty}^t V(t) dt & V = L \frac{di}{dt} \\ &= \frac{1}{5} \left(\int_{-\infty}^0 0 dt + \int_0^5 30t^2 dt \right) & \Rightarrow di = \frac{1}{L} V dt \\ &= \frac{1}{5} \int_0^5 30t^2 dt & \Rightarrow i = \int_L^t \frac{1}{L} V dt \\ &= \frac{1}{5} (15 \times 5^3) \Rightarrow i = 2 \times 125 A & = \frac{1}{L} \int_{-\infty}^t V dt \end{aligned}$$


$$W = \frac{1}{2} \times 5 \times (250)^2 \quad [As \quad V(t) = 0 \quad \forall t < 0]$$

$$= \frac{1}{2} \times 5 \times 250 \times 250$$


$$W = 156.25 \text{ kJ}$$

$$W]_0^5 = \frac{1}{2} Li^2 - \frac{1}{2} L(i_0)^2$$

→ Inductors in Series :

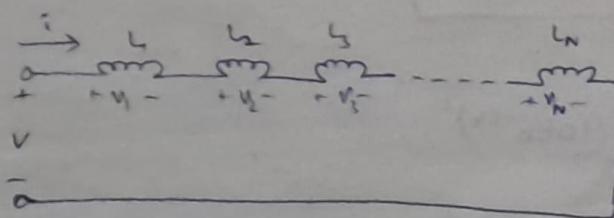

Let us study only Two Inductors:

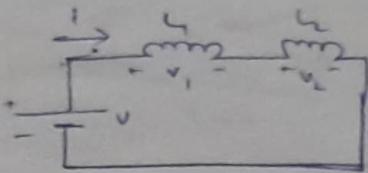

According to KVL:

$$V = V_1 + V_2$$

$$\Rightarrow V = L_1 \cdot \frac{di}{dt} + L_2 \cdot \frac{di}{dt}$$

$$\therefore L_{eq} = L_1 + L_2$$

$$\text{Let } V = L_{eq} \frac{di}{dt}$$


$$\therefore \rightarrow L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$

for N Inductors,


$$L_{eq} = \sum_{i=1}^N L_i$$

$$\text{i.e. } L_{eq} = L_1 + L_2 + L_3 + \dots + L_N$$

→ Inductors in Parallel:

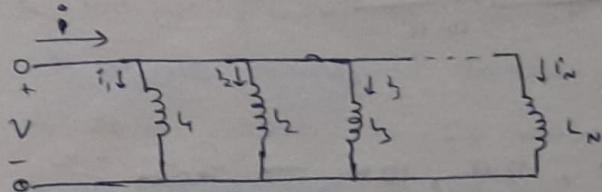

Let us consider only two Inductors:

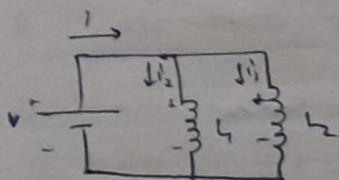

According to KCL:

$$i = i_1 + i_2$$

$$\Rightarrow \frac{1}{L_1} \int_v dt + \frac{1}{L_2} \int_v dt = i$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\text{Let } i = \frac{1}{L_{eq}} \int_v dt$$

$$\Rightarrow \frac{1}{L_{eq}} \int_v dt = \frac{1}{L_1} \int_v dt + \frac{1}{L_2} \int_v dt$$

For N Inductors,


$$L_{eq} = \left(\frac{1}{\sum_{i=1}^n \frac{1}{L_i}} \right)^{-1}$$

i.e., $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_n}$

Series combination of Resistors is similar to that of
N Inductors &

Parallel combination of Resistors is similar to that of
N Inductors

Q) Find L_{eq}

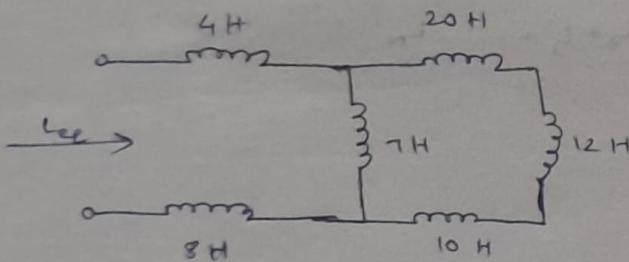

20H, 12H, 10H \rightarrow series

$$\therefore 42H$$


42H and 7H \rightarrow Parallel

$$\therefore 6H$$


4H, 6H and 8H \rightarrow Series

$$\therefore L_{eq} = 18H$$


Q)

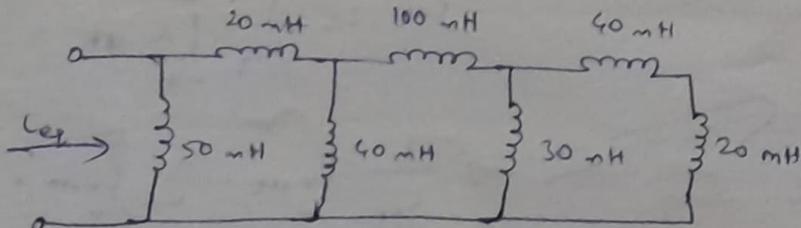

Ans : 25 mH

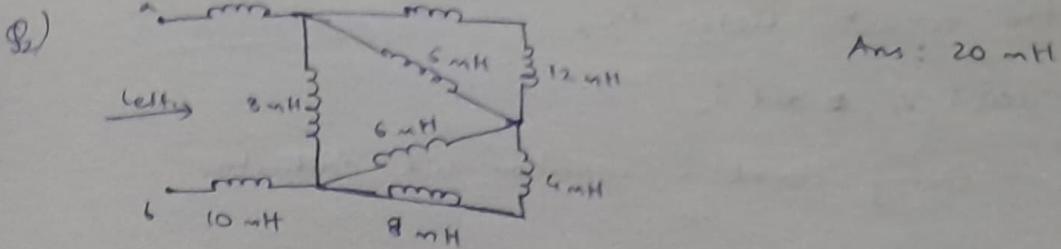

Q₂)

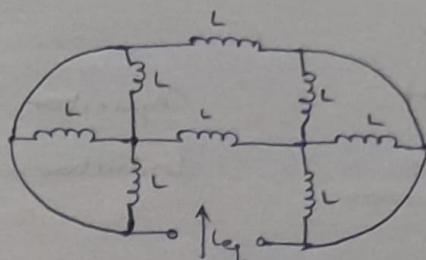

~~Ans: 20 mH~~

Ans: $\left(\frac{\Sigma}{3}\right) L$

A₁)

$$\begin{aligned}
 & 20 \text{ mH} \text{ & } 40 \text{ mH} \text{ series} \Rightarrow 60 \text{ mH} \\
 & 60 \text{ mH} \text{ & } 30 \text{ mH} \text{ parallel} \Rightarrow 20 \text{ mH} \\
 & 20 \text{ mH} \text{ & } 100 \text{ mH} \text{ series} \Rightarrow 120 \text{ mH} \\
 & 120 \text{ mH} \text{ & } 40 \text{ mH} \text{ parallel} \Rightarrow 30 \text{ mH} \\
 & 30 \text{ mH} \text{ & } 20 \text{ mH} \text{ series} \Rightarrow 50 \text{ mH} \\
 & 50 \text{ mH} \text{ & } 50 \text{ mH} \text{ parallel} \Rightarrow \underline{25 \text{ mH}}
 \end{aligned}$$

Q₂)

A₂)

$$\begin{aligned}
 & 8 \text{ mH} \text{ & } 12 \text{ mH} \text{ series} \Rightarrow 20 \text{ mH} \text{ (up)} \\
 & 4 \text{ mH} \text{ & } 8 \text{ mH} \text{ series} \Rightarrow 12 \text{ mH} \text{ (down)}
 \end{aligned}$$

$$20 \text{ mH} \text{ & } 5 \text{ mH} \text{ parallel} \Rightarrow 4 \text{ mH}$$

$$12 \text{ mH} \text{ & } 6 \text{ mH} \text{ parallel} \Rightarrow 4 \text{ mH}$$

$$4 \text{ mH} \text{ & } 4 \text{ mH} \text{ series} \Rightarrow 8 \text{ mH}$$


$$8 \text{ mH} \text{ & } 8 \text{ mH} \text{ parallel} \Rightarrow 4 \text{ mH}$$

$$4 \text{ mH}, 6 \text{ mH} \text{ & } 10 \text{ mH} \text{ series} \Rightarrow \underline{20 \text{ mH}}$$


Q7 Consider the circuit. Under DC,

Find (a) i , V_C , ϕ and i_L

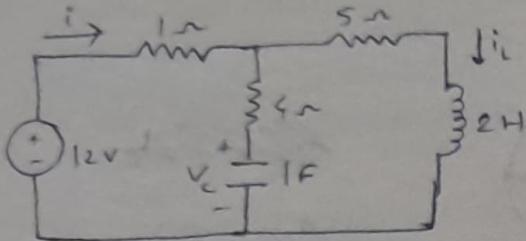(b) Energy stored in Capacitor and Inductor



Capacitor - Open
Inductor - Close

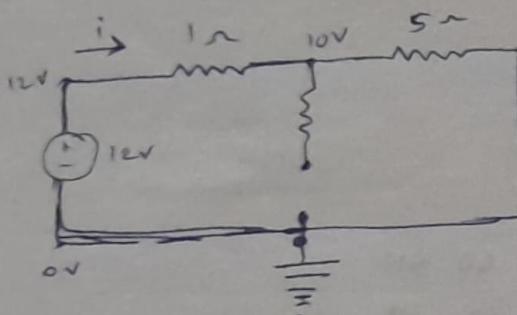

$$i = \frac{12}{6} = 2 \text{ A}$$

$$V_C = 10 \text{ V}$$

$$i_L = i = 2 \text{ A}$$

$$E_{\text{Cap.}} = \frac{1}{2} CV^2$$

$$W_{\text{ind.}} = \frac{1}{2} Li^2$$




$$= \frac{1}{2} \times 1 \times 10^2$$

$$= \frac{1}{2} \times 2 \times 4$$

$$\Rightarrow E_{\text{Cap.}} = 50 \text{ J}$$

$$\Rightarrow E_{\text{ind.}} = 4 \text{ J}$$

(g)

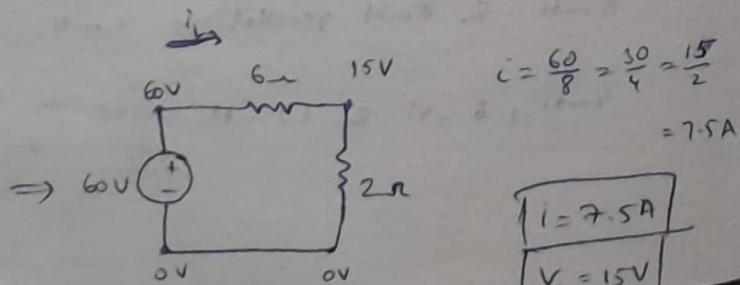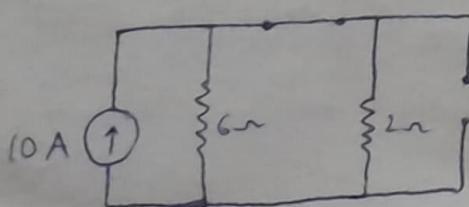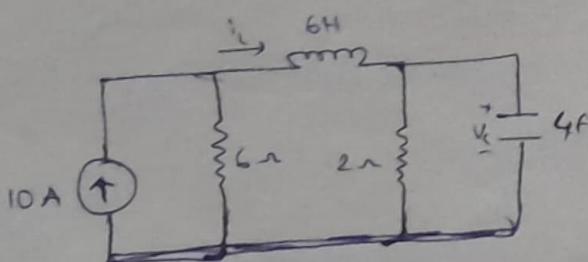

$$V_C = 15V$$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 15 \times 15 \times 4$$




$$E = 450J$$

$$E_{ind} = \frac{1}{2} Li^2$$

$$= \frac{1}{2} \times 6 \times \frac{15^2}{4}$$

$$E_{ind} = 168.75 J$$

Q)

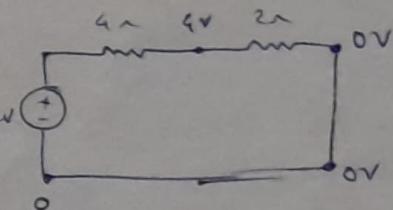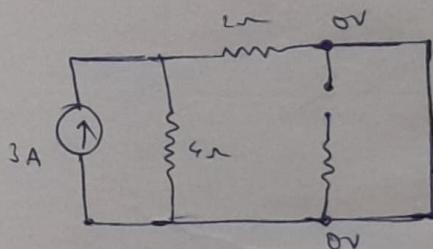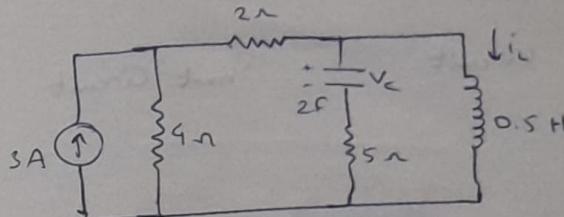

$$i = \frac{12}{6} = 2A$$

$$V_C = 0V \Rightarrow W_C = 0J$$

$$i = 2A$$



$$W_L = \frac{1}{2} \times \frac{1}{2} \times 4 = 1J$$

$$W_L = 1J$$

Relation

V - I

Resistor (R)

$$V = iR$$

Capacitor (C)

$$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

Inductor (L)

$$V = L \frac{di}{dt}$$

I - V

$$i = \frac{V}{R}$$

$$i = C \cdot \frac{dv}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

P or W

$$P = i^2 R = \frac{V^2}{R}$$

$$W = \frac{1}{2} C V^2$$

$$W = \frac{1}{2} L i^2$$

Series

$$R_{eq} = R_1 + R_2$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$L_{eq} = L_1 + L_2$$

Parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$C_{eq} = C_1 + C_2$$

$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

At DC :

Same

Open Circuit

Short Circuit

Circuit

variable

that cannot

; None

change

abruptly

V

i


CHAPTER-7 : FIRST-ORDER CIRCUITS

→ Excitation :

- (i) No External Source : (Source Free Response)
Initial Energy stored in Capacitor or Inductor.

(ii) External Source

→ Source free RC Circuits

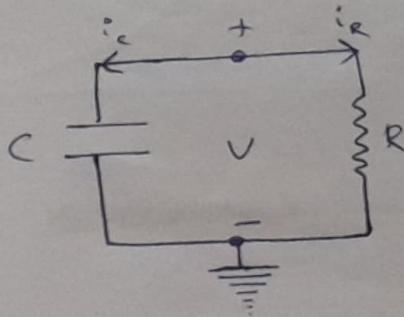

Response is Voltage across the capacitor,
 $v_c(t)$

Apply KCL at + Node :

$$i_R + i_c = 0$$

~~$$\frac{V_R}{R} + C \cdot \frac{dV}{dt} = 0$$~~

$$\Rightarrow \boxed{\frac{V_R}{R} + C \cdot \frac{dV}{dt} = 0}$$

Assume Initial Voltage across the Capacitor $v_0 = v(0)$
[$@t=0$]

$$\Rightarrow C \cdot \frac{dV}{dt} = -\frac{V_R}{R}$$

$$W_0 = \frac{1}{2} C V_0^2$$

$$\Rightarrow \frac{dV}{dt} = -\frac{V_R}{RC}$$

$$\Rightarrow dV = -\frac{V_R}{RC} dt$$

$$\Rightarrow \int_{V_0}^V dV = \int_0^t -\frac{V_R}{RC} dt$$

$$\Rightarrow \int_{V_0}^V \frac{-1}{V} dV = \int_0^t \frac{1}{RC} dt$$

$$\Rightarrow \int_V^{V_0} \frac{1}{V} dV = \int_0^t \frac{1}{RC} dt$$

$$= \frac{t}{RC}$$

$$\Rightarrow \ln(V_0) - \ln|V| = \frac{t}{RC}$$


$$\Rightarrow \ln\left(\left|\frac{V_0}{V}\right|\right) = \frac{t}{RC}$$

$$\Rightarrow \ln\left(\frac{V}{V_0}\right) = \frac{-t}{RC}$$

$$\rightarrow \frac{V}{V_0} = e^{-\frac{t}{RC}}$$

$$\Rightarrow V = V_0 \cdot e^{-\frac{t}{RC}}$$

$$V(t) = V_0 \cdot e^{-\frac{t}{RC}}$$

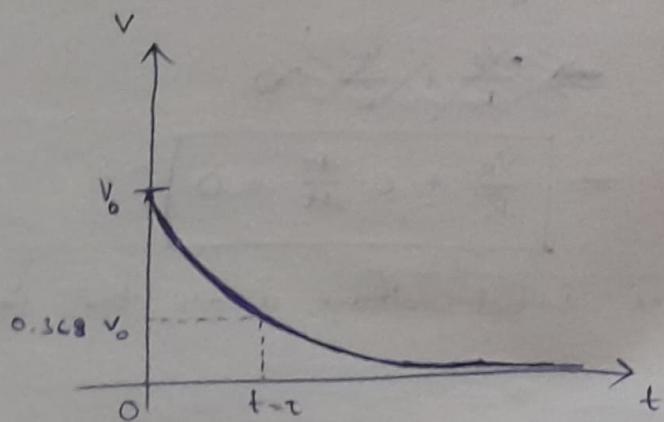

$RC \rightarrow$ Time Constant (τ)

$$RC = \tau$$

$$V_t = V_0 e^{-\frac{t}{\tau}}$$

$$\begin{aligned} @ t = \tau, \\ V(t) &= V_0 \cdot e^{-\frac{\tau}{\tau}} \\ &= V_0 \cdot e^{-1} \\ &= 0.368 V_0 \\ &= (36.8\%) V_0 \end{aligned}$$

V decays faster for small T &
 v decays slower for large T .

If no. of Resistors are parallel with C ,


$$\boxed{T = R_{\text{eq}} \cdot C}$$

$$i_R(t) = \frac{V(t)}{R} = \frac{V_0}{R} e^{-t/T}$$

$$P(t) = V i_R = \frac{V_0^2}{R} e^{-2t/T}$$

$$W_R(\infty) \rightarrow \frac{1}{2} C V_0^2$$

Q) Let $V_C(0) = 15 \text{ V}$

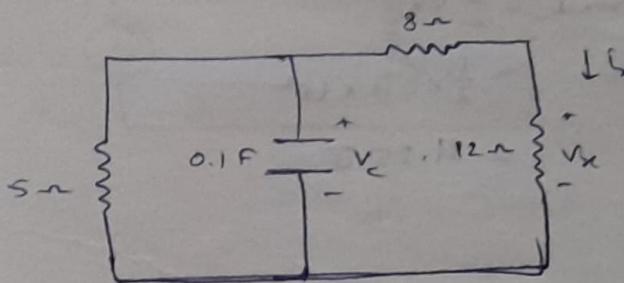

Find V_C , V_x and i_x for $t > 0$

8 ohms and 12 ohms are in Series $\Rightarrow 20 \text{ ohms}$

20 ohms and 5 ohms are in Parallel $\Rightarrow \frac{20 \times 5}{25} = 4 \text{ ohms}$

$$R_{\text{eff}} = 4 \text{ ohms}$$

$$T = 4 \times 0.1 = 0.4 \text{ s}$$

$$\boxed{V_C(t) = 15 \times e^{-t/0.4}}$$

$$\boxed{V_R(t) = 15 e^{-t/0.4} \text{ V}} \quad (\text{across } 20 \text{ ohm Resistor})$$

$$V_{12A} = \frac{V \times 12}{20}$$

$$\Rightarrow V_x = 15 \times e^{-\frac{t}{0.4}} \times \frac{12}{20}$$

$$V_x = 9 e^{-\frac{t}{0.4}} V$$

$$i_x = \frac{V_x(t)}{R} = \frac{9e^{-\frac{t}{0.4}}}{12}$$

$$= \frac{3}{4} e^{-\frac{t}{0.4}}$$

$$i_x = \frac{3}{4} e^{-\frac{t}{0.4}} A$$

$$\text{Initial Energy Stored} = \frac{1}{2} C V^2$$


$$= \frac{1}{2} \times 0.1 \times 15^2$$

$$= 11.25 J$$


(q) Switch has been closed for a long time, and opened at $t=0$.

Find $v(t)$ for $t \geq 0$. Calculate Initial Energy stored in the capacitor.

(i) For $t < 0$:

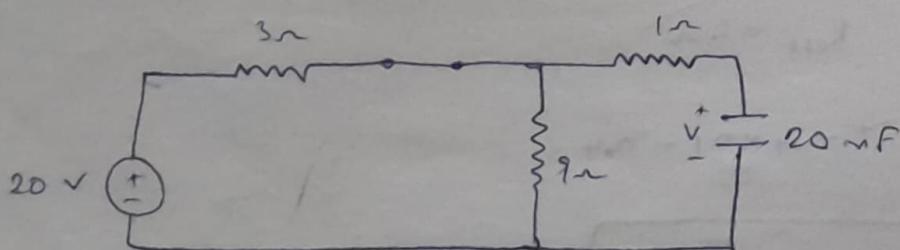

Capacitor \rightarrow Open Circuited

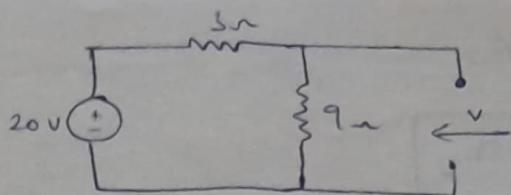

$$V_{9\text{ ohm}} = 15 \text{ V}$$


$$V = \frac{20 \times 9}{3 + 9} = \frac{180}{12} = \frac{60}{4} = 15 \text{ V}$$

$$\Downarrow V_o = 15 \text{ V}$$


$$V = 15 \text{ V}$$

$$V(t) = 15 \text{ V}$$

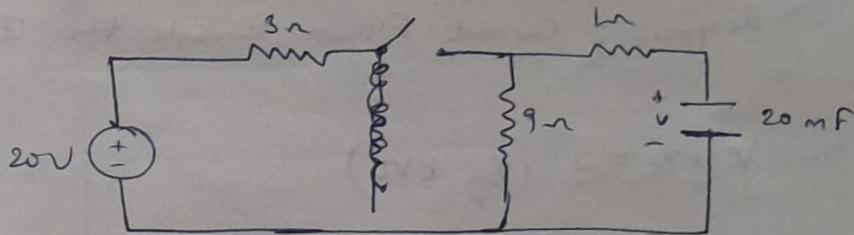(ii) At $t=0$, Voltage cannot be changed inst. for cap.



$$V_c = V_o = 15 \text{ V}$$

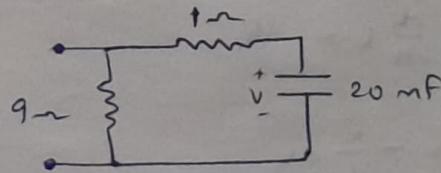


$$W = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 20 \times 10^{-3} \times 15^2$$

$$W = 2.25 \text{ mJ}$$

(iii) A' for $t > 0$,

switch is open

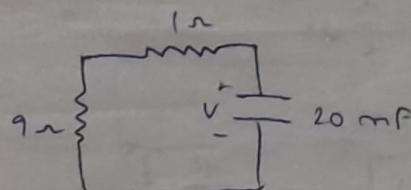

$$R_{\text{eff}} = 10 \text{ ohm}$$


$$t = 10 \times 20 \times 10^{-3}$$

$$t = 0.2 \text{ s}$$

$$\therefore V_o = -15e^{-t/0.2}$$

$$V_o = -15e^{-5t} \text{ V}$$

→ Source free RL Circuits :

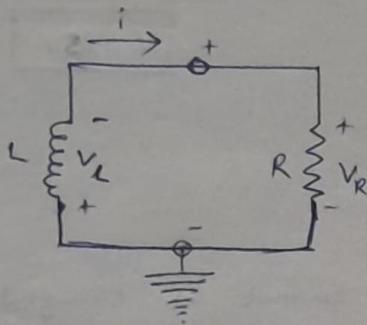

Response : Current flows through the Inductor

$$V_L + V_R = 0 \quad (\text{By KVL})$$

$$\Rightarrow L \frac{di}{dt} + iR = 0$$

$$\Rightarrow \cancel{\frac{d}{dt}} \frac{di}{dt} L = -iR$$

$$\Rightarrow \frac{di}{i} = -\frac{R}{L} dt$$

At $t=0$, let initial ~~current~~ Current flow through the Inductor, $i(0) = i_0$

$$\text{Initial Energy Stored} = W_0 = \frac{1}{2} L i_0^2$$

$$\int_{i_0}^i \frac{di}{i} = \int_0^t -\frac{R}{L} dt$$

$$\Rightarrow \left[\ln(i) \right]_{i_0}^i = -\left[\frac{R}{L} t \right]_0^t$$

$$\Rightarrow \ln\left(\frac{i}{i_0}\right) = -\frac{R}{L}t$$

$$\Rightarrow \frac{i}{i_0} = e^{-R_L t}$$

$$\Rightarrow i = i_0 \cdot e^{-R_L t}$$



$$\boxed{i = i_0 \cdot e^{-\frac{Rt}{L}}}$$

$$i = i_0 \cdot e^{-t/(L/R)}$$

$$\boxed{i = i_0 \cdot e^{-t/\tau}}$$

$$\boxed{\tau = L/R}$$

$$\boxed{R \rightarrow R_{cap}}$$

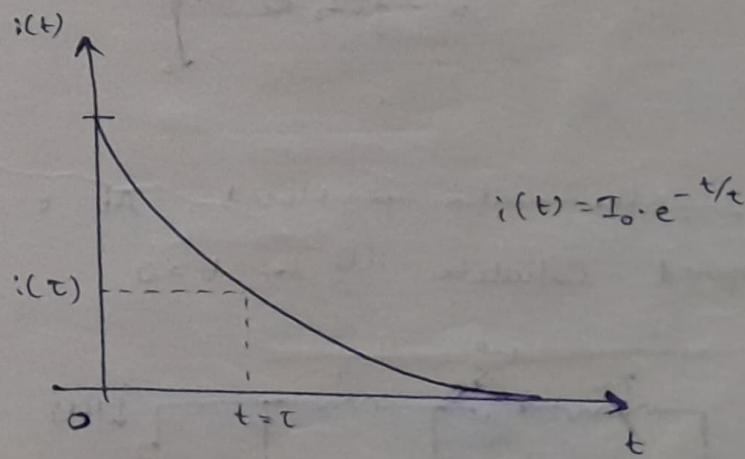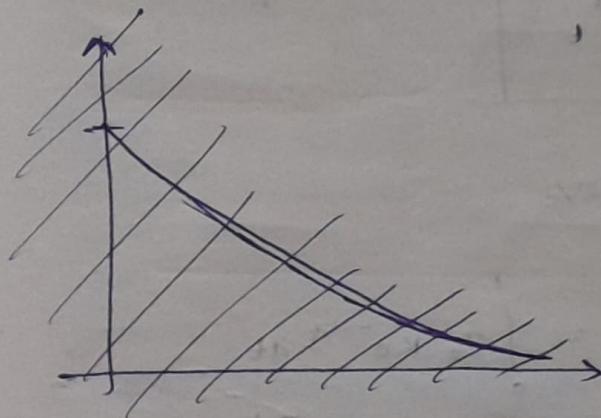

$$t = \tau \Rightarrow i_0 = I_0 e^{-1}$$

$$\boxed{i_\tau = 0.368 I_0}$$


$\tau \rightarrow \text{large} : \text{Slow Decay}$
 $\tau \rightarrow \infty \text{ small} : \text{Fast Decay}$

Comparison between RC and a RL Circuit

RL

$$(i) i(t) = I_0 e^{-\frac{t}{\tau}}$$


$$\tau = \frac{L}{R}$$

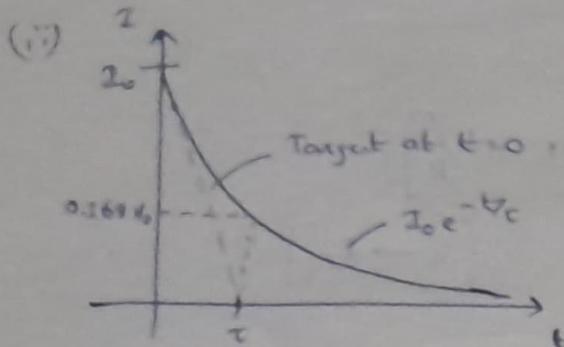

RC

$$V(t) = V_0 e^{-\frac{t}{\tau}}$$

$$\tau = RC$$

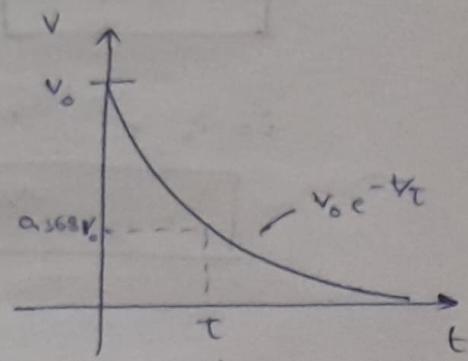


$$P = V_R i = I_0^2 R e^{-2\frac{t}{\tau}}$$



$$W_R(t) = \int_0^t P dt = \int_0^t I_0^2 R e^{-2\frac{t}{\tau}} dt$$

$$= -\frac{1}{2} \tau I_0^2 R e^{-2\frac{t}{\tau}} \Big|_0^t \quad \left[\tau = \frac{L}{R} \right]$$

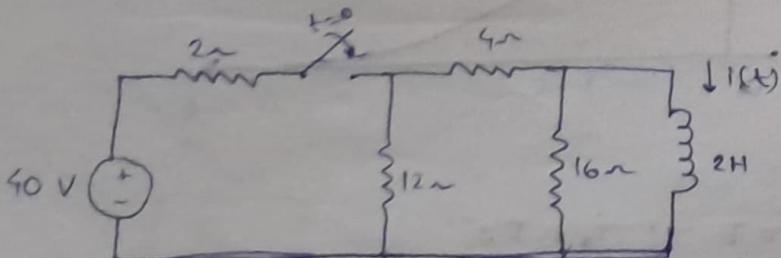- g) When $t < 0$, the switch is closed. At $t=0$, the switch is opened. Calculate $i(t)$ for $t > 0$



(a) $t < 0 \rightarrow$ Switch is closed

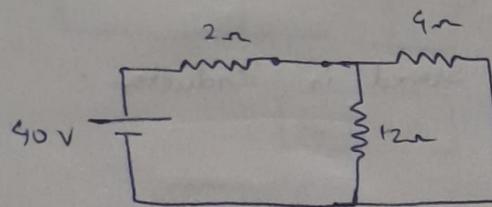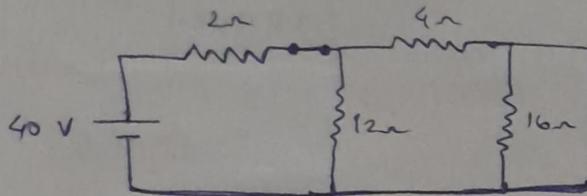


$$(4\Omega \parallel 12\Omega) + 2\Omega = 3\Omega + 2\Omega = 5\Omega$$

$$i_{4\Omega} = \frac{12 \times 8}{12+4} = \frac{12 \times 8}{16} = 6 \text{ A}$$

$$i_{\text{total}} = \frac{40}{5} = 8 \text{ A}$$

$$i_{4\Omega} = i_L = 6 \text{ A}$$


(b) $t = 0 \rightarrow$ Switch is opened

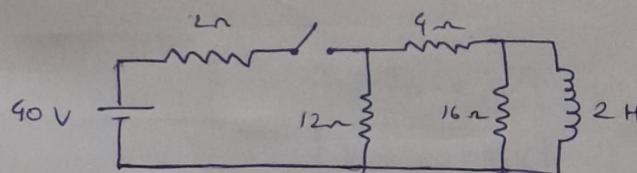

$$i_L = 6 \text{ A} = i_o$$

$$\boxed{i_o = 6 \text{ A}}$$

(c) $t > 0$

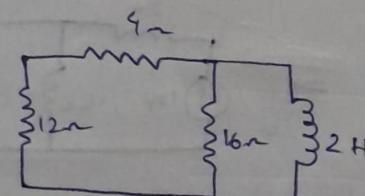

~~Given~~

$$4\Omega + 12\Omega = 16\Omega$$

$$16\Omega \parallel 16\Omega = 8\Omega$$

$$\boxed{R_{eq} = 8\Omega}$$

$$\tau = L/R = 2/8 = \frac{1}{4} \text{ s}$$

$$i = i_0 \cdot e^{-t/\tau}$$

$$\Rightarrow i = 6 \cdot e^{-4t}$$

$$i(t) = 6e^{-4t} \text{ A}$$


Calculate Initial Energy stored in Inductor:

$$W_0 = \frac{1}{2} L i_0^2$$

$$\Rightarrow W_0 = \frac{1}{2} \times 2 \times (6)^2$$

$$W_0 = 36 \text{ J}$$




Q)

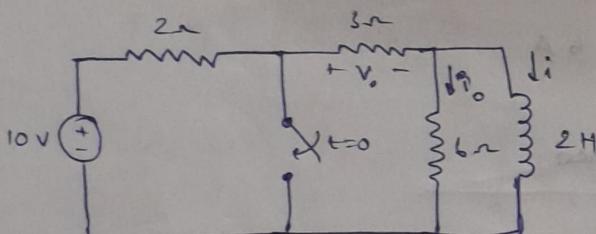


find i, i_0, v_0

Assuming Switch was open for a long time

for $t < 0$:

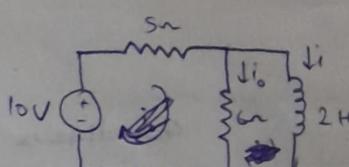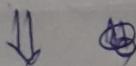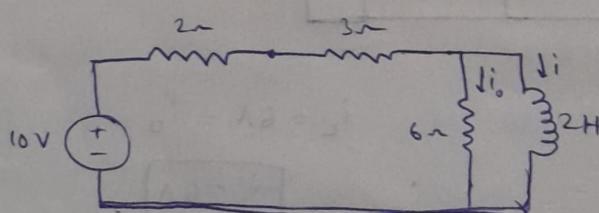

\Rightarrow

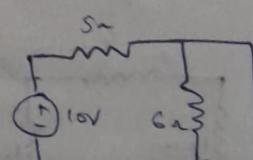

$$i = 2 \text{ A}$$


$$i_0 = 0 \text{ A}$$

$$V_o(t) = 3(i(t)) = 3 \times 2 = 6 \text{ V} \quad \text{for } t < 0$$

$$[i_0 = 2 \text{ A}]$$


$$[V_o = 6 \text{ V}]$$

For $t = 0^+$

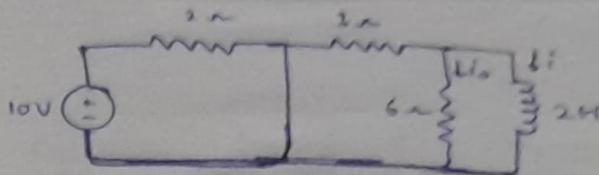


$$[i_0 = 2 \text{ A}]$$

For $t > 0^+$

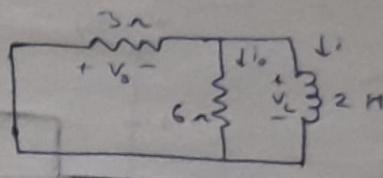

$$R_{eq} = 2 \text{ ohm}$$

$$\tau = L/R = 2/2 = 1 \text{ s}$$

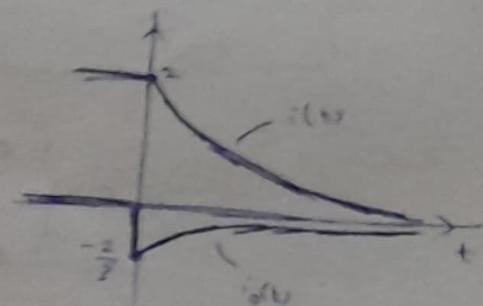

$$I = I_0 \cdot e^{-t/\tau}$$

$$[I = 2 e^{-t} \text{ A}]$$

$$W_0 = \frac{1}{2} L i_0^2$$

$$\Rightarrow W_0 = \frac{1}{2} \times 2 \times 2^2$$

$$[W_0 = 4 \text{ J}]$$

$$V_o(t) = -V_L = -L \cdot \frac{di}{dt}$$

$$= -2(-2e^{-t})$$

$$[V_o(t) = 4e^{-t}]$$

$$i_o(t) = \frac{V_L}{L}$$


$$[i_o(t) = -\frac{2}{3} e^{-t} \text{ A}]$$

→ Unit-Step function


$$\forall t < 0, u(t) = 0$$

$$\forall t > 0, u(t) = 1$$

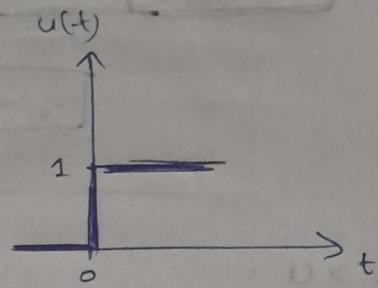
$$u(t) = \begin{cases} 0, & t < 0 \\ 1, & t > 0 \end{cases}$$


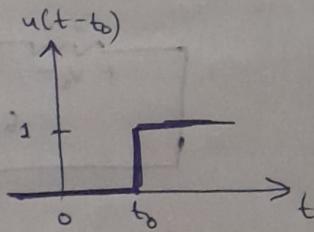
$$u(t-t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$





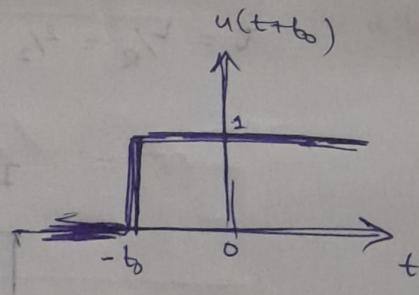
$$u(t+t_0) = \begin{cases} 0, & t < -t_0 \\ 1, & t > -t_0 \end{cases}$$




Represent as Abrupt Source :


(i) Voltage Source

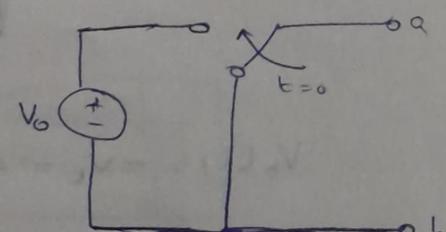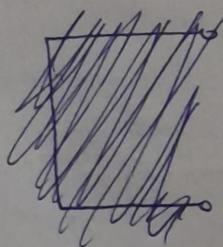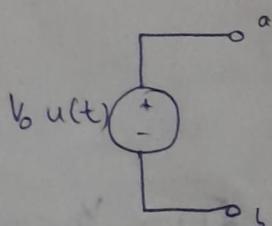

(ii) Current Source

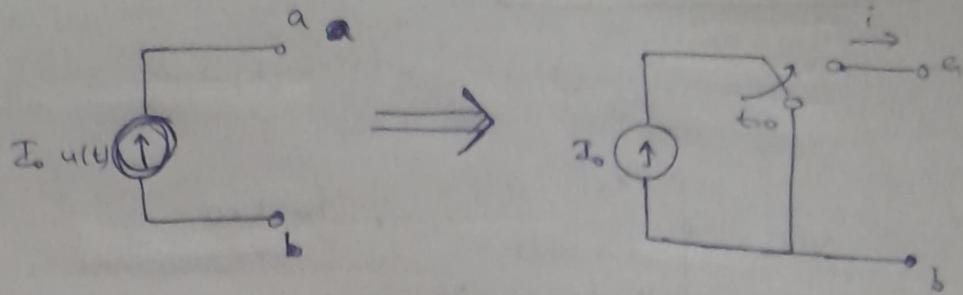


→ Step Response of an RC Circuit

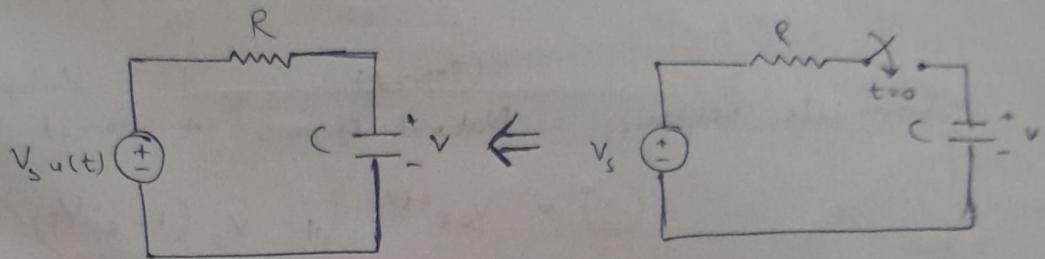

Applying KVL :

$$V(0^-) = V(0^+) = V_0$$

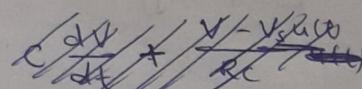

$$C \frac{dv}{dt} + \frac{v - V_s u(t)}{R} = 0$$

$$\frac{dv}{dt} = - \frac{v - V_s u(t)}{RC}$$

$$[u(t) = 1]$$

$$\frac{dv}{v - V_s} = - \frac{dt}{RC}$$

$$\Rightarrow \ln |v - V_s| \Big|_{V_0}^{V(t)} = - \left[\frac{t}{RC} \right]_0^t$$

$$\Rightarrow \ln (v(t) - V_s) - \ln (V_0 - V_s) = - \frac{t}{RC}$$

$$\Rightarrow \ln \left(\frac{v - V_s}{V_0 - V_s} \right) = - \frac{t}{RC}$$

$$\Rightarrow \frac{v - V_s}{V_0 - V_s} = e^{-t/\tau} \quad [\tau = RC]$$

$$V(t) = V_s + (V_0 - V_s)e^{-t/\tau} \quad \text{for } t > 0$$

$$V(t) = \begin{cases} V_0 & , \text{ for } t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & , \text{ for } t > 0 \end{cases}$$

V_s : Final Value at $t \rightarrow \infty$

$$\begin{aligned} \text{Complete Response} &= \underset{\substack{\text{(Stared)} \\ \text{Natural Response}}}{\text{Natural Response}} + \underset{\substack{\text{(Independent)} \\ \text{Forced Response}}}{\text{Forced Response}} \\ &= V_0 e^{-t/\tau} + V_s (1 - e^{-t/\tau}) \end{aligned}$$

$$\text{Complete Response} = \underset{\substack{\text{[Temporary]} \\ \text{Transient Response}}}{\text{Transient Response}} + \underset{\substack{\text{[Permanent]} \\ \text{Steady-State Response}}}{\text{Steady-State Response}}$$

$$V(t) = V_\infty + [V(0^+) - V(\infty)] e^{-t/\tau}$$

$$[V(0^+) = V(0^-) = V_0]$$

The complete Response :

Independent Response \Rightarrow Forced Response \rightarrow Steady State Response
 $\qquad\qquad\qquad$ (Permanent)

Transient Response \rightarrow Temporary Response



Step Response of RL Circuit

$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau} u(t)$$

Initial Current: $i(0^-) = i(0^+) = i(0) = I_0$

Final Current: $i_\infty = V_s/R$

$$\tau = L/R$$

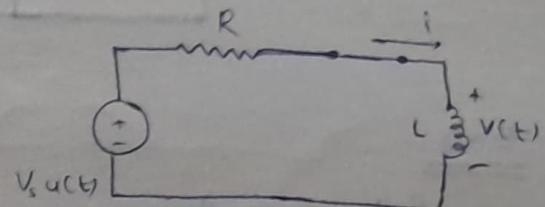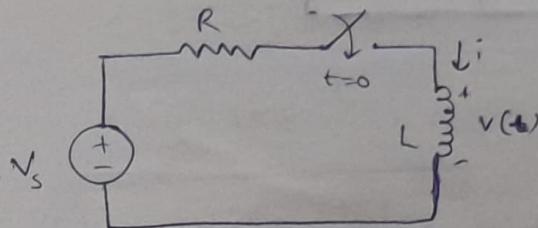

~~Exponential Decay~~

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$

↴ Natural Response (Temporary)
 (Transience)

↴ Steady State Response
 (Permanent)

Three steps to find out step response of RL circuit:

(i) Find Initial Inductor Current

$$i(0) \text{ at } t = 0^+$$


(ii) Find Final Inductor Current

$$I_\infty = V_s/R$$

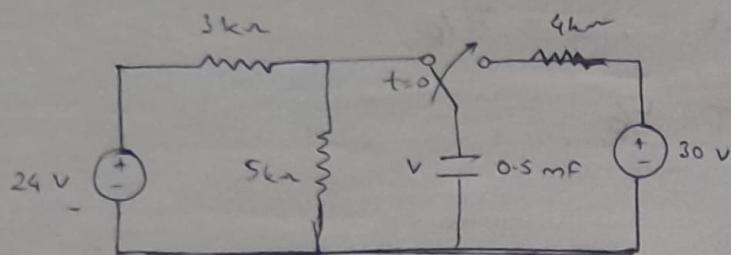(iii) Find Time Constant


$$\tau = L/R_{eq}$$

Q) The switch in the figure has been in Position A for a long time. At $t=0$, the switch moves to B. Determine $v(t)$ for $t > 0$ and calculate its value at $t = 1\text{s}$ and 4s .



$t < 0$:

Switch is in A :

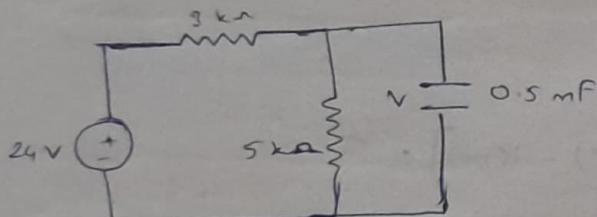



$$V_{cap} = V_{5k\Omega} = \frac{24 \times 5}{5+3} = 15 \text{ V}$$

$$V_{cap.} = V(0^-) = 15 \text{ V}$$

$t = 0$:

$$V(0^-) = V(0^+) = V(0) = V_0 = 15 \text{ V}$$

$t > 0$:

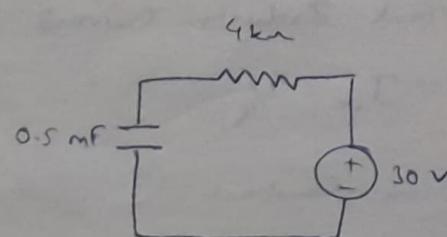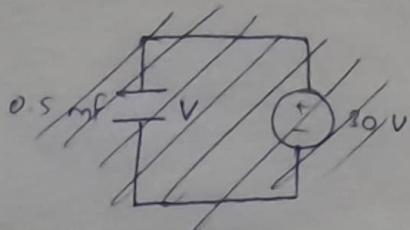

$$\tau = RC$$

$$\cancel{t = 0.5 \times 10^{-1}}$$

$$T = RC = 4 \times 10^{-3} \times \frac{1}{2} \times 10^3 = 2 \text{ s}$$

$$\boxed{T = 2 \text{ s}}$$

$$\boxed{V_\infty = 30 \text{ V}}$$

$$\begin{aligned}V_t &= V(\infty) + [V(0^+) - V(\infty)] e^{-t/T} \\&= 30 + (15 - 30) e^{-t/2} \\&= 30 - 15 e^{-t/2}\end{aligned}$$


$$\boxed{V_t = 15(2 - e^{-t/2}) \text{ V}}$$

$$V(1) = 15(2 - e^{-1/2}) = 20.9 \text{ V}$$


$$V(4) = 15(2 - e^{-2}) = 27.97 \text{ V}$$

Q) find $i(t)$


Assume switch is closed since long time

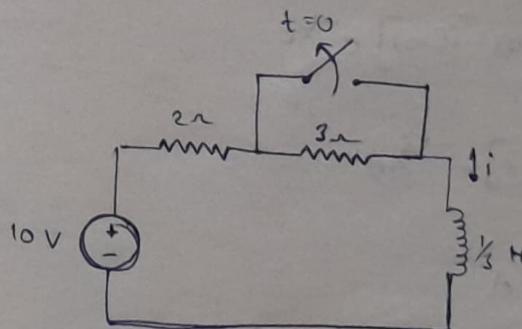

$t < 0$:

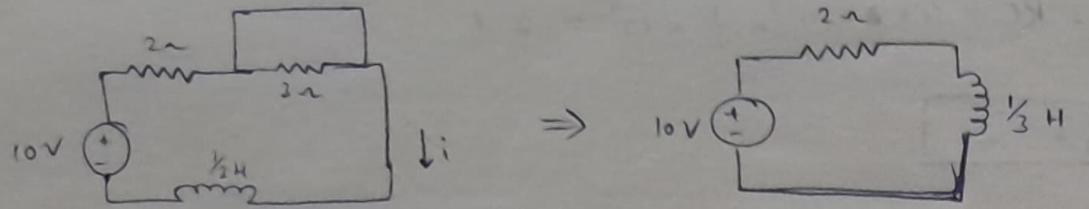

\Rightarrow

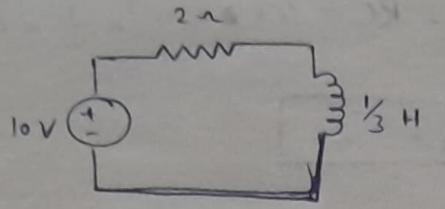


$$i = 5 \text{ A}$$

$t = 0$

$$i(0^-) = i(0^+) = i(0) = i_0 = 5 \text{ A}$$

$t > 0$

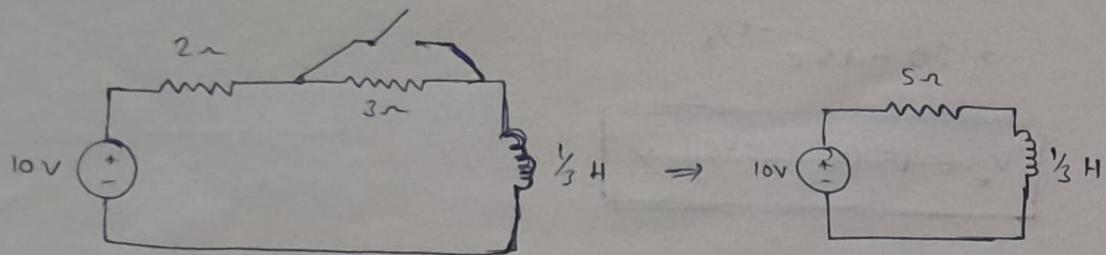

$$\tau = \frac{L}{R_{eq}} = \frac{1/3}{5} = \frac{1}{15} \text{ s}$$

$$= 0.067 \text{ s}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \quad i(\infty) = \frac{10}{5} = 2 \text{ A}$$


$$\Rightarrow i(t) = \frac{V_0}{R_{eq}} + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 2 + [5 - 2] e^{-t/(15)}$$

$$= 2 + 3e^{-15t} \text{ A}$$

$$\boxed{\therefore i(t) = 2 + 3e^{-15t} \text{ A}}$$

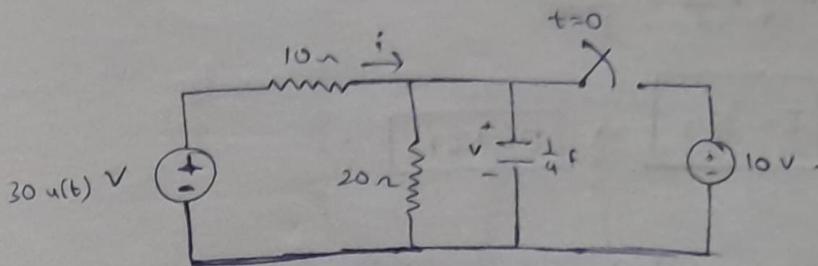
(g) The switch has been closed for a long time and is opened at $t=0$. Find i and v for all ~~time~~ time.




for $t < 0$:

By Definition,
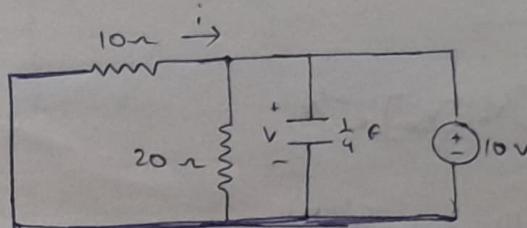
$$20 u(t) = \begin{cases} 0, & t < 0 \\ 20, & t > 0 \end{cases}$$



$$\frac{10 \times 20}{30}$$

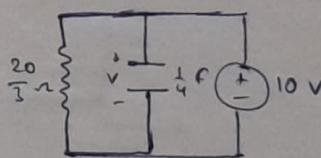

$$V(0^-) = 10V$$



$$V_c = 10V$$

Under DC,
Capacitor - Open Circuit

for $t = 0$:

$$V(0^-) = V(0^+) = V(0) = V_0 = 10V$$

for $t > 0$:

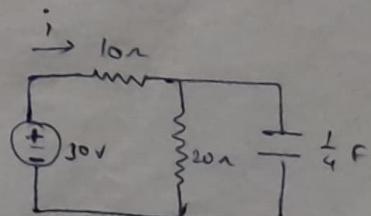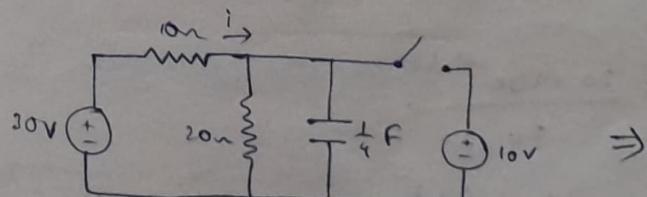

$$R_{eq} = \frac{20 \times 10}{30} = \frac{20}{3} \Omega$$

$$\tau = RC = \frac{1}{4} \times \frac{20}{3} = \frac{5}{3} \text{ s}$$

$$\boxed{\tau = \frac{5}{3} \text{ s}} \Rightarrow \boxed{\tau = 1.67 \text{ s}}$$

$$V_{\text{cap.}} = V_{20\text{m}} = \frac{30 \times 20}{20+10} = 20 \text{ V}$$

$$\boxed{V(\infty) = 20 \text{ V}}$$

$$V(t) = V_{\infty} + [V_0 - V_{\infty}] e^{-\frac{t}{\tau}}$$

$$= 20 + (10 - 20) e^{-t/(5s)}$$

$$= 20 - 10 e^{-\frac{2t}{5}}$$

$$\boxed{V(t) = 20 - 10 e^{-0.6t}}$$

$$i = C \frac{dV}{dt}$$

$$= \frac{1}{4} \times 10 e^{-0.6t} \times \frac{+3}{5}$$

$$i_{20\text{m}} = -1 \text{ A}$$

$$\boxed{i_{\text{cap.}} = \frac{+3}{2} e^{-0.6t}}$$


$$i_{20\text{m}} = 1 - \frac{1}{2} e^{-0.6t}$$

$$\therefore \boxed{\frac{V_{20\text{m}}}{20} = \frac{20 - 10 e^{-0.6t}}{20}}$$


$$= 1 - \frac{1}{2} e^{-0.6t}$$

$$\therefore i = i_{20\text{m}} + i_{\text{cap.}} = 1 + \frac{1}{2} e^{-0.6t}$$

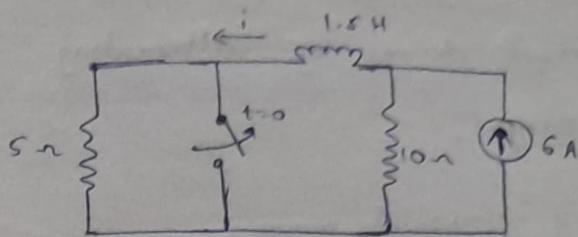H
Q) The switch in the fig. has been closed for long time
Open at $t=0$. Find $i(t)$ for $t > 0$



for $t < 0$:

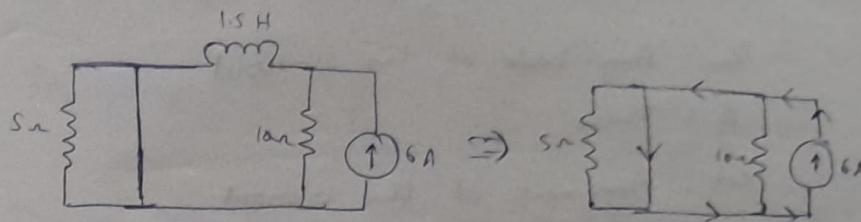


$$\therefore i_0 = 6A$$

$t=0$:

$$i(0^-) = i(0^+) = i(0) = 6A \approx i_0$$

$t > 0$:

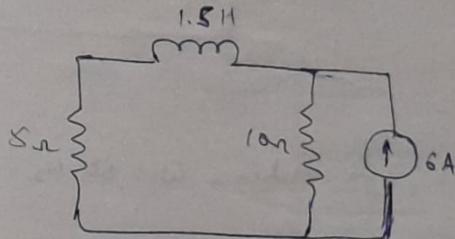

$$R_{eq} = 5\Omega + 10\Omega = 15\Omega$$

$$\tau = L/R_{eq} = 1.5/15 = 0.1$$

$$i_\infty = i_{sn}$$

~~60/15 = 4A~~

By Source Transformation,

$$i_\infty = \frac{V_0}{R_{eq}} = \frac{60}{15} = 4A$$

$$\therefore i(t) = i_\infty + (i_0 - i_\infty) e^{-t/\tau}$$

$$= 4 + 2e^{-t/0.1}$$

$$\therefore i(t) = 4 + 2e^{-10t} A$$

CHAPTER-9: AC Circuits

→ Sinusoids and Phasor: ~~Phasor~~

AC Circuit: The circuit driven by Alternating Currents and Voltages.

General expression for a sinusoidal wave,

$$V(t) = V_m \sin(\omega t + \phi)$$

V_m : Amplitude of the sinusoid

ϕ : Phase

ωt : Argument of the solenoid

ω : Angular frequency in radians/s

Frequency (f) = no. of ~~cycles~~ cycles/s

$$= \frac{1}{T}$$

$$\omega = 2\pi f$$

$$T = \frac{2\pi}{\omega}, f = \frac{1}{T}$$

$$\omega = \frac{2\pi}{T} = 2\pi f$$

In India, $\omega = 50 \text{ rad/s}$

$$\boxed{\omega = 2\pi f \text{ rad/s}}$$

For Calculations:

$$\sin(\omega t \pm \pi) = -\sin(\omega t)$$

~~Stability note~~

(i) Amplitudes must be positive

$$\cos(\omega t \pm \pi) = -\cos(\omega t)$$

(ii) ω should be same.

$$\sin(\omega t \pm 90^\circ) = \pm \cos(\omega t)$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin(\omega t)$$

g) Given a Sinusoid, $5 \sin(4\pi t - \frac{\pi}{3})$

Calculate its Amplitude, Phase, Angular frequency, period and frequency.

Sol) Amplitude = 5

Phase = $-\frac{\pi}{3}$

Angular frequency = 4π rad/s

Time period = $\frac{2\pi}{4\pi} = \frac{1}{2}$ s

Frequency = $\frac{1}{T} = \frac{1}{\frac{1}{2}} = 2$ Hz

g) Find the phase angle between $i_1 = -4 \sin(377t + 25^\circ)$

$$i_2 = 5 \cos(377t - 40^\circ)$$

Does i_1 lag or lead?

$$\therefore i_1 = -4 \sin(377t + 25^\circ)$$

$$\cancel{-4 \sin}$$

$$= 4 \cos(377t + 115^\circ)$$

$$\left[\begin{array}{l} 4 \cos(377t + 115^\circ) \\ = 4 \cos(90^\circ + 377t + 25^\circ) \end{array} \right]$$

$$\therefore i_1 = 4 \cos(377t + 115^\circ)$$

$$i_2 = 5 \cos(377t - 40^\circ)$$

i_1 leads i_2 by $115^\circ - (-40^\circ) = 155^\circ$

Q) Calculate the phase angle between $V_1 = -10 \cos(\omega t + 50^\circ)$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$= 10 \sin(\omega t - 40^\circ)$$

~~$$\cancel{-10 \cos(\omega t + 50^\circ)}$$~~

$$(OR)$$

$$= 10 \sin(\omega t + 320^\circ)$$

$$= 10 \sin(\omega t + 360^\circ - 40^\circ)$$

$$= 10 \sin(\omega t - 40^\circ)$$

V_2 leads V_1 by 30°

by $-10 - (-40)$

by $40 - 10 = 30^\circ$

→ Phasor:

→ Complex Number

→ Vector Quantity. [Phase & Amplitude]

→ Representation:

① Rectangular form

$$z = x + jy$$

$$[j = \sqrt{-1}]$$


$$= r(\cos\phi + j\sin\phi)$$

$$= re^{j\phi}$$

$$\left[e^{j\phi} = \cos\phi + j\sin\phi \right]$$

$$r = \sqrt{x^2 + y^2}$$
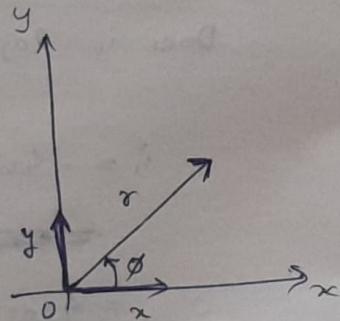
$$\phi = \tan^{-1}\left(\frac{y}{x}\right)$$



$$\begin{aligned} z_1 &= a_1 + jb_1 \\ z_2 &= a_2 + jb_2 \end{aligned} \quad] \Rightarrow (z_1 + z_2) = (a_1 + a_2) + j(b_1 + b_2)$$

If adding (or) subtracting two phasors, they must be in rectangular form.

If Multiplying (or) Dividing two Phasors, they must be in Polar form.

$$z = x + jy = r \angle \phi$$

$$z_1 = a_1 + jb_1 = r_1 \angle \phi_1$$

$$z_2 = a_2 + jb_2 = r_2 \angle \phi_2$$

$$\text{Note: } z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

$$\sqrt{z} = \sqrt{r} \angle \frac{\phi}{2}$$

~~De Moivre's~~

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

Q) Evaluate the following complex numbers

$$(a) (40 \angle 50^\circ + 20 \angle -10^\circ)^{-\frac{1}{2}}$$

$$z_1 = 40 \angle 50^\circ$$

$$r_1 = 40 \text{ magnitude}$$

$$z_2 = 20 \angle -30^\circ$$

$$r_2 = 20$$

$$z_1 = 25.7 + j(10.65)$$

$$z_2 = 17.32 + j(-10)$$

$$z_1 + z_2 = (25.7 + 17.32) + j(10.65 - 10)$$

$$= 43.03 + j 20.64$$

$$= 47.7 \angle 25.625$$

$$\sqrt{z_1 + z_2} = 6.91 \angle 72.81^\circ$$

$$(b) [(5+2j)(-1+4j)] = 5 \angle 60^\circ$$

$$= [-13+18j - 5 \angle 60^\circ]$$

$$(5.285 \angle 21.8^\circ)(4.12 \angle 104.7^\circ)$$

(OR)

$$= [-13+18j - (2.5 + 4.33j)]$$

$$= [-15.5 - j(13.7)]$$

H.W

$$(c) \frac{10+5j+3\angle 40^\circ}{-3+4j} + 10 \angle 30^\circ + 5j$$

$$\text{Ans: } 8.293 + 7.2j$$

$$\rightarrow V(t) = V_m \cos(\omega t + \phi) \quad [\text{Time Domain}]$$



$$V = V_m \angle \phi \quad [\text{Phasor Domain}]$$

Only represented in cosine form (Alexander Book)

Represented in sine form in Indian ~~A~~ Books

Q) Transform following sinusoids into Phasor:

$$i = 6 \cos(30t - 40^\circ) A$$

$$V = -4 \sin(30t + 50^\circ) V$$

~~$$i = 6 \angle -40^\circ A$$~~

$$V = -4 \sin(30t + 50^\circ)$$

~~$$i = 6 \angle -40^\circ A$$~~
~~$$V = -4 \sin(30t + 50^\circ)$$~~

$$V = 4 \angle 140^\circ V$$

$$= 4 \cos(90 + (30t + 50))$$

$$= 4 \cos(30t + 140^\circ)$$





Phasor Analysis applies only when frequency is constant.

$$★ v(t) \longleftrightarrow v = v L \phi$$

$$\frac{dv}{dt} \longleftrightarrow j\omega v$$

$$\int v dt \longleftrightarrow \frac{v}{j\omega}$$

→ Phasor Relationship:

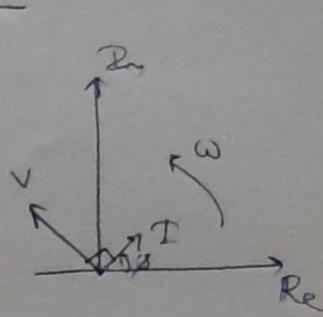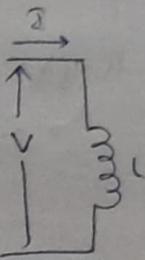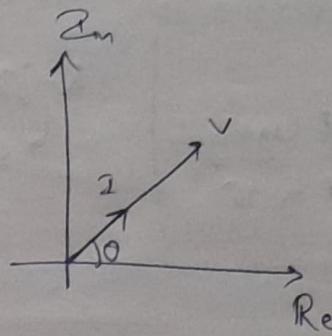
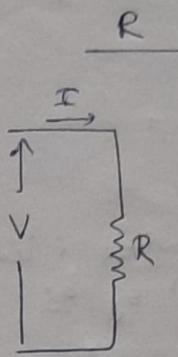


∴ I & V are in Phase

$$\& V = IR \Rightarrow I = \frac{V}{R}$$

∴ Current lags behind Voltage by 90° .
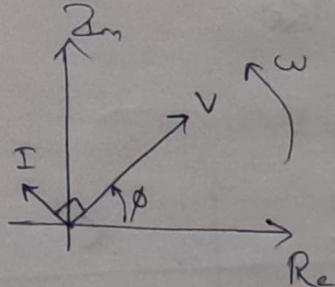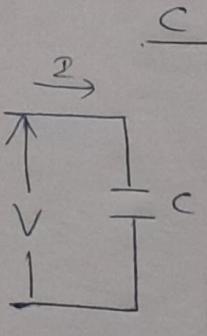
$$\& V = L \frac{di}{dt} \Rightarrow V = L j \omega I$$



∴ Current leads Voltage by 90°

$$I = C \frac{dv}{dt} \Rightarrow I = C j \omega V$$

\rightarrow Impedance: (z)

↳ AC Resistance

$$Z = \frac{V}{I}$$

Phasor Quantity
Phasor Quantity

$$\text{Phasor } (z) = R \pm jX \quad \left\{ \begin{array}{l} \text{For } L, z = R + jX \\ \text{For } C, z = R - jX \end{array} \right.$$

Reactance


$R+jX$

Signifies i lagging
behind V by 90°

$R-jX$

Signifies i leading V
by 90°

$$Z = \sqrt{R^2 + X^2}$$

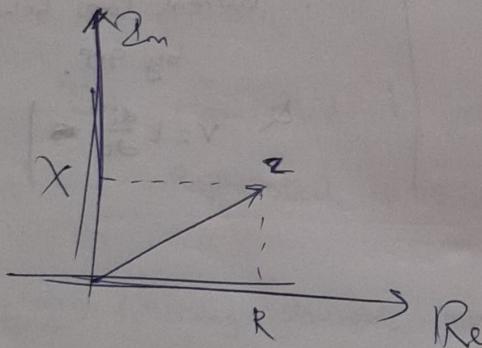

R

$$Z = R$$

L

$$Z = j\omega L$$

C

$$Z = \frac{1}{j\omega C}$$

$$\Rightarrow Z = -\frac{j}{\omega C}$$

$$Z_{eq} = R + j(X_L \pm X_C)$$

Note: The parameters must be expressed in Phasor Domain

Q) $V = 12 \cos(60t + 45^\circ)$

$L = 0.1 \text{ H}$


Find Steady state current

Sol:

$$V = 12 \cos(60t + 45^\circ)$$

$$\Rightarrow V = 12 \angle 45^\circ$$
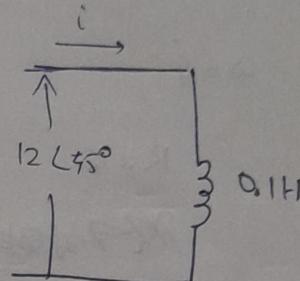
$$Z = jL\omega = j \times 0.1 \times 60 = 6j \Omega$$



$$\therefore i = \frac{V}{Z} = \frac{12 \angle 45^\circ}{6 \angle 90^\circ} = 2 \angle -45^\circ \text{ A}$$

$$\Rightarrow i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

Q) $V(t) = 6 \cos(100t - 30^\circ)$

$C = 50 \mu\text{F}$

Sol:

$$V = 6 \angle -30^\circ$$

$$Z_C = \frac{-j}{C\omega} = \frac{-j}{100 \times 50} = -200j = Z$$

$$i = \frac{V}{Z} = \frac{6 \angle -30^\circ}{200 \angle -90^\circ} = 0.03 \angle 60^\circ \text{ A}$$


$$\therefore i = 0.03 \cos(100t + 60^\circ) \text{ A}$$

→ Reciprocal of Impedance (Z) is Y (Admittance)

$$Y = \frac{1}{Z} = \frac{I}{V}$$

Unit of Y : Ω^{-1} (mho), S (Siemens)

(Q) Find $v(t)$ & $i(t)$

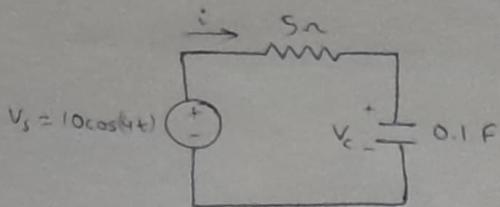

Sol:

$$\omega = 4$$

$$R = 5$$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{4 \times 0.1} = -2.5 j$$

~~Re-arrange to get $i = V_s / Z$~~

$$Z = 5 - 2.5j = 5.62 \angle -26.565^\circ$$


$$\Rightarrow I = \frac{V}{Z} = \frac{10 \angle 0^\circ}{5.62 \angle -26.565^\circ} = 1.786 \angle 26.565^\circ A$$

$$\& V_C = I Z_C$$

$$= (1.786 \angle 26.565^\circ)(2.5 \angle -90^\circ)$$

$$\Rightarrow V_C = 4.464 \angle -63.435^\circ V \Rightarrow V_C = 4.464 \cos(4t - 63.435^\circ) V$$

(P) Determine $v(t)$ & $i(t)$

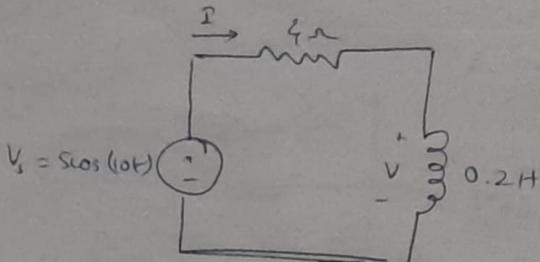

$$\begin{aligned} X_L &= j\omega L \\ &= j \times 10 \times 0.2 \\ &= 2j \\ &= 2 \angle 90^\circ \end{aligned}$$

Sol:

$$i(t) = \frac{V(t)}{Z} = \frac{5 \angle 0^\circ}{4 + 2j}$$

$$= 1.12 \angle -26.565^\circ A$$

$$\therefore i(t) = 1.12 \cos(10t - 26.565^\circ)$$

$$V(t) = I X_L$$


$$= (1.12 \angle -26.565^\circ) (2 \angle 90^\circ)$$

$$= 2.24 \angle 63.435^\circ V$$

$$\therefore V(t) = 2.24 \cos(10t + 62.435^\circ) V$$

Impedances Combination:

Series :

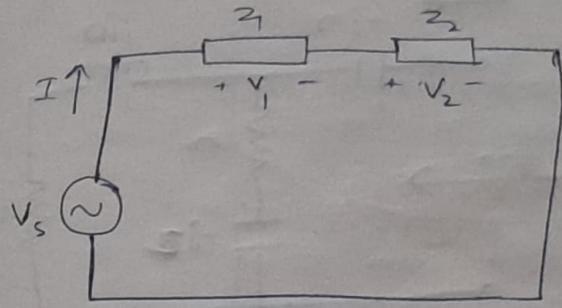

$$V_s = V_1 + V_2$$

$$I Z_{eq} = I Z_1 + I Z_2$$


$$\Rightarrow Z_{eq} = Z_1 + Z_2$$

$$\begin{aligned} I &= \frac{V}{Z_{eq}} \\ I &= \frac{V}{Z_1 + Z_2} \end{aligned}$$

By Voltage Division Techniques,

$$V_1 = \frac{Z_1 V}{Z_1 + Z_2} \quad \& \quad V_2 = \frac{Z_2 V}{Z_1 + Z_2}$$

Parallel :

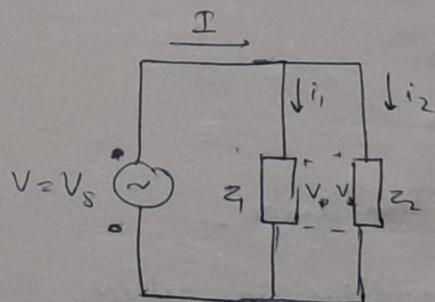

$$I = i_1 + i_2$$

$$\Rightarrow \frac{V}{Z_{eq}} = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$\Rightarrow \frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\boxed{Y_{eq} = Y_1 + Y_2}$$


$$V = I Z_{eq}$$

$$V = I \left(\frac{Z_1 Z_2}{Z_1 + Z_2} \right)$$

From Current Division Techniques

$$i_1 = \frac{Z_2}{Z_1 + Z_2} \cdot I \quad \& \quad i_2 = \frac{Z_1}{Z_1 + Z_2} \cdot I$$

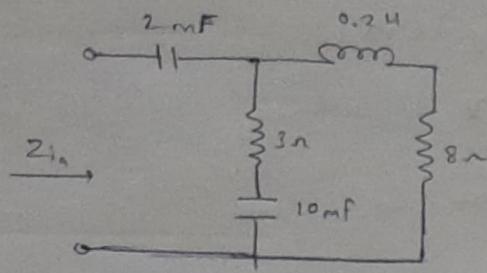Q) Determine Input Impedance, $\omega = 50 \text{ rad/s}$




Sol :

$$X_L = j \times 0.2 \times 50 = j10$$

$$X_{C_2} = \frac{-j}{2 \times 10^{-3} \times 50} = -j10$$
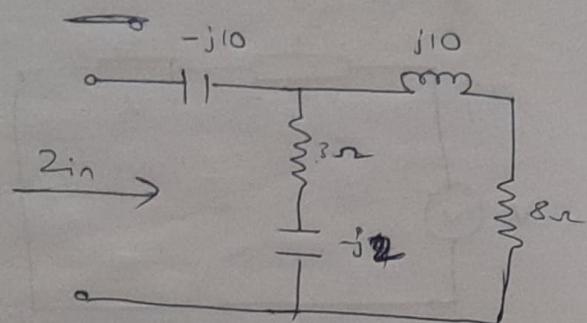
$$X_{C_{10}} = \frac{-j}{10 \times 10^{-3} \times 50} = -j2$$



$$(8 + j10) || (3 - j2) + (-j10) = Z_{eq}$$

$$\Rightarrow Z_{eq} = -j10 + \frac{(12.8 \angle 51.34^\circ)(3.56 \angle -33.69^\circ)}{11 + j8}$$

$$= -j10 + (3.22 - 1.07j)$$


~~$$Z_{eq} = 3.22 - 11.07j$$~~

$$\therefore Z_{eq} = 3.22 - 11.07j$$

Note : -j Represents nature of total Impedance.

\therefore Here, Total Impedance is Capacitive in nature.

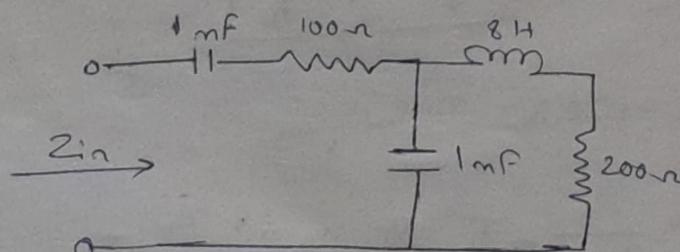
Q) Determine Input Impedance, $\omega = 10 \text{ rad/s}$



Ans:

$$Z_{eq} = 199.52 - j195$$


g) Determine $V_o(t)$

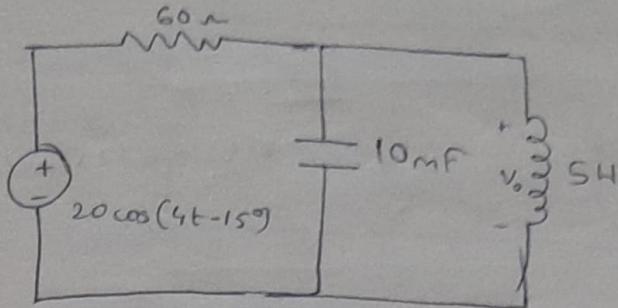

Sol:

$$X_C = \frac{-j}{10 \times 10^{-3} \times 4} = -25j \quad \left[X_C = \frac{-j}{C\omega} \right]$$
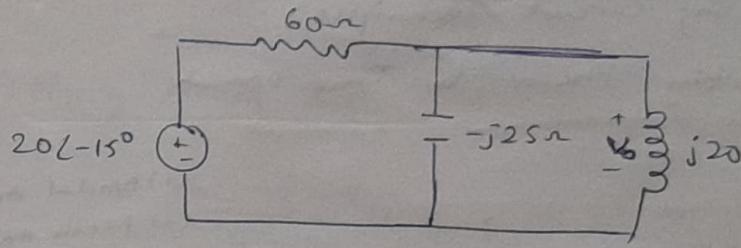
$$X_L = j\omega L = j \times 4 \times 5 = j20 \quad \Omega$$



$$Z_{eq} = 60 + \frac{(-j25)(j20)}{-j5}$$

$$\Rightarrow Z_{eq} = 60 + j100$$

$$V_{j20} = V_{-j25}$$


$$V_{100j} = V \times \frac{j100}{60 + j100} = \frac{(20∠-15^\circ)(100∠90^\circ)}{(116.62∠59.036^\circ)}$$

$$\Rightarrow V_{100j} = 16.488 + 4.7167j = V_o$$

$$\therefore V_o = 17.15 \angle 15.93^\circ V$$

$$\therefore V_o = 17.15 \cos(4t + 15.93^\circ) V$$


g) Determine $i(t)$ in given circuit

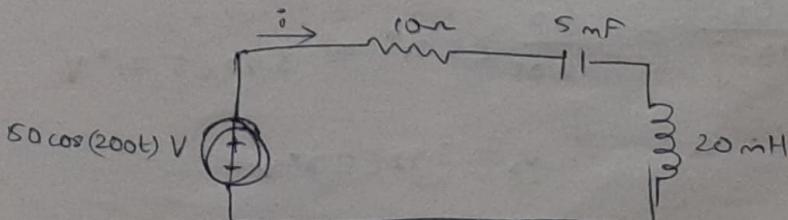

Sol:

$$i(t) = 4.789 \angle -16.7^\circ A$$

Q) Find $v(t)$

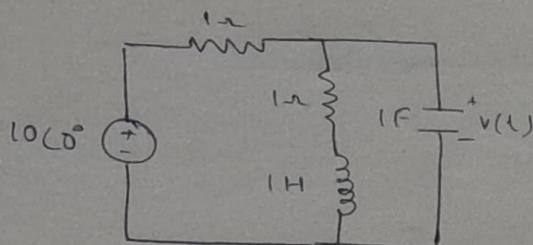

Sol:

$$V(t) = 6.325 \cos(t - 18.43^\circ) V$$

CHAPTER-10

(SINUSOIDAL STEADY STATE ANALYSIS)


→ Steps while solving:

- ① Transform the circuit into Phasor (or) Frequency domain
- ② Solve the problem using Circuit Techniques
- ③ Transform the resulting Phasor to Time Domain

→ Nodal Analysis

Q) ~~Find~~ Find V_o using Nodal Analysis

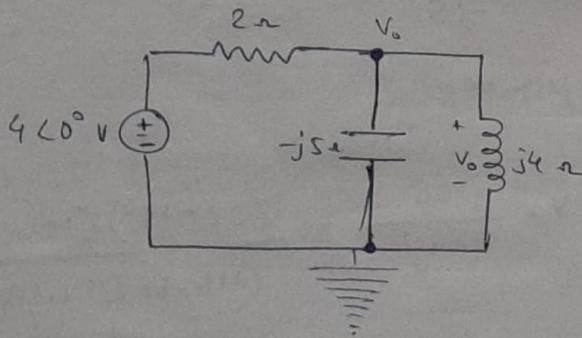- (1) Nodal Analysis
- (2) Mesh Analysis
- (3) Superposition Theorem
- (4) Thevenin/Norton's Theorem



Sol: At top Node:


$$-\frac{V_o - 4\angle 0^\circ}{2} = \frac{V_o}{-j5} + \frac{V_o}{j4} \Rightarrow \frac{V_o - 4\angle 0^\circ}{2} = V_o j \left(\frac{1}{4} - \frac{1}{5} \right) = \frac{V_o j}{20}$$

$$\Rightarrow 40 = V_o (10 + j)$$


$$\Rightarrow V_o = \frac{40}{10 - j} = \frac{40}{10.05} \angle 5.71^\circ = 3.98 \angle 5.71^\circ V$$

$$\therefore V_o = 3.98 \angle 5.71^\circ V$$

Q) find $v_o(t)$

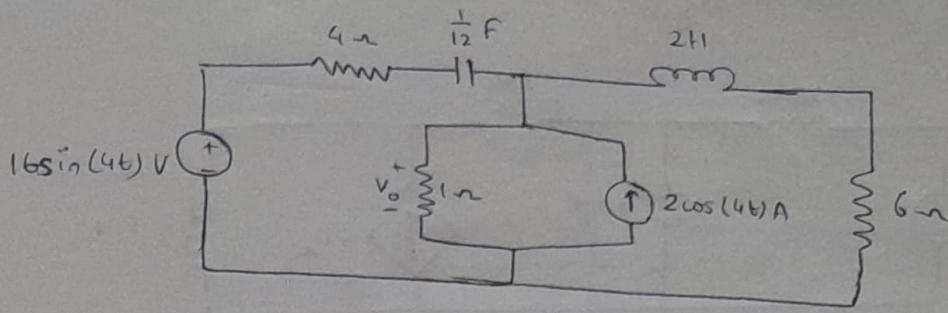

Sol:

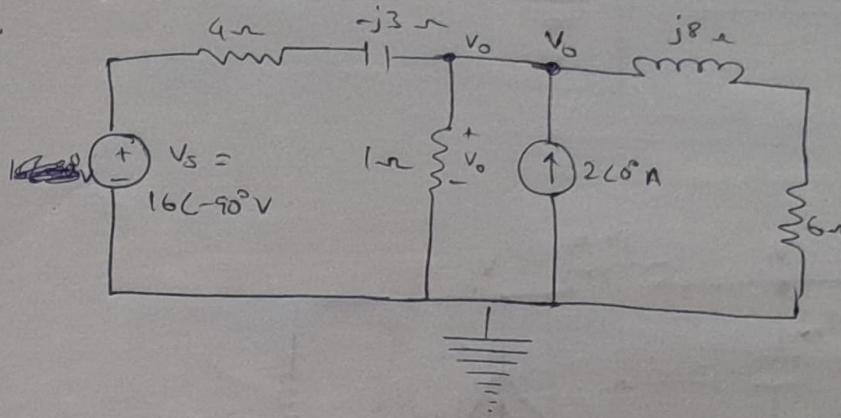

$$\begin{aligned} 16\sin(4t) \text{ V} &= 16L - 90^\circ \text{ V} \\ \frac{1}{12} \text{ F} &= \frac{-j}{\frac{1}{12} \times 4} = -j3 \text{ ohm} \\ 2\cos(4t) \text{ A} &= 2L^0 \text{ A} \\ 2H &= j\omega L = 8j \text{ ohm} \end{aligned}$$

Applying Nodal Analysis @ Node v_o :

$$\frac{16L - 90^\circ - v_o}{4 - j3} + 2L^0 = \frac{v_o}{1} + \frac{v_o - 0}{6 + j8}$$

$$= v_o \left(\frac{53}{50} - \frac{2j}{25} \right)$$

$$\Rightarrow \frac{16L - 90^\circ}{5L - 36.87^\circ} + 2L^0 = v_o \left(\frac{51 - 4j}{50} + \frac{1}{4 - j3} \right)$$

$$\Rightarrow \frac{98 - 64j}{25} = \cancel{v_b \left(\frac{61 + j2}{50} \right)}$$


~~$$\Rightarrow \frac{98 - 64j}{25} = \cancel{v_b \left(\frac{61 + j2}{50} \right)}$$~~

$$\Rightarrow v_o = \frac{196 - 128j}{61 + j2}$$


$$\therefore v_o = 3.815 \angle -35.025^\circ \text{ V}$$

$$\therefore v_o(t) = 3.815 \cos(4t - 35.025^\circ) \text{ V}$$

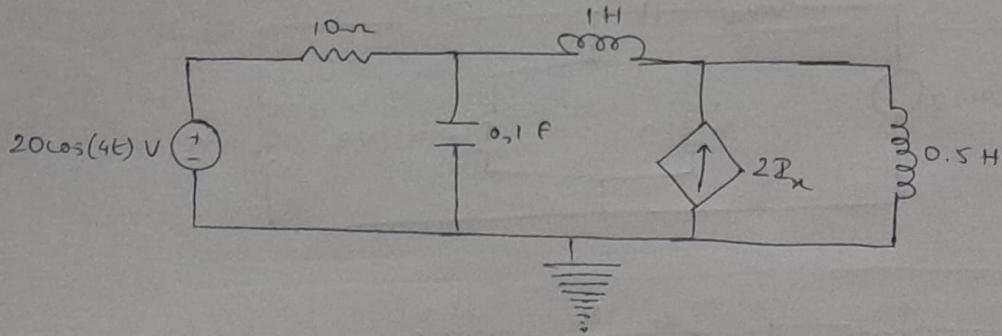Q) Find \mathcal{D}_x using Nodal Analysis:



Sol:

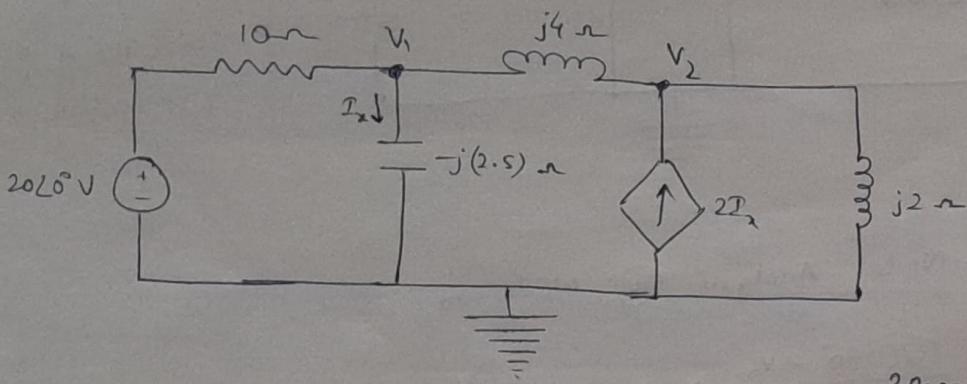

Applying Nodal Analysis:

@ V_1 :

$$\frac{20\cos^0 - V_1}{10} = \frac{V_1 - V_2}{j4} + \frac{V_1 - 0}{-j(2.5)} \quad \text{--- (1)}$$

@ V_2 :

$$2\mathcal{D}_x = \frac{V_2 - V_1}{j4} + \frac{V_2 - 0}{j2}$$

$$\Rightarrow \frac{4jV_1}{5} = \frac{V_2 - V_1}{j4} + \frac{V_2}{j2} \quad \text{--- (2)}$$

$$\begin{aligned} 20\cos(4t) V &\rightarrow 20\cos^0 V \\ 1 H &\rightarrow j \times 4 \times 1 = j4 \text{ n} \\ 0.5 H &\rightarrow j \times 4 \times 0.5 = j2 \text{ n} \\ 0.1 F &\rightarrow -\frac{j}{4 \times 0.1} = -j(2.5) \end{aligned}$$


$$\left[\begin{array}{l} \mathcal{D}_x = \frac{V_1 - 0}{-j(2.5)} \\ \therefore \mathcal{D}_x = \frac{2jV_1}{5} \text{ A} \end{array} \right]$$

By solving (1) and (2):


$$\begin{aligned} V_1 &= 18.97 \angle 18.43^\circ V \\ &= 18.97 \cos(4t + 18.43^\circ) V \end{aligned}$$

$$\begin{aligned} V_2 &= 13.91 \angle 198.3^\circ V \\ &= 13.91 \cos(4t + 198.3^\circ) V \end{aligned}$$

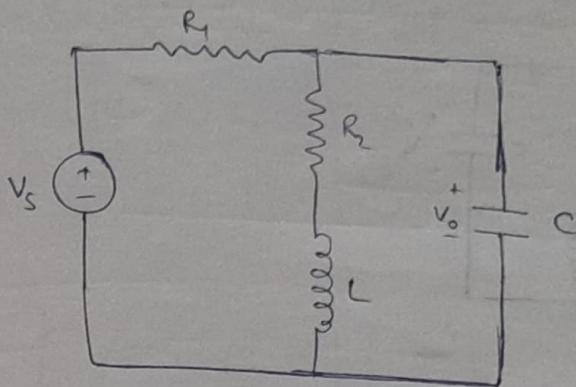Q) Find V_o/V_s Using Nodal Analysis in given circuit :



Sol :

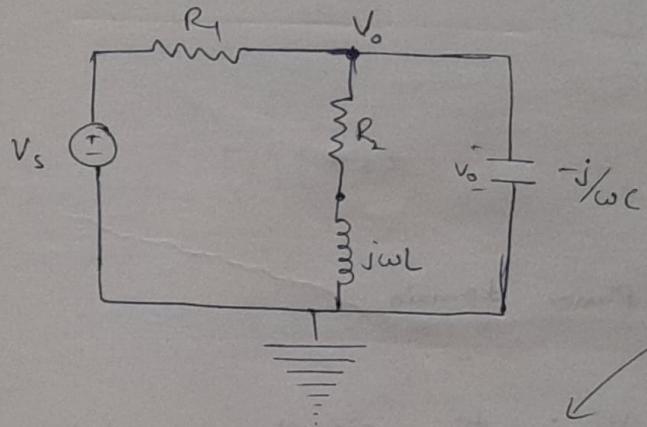

By Applying Nodal Analysis @ Node V_o

$$L \rightarrow jwL$$

$$C \rightarrow -j/wC = 1/jwC$$

$$R_1 \rightarrow R_1$$

$$R_2 \rightarrow R_2$$

$$V_s \rightarrow V_s$$

$$\frac{V_s - V_o}{R_1} = \frac{V_o - 0}{1/jwC} + \frac{V_o - 0}{R_2 + jwL}$$

$$\Rightarrow \frac{V_s}{R_1} - \frac{V_o}{R_1} = (jwC)V_o + \frac{V_o}{R_2 + jwL}$$

$$\Rightarrow \frac{V_s}{R_1} = V_o \left(jwC + \frac{1}{R_1} + \frac{1}{R_2 + jwL} \right)$$


$$\Rightarrow \frac{V_s}{V_o} = \left(jwC R_1 + 1 + \frac{R_1}{R_2 + jwL} \right)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{R_2 + jwL}{(R_2 + jwL)(1 + jwC R_1) + R_1} = \frac{R_2 + jwL}{R_1 + R_2 + jwL - \omega^2 L C R_1 + jw R_2 R_1 C}$$

$$\therefore \frac{V_o}{V_s} = \frac{R_2 + jwL}{R_1 + R_2 - \omega^2 L C R_1 + jw(L + R_2 R_1 C)}$$

Q) For the given circuit, find V_o/V_s using Nodal Analysis

[H.W)

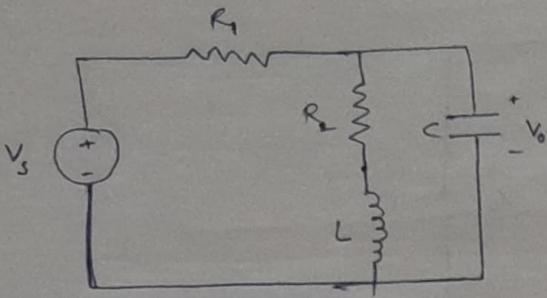

Sol:

$$\frac{V_o}{V_s} = \frac{R_2 + j\omega L}{R_1 + R_2 - \omega^2 L C R_1 + j\omega (L + R_1 R_2 C)}$$


→ Mesh Analysis:

→ KVL for Loop

(To find loop current)

① Parameters should be in Phasor domain

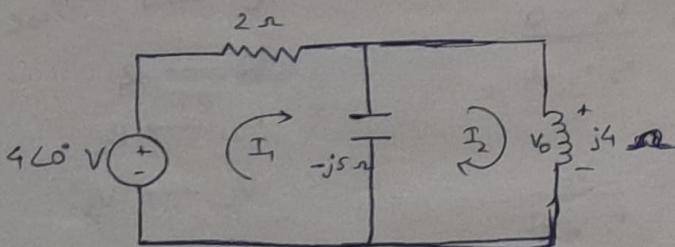Q) Use Mesh Analysis to find V_o in the circuit given below



$$[V_o = I_2 \cdot j4]$$

Apply KVL for loop 1:

$$+ 4∠0^\circ - 2I_1 - (-j5)[I_1 - I_2] = 0$$

$$\Rightarrow 4∠0^\circ - 2I_1 + j5(I_1 - I_2) = 0$$

$$\Rightarrow -I_1(2 - j5) - j5I_2 = -4∠0^\circ$$

$$\Rightarrow (2 - j5)I_1 + j5I_2 = 4∠0^\circ \quad \text{--- (1)}$$

Apply KVL for loop 2:

$$-(-j5)[I_2 - I_1] - I_2 \cdot (j4) = 0$$

$$\Rightarrow (j5 - j4)I_2 - j5(I_1) = 0$$

$$\Rightarrow (j5)I_1 - (j5 - j4)I_2 = 0 \quad -\textcircled{2}$$

$$\begin{bmatrix} j5 & j4 - j5 \\ 2 - j5 & j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 4 \angle 0^\circ \end{bmatrix}$$

$$[4 \angle 0^\circ = 4 + 0j]$$

$$[R][x] = [v]$$

$$\nabla = (j5)^2 - (j4 - j5)(2 - j5)$$

$$= (j5)^2 - 2j4 + j4 \cdot j5 + 2j5 - (j5)^2$$

$$\Rightarrow \nabla = -2(j4) + j4 \cdot j5 + 2(j5)$$
$$= 20 - j2$$

$$\nabla I_2 = \begin{bmatrix} j5 & 0 \\ 2 - j5 & 4 \angle 0^\circ \end{bmatrix}$$

$$= j5 \cdot 4 \angle 0^\circ$$

$$= -20j$$

$$[I_1 = \frac{1}{5} I_2]$$


$$I_2 = \frac{\nabla I_2}{\nabla 1} = \frac{-20j}{20 - j2}$$

$$I_2 = \frac{1}{0.1 + j}$$


$$= 0.995 \angle -84.2^\circ$$

$$V_o = j4 I_2 = \frac{j4}{0.1 + j} = \frac{j4}{1.00499 \angle 84.29^\circ} = 3.98 \angle 5.71^\circ V$$

Q) Find I_o in circuit below

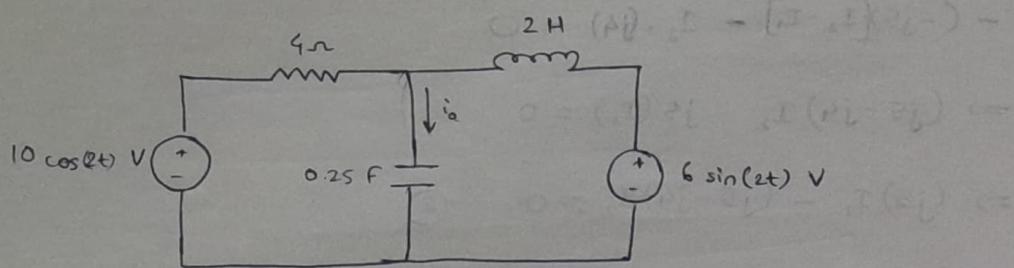

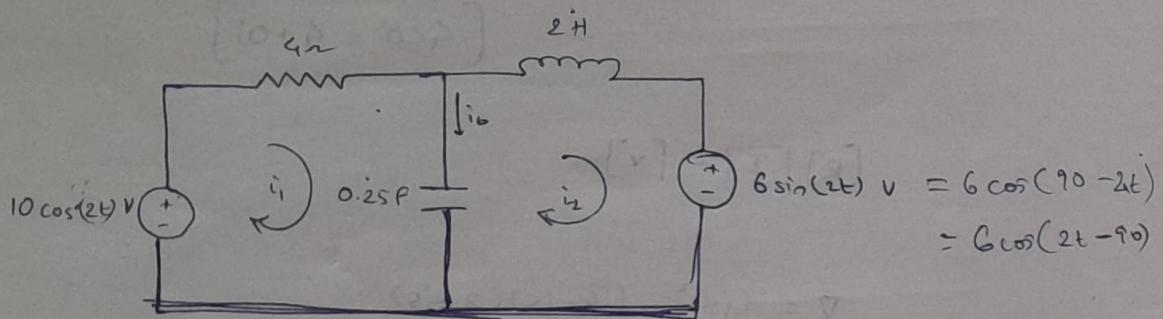Assume i_1 in left loop and
 i_2 in right loop




$$V = 10 \angle 0^\circ \text{ V}$$

$$R = 4\Omega$$

$$0.25 F \rightarrow \frac{1}{j2 \times 0.25} = -j2$$

$$2H \rightarrow j2 \cdot 2 = j4$$
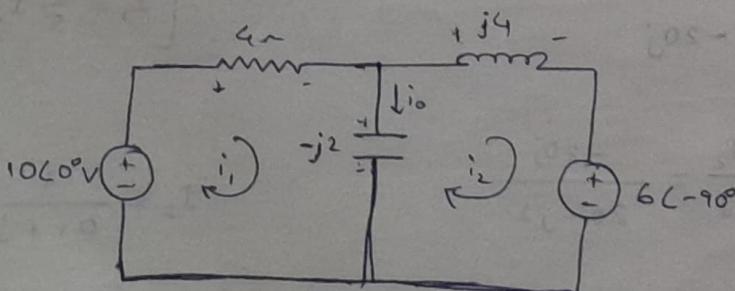
$$6 \sin(2t) \rightarrow 6 \angle -90^\circ$$



Applying KVL:

$$\textcircled{1} \rightarrow +10\angle 0^\circ - 4i_1 - (-j2)(i_1 - i_2) = 0$$

$$\Rightarrow 10\angle 0^\circ - 4i_1 + j2(i_1 - i_2) = 0$$

$$\Rightarrow \cancel{i_1}(j2 - 4) - i_2(j2) = -10\angle 0^\circ$$

$$\Rightarrow i_1(4 - j2) + i_2(j2) = 10\angle 0^\circ \quad \textcircled{1}$$

$$\Rightarrow i_1(2 - j) + i_2(j) = 5\angle 0^\circ$$

$$\textcircled{2} \rightarrow -j4 \cdot i_2 - 6\angle -90^\circ - (-j2)(i_2 - i_1) = 0$$

$$\Rightarrow -j4i_2 - 6\angle -90^\circ + j2(i_2 - i_1) = 0$$

$$\Rightarrow j4i_2 + 6\angle -90^\circ + j2(i_1 - i_2) = 0$$

~~$$\Rightarrow -j2i_1 - (j4 - j2)i_2 = 6\angle -90^\circ$$~~

~~$$\Rightarrow -j2i_1 - j2i_2 = 6\angle -90^\circ \quad \textcircled{2}$$~~

~~$$\Rightarrow -j2i_1 - j2i_2 = -6j \Rightarrow \boxed{i_1 + i_2 = 3}$$~~

$$i_1(4 - j2 - j2) = 10\angle 0^\circ + 6\angle -90^\circ$$

$$\Rightarrow i_1(4 - j4) = (10 + 0j) + (0 - 6j)$$

$$= 10 - 6j$$

$$= 11.662 \angle -30.96^\circ$$

$$i_1 = \frac{11.662 \angle -30.96^\circ}{4 - j4} = \frac{10 - 6j}{4 - 4j} = \frac{5 - 3j}{2 - 2j}$$

$$i_2 = 3 - i_1$$

$$= 3 - \frac{5 - 3j}{2 - 2j}$$

$$= \frac{6 - 6j - 5 + 3j}{2 - 2j}$$

$$\boxed{i_2 = \frac{1 - 3j}{2 - 2j}}$$


$$\boxed{i_1 = \frac{5 - 3j}{2 - 2j}}$$

$$I_o = i_1 - i_2 = \frac{5 - 3j - 1 + 3j}{2 - 2j} = \frac{4}{2 - 2j} = \frac{2}{1 - j} = 1 + j$$

$$i_o = 1.414 \angle 45^\circ$$

$$= 1.414 \cos(2t + 45^\circ)$$

Q) Determine I_o using Mesh Analysis

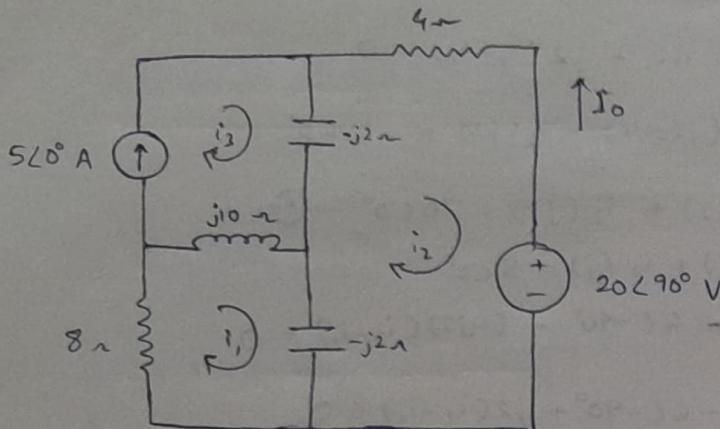

$$i_o = -i_2$$

$$\boxed{i_o = -6.12 \angle 144.78^\circ A}$$

~~-8i_1 - j10(i_1 - i_3) - (-j2)(i_1 - i_2) = 0~~

$$\text{---} \quad \Rightarrow -8i_1 - j10(i_1 - i_3) - (-j2)(i_1 - i_2) = 0$$

$$\Rightarrow -8i_1(1+j) - 2i_2(j) + 10i_3(j) = 0$$

$$\Rightarrow 4i_1(1+j) + i_2(j) + 5i_3(j) = 0 \quad -\textcircled{1}$$

$$\textcircled{2} \rightarrow -(-j2)(i_2 - i_1) - (-j2)(i_2 - i_3) - 4i_2 - 20 \angle 90^\circ = 0$$

$$\Rightarrow j2(i_2 - i_1) + j2(i_2 - i_3) - 4i_2 = 20 \angle 90^\circ$$

$$\Rightarrow j2(2i_2 - i_1 - i_3) - 4i_2 = 20 \angle 90^\circ$$

$$\Rightarrow i_1(-j2) + i_2(34 - 4) + i_3(-j2) = 20 \angle 90^\circ \quad -\textcircled{2}$$

$$\textcircled{3} \rightarrow -(-j2)(i_1 - i_2) - j10(i_3 - i_1) = 0$$

$$\Rightarrow j2(i_3 - i_2) - j10(i_3 - i_1) = 0$$

$$\Rightarrow j2(5 - i_2) - j10(5 - i_1) = 0$$

$$\Rightarrow -j(40) - j10(i_1) - j2(i_2) = 0$$

$$\Rightarrow 10i_1 + 2i_2 = 40 \Rightarrow \boxed{5i_1 + i_2 = 20} \quad -\textcircled{3}$$

Put ① in ① :

$$\Rightarrow 4\left(\frac{20-i_2}{5}\right)(1+j) + i_2(j) - 25j = 0$$

$$\Rightarrow 8 - 4(20-i_2)(1+j) + 5i_2(j) - 125j = 0$$

$$\Rightarrow (80-4i_2)(1+j) + i_2(j5) - (125j) = 0$$

$$\Rightarrow \underline{80} + \underline{80j} - \underline{4i_2} - \underline{4j(i_2)} + \underline{(j5)i_2} - \underline{125j} = 0$$

$$\Rightarrow -45j - 4i_2 + i_2(j9) + 80 = 0$$

$$\Rightarrow i_2(-4+j9) - 45j = -80$$

$$\Rightarrow i_2(4j9-4) + 45j = 80 \quad \text{--- (4)}$$

$$\Rightarrow i_2 = \frac{80-45j}{-4+j9}$$

$$i_2 = \frac{91.7818 \angle -29.3578}{9.8489 \angle 113.9625}$$


$$\boxed{i_2 = 9.32 \angle -143.32 \text{ A}}$$

1/1/23

→ Superposition Theorem:

Applicable to linear Circuits

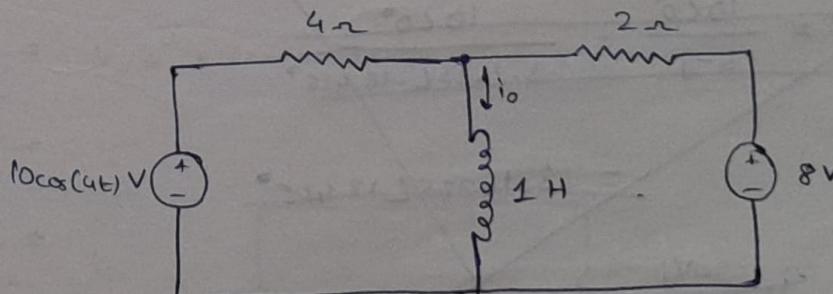Q) Determine i_o using Superposition Theorem:




(i) Convert time domain to Phasor Domain


$$1 \text{ H} \rightarrow j \times 1 \times 4 = j4$$

$$8 \text{ V} \rightarrow 8 \angle 0^\circ$$
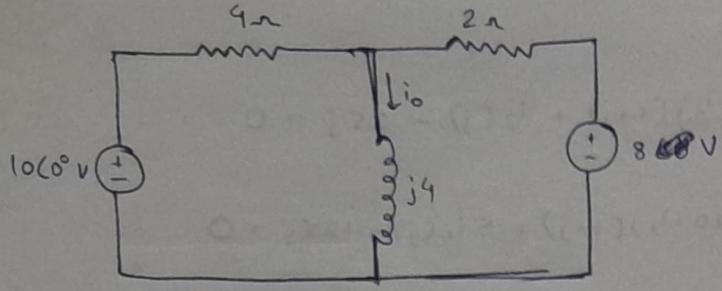
$$10 \cos(4t) \rightarrow 10 \angle 0^\circ$$



Finding i_{o_1} by shorting 8V source

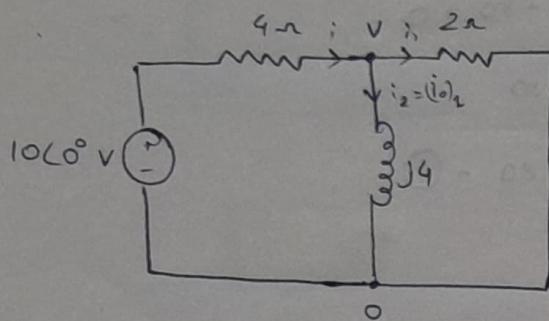

$$\frac{10\angle 0^\circ - V}{4} = \frac{V - 0}{2} + \frac{V - 0}{j4}$$

$$\Rightarrow \frac{10\angle 0^\circ - V}{4} = \frac{V}{2} - \frac{Vj}{4}$$

$$\Rightarrow 10\angle 0^\circ - V = 2V - Vj \quad \rightarrow V = \frac{10}{3-j}$$

$$\Rightarrow 10\angle 0^\circ = V(3-j) \quad \rightarrow i_2 = -\frac{(10)}{3-j} j$$

$$\Rightarrow V = \frac{10\angle 0^\circ}{3-j} = \frac{10\angle 0^\circ}{3.16225(-18.425^\circ)}$$

$$= 3.16225 \angle 18.425^\circ$$

$$= -\frac{(3.16225 \angle 18.425^\circ)(1 \angle 90^\circ)}{4}$$



$$= -0.63245 \angle 108.425^\circ$$

$$= \frac{1-3j}{4}$$

Correct Ans: ~~0.7915 & -71.56~~

$$(i_o)_1 = 0.79057 \angle -71.56^\circ \quad \text{--- (1)}$$

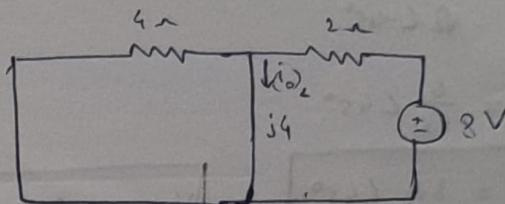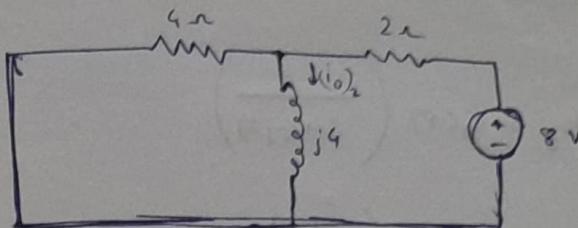Finding $(i_o)_2$ by shorting 10C° source



In DC,

Inductor is shorted

$$(i_o)_2 = \frac{8}{2} = 4 \text{ A}$$


$$i_o = (i_o)_1 + (i_o)_2$$

$$\Rightarrow i_o = 0.79057 \angle -71.56^\circ + 4 \text{ A}$$

$$\Rightarrow i_o = 4 + 0.79 \cos(4t - 71.56^\circ) \text{ A}$$

Q) Find v_o for the circuit
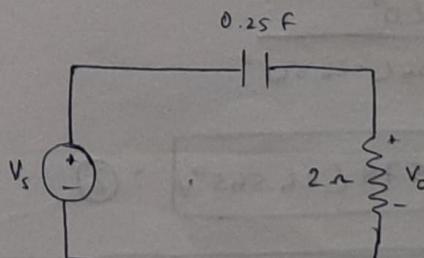
$$v_s = 6 \cos(2t) + 4 \sin(4t) \text{ V}$$




A:

$$(i) v_s = 6 \cos(2t) [v_{o_1}]$$

$$(ii) v_s = 4 \sin(4t) [v_{o_2}]$$

This problem can be solved only using Superposition Theorem
(1 m)

(i)

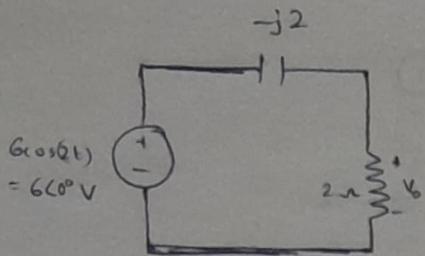

$$\begin{aligned} \cancel{\text{V}}_{\text{out}} &= \cancel{\text{V}}_o \\ jx \cancel{\frac{1}{4}} \times 2 &= \frac{2}{j} \\ &= -2j \end{aligned}$$

$$V_{o_1} = (6\angle 0^\circ) \left(\frac{\frac{2}{j}}{2 + (-j2)} \right)$$

$$= 6\angle 0^\circ \left(\frac{1}{1-j} \right)$$

$$= \frac{6\angle 0^\circ}{\sqrt{2} \angle -45^\circ}$$


$$= \frac{6}{\sqrt{2}} \angle 45^\circ$$

$$V_{o_1} = 3\sqrt{2} \angle 45^\circ V$$

$$V_{o_1} = 4.243 \angle 45^\circ V$$

①

(ii)

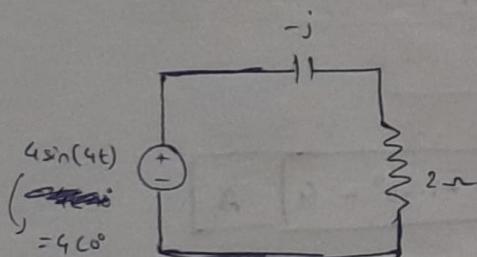

$$\cancel{\text{V}}_{\text{out}} = -j$$

~~sin → Convert into cos
only when Angular
frequencies are
same.~~

$$V_{o_2} = (4\angle 0^\circ) \left(\frac{2}{2-j} \right)$$

$$= \frac{8\angle 0^\circ}{2.236 \angle -26.565^\circ}$$

$$V_{o_2} = 3.578 \angle 26.565^\circ V$$


Any AC Load cannot
be excited/supplied
by 2 Different AC
sources with 2 ~~different~~
different frequency
components in real time

$$V_o = 4.243 \cos(2t + 45^\circ) + 3.578 \sin(4t + 26.565^\circ) V$$


Cannot be simplified further.

1/11/23

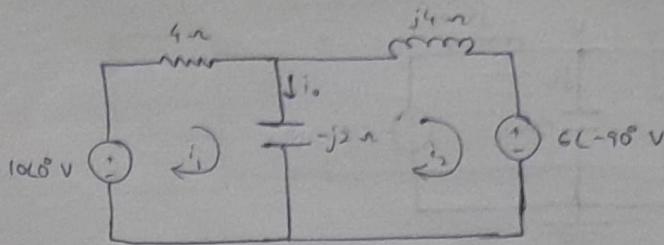(g) Find i_0 using Superposition Theorem:



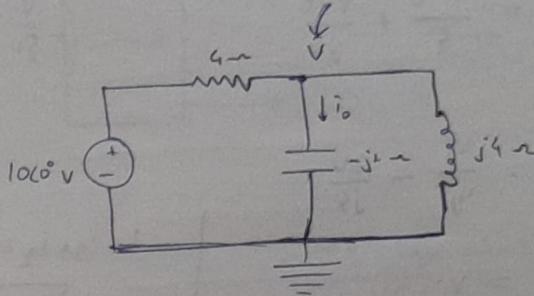A Shorting $6\angle-90^\circ$ Source first to find i_{o_1}



$$\frac{V-10}{4} + \frac{V-0}{-j2} + \frac{V-0}{j4} = 0$$

By Nodal Analysis,

$$-\frac{V-10\angle 0^\circ}{4} = \frac{V-0}{-j2} + \frac{V-0}{j4}$$

$$\Rightarrow \frac{V-10\angle 0^\circ}{4} = -\frac{V_j}{2} + \frac{V_j}{4}$$

$$\Rightarrow V-10\angle 0^\circ = -2V_j + V_j = -V_j$$

$$\Rightarrow 10\angle 0^\circ = V(1+j)$$

$$\Rightarrow V \cdot \frac{1+j}{10\angle 0^\circ} = \frac{1+j}{10}$$

$$V = \frac{1+j}{10}$$

$$V = \frac{10}{1+j}$$

$$i_{o_1} = \frac{V_j}{2} = \frac{j}{2} \left(\frac{1+j}{10} \right)$$

$$i_{o_1} = \frac{V_j}{2} = \frac{j}{2} \left(\frac{10}{1+j} \right)$$

$$= \frac{-1+j}{20} = \frac{\sqrt{2} \angle 135^\circ}{20\angle 0^\circ}$$

$$= \frac{5j}{1+j}$$

$$i_{o_1} = \frac{\sqrt{2} \angle 135^\circ}{20\angle 0^\circ}$$

$$i_{o_1} = \frac{5}{2} j(1-j)$$

$$i_{o_1} = 0.0707 \angle 135^\circ$$

$$i_{o_1} = \frac{x_1}{20} \angle 135^\circ$$


$$i_{o_1} = -0.05 + 0.05j$$

Generally
 $\omega = 2 \text{ rad/s}$
 (2π radian)

$$i_{o_1} = \frac{5}{2}(1+j)$$

$$i_{o_1} = 3.535 \angle 45^\circ$$

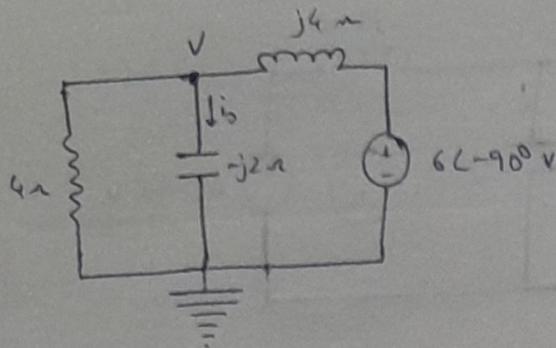Shorting 10C° source to find i_{o_2}, i_o .



$$\frac{6L-90^{\circ}-V}{j4} = \frac{V-0}{j} + \frac{V-0}{-j2} \quad \left(-\frac{V}{j2} = \frac{V_j}{2} \right)$$

$$\Rightarrow \frac{6L-90^{\circ}-V}{j4} = \frac{V_j}{4j} - \frac{2V}{j4}$$

$$\Rightarrow 6L-90^{\circ}-V = V_j - 2V$$

$$\Rightarrow 6L-90^{\circ} = V(j-1)$$

$$\Rightarrow V = \frac{6L-90^{\circ}}{j-1}$$

$$i_{o_2} = \frac{V-0}{-j2} = \frac{V_j}{2}$$

$$i_{o_2} = \frac{j}{2} \left(\frac{-6j}{j-1} \right)$$

$$= \frac{6}{2j-2}$$

$$i_{o_2} = \frac{3}{j-1}$$

$$\Rightarrow i_{o_2} = \frac{3L0^{\circ}}{\sqrt{2} L 135^{\circ}}$$

$$i_{o_2} = \frac{3}{\sqrt{2}} L -135^{\circ}$$

$$\Rightarrow \boxed{i_{o_2} = \frac{3\sqrt{2}}{2} L -135^{\circ}}$$

$$i_o = i_{o_1} + i_{o_2} = \frac{5}{2}(1+j) - \frac{3}{2}(1+j)$$

$$\boxed{i_o = 1+j}$$

$$\therefore i_o = \sqrt{2} L 45^{\circ}$$



Correct Ans:

~~$$i_o(t) = \sqrt{2} \cos(2t+45^{\circ})$$~~


~~$$\begin{aligned}
 i_o &= i_{o_1} + i_{o_2} = -\frac{3}{2}(j+1) + \frac{5}{2}(1+j) \\
 &= -\frac{30j}{20} - \frac{30}{20} - \frac{1}{20} + \frac{j}{20} \\
 &= -\frac{29j}{20} + \frac{31}{20} \\
 &= -1.55 - 1.45j \\
 \Rightarrow i_o &= 2.1225 L -135^{\circ}
 \end{aligned}$$~~

~~$$\boxed{i_{o_2} = 2.12132 L -135^{\circ}}$$~~

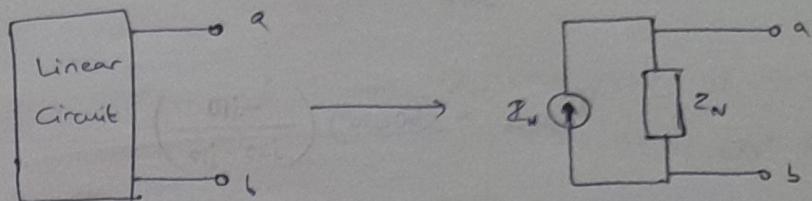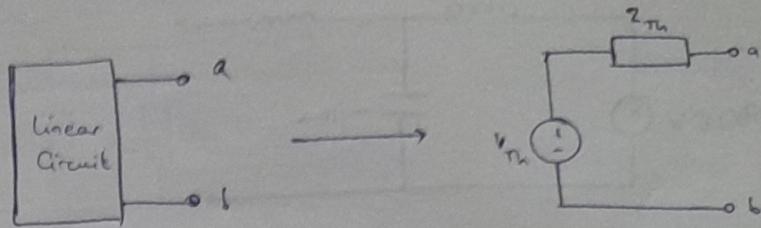→ Thévenin's & Norton's Equivalent Circuit:




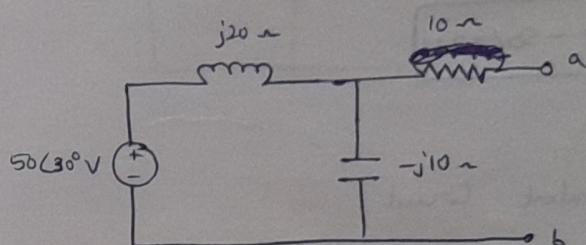(g) Find Thévenin's and Norton's Equivalent Circuit @ terminals ab.



(i) Convert all quantities into Phasor Domain

For finding Z_{Th} :

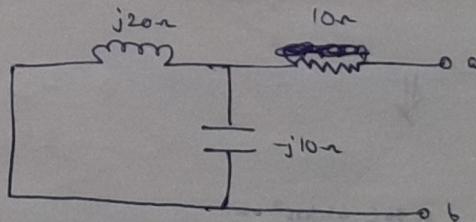

$$j20 \parallel -j10$$


$$\Rightarrow \frac{j20 \times -j10}{10j}$$

$$\Rightarrow \frac{20}{j} \Rightarrow -20j \Omega$$

$$-20j \parallel 10 \Omega \text{ Series with } 10 \Omega = \underline{10-20j} = 22.36 \angle -63.435 \Omega$$

$$Z_{Th} = 10-20j \Omega$$

For finding V_{Th} :

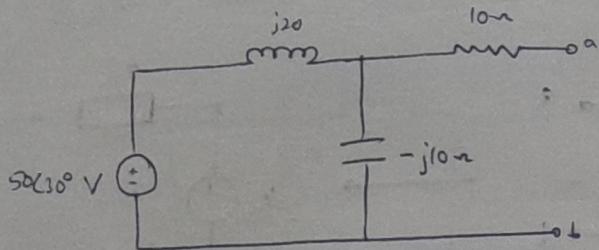

$$V_{ab} = V_{-j10\text{ }\Omega}$$

$$V_{-j10\text{ }\Omega} = (50 \angle 30^\circ) \left(\frac{-j10}{j20 - j10} \right)$$



$$= (50 \angle 30^\circ) (-1)$$

$$[-1 = -1 \angle 0^\circ]$$


$$= -50 \angle 30^\circ$$

$$\boxed{V_{Th} = -50 \angle 30^\circ \text{ V}}$$

∴ Thévenin's Equivalent Circuit:

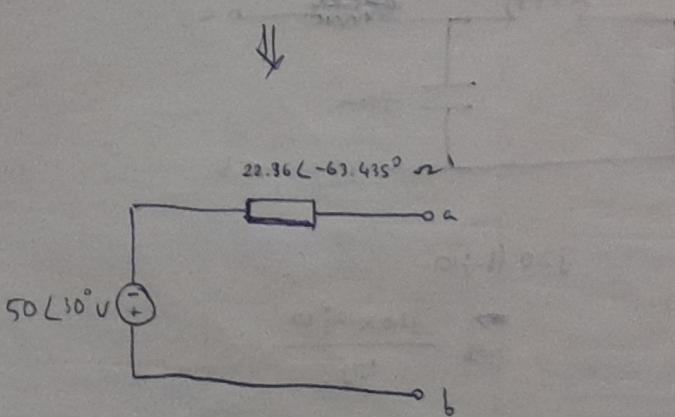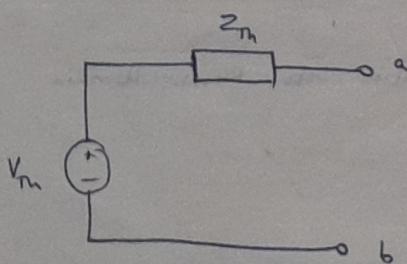

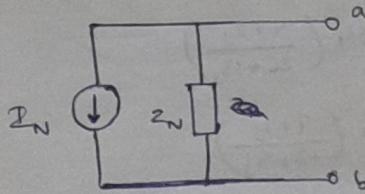For Finding Norton's Equivalent Circuit :




$$Z_N = Z_{Th}$$


$$(Z_N)^{-1} = \left(\frac{V_{Th}}{Z_{Th}} \right)^{-1} = \frac{22.361 \angle -63.435^\circ}{50 \angle 30^\circ} \text{ A}$$

$$\Rightarrow (Z_N)^{-1} = 0.447 \angle -93.435^\circ \text{ A}$$
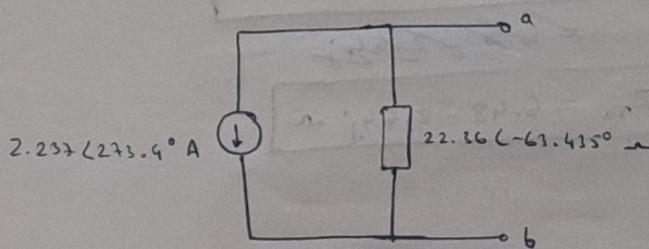
$$= 2.237 \angle 93.435^\circ \text{ A}$$




(Q)

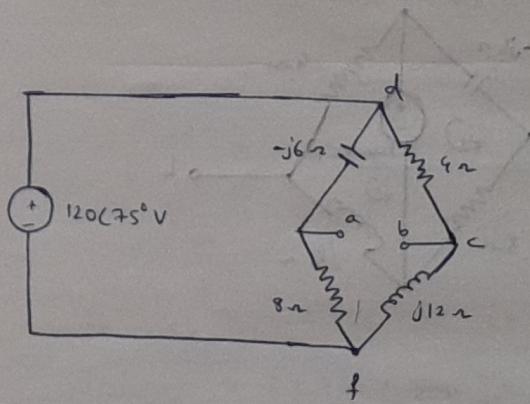

Find Thévenin's Eq. ckt.
and Norton's Eq. ckt.

$\frac{V_{Th}}{Z_{Th}}$:

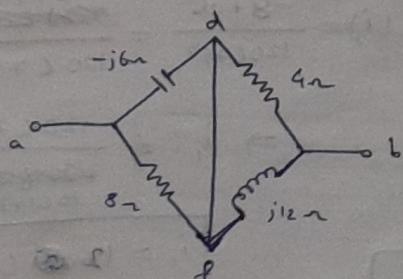

$$Z_{Th} = -j6 \parallel 8 \Omega + 4 \parallel j12 \Omega$$

$$= \frac{-48j}{8-6j} + \frac{j48}{4+j12j}$$

$$\therefore Z_{Th} = j48 \left(\frac{1}{4+j12j} - \frac{1}{8-6j} \right)$$

$$= j48 \left(\frac{8-6j-4-j2j}{104+72j} \right)$$

$$= 48 \left(\frac{18+4j}{104+72j} \right)$$

$$\Rightarrow Z_m = 48 \left(\frac{9+2j}{52+36j} \right)$$

$$= 24 \left(\frac{9+2j}{26+18j} \right)$$

$$= 12 \left(\frac{9+2j}{13+9j} \right)$$

$$= \frac{108 + 24j}{13 + 9j}$$


$$= \frac{110.6 \angle 12.53^\circ}{15.8 \angle 34.7^\circ}$$

$$Z_m = 7 \angle -22.17^\circ \Omega$$

$$= 6.48 - 2.64j \Omega$$

$$Z_m = 6.48 - 2.64j \Omega$$

For finding V_m :

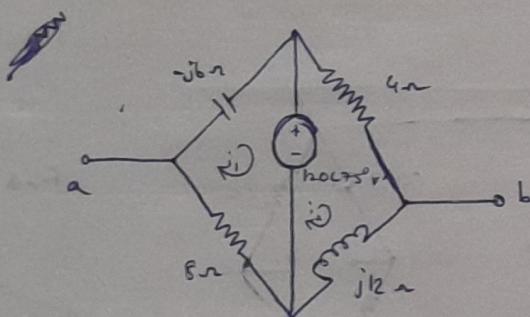

$$-8i_1 + j6i_1 - 120 \angle 75^\circ = 0 \quad \text{---(1)}$$

$$120 \angle 75^\circ = i_1 (-8 + j6)$$

$$120 \angle 75^\circ - 4i_2 - j12i_2 = 0$$

$$\Rightarrow 120 \angle 75^\circ = i_2 (4 + j12)$$

$$\Rightarrow i_2 = \frac{120 \angle 75^\circ}{12.65 \angle 71.565^\circ}$$

$$i_2 = 9.4862 \angle 3.435^\circ \text{ A}$$

$$i_2 = 9.47 + 0.568j \text{ A}$$

$$(i_1)^{-1} = \frac{-8 + j6}{120 \angle 75^\circ} = \frac{10 \angle 143.13^\circ}{120 \angle 75^\circ}$$

$$\Rightarrow i_1 = \frac{120 \angle 75^\circ}{10 \angle 143.13^\circ} = 12 \angle -68.13^\circ$$

$$i_1 = 12 \angle -68.13^\circ \text{ A}$$

$$i_1 = 10.95 \angle -12.562^\circ \text{ A}$$

$$i_1 = 4.47 - 11.136j \text{ A}$$

$A_m = 38 \angle 220^\circ V$

$$V_a + j6i_1 - 4i_2 = V_b$$

$$\Rightarrow V_{ba} = j6i_1 - 4i_2$$

$$= j6(4.47 - 11.176j) - 4(9.47 + 0.568j)$$

$$= 6(11.136 + 4.42j) - 4(9.47 + 0.568j)$$

$$= \cancel{66.816} + 26.82j - 37.88 - 2.272j$$

$$= 28.936 + 24.548j$$

$$\Rightarrow V_{ba} = 37.946 \angle 90.31^\circ$$

$$V_{Tn} = V_{ab} = -28.936 - 24.548j$$

$$= 37.946 \angle 220.31^\circ$$

$$V_{Tn} = 37.946 \angle 220.31^\circ$$

$$\therefore I_N = \frac{V_{Tn}}{Z_n} = \frac{38 \angle 220^\circ}{7 \angle -22.17^\circ}$$

$$I_N = 5.4286 \angle 242.17^\circ$$

6/11/23

AC Power Analysis : (CHAPTER - 11)

(i) Instantaneous Power :

$$P(t) = V(t) \times i(t)$$

Power is absorbed by any electrical load at any instant of time.

Rate at which Power is being absorbed.

Non-measurable Power by any Instrument.

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = i_m \cos(\omega t + \theta_i)$$

$$\Rightarrow P_t = V(t) \times i(t)$$

$$= V_{\min} i_m \cos(\omega t + \theta_v) \cdot \cos(\omega t + \theta_i)$$

$$\Rightarrow P(t) = V_{\min} \left[\frac{1}{2} (\cos(\omega t + \theta_v - \omega t - \theta_i)) + \frac{1}{2} (\cos(\omega t + \theta_v + \omega t + \theta_i)) \right]$$

$$= V_{\min} \left[\frac{1}{2} \cos(\theta_v - \theta_i) + \frac{1}{2} \cos(2\omega t + \theta_v + \theta_i) \right]$$

$$= \underbrace{\frac{1}{2} V_{\min} \cos(\theta_v - \theta_i)}_{\text{Constant Power}} + \underbrace{\frac{1}{2} V_{\min} \cos(2\omega t + \theta_v + \theta_i)}_{\text{Sinusoidal Power at } 2\omega t \approx 0}$$

(Time Independent)

[Cannot be measured]

(ii) Average Power :

Area Under the curve
Base

i.e. Average of Instantaneous Power over a cycle.

$$P = \frac{1}{T} \int_0^T p(t) dt$$

$$\Rightarrow P = \frac{1}{T} \int_0^T \frac{1}{2} V_m \sin(\omega t) (\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)) dt$$

$$= \frac{V_m \cdot i_m}{2T} \int_0^T \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i) dt$$

$$= \frac{V_m \cdot i_m}{2T} \left[T \cos(\theta_v - \theta_i) + \frac{\sin(2\omega T + \theta_v + \theta_i)}{2\omega} \right]_0^T$$

$$= \frac{V_m \cdot i_m}{2} \left[\cos(\theta_v - \theta_i) + \frac{\sin(2\omega T + \theta_v + \theta_i)}{2\omega T} - \frac{\sin(\theta_v + \theta_i)}{2\omega T} \right]$$

$$= \frac{1}{2} V_m \cdot i_m \left[\cos(\theta_v - \theta_i) + \frac{2 \cos(\omega T + \theta_v + \theta_i) \cdot \sin(\omega T)}{2\omega T} \right]$$

$$= \frac{1}{2} V_m \cdot i_m \left[\cos(\theta_v - \theta_i) + \frac{\cos(\omega T + \theta_v + \theta_i) \cdot \sin(\omega T)}{\omega T} \right]$$

$$= \frac{1}{2} V_m \cdot i_m \left[\cos(\theta_v - \theta_i) + \frac{\cos(2\pi + \theta_v + \theta_i) \cdot \sin(2\pi)}{\omega T} \right]$$

$$\omega = \frac{2\pi}{T}$$

$$P_{avg.} = \frac{1}{2} V_m \cdot i_m \cos(\theta_v - \theta_i)$$

$$\sin(2\pi) = 0$$

Not time dependent

Purely Resistive Load case : $\theta_v = \theta_i$

(2n Phase)

$$\therefore P = \frac{1}{2} V_m \cdot i_m$$

Purely Reactive Load Case : $\theta_v - \theta_i = \pm 90^\circ$

$$P = 0$$

Current lags Voltage by 90° in Purely Inductive Load.

Voltage lags current by 90° in Purely Capacitor load.

$P=0$ means that the circuit absorbs no average Power.

Q) Calculate $P(t)$ and P_{avg} . of Passive linear Network

$$V(t) = 120 \cos(377t + 45^\circ) V$$

$$i(t) = 10 \cos(377t - 10^\circ) A$$

$$P = \frac{1}{2} V_m \cdot I_m (\cos(\theta_v - \theta_i))$$

$$= \frac{1}{2} \times 10 \times 120 \times \cos(55^\circ)$$

$$= 600 \cos(55^\circ)$$

$$= 344.146 W$$

$$\therefore P_{avg} = 344.146 W$$

[50 Hz]

$$P(t) = \frac{1}{2} V_m i_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_{min} \cos(2\omega t + \theta_v + \theta_i)$$

$$= 344.146 + 600 \cos(2\omega t + 35^\circ)$$

$$P(t) = 344.146 + 600 \cos(6754t + 35^\circ) W \quad [\omega = 377]$$

Q) $V(t) = 330 \cos(10t + 20^\circ) V$

$$i(t) = 33 \sin(10t + 60^\circ) A$$

Calculate P and $p(t)$

$$P = \frac{1}{2} \times 330 \times 33 \times \cos(20 - 40^\circ)$$

$$= \frac{1}{2} \times 330 \times 33 \times \cos(50^\circ)$$

$$\Rightarrow P = 3.5 kW$$

$$33 \sin(10t + 60^\circ)$$

$$= 33 \cos(90 - (10t + 60^\circ))$$

$$= 33 \cos(10t - 30^\circ)$$

$$P(t) = 3.5 \text{ kW} + \frac{1}{2} \times 330 \times 13 \times \cos(20t - 10^\circ)$$

$$\therefore \phi(t) = 3.5 \text{ kW} + 5.445 \cos(20t - 10^\circ) \text{ kW}$$

(Q) $P_{avg} = ?$

$$Z = (30 - j70) \Omega$$

$$V = 120 \text{ V}$$

$$\theta \quad V = 120 \angle 0^\circ \text{ V}$$

$$i = \frac{V}{Z} = \frac{120 \angle 0^\circ}{76.16 \angle -66.8^\circ} = A$$

$$i = 1.5756 \angle 66.8^\circ A$$

$$\therefore V = 120 \cos(\omega t) \text{ V}$$

$$i = 1.5756 \cos(\omega t + 66.8^\circ) A$$

$$P = \frac{1}{2} \times 120 \times 1.5756 \times \cos(-66.8^\circ) \text{ W}$$

$$= 60 \times 1.5756 \times \cos(66.8^\circ) \text{ W}$$

$$\Rightarrow P_{avg} = 37.2417 \text{ W}$$

(Q) ~~$\theta = -22^\circ$~~ $i = 33 \angle 20^\circ A$

$$Z = 40 \angle -22^\circ \Omega, P_{avg} = ?$$

$$V = 1320 \angle 0^\circ \text{ V}$$

$$V = 1320 \cos(\omega t + 0^\circ) \text{ V}$$


$$i = 33 \cos(\omega t + 20^\circ) A$$

$$P = \frac{1}{2} \times 1320 \times 33 \times \cos(-22^\circ)$$

$$\Rightarrow P = 20.194 \text{ kW}$$

$$\therefore P_{avg} = 20.2 \text{ kW}$$

9)

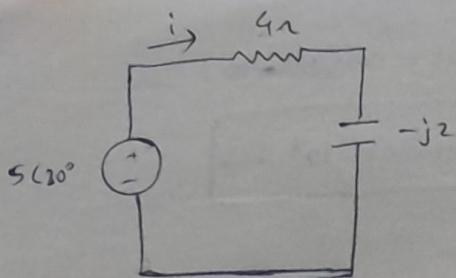

Find P_{avg_s} , P_{avg_R} , $P_{avg_{Cap}}$

$$v(t) = 5 \cos(\omega t + 30^\circ)$$

$$z = 4 - j2$$

$$i(t) = \frac{5 \angle 30^\circ}{4 + j(-2)}$$

$$i(t) = 1.1186 \angle 56.565^\circ \text{ A}$$

$$P_{avg \text{ (source)}} = \frac{1}{2} \times 5 \times 1.1186 \times \cos(30^\circ - 56.565^\circ)$$

$$\Rightarrow P_{avg \text{ source}} = 2.5 \text{ W}$$

$$P_{avg \cdot 4\Omega} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$V_{4\Omega} = 5 \angle 30^\circ \left(\frac{4}{4-j2} \right)$$

$$\Rightarrow V_{4\Omega} = 4.472 \angle 56.565^\circ$$

(Capacitor does not consume any avg. Power)

$$\therefore P_{avg_{4\Omega}} = \frac{1}{2} \times 4.472 \times 1.1186 \times \cos(0^\circ)$$

$$= 5 \text{ W}$$

$$\therefore P_{avg_{4\Omega}} = 5 \text{ W}$$

$$P_{avg_{-j2}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$V_{-j2} = 5 \angle 30^\circ \left(\frac{-j2}{4-j2} \right)$$

$$\Rightarrow V_{-j2} = 2.236 \angle -33.435^\circ$$


$$\therefore P_{avg_{-j2}} = \frac{1}{2} \times 5 \times 1.1186 \times \cos(-33.435^\circ - 56.565^\circ)$$

$$= () \times \cos 90^\circ$$

$$= 0$$

$$\therefore P_{avg \text{ cap}} = 0$$

Q)

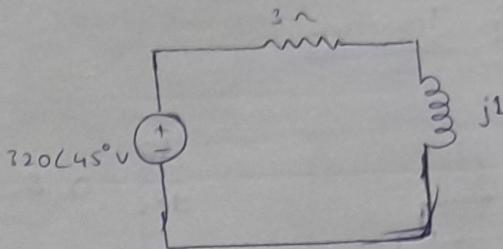

Find Avg. of source, Absorbed by Resistor & ~~Inductor~~

$$P_{avg}(\text{Inductor}) = 0 \quad \xrightarrow{\text{Reason}}$$

$$V_{j1} = 320\angle 45^\circ \times \frac{j1}{3+j1}$$

$$\& P_{avg}(\text{source}) = P_{avg}(3\Omega)$$

$$V_{j1} = 101.2 \angle 116.565^\circ$$

$$i = \frac{V}{Z} = \frac{320\angle 45^\circ}{2.1628(18.435^\circ)}$$

$$\Rightarrow i = 101.2 \angle 26.565^\circ \text{ A}$$


$$\therefore P_{avg} = \frac{1}{2} V_m R_m \cos(\alpha - \phi)$$

$$= \frac{1}{2} V_m R_m \cos 90^\circ \\ = 0$$

$$P = \frac{1}{2} \times 320 \times 101.2 \times \cos(45^\circ - 26.565^\circ)$$

$$\therefore P_{avg} = 15361.1 \text{ W}$$

$$P = 15.36 \text{ kW} \rightarrow \text{Source}$$

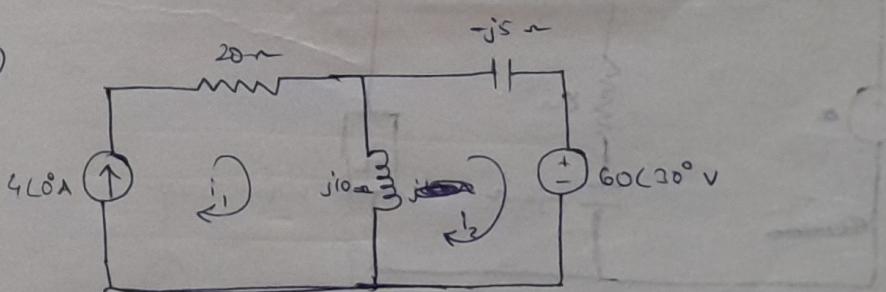H.W
Q)

Find Avg. Power generated by each source and
Avg. Power absorbed by each passive element.

$$i_1 = 4\angle 0^\circ \text{ A}$$


i2

$$-60\angle 30^\circ - j10(i_2 - i_1) + j5(i_2) = 0$$

$$\Rightarrow 60\angle 30^\circ = j10(i_2 - 4) - j5(i_2)$$

$$\Rightarrow 60\angle 30^\circ + j40^\circ = -j5 i_2$$

→ Maximum Average Power Transform :

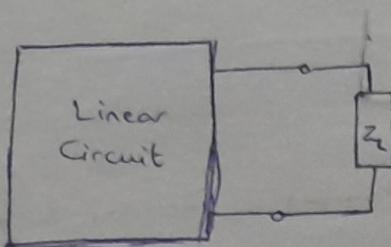

(a)


$$\frac{dP}{dR_L} = 0 \text{ & } \frac{dP}{dX_L} = 0$$

$$\Rightarrow Z_L = Z_{Th}$$

$$\begin{cases} R_L = R_{Th} \\ X_L = X_{Th} \end{cases}$$

$$Z_{Th} = R_{Th} + jX_{Th}$$

$$Z_L = R_L + jX_L$$

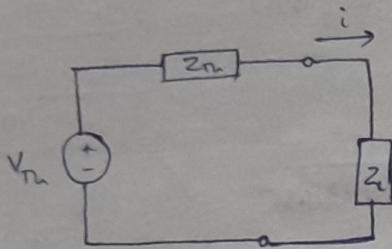

$$P_{max.} = \frac{|V_m|^2}{8R_{Th}}$$


$$X_L = -X_{Th}$$

$$R_L = R_{Th}$$


If load is purely Real,

$$R_L = |Z_{Th}|$$


(b)

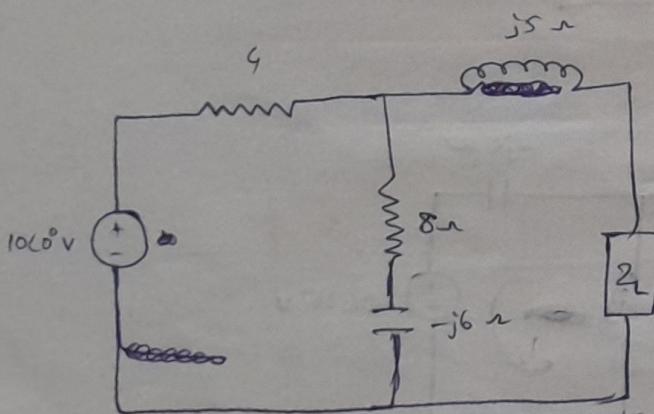

Z_{Th} :

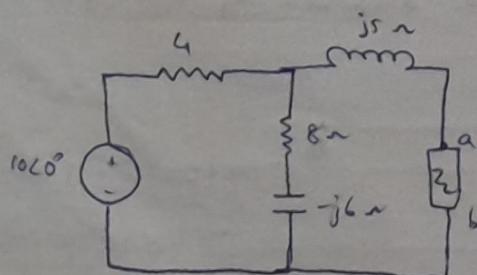

Short Sources

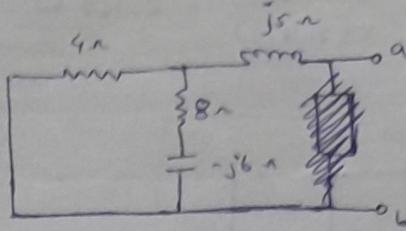

$$Z_{Th} = [(8-j6) \parallel 4\Omega] + j5$$

$$Z_{Th} = \frac{(8-j6) \times 4}{12-j6} + j5$$

$$Z_{Th} = \frac{(8-j6)(2)}{6-j3} + j5$$

~~22~~

$$= 4 \cdot \left(\frac{4-j3}{6-j3} \right) + j5$$

$$= \frac{16-j12+j30+j5}{6-j3}$$


$$= \frac{31+j18}{6-j3} = \frac{35.847 \angle 30.14^\circ}{6.71 \angle -26.565^\circ}$$

$$= 5.34 \angle 56.705^\circ$$

~~$$= 5.34 \angle 56.705^\circ$$~~

$$Z_{Th} = 2.93 + j4.46 \Rightarrow Z_L = Z_{Th} = 2.93 - j4.46$$

for V_{Th} :

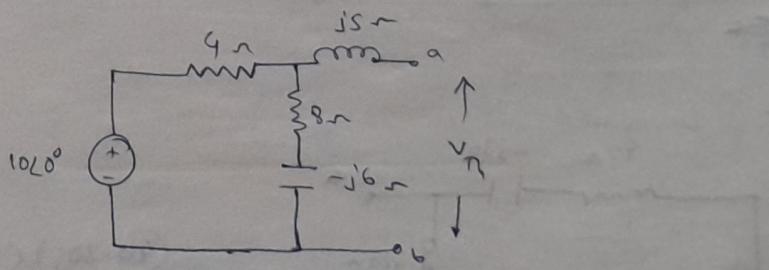


$$V_{Th} = \frac{8-j6}{4+8-j6} (10) = \frac{10 \angle -36.87^\circ}{13.416 \angle -26.565^\circ} (10)$$

$$= 7.454 \angle -10.3^\circ V$$



$$Z_L = Z_{Th} = (2.93 - j4.46) \Omega$$

$$P_{\max.} = \frac{V_m^2}{8R_L} = \frac{(7.454)^2}{8(2.933)} = 2.368 \text{ W}$$

Q)

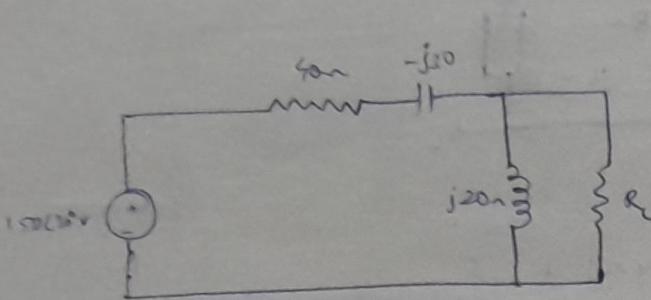

for finding V_{ab} :

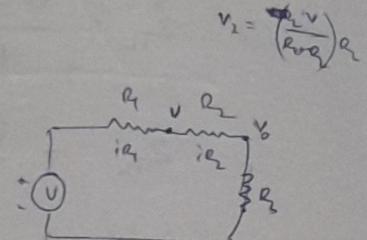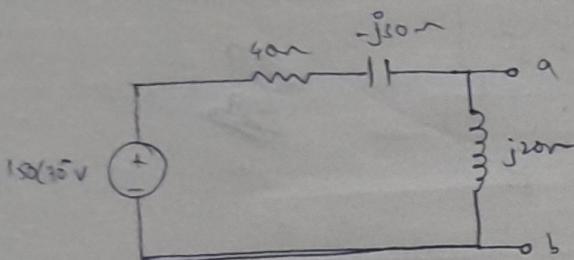

$$V_0 = U - iR_1 - iR_L = U_0$$

$$V_{Th} = V_{ab} = (150 \angle 30^\circ) \left(\frac{-j20}{40 - j10} \right)$$

$$Z_{eff} = 40 - j10$$


$$= (150 \angle 30^\circ) \left(\frac{20 \angle 90^\circ}{41.23 \angle -14.03^\circ} \right) \Rightarrow$$

~~$$V_{Th} = 600 \angle 156.8^\circ$$~~

~~$$V_{Th} = 72.761 \angle 134.036^\circ$$~~

~~Z_{Th}~~

for R_{Th} :

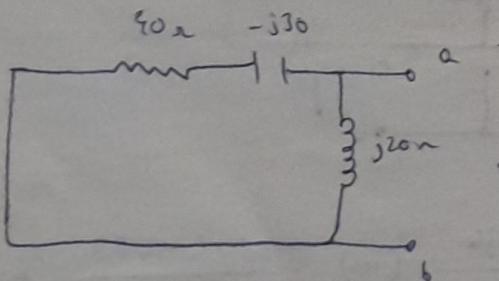

$$Z_{Th} = \frac{(40 - 30j)(20j)}{(40 - 10j)} = \frac{(50 \angle -36.87^\circ)(20 \angle 90^\circ)}{41.23 \angle -14^\circ}$$

$$R_{Th} = 9.411$$

$$Z_{Th} = Z_L = 9.411 - 22.3j$$

$$P_{\max} = \frac{(72.761)^2}{8 \times 9.411} = 70.32 \text{ W} \Rightarrow \therefore P_{\max} = 70.32 \text{ W}$$

$$\Rightarrow R_{Th} = 9.411 + 22.3j$$

$$= 24.2 \angle -67.12^\circ$$

→ Effective (or) RMS value :

Any electrical Device is rated as RMS values.

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$\text{Now } i(t) = i_m \cos(\omega t)$$

$$\Rightarrow I_{\text{rms}} = \frac{i_m}{\sqrt{2}} \quad \& \quad V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

i_m → Max value


i_{rms} → rms value

$$P = \frac{1}{2} V_m i_m \cos(\theta_v - \theta_i)$$

$$\Rightarrow P = V_{\text{rms}} \cdot i_{\text{rms}} \cdot \cos(\theta_v - \theta_i)$$

Q) Half-wave Rectified sine wave

10 ohm Resistor, Find ~~V~~ V_{RMS}

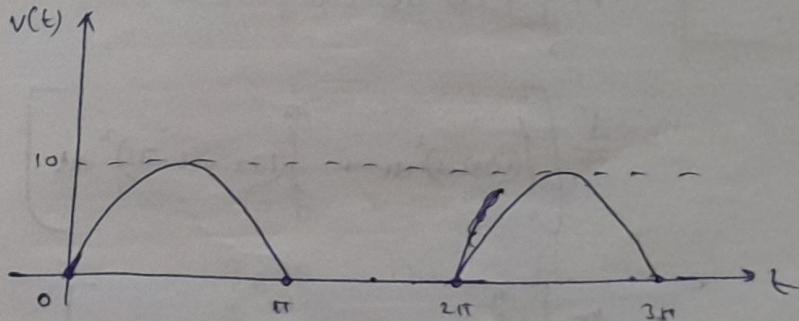

[$T = 2\pi$ is the time period]

~~Ans~~

$$v(t) = \begin{cases} 10 \sin(t) & : 0 < t < \pi \\ 0 & : \pi < t < 2\pi \end{cases}$$


$$V_{\text{rms}}^2 = \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{2\pi} \left(\int_0^\pi (10 \sin t)^2 dt + \int_\pi^{2\pi} 0 dt \right)$$

$$= 25 \text{ V}$$

$$\Rightarrow V_{\text{rms}} = 5 \text{ V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{5^2}{10} = \frac{25}{10} = 2.5$$

Q2) $R = 10\Omega$

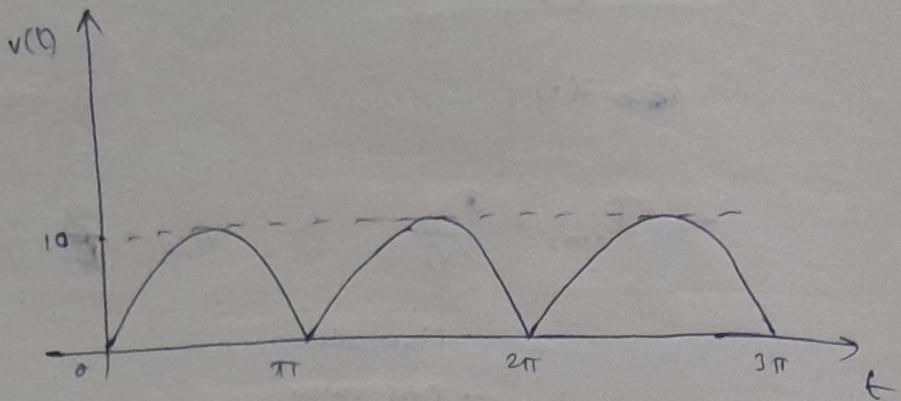

Ans : Time period, $T = 2\pi$

$$v(t) = \begin{cases} 10\sin(t), & 0 < t < \pi \\ 10\sin(t-\pi), & \pi < t < 2\pi \end{cases}$$

$$V_{rms}^2 = \frac{1}{T} \int_0^{2\pi} v^2(t) dt$$

$$= \frac{1}{2\pi} \left[\int_0^{\pi} (10\sin t)^2 dt + \int_{\pi}^{2\pi} (10\sin(t-\pi))^2 dt \right]$$

$$= \frac{100}{2\pi} \left[\int_0^{\pi} \sin^2 t dt + \int_{\pi}^{2\pi} \sin^2(\pi-t) dt \right]$$

$$= \frac{100}{2\pi} \left[\int_0^{\pi} \sin^2 t dt + \int_{\pi}^{2\pi} \sin^2 t dt \right]$$

$$= \frac{100}{2\pi} \left[\int_0^{\pi} \sin^2 t dt \right]$$

$$= \frac{50}{\pi} \times \left[\frac{t}{2} - \frac{1}{4} \sin(2t) \right]_0^{\pi}$$

$$\int \sin^2 t dt$$

$$= \int \frac{1 - \cos 2t}{2} dt$$

$$= \frac{1}{2} \int 1 - \frac{\cos(2t)}{2} dt$$

$$= \frac{t}{2}$$

$$= 50\pi \times (\pi - 0)$$

$$= 50\pi$$

$$V_{rms} = 50\pi V$$

$$\boxed{V_{rms} = 50 V}$$

$$P = \frac{V_{rms}^2}{R} = \frac{50}{10} = 5 W$$

$$\boxed{P = 5 W}$$

Apparent Power (S)

Rating of an electrical equipment.

$$P = V_{rms} \cdot i_{rms} \cdot \cos(\theta_v - \theta_i)$$

$$= Vi \cdot \cos(\theta_v - \theta_i)$$

$$\therefore P = S \cos(\theta_v - \theta_i)$$

Active Power $[S = V_{rms} \times i_{rms}]$

$$\& [\cos(\theta_v - \theta_i) = pf]$$

P : Avg. Power (or)
Real Power (or)
Useful Power.

Power factor $\equiv \cos(\theta_v - \theta_i)$

$\theta_v - \theta_i$ = Phase diff. b/w v and i .

Units of S : VA or Volt-amperes.

Units of P : Watt

~~Power factor $\frac{P}{S}$~~

Power factor $= \frac{P}{S}$

Purely Resistive Load (R) $\Rightarrow \theta_v - \theta_i = 0 \Rightarrow P/s = 1$, All Power is being Consumed
 $Pf = 1$
[Unity Power factor]

Purely Reactive Load (L or C) $\Rightarrow \theta_v - \theta_i = 90^\circ \Rightarrow P/s = 0$, No Real power consumption
 $Pf = 0$

Resistive & Reactive Load (R and L or C) $\Rightarrow \theta_v - \theta_i > 0 \Rightarrow$ lagging (Inductive Load)
 $\theta_v - \theta_i < 0 \Rightarrow$ leading (Capacitive load)

90% of Real loads are RL loads.


Current lags behind Voltage

Power factor \propto Efficiency \propto Performance

$$0 \leq \text{Power factor} \leq 1$$

We use Capacitor invariably as a condenser in electrical loads in order to improve the Power factor.

\rightarrow Complex Power:

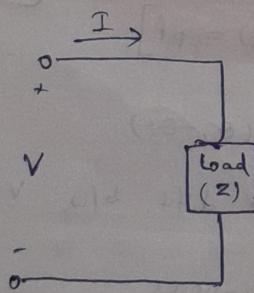

$$V = V_m \angle \theta_v$$

$$i = i_m \angle \theta_i$$

$$V_i = V_i (\cos \theta + j \sin \theta)$$

$$= V_i \cos \theta + j V_i \sin \theta$$

$$\text{P} = V_{rms} \cdot i_{rms}$$

$$S = V_i^*$$

$$= V_{rms} \cdot i_{rms} \cdot L(\theta_v - \theta_i)$$

$$S = P + Qj$$

$$\Rightarrow S = V_{rms} \cos(\theta_v - \theta_i) - \cancel{V_{rms} \sin(\theta_v - \theta_i)}$$

$$+ j V_{rms} \sin(\theta_v - \theta_i)$$

$$S = P + jQ$$

Q: Reactive Power

$$S = P + j\varphi$$

S: Apparent Power (VA)

P: Real Power (W)

$$\downarrow \text{v} \cos \theta$$

Q: Reactive Power (VAR)

$$\downarrow \text{v} \sin \theta = V_{rms} \cdot I_{rms} \cdot \sin(\theta_v - \theta_i)$$

$\varphi = 0$ for Resistive Loads (Unity pf)

$\varphi < 0$ for Capacitive Loads (Leading pf)

$\varphi > 0$ for Inductive Loads (Lagging pf)

Reactive Power: The power which allows the work to happen (Power required to create magnetic field)


$$S = V_{rms} \cdot I_{rms} \cos(\theta_v - \theta_i) + j V_{rms} \cdot I_{rms} \underbrace{\sin(\theta_v - \theta_i)}_{\varphi}$$
$$P + j \varphi$$

Apparent Power, $S = |S|$

Real Power, $P = \operatorname{Re}(S)$

Reactive Power, $\varphi = \operatorname{Im}(S)$
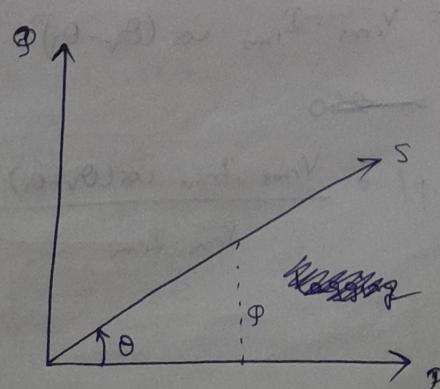
$$\text{pf} = P/S = \cos(\theta_v - \theta_i)$$



$$\cos \theta = \frac{P}{S}$$

$$S = P + j\varphi = \sqrt{P^2 + \varphi^2}$$

Purely Resistive Load (R) $\Rightarrow \theta_v - \theta_i = 0 \Rightarrow P_f = 1$, All Power is being Consumed

Purely Reactive Load (C or L) $\Rightarrow \theta_v - \theta_i = 90^\circ \Rightarrow P_f = 0$, No Real Power consumption

Resistive & Reactive Load (R and X) $\Rightarrow \theta_v - \theta_i > 0 \Rightarrow$ lagging (Inductive load) [Pcs]
 $\theta_v - \theta_i < 0 \Rightarrow$ leading (Capacitive load)

90% of Real loads are RL loads.


Current lags behind Voltage

Power factor \propto Efficiency \propto Performance

$$0 \leq \text{Power factor} \leq 1$$

We use Capacitor invariably as a condenser in electrical loads in order to improve the Power factor.

\rightarrow Complex Power:

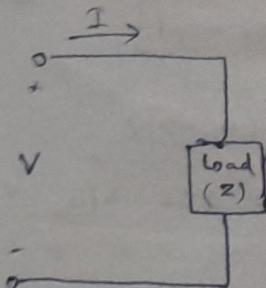

$$V = V_m \angle \theta_v$$

$$i = i_m \angle \theta_i$$

$$V_i = V_i (\cos \theta + j \sin \theta)$$

$$= V_i \cos \theta + j V_i \sin \theta$$

$$\therefore P = V_{rms} \cdot i_{rms}$$

$$S = V_i^*$$

$$= V_{rms} \cdot i_{rms} \cdot (\theta_v - \theta_i)$$

$$S = P + Qj$$

$$\Rightarrow S = V_{rms} (\cos(\theta_v - \theta_i) - \cancel{j \sin(\theta_v - \theta_i)}) + j V_{rms} \sin(\theta_v - \theta_i)$$

$$\boxed{S = P + jQ}$$

\textcircled{Q} : Reactive Power

$$S = P + jQ$$

S : Apparent Power (VA)

P : Real Power (W)

$\downarrow \text{ vice: } \theta$

Q : Reactive Power (VAR)

$$\downarrow \text{vising} = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \sin(\theta_v - \theta_i)$$

$Q = 0$ for Resistive Loads (Unity pf)

$Q < 0$ for Capacitive Loads (Leading pf)

$Q > 0$ for Inductive Loads (Lagging pf)

Reactive Power: The power which allows the work to happen (Power required to create magnetic field)


$$S = \underbrace{V_{\text{rms}} \cdot I_{\text{rms}} \cos(\theta_v - \theta_i)}_P + \underbrace{j V_{\text{rms}} \cdot I_{\text{rms}} \cdot \sin(\theta_v - \theta_i)}_{j Q}$$

Apparent Power, $S = |S|$

Real Power, $P = \text{Re}(S)$

Reactive Power, $Q = \text{Im}(S)$

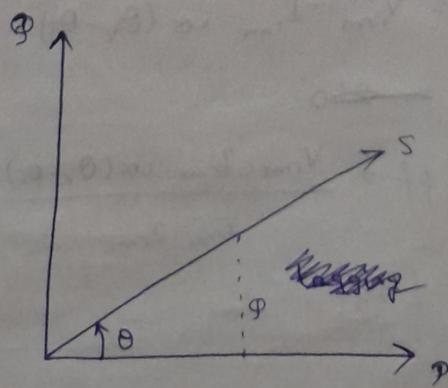
$$\text{pf} = P/S = \cos(\theta_v - \theta_i)$$




$$\cos \theta = \frac{P}{S}$$

$$S = P + jQ = \sqrt{P^2 + Q^2}$$

(Lagging)

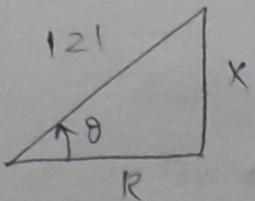
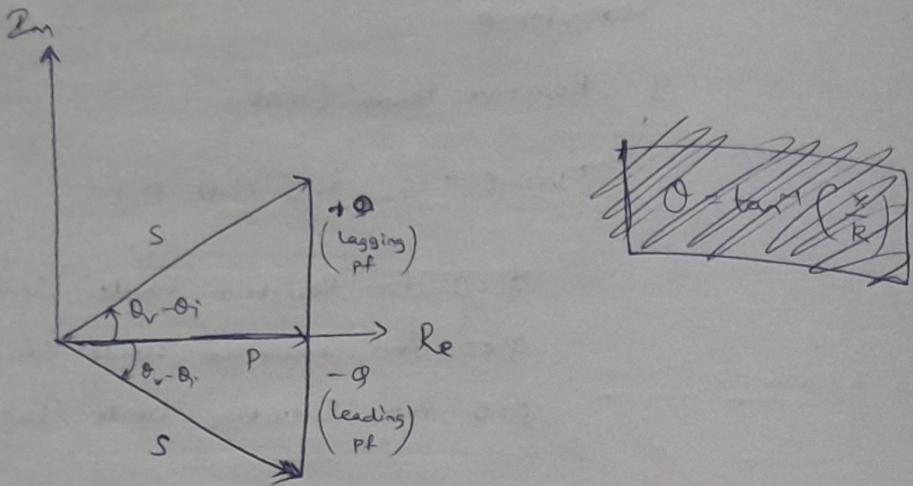
$$\theta = \tan^{-1}\left(\frac{X}{R}\right)$$



Q) ~~Answer the following~~

$$i(t) = 4 \cos(100\pi t + 10^\circ) \text{ A}$$

$$v(t) = 120 \cos(100\pi t - 20^\circ) \text{ V}$$

$$\text{Apparent Power} = V_{\text{rms}} \cdot I_{\text{rms}}$$

$$\Rightarrow S = \cancel{4} \times \frac{4}{\sqrt{2}} \times \frac{120}{\sqrt{2}} \text{ VA}$$

$$\Rightarrow S = 240 \text{ VA}$$

$$\text{Power factor} = \frac{P}{S}$$

$$P = V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos(\theta_V - \theta_I)$$

~~240~~

$$\Rightarrow \text{pf} = \frac{V_{\text{rms}} \cdot I_{\text{rms}} \cdot \cos(\theta_V - \theta_I)}{V_{\text{rms}} \cdot I_{\text{rms}}} = \cos(\theta_V - \theta_I)$$

$$= \cos(-30^\circ)$$

$$= \frac{\sqrt{3}}{2} \leftarrow \text{Negative}$$

$$= 0.866 \leftarrow$$

Capacitive $\Leftarrow [\because \text{Leading}]$

$$\Rightarrow \text{pf} = \frac{R}{Z}$$


$$Z = \frac{V}{I} = \frac{120 \cos(100\pi t - 20^\circ)}{4 \cos(100\pi t + 10^\circ)} \approx \frac{120 \angle -20^\circ}{4 \angle 10^\circ} \approx$$

$$\Rightarrow Z = 30 \angle -30^\circ \Omega$$

$$\Rightarrow Z = 25.98 - j15 \Omega$$

$$\cos(-30^\circ) = 0.866 \leftarrow \text{[Leading]}$$
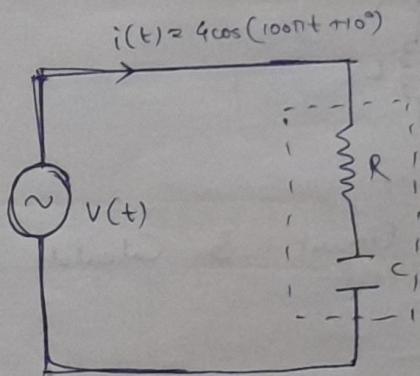
$$\tan^{-1}\left(\frac{-15}{25.98}\right) = \tan^{-1}(0.577) \\ = -30^\circ$$



$$Z_L = R + jX_C, X_C = -j15 \\ = 25.98 - j15 \quad \swarrow$$

$$X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} \\ \Rightarrow -15j = -\frac{j}{\omega C}$$

$$(\omega = 100\pi)$$

↓

$$C = 212.2 \mu F$$

$$\& R = 25.98 \Omega$$

Q) Find pf and App. Power

$$Z = 60 + j40 \Omega$$

$$V(t) = 320 \cos(377t + 10^\circ) V$$

$$\therefore i = \frac{V(t)}{Z} = \frac{320 \angle 10^\circ}{72.111 \angle 33.7^\circ} = 4.44 \angle -23.7^\circ A$$

$$\therefore i = 4.063 - j1.78 A$$

$$S = V_{rms} \cdot I_{rms} = \frac{320}{\sqrt{2}} \times \frac{4.44}{\sqrt{2}} = 710.4 \text{ VA}$$

$$pf = \frac{V_{rms} \cdot I_{rms} \cdot \cos(\theta_r - \theta_i)}{V_{rms} \cdot I_{rms}} = \frac{P}{S}$$


$$= \cos(10^\circ - 21.69^\circ)$$

$$= \cos(-11.69^\circ)$$


$$\Rightarrow pf = 0.832 (+) \text{ Lagging}$$

[Lagging]

↳ Inductive Load

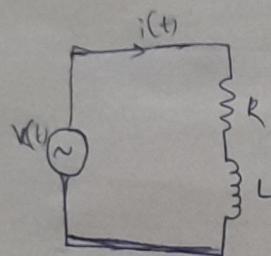

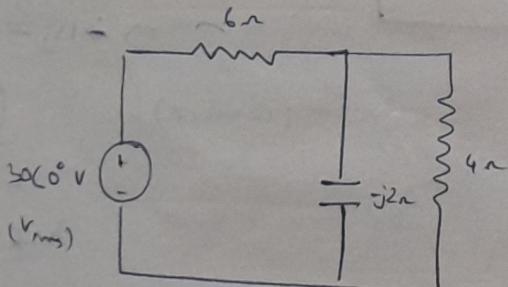Q) Determine pf of Entire Circuit & Calculate Avg. Power



~~Z_{eq}~~ $Z_{eq} = \frac{4 \times (-j2)}{4 - j2} + 6$

$= \frac{-j8}{4 - j2} + 6$

$= \frac{-j8(4 + j2)}{16 + 4} + 6$

$= \frac{-j2(4 + j2)}{5} + 6$

$= \frac{4 - j8}{5} + 6 = \frac{34 - j8}{5}$

$$Z_{eq} = 6.8 - 1.6j \Omega \Rightarrow Z_{eq} = 6.985 \angle -13.24^\circ$$

$$\theta = \tan^{-1} \left(\frac{-1.6}{6.8} \right)$$

$$\varphi = \frac{30^\circ - 13.24^\circ}{6.985} = 12.74^\circ$$

$$\approx \tan^{-1} (-0.235)$$

$$\Rightarrow I_{rms} = 4.29 \angle 13.24^\circ A$$

$$\Rightarrow \theta = 13.24^\circ \text{ (Leading)}$$

$$\cos \theta = pf = \cos(13.24^\circ) = 0.973$$

$$\therefore [pf = 0.973] \text{ [Leading]}$$

$$\Phi \quad S = (V_{rms}) \cdot (I_{rms}) = \left(\frac{320}{\sqrt{2}} \right) \times \left(\frac{4.296}{\sqrt{2}} \right)$$

$$S = 188 \text{ VA}$$

$$P = \underline{188 \times 0.973} = 125 \text{ W}$$

$$(OR) \quad P = I^2 R_L = (4.296)^2 \times 6.8 = 125 \text{ W}$$

$$\text{Q) } V(t) = 60 \cos(\omega t - 10^\circ) \text{ V}$$

$$I(t) = 1.5 \cos(\omega t + 50^\circ) \text{ A}$$

(a) Find Complex & Apparent Power

(b) Find Real & Reactive Powers

(c) Power Factor & Load Impedance

$$(a) \quad S = V_{rms} \cdot I_{rms} \text{ (Apparent Power)}$$

$$= \frac{60}{\sqrt{2}} \times \frac{1.5}{\sqrt{2}}$$

$$S = 45 \text{ VA}$$

$$S = V_{rms} \cdot I_{rms} \angle 0^\circ - 0^\circ \text{ (Complex Power)}$$

$$= 45 \angle (-10^\circ - 50^\circ)$$

$$\Rightarrow [S = 45 \angle -60^\circ (\text{VA}) \Rightarrow S = 22.5 - 38.92j \text{ (VA)}]$$

(b) Real Power & Reactive Power

$$S = 22.5 - 38.97j$$

↓ ↓
P Q

P: Real Power

Q: Reactive Power

$$\boxed{P = 22.5 \text{ W}}$$

$$\boxed{Q = -38.97 \text{ VAR}}$$

$$(C) \quad pf = \frac{V_{rms} \cdot P_{rms} \cdot \cos(\theta_r - \theta_i)}{V_{rms} \cdot I_{rms}} = \cos(\theta_r - \theta_i)$$


$$pf = \cos(-10^\circ - 50^\circ)$$

$$= \cos(-60^\circ) \quad (-)$$

~~$$-0.5 = 0.5$$~~

$$\boxed{pf = (-)0.5} \rightarrow \text{Leading}$$

\hookrightarrow Capacitive Load

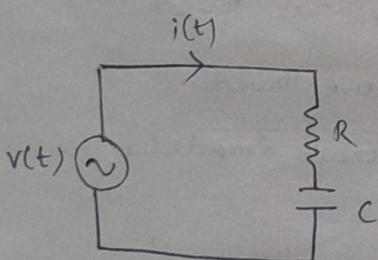

~~$$Z_L = R + jX_C$$~~

$$\Rightarrow Z_L = 20 - j34.64$$

$$Z = \frac{v(t)}{i(t)} = \frac{60 \angle -10^\circ}{1.5 \angle 50^\circ}$$

$$= 40 \angle -60^\circ$$

$$= 20 - j34.64$$

$$X_C = 34.64j = \frac{1}{\omega C}$$

$$\Rightarrow -34.64j = -\frac{j}{\omega C}$$

$$\Rightarrow C = \frac{1}{34.64 \times 10^{-3}}$$

$$\boxed{C = \frac{1}{34.64 \times 10^{-3}} \text{ F}}$$

$$H.W \quad (g) \quad V_{rms} = 110 \angle 85^\circ V$$

$$I_{rms} = 0.4 \angle 15^\circ A$$

Calculate (a), (b), (c)

Ans : (a) $44 \angle 70^\circ \text{ VA}$

44 VA

(b) 15.05 W

41.35 VAR

(c) 0.342 (lagging)

$$94.06 + j258.4 \text{ VA}$$

$$(a) \quad S = V_{rms} \cdot I_{rms} \quad [\text{Apparent Power}]$$

$$= \frac{110}{\sqrt{2}} \times \frac{0.4}{\sqrt{2}}$$

$$= 22 \text{ VA}$$

$$\boxed{S = 22 \text{ VA}}$$

$$S = V_{rms} \cdot I_{rms} \cdot \cos(\theta_v - \theta_i) \quad [\text{Complex Power}]$$

$$= \frac{110}{\sqrt{2}} \times \frac{0.4}{\sqrt{2}} \times \cos(85^\circ - 15^\circ)$$

$$= 22 \angle 70^\circ \text{ VA} = 7.524 + 20.67j$$

$$\boxed{S = 7.524 + 20.67j}$$

$$\boxed{S = 22 \angle 70^\circ \text{ VA}}$$

$$(b) \quad S = 7.524 + 20.67j$$

$$\begin{array}{c} \downarrow \\ P \end{array} \quad \begin{array}{c} \downarrow \\ Q \end{array}$$

P: Real Power

Q: Reactive Power

$$\boxed{P = 7.524 \text{ W}}$$

$$\boxed{Q = 20.67 \text{ VAR}}$$

$$(c) \quad \text{pf} = \cos(\theta_v - \theta_i) = \cos(85^\circ - 15^\circ) = \cos(70^\circ) \quad (\rightarrow)$$

15/11/22

TRANSFORMERS :

CHAPTER - 12


⇒ Transformer : Transfers energy from one circuit to another, at constant frequency (Ac) by the principle of ~~of~~ Faraday's Laws of EMI.

static Device

Power Transfer is possible by changing the voltage level.

Efficiency : 99.5% (Very High)

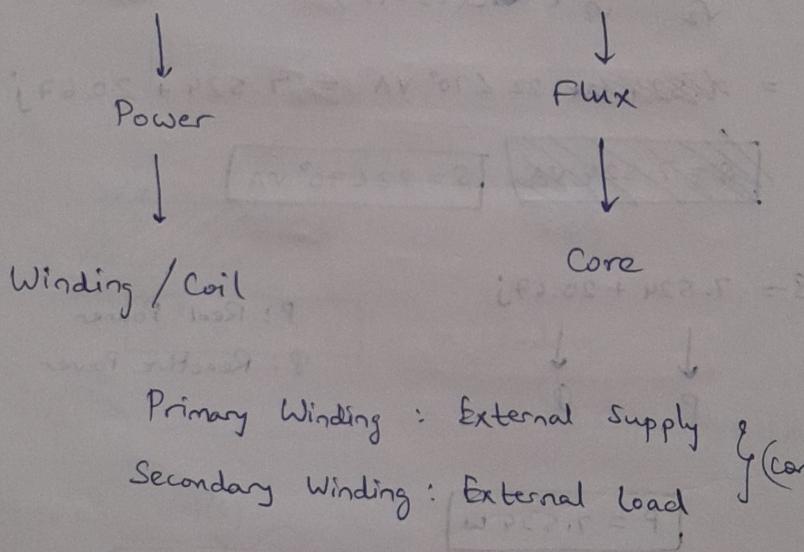Electrical Circuit \longleftrightarrow Magnetic Circuit



Both Windings are magnetically coupled but electrically isolated.

⇒ Faraday's Law of EMI :

① ~~Generator~~ Generator Law :

When A rotating conductor is placed in a uniform magnetic field, It cuts the magnetic lines of flux and EMF is introduced in it.

② Motoring Law :

When a current carrying conductor is placed in a

uniform magnetic field, then it experiences a mechanical force on it.


Both Laws produce dynamically induced EMFs.

⇒ Transformer Action:

An EMF induced in a coil is directly proportional to rate of change of flux linkage in it.

$$\text{EMF} \propto -\frac{d\phi}{dt}$$

[Negative sign indicates Lenz's Law]

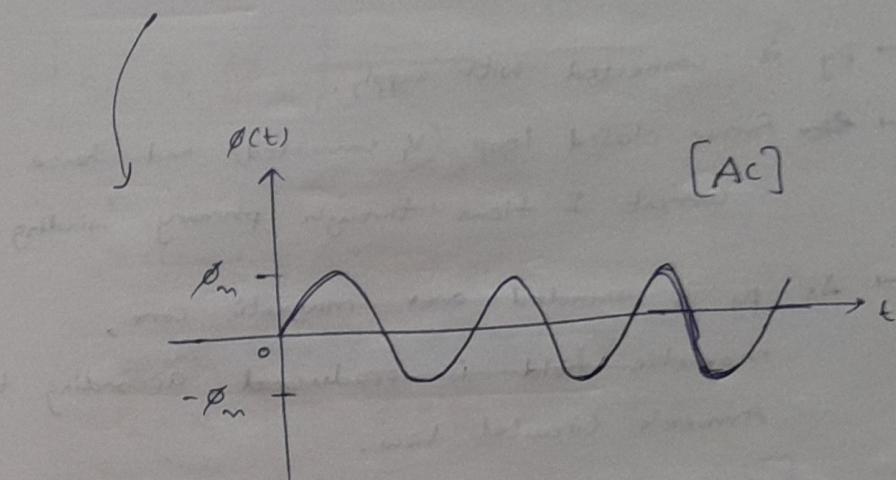


Transformer responds only to Time varying magnetic flux i.e. AC circuits, not DC.

Core : Produces Magnetic field in the Transformer

↳ Made of Magnetic Material (High Grade Silica Steel)

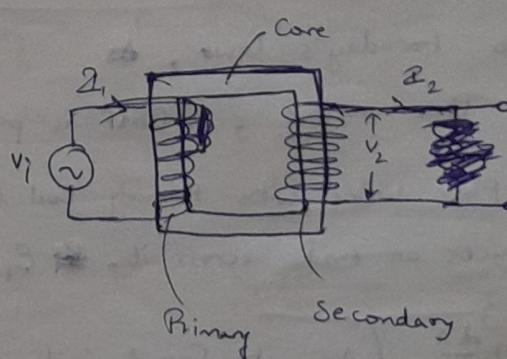↳ Minimum Energy Loss
(Minimum Reluctance)




$$P_1 = I_1 V_1$$

$$V_1 I_1 \longrightarrow V_2 I_2$$

$$P_2 = I_2 V_2$$

⇒ Basic Principle :

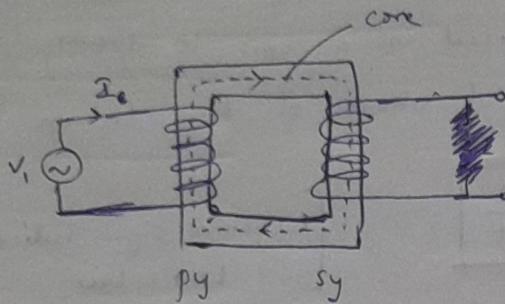


I_e : Excitation Current

- py is connected with supply.
- ~~the~~ forms closed loop (V_1 connected) and hence current I flows through primary winding.
- As py is wounded over magnetic core, magnetic field is produced according to Ampere's Circuital Law.

[Flux is confined to Magnetic Core]

- ϕ_m flows through the magnetic core

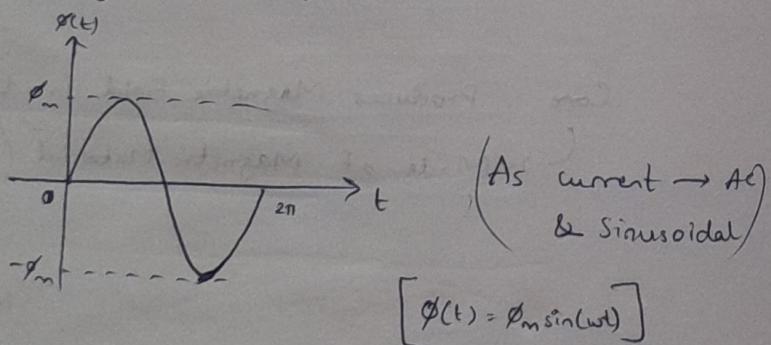

- According to Faraday's law, As ϕ is time varying, ∵ EMF is produced Magnetic Flux links with Primary Coil / Winding and it induces an emf across it, E_1

$$E \propto (-) \frac{d\phi}{dt} \quad [\text{Acc. to Faraday's law}]$$

$$E_1 = N_1 \frac{d\phi}{dt} \quad (1)$$

λ : Flux linkage
 ϕ : Flux

N_1 : No. of turns in the primary winding/coil

E_1 : EMF induced in the primary coil/windings

→ Further, the flux lines link with secondary coil/winding and hence ~~hence~~ EMF is induced in the secondary coil, E_2 .

$$E_2 = N_2 \frac{d\phi}{dt} \quad (2)$$

N_2 : No. of turns in the secondary coil/windings

$$\begin{aligned} E_1 &\propto N_1 \\ E_2 &\propto N_2 \end{aligned} \quad \left[\frac{E_1}{E_2} = \frac{N_1}{N_2} \right]$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

Transformation Ratio

$$\text{Ex. } 230/12V \rightarrow N_1 > N_2$$

(P) (S)

$$E_1 < E_2$$

[Step-Down Transformer]

16/11/23

⇒ EMF equation of a Transformer:

According to Faraday's law of EMI,

Induced EMF in coil

$$E_1 \propto \left(\frac{d\lambda}{dt} \right)$$

$$E_1 = -N_1 \frac{d\phi}{dt}$$

N_1 : No. of turns of Primary
 E_1 : EMF induced in Primary

Ignore Lenz law Temporarily,

$$E_1 = N_1 \cdot \frac{d\phi}{dt}$$

$$= N_1 \cdot \frac{d}{dt} [\phi_m \sin(\omega t)]$$

$$= N_1 \cdot \phi_m \cdot \omega \cdot \cos(\omega t)$$

$$\therefore E_1 = N_1 \phi_m \omega \cos(\omega t)$$

$$E_{1\max} = N_1 \phi_m \omega \text{ Volts}$$

$$\therefore E_{1\max} = N_1 \cdot \phi_m \cdot 2\pi f \text{ Volts}$$

$$E_{1\text{rms}} = \frac{E_{1\max}}{\sqrt{2}} = \frac{N_1 \phi_m \cdot 2\pi f}{\sqrt{2}}$$

$$= \sqrt{2} N_1 \phi_m \pi f$$

$$= 4.443 N_1 \phi_m f$$

$$\therefore E_1 = 4.443 N_1 \phi_m f \text{ Volts (RMS)}$$

where E_1 : EMF induced in primary coil (RMS)

f : Supply frequency in Hertz

ϕ_m : Max. flux in the core (Weber)

N_1 : No. of turns of Primary coil

Similarly,

$$\therefore E_2 = 4.443 \cdot N_2 \phi_m f$$

$$\therefore E_1 \propto N_1$$

$$E_2 \propto N_2$$

$$\Rightarrow \frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

Transformer Ratio

Input Power = Output Power

$$i_1 V_1 = i_2 V_2$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{i_2}{i_1} = K$$

[Ohm's law is
Violated]

$$\frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{I_1}{I_2} = k$$

if $N_2 > N_1 \Rightarrow E_2 > E_1$

↳ Step-Up Transformer

if $N_1 > N_2 \Rightarrow E_1 > E_2$

↳ Step-down Transformer

if $N_1 = N_2 \Rightarrow E_1 = E_2 \Rightarrow k = 1$

↳ 1:1 Ratio Transformer

[Isolation Transformer]

↳ Safety Purposes,

Isolates two electrically.

→ According to Application, Transformer is classified into two types :

① Power Transformer :

↳ Installed at Power Plant

Power \rightarrow MW

11 kV / 400-600 kV

\therefore Step-Up Transformer

② Distribution Transformer :

↳ Installed at Locality (House / Local)
[Consumer Premises]

Power \rightarrow kW

11 kV / 415 V Three Phase AC

\therefore Step down Transformer

$$\textcircled{P}) \quad \Phi_{\max} = 1.2 \text{ Wb/m}^2$$

$$250/3000 \text{ V} \Rightarrow E_1 = 250 \text{ V}$$

$$E_2 = 3000 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$E \text{ per turn} = 8 \text{ V}$$

Mineral
Oil
↓
Coolant

(i) find N_1 & N_2

(ii) find Area of the core

A)

$$\boxed{\Phi_{\max} = B_{\max} \cdot A_c}$$

~~$$E_2 = N_2 f$$~~

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$(i) \quad N_1 = \frac{250}{8} = 32 \text{ turns [even]}$$

$$N_2 = \frac{3000}{8} = 375 \approx 376 \text{ turns [even]}$$

$$(ii) \quad E_1 = 4.443 N_1 \Phi_{\max} f$$

$$\Rightarrow 250 = (\sqrt{2}\pi) \times 32 \times \Phi_m \times 50$$

$$\Rightarrow \frac{s}{32\pi\sqrt{2}} = B_{\max} \times A_c$$

$$\Rightarrow A_c = \frac{s}{32 \times 1.2 \pi \sqrt{2}} = 0.03 \text{ m}^2$$

$$\boxed{\therefore A_c = 293.07 \text{ cm}^2}$$

$$\textcircled{Q}) \quad N_1 = 400 \text{ turns}$$

$$N_2 = 1000 \text{ turns}$$

$$A_c = 60 \text{ cm}^2$$

$$f = 50 \text{ Hz}$$

$$E_1 = 520 \text{ V}$$

Calculate (i) ~~Φ_m~~ B_{\max}

(ii) E_2

$$\text{A) } \text{(ii)} \quad \frac{\mathcal{E}_2}{\mathcal{E}_1} = \frac{N_2}{N_1}$$

$$\Rightarrow \mathcal{E}_2 = \frac{N_2}{N_1} \times \mathcal{E}_1$$

$$= \frac{1000}{400} \times 520$$

$$= \frac{5200}{4}$$

$$\Rightarrow \boxed{\mathcal{E}_2 = 1300 \text{ V}}$$



$$\text{(i) } B_{\max} = \frac{\Phi_{\max}}{A_c} = \frac{\mathcal{E}_1}{\sqrt{2\pi} N_1 f A_c}$$

$$\text{As } \mathcal{E}_1 = (6\pi) N_1 \Phi_m f$$

$$\Rightarrow \Phi_m = \frac{\mathcal{E}_1}{\sqrt{2\pi} N_1 f}$$

$$\therefore B_{\max} = \frac{520 \times 10^4}{\sqrt{2\pi} \times 400 \times 50 \times 60} \quad [A_c = 60 \times 10^{-4} \text{ m}^2]$$

$$= \frac{520}{\sqrt{2\pi} \times 120}$$

$$= 0.975 \text{ W/m}^2$$

$$\therefore B_{\max} = 0.975 \text{ W/m}^2 \rightarrow \text{RMS Value}$$

But No Multiplication of $\sqrt{2}$

\because Magnetic Parameter do not have RMS (or) max.

H.W
Q)

$$N_1 = 500 \text{ turns}$$

$$N_2 = 50 \text{ turns}$$

$$V_1 = 3000 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$i_1 = ? , i_2 = ? \text{ (full load currents)}$$

$$\mathcal{E}_2 = ? , \Phi_m = ?$$

Neglect Leakage drop


$\frac{V_1}{V_2} = \frac{N_1}{N_2}$

25 kVA transformer

$$\text{A) } V_{rms} = 8rms = 25 \text{ kVA} \Rightarrow V_1 I_1 = V_2 I_2 = 25 \text{ kVA}$$

20/11/23

→ Transformer on No-Load :

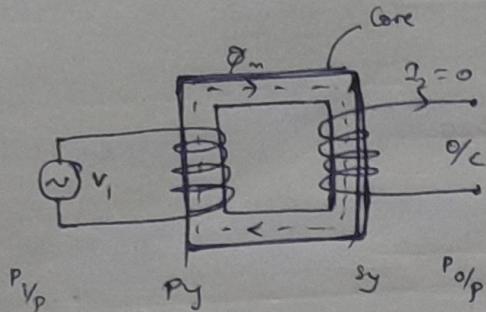

Ideal Transformer :

→ 100% Efficiency

No Losses →

- Winding loss (Copper loss)
[Ohm's Law]
- Core loss (Iron loss)
[Magnetic loss]

→ No leakage flux

→ It is not reliable in practice magnetic loss.

→ When supply is connected to P_y , I_2 flows through it.

→ P_{sy} is open circuited $\therefore I_2 = 0$

No Load is connected

$$\rightarrow P_{\text{output}} = 0 \quad \left[\because P_2 = I_2 V_2 = 0 \right]$$

↑
0

$$(P_{sy} \approx 0)$$

→ $P_{sy} = (\text{magnetic loss in the core}) + (\text{copper loss in the } P_y)$

→ No Load current (I_0) is 2 to 6% of I_{rated} .
↳ very minimum

→ P_y copper loss ($I_0^2 R$) is negligible

\therefore No Load Input Power (W_0) = Magnetic loss in the core

→ I_μ : Magnetising current

= Flux Producing Component


→ I_c : Core loss Current

= Core loss Component

$$\Rightarrow I_o = I_\mu + I_c$$

$$\boxed{I_o = I_\mu + I_c}$$

→ Phasor Diagram:

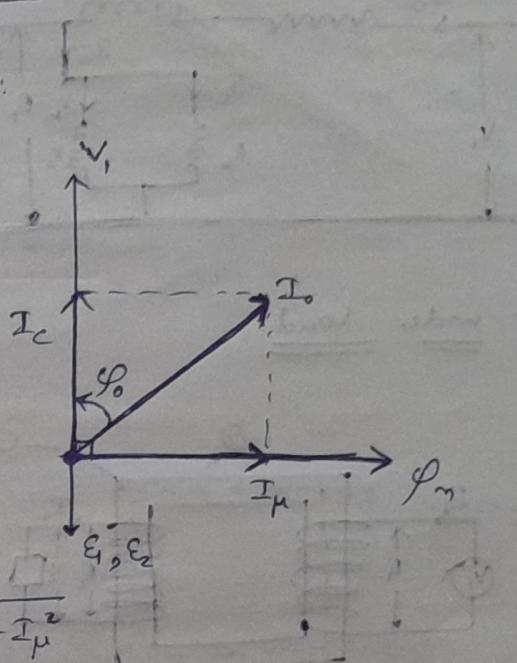

$$I_o = \sqrt{I_c^2 + I_\mu^2}$$

$$\cos(\phi_o) = \frac{I_c}{I_o}$$

$$\sin(\phi_o) = \frac{I_\mu}{I_o}$$

$$\Rightarrow I_c = I_o \cos(\phi_o)$$

$$\Rightarrow I_\mu = I_o \sin(\phi_o)$$

Note :

$$\textcircled{1} \quad I_o = \sqrt{I_c^2 + I_\mu^2}$$

$$\textcircled{2} \quad \cos(\phi_o) = \frac{I_c}{I_o}$$

$$\textcircled{3} \quad I_c = I_o \cos(\phi_o)$$

$$\textcircled{4} \quad I_\mu = I_o \sin(\phi_o)$$

No-Load Power factor ~~(cos(phi_o))~~ :


$$\phi_o < 90^\circ$$

Assume $\phi_o = 80^\circ$,


$$\cos(\phi_o) = 0.17 \text{ lagging}$$

∴ Behaves Mostly Inductive
Very low pf.

Equivalent Circuit:

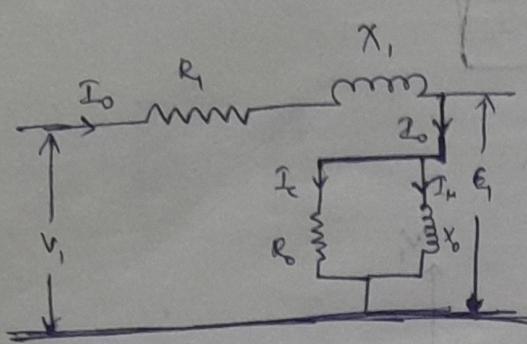


→ Transformer under Load:

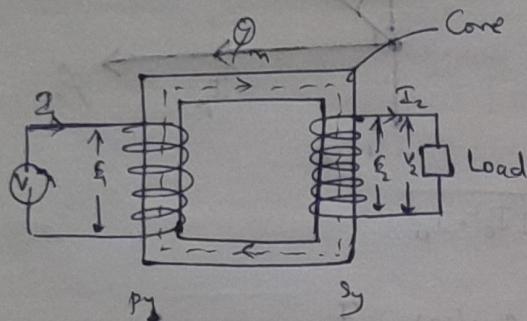

→ On load, I_2 flows

→ Flux Φ_m is constant.
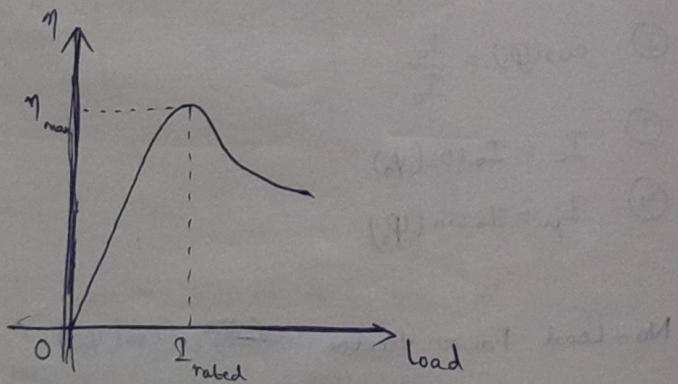
$$\text{If } I_2 \uparrow \Rightarrow P_{\text{op}} \uparrow \Rightarrow \Sigma \uparrow (\because I_2' \uparrow) \Rightarrow P_{\text{op}} \uparrow \Rightarrow \eta \uparrow$$



$$\text{Efficiency } (\eta) = \frac{\text{Output Power}}{\text{Input Power}} \times 100 \%$$

$$= \frac{P_{\text{op}} \times 100}{P_{\text{op}} + \text{Losses}} \% = \frac{B \cdot P_{\text{op}} \times 100}{P_{\text{op}} + P_{\text{core}} + P_{\text{Cu}}} \%$$

P_{core} : Constant

P_{cu} : Variable [As $P_{cu} = i^2 R$, i is variable]

$$P_{core} = P_{cu} \Rightarrow \text{Efficiency} = \text{maximum}$$

\therefore Variable loss \rightarrow Constant loss

Transformers — Rated in kVA

Motors — Rated in W or hp

Reason:

2/11/22

Electrical Machines are electromechanical energy conversion devices.

(1) Electrical Energy to Mechanical Energy

↳ Electrical Motor

(2) Mechanical Energy to Electrical Energy

↳ ~~Generators~~

Electrical Machines

1
Static
Machine

1
Transformer

1
Rotating
Machine

DC
Machinery

DC
Generator

DC
Motor

AC
Machines

Synchronous
Machine

(Power Plants)

(Alternator)
Synchronous
Generator

Asynchronous
Machine

Synchronous
Motor

Induction
Machines

o o [1 phase] \rightarrow 230V
 P N (AC)

o o o o (N: Neutral)
 R Y B N [3 phase]
 (AC)

1 phase \rightarrow Used to Transport 1 kW (Domestic)
 3 phase \rightarrow Used to Transport 3 kW (Industry)

Media for Energy conversion - Magnetic Field
 \therefore Electromagnetic conversion principle

Two electromagnetic conversion principles:

(1) Conductor moves in magnetic field

\therefore Induced Voltage in conductor

[Generator Action]

(2) Current carrying conductor placed in Magnetic field

\therefore Conductor experiences mechanical force.

[Motor action]

Fleming's Right hand Rule : (OR) curling left hand

Induced EMF direction



Thumb: Magnetic field

palm faces Magnetic Field

Index: Direction of Rotation

Curl in direction of Rotation

Middle: Induced EMF (E)

Thumb: Induced EMF

$$E \propto Blv$$

— Generator


$$T \propto bli$$

— Motor


(Q) H.W) Why Magnetic field?
Why not Electric field?

$$E = (\vec{V} \times \vec{B}) \cdot \vec{l}$$

Any Electrical Machine

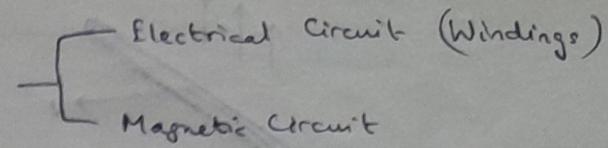

Any Electrical Machine

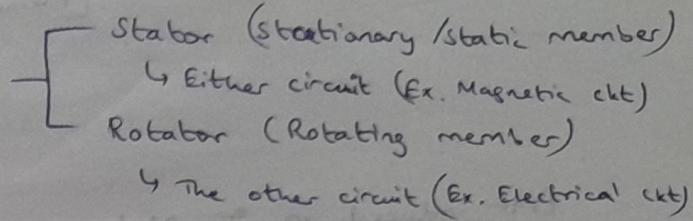

For DC machine:

Stator: Magnetic ckt (Field system)

Rotar: Electrical ckt (Armature)

$$\text{Force} = i(\vec{l} \times \vec{B}) =$$

$$|F| = ilB \text{ N}$$

$$T = \vec{r} \times \vec{F}$$

$$|T| = Fr \text{ N.m}$$

Motor

In DC machine,


Rotar is AKA Armature

& current supplied to Motor i.e. i_a is

Armature current.

$$F = i_a l B$$

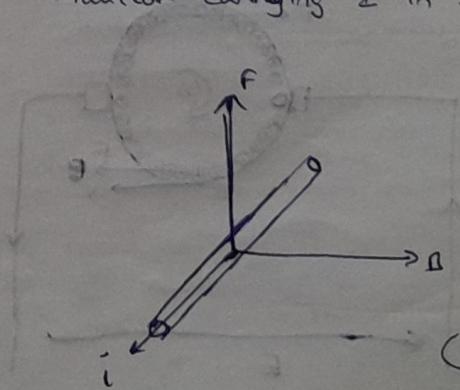(i) Force on Conductor carrying I in field B




$$F = i(\vec{l} \times \vec{B})$$

l : Length of conductor
in field.

(Fleming's Left Hand Rule)
(Motor Action)

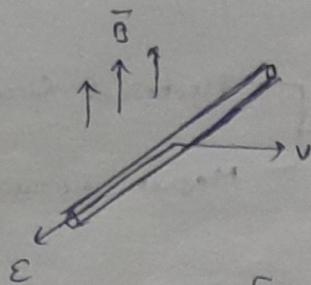(2) Voltage (E) Induced in conductor travelling in field B .



$$E = (\vec{v} \times \vec{B}) \cdot \vec{l}$$

~~$E = v(B \times l)$~~

E : Voltage Induced along length l

[Fleming's Right Hand Rule]
(Generating Action)

EMF induced in DC Motor:

$$E = NBvl \quad \therefore E = Ne$$

induced in each conductor

$v = r\omega$

induced in all conductors 'N'

[ω : Angular velocity, rad/s]

$$E = N\omega r Bl$$

$$\therefore E = kw$$

$$\boxed{E \propto \omega}$$


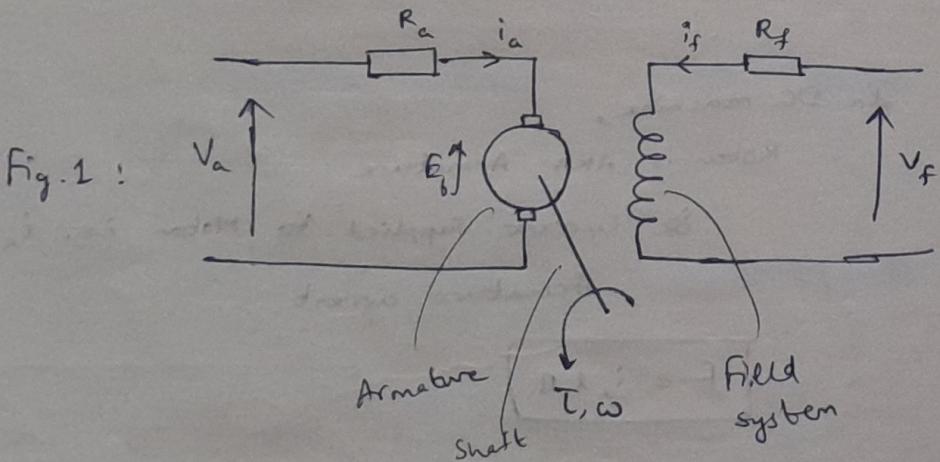


Fig. 2 :

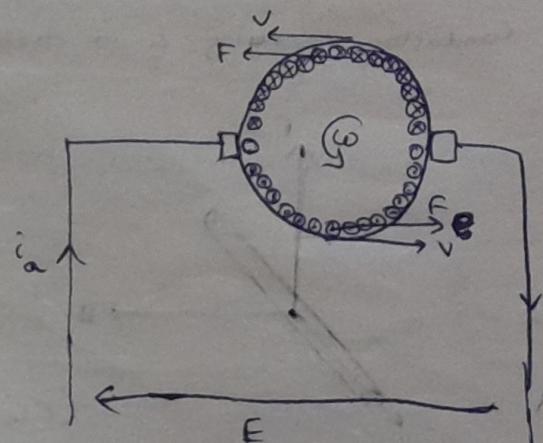

DC machine is AKA Conduction Machine.
Need current in both Armature & field system.
 \therefore No connection b/w Primary & Secondary Windings
in Transformer, Works through Mutual
Induction — AC Not DC.

DC Motor — Double Excitation Machine

\downarrow \therefore Should excite both Rotor & Stator.
Not Poppular \leftarrow Reason \rightarrow (.: Bulky & Needs maintenance)
(Outdated) \therefore Not used in Industry

Modified DC Motors : Permanent Magnet Motors
(or)

Permanent Magnets \leftarrow Brushless Motor (BLDC Motors)
Ex. NeFeDb \rightarrow ferrites \rightarrow Does not require external excitation,
(Rare Earth Metals) \therefore Field system removed $\rightarrow \eta > 90\%$ \downarrow Energy loss

Samarium Cobalt

~~DC M~~

DC Motor : Universal Motor

\hookrightarrow Works with DC current and AC current

\rightarrow Three-Phase Induction Motor:

\rightarrow ~~Most~~ Most frequently encountered machines at
households

\rightarrow Rugged, Cheap, Easy maintenance, Simple design,
wide ranges of power rating, Constant speed motor,

\rightarrow Variable speed control is difficult

\rightarrow Parts of Induction Motor:

- (i) Stator
- (ii) Rotor

Stator - Electrical ckt

Rotor - Magnetic ckt

→ Works with the principle of Transformer Action (Mutual Induction)
∴ Essentially a Rotating Transformer

Stator : Primary coil
Rotor : Secondary coil] Similarity

Supply \oplus to Stator \Rightarrow ~~Moving~~ Rotor Rotates

No connection b/w Stator & Rotor

∴ Induction principle

∴ Induction Motor

→ According to Rotor's construction, ~~Construction~~ Classified into two types :

(a) Squirrel-Cage Rotor

(b) Wound Rotor (Slip-Ring Rotor)

28/11/23

Induction Motors → Workhorse of Industry

Wound Rotor → Variable speed application

Squirrel cage Rotor → Constant speed application

Wound Rotor → high starting torque than

Squirrel cage

i.e. Motor starts with load



Ex. Lift, Train, Grinder

Adding external Rheostat

∴ Need frequent maintenance

& Efficiency is less than squirrel cage rotor.

→ How magnetic field is created:

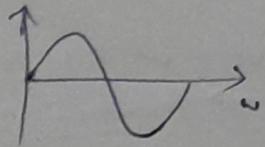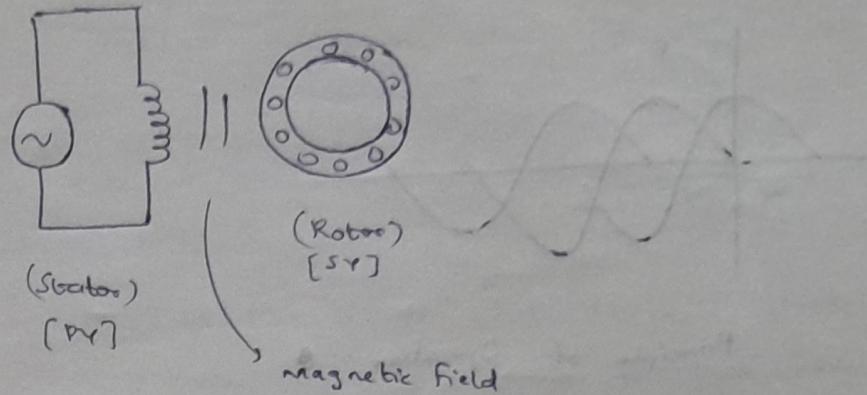

Time varying magnetic field



$$\omega = 2\pi f$$

$$\Rightarrow \omega_e = 2\pi f_e$$

f_e : Supply frequency
↳ (electrical frequency)

i.e. Revolving Magnetic Field

$$\omega_s = \frac{2}{P} \omega_e$$

↳ electrical Angular frequency
↳ mechanical Angular frequency

[P : No. of Poles]

ω_s : Synchronous speed

$$\omega_s \approx n_s = \frac{120f}{P} \text{ rpm}$$

If $f_e = 50 \text{ Hz}$,

$$\therefore \omega = 2\pi f_e = 314 \text{ rad/s}$$

$$P=2 \Rightarrow n_s = 3000 \text{ rpm} \Rightarrow \omega_s = 314 \text{ rad/s}$$

$$P=4 \Rightarrow n_s = 1500 \text{ rpm} \Rightarrow \omega_s = 157 \text{ rad/s}$$

$$P=6 \Rightarrow n_s = 1000 \text{ rpm} \Rightarrow \omega_s = 105 \text{ rad/s}$$


Max. speed available : 3000 rpm

\therefore Minimum no. of poles = 2

(N & S)

Magnetic Monopoles Don't exist.

Three Phase System:

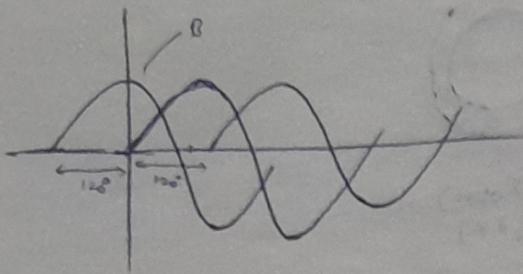

Principle of Operation:

Three Phase

- A time phase distribution of Three Phase AC Supply is given to a Three Phase Stator Winding of Production Motor which is spatially distributed.

A revolving magnetic field is created in the stator winding which runs at synchronous speed. (n_s)

This revolving magnetic field ~~cut~~ is cut by stationary rotor conductor. And hence EMF is induced in the Rotor Conductor.

As the Rotor conductors are permanently short circuited, a current flows through it.

And hence, a magnetic field is created on rotor conductors (Ampere Circuital Law)

$$F = BIL$$

$$\Rightarrow F = B_s \times B_r$$

$$T \propto (F \times r)$$

$$T = k B_R \times B_s$$

Torque is produced in the motor due to interaction of those two magnetic fields.

→ At what speed Motor will run?

$$\frac{\text{Speed of Rotating Magnetic Field of the stator}}{\text{Field of the stator}} = \frac{120f}{P} \quad (n_s)$$

$n_m \rightarrow$ Motor Speed

If $n_m = n_s$,

No Interaction between both Magnetic fields.

∴ Both Appear stationary to each other.

∴ Rotating Magnetic field will not cut the Rotor.

i.e. No Induced EMF in the Rotor.

i.e. No Current produced in the Rotor.

∴ No Magnetic field is created

∴ No Torque is Produced.

∴ Rotor speed falls below synchronous speed.

∴ Speed of Motor/Rotor should be less than synch.

speed of the magnetic field

i.e. Relative speed exists.

~~$n_m > n_s$~~ → Always for Induction Motor.

i.e. $n_m < n_s \Rightarrow$ Motoring operation takes place

↳ Asynchronous Motor

Slip Speed (n_{slip})

$$\Rightarrow n_{\text{slip}} = n_{\text{sync}} - n_m$$

$$\boxed{\therefore n_{\text{slip}} = n_s - n_m}$$

$$\boxed{\% \text{ slip} = \frac{n_s - n_m}{n_s} \times 100 \%}$$

$$\therefore S\% = \frac{n_s - n_m}{n_s} \times 100 \%.$$

$$\& n_s = \frac{120f}{P}$$

n_m : Motor speed (rpm)

If Rotor runs at synchronous speed,

$$S = 0\% \Rightarrow \text{slip} = 0$$

If Rotor is stationary,

$$S = 100\% \Rightarrow \text{slip} = 1$$

$$\text{Slip} = \frac{n_s - n_m}{n_s}$$

S , Slip \rightarrow Ratio
 \therefore No Units

Slip varies between
0 and 1 for
Induction Motor.

Full load Slip \rightarrow 4 to 6 %.

\rightarrow Frequency of an Induced EMF:

Because of slip,

frequency_{rotor} \neq frequency_{stator} in motor.

$$f_r \neq f_s$$

\nwarrow supply frequency

$\left\{ \begin{array}{l} \text{In Transformer,} \\ f_s = f_p \end{array} \right.$

$$f_r = \frac{P \times n}{120}$$

P: no. of stator Poles

$$= \frac{P(n_s - n_m)}{120}$$

S: slip

$$= \frac{P \times s n_s}{120}$$

n: slip speed (rpm)

$$= S f_e \Rightarrow$$

$$\boxed{f_r = S f_e}$$

(OR)

$$\boxed{f_r = S f_s}$$

If $S = 1 \Rightarrow f_r = f_s$

Induction Motor does not run,

It's a static device in this condition

i.e. Transformer.

30/11/22

$$\rightarrow n_{\text{slip}} = n_{\text{sync}} - n_m$$

↓ ↓ ↗
 slip speed synchronous speed Actual motor speed
 ↗ speed of revolving magnetic field of stator

$$n_{\text{sync}} = \frac{120 f_e}{P}$$

p: no. of poles

f_e: supply frequency (f_s)

$$n_m < n_{\text{sync}}$$

$$\text{If } s=1 \Rightarrow n_m = 0$$

$$\left[s = \frac{n_s - n_m}{n_s} \right]$$

$$\text{If } s < 1 \Rightarrow n_m < n_{\text{sync}}$$

$$f_r = s f_e$$

↓
supply frequency

frequency of motor induced emf

→

$$P_{\text{mech}} = T_m \times \omega_m$$

↓ ↓
 Mechanical Power developed in Inductor Motor Mechanical speed of motor (rad/s)

Torque T_m (N-m)

$$P_{\text{mech}} = \frac{T_m (2\pi n_m)}{60}$$

$$\left[\omega_m = \frac{2\pi n_m}{60} \right]$$

$$\Rightarrow P_m = \frac{2\pi (T_m \omega_m)}{60} \text{ Watts}$$



n_m : motor speed

T_m : Motor Torque / shaft Torque

$$\rightarrow 1 \text{ hp} = 746 \text{ Watt}$$

Usually Mech. power is measured in hp.

[horsepowers]



$$n_m = n_{\text{sync}} (1-s)$$

↓
motor/rotor speed

Q) 208 V, 10 Hp, four pole, 60 Hz,
 Y-connected Production Motor,
 Full load slip of 5%

- (i) $n_{\text{sync}} = ?$
- (ii) $n_m = ? @ \text{rated load}$
- (iii) $f_r = ? @ \text{rated load}$
- (iv) $T_m = ? @ \text{rated load}$

Sol:

$$P_m = \frac{2\pi(T_m)n_m}{60}$$

$$\Rightarrow 7460 \times 60 = 2\pi \times T_m \times n_m$$

$$\Rightarrow T_m \times n_m = \frac{7460 \times 60}{2\pi} - \textcircled{1} \Rightarrow T_m = \frac{7460 \times 60}{2\pi \times 1800}$$

$$\therefore T_m = 39.57653 \text{ Nm}$$

$$f_r = \frac{P \times n_m}{120}$$

$$\text{& } \text{(ii)} \quad \therefore \text{slip} = \left(\frac{n_{\text{sync}} - n_m}{n_{\text{sync}}} \right) \times 100 \%$$

$$\text{(iii)} \quad \begin{cases} \text{slip} = 0.05 \\ f_e = 60 \\ f_r = s f_e \\ = 60 \times 0.05 \\ \boxed{f_r = 3} \end{cases}$$

$$\Rightarrow s = \frac{n_{\text{sync}} - n_m}{n_{\text{sync}}} \times 100$$

$$\Rightarrow \frac{1}{20} = \frac{n_{\text{sync}} - n_m}{n_{\text{sync}}}$$

$$\Rightarrow \boxed{\frac{n_m}{n_{\text{sync}}} = \frac{19}{20}}$$

$$\Rightarrow 60 = \frac{4 \times n_{\text{sync}}}{120}$$

$$\Rightarrow \boxed{n_{\text{sync}} = 1800 \text{ rpm}}$$

$$(i) \quad f_r = \frac{P \times n_m}{120}$$

$$s f_e = \frac{P \times n_s}{120}$$

$$\Rightarrow \boxed{f_r = \frac{P \times n_s}{120}}$$

$$n_m = \frac{19}{20} \times 1800$$

$$\therefore n_m = 1710 \text{ rpm}$$



- (g) 3-Phase Cage Rotor,
 3 Poles, $f_e = 50 \text{ Hz}$
 - Pairs
 On Runs @ 960 rpm (n_m)
 $T_n = 40 \text{ Nm}$

- (i) ω of rotating field produced by stator winding
- (ii) Slip
- (iii) f_{rotor}
- (iv) Power mech.

Sol:

$$(i) n_m = n_{sync}(1-s)$$

$$n_{sync} = \frac{120 \times f_e}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\therefore n_{sync} = 1000 \text{ rpm}$$

$$(ii) \Rightarrow \frac{n_m}{n_{sync}} = 1-s$$

$$\Rightarrow \frac{960}{1000} = 1-s \Rightarrow s = \frac{40}{1000}$$

$$\therefore s = 0.04 \Rightarrow \text{Slip} = 0.04$$

$$(iii) f_r = s f_e$$

∴

$$\text{Slip} = 4\%$$

$$\Rightarrow f_{rotor} = 0.04 \times 50$$

$$\therefore f_{rotor} = 2 \text{ Hz}$$

(iv)

$$P_{mech} = \frac{2\pi \times T_n \times n_m}{60} \Rightarrow P_{mech} = \frac{2\pi \times 40 \times 960}{60}$$

$$\Rightarrow P_{mech} = 4021.24 \text{ Watts}$$

$$\therefore P_{mech} = 4.02 \text{ kW}$$

Q) 8 pole Induction Motor, $f_s = 50 \text{ Hz}$, $f_m = 1.5 \text{ Hz}$

(i) $n_m = ?$

(ii) $\text{slip} = ?$

Sol:

$$n_s = \frac{120 \times f_c}{P} \Rightarrow n_s = \frac{120 \times 50}{8}$$

$$\Rightarrow n_s = 750 \text{ rpm}$$

$$(ii) f_r = s f_c$$

$$\Rightarrow 1.5 = (s) \times 50$$

$$\Rightarrow s = \frac{1.5}{50} = 0.03$$

$$\boxed{\therefore \text{slip} = 0.03} \Rightarrow \boxed{\text{slip \%} = 3\%}$$

$$(i) n_m = n_{\text{sync}} (1-s)$$

$$\Rightarrow n_m = 750 (1 - 0.03)$$

$$\boxed{\therefore n_m = 727.5 \text{ rpm}}$$

Q) 6 pole, 3 Phase, 50 Hz Induction Motor

Full load Torque = 150 Nm

$$f_m = 120 \text{ cycles/min} \quad \text{Find } P_{\text{shaft}}$$

$$= 2 \text{ Hz}$$

$$[f_m = 2 \text{ cycles/sec}]$$

Sol:

$$P = \frac{2\pi T_m n_m}{60} = \frac{2\pi \times 150 \times 120}{60} = 5\pi \times 120$$

$$1' \text{ cycle/second} \\ 1' \text{ Hz} = \cancel{1 \text{ cycle/second}} \\ 1' \text{ Hz} = \frac{x \text{ cycles}}{1 \text{ second}}$$

~~$$f_r = \frac{P \times n_s}{120} \Rightarrow n_s = \frac{120 \times f_r}{P}$$~~

$$\Rightarrow n_s = \frac{120 \times 50}{6} = 1000$$

$$\Rightarrow \boxed{n_s = 1000 \text{ rpm}}$$

$$n_m = n_{\text{sync}} (1 - \frac{f_r}{f_c})$$


$$= 1000 \left(1 - \frac{50}{50}\right)$$

$$\therefore n_m = 960$$


$$\Rightarrow P_{\text{shaft}} = 5\pi \times 960 = 15.08 \text{ kW}$$

21/1/23


Semiconductor Diodes

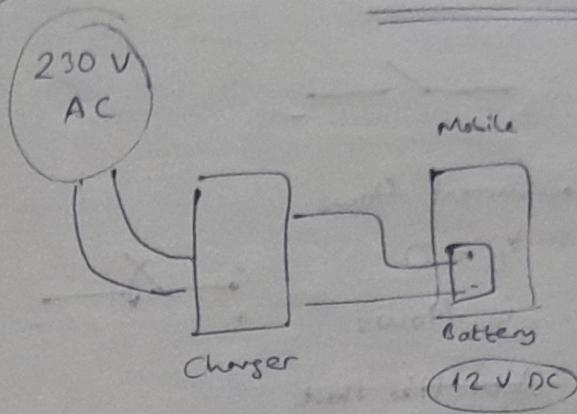

Charger :

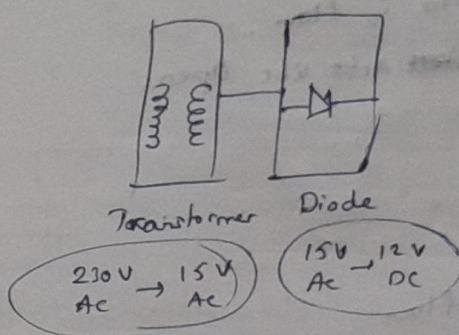

Rectifier :

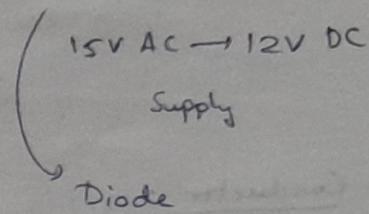

→ Semiconductor Diode :


Basic Building block of electronic circuits.

Diode \rightarrow \underbrace{PI}_{2} + $\underbrace{ODE}_{\text{electrode}}$

\therefore Diode : 2 electrodes / 2 terminals

[Anode & Cathode]

Symbol :

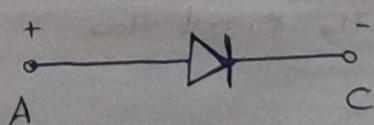

$i_1 \rightarrow$
 $i_1 \leftarrow \times$

Only unidirectional current flow


Diode : Unilateral Device

↳ Electronic Switch

Diode is On \rightarrow Current flows

$$V_D = 0$$

i_D flows

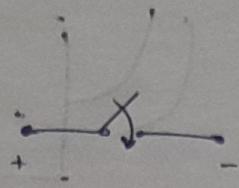

Acts like short

Diode is Off \rightarrow Current does not flow

$$V_D = \text{Supply Voltage}$$

No i_D flow.

~~Act~~ Acts like Open.

\rightarrow Conductor :

↳ Allows the current flow

Ex. Copper / Aluminium, etc

Insulator :

↳ Isolates the current flow, Reduces to minimum current flow
Ex. Polythene, PVC, ~~Parsalein~~, etc

Property holds till Threshold Temp

After Breakdown Temp., Material acts like conductor

Semiconductor :

Ex. GaAs, Ge, Si, etc

Properties lie b/w Conductor & Insulator.

Able to control the current flow.

\rightarrow Pure semiconductor :

- No. of e^- = no. of holes

- Can't Control Electric Current \therefore Not Useful

- $e^- \rightarrow$ -ve charge carriers
- holes \rightarrow +ve charge carriers [holes are absence of e^-]
- Intrinsic Semiconductor \leftrightarrow Pure Semiconductors

→ Extrinsic Semiconductors :

↳ Add some Impurity, so that electrical current flow can be controlled.

Process : Doping

∴ Electrical characteristics are Improved.

Doped Semiconductor materials

n-type

Majority carriers : e^-

p-type

Majority carriers : holes

Gap b/w Valency Band and Conduction band - Band gap (eV)

Doped Semiconductors have greater conductivity than pure conductors.

Band Gap for Germanium Semiconductor : 0.7 eV

Band Gap for Silicon Semiconductor : 1.12 eV

GaAs \rightarrow LED, laser

Si, Ge \rightarrow Rectifiers

Si more preferable than Ge

\therefore Band gap is more.

\therefore Sustains high Temp, upto 200°C.



(Whereas Ge sustains upto 160°C only)

Si - Naturally Available in Earth (Sand) (i.e. cheap)

[SiO_2 (silica)]

\rightarrow p-n junction

~~reverse~~:

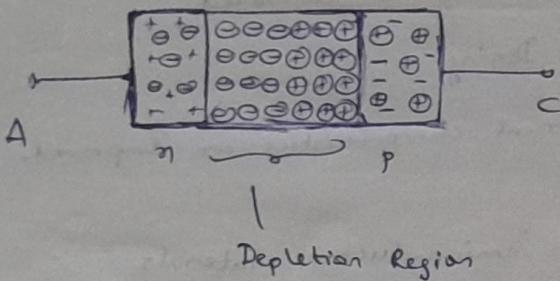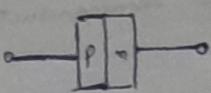

→ forms an electric potential across depletion region

↓
Barrier Potential

$$= 0.7 \text{ V for Si}$$

~~$= 0.12 \text{ V for Ge}$~~

$$= 0.3 \text{ V for Ge}$$

$$= 1.2 \text{ V for GaAs}$$

Characteristics: ~~without any bias~~

(i) No bias: No ext ~~Voltage~~ Voltage

$$(V_{AC} = 0)$$

(ii) Forward Biasing:

With Voltage $V_{AC} < 0.7$: (for Si)

$\therefore i_d = 0$, no current flow

$i_d \approx 0$ \because Minority Carriers ($i_d > 0$)

With Voltage $V_{AC} > 0.7$ (for Si)

\therefore Current flows

Diode starts Conducting

$$(i_d \propto V_{AC})$$

Anode : Connected with +ve of supply


Cathode : Connected with -ve of supply.

(iii) Reverse Biasing :

Anode : Connected with -ve of supply

Cathode : Connected with +ve of supply

Diode is said to be off state.

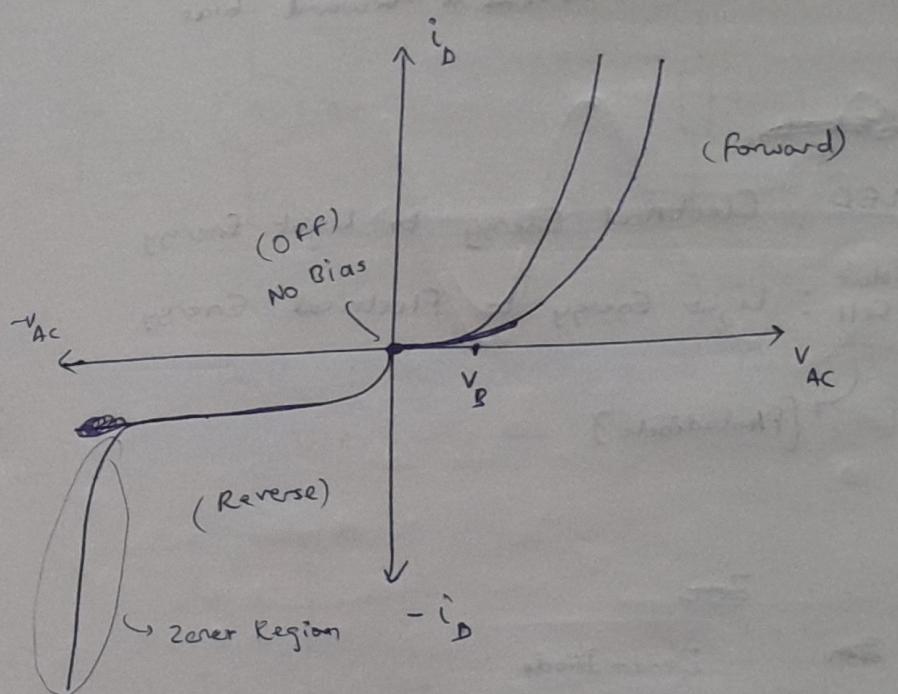

for Both Operating characteristics,

Junction Temp. should be within Threshold value


If it exceeds, Breakdown Voltage
(Diode damages)

In order to safely operate the diode,
We use heat sink.

→ Zener Region :

Zener Voltage : Voltage Remains const. during Reverse Bias

Zener Diode → Voltage Regulator

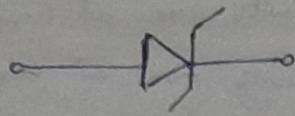

During Reverse Bias, Diode can be easily damaged
 ∵ Temp. Rise

But Zener Diode won't get damaged.
 (Red Colour)

p-n junction diode : Rectifier
 (Black colour) → Works in forward bias

~~LED~~

LED : Electrical Energy to Light Energy

Solar Cell : Light Energy to Electrical Energy

↳ [Photodiode]


~~Zener~~

~~Z.~~ Zener Diode :



↳ Indicates Cathode
 (Curve)

→ Schottky Diode :

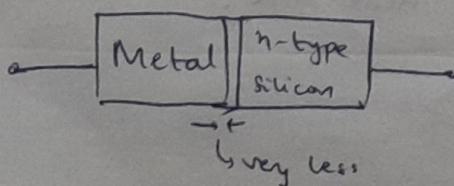

Use : High Switching speed applications

→ Application of Diodes :


~~Generally~~ Used as Rectifiers

to convert Sinoidal voltages into Unidirectional (DC)


(AC),

Voltages.


(i) Half-Wave Rectifiers

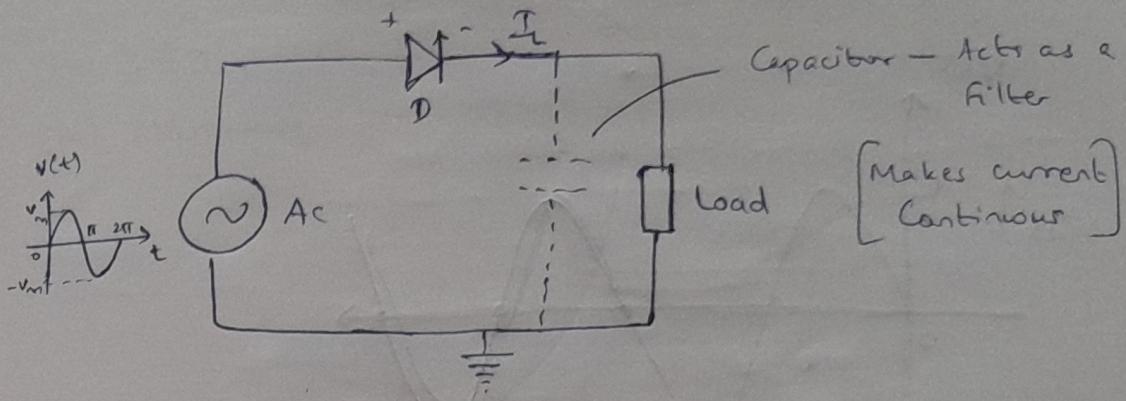

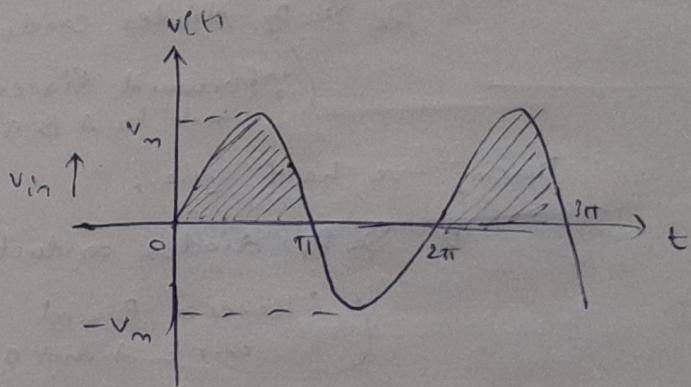Half of the AC cycle is rectified &
Uses only one Diode



forward Bias → + is connected to +ve


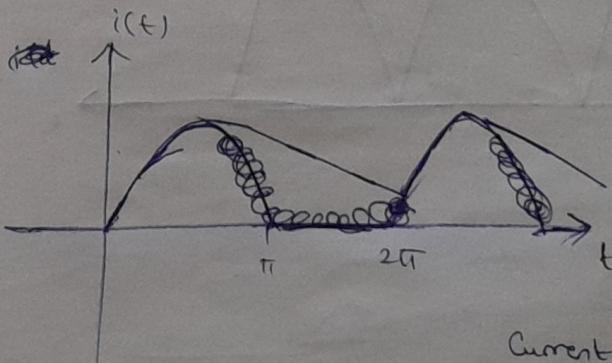


(Without filter)

Current flow is not continuous

∴ To make continuous, Capacitor is added.

→ Full Wave:

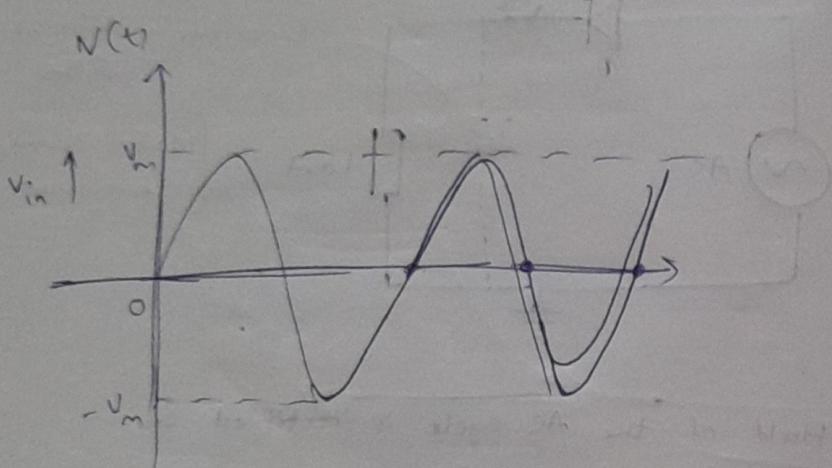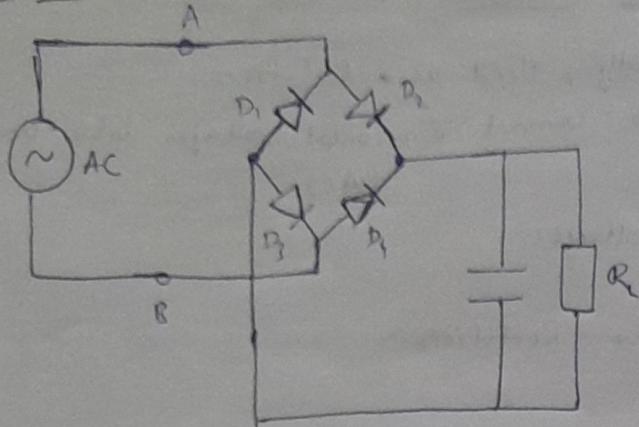


During the half cycle,

D_2 & D_3 diodes conduct
(∴ Forward Biased)
w.r.t to A & B

During -ve half cycle ,

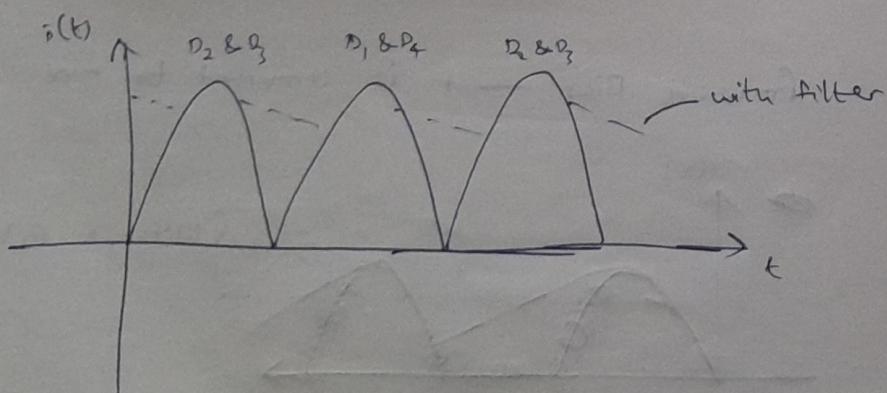D_1 & D_4 diodes conduct
(∴ Reverse Biased
w.r.t A and B)



→ Applications of Diodes

- (i) Rectifier Circuits,
- (ii) Power Supplies ,
- (iii) Wave shaping Circuits
(Clippers & Clampers)
- (iv) Time Delay Circuits
(Running light)
- (v) LEDs
- (vi) Microwave communications

6/11/23

Operational Amplifiers

CHAPTER - 5

(Op-Amp)

Very High Gain Amplifier
(10^4 to 10^6)

$$\rightarrow \text{Gain} = \frac{\text{Output voltage}}{\text{Input voltage}}$$


→ Single Output, ~~Double~~ ~~Except~~ Two Terminal Input Device

→ Input Impedance $\uparrow\uparrow$

Output Impedance $\downarrow\downarrow$

→ Assume Op-Amp to be black box

→

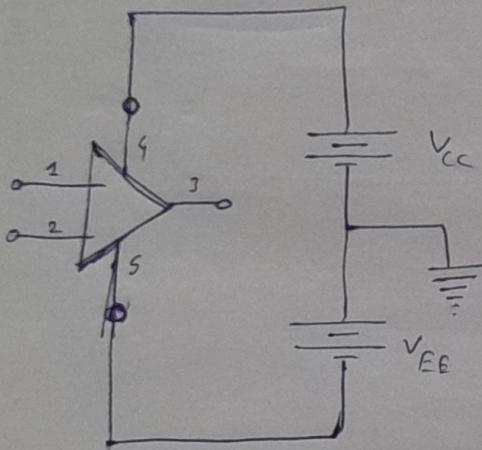

Terminal 1 : Inverting Input

Terminal 2 : Non-Inverting Input

Terminal 3 : Output

Terminal 4 : Positive supply V_{cc}

Terminal 5 : Negative supply V_{ee}

→ Ideal Gain:

$$V_3 = A(V_2 - V_1)$$

Ideal Input Impedance $= \infty$

Ideal Output Impedance $= 0$

Differential Gain (A) $= \infty$

Bandwidth Gain is const. from DC to high frequency

Amplifier with ∞ gain — No Use &
— Practically Impossible

V_o : Output Voltage (V)

A: Gain

V_2 : Non-Inverting Input (V)

V_1 : Inverting Input (V)


Ideal Op-Amp \rightarrow zero common-mode gain ($A_{cm} = 0$)

→ Complete common-mode rejection
→ Infinite Bandwidth

→ Types of Op-Amp :

- Inverting Op-Amp
- Non-Inverting Op-Amp

(①) Inverting Amplifier :

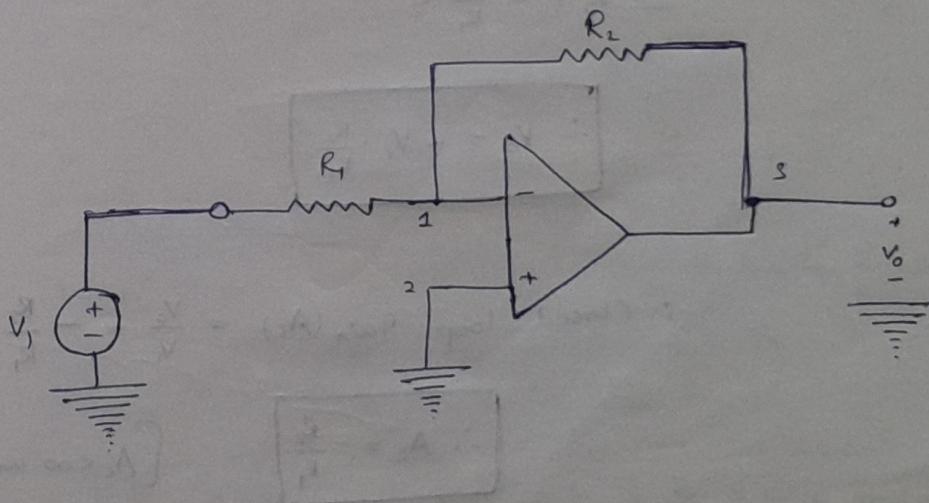

Source is applied to Inverting (terminal) input.
Non-Inverting (terminal) input is grounded.

In order to limit the gain, Resistance R_2 is connected b/w Non-Inverting terminal & Output Terminal. R_2 : Negative feedback &

~~negative feedback~~

~~negative feedback~~

R_2 AKA Feedback Resistance.

→ Relationship b/w V_o and V_i :

$$+V_1 - I(R_1 + R_2) = V_o$$

$$\Rightarrow A_1 = \frac{V_1 - V_o}{R_1 + R_2}$$

Current flowing through inverting Terminal from source = I_1

If Ideal Op-Amp, infinite Input Impedance




No current to non-inverting terminal

$$V_i = I_1 R_1$$

$$\Rightarrow A_1 = \frac{V_i}{R_1}$$

$$V_o = I_2 R_2$$

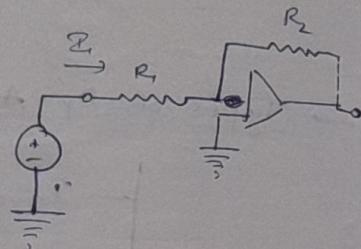

But Negative Feedback

$$\Rightarrow V_o = -I_1 R_2$$

$$\therefore V_o = -\frac{V_i}{R_1} R_2$$

$$\boxed{\therefore V_o = -V_i \cdot \frac{R_2}{R_1}}$$

$$\therefore \text{Closed loop gain } (A_C) = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$\boxed{\therefore A_C = -\frac{R_2}{R_1}}$$

$[A_C < \infty \text{ and is finite}]$

Voltage @ Inverting Terminal = 0

(Virtual Ground) $\therefore V_b = 0 \therefore V_a = 0$

$$I_1 = \frac{V_i - V_{\text{virtual}}}{R_1} = \frac{V_i - 0}{R_1} = \frac{V_i}{R_1}$$

$$I_2 = \cancel{V_{\text{virtual}}} \frac{V_{\text{virtual}} - V_o}{R_2} = \frac{0 - V_o}{R_2} = -\frac{V_o}{R_2}$$

$$\& I_2 = I_1$$

Negative sign indicates Inverting the signal

i.e. 180° phase diff. b/w Input & Output Voltages

Ex. Input : Sine wave


Output : Cos wave

→ Application of Inverted Configuration:

(Weighted summer).

Output Voltage = Weighted sum of all Input
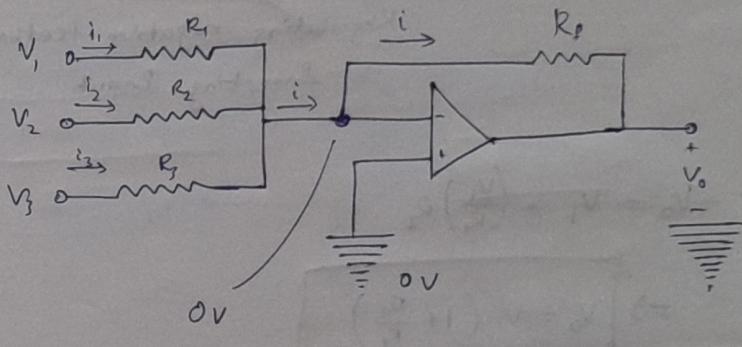
$$\text{i.e. } V_o = V_1 + V_2 + V_3 + \dots$$



$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

↪ Weighted sum of Inputs


Hence :

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \dots + \frac{R_f}{R_n} V_n \right)$$

$[R_f$: Resistance b/w Inverted Input & Output Terminal]

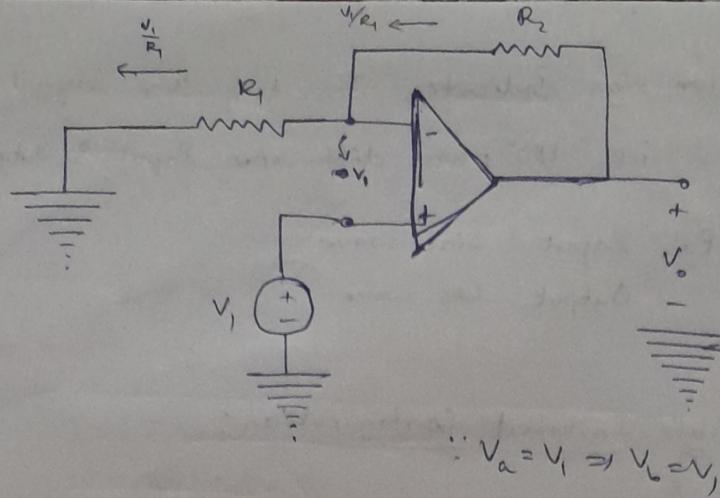(2) Non-Inverting Op-Amp :

Polarity / Phase of Output is same as Input.



$$\therefore V_a = V_1 \Rightarrow V_b = V_1$$

Source is Applied to Non-Inverting Terminal
Inverted (Terminal) Input is grounded through R_2

R_1 & R_2 forms Voltage Divider Circuit.

Act as a Voltage Divider,

Regulating negative feedback to the
Inverting Input

$$V_o = V_1 + \left(\frac{V_1}{R_1}\right) R_2$$

$$\Rightarrow V_o = V_1 \left(1 + \frac{R_2}{R_1}\right)$$

As Negative Feedback, $\beta_1 = -\frac{V_f}{R_1}$



$$\beta_1 = \frac{V_f}{R_1}$$


~~Closed Loop Gain~~ Closed Loop Gain (A_c) = $\frac{V_o}{V_1}$

$$= 1 + \frac{R_2}{R_1}$$

$$\therefore A_c = 1 + \frac{R_2}{R_1}$$

$A_c < \infty$ & is finite

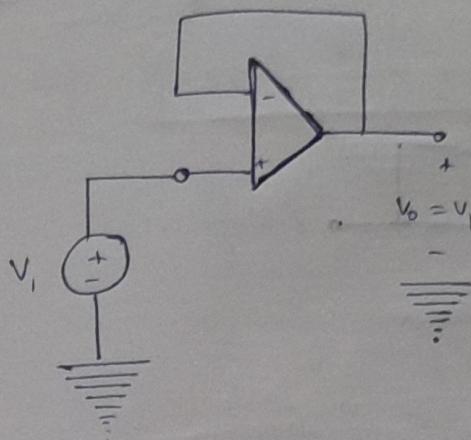
→ Application of Non-Inverting Op-Amp:
(Buffer / Voltage Follower)



Unity Gain - Buffer
~~OR~~

Follower Amplifier

Equivalent Circuit:

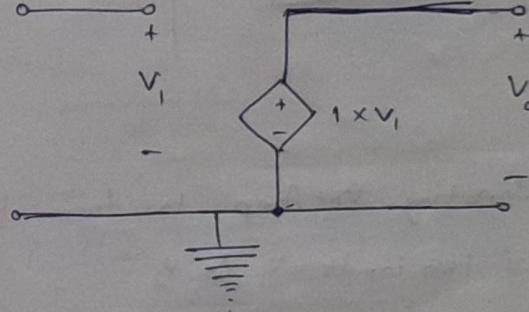

$$\text{Gain} = 1$$

$$\text{Input Voltage} = \text{Output Voltage}$$

This Op-Amp is used after Amplification of another circuit.

It acts as a Buffer ∵ Output Voltage always follows
Input Voltage

Buffer Amplification [Transformer : Electrical Buffer Amplifier]

Buffer → Impedance Matching Device

[In order to extract Max possible Power by
Load Resistance = Source Resistance]

(g) Use circuit below to design an Inverted Amplifier.


$$\text{Gain} = -10$$

$$\text{Input } R = 100 \text{ k}\Omega$$

$$\begin{cases} R_1 = 100 \text{ k}\Omega \\ R_2 = 1 \text{ M}\Omega \end{cases}$$

Find R_1 & R_2

Sol:

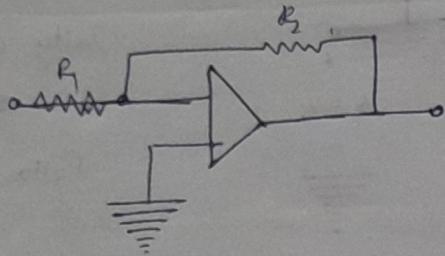

$$A_c = \text{Gain} = -\frac{R_2}{R_1}$$

$$\Rightarrow 10 = \frac{R_2}{R_1}$$

$$\boxed{R_2 = 10R_1}$$

$$R_1 = 100 \text{ k}\Omega$$

$$\Rightarrow R_2 = 10 \times 100 \text{ k}\Omega \\ = 1000 \text{ k}\Omega$$

$$\boxed{\therefore R_2 = 1 \text{ M}\Omega}$$

Feedback
Resistance

(g) Design an Inverting Op-Amp to form Weighted-sum V_o of two inputs V_1 & V_2


$$V_o = -(V_1 + 5V_2)$$

$$\text{Max Output Voltage} = 10 \text{ V}$$

$$\text{Max Current in Feedback Resistor} = 1 \text{ mA}$$

Design R_1 , R_2 & R_f

Sol:

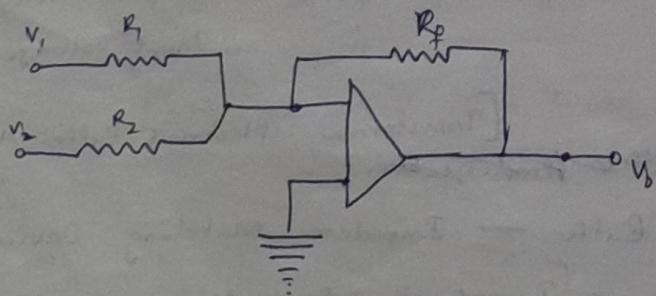

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2\right)$$

$$V_o = -(V_1 + S V_2)$$

$$\Rightarrow V_1 + S V_2 = \left(\frac{R_f}{R_1}\right) V_1 + \left(\frac{R_f}{R_2}\right) V_2$$

$$\therefore \frac{R_f}{R_1} = 1 \Rightarrow R_f = R_1$$

$$\frac{R_f}{R_2} = S \Rightarrow R_f = S R_2$$

$$\Rightarrow R_1 = S R_2$$

$$\frac{10}{R_f} \leq 1 \text{ mA} \Rightarrow R_f \geq 10 \text{ k}\Omega$$


Assume $R_f = 10 \text{ k}\Omega$

$$\therefore R_1 = 10 \text{ k}\Omega$$

$$\therefore R_2 = 2 \text{ k}\Omega \quad \left[\because \frac{10}{S} = 2 \right]$$

$$\therefore (R_f, R_1, R_2) = (10, 10, 2) \text{ k}\Omega$$


H.W
Q1)

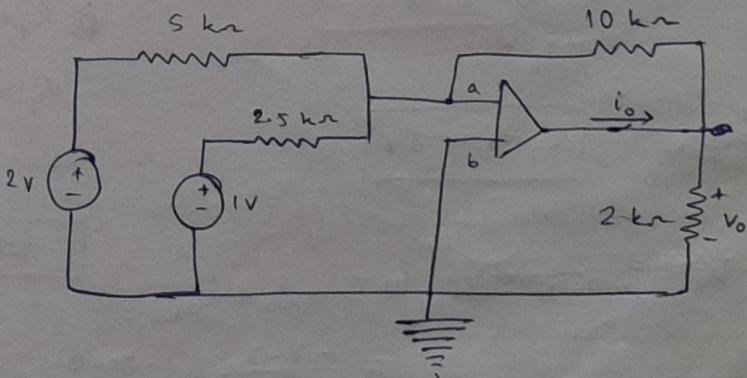

End-Sem:
(Pattern)
10 φ
↓
1φ - 5m


Find i_o & V_o

K.W.
Q2)

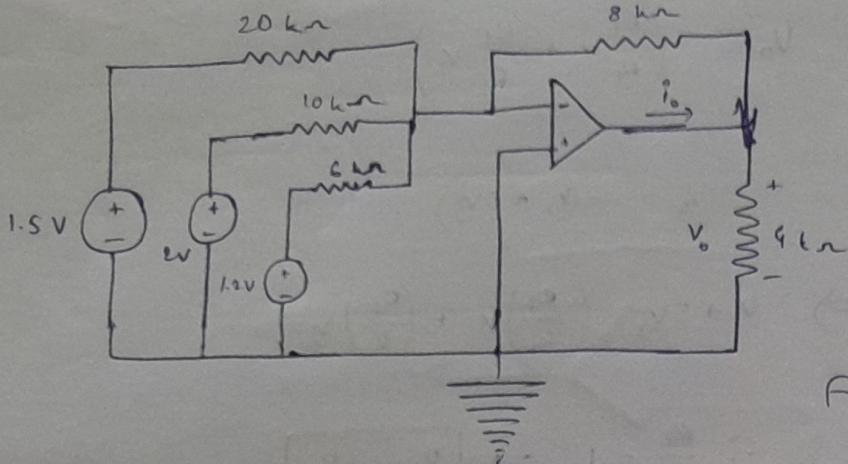

Find i_o & V_o

Sol
(Q2)

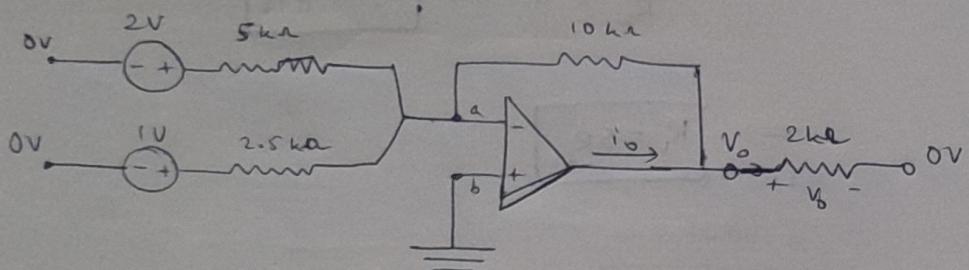

$$V_b = 0 \because \text{Grounded}$$

$$V_1 = 2V$$

$$V_2 = 1V$$

~~V_o = 20~~ as for Practical
Terminal

$V_a = 20$ \because Terminal is
Virtual Ground

~~X X X X X X V₂~~

$$V_o = -\left[\frac{(R_f)}{R_1}V_1 + \frac{(R_f)}{R_2}V_2\right]$$

$$\Rightarrow V_o = -\left[\left(\frac{10 \times 10^3}{5 \times 10^3}\right)(2) + \left(\frac{10 \times 10^3}{2.5 \times 10^3}\right)(1)\right]$$

$$= -(4 + 4)$$

$$= -8V$$

$$R_{eq} = \frac{5 \times 5k}{15k}$$

$$\therefore R_{eq} = 5k$$

$$Gain = -\frac{R_f}{R_{eq}} = -\frac{10}{5k}$$

$$\therefore Gain = -6$$

~~-~~ $\therefore V_o = -8V$


$$i_o = i_{10k\Omega} + i_{2k\Omega}$$

$$= \frac{-8-0}{10k\Omega} + \frac{-8-0}{4k\Omega}$$

$$= -0.8mA - 0.4mA$$

$$\therefore i_o = -4.8mA$$

Q2)

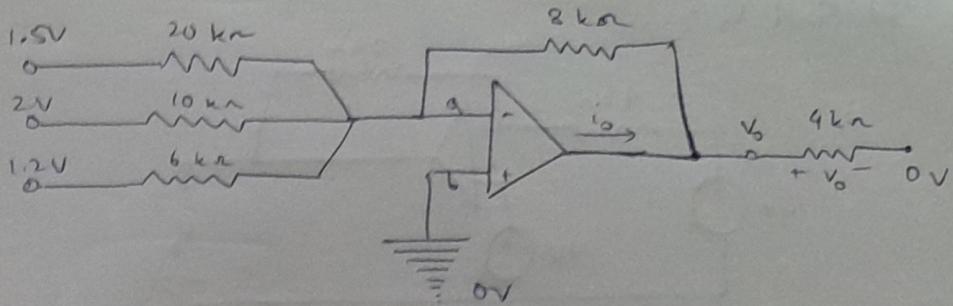

$V_0 = 0$ " Grounded

$V_a = 0$ " Positive
Impedance
to Inverting
Terminal

$$V_1 = 1.5 \text{ V} \quad \& \quad R_1 = 20 \text{ k}\Omega$$

$$V_2 = 2 \text{ V} \quad \& \quad R_2 = 10 \text{ k}\Omega$$

$$V_3 = 1.2 \text{ V} \quad \& \quad R_3 = 6 \text{ k}\Omega$$

$$V_o = - \left[\left(\frac{R_f}{R_1} \right) V_1 + \left(\frac{R_f}{R_2} \right) V_2 + \left(\frac{R_f}{R_3} \right) V_3 \right]$$

$$\Rightarrow V_o = - \left[\frac{8}{20} \left(\frac{3}{2} \right) + \frac{8}{10} (2) + \frac{8}{6} \left(\frac{6}{5} \right) \right]$$

$$= - \left[\frac{1}{5} + \frac{8}{5} + \frac{8}{5} \right] \quad (\text{OR})$$

$$= - \frac{19}{5} \text{ V}$$

$$\frac{1}{R_{eq}} = \frac{2}{3} + \frac{1}{2} + \frac{5}{6}$$

$$= \frac{4+3+5}{6}$$

$$i_o = i_{8 \text{ k}\Omega} + i_{4 \text{ k}\Omega}$$

$$R_{eq} = \frac{6}{12} = \frac{1}{2} \text{ k}\Omega$$

$$\Rightarrow \frac{V_o - 0}{8 \text{ k}\Omega} + \frac{V_o - 0}{4 \text{ k}\Omega}$$

$$V_{eq} = R_{eq} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$= \frac{1}{2} \left(\frac{3}{40} + \frac{2}{10} + \frac{1}{5} \right)$$

$$= \frac{19}{80} \text{ V}$$

$$= -3.8 \left(\frac{1}{8} + \frac{1}{4} \right) \text{ mA}$$

$$= -\frac{19}{5} \times \frac{3}{8} \text{ mA}$$

$$= -\frac{57}{40} \text{ mA}$$

$$\therefore i_o = -1.425 \text{ mA}$$

$$R_{eq} = \frac{1}{2} \text{ k}\Omega$$

$$V_{eq} = \frac{19}{80} \text{ V}$$


$$V_o = -\frac{8}{(1/2)} \times \frac{19}{80}$$

$$V_o = -\frac{19}{5} \text{ V}$$


$$\text{Gain} = -\frac{R_f}{R_{eq} \infty} = -\frac{8}{1/2}$$

$$\therefore \text{Gain} = -16$$

Q) Find V_o :

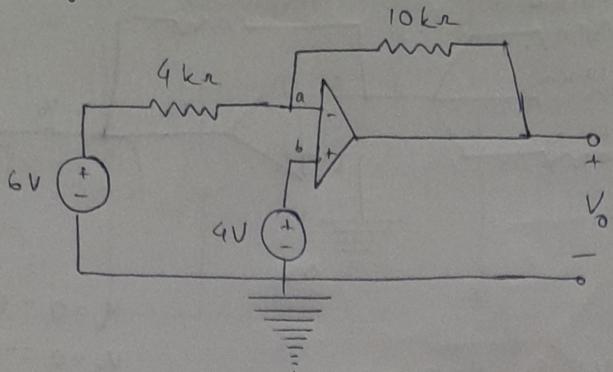

Sol:

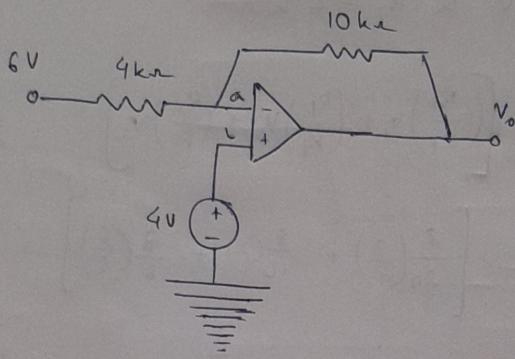

$$V_{o_2} = V_2 \left(1 + \frac{R_f}{R_1}\right)$$

$$\Rightarrow V_{o_2} = 4 \left(1 + \frac{10}{4}\right)$$

$$= 14 \text{ V}$$

$$\therefore V_{o_2} = 14 \text{ V}$$

$$A_{C_2} = \frac{V_o}{V_2} = \frac{14}{4} = \frac{7}{2}$$

$$V_o = (14 - 15) \text{ V}$$

$$\therefore V_o = -1 \text{ V}$$

$$V_{o_1} = -V_1 \left(\frac{R_f}{R_1}\right)$$

$$= -6 \times \frac{10}{4}$$

$$= -15 \text{ V}$$

$$\therefore V_{o_1} = -15 \text{ V}$$

$$A_{C_1} = \frac{V_o}{V_1} = \frac{-15}{6} = -\frac{5}{2}$$

$$V_a = V_b$$

Whatever $V_b =$, same V_a is.

$$V_a = V_b = 4$$

$$\text{Gain}_2 = A_{C_2} = 1 + \frac{R_2}{R_1}$$

$$A_{C_2} = 1 + \frac{10}{4} = \frac{7}{2}$$

$$\boxed{A_{C_2} = \frac{7}{2}}$$

$$\text{Gain}_1 = A_{C_1} = -\frac{R_f}{R_1}$$

$$\boxed{A_{C_1} = -\frac{5}{2}}$$

$$\boxed{\therefore A_C = 1}$$