

Q1

Basic diff betw network & ckt.

ckt - loop or mesh - closed path

interconnections of ckt is nw.

Building - Network
 rooms - ckt

→ Basics : Passive, lumped R, L, C & Ohm's Law.

→ In presence of active sources (V & I), → Passive, lumped (R, L, C) will always absorb energy → current flows from +ve to -ve terminals.

→ In the absence of V & I → the stored energy in L & C will be delivered to the memoryless Resistor → current flows from -ve to +ve terminals.

Q112 Ohm's Law basic

electromagnetic theory : $\vec{J} = \sigma \vec{E}$ ^{conductivity}
 \downarrow ^{current density}

$$\vec{E} = \frac{\vec{V}}{l}$$

l = length of the conductor




$$\vec{J} = \frac{i}{S} \quad (A/m^2)$$

$$J = \sigma E \Rightarrow \frac{i}{S} = \sigma \frac{V}{l} \Rightarrow V = \left(\frac{l}{\sigma S} \right) \cdot i \Rightarrow V = R \cdot i$$

$$R = \left(\frac{l}{\sigma S} \right) = 0.6m = 0.6 \Omega$$

→ Limitation : linear V & I relation

'R' constant i.e. temp. const.

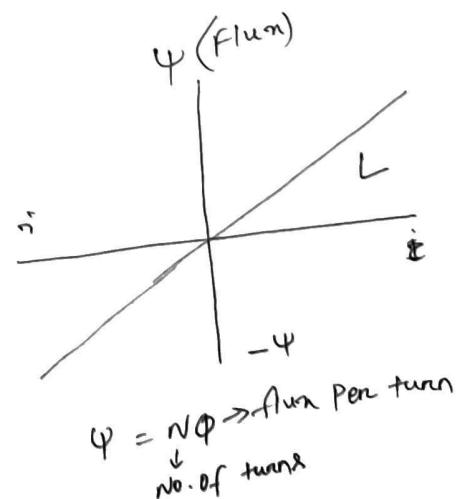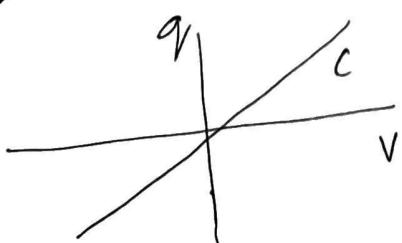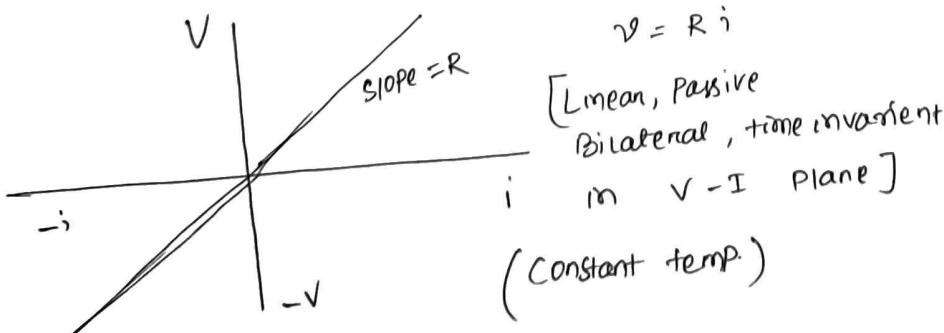T↑ ⇒ l↑, S↑, $\frac{l}{S} \approx$ almost const., σ↓, so RTAll unit of σ & $\Omega (S^{-1} m)$ 

$$V = L \frac{di}{dt}$$




$$E = \frac{1}{2} L i^2 \quad (\text{J})$$

$$i = C \frac{dv}{dt}$$

$$E = \frac{1}{2} C v^2 \quad (\text{J})$$

Inductor will store the energy in magnetic field in the form of current and the capacitor will store the energy in electric field in the form of voltage.

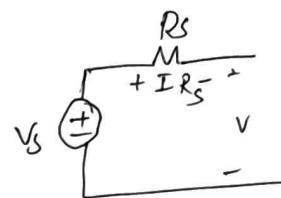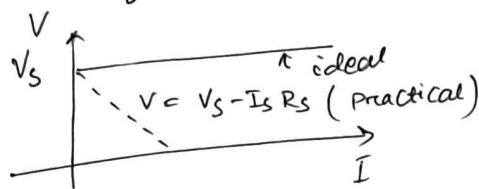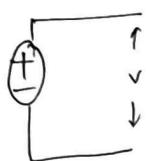\oplus/\ominus what is an ideal voltage source & practical






Load voltage is independent of load current

[Load voltage is a func of load current]

All sources : Active, unilateral.

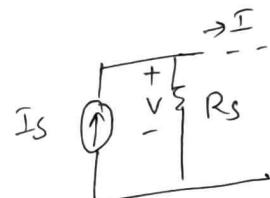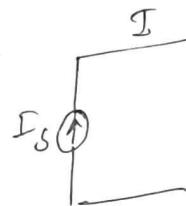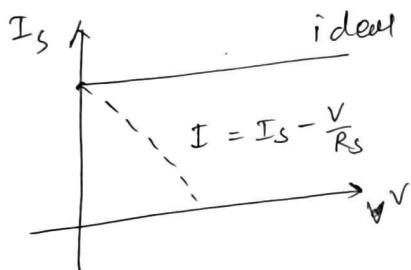
\oplus/\ominus ideal current source & practical



\rightarrow KCL + Ohm's law = Nodal

KVL + Ohm's law = mesh.


$\Rightarrow \oplus/\ominus$

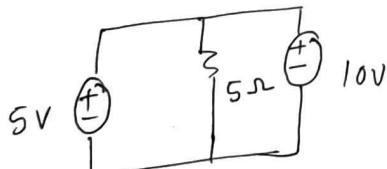



(X)

current through 5Ω resistor.

\oplus/\ominus

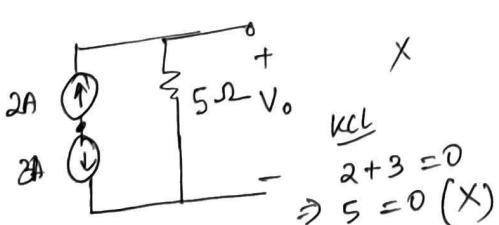

\oplus/\ominus

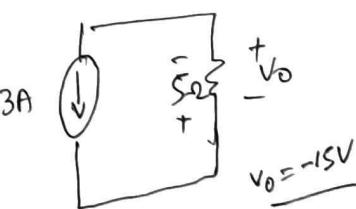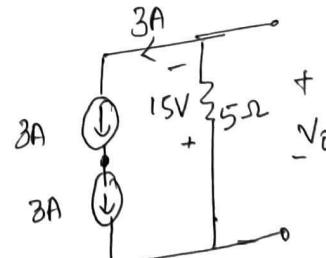

\rightarrow Superposition is not applicable if violation of KCL

(2)


Total 8 forms of ohm's law:

$$\textcircled{1} \quad \vec{J} = \sigma \vec{E} ; \quad \textcircled{3} \quad I = GV \text{ conductance}$$


$$\textcircled{2} \quad V = RI ; \quad R = \frac{V}{I} \quad \textcircled{4} \quad V = R \frac{dQ}{dt}$$

$$\textcircled{5} \quad V = L \frac{di}{dt} \quad \textcircled{6} \quad i = \frac{1}{L} \int_{-\infty}^t V dt$$
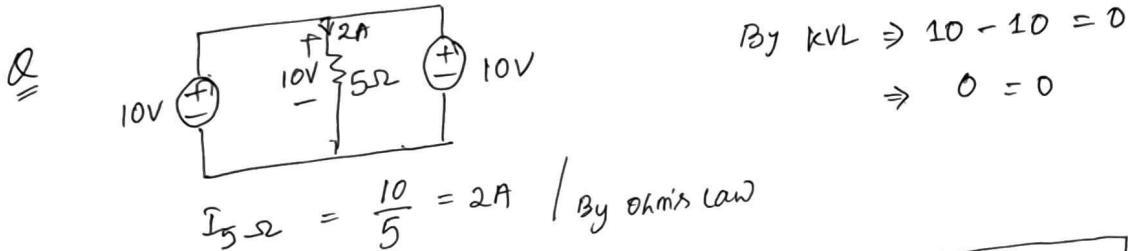
$$\textcircled{7} \quad i = C \frac{dv}{dt} \quad \textcircled{8} \quad v = \frac{1}{C} \int_{-\infty}^t i dt$$




Superposition :


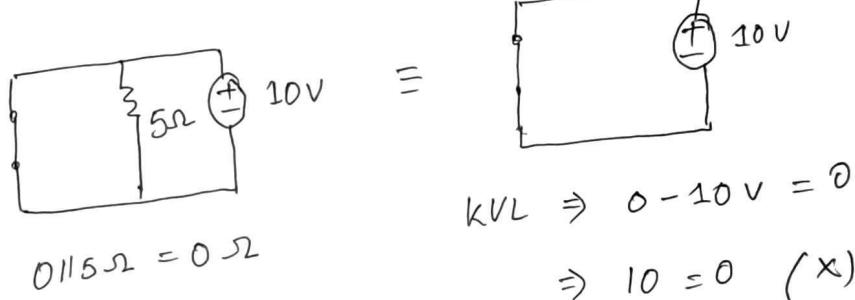


Violation KVL

Note: Ohm's law is applicable to any ckt i.e. may be lumped or distributed.
 but K' law is only for lumped n/w.

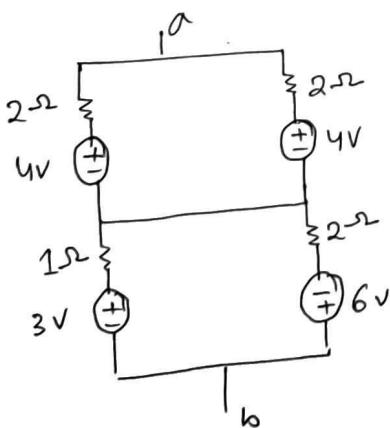 $\rightarrow \textcircled{1}$ 


Simplify the n/w betw 'a' & 'b'

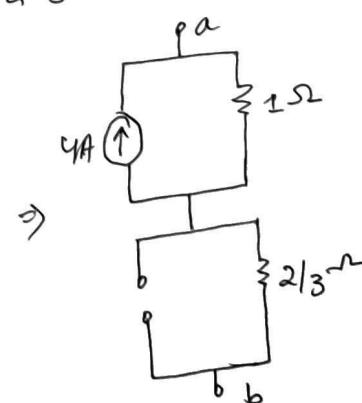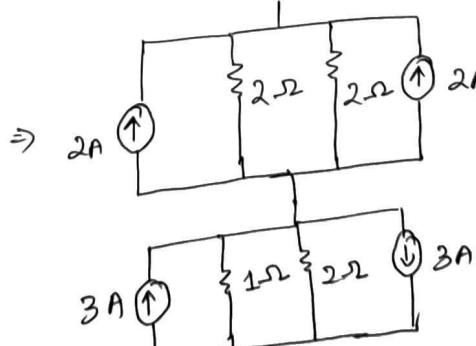

$$L = \frac{\mu_0 N^2 A}{c}$$



(2)

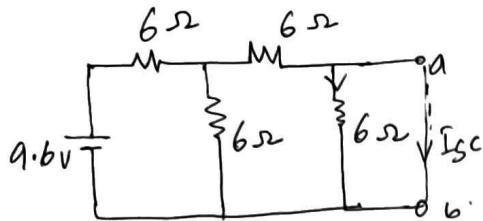


Determine the current through the ideal ammeter connected across a & b

Note :




* For an ideal ammeter $R_i = 0$

(A Practical Ammeter)

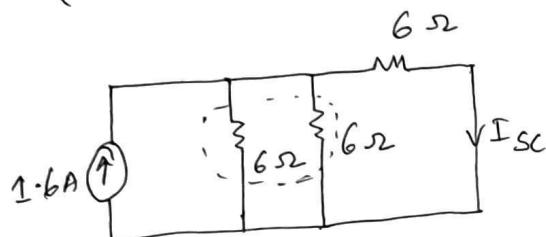


$$I_{sc} = \frac{1.6 \times 3}{6+3} = \frac{1.6}{3} A$$

(3)


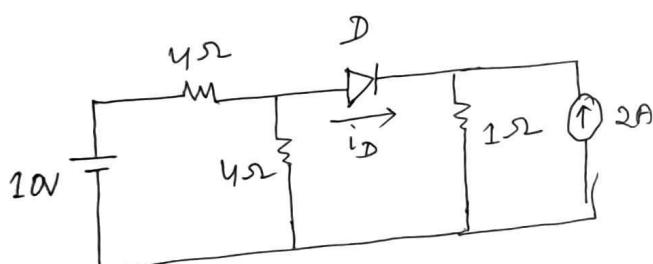


The current through the ideal diode 'D' is ?

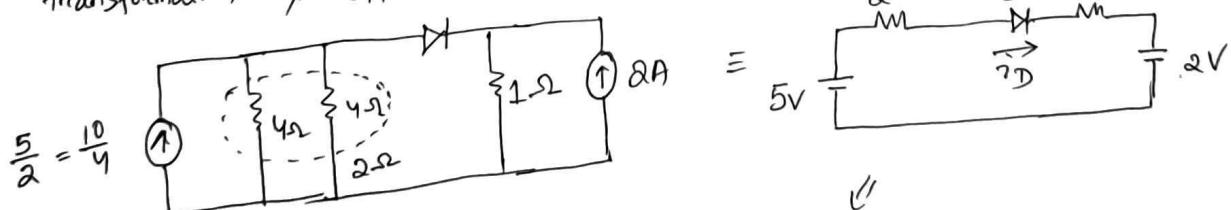Note : Since the diode is a non-linear element, the law is non-linear and hence superposition theorem is not applicable, so here the source transformation is applicable.



rotate and rearrange :

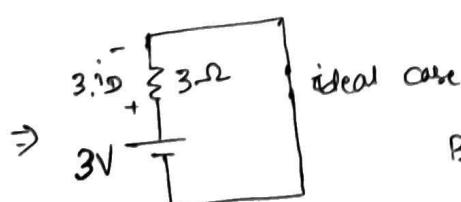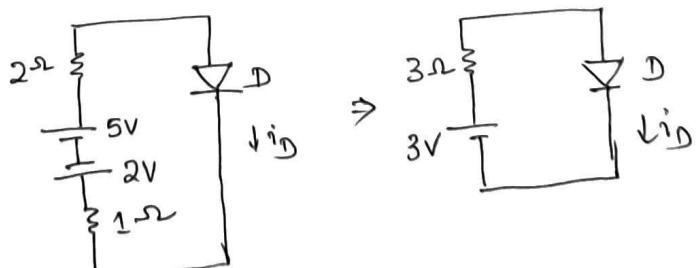

$$\begin{aligned} \text{By KVL} \Rightarrow 3 - 3 \cdot i_D &= 0 \\ \Rightarrow i_D &= 1 A \end{aligned}$$

(3)

Tellegen's Theorem

Defn : In an arbitrary n/w, the algebraic sum of powers at any given instant is zero.

i.e. Power delivered by some elements is equal to the power absorbed by remaining elements present in the n/w.

→ When the current enters at the -ve terminal of an element then that element will deliver the power, otherwise it will absorb the power.

→ The sources can deliver the power or it can absorb the power, whereas the passive elements will always absorb the power, since the currents will enter at the +ve terminal in the respective R, L, C.

Properties -

→ This theorem depends on the voltage and current product in an element.



→ This theorem depends on the voltage and current product in an element (linear, non-linear, active, but not on the type of the element (linear, non-linear, active, passive, etc.) i.e. independent of the nature of the element like KCL & KVL)

→ The theorem expresses conservation of power (energy) in every lumped electric Ckt.

$$\left\{ \begin{array}{l} \text{KVL = conservation of energy} \\ \text{KCL = conservation of charge.} \end{array} \right.$$

Note: While verifying the Tellegen's theorem, do not disturb the original n/w given for evaluating the voltages & currents in each and every element of the n/w.

Q/H verify

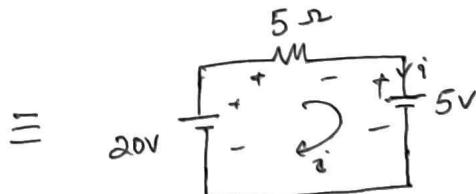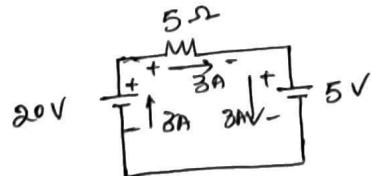

$$P_{20V} = 20 \times 3 = 60W \text{ (del)}$$

$$P_{15V} = 15 \times 3 = 45W \text{ (abs)} = P_{5\Omega}$$

$$P_{5V} = 5 \times 3 = 15W \text{ (abs)}$$


By KVL

$$\Rightarrow 20 - 5i - 5 = 0$$

$$\Rightarrow i = \frac{20-5}{5} = 3A$$

So, $P_{del} = 60W = P_{abs}$ i.e. conservation of power.

Q1

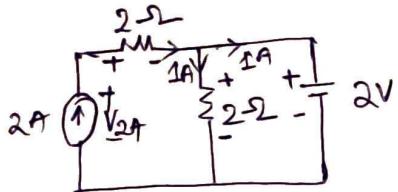

By KVL

$$V_{2A} - 4 - 2 = 0$$

$$\Rightarrow V_{2A} = 6V$$


$$P_{2A} = 2 \times 6 = 12 \text{ (del)}$$

$$P_{2\Omega} = 2 \times 4 = 8W \text{ (abs)}$$

$$P_{2\Omega} = 2 \times 1 = 2W \text{ (abs)}$$

$$P_{2V} = 2 \times 1 = 2W \text{ (abs)}$$

Q2

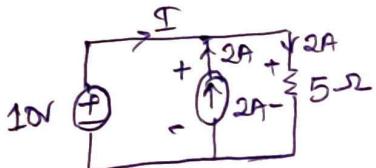By KCL $\Rightarrow -I - 2 + 2 = 0$


$$\Rightarrow I = 0$$

$$P_{10V} = 10 \times 0 = 0W$$

$$P_{2A} = 10 \times 2 = 20W \text{ (del)}$$

$$P_{5\Omega} = 10 \times 2 = 20W \text{ (abs)}$$

Q3

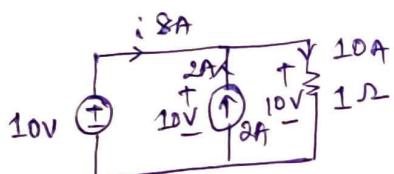By KCL $\Rightarrow -I - 2 + 10 = 0$


$$\Rightarrow I = 8A$$

$$P_{10V} = 10 \times 8 = 80W \text{ (del)}$$

$$P_{2A} = 10 \times 2 = 20W \text{ (del)}$$

$$P_{1\Omega} = 10 \times 10 = 100W \text{ (abs)}$$

Q4

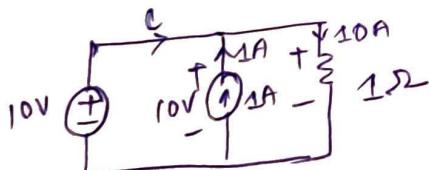By KCL $\Rightarrow -I - 1 + 10 = 0$


$$\Rightarrow I = 9$$

$$P_{10V} = 10 \times 9 = 90W \text{ (del)}$$

$$P_{2A} = 10 \times 1 = 10W \text{ (del)}$$

$$P_{1\Omega} = 10 \times 10 = 100W \text{ (abs)}$$

Q5

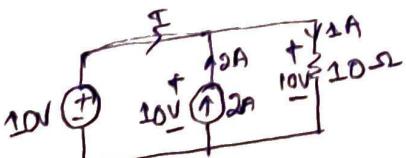By KCL $\Rightarrow -I - 2 + 1 = 0$

$$\Rightarrow I = -1$$

$$P_{10V} = 10 \times 1 = 10W \text{ (abs)}$$

$$P_{2A} = 10 \times 2 = 20W \text{ (del)}$$


$$P_{10\Omega} = 10 \times 1 = 10W \text{ (abs)}$$

From the above 4 problems, the current through an ideal voltage source can be any value i.e. unknown, it is decided by the other elements (magnitudes) present in the circuit.

(4)

Some more examples on Tellegen's thm:

Q41

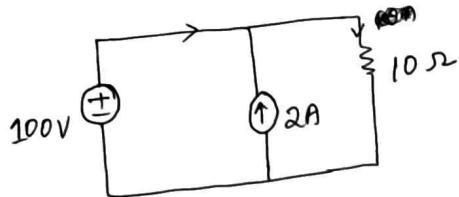


$$\begin{aligned} \text{KCL} \\ -I - 2A + 10A = 0 \\ \Rightarrow -I + 8 = 0 \Rightarrow I = 8A \end{aligned}$$

$$P_{100V} = 100 \times 8 = 800 \text{ W (del)}$$


$$P_{2A} = 100 \times 2 = 200 \text{ W (del)}$$

$$P_{10\Omega} = 100 \times 10 = 1000 \text{ W (abs)}$$

Q41

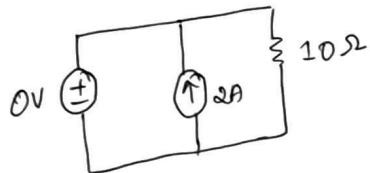

≡

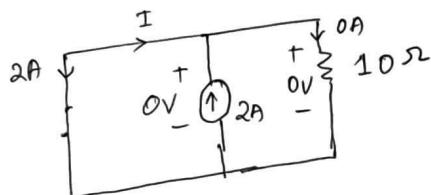

$$\text{By KCL} \Rightarrow -I - 2 + 0 = 0 \Rightarrow I = -2A$$


$$P_{2A} = 0 \times 2 = 0 \text{ W}$$

$$P_{10\Omega} = 0 \times 0 = 0 \text{ W}$$

$$P_{\text{del}} = P_{\text{abs}} = 0 \text{ W}$$

Note: Voltage across an ideal current source can be any value i.e. unknown, if it is decided by the other elements (magnitude) present in the n/w.

Q41

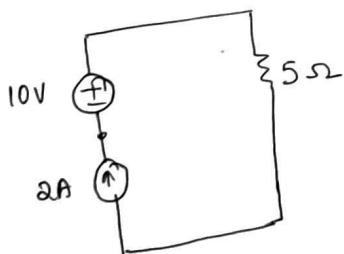


$$\begin{aligned} \text{By KVL} \Rightarrow V_{2A} + 10 - 10 &= 0 \\ V_{2A} &= 0 \text{ V} \end{aligned}$$

$$P_{2A} = 0 \times 2 = 0 \text{ W} ; P_{10V} = 10 \times 2 = 20 \text{ W (del)}$$





$$P_{5\Omega} = 10 \times 2 = 20 \text{ W (abs)}$$

Q41

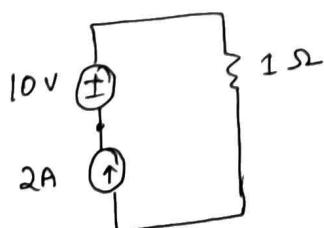

$$\begin{aligned} V_{2A} + 10 - 2 &= 0 \\ \Rightarrow V_{2A} &= -8 \text{ V} \\ P_{2A} &= 8 \times 2 = 16 \text{ W (abs)} \\ P_{10V} &= 10 \times 2 = 20 \text{ W (del)} \\ P_{1\Omega} &= 2 \times 2 = 4 \text{ W (abs)} \end{aligned}$$

→ The dependent or controlled sources

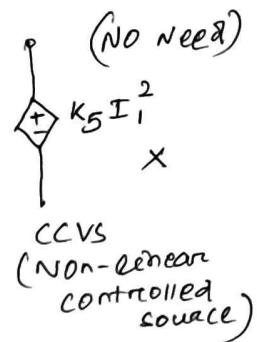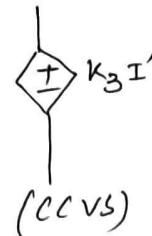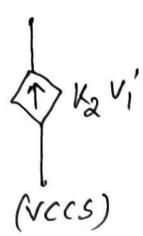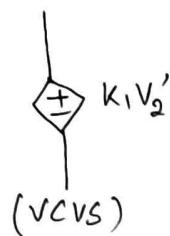



Linear controlled sources w.r.t the controlled variable, not w.r.t voltage and current relation.

→ Here $K_1, K_2 \dots K_5$ are constants and V_1, V_2, I_1, I_2 are the controlled variables.

- * w.r.t the controlled variable only the dependent sources said to be linear, active and bilateral. The presence of these elements make the network a linear, active and bilateral
- * The controlled sources are said to be the sources i.e. active elements only in the presence of at least one independent source, then only the controlled variable are non-zero and hence their magnitudes are non-zero.


Source Transformation

- It is a simplification technique, which eliminates the extra nodes present in the network and it is applicable to ~~not~~ only for the practical sources.
- It is impossible to convert an ideal voltage source into its equivalent current source and vice versa, since the violation of KCL & KVL
- The Source transformation is applicable to even for the dependent sources, provided the controlled variable is outside the branches, where the source transformation is applied.

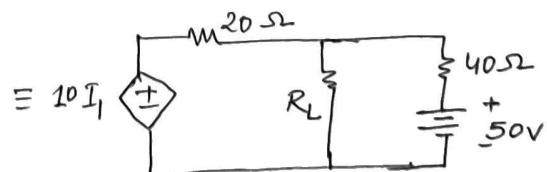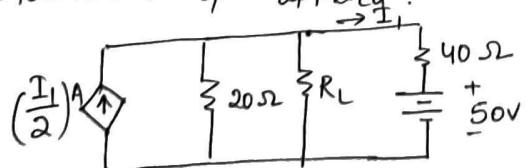

Both will give same Thevenin's and Norton's equivalent.

NODAL

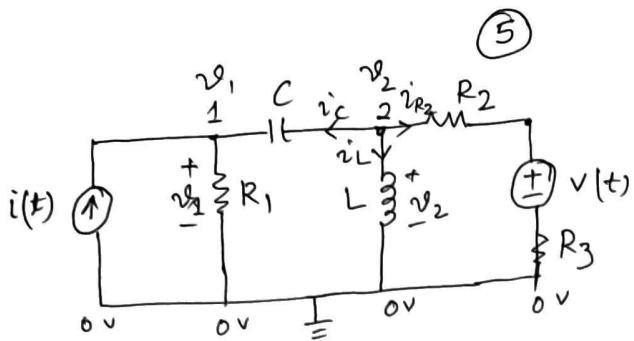

→ identify the number of nodes

→ Assign the node voltages with ref to the ground node
→ KCL + Ohm's law.

Node ②


$$v_2 > v_1$$

$$v_2 > 0$$

$$v_2 > v(t)$$


$$i_C + i_L + i_{R_2} = 0$$
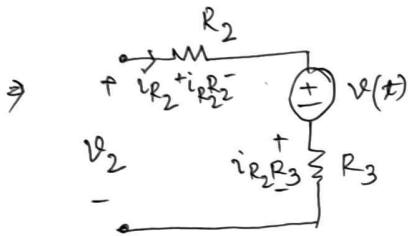
$$\Rightarrow C \frac{d}{dt} (v_2 - v_1) + \frac{1}{L} \int_{-\infty}^t v_2 dt + \frac{v_2 - v(t)}{R_2 + R_3} = 0$$



$$v_2 - i_{R_2} R_2 - v(t) - i_{R_2} R_3 = 0$$
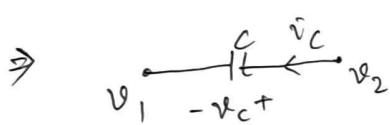
$$\Rightarrow i_{R_2} = \frac{v_2 - v(t)}{R_2 + R_3} \text{ A}$$



$$i_C = C \frac{dv_C}{dt} \quad \text{Ohm's Law}$$

$$v_1 + v_C - v_2 = 0 \Rightarrow v_C = v_2 - v_1$$


$$i_C = C \frac{d}{dt} (v_2 - v_1)$$

Node ①

$$v_1 > v_2$$

$$v_1 > 0$$
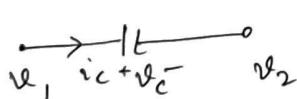
$$-i(t) + \frac{v_1}{R_1} + C \frac{d}{dt} (v_1 - v_2) = 0$$




$$i_C = C \frac{dv_C}{dt}$$

$$v_1 - v_C - v_2 = 0 \Rightarrow v_C = v_1 - v_2 \Rightarrow$$

$$i_C = C \frac{d}{dt} (v_1 - v_2)$$

MESH

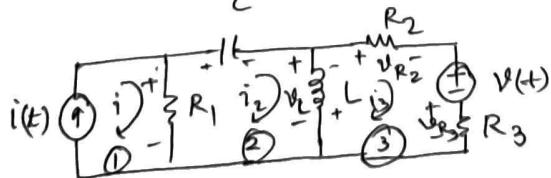

* Equivalent circuit

* Star-delta

(Y-Δ)

→ identify the no. of meshes


→ Assign the mesh currents in the clockwise direction

→ KVL + Ohm's law

Mesh ③

$$i_3 > i_2$$

$$i_3 > i_1$$

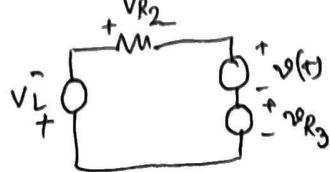


$$v_L = L \frac{d}{dt} (i_3 - i_2) , \quad v_{R_2} = R_2 \cdot i_3 , \quad v_{R_3} = R_3 \cdot i_3$$

$$-v_L - v_{R_2} - v(t) - v_{R_3} = 0$$

$$-L \frac{d}{dt} (i_3 - i_2) - R_2 i_3 - v(t) - R_3 \cdot i_3 = 0$$

Mesh ②
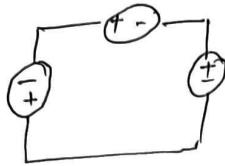
$$\begin{aligned} i_2 &> i_1 \\ i_2 &> i_3 \end{aligned}$$



$$v_{R_1} = R_1 (i_2 - i_1)$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i_2 dt$$


$$v_L = L \frac{d}{dt} (i_2 - i_3)$$

$$-v_{R_1} - v_C - v_L = 0$$

$$-R_1 (i_2 - i_1) - \frac{1}{C} \int_{-\infty}^t i_2 dt - L \frac{d}{dt} (i_2 - i_3) = 0$$

Mesh ③
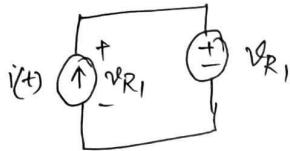
$$\begin{aligned} i_1 &> i_2 \\ i_1 &> i_3 \end{aligned}$$



$$v_{R_1} = R_1 (i_1 - i_2)$$


$$v_{R_1} - v_{R_1} = 0$$

$$i_1 = i(t)$$

The equivalent circuit :-

⑥ Another way Dependent Sources


①

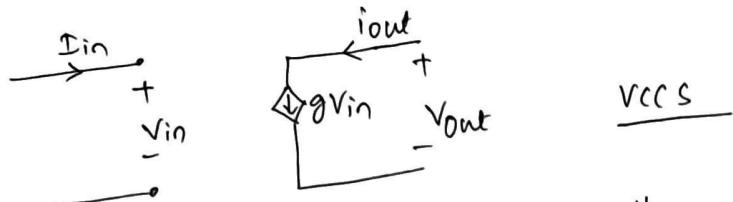

VCCS

"transconductance" unit "A/V"
if g is the gain of the VCCS
 $I_{in} = 0$

②

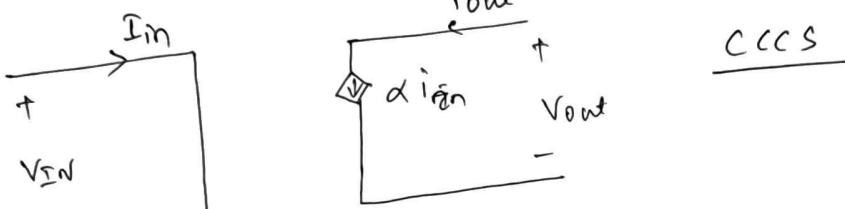

CCCS


$$I_{out} = \alpha I_{in}$$

α : current transfer ratio

$$V_{in} = 0$$

unit A/A

③

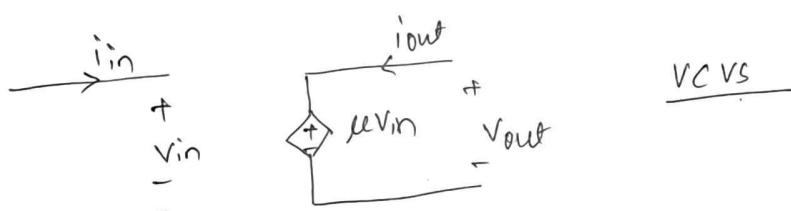


VCVS

$V_{out} = \mu V_{in}$ ' μ ' is the gain with unit V/V
voltage transfer ratio

$$I_{in} = 0$$

④

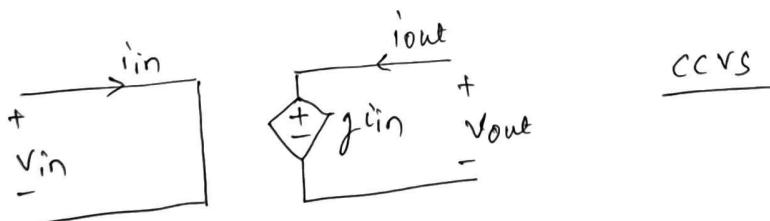

CCVS

$V_{out} = j I_{in}$ ' j ' = transresistance unit of resistance


Note: The presence of the dependent sources does not alter the manner in which our approach to circuit analysis is applied.

first analyze the i/p side then o/p side.

→ on an idealized dependent source, the i/p port (control port)

↳ an open circuit if the guiding variable is a voltage.

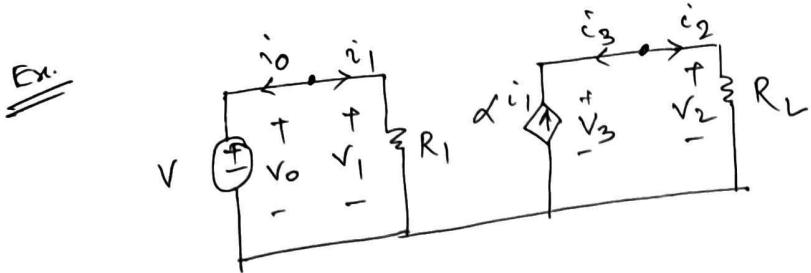→ i/p is short circuit if the guiding variable is a current.



$$V_0 = V = V_1$$

$$V_1 = i_1 R_1 \quad V_2 = i_2 R_2$$

$$i_3 = -\alpha i_1$$

KCL

$$i_0 + i_1 = 0$$



$$i_2 + i_3 = 0$$

KVL

$$V_0 = V_1 \quad \Rightarrow -i_0 = i_1 = \frac{V}{R_1}$$

$$V_2 = V_3 \quad \Rightarrow -i_3 = i_2 = \frac{\alpha V}{R_1}$$

$$V_2 = V_3 = \frac{\alpha R_2 V}{R_1}$$

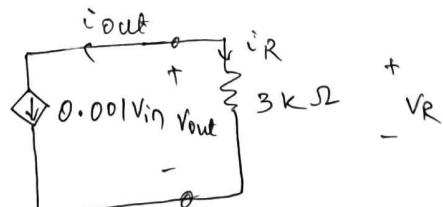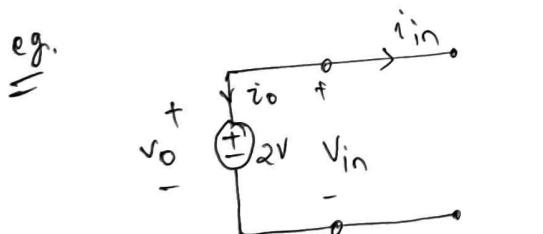

Find out all the branch variables.

$$0.001 V_{in} = 0.002 A$$

$$i_{out} = 0.002 A$$

$$i_R = -0.002 A$$


$$V_R = 3 \times 10^3 \times i_R = -6 V$$

$$V_{out} = V_R = -6 V$$

Power into the dependent current source

$$V_{out} \times i_{out} = -6 \times 0.002 = -0.012 W$$

mesh
Ex

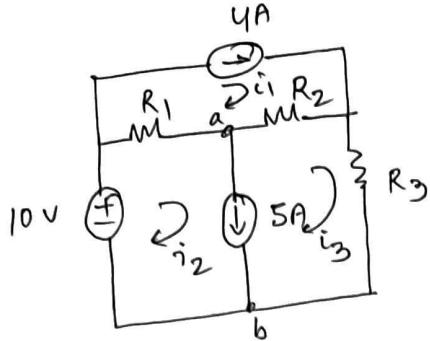

(7)

$$R_1 = R_2 = 1\Omega \quad \text{and} \quad R_3 = 2\Omega$$

$$i_1 = 4$$

mesh ①

$$i_2 - i_3 = 5$$

mesh ②

$$R_1 (i_2 - i_1) + V_{ab} = 10$$

mesh ③

$$R_2 (i_3 - i_1) + R_3 i_3 = V_{ab}$$


$$R_1 (i_2 - 4) + R_2 (i_3 - 4) + R_3 i_3 = 10$$

$$\Rightarrow R_1 (5 + i_3 - 4) + R_2 (i_3 - 4) + R_3 i_3 = 10$$

$$\Rightarrow i_3 = \frac{13}{4} \text{ A} \quad \& \quad i_2 = 5 + i_3 = \frac{33}{4} \text{ A} .$$

Note: When a CR† contains a dependent source, the controlling current or voltage of that dependent source must be expressed as a function of the mesh currents.

Ex

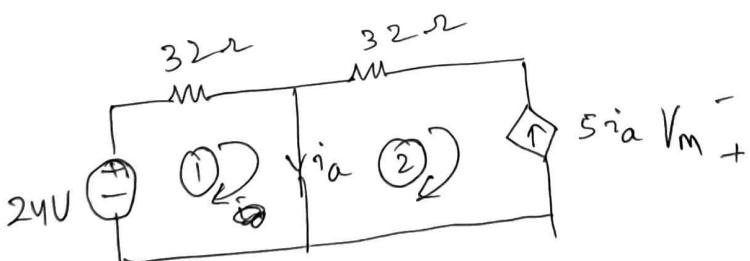

$$i_a = i_1 - i_2 \Rightarrow 5i_a = -i_2 .$$

$$i_2 = -5i_a = -5(i_1 - i_2)$$

$$\Rightarrow -4i_2 = -5i_1 \Rightarrow i_2 = \frac{5}{4}i_1$$

$$\Rightarrow 32i_1 - 24 = 0 \Rightarrow i_1 = \frac{3}{4} \text{ A}$$


$$i_2 = \frac{5}{4}i_1 = \frac{15}{16} \text{ A}$$

mesh ②

$$32i_2 - V_m = 0 \Rightarrow V_m = 32i_2$$



$$\Rightarrow V_m = 32 \left(\frac{15}{16} \right) = 30 \text{ V}$$

Ex ②
pending

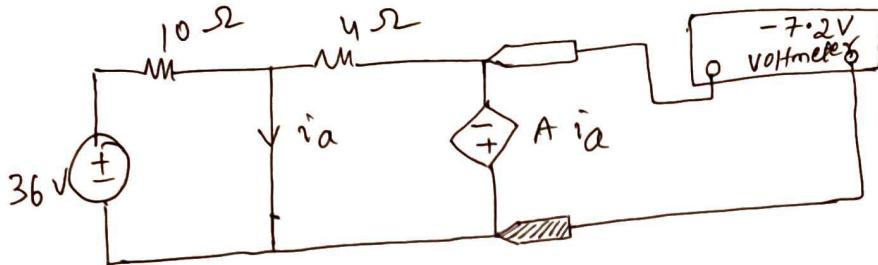

find the value of gain, A , of the CCVS.

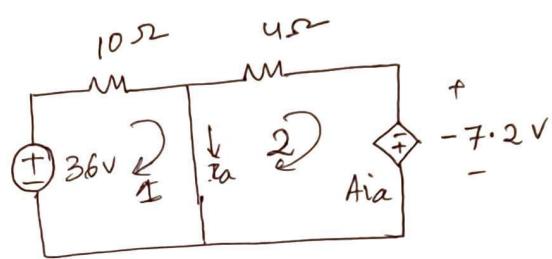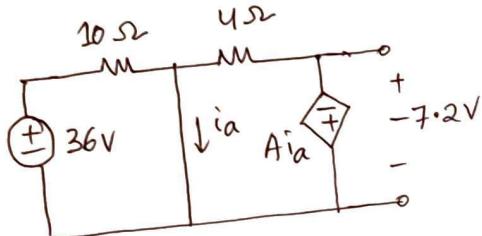Step 1 replace the voltmeter by an equivalent open ckt and labeling the voltage measured by the voltmeter.



$$Ai_a = -(-7.2) = 7.2 \text{ V}$$

Note: The controlling current of the dependent source, i_a , is the current in a short circuit. The short circuit current can be expressed in terms of the mesh current as

$$i_a = i_1 - i_2$$

Apply KVL to mesh 1 to get $10i_1 - 36 = 0 \Rightarrow i_1 = 3.6 \text{ A}$


KVL to mesh 2 to get :-

$$4i_2 + (-7.2) = 0 \Rightarrow i_2 = 1.8 \text{ A}$$

$$A = \frac{Ai_a}{i_a} = \frac{Aix_a}{i_a} = \frac{Ai_a}{i_1 - i_2} = \frac{7.2}{3.6 - 1.8} = 4 \text{ V/A}$$

(8)

Super mesh :-

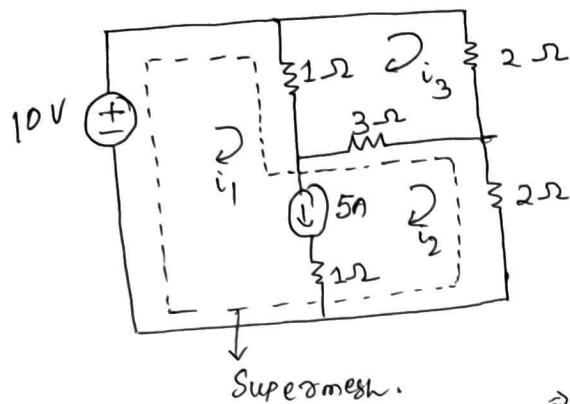

It is impossible to write the mesh eqns for the meshes ① and ③ independently, \Rightarrow Supermesh.

$$\begin{aligned} -10 + 1(i_1 - i_3) + 3(i_2 - i_3) + 2i_2 &= 10 \\ \Rightarrow i_1 - i_3 + 3i_2 - 3i_3 + 2i_2 &= 10 \\ \Rightarrow i_1 - 4i_3 + 5i_2 &= 10 \quad (\text{KVL for super mesh}) \end{aligned}$$

Mesh ③

$$\begin{aligned} 1(i_3 - i_1) + 2i_3 + 3(i_3 - i_2) &= 0 \\ i_3 - i_1 + 2i_3 + 3i_3 - 3i_2 &= 0 \\ \Rightarrow 6i_3 - 3i_2 - i_1 &= 0 \\ \Rightarrow i_1 - i_2 &= 5 \\ \Rightarrow 1i_1 + 5i_2 - 4i_3 &= 10 \\ \Rightarrow -1i_1 - 3i_2 + 6i_3 &= 0 \end{aligned}$$

$$\text{Current source } \Rightarrow 1i_1 - 1i_2 = 5$$

$$i_2 = 2.5 \text{ A}, i_1 = 7.5 \text{ A} \& i_3 = 2.5 \text{ A}$$

Case

Method

- ① A current source appears on the periphery of only one mesh 'n'

\Rightarrow Equate the mesh current i_n to the current source accounting for the direction of the current source.

- ② A current source is common to two meshes

\Rightarrow Assume a voltage V_{ab} across the terminal of the current source, write the KVL eqns for the two meshes and add them to eliminate V_{ab} .

Or
Create a supermesh as the



Types of element

- ① Active and passive
- ② Linear and non-linear
- ③ Bilateral and unilateral
- ④ Distributed and lumped
- ⑤ Time invariant and time varying


Linear: * characteristic is a straight line through the origin, otherwise it is said to be non-linear.

Bilateral: Same impedance for the different directions of the same current flow otherwise unilateral.

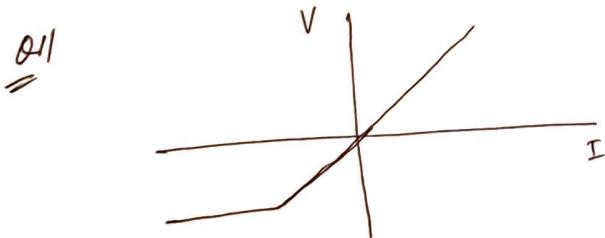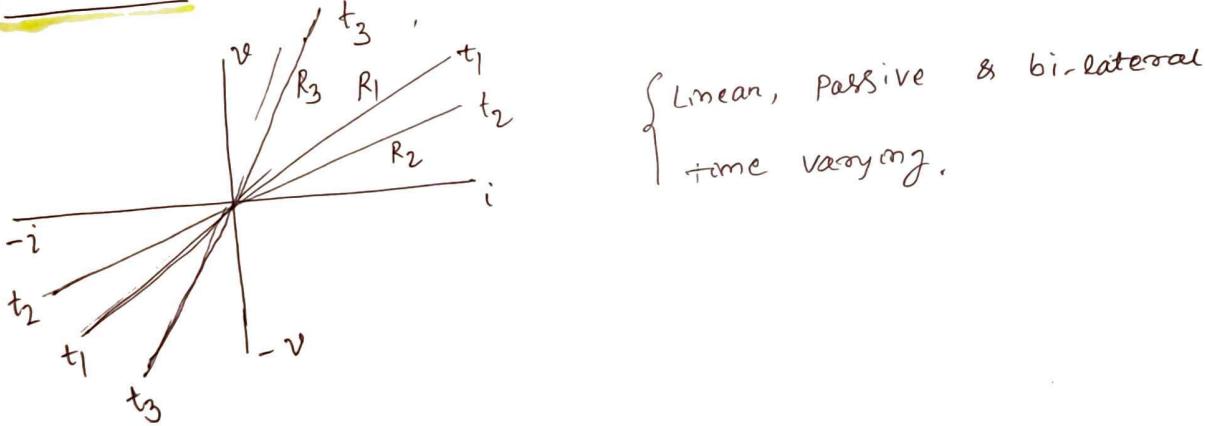
Time varying: Characteristic change with respect to time



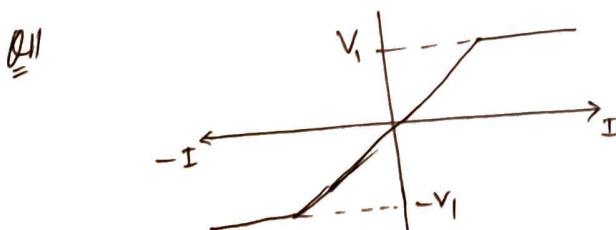Non-linear
passive (slope is +ve)
unilateral.




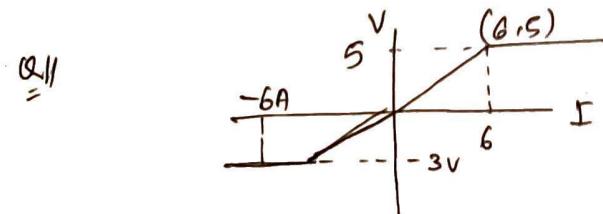→ Bilateral
→ Passive Slope is +ve
→ Non-linear




Non-linear
unilateral
passive

IES - 04
QII

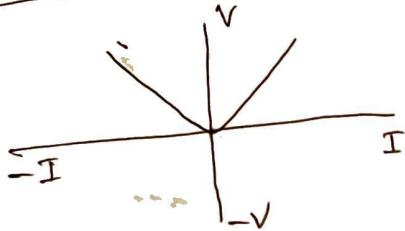


- ⑨
- Non-linear
 - unilateral
 - ACTIVE

QII $i = 2V^2$

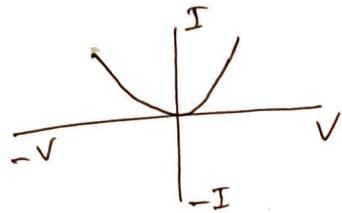


Non-linear
unilateral ($Z_1 \neq Z_2$)
Active

QII *

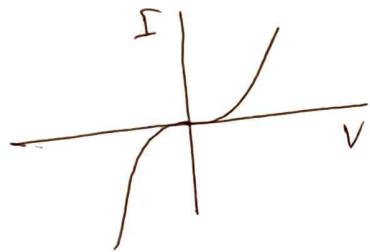

- Non-linear
- passive
- Bilateral $Z_1 = Z_2$

QII

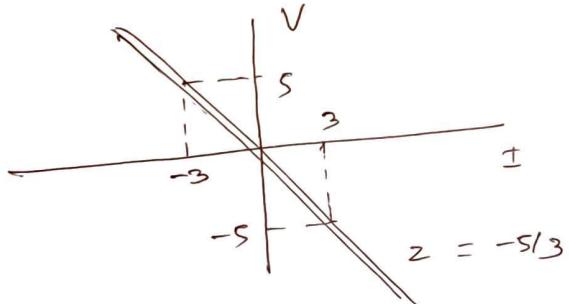

Active
Bilateral
Linear


Note : all linear elements are bilateral but reverse is not true



Node analysis

- It is very simple, but complicated by the presence of floating independent voltage sources and by the presence of dependent sources.
- Floating independent voltage source is a source that has neither terminal connected to ground nor through one or more other independent voltage sources.

Ex:

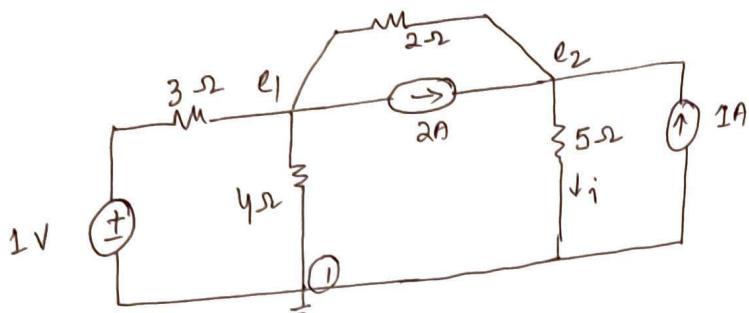

Determine the current 'i' through 5Ω resistor.

→ Use node method to solve the CKT

- ① Step 1 - Choose node 1 as ground node
- ② Step 2 - Label the potentials of the remaining with respect to the ground node.

$$\text{KCL} \quad \frac{e_1 - 1}{3} + \frac{e_1}{4} + \frac{e_1 - e_2}{2} + 2 = 0 \quad \text{--- (I)}$$

$$-2 + \frac{e_2 - e_1}{2} + \frac{e_2}{5} - 1 = 0 \quad \text{--- (II)}$$


$$e_1 = 0.65, e_2 = 4.75$$

$$i = \frac{4.75}{5} = 0.95 \text{ A}$$

Floating case

- The regular node analysis does not work if that the element law for an independent voltage source does not relate its branch current to its branch voltage.

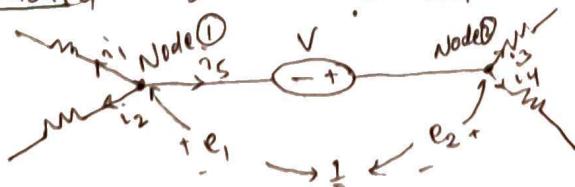- To apply node analysis to a circuit containing a floating voltage source we must realize that the node voltage at the terminals of the source are directly related by the element law for that source.




$$e_2 = V + e_1$$

$$i_1 + i_2 + i_3 + i_4 = 0$$

KCL for super node


(Eqn ①)

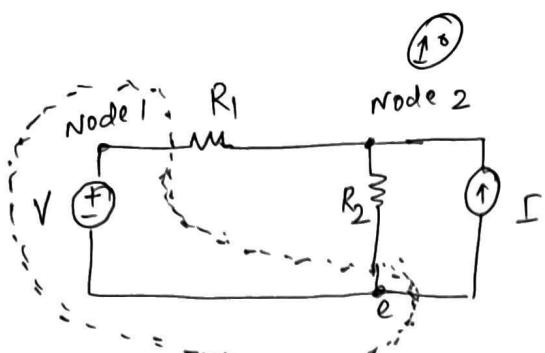

$$\frac{e+v}{R_1} + \frac{e}{R_2} + I = 0 \quad \checkmark$$

$$e = \frac{-R_1 R_2}{R_1 + R_2} I - \frac{R_2}{R_1 + R_2} v \quad \checkmark$$

②

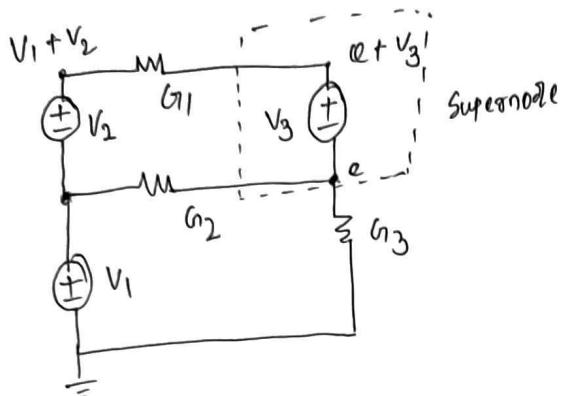

$$G_1(e + v_3) - (v_1 + v_2) + G_2(e - v_1) + G_3 e = 0$$


$$\Rightarrow e = \frac{(G_1 + G_2)v_1 + G_1 v_2 - G_1 v_3}{G_1 + G_2 + G_3} \quad \checkmark$$

Case ① The voltage source connects node of and the reference node.

→ Set v_g equal to the source voltage accounting for the polarities and proceed to write the KCL at the remaining node. ✓

Case ② - The voltage source lies betw two nodes 'a' and 'b'.

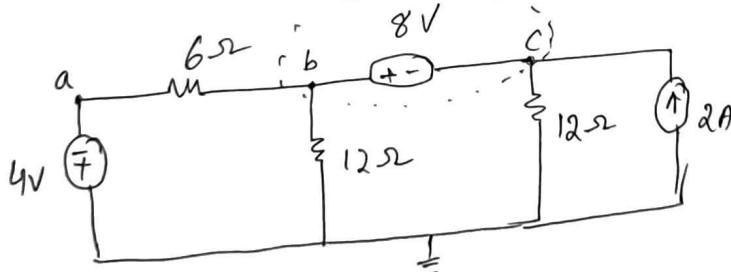→ Create a supernode that incorporates 'a' and 'b' and equate the sum of all the currents into the super node to zero. ✓



$$v_a = -4V, v_b = v_c + 8 \quad \checkmark$$

$$\text{KCL at supernode} \Rightarrow \frac{v_b - v_a}{6} + \frac{v_b}{12} + \frac{v_c}{12} = 2 \quad -\text{①}$$

$$3v_b + v_c = 24 + 2v_a \quad \checkmark$$

$$\stackrel{(2)}{\Rightarrow} v_a = -4V \quad \text{and} \quad v_b = v_c + 8 \quad -\text{③}$$


$$3(v_c + 8) + v_c = 24 + 2(-4) \Rightarrow v_c = -2V \quad \checkmark$$

$$v_b = v_c + 8 = -2 + 8 = 6V$$

Node voltage with dependent sources :-

→ When a circuit contains a dependent source, the controlling current or voltage of that dependent source must be expressed as a function of the node voltages.

Eg.

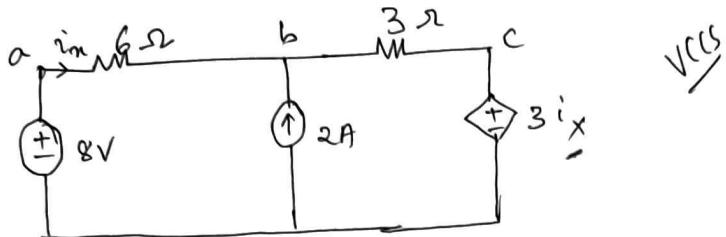

The controlling current 'i_m'

$$i_m = \frac{V_a - V_b}{6}$$

$$V_a = 8V$$

$$i_m = \frac{8 - V_b}{6}$$

at 'c'

$$V_c = 3i_m = 3\left(\frac{8 - V_b}{6}\right) = 4 - \frac{V_b}{2}$$

KCL at node 'b'


$$\frac{8 - V_b}{6} + 2 = \frac{V_b - V_c}{3}$$

$$\Rightarrow \frac{8 - V_b}{6} + 2 = V_b - \left(4 - \frac{V_b}{2}\right) = \frac{V_b}{2} - \frac{4}{3}$$

$$V_b = 7V \quad ; \quad V_c = 4 - \frac{V_b}{2} = \frac{1}{2}V$$

Eg

V_{CIS}

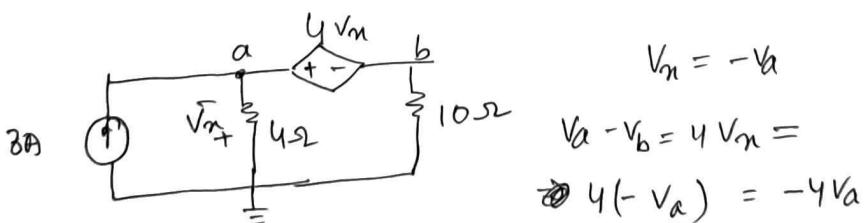


KCL at supernode

$$3 = \frac{V_a}{4} + \frac{V_b}{10} \Rightarrow 3 = \frac{V_a}{4} + \frac{5V_a}{10} \Rightarrow \frac{3}{4}V_a$$

$$\Rightarrow V_a = 4V \quad \Rightarrow V_b = 5V_a = 20V$$

$$\boxed{V_b = 5V_a}$$

③

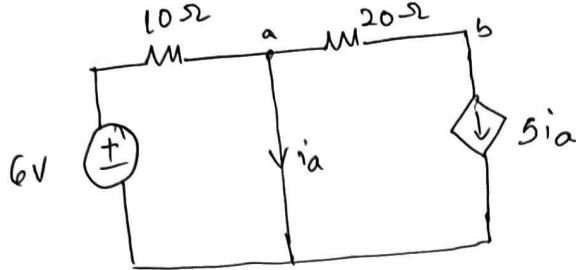CCCS Eg.

KCL at 'a'

$$\frac{6 - V_a}{10} = i_a + \frac{V_a - V_b}{20} - 0$$


$$V_a = 0 \quad (2) \quad i_a = \frac{12 + V_b}{20}$$

KCL at 'b'

$$\frac{0 - V_b}{20} = 5 i_a \Rightarrow \frac{0 - V_b}{20} = 5 \left(\frac{12 + V_b}{20} \right)$$

$$\Rightarrow V_b = -10 \text{ V}$$

Q11

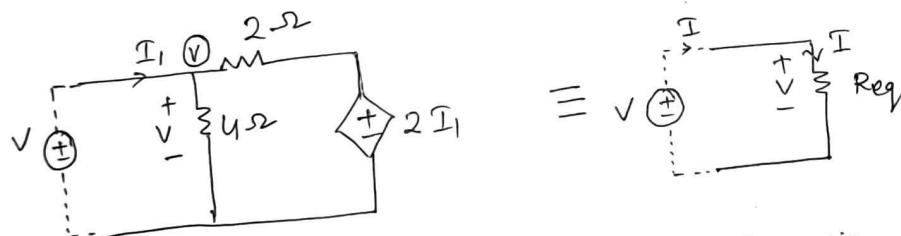


The ckt shown above will act as a load resistor of

- (a) $\frac{1}{3} \Omega$ (b) $\frac{2}{3} \Omega$ (c) $\frac{4}{3} \Omega$ (d) $\frac{8}{3} \Omega$

Note: Since no independent source in the n/w, the n/w is said to be unenergised, so called a dead n/w. The behavior of this n/w if a load resistor behavior.

$$-I_1 + \frac{V - 0}{4} + \frac{V - 2I_1}{2} = 0$$
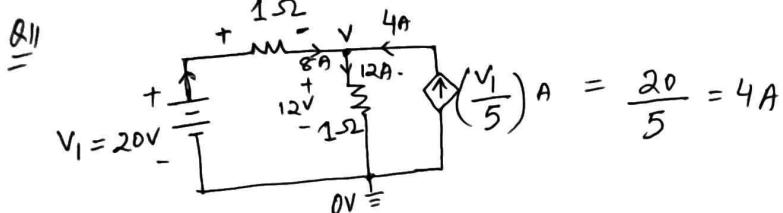
$$\Rightarrow \frac{V}{I} = R_{eq} = \frac{8}{3} \Omega$$



$$\frac{V-20}{1} + \frac{V}{1} - 4 = 0$$

$$\Rightarrow V = 12V$$

$$P_{\left(\frac{V_1}{5}\right)A} = 12 \times 4 = 48W \text{ (del)}$$

Verify V.T.T

$$P_{20V} = 20 \times 8 = 160W \text{ (del)}$$

$$P_{12\Omega} = 8 \times 8 = 64W \text{ (abs)}$$

$$P_{12\Omega} = 12 \times 12 = 144W \text{ (abs)}$$


$$P_{\left(\frac{V_1}{5}\right)} = 48W \text{ (del)}$$

The dependent source shown in fig

- (a) delivers 24W
- (b) absorbs 24W
- (c) delivers 48W
- (d) absorbs 48W

$$\begin{aligned} P_{\text{total}}^{(\text{abs})} &= 64 + 144 = 208W \\ P_{\text{total}} \text{ (del)} &= 160 + 48 \\ &= 208W \end{aligned}$$

Q11 Det I

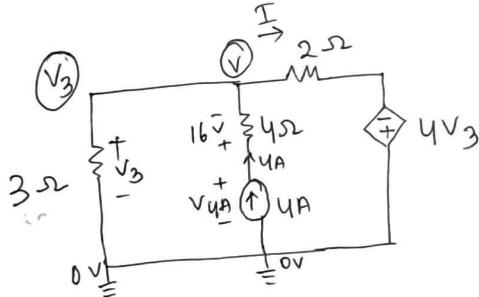

$$V_3 = V$$

$$\frac{V_3}{3} - 4 + \frac{V_3 + 4V_3}{2} = 0$$

$$\Rightarrow V_3 = \frac{24}{17}V$$

$$I = \frac{V_3 + 4V_3}{2} = \frac{60}{17}A$$


$$KVL \Rightarrow V_3 + 16 - V_{4A} = 0$$

$$V_{4A} = \left(16 + \frac{24}{17}\right)V = 17.41V$$

$$\underline{H.W} \quad V.T.T \quad P_{3\Omega} = \frac{8}{17} \times \frac{24}{17} \text{ (abs)} = 0.66W \text{ (abs)} ; \quad P_{4\Omega} = 64W \text{ (abs)}$$

$$P_{2\Omega} = \frac{60}{17} \times \frac{120}{17} = 24.91W \text{ (abs)} ; \quad P_{4V3} = 19.93W \text{ (del)} \\ P_{4V3} = 69.64W \text{ (del)}$$
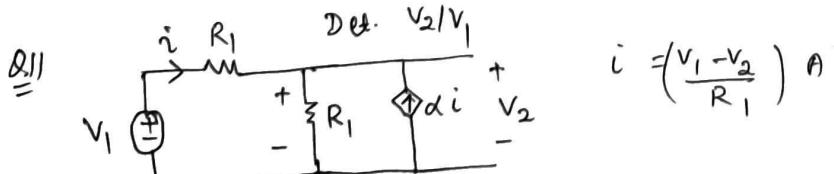
$$P_{\text{abs}} = P_{\text{del}} = 89.57W$$




Proof $KVL: V_1 - R_1 i - V_2 = 0$
 $\Rightarrow i = \left(\frac{V_1 - V_2}{R_1}\right) A$

$$\text{Nodal} \quad -i + \frac{V_2}{R_1} - di = 0 \Rightarrow (1+d)i = \frac{V_2}{R_1} \Rightarrow (1+d)\left(\frac{V_1 - V_2}{R_1}\right) = \frac{V_2}{R_1}$$

$$\Rightarrow (1+d)V_1 - (1+d)V_2 - V_2 = 0 \Rightarrow (1+d)V_1 - (2+d)V_2 = 0$$

$$\Rightarrow (1+d)V_1 = (2+d)V_2 \Rightarrow \boxed{\frac{V_2}{V_1} = \frac{1+d}{2+d}}$$

(12)

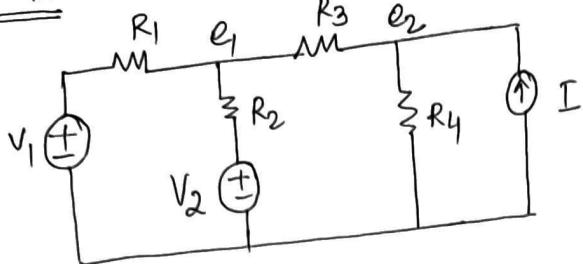Superposition Thm.

A n/w with three sources.

After node analysis (in terms of conductance)

$$(V_1 - e_1) G_1 + (V_2 - e_1) G_2 + (e_2 - e_1) G_3 = 0$$

$$\Rightarrow (e_1 - e_2) G_3 - e_2 G_4 + I = 0$$

Collecting the source terms on the left side

$$V_1 G_1 + V_2 G_2 = e_1 (G_1 + G_2 + G_3) - e_2 G_3$$

$$I = -e_1 G_3 + e_2 (G_3 + G_4)$$

Write the eqn for e_1

$$e_1 = \frac{(V_1 G_1 + V_2 G_2)(G_3 + G_4) + I G_3}{(G_1 + G_2 + G_3)(G_3 + G_4) - G_3^2}$$

$$= \frac{V_1 G_1 (G_3 + G_4) + V_2 G_2 (G_3 + G_4) + I G_3}{G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4 + G_3 G_4}$$

→ All denominator terms are of the same sign. Thus, the denominator can't be made zero for any non-zero value of conductance.

→ Each term on the right consists of one source term multiplied by a resistive (or conductive) factor.

→ Because of linearity, the first term remains unchanged if the other two sources are set to zero.

$$\left\{ \begin{array}{l} \text{Additivity} \Rightarrow f(x_1 + x_2) = f(x_1) + f(x_2) \\ \text{Homogeneity} \Rightarrow f(ax) = a f(x) \end{array} \right.$$

→ Setting a voltage source to zero is equivalent to replacing that source by a short ckt.


→ Similarly, current source to zero means open ckt.

→ In a linear N/W : With a number of independent sources, the response can be found by summing the responses to each independent sources acting alone with all other independent sources set to zero.

Superposition Rule for dependent Sources :-

→ A practical way is to leave all the dependent sources in the Ckt. The N/W can then be solved for one independent source at a time by setting all other independent sources to zero, and summing the individual responses.


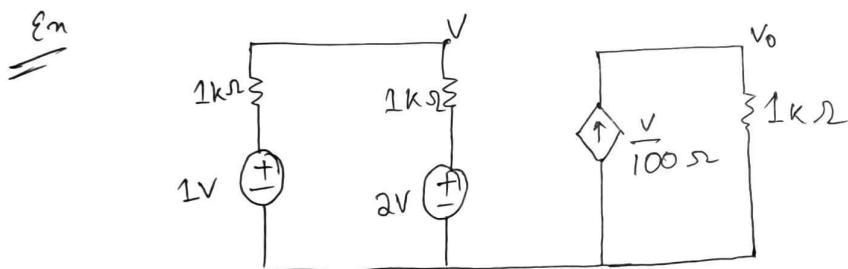
→ If a dependent source is present, it is never deactivated and must remain active (unaltered) during the superposition process.



Find V_o .

⇒ 1V Source acting alone :-
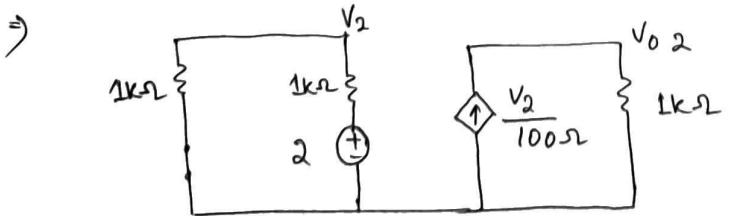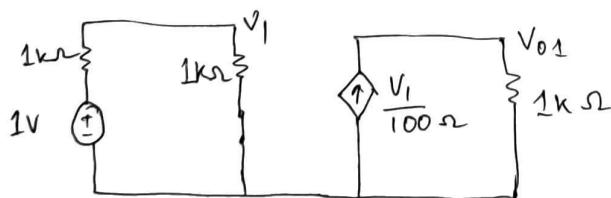
$$V_1 = 0.5V \Rightarrow V_{o1} = \frac{1}{100} V_1 \times 1k\Omega = 5V$$



$$\begin{aligned} V_2 &= 1V \\ V_{o2} &= \frac{1}{100} V_2 \times 1k\Omega \\ &= 10V \end{aligned}$$

$$V_o = \underline{V_{o1} + V_{o2} = 15V}$$

The need of thm

(13)

: in a complicated n/w in presence of several sources, nodes, and meshes if the response in a single element is desired, then the n/w thm one used.

Properties of SPT



- (i) This thm is applicable only for linear n/w.
i.e. n/w with R, L, C, transformer and linear controlled sources as element.
- (ii) Both for active & passive.

Homogeneity principle:

It is a principle obeyed by all the linear n/w.





Defn :- in a linear n/w, if the excitation is multiplied with a constant 'K' then the responses in all the other branches in the n/w are also multiplied with same constant 'K'.

Proof

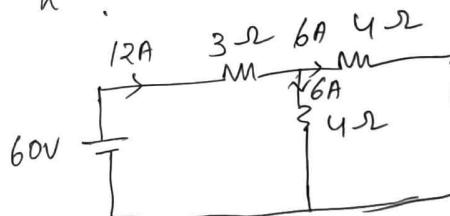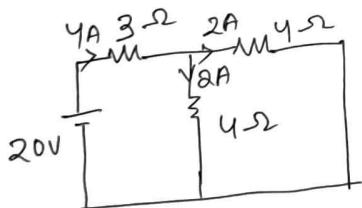


Excitation is multiplied by 3
and hence the response also.

All Det 'I'

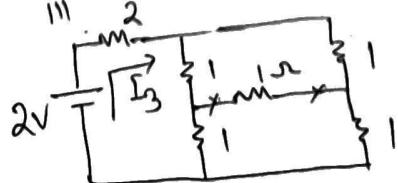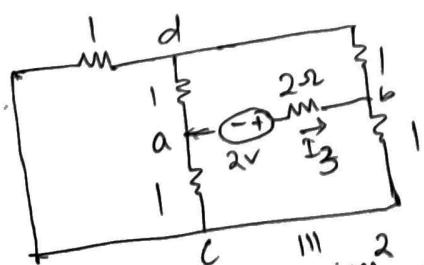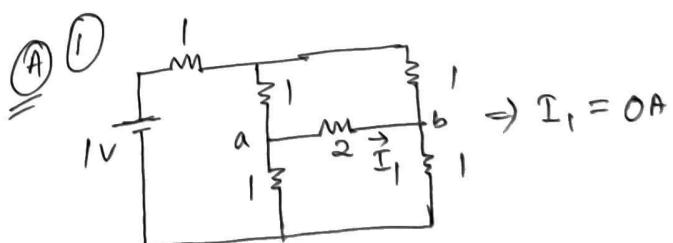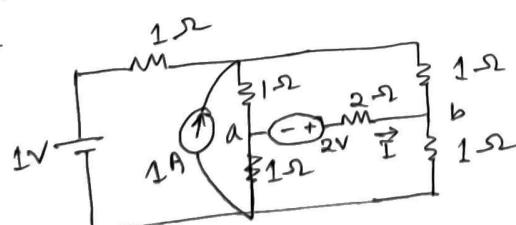


$$I_3 = \frac{2}{2 + (2|1|2)} = \frac{2}{3} A$$

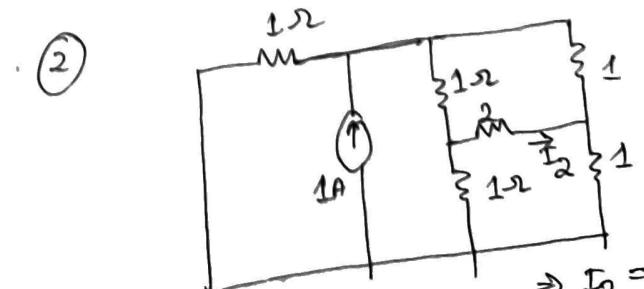



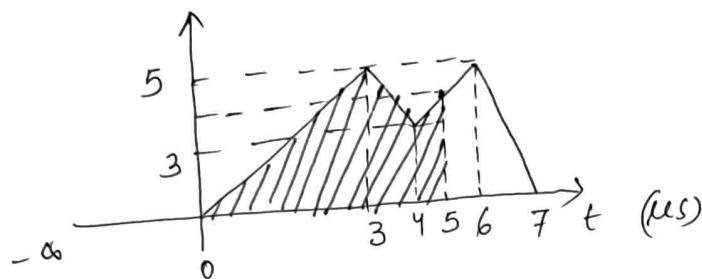Problems on the Power and Energy :-

- ① Figure shows the current flowing through a capacitor. Determine the charge acquired by the capacitor upto the first 5 μs if .



$$i(t) = \frac{d\varphi(t)}{dt} \text{ Amperes}$$

$$d\varphi(t) = i(t) dt \Rightarrow \varphi = \int_{-\infty}^t i(t). dt$$

$= \int_0^{5 \mu s} i(t) dt = \text{Area under } i(t) \text{ upto } 5 \mu s$

(4, 3) (6, 5)





$$\text{Slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{5 - 3}{6 - 4} = 1$$

$$\varphi = \varphi_1 \Big|_{0-3 \mu s} + \varphi_2 \Big|_{3-4 \mu s} + \varphi_3 \Big|_{4-5 \mu s}$$

$$= \left(\frac{1}{2} \times 3 \times 5 \right) + \left[\left(\frac{1}{2} \times 1 \times 2 \right) + (1 \times 3) \right] + \left(\frac{1}{2} \times 1 \times 1 + 1 \times 3 \right)$$


$$= 15 \mu s$$

Q1

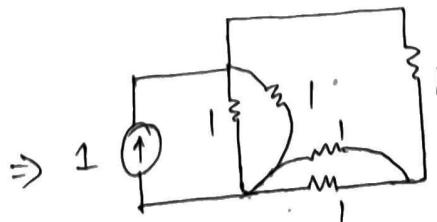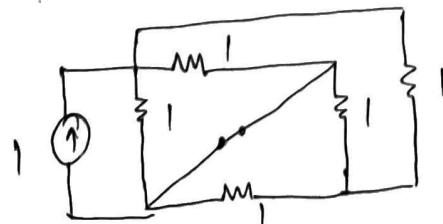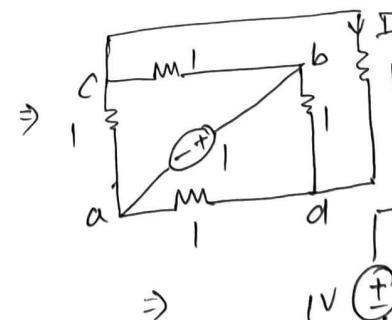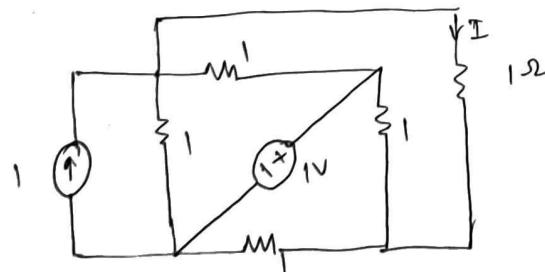


$$I_2 = \frac{1 \times 0.5}{0.5 + 1.5} = 0.25 A = I$$

Q4

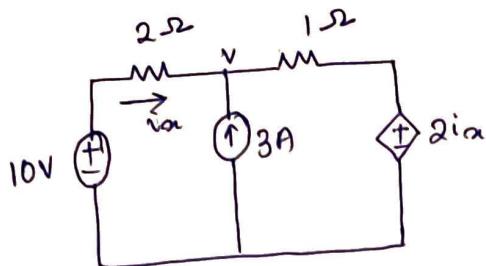QII Det i_x Method ① NDA


$$i_x = \frac{10 - V}{2} \text{ A}$$

$$\frac{V - 10}{2} - 3 + \frac{V - 2i_x}{1} = 0 \Rightarrow V = 7.2V, i_x = 1.4A$$

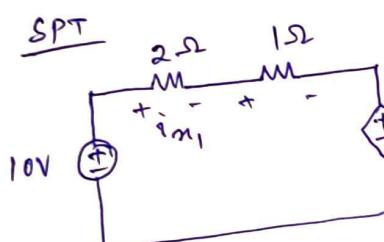Method ② SPT

$$10 - 2i_{m1} - i_x - 2i_{m1} = 0$$

$$\Rightarrow i_{m1} = 2A$$

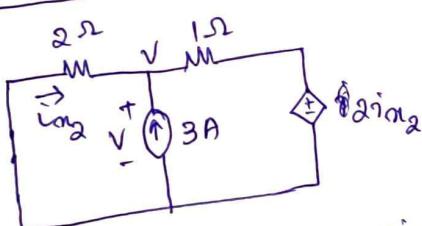


$$\begin{aligned} & \xrightarrow{\text{KVL}} -2i_{m2} - V = 0 \\ & \Rightarrow V = 2i_{m2} \end{aligned}$$

$$\text{NODAL} \quad -i_{m2} - 3 + \frac{V - 2i_{m2}}{1} = 0 \Rightarrow i_{m2} = -0.6A$$

$$\text{By SPT} \quad i_x = i_{m1} + i_{m2} = 2 + (-0.6) = 1.4A.$$

QII

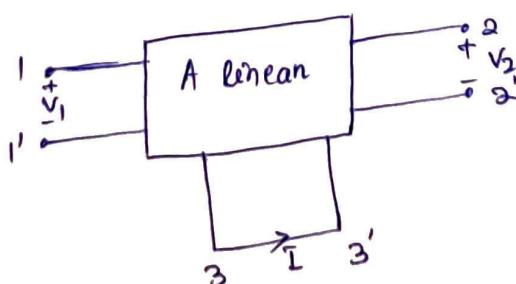Det I when $V_1 = 10V$ & $V_2 = -5V$

V_1	V_2	I
2	0	0.5A
0	5V	-1A

$$\begin{aligned} I &= k_1 V_1 + k_2 V_2 \Rightarrow 0.5 = k_1 \cdot 2 + 0 \Rightarrow k_1 = \frac{1}{4} \\ &\Rightarrow -1 = 0 + k_2 \cdot 5 \Rightarrow k_2 = -\frac{1}{5} \end{aligned}$$

$$I = \frac{V_1}{4} - \frac{V_2}{5} \Rightarrow \frac{10}{4} + \frac{5}{5} = 2.5 + 1 = \underline{3.5}$$

Ans

Q11 A network contains several resistors, one of which is designated as 'R' and two DC sources. The power consumed by the 'R' is 'P' when the +ve source is acting alone and P_2 when the second source is acting alone. If both the sources are acting simultaneously then the power dissipated by 'R' is.

$$\textcircled{A} \quad \begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{---} \\ | \qquad R \\ | \end{array} \quad I^2 R = P_1 \text{ (given)} \Rightarrow I_1 = \sqrt{\frac{P_1}{R}} \quad \text{---} \textcircled{1}$$

$$I_2^2 R = P_2 \text{ (given)} \Rightarrow I_2 = \sqrt{\frac{P_2}{R}} \quad \text{---} \textcircled{2}$$

$$\text{By SPT} \quad I = I_1 + I_2 = \left(\sqrt{\frac{P_1}{R}} + \sqrt{\frac{P_2}{R}} \right) A$$

$$\begin{array}{c} \xrightarrow{\hspace{1cm}} \\ \text{---} \\ | \qquad R \\ | \\ + \quad - \end{array} \quad \text{When } V = IR$$

$$\text{By Tellegen's thm} \quad P = VI = R I \cdot I = I^2 R = \left(\sqrt{P_1} \pm \sqrt{P_2} \right)^2 W$$

Q11 If $P_1 = 18W$ & $P_2 = 50W$ then P_{\max} & P_{\min} are

$$P = \left(\sqrt{18} \pm \sqrt{50} \right)^2 = 2 (3 \pm 5)^2$$

$$P_{\max} = 2 (3+5)^2 = 128W$$






$$P_{\min} = 2 (3-5)^2 = 8W$$

(15)

The Thevenin's and Norton's Theorem :-

Properties : Same as SPT


Procedure :

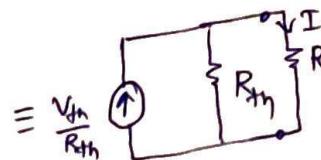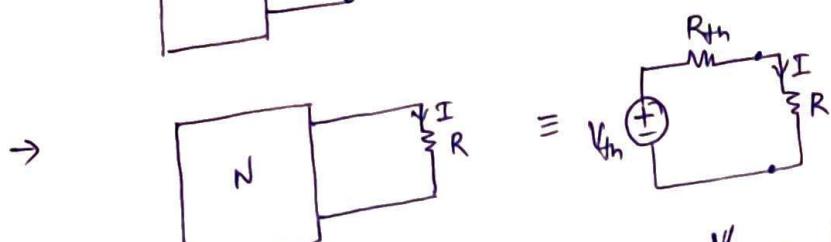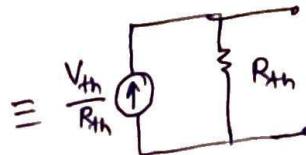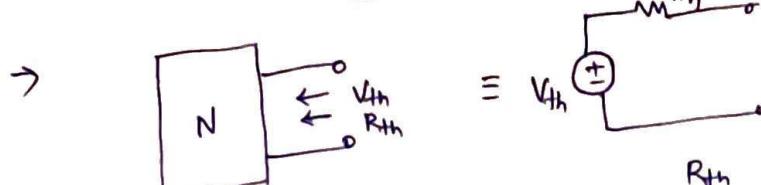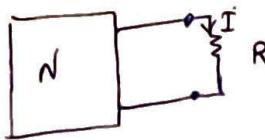

$$I = \frac{\frac{V_{th} \times R_{th}}{R_{th} + R}}{R_{th} + R} = \frac{V_{th}}{R_{th} + R}$$

3 cases

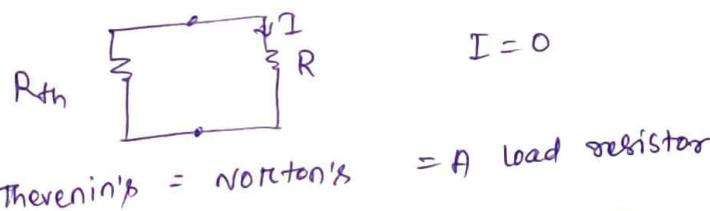
- ① All are independent sources $\Rightarrow V_{th}, R_{th}$
- ② Atleast one independent source and atleast one dependent source
- ③ All are dependent sources $\Rightarrow V_{th} = 0; I_m = 0A, \text{ but } R_{th} \neq 0$



$$I = 0$$

= A load resistor

Case ①
 \Leftrightarrow

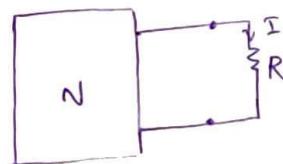


$I = 3A \text{ & } 1.5A \text{ when } R = 0\Omega \text{ & } 2\Omega, \text{ respectively}$

Det I when $R = 1\Omega$

④

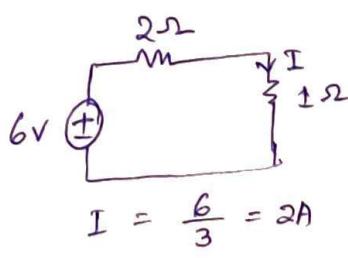
$$\frac{V_{th}}{R_{th}} = 3 \quad \parallel \quad V_{th} = 6V \\ \frac{V_{th}}{R_{th}+2} = 1.5 \quad \quad \quad R_{th} = 2\Omega$$




Q1 An ideal voltage and current sources are connected in parallel, this combination will have

- (a) Both Thevenin's and Norton's equivalent
- (b) Thevenin's but ^{not} Norton's
- (c) Norton's but not Thevenin's
- (d) Neither Norton nor Thevenin

A

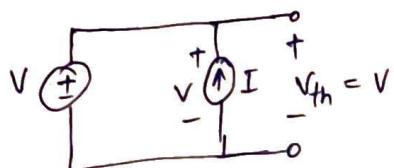


$$\leftarrow R_{th} = 0$$

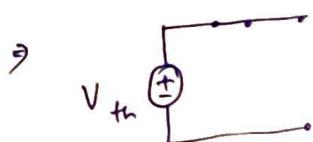

An ideal voltage source


Note: It is impossible to convert an ideal voltage source into its equivalent current source and hence Norton's equivalent does not exist.

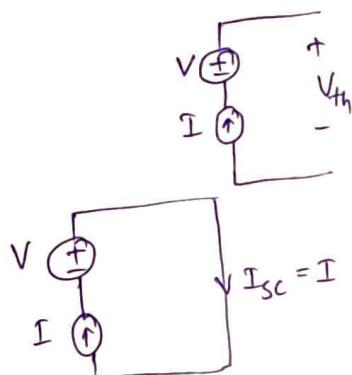Q2 In the above case if the elements are connected in series.




$$\begin{aligned} \text{KVL} \Rightarrow V_{th} &= V + \text{any value} \\ &= \text{Any value} = \text{unknown?} \end{aligned}$$

$$\leftarrow R_{th} = \infty$$

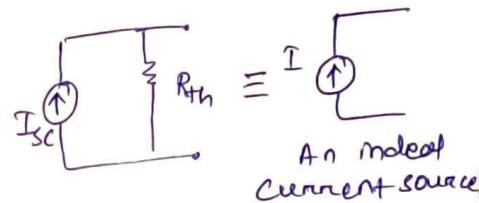

An ideal current source

Q3

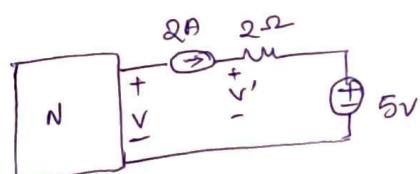


Def. 'V'

- (a) 9V (b) 5V (c) 1V (d) None

$$\text{KVL} \Rightarrow V' - 4 - 5 = 0 \Rightarrow V' = 9V$$

$$\text{KVL} \Rightarrow V = V' + \text{Any value} = 9 + \text{Any value} = \text{Any value} = \text{None}$$

Thevenin's

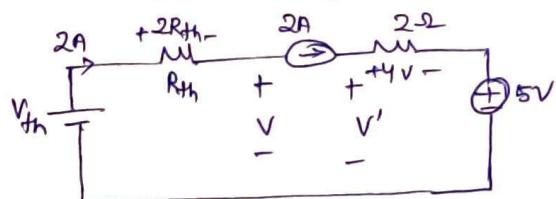

KVL

$$V_{th} - 2R_{th} - V = 0$$

$$\Rightarrow V = V_{th} - 2R_{th} = \text{un-known.}$$


7d

1


25A

(16)

$$G = \frac{1}{R}$$

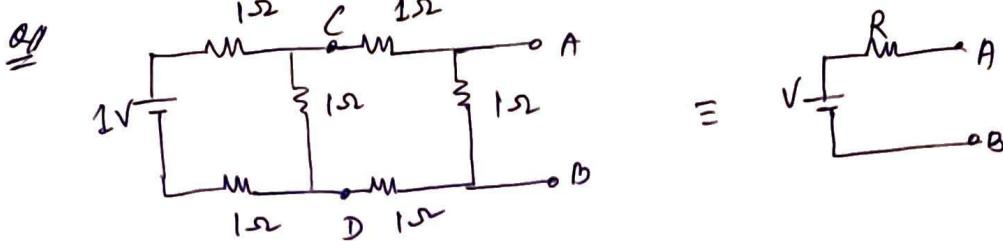


$$\equiv V \frac{1}{R} \rightarrow A$$

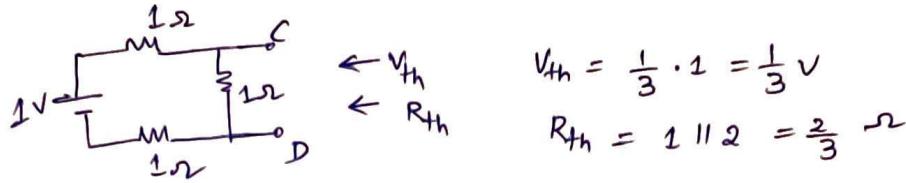


$$V_{th} = \frac{1}{3} \cdot 1 = \frac{1}{3} V$$
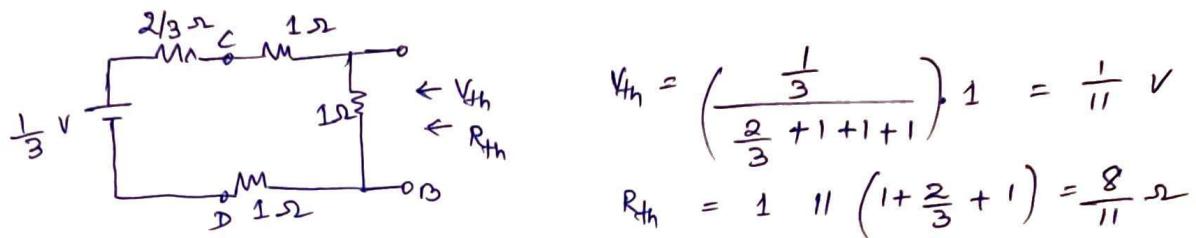
$$R_{th} = 1 \parallel 2 = \frac{2}{3} \Omega$$



$$V_{th} = \left(\frac{\frac{1}{3}}{\frac{2}{3} + 1 + 1 + 1} \right) \cdot 1 = \frac{1}{11} V$$

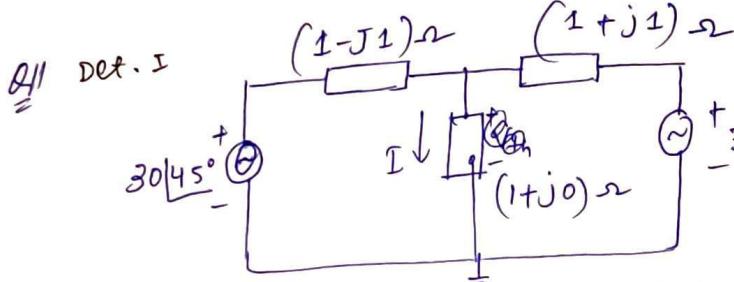
$$R_{th} = 1 \parallel \left(1 + \frac{2}{3} + 1 \right) = \frac{8}{11} \Omega$$



NDA

$$\frac{V - 30\angle 45^\circ}{1-j1} + \frac{V}{1+j1} + \frac{V - 30\angle -45^\circ}{1+j2} = 0$$
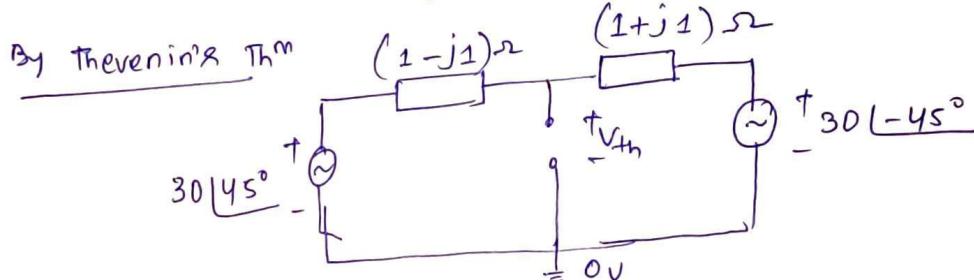
$$\Rightarrow V - () = 0 \Rightarrow V = 0 \Rightarrow I = 0 A$$





Nodal

$$\frac{V_{th} - 30\angle 45^\circ}{1-j1} + \frac{V_{th} - 30\angle -45^\circ}{1+j1} = 0$$

$$\Rightarrow V_{th} = 0$$
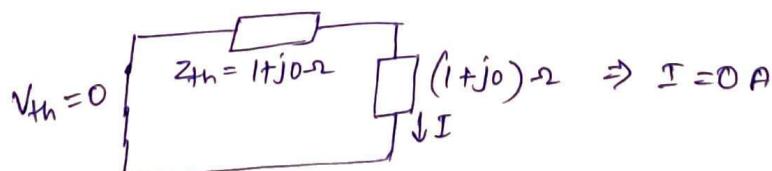
$$Z_{th} = (1-j1) \parallel (1+j1) = (1+j0) \Omega$$




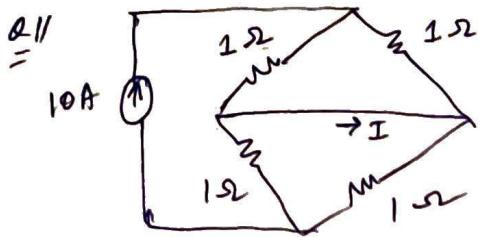

Prove $I = 0 \text{ A}$

$$1 \times 1 = 1 \times 1 \Rightarrow I = 0 \text{ A}$$

Proof

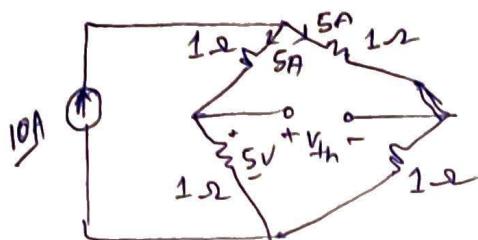


KVL

$$5 - V_{th} - 5 = 0$$

$$\Rightarrow V_{th} = 0 \text{ V}$$

$$R_{th} = 2 \parallel 2 = 1 \Omega$$

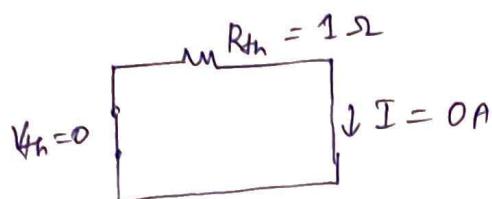

Obs: The open circuit voltage V_{th} and the S.C. current I_{sc} are independent of the load magnitude, since we are opening the load for V_{th} and shorting the load for I_{sc} .

Case - ②



Determine the Thevenin's equivalent and Norton's equivalent across AB.

Ans


$$V_{th} = V_m$$

Nodal

$$\frac{V_m - 4}{2k} = \frac{V_m}{4000} \Rightarrow \frac{V_m - 4}{2000} = \frac{V_m}{4000} \Rightarrow \frac{V_m - 4}{2000} = \frac{V_m}{4000}$$

$$2V_m - 8 = V_m \Rightarrow V_m = 8 \text{ V} = V_{th}$$



$\frac{I_{sc}}{=}$

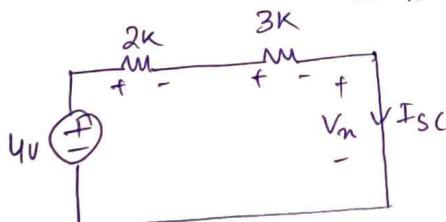

$$V_m = 0$$

$$\begin{aligned} \text{KVL} \quad 4 - 5 \times 10^3 \cdot I_{sc} &= 0 \\ \Rightarrow I_{sc} &= \frac{4}{5} \text{ mA} \end{aligned}$$
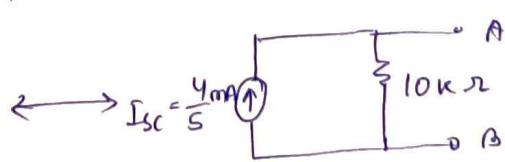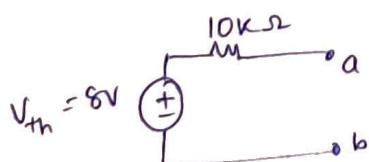
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{\frac{4}{5} \times 10^{-3}} = 10 \text{ k}\Omega$$




7d
1

25A

(17)

case f2 (repeat)


Q11 Determine the Thevenin's equivalent and Norton's equivalent across AB.

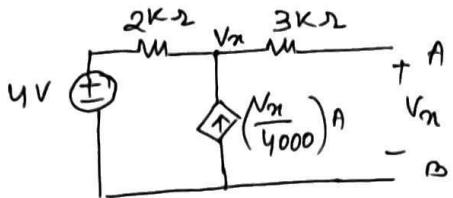Ans

$$V_{th} : V_{th} = V_m$$


NODAL $\frac{V_x - 4}{2k} = \frac{V_x}{4000} \Rightarrow \frac{V_x - 4}{2000} = \frac{V_x}{4000}$

$$\Rightarrow 2V_x - 8 = V_x \Rightarrow V_x = 8V = V_{th}$$


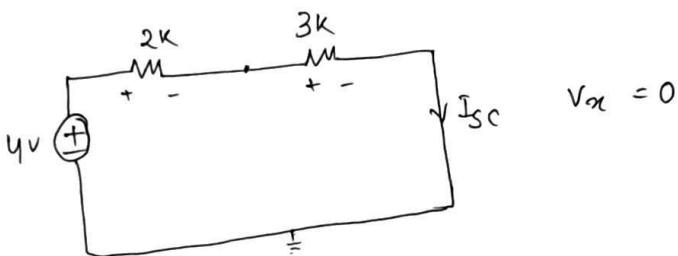
Norton

KVL $4 - 5 \times 10^3 \cdot I_{sc} = 0 \Rightarrow I_{sc} = \frac{4}{5} \text{ mA}$
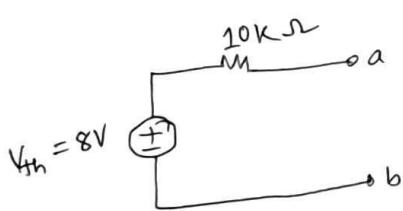
$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{\frac{4}{5} \times 10^{-3}} = 10k\Omega$$



$$\leftrightarrow I_{sc} = \frac{4}{5} \text{ mA}$$

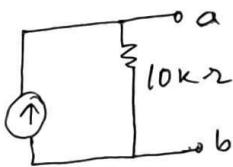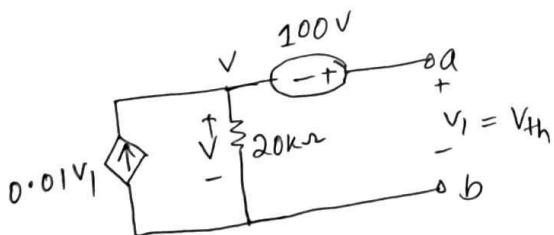
Q11By KVL

$$\therefore V + 100 - V_1 = 0 \\ \Rightarrow V = V_1 - 100$$

$$V_{th} : V_1 = V_{th} \quad \text{Nodal} \quad -0.01V_1 + \frac{V}{20k} + 0 = 0$$

$$\Rightarrow 200V_1 + V = 0 \Rightarrow -200V_1 + V_1 - 100 = 0$$

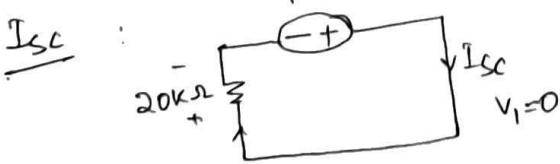
$$\Rightarrow V_1 = -\frac{100}{199} = -502.5 \text{ mV} = V_{th}$$




$$\text{By KVL} \Rightarrow 100 - 20 \times 10^3 \cdot I_{sc} = 0$$

$$\Rightarrow I_{sc} = 5 \text{ mA}$$

$$R_{th} = \left| \frac{V_{th}}{I_{sc}} \right| = 100.5 \Omega$$

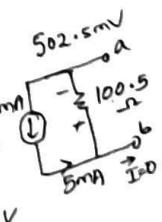

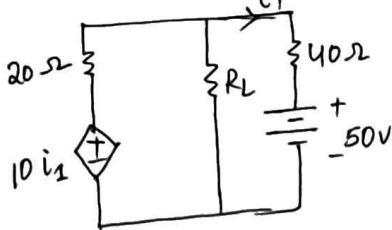All Det Thevenin's & Norton's equivalent across R_L




(A)

$$\begin{aligned} \text{Circuit: } & 20\Omega \text{ in series with } 10i_1 \text{ in parallel with } R_L \text{ in series with } -50V \\ \Rightarrow & \frac{V_{th} - 10i_1}{20} + i_1 = 0 \\ \Rightarrow & V_{th} - 10i_1 + 20i_1 = 0 \\ \Rightarrow & V_{th} + 10i_1 = 0 \\ (\because) & i_1 = \frac{V_{th} - 50}{40} \text{ A} \end{aligned}$$


$$V_{th} + 10 \left(\frac{V_{th} - 50}{40} \right) = 0 \Rightarrow V_{th} = 10V.$$

$$\begin{aligned} I_{SC} : \quad & 20\Omega \text{ in series with } 10i_1 \text{ in parallel with } R_L \text{ in series with } -50V \\ \text{NODAL: } & \frac{0 - 10i_1}{20} + i_{SC} + i_1 = 0 \\ \Rightarrow & i_{SC} = -\frac{i_1}{2} \mid i_1 = \frac{0 - 50}{40} \\ \Rightarrow & i_{SC} = \frac{5}{8}A \end{aligned}$$
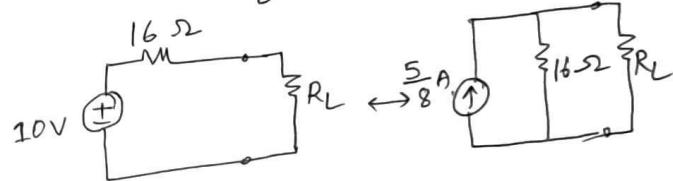
$$R_{th} = \frac{V_{th}}{I_{SC}} = \frac{10}{5/8} = 16\Omega.$$



All

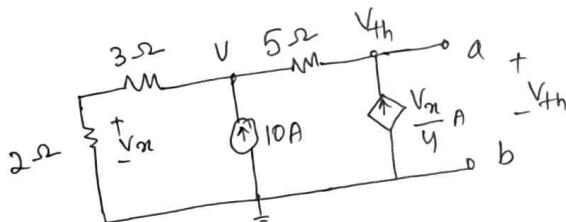

$$\underline{V_{th}:} \quad V_n = V_{2\Omega} = I_{2\Omega} \cdot 2 = \left(\frac{V - 0}{5} \right) 2 = \frac{2}{5}V$$

$$\underline{\text{Nodal:}} \quad \frac{V}{5} - 10 + \frac{V - V_{th}}{5} = 0 \Rightarrow 2V - V_{th} = 50 \quad (1)$$

$$\begin{aligned} \underline{\text{Nodal:}} \quad & \frac{V_{th} - V}{5} - \frac{V_n}{4} = 0 \Rightarrow \frac{V_{th} - V}{5} - \frac{2V}{20} = 0 \quad \left(\because V_n = \frac{2}{5}V \right) \\ & \Rightarrow V = \frac{2}{3}V_{th} \quad (2) \end{aligned}$$

eqn (1) & (2)


$$\begin{aligned} 2V - V_{th} &= 50 \\ 3V - 2V_{th} &= 0 \\ \hline V &= 100V \end{aligned}$$

$$V_{th} = 150V$$

d

5A

(18)

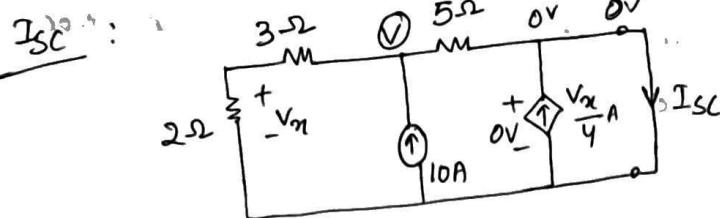

$$\text{Nodal} \rightarrow \frac{V}{5} - 10 + \frac{V-0}{5} = 0$$

$$\Rightarrow V = 25 \text{ V}$$

$$V_x = \frac{2}{5} \times V = 10 \text{ V}$$

Nodal \Rightarrow



$$\frac{0-V}{5} - \frac{V_x}{4} + I_{SC} = 0$$

$$\Rightarrow I_{SC} = \frac{V}{5} + \frac{V_x}{4} = \frac{25}{5} + \frac{10}{4} = \frac{15}{2} \text{ A}$$

$$R_{th} = \frac{V_{th}}{I_{SC}} = \frac{150}{(15/2)} = 20 \Omega$$




Case (III)

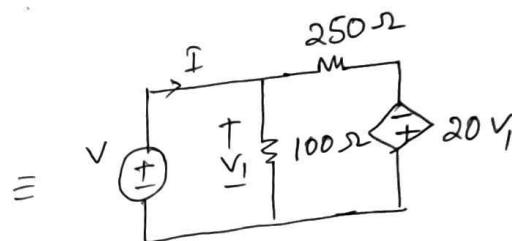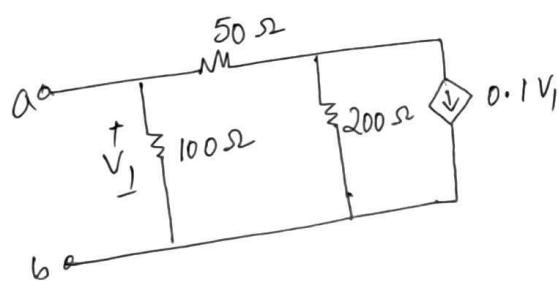

$$V_1 = V \Rightarrow \text{Nodal} \Rightarrow -I + \frac{V}{100} + \frac{V+20V_1}{250} = 0$$

$$\Rightarrow \frac{V}{I} = R_{th} = \frac{1}{\frac{1}{100} + \frac{21}{250}} = 10.6 \Omega$$

$$R_{th} = 10.6 \Omega$$

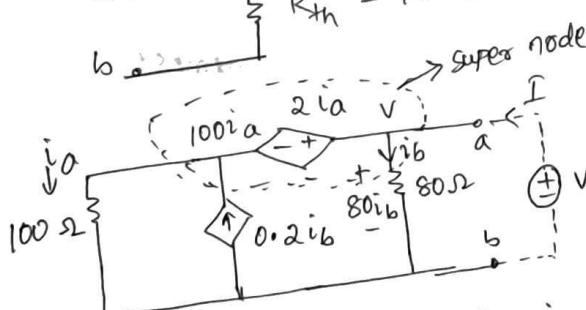

Thevenin's & Norton's eq'

Q11

$$\text{Super node eqn} \Rightarrow i_a - 0.2i_b + i_b - I = 0$$

$$\Rightarrow I = i_a + 0.8i_b \quad ; \quad V = 80i_b \Rightarrow i_b = \frac{V}{80}$$

inside the super node always KVL is written $\Rightarrow 100i_a + 2i_a - V = 0$

$$\Rightarrow i_a = \frac{V}{102}$$

$$50 \cdot 5 \Omega \left[\begin{array}{c} a \\ b \end{array} \right] \quad \text{eqn(1)} \Rightarrow I = \frac{V}{102} + 0.8 \times \frac{V}{80} \Rightarrow \frac{V}{I} = R_{th} = \frac{1}{\frac{1}{102} + \frac{1}{80}} = 50.5 \Omega$$


MPT

Same as SPT

→ This thm is applicable only when the load is a variable, otherwise choose the minimum internal impedance of the source, which results a maximum current through the fixed load and hence a maximum power is appeared across the load.

Under the variable load condn -

① R_s and R_L -

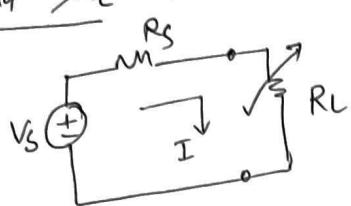

$$I = \frac{V_s}{R_s + R_L}$$

$$P = I^2 R_L = \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2} \text{ watt}$$

$$\frac{dP}{dR_L} = \frac{V_s^2 \left[(R_s + R_L)^2 \cdot 1 - R_L \cdot 2(R_s + R_L) \right]}{(R_s + R_L)^4}$$

$$\text{for MPT } \frac{dP}{dR_L} = 0 \Rightarrow R_L = R_s$$

$$P_{\max} = P \Big|_{R_L = R_s} = \frac{V_s^2}{4R_s} \text{ watt}$$

$$P_{\text{del}} = P_{\text{abs}}$$

$$P_T = I^2 R_s + I \cdot R_L \Big|_{R_L = R_s}$$

$$= \frac{V_s^2}{2R_s} \text{ watt}$$

$$\eta \text{ (efficiency)} = \frac{\text{useful power}}{\text{Total power}} = \frac{\frac{V_s^2}{4R_s}}{\frac{V_s^2}{2R_s}} = \frac{1}{2} = 0.5.$$

$$\therefore \eta = 50\%.$$

→ So, the efficiency of the max power transform thm is atmost 50%.

② Z_s and Z_L →

$Z_s = (R_s + jX_s)^{-2}$
 $Z_L = (R_L + jX_L)^{-2}$

$I = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$
 $\Rightarrow P = |I|^2 R_L \text{ watt}$
 $= \frac{V_s^2 \cdot R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \text{ watt}$

(19)

2(i) : only R_L is a variable.

$$\frac{dP}{dR_L} = \frac{V_S^2 \left[(R_S + R_L)^2 + (x_S + x_L)^2 \cdot 1 - R_L \cdot 2(R_S + R_L) \right]}{()^2}$$

For MPT ; $\frac{dP}{dR_L} = 0 \Rightarrow R_L = \sqrt{R_S^2 + (x_S + x_L)^2} - \underline{\underline{2}}$

$$P_{\max} = P|_{R_L} = \sqrt{R_S^2 + (x_S + x_L)^2}$$

$$\therefore n < 50\%$$

2(ii) only x_L is a variable

$$\frac{dP}{dx_L} = \frac{V_S^2 \left[(R_S + R_L)^2 + (x_S + x_L)^2 \cdot 0 - R_L \cdot 2(x_S + x_L) \right]}{()^2}$$

For MPT $\frac{dP}{dx_L} = 0 \Rightarrow x_S + x_L = 0$

$$P_{\max} = \bigcirc P|_{x_S + x_L = 0}$$

$$\therefore n < 50\%$$

2(iii) Both R_L and x_L are varied simultaneouslyIn this case both the condⁿ

$$R_L = \sqrt{R_S^2 + (x_S + x_L)^2} \quad \& \quad x_S + x_L = 0 \quad \text{are valid}$$

$$\begin{array}{l} R_L = R_S \\ x_L = -x_S \end{array} \quad \left. \begin{array}{l} \text{so, } z_L = R_L + j x_L \\ \quad \quad \quad = R_S - j x_S \end{array} \right.$$

$$\boxed{z_L = z_S^*} \quad \underline{\underline{2}}$$

$$P_{\max} = P|_{\substack{R_L = R_S \\ x_L = -x_S}} = \frac{V_S^2}{4R_L} \quad \boxed{\therefore n = 50\%}$$




(3) z_S and R_L :- get is a special case of 2(i) with $x_L = 0$

$$\text{so, for MPT} \Rightarrow R_L = \sqrt{R_S^2 + (x_S + x_L)^2} \Big|_{x_L=0}$$

$$R_L = \sqrt{R_S^2 + x_S^2} \quad \underline{\underline{2}} \quad R_L = |R_S + j x_S| \quad \underline{\underline{2}} = |z_S| \quad \underline{\underline{2}}$$

$$P_{\max} = P|_{R_L = |z_S|} \quad \boxed{\therefore n < 50\%}$$

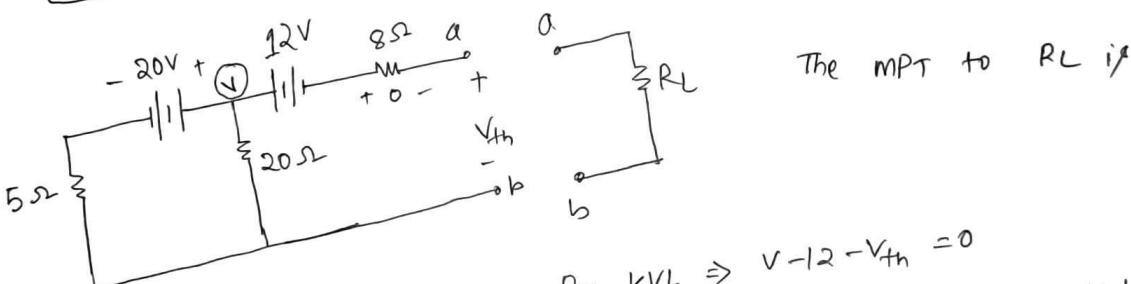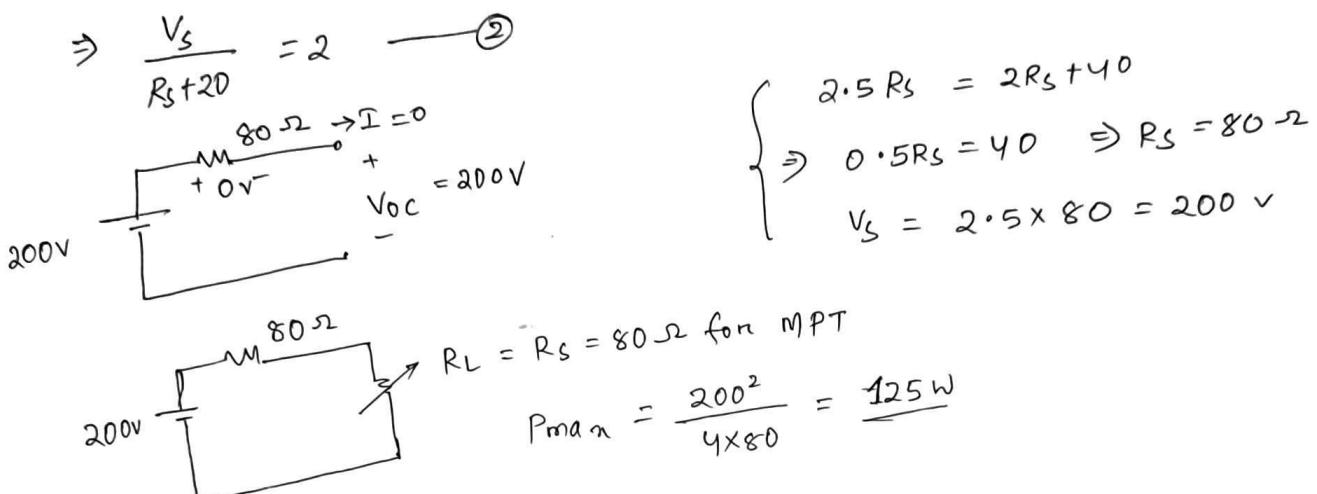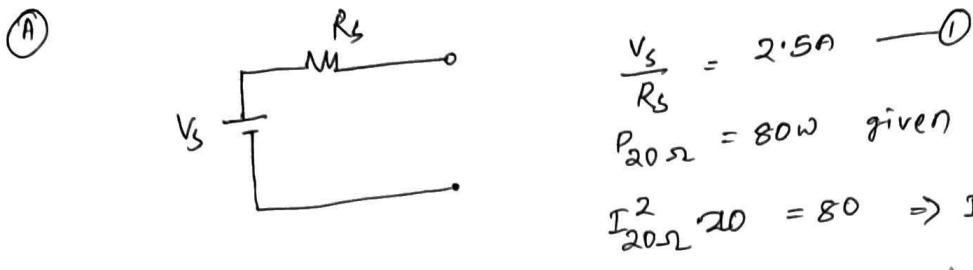~~Q1~~ A practical d.c. source when it is short circuited, then supplies a current of 2.5 Amps and it can provide a power of 80 watts to a 20Ω load. Determine the open circuit voltage and the value of R_L for MPT.






$$\text{By KVL} \Rightarrow V - 12 - V_{th} = 0$$

$$\Rightarrow V = V_{th} + 12 \Rightarrow V_{th} = V - 12$$


NODAL
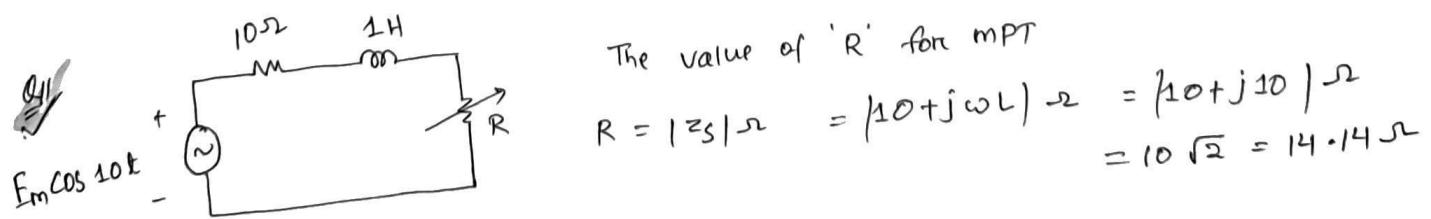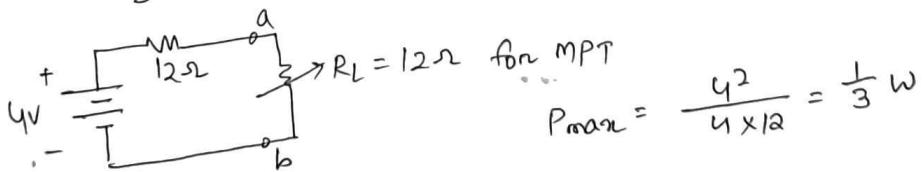
$$\frac{V-20}{5} + \frac{V}{20} + 0 = 0 \Rightarrow V = 16 \text{ V} \Rightarrow V_{th} = 4 \text{ V}$$



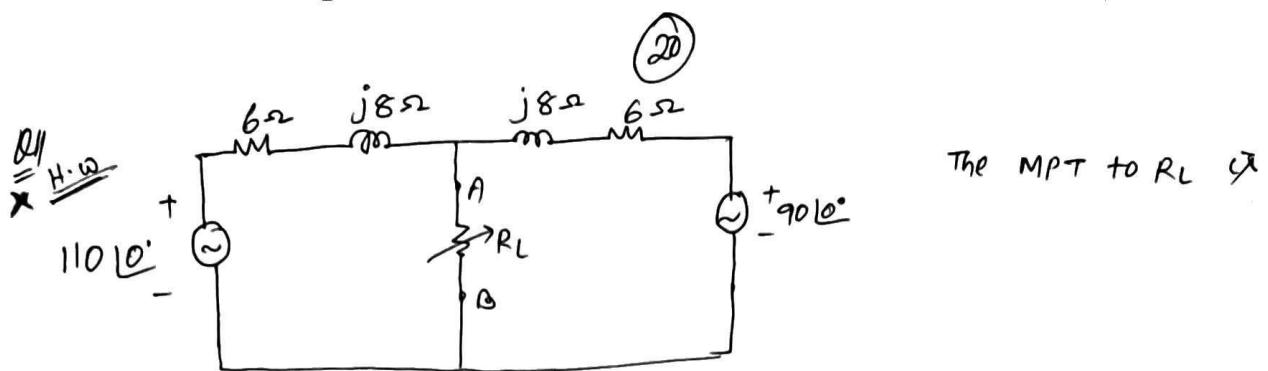


The MPT to R_L is

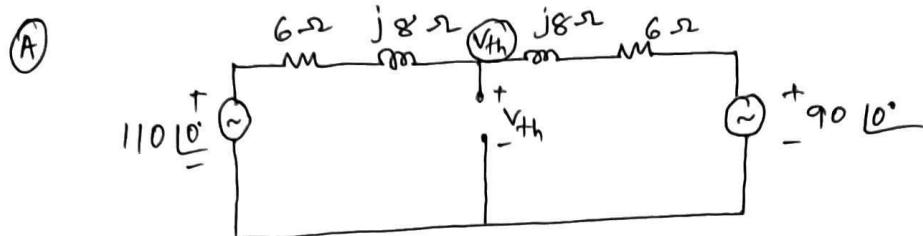

$$\text{NODAL} \Rightarrow \frac{V_{th} - 110\angle 10^\circ}{6 + j8} + \frac{V_{th} - 90\angle 10^\circ}{6 + j8} = 0$$


$$\Rightarrow 2V_{th} = 200\angle 10^\circ \Rightarrow V_{th} = 100\angle 10^\circ$$
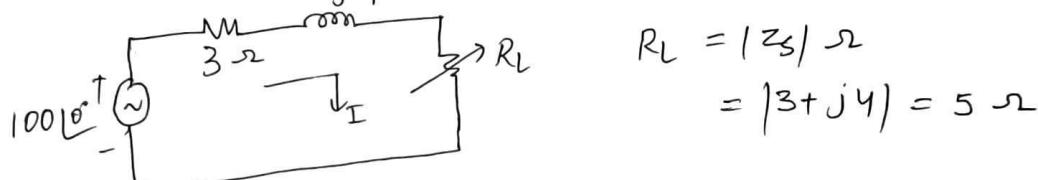
$$Z_{th} = (6 + j8) \parallel (6 + j8) = Z_{112} = \frac{Z}{2} = (3 + j4)\Omega$$



$$R_L = |Z_S| \Omega \\ = |3 + j4| = 5 \Omega$$

$$I = \frac{100\angle 10^\circ}{3 + j4 + 5}; P_{max} = |I|^2 \cdot 5 = 625 \text{ W.}$$

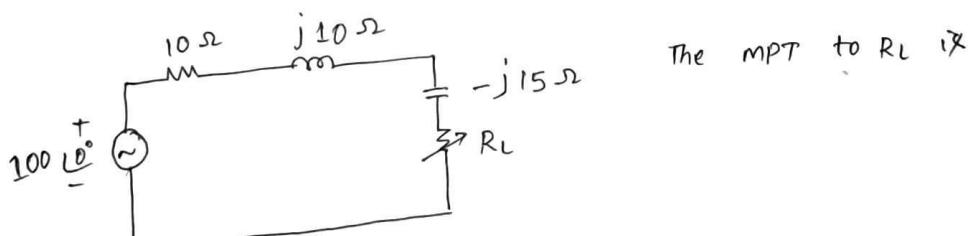


(A)

$$Z_L = R_L - j15 = R_L + j(-15) \\ = R_L + j X_L \quad \text{where } X_L = -15$$

$$\text{so, for MPT} \quad R_L = \sqrt{R_S^2 + (X_S + X_L)^2} = \sqrt{10 + (10 - 15)^2} = 5\sqrt{5} \Omega$$

$$I = \frac{100\angle 10^\circ}{10 + j10 - j15 + 5\sqrt{5}}; P_{max} = |I|^2 \cdot 5\sqrt{5} = 236 \text{ W.}$$

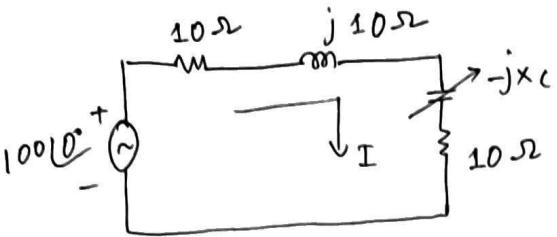


$$\begin{aligned} z_L &= 10 - jX_L \\ &= 10 + j(-X_C) \\ &= R_L + jX_L \quad \text{where } X_L = -X_C. \end{aligned}$$

$$I = \frac{100 \angle 0^\circ}{10 + j10 - j10 + 10} = 5 \angle 0^\circ A$$

$$P_{\max} = |I|^2 \cdot R_L = 5^2 \times 10 = 250 \text{ W.}$$
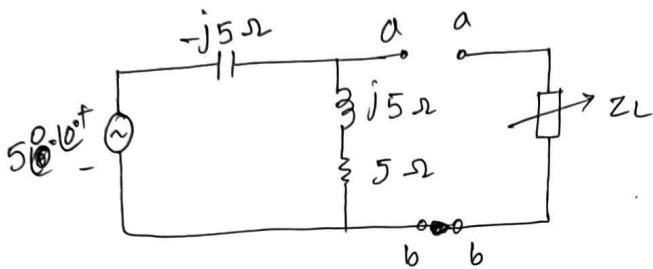
$$\left\{ \begin{array}{l} \text{For MPT} \\ X_S + X_L = 0 \\ \Rightarrow 10 - X_C = 0 \\ \Rightarrow X_C = 10 \end{array} \right.$$



The maximum true power delivered to Z_L


$$V_{th} = \left(\frac{50 \angle 0^\circ}{-j5 + j5 + 5} \right) \cdot (j5 + 5) = 10 \angle 0^\circ \cdot 5\sqrt{2} \angle 45^\circ$$

$$= 50\sqrt{2} \angle 45^\circ$$

$$Z_{th} = (-j5) \parallel (j5 + 5)$$


$$= (5 - j5) \Omega$$

$$Z_{th} = (5 - j5) \Omega$$

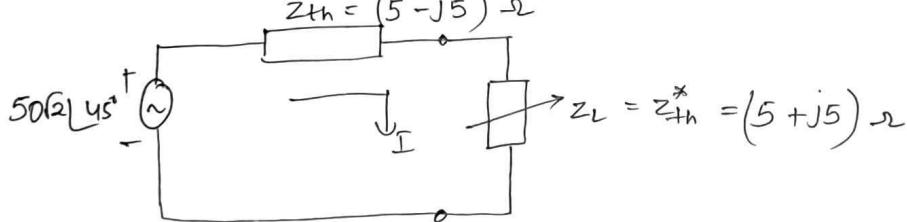

$$I = \frac{50\sqrt{2} \angle 45^\circ}{5 - j5 + 5 + j5} = 5\sqrt{2} \angle 45^\circ$$

$$P_{\max} = |I|^2 R_L = (5\sqrt{2})^2 \cdot 5 = 250 \text{ W.}$$

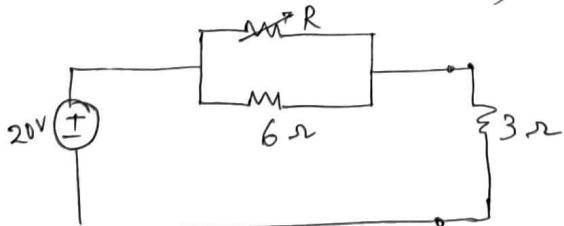

- (a) 3Ω (b) 6Ω (c) 9Ω (d) 12Ω

The value of 'R' for MPT. to the 3Ω resistor is


$$P_{3\Omega} = I_{3\Omega}^2 \cdot 3 \text{ W} \quad \Rightarrow \quad I_{3\Omega} = \left(\frac{20}{R_{eq} + 3} \right) \text{ A} ; \quad R_{eq} = 6 \parallel R$$

$$R = 3\Omega \Rightarrow R_{eq} = 6 \parallel 3 = 2\Omega$$

$$I_{3\Omega \max} = \frac{20}{2+3} = 4 \text{ A} ; \quad P_{3\Omega \max} = 4^2 \times 3 = 48 \text{ W.}$$


(21)

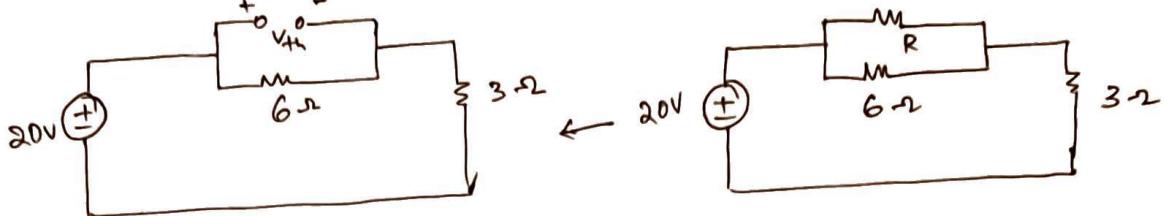Q11) In the above problem, the maximum power delivered to R' is



$$V_{Th} = \left(\frac{20}{6+3} \right) \cdot 6 = \frac{40}{3} \text{ V}$$


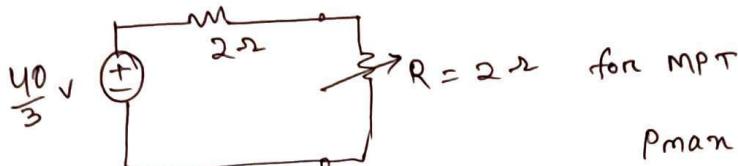
$$R_{Th} = 6 \parallel 3 = 2 \text{ ohm}$$



$$P_{max} = \frac{\left(\frac{40}{3}\right)^2}{4 \times 2} \text{ W.}$$

The Reciprocity Thm.

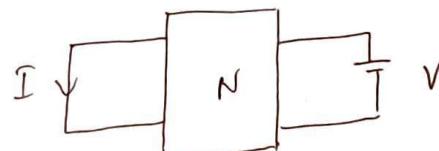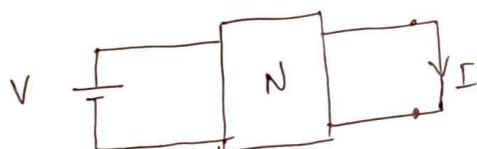
⇒ In a linear, passive and bilateral network, the ratio of response to excitation is constant even though the source is interchange from the O/P terminals to the O/P terminals.



$$\text{i.e. } \frac{I}{V} = \text{constant} \Rightarrow \boxed{\frac{I_1}{V_1} = \frac{I_2}{V_2}}$$


⇒ Not applicable to dependent sources.

Proof

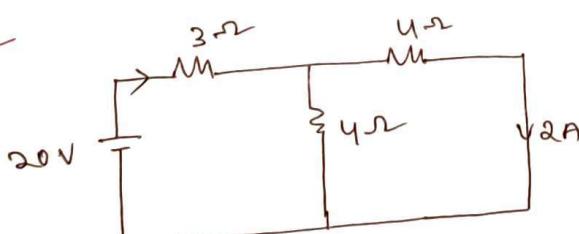


$$R_{eq} = 4 + (4 \parallel 3) = \frac{40}{7} \text{ ohm}$$
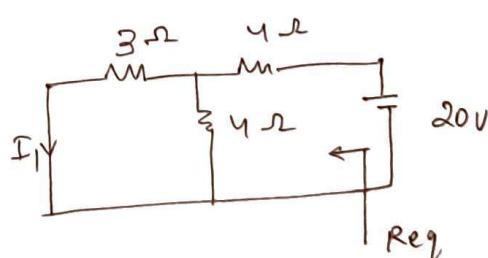
$$I = \frac{20}{40/7} = \frac{7}{2} \text{ A}$$



$$I_1 = \frac{\frac{7}{2} \cdot 4}{3+4} = 2 \text{ A}$$


Q11

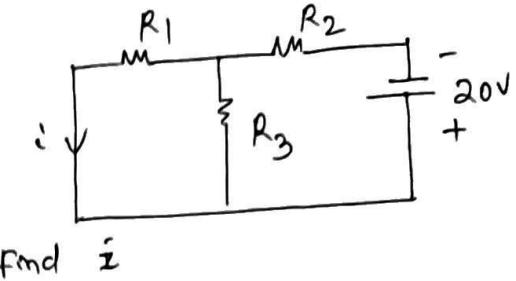

$$\frac{I_1}{V_1} = \frac{I_2}{V_2} \Rightarrow \frac{2}{10} = \frac{I}{-20} \Rightarrow I = -4A.$$




-.-

MPT using dependent source:

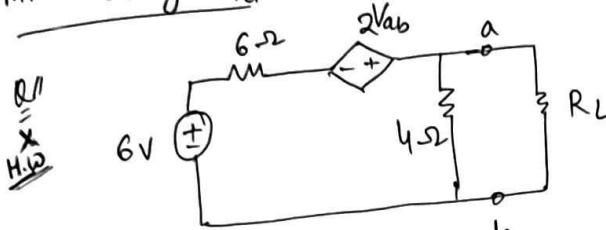

Find the load R_L that will result in MPT & determine P_{max} .

Theremin eqn.

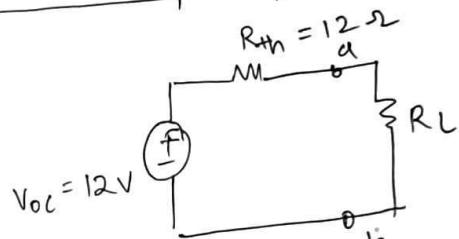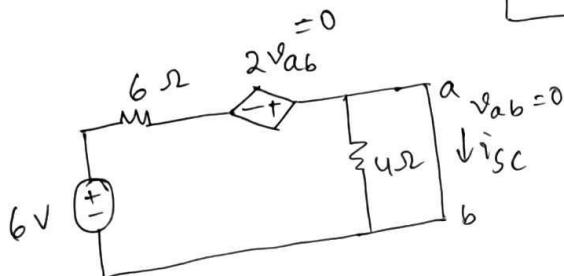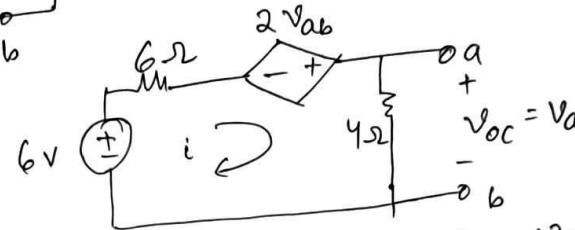

$$V_{th} \quad -6 + 10i_1 - 2V_{ab} = 0$$

$$\Rightarrow 10i - 8i = 6$$

$$V_{ab} = V_{oc} = 4i$$

$$i = 3A \quad ; \quad V_{oc} = 4i = 12V$$

$$I_{sc} \quad -6 + 6i_{sc} = 0 \Rightarrow i_{sc} = 1A$$

$$R_{th} = \frac{V_{oc}}{i_{sc}} = 12\Omega$$

MPT

$$R_L = R_{th} = 12\Omega$$

$$P_{max} = \frac{V_{oc}^2}{4R_L} = \frac{12^2}{4 \times 12} = \underline{\underline{3W}}$$

Q12

1A

(22)

Q11

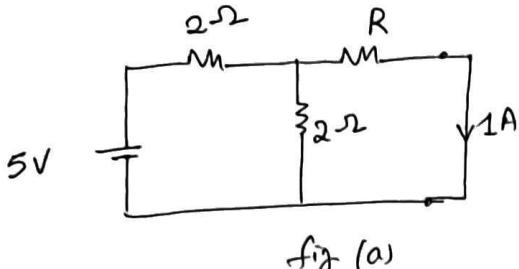


fig (a)

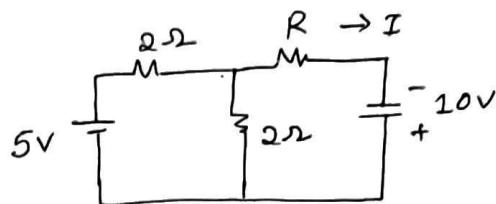


fig (b)


use the data given in fig (a)

~~Ans~~


By SPT to fig (b) \Rightarrow

\rightarrow The current due to 5V source alone $\Rightarrow I_1 = 1 \text{ Amp}$

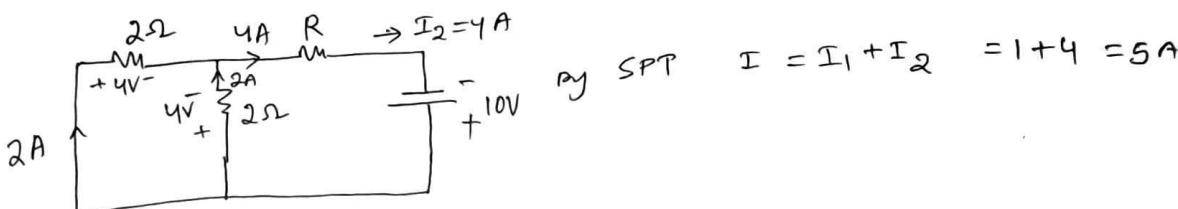
\rightarrow By homogeneity and reciprocity principle to fig (a),
also by reversing the source polarities



Q11

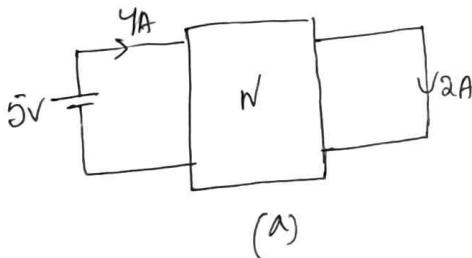

(a)

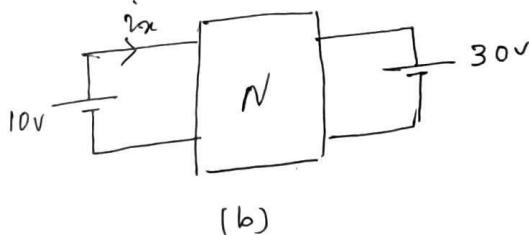

(b)

Network 'N' contains only resistors, use the data given in fig (a)


Find the current i_m in fig (b)

Ans

By SPT to fig (b) \Rightarrow The current due to 10V source alone

$$= i_{m1} = 2 \times 4 = 8 \text{ Amperes}$$

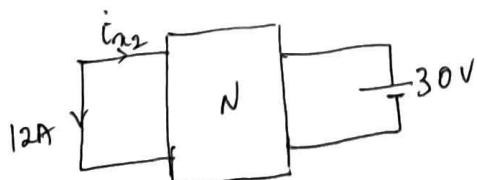
By homogeneity & reciprocity principle to fig (a)




$$i_{m2} = -12A$$

By SPT $\Rightarrow i_m = i_{m1} + i_{m2} = 8 - 12 = -4A$

Q11
H.W

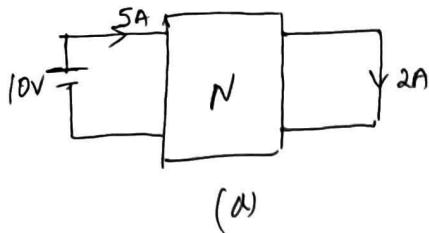


(a)

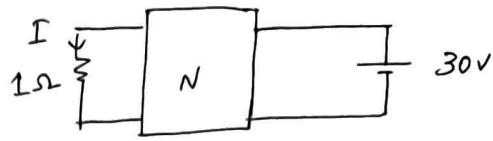

(b)


N/W 'N' contains only resistances, use the data given in fig.(a) find the current 'I' in fig.(b)

(A)

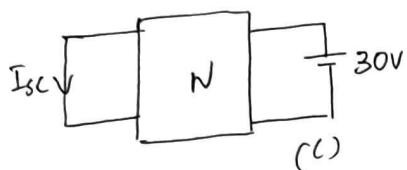

By homogeneity & reciprocity principles to

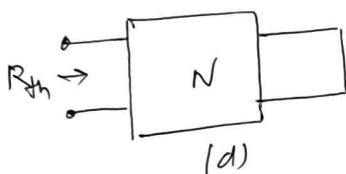
$$\text{fig (a)} \quad I_{SC} = 6 \text{ AMP}$$



$$\equiv \frac{1}{R_{th}}$$

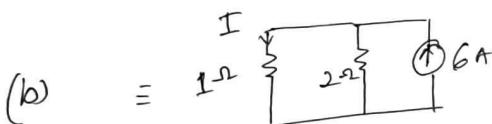
(a) → energized version of (d)

$$10V \quad \frac{5A}{R_{th}} \quad R_{th} = \frac{10}{5} = 2\Omega$$



$$I = \frac{6 \times 2}{2+1} = 4 \text{ A}$$

Q11 H.W


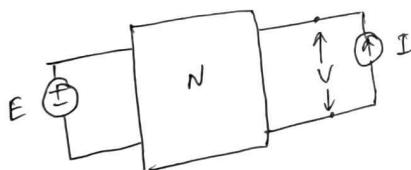


The 'N' contains only resistances.


$$\begin{aligned} E &= 1V && \text{& } 0V \\ I &= 0A && \text{& } 2A \\ V &= 3V && \text{& } 2V \end{aligned} \quad \text{respectively}$$

If $E = 10V$ and I is replaced by $R = 2\Omega$ then $V = ?$


(A)

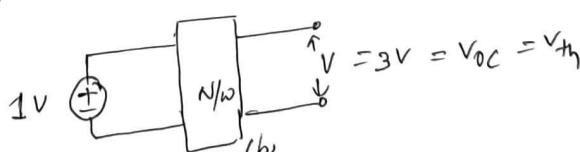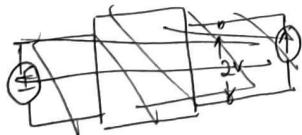

$$R_{th} = \frac{2V}{2A} = 1\Omega$$

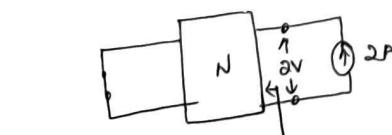

$$\equiv \frac{2A}{2V} R_{th} \quad 2A$$

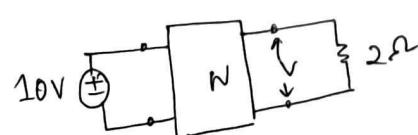

$$\equiv 30V \quad 2\Omega$$


By homogeneity to (b)

$$\begin{aligned} 1V &\rightarrow 3V \\ 10V &\rightarrow 30V \end{aligned}$$

$$\begin{aligned} V &= \frac{30}{3} \times 2 \\ &= 20V \end{aligned}$$

(23)

The Millman's thm :-

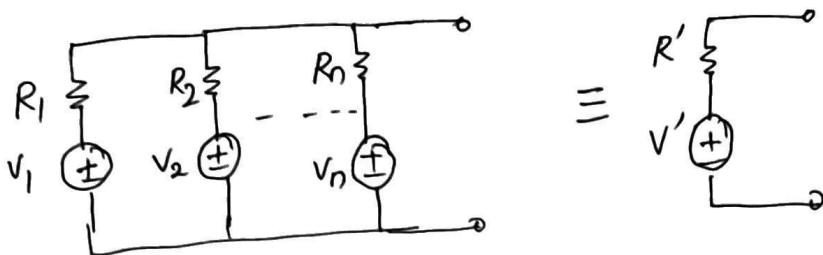


$$V' = \frac{V_1 G_1 + V_2 G_2 + V_3 G_3 + \dots + V_n G_n}{G_1 + G_2 + G_3 + \dots + G_n}$$

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

$$G' = G_1 + G_2 + G_3 + \dots + G_n$$

$$R' = \frac{1}{G'} = \frac{1}{G_1 + G_2 + \dots + G_n}$$

→ In the above case of the polarity of the source V_2 are reversed then V_2 is replaced by $-V_2$ in the expression of V'

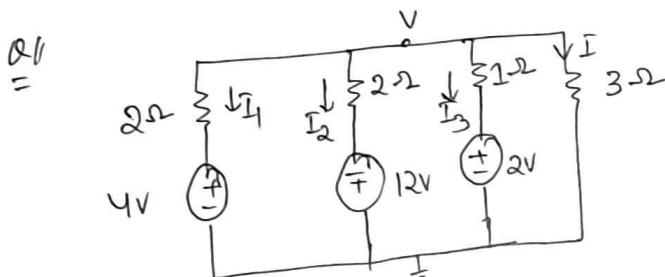

det I.

$$V' = \frac{4 \cdot \frac{1}{2} - 12 \cdot \frac{1}{2} + 2 \cdot \frac{1}{1}}{\frac{1}{2} + \frac{1}{2} + \frac{1}{1}} = -1V$$

$$R' = \frac{1}{\frac{1}{2} + \frac{1}{2} + 1} = \frac{1}{2}\Omega$$

$$I = \frac{V'}{R' + 3} = \frac{-1}{\frac{1}{2} + 3} = -\frac{2}{7}A$$

Another method NODAL $\Rightarrow \frac{V-4}{2} + \frac{V+12}{2} + \frac{V-2}{1} + \frac{V}{3} = 0$


$$\Rightarrow V = -\frac{6}{7}V$$

$$I = \frac{V}{3} = -\frac{2}{7}A$$

$$I_1 = \left(\frac{V-4}{2} \right) A, \quad I_2 = \left(\frac{V+12}{2} \right) A, \quad I_3 = \left(\frac{V-2}{1} \right) A$$

$$= -\frac{17}{7}, \quad = \frac{39}{7}, \quad = -\frac{20}{7}$$

VTT

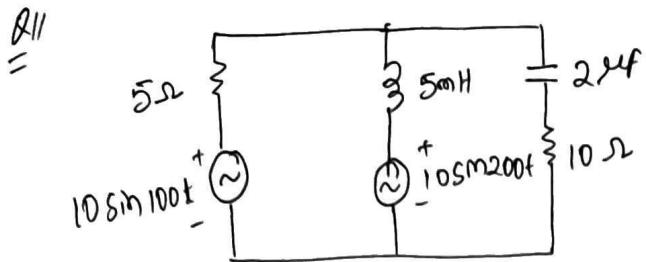


Which one of the following thm can be conveniently used to evaluate the response on the 10Ω resistor.

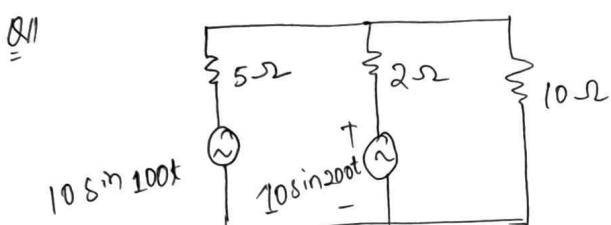- (a) Thévenin thm (b) MPTT (c) Millman's thm (d) SPT.

Note: Since, two different freq. are operating on the L/C simultaneously, always the SPT is used to evaluate the response, since the reactive elements are freq. sensitive. $Z_L = j\omega L \text{ and } Z_C = \frac{1}{j\omega C}$.

- ② In the above problem, both the sources are 100 radian/sec, then Millman's thm is more conveniently used.



$$V' = \frac{10 \sin 100t \cdot \frac{1}{5} + 10 \sin 200t \cdot \frac{1}{2}}{\frac{1}{5} + \frac{1}{2}}$$

$$R' = \frac{1}{\frac{1}{5} + \frac{1}{2}} \Omega$$


$$I_{10\Omega} = \left(\frac{V'}{R'+10} \right) A$$

→ So, here no reactive components then Millman's thm is best suited.

-o-

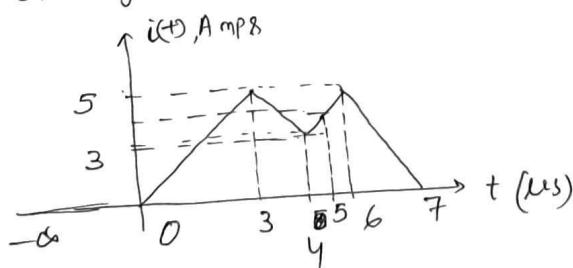Problems on the Power and Energy:

- QII Figure shows the current flowing through a capacitor. Determine the charge acquired by the capacitor upto first $5\mu s$



Ans $i(t) = \frac{d\phi(t)}{dt} \text{ Amps} \Rightarrow d\phi(t) = i(t) dt \Rightarrow q = \int_{-\infty}^t i(t) dt$

Slope = $\frac{5-3}{6-4} = 1$

$q_1 = q_1|_{0-3\mu s} + q_2|_{3-4\mu s} + q_3|_{4-5\mu s} = \frac{1}{2}(\frac{1}{2} \times 3 \times 5) + (\frac{1}{2} \times 1 \times 2) + (1 \times 3)$

$+ (\frac{1}{2} \times 1 \times 1) + (1 \times 3) = 15 \text{ coulombs}$

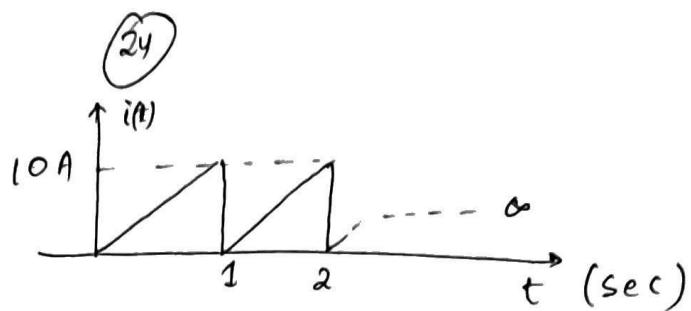
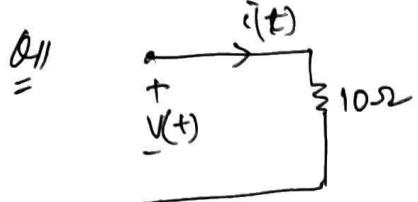


Fig. shows the current flowing through a 10Ω resistor. Determine the average power dissipated by the resistor.

Soln The given signal is a periodic signal of period 1 sec. Let's assume 1 period.

$$\text{Slope} = \frac{10-0}{1-0} = 10$$

$$y = mx \Rightarrow i = 10t \text{ A for } 0 \leq t \leq 1 \text{ sec.}$$

$$\begin{aligned} \text{The instantaneous Power} \Rightarrow P(t) &= i^2(t) R = (10t)^2 \cdot 10 \\ &= 1000t^2 \text{ W for } 0 \leq t \leq 1 \text{ sec.} \end{aligned}$$

$$P(0) = 0 \text{ W} \Rightarrow P_{\min}$$

$$P(1) = 1000 \text{ W} \Rightarrow P_{\max}$$


- Betw 0 & 1, the inst. Power continuously varied in a non-linear fashion and hence is of no meaning, so, the unique average power

The energy absorbed over one period

$$P_{\text{avg}} =$$


$$= \frac{\frac{1}{2} \int_0^1 i^2 R dt}{1 \text{ sec}} = \frac{\frac{1}{2} \int_0^1 (10t)^2 \cdot 10 dt}{1 \text{ sec}}$$
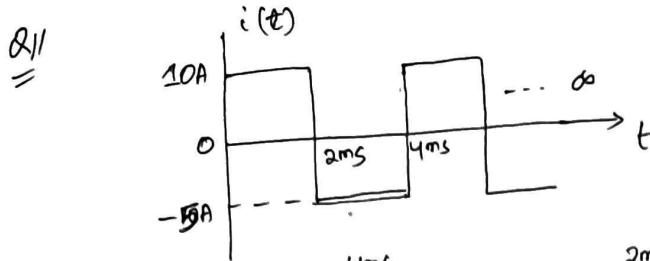
$$= \frac{\frac{1000}{3} \text{ J}}{1 \text{ sec}} = \frac{1000}{3} \text{ watt.}$$



$$P_{avg} = \frac{\int_0^{4ms} i^2 \cdot R dt}{4ms} = \frac{\int_0^{2ms} 10^2 \cdot 10 \cdot dt + \int_{2ms}^{4ms} (-5)^2 \cdot 10 \cdot dt}{4ms}$$

$$= 625W$$

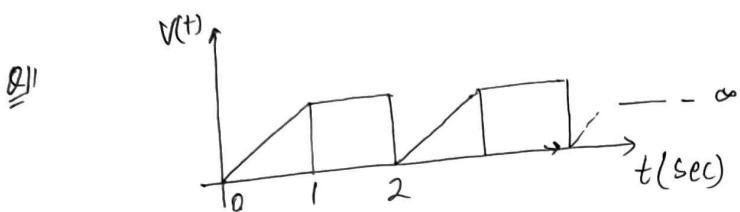

$$\text{Slope} = \frac{1-0}{1-0} = 1$$

$$V(t) = \begin{cases} 1 \cdot t & \text{for } 0 \leq t \leq 1\text{ sec} \\ 1 & \text{for } 1 \leq t \leq 2\text{ sec} \end{cases}$$

$$P_{avg} = \frac{\int_0^{2\text{ sec}} \frac{V^2}{R} \cdot dt}{2\text{ sec}} = \frac{\int_0^1 \frac{t^2}{10} dt + \int_1^2 \frac{1^2}{10} \cdot dt}{2} = \frac{1}{15} \text{ watt.}$$

Note: For any general period 'T' .

(i) In case of a current wave form

$$P_{avg} = \frac{\int_0^T i^2 R dt}{T} = \frac{1}{T} \int_0^T i^2 \cdot dt \cdot R.$$

$P_{avg} = I_{rms}^2 \cdot R$

(ii) In case of a voltage wave form

$$P_{avg} = \frac{\int_0^T \frac{v^2}{R} \cdot dt}{T} = \frac{1}{T} \int_0^T V^2 \cdot dt \cdot \frac{1}{R} \Rightarrow \boxed{P_{avg.} = \frac{V_{rms}^2}{R.}}$$

(25)


Network graph Theory

- N/W may contain passive as well as active elements.
 - An element is connected between two terminals : branch
 - node : position at which two or more than two branches are connected together
 - loop : Any single closed path of a N/W
- NOTE : R, L, C (elements) are replaced by lines.


Voltage Source : with S.C or internal impedance

Current Source : " O.C

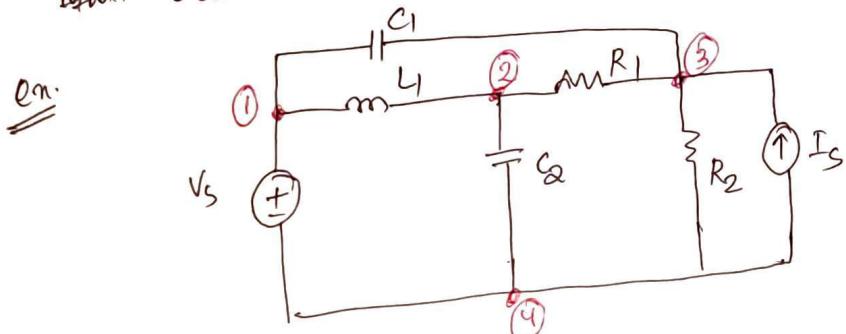- A graphical representation of electrical circuits, it is used to analyze complex networks electric Ckt's into N/W graphs



N/W graphs of the Ckt.

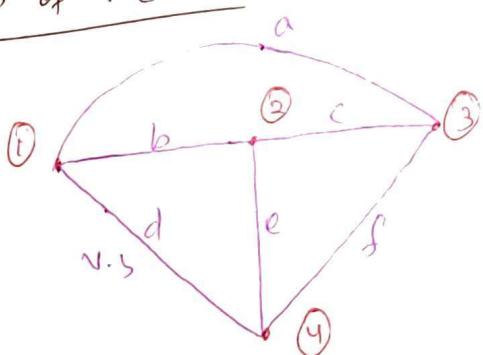

Nodes & branched
passive elements
(R, L, C)

voltage - S.C.
current - O.C.

→ Line segments left of elements or V.S.
will be branched


Types :

- connected & unconnected
- Directed & undirected

Eg

unconnected graph

①.

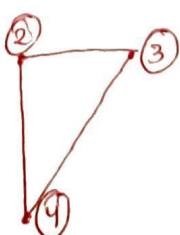


- not a single branch or connected to node '1'
- node ① becomes an isolated node.

Connected.


→ at least one branch is connected to a node

or no node should be left isolated.

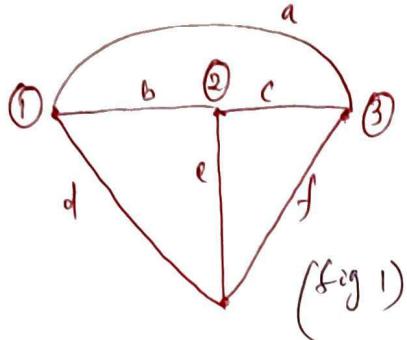

Directed / Oriented

The branches are connected with arrows.

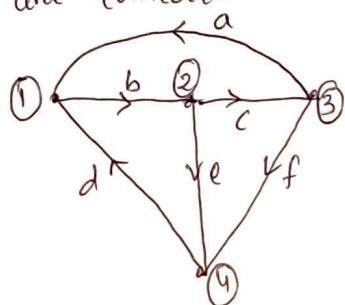


undirected/ un oriented

: No arrows (fig 1)

Sub graphs : By removing some nodes or branches in a given graph,

subset of that graph.


no. of branches are less

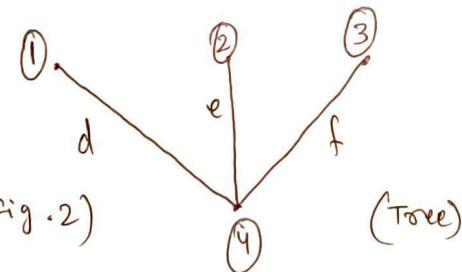

Tree
CO-Tree

connected subgraph :

{ no loop
{ no nodes are left.

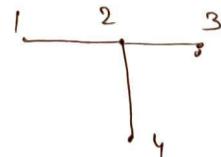


complement of tree.

→ branches of tree : twigs. eg. Fig. 2 (d, e, f)



→ remaining branches : a, b, c links/chords

(26)

eg.

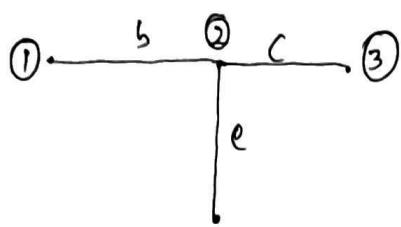

Tree - b, c, e twigs.

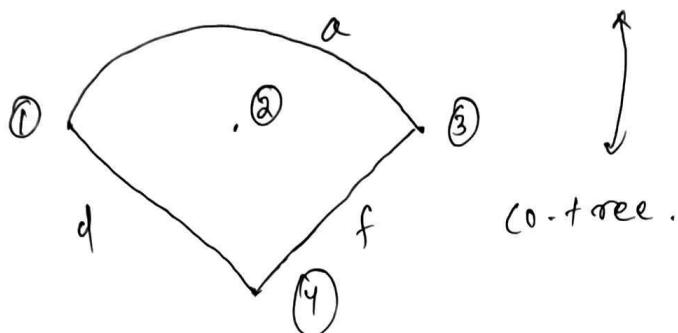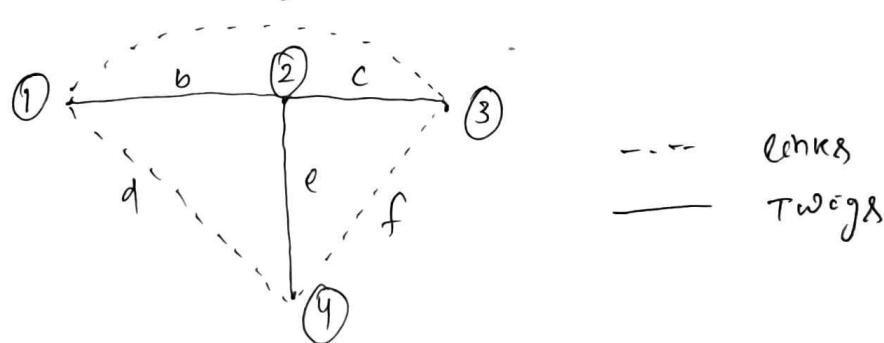Links & twigs \rightarrow combine \rightarrow branches of the graph,

Links + twigs = no. of branches.

$$L + T = B \quad \text{--- (1)}$$

$$T = N-1 \quad \text{--- (2)}$$


\downarrow
Nodes in a graph

$$L + N-1 = B \quad \Rightarrow \boxed{L = B-N+1}$$

Incidence matrix -

- This matrix provides the information about the incidence of branches at different nodes.
- Incidence matrix : each row of the matrix \rightarrow corresponding node of the graph
each column represents \rightarrow branch of the graph.
- If the graph has 'n' nodes and 'b' branches, the order of the matrix is ' $n \times b$ '. The elements a_{ij} of the matrix are identified as:

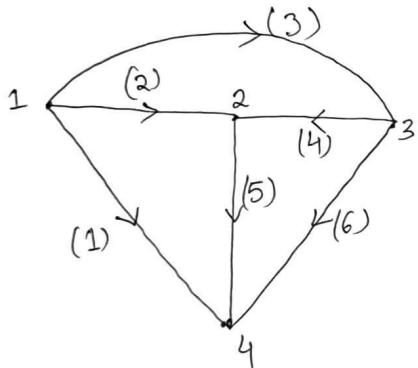 - $a_{ij} = 1$; if the branch 'j' is incident at node 'i' and is oriented away from the node 'i'.
 - $a_{ij} = -1$, if the branch 'j' is incident at node 'i' and is directed towards the node 'i'.
 - $a_{ij} = 0$, if the branch 'j' is not incident at node 'i'.



The incident matrix

Nodes	Branches					
	1	2	3	4	5	6
1	1	1	1	0	0	0
2	0	-1	0	-1	1	0
3	0	0	-1	1	0	1
4	-1	0	0	0	-1	-1

- The matrix A_i is of the order 4×6 and satisfies the following
 - The algebraic sum of any column of A_i is 'zero'
 - The determinant of A_i of a closed loop is 'zero'


Note : If any row is removed from the incidence matrix A_i , the remaining matrix is known as a reduced incidence matrix ' A' .
The order of the reduced matrix ' A' is $(n-1) \times b$ i.e. it has $(n-1)$ rows and 'b' columns. The row corresponding to the reference node is deleted.

(27)

Q. node '4' is called the reference node. the reduced incidence matrix 'A' is given by.

$$\begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \left[\begin{matrix} 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 & 0 & 1 \end{matrix} \right] \end{matrix}$$


eg connected Subgraph / Tree

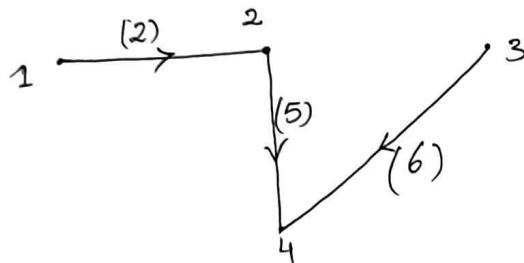

→ First the element of matrix 'A' for twigs and then the remaining for links.

	Twigs			Links		
Nodes	2	5	6	1	3	4
1	1	0	0	1	1	0
2	-1	1	0	0	0	-1
3	0	0	1	0	-1	-1

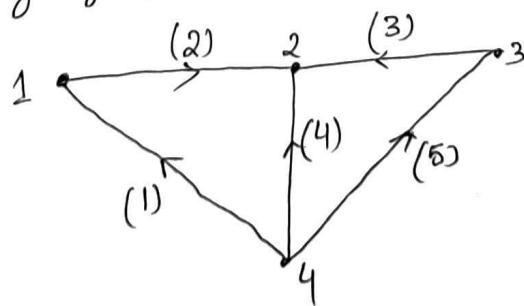
Question
For the following graph, find the incidence matrix



$$A_i = \begin{matrix} & \text{Branches} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \left[\begin{matrix} 1 & 2 & 3 & 4 & 5 \\ -1 & 1 & 0 & 0 & 0 \\ 0 & -1 & -1 & -1 & 0 \\ 0 & 0 & 1 & 0 & -1 \\ 1 & 0 & 0 & 1 & 1 \end{matrix} \right] \end{matrix}$$

Loop matrix :

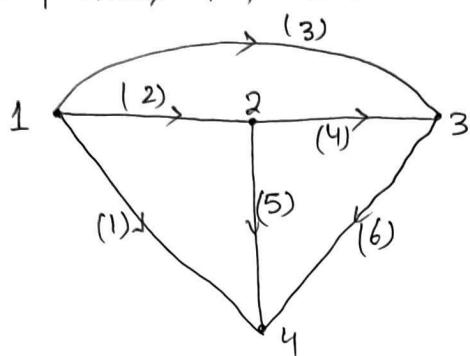- From the incidence matrix we get the idea regarding the number of nodes and branches as well as their connection and orientation of the branches to the respective nodes.
- However, it can't provide any idea regarding the interconnection of branches which form loops.
- The loop matrix provides this idea



If a graph has 'n' nodes and 'b' branches, the loop matrix will have 'b' columns and the number of rows will be the number of possible loops.









$b_{ij} \Rightarrow$ the elements b_{ij} of the loop matrix will satisfy the following conventions

- $b_{ij} = 1$, if branch 'j' is in loop 'i' and their directions coincide
- $= -1$, if branch 'j' is in loop 'i' and their directions don't coincide
- $= 0$, if branch 'j' is not in loop 'i'.

Seven possible loops :

$B =$	Loops	Branches						
		1	2	3	4	5	6	7
	1							
	2							
	3							
	4							
	5							
	6							
	7							

(28) All possible loops

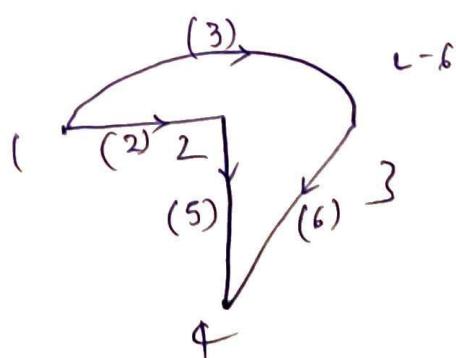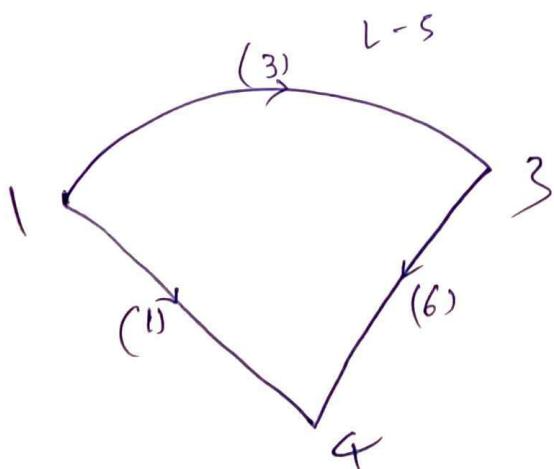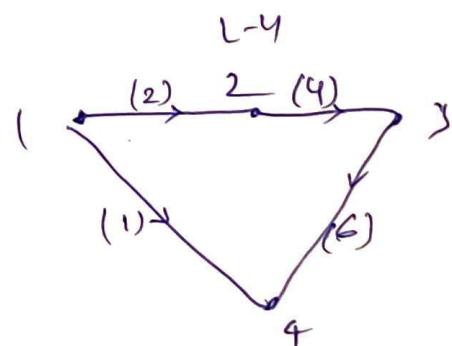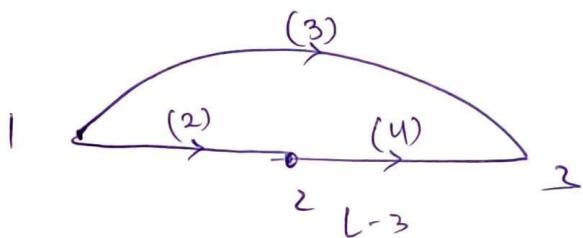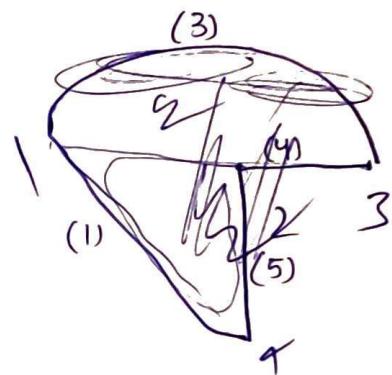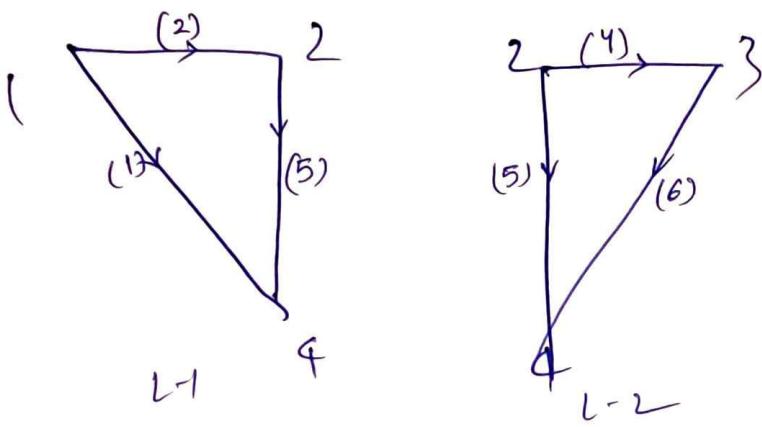
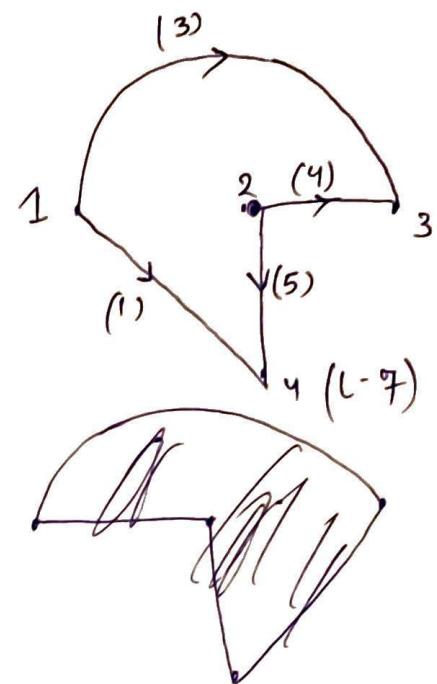
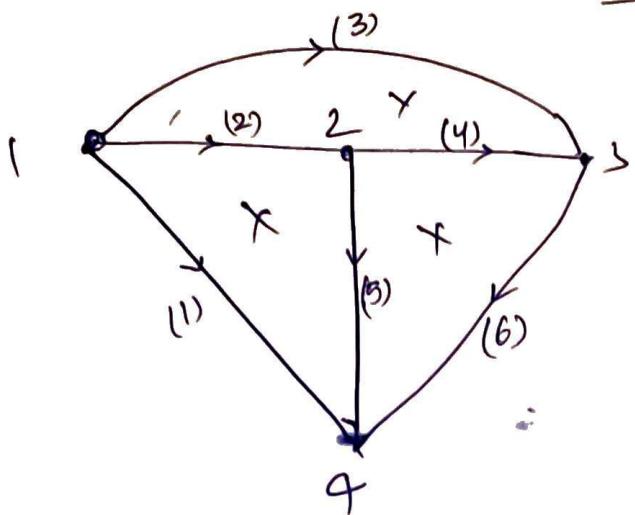


Cut Set

(After Tie set)


→ Here we remove some branches, which may or may not be identical to each other and it bisects graph into two divisions.

→ Find the cut set of given graph.

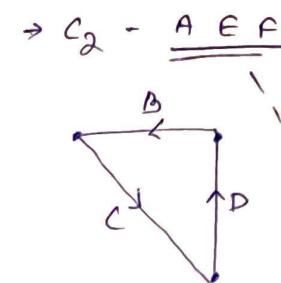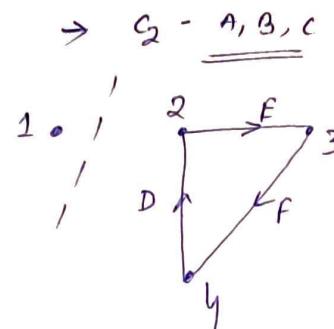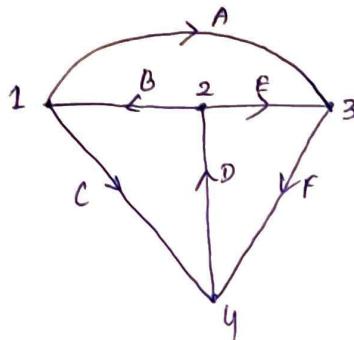

Fundamental Cut Set

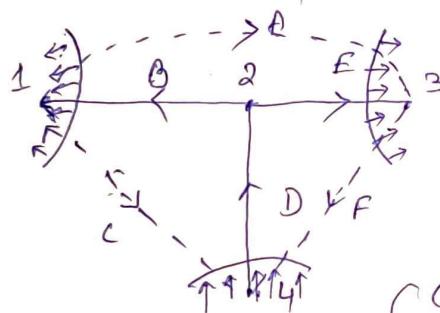- For a given tree of graph, the cut set that contains one twig and rest link is referred fundamental cut set.



Twigs B E D
Links A C F

$$\left\{ \begin{array}{l} C_1 = \underline{\underline{B \ A \ C}} \\ C_2 = \underline{\underline{E \ A \ F}} \\ C_3 = \underline{\underline{D \ C \ F}} \end{array} \right.$$

Cut set	Branches					
	A	B	C	D	E	F
C_1	-1	1	-1	0	0	0
C_2	1	0	0	0	1	-1
C_3	0	0	-1	1	0	-1

Cut set matrix

* It represents orientation of branches with respect to fundamental cut set.

* Direction of cut set is in the direction of Twig of fundamental cut set

* $\alpha_{ij} = \begin{cases} +1 & \text{Direction of branch in cut set direction} \\ -1 & " " " \text{ opposite to cut set direction} \\ 0 & \text{Branch is not connected on the cut set.} \end{cases}$

$$\alpha_{ij} = \begin{cases} +1 \\ -1 \\ 0 \end{cases}$$

Direction of branch in cut set direction
" " " opposite to cut set direction
Branch is not connected on the cut set.

* Each fundamental cut set represents an equipotential surface.

* Cut set and Tie set are dual to each other.

(29)

Before Circ. Set

Fundamental loop matrix or Tie-set matrix

- The n/w matrices will help to keep the data more organized when you keep them in rows & columns to make computation easier.
- Complex calculation will be easier.


(i) Fundamental Loop matrix

(ii) Fundamental cut set matrix


(iii) Incidence matrix.

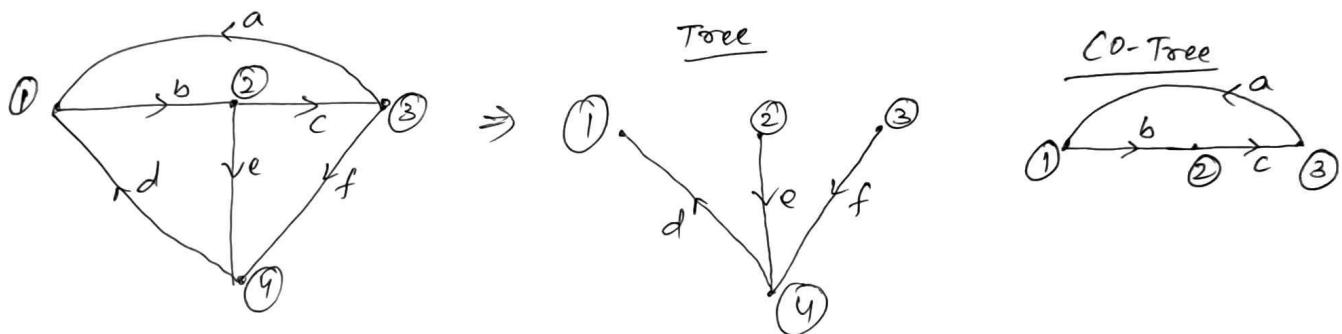(i) Fundamental loop matrix : It will help to calculate branch currents in a ckt.

f-loop : contains only one link & one/more twigs.



One link at a time.

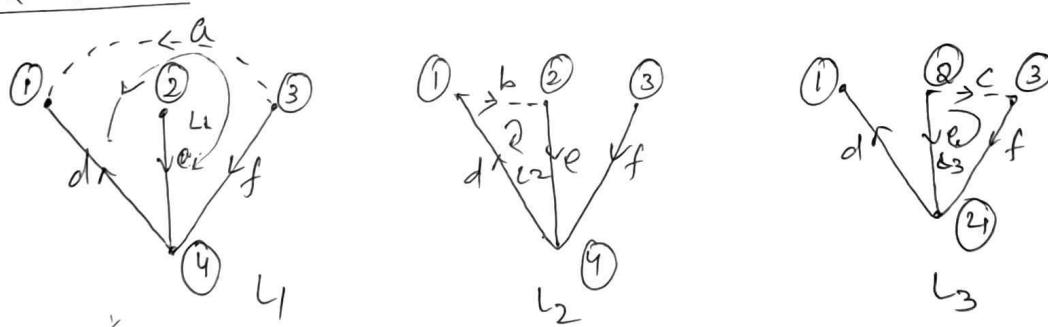

How many fundamental loops = no. of links

Note : The direction of loop will be the direction of link.


$$B = \begin{bmatrix} l_1 & l_2 & l_3 \end{bmatrix} = \begin{bmatrix} a & b & c \\ d & e & f \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & -1 \\ 0 & 1 & 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 0 & -1 & 1 \end{bmatrix}$$

for each tree there will be a fundamental matrix.

Tie set

(~~def~~)

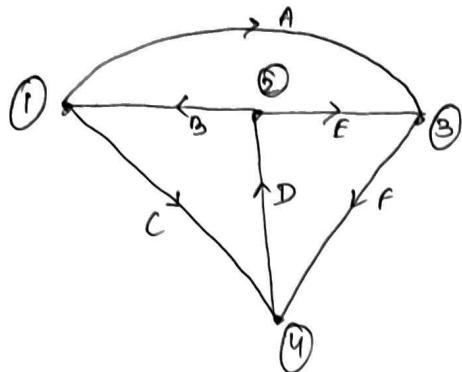→ Tie set is a set of branches which forms a loop irrespective of direction of branch.




Tie sets

A_BE, B_CD, D_EF, A_CF, A_CD_E, A_BD_F
C_BE_F.

Fundamental Tie Set

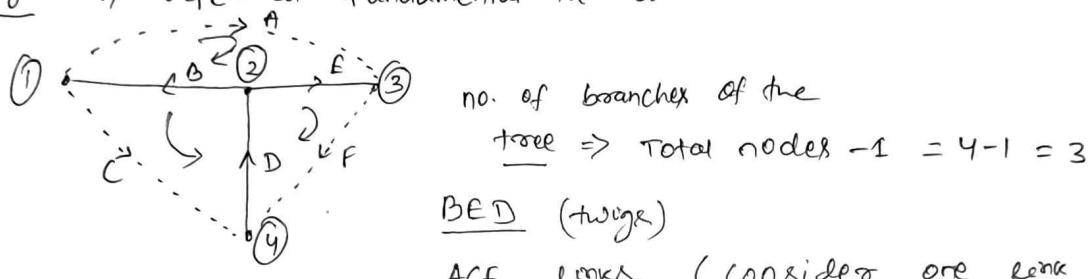→ For a given Tree of graph, the tie set that contains one link and rest twigs is referred fundamental tie set.



Fundamental tie set: A_BE, C_BD, F_DE
L₁ L₂ L₃

Tie set matrix: It represents orientation of branches w.r.t. tie set current.
with fundamental tie set, assume tie set current in same direction of link.

$$a_{ij} = \begin{cases} +1, & \text{Direction of tie set current in the direction of branch} \\ -1, & " " " \quad \text{opposite direction of branch} \\ 0, & \text{Branch is not connected in the tie set current} \end{cases}$$

Loops	Branches					
	A	B	C	D	E	F
L ₁	1	1	0	0	-1	0
L ₂	0	1	1	1	0	0
L ₃	0	0	0	1	1	1

Fundamental loop matrix



b

1

15A

(30)

Essential & key points of cut set matrix

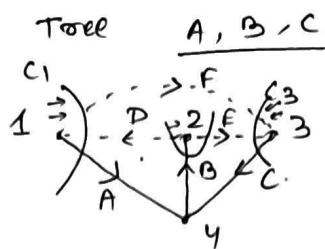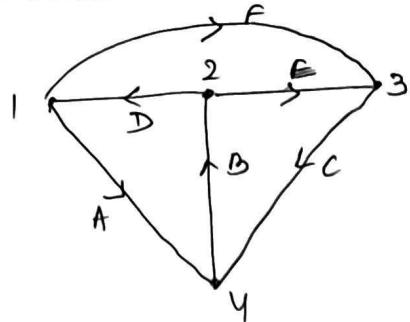

Link \Rightarrow DEF
Twig \Rightarrow A, BC

Tie set (one link & rest twig)

$$L_1 = \underline{D} \quad \underline{A \ B}$$

$$L_2 = \underline{E} \quad \underline{C \ 0}$$

$$L_3 = \underline{F} \quad \underline{AC}$$

$$B =$$

Direction of link = Direction of loop.

Branches

loopx	A	B	C	D	E	F
L ₁	1	1	0	1	0	0
L ₂	0	1	1	0	1	0
L ₃	-1	0	1	0	0	1

Twig Link

Cut set

Fundamental cut set

(one twig & rest link)

Direction of twig.

$$C_1 = \underline{A \ DF}$$

$$C_2 = \underline{B \ DE}$$

$$C_3 = \underline{C \ EF}$$

$$C =$$

Cut set	A	B	C	D	E	F
C ₁	1	0	0	-1	0	1
C ₂	0	1	0	-1	-1	0
C ₃	0	0	1	0	-1	-1

Branches

Twig Link

[Properties]

$$\rightarrow [B]_{\text{link}} = [I]$$

$$\rightarrow [C]_{\text{twig}} = [I]$$


$$\rightarrow [B]_{\text{twig}} = -[C]_{\text{link}}^T$$

$$\rightarrow [C]_{\text{link}} = -[B]_{\text{twig}}^T$$

* twig & link are in sequence.




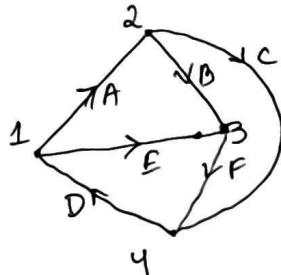KVL & KCL eq. by Cutset Matrix & Tie set matrix



Q) Derive KVL and KCL eq's using Tie set and cutset matrix.
Consider A, B, & C branches of tree for given graph.
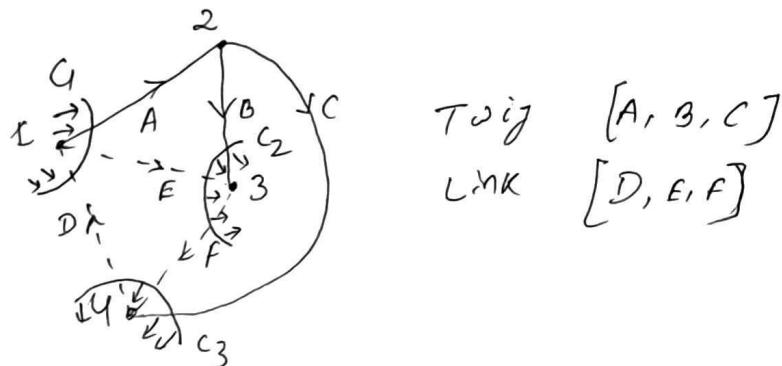
$$\text{Tree} = 4 - 1 = 3 \text{ branches}$$



Tie set matrix (one link & rest twigs)

fundamental loops	D	A C	L ₁
	E	B A	L ₂
	F	B C	L ₃
Direction of loop = Direction of link	-	-	
	-	-	

Branches

Loops &	Branches					
	A	B	C	D	E	F
L ₁	1	0	1	1	0	0
L ₂	-1	-1	0	0	1	0
L ₃	0	1	-1	0	0	1

Cut set matrix

Fundamental cutset [One twig & rest link]

Direction of twigs.

$$C_1 = \underline{\text{twig}} \quad \underline{\text{link}} \\ C_1 = \underline{A} \quad \underline{E \quad D}$$

$$C_2 = \underline{B \quad E} \quad \underline{F}$$

$$C_3 = \underline{C \quad D \quad F}$$

Cut set	Branches					
	A	B	C	D	E	F
C ₁	1	0	0	-1	1	0
C ₂	0	1	0	0	1	-1
C ₃	0	0	1	-1	0	1

$$[B] = \begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 0 \\ -1 & -1 & 0 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix} ; \quad \begin{array}{l} \text{Twigs} \\ \downarrow \\ [I] \end{array}$$

$$\Rightarrow [B_{\text{link}}] = [I] ; \rightarrow [C_{\text{twig}}] = [I] ; [B]_{\text{twig}} = -[C]^T_{\text{link}}$$

$$\rightarrow [C_{\text{link}}] = -[B_{\text{twig}}]^T$$

\Rightarrow KVL eqn by Tie Set matrix.

\rightarrow voltage matrix.

$$[B] \begin{bmatrix} v_a \\ v_b \\ v_c \\ v_d \\ v_e \\ v_f \end{bmatrix} = [0]$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 1 & 1 & 0 & 0 \\ -1 & -1 & 0 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_a \\ v_b \\ v_c \\ v_d \\ v_e \\ v_f \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

Tie Set

$$\begin{aligned} \Rightarrow v_a + v_c + v_d &= 0 & -\textcircled{1} \\ \Rightarrow -v_a - v_b + v_e &= 0 & -\textcircled{2} \\ \Rightarrow v_b - v_c + v_f &= 0 & -\textcircled{3} \end{aligned} \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{KVL eqn}$$

L₁

L₂

L₃

Current eqn by tie set.

$$\Rightarrow [B]^T [I_{\text{set}}] = [I_{\text{branch}}]$$

$$\Rightarrow \begin{bmatrix} 1 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_{\text{set}_1} \\ I_{\text{set}_2} \\ I_{\text{set}_3} \end{bmatrix} = \begin{bmatrix} I_a \\ I_b \\ I_c \\ I_d \\ I_e \\ I_f \end{bmatrix}$$

$$\Rightarrow I_a = I_{\text{set}_1} - I_{\text{set}_2}$$

$$I_b = I_{\text{set}_2} + I_{\text{set}_3}$$

$$I_c = I_{\text{set}_1} - I_{\text{set}_3}$$

$$I_d = I_{\text{set}_1}$$

$$I_e = I_{\text{set}_2}$$

$$I_f = I_{\text{set}_3}$$

KCL by cut set matrin

$$\Rightarrow [C] [I_{\text{branch}}] = [0]$$

$$\Rightarrow \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \\ I_d \\ I_e \\ I_f \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{cases} I_a - I_d + I_c = 0 & -\text{D} \\ I_b + I_c + I_f = 0 & -\text{E} \\ I_c - I_d + I_f = 0 & -\text{F} \end{cases} \quad \begin{bmatrix} C_1 \\ C_2 \\ C_3 \end{bmatrix}$$


Voltage eqn by cut set matrin

$$\Rightarrow [C]^T [V_{\text{set}}] = [V_{\text{branch}}]$$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} v_{\text{set}_1} \\ v_{\text{set}_2} \\ v_{\text{set}_3} \end{bmatrix} = \begin{bmatrix} v_a \\ v_b \\ v_c \\ v_d \\ v_e \\ v_f \end{bmatrix}$$

$$\left. \begin{array}{l} \Rightarrow v_a = \cancel{v_{\text{cut}_1}} \\ v_b = v_{\text{cut}_2} \\ v_c = v_{\text{cut}_3} \\ v_d = -v_{\text{cut}_1} - v_{\text{cut}_3} \\ v_e = v_{\text{cut}_1} + v_{\text{cut}_2} \\ v_f = -v_{\text{cut}_2} + v_{\text{cut}_3} \end{array} \right\}$$

QII


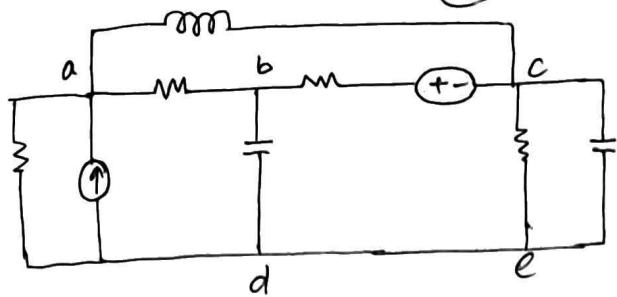


(33) ①

Draw the graph, one tree & co-tree



Ans

$$N = 4, B = 7$$

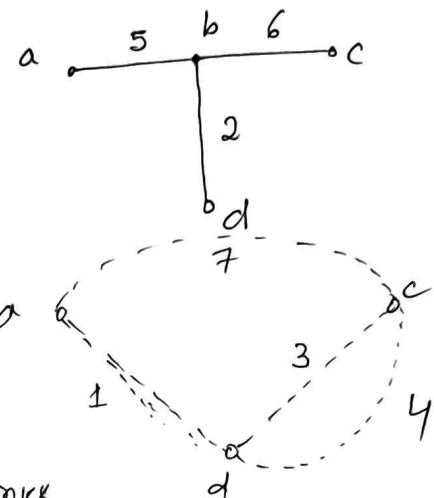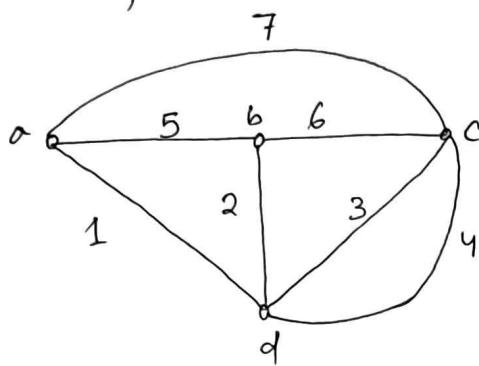

$$L = B - N + 1 = 7 - 4 + 1 = 4 \text{ links}$$

QII

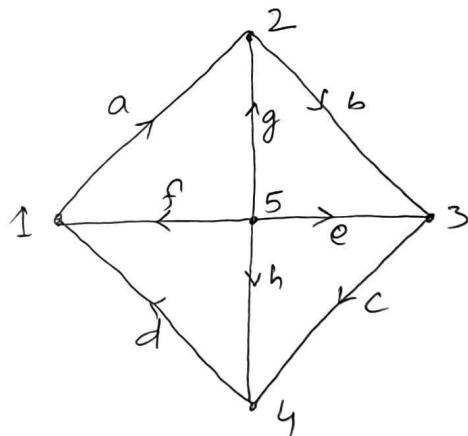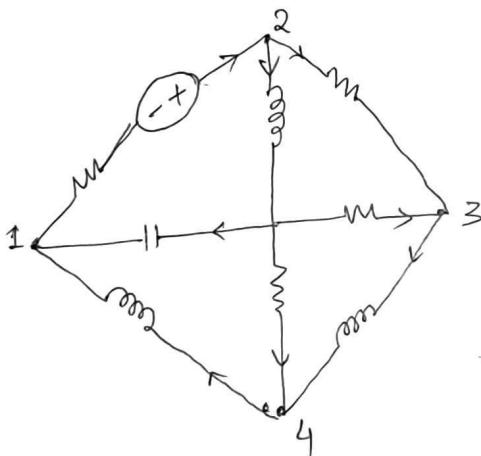A


$$N = 5; B = 8$$

$a_{ik} = 1$, if the current of branch k leaves the node i
 $= -1$, " enters node i "
 $= 0$, k is not connected with node i .

Node	Branches							
	a	b	c	d	e	f	g	h
1	+1	0	0	-1	0	-1	0	0
2	-1	+1	0	0	0	0	-1	0
3	0	-1	+1	0	-1	0	0	0
4	0	0	-1	+1	0	0	0	-1
5	0	0	0	0	+1	+1	+1	+1

R11 incidence matrix
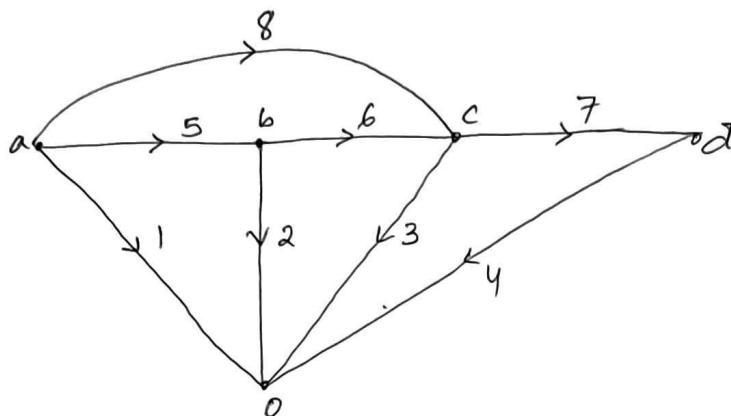
$$a \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ b & 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ c & 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ d & 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$



→ It can be seen that it is a reduced mat. Incidence matrix.

Branches 1, 2, 3, & 4 are to be connected to the reference node.

→ Branch '5' betn a & b


'6' " b & c

'7' " c & d

'8' " a & c


R11 incidence matrix
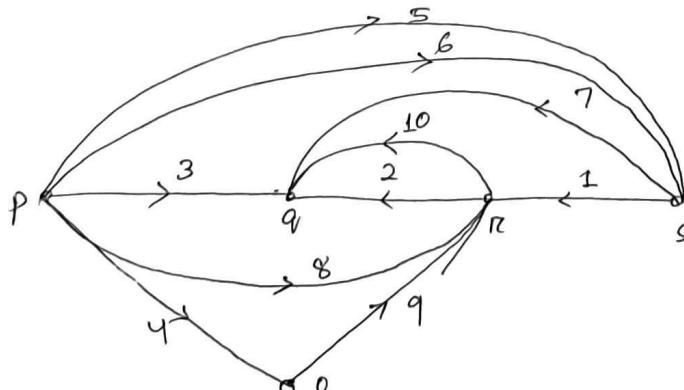
$$P \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 & 10 \\ 0 & 0 & 1 & 1 & 1 & 1 & 0 & 1 & 0 & 0 \\ q & 0 & -1 & -1 & 0 & 0 & 0 & -1 & 0 & 0 & -1 \\ r & -1 & 1 & 0 & 0 & 0 & 0 & 0 & -1 & -1 & 1 \\ s & 1 & 0 & 0 & 0 & -1 & -1 & 1 & 0 & 0 & 0 \end{bmatrix}$$



Sum of the elements
in columns 4, 9 are
not zero.

Therefore it is a reduced
matrix.

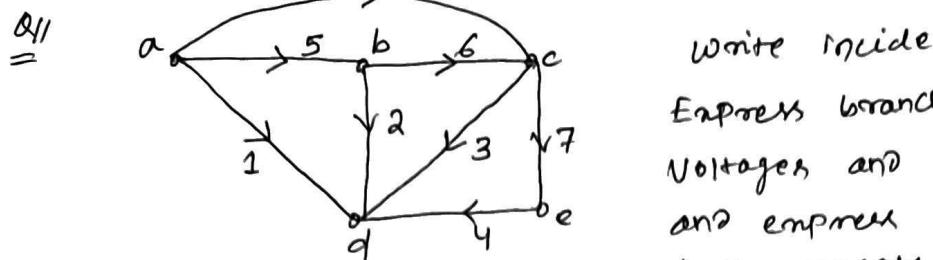

③ 34

Write incidence matrix.
Express branch voltage in terms of node voltages and then write a loop matrix and express branch current in terms of loop currents.


A

$$\begin{array}{ccccccccc} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ \text{a} & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 1 \\ \text{b} & 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ \text{c} & 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ \text{d} & -1 & -1 & -1 & -1 & 0 & 0 & 0 & 0 \\ \text{e} & 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{array}$$

Branch voltages in terms of node voltages are

$$V_1 = e_a - e_d$$

$$V_2 = e_b - e_d \quad \text{etc.}$$

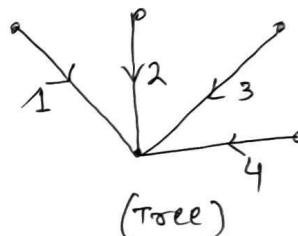

for loop (tie-set) matrix,

$$L = B - N + 1 = 8 - 5 + 1 = 4$$

$$\text{twigs} = (1, 2, 3, 4) \quad ; \quad \text{links} = (5, 6, 7, 8)$$

one link at a time

$$\begin{array}{ccccccccc} & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ i_1 = J_5 & -1 & 1 & 0 & 0 & 1 & 0 & 0 & 0 \\ J_6 & 0 & -1 & 1 & 0 & 0 & 1 & 0 & 0 \\ J_7 & 0 & 0 & -1 & 1 & 0 & 0 & 1 & 0 \\ J_8 & -1 & 0 & 1 & 0 & 0 & 0 & 0 & 1 \end{array}$$

twigs links

branch current in terms of loop currents

$$J_1 = -i_1 - i_4 \quad ; \quad J_2 = i_1 - i_2 \quad \text{etc.}$$

on a singly connected n/w if there are b number of branches and n no. of nodes then the no. of independent meshes M and independent nodes N are respectively

$$L = b - n + 1 \quad \text{How many current eqn.?}$$

$$N = n - 1 \Rightarrow \text{How many nodal eqn? or voltage eqn.}$$

Q1 convert matrix to graph


$$[C] = \begin{bmatrix} A & B & C & D & E & F & G \\ C_1 & 0 & 0 & 0 & 1 & 0 & -1 & 0 \\ C_2 & 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ C_3 & 0 & 1 & 1 & 0 & 1 & 0 & 0 \\ C_4 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$[C] = \begin{bmatrix} D & G & E & A & B & C & F \\ C_1 & 1 & 0 & 0 & 0 & 0 & 0 & -1 \\ C_2 & 0 & 1 & 0 & 0 & 0 & 1 & 1 \\ C_3 & 0 & 0 & 1 & 0 & 1 & 1 & 0 \\ C_4 & 0 & 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{array}{l} \text{Twigs} \\ \text{Links} \end{array}$$

$$\text{Links} = \text{Total loops} = 3 = L$$

$$\text{branches} = 7 = b$$

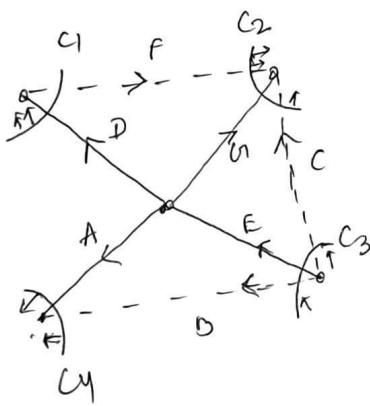
$$\Rightarrow L = b - n + 1 \Rightarrow 3 = 7 - 5 + 1 \Rightarrow n = 5 \text{ (nodes)}$$



- * Twig towards center so that it will not interfere with anyone.
- * Links at edges.

~~Don't solve~~
P1

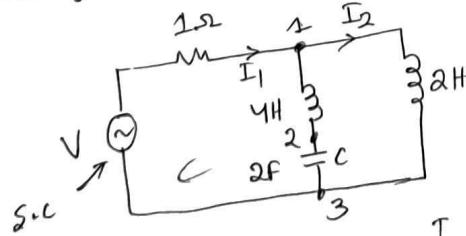for the n/w, calculate the following data.
The graph, one tree, cut set matrix, KCL eqn, voltage eqn.



$$n = 3 \\ \text{Tree } T = n - 1 \\ = 2$$

$$[C] = \begin{bmatrix} A & B & C & D \\ C_1 & 1 & 0 & 1 \\ C_2 & -1 & 0 & 1 & 1 \end{bmatrix}$$



$$C_1 = B \setminus D \\ C_2 = C \setminus D$$

$$\left. \begin{aligned} -I_a + I_b + I_d &= 0 \\ -I_a + I_c + I_d &= 0 \end{aligned} \right\} \text{KCL}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \\ I_d \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Voltage eqn by cut set.

$$\Rightarrow [C]^T [V_{\text{cut}}] = [V_{\text{branch}}]$$

$$\Rightarrow \begin{bmatrix} -1 & -1 \\ 1 & 0 \\ 0 & 1 \\ 1 & 1 \end{bmatrix} [V_{\text{cut}_1}, V_{\text{cut}_2}] = \begin{bmatrix} V_a \\ V_b \\ V_c \\ V_d \end{bmatrix}$$

$$\left. \begin{array}{l} V_a = -V_{\text{cut}_1} - V_{\text{cut}_2} \\ V_b = V_{\text{cut}_1} \\ V_c = V_{\text{cut}_2} \\ V_d = V_{\text{cut}_1} + V_{\text{cut}_2} \end{array} \right\} \xrightarrow{\text{KVL}}$$

Q11 A reduced incidence matrix of a graph is given by.

$$[A_r] = \begin{bmatrix} -1 & 0 & 1 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 & -1 \\ 0 & 1 & -1 & -1 & 0 & 0 \end{bmatrix}$$


→ 1 row is removed, column wise summation is zero
[UPSC 2002]

The no. of possible trees are

$$\begin{aligned} \text{Ans} \quad \text{Total possible trees} &= \det [A_r] [A_r]^T \\ &= \det \begin{bmatrix} 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 \end{bmatrix} \\ &= 4(9-1) + 1(3-2) - 2(1+6) \\ &= 32 - 5 - 14 \\ &= \underline{13} \end{aligned}$$

Some doubts ; Total no. of { $\frac{\text{voltage}}{\text{current}}$ eqn } = n-1
 $\frac{\text{Voltage}}{\text{Current}}$ n = b-n+1

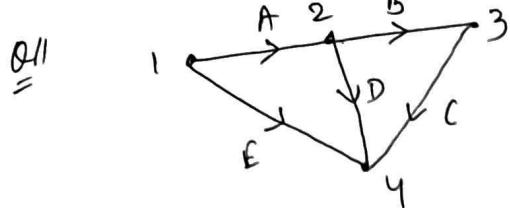\Leftrightarrow incidence matrix \Rightarrow column wise $\sum = 0$



Nodes	Branches				
	A	B	C	D	E
1	1	0	0	0	1
2	-1	1	0	1	0
3	0	-1	1	0	-1
4	0	0	-1	-1	-1

reduced incidence matrix \Rightarrow remove any row

$$[A_{\text{red}}] = \begin{bmatrix} 1 & 0 & 0 & 0 & 1 \\ -1 & 1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 \end{bmatrix}_{3 \times 5}$$

$$\text{Total no. Trees} = \det [A_{12}] [A_{13}]^T$$

$$= \det \begin{bmatrix} 2 & -1 & 0 \\ -1 & 3 & -1 \\ 0 & -1 & 2 \end{bmatrix}_{3 \times 3}$$

$$= 2(6-1) + 1(-2)$$



$$= 8$$

\Leftrightarrow f cut set matrix of a graph is given



$$Q_f = G \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 1 & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & 1 & 0 \end{bmatrix}$$

one Two cut
set link

The oriented graph of the nw

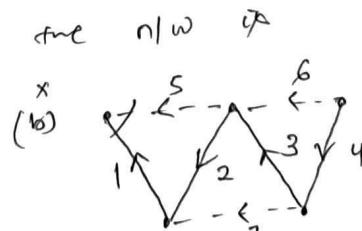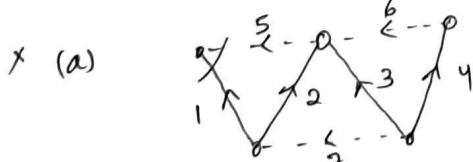





(c)

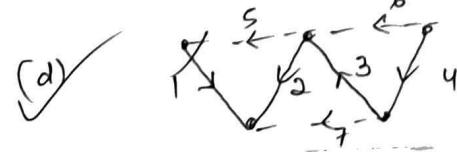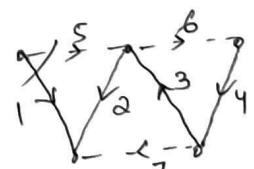

Q11

$$Q_F = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 0 & 1 & -1 & 0 \end{bmatrix} \begin{array}{l} c_1 \\ c_2 \\ c_3 \\ c_4 \end{array}$$





(34)

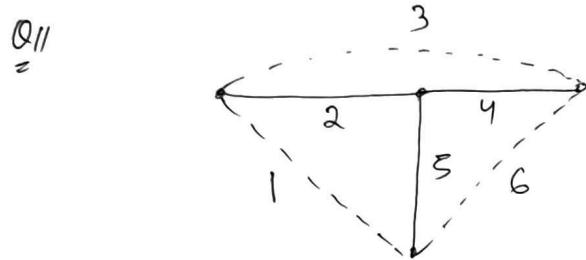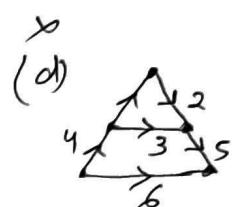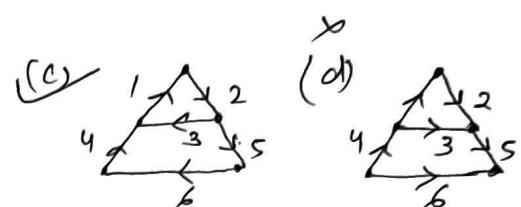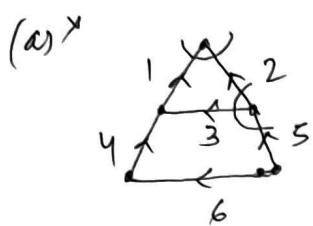

Fundament set matrix / Tie set matrix

$$D_f = \begin{bmatrix} 1 & 1 & 0 & 0 & 1 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \begin{array}{l} L_1 \\ L_2 \\ L_3 \end{array}$$

one link & rest twigs.

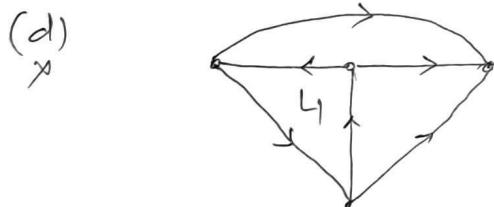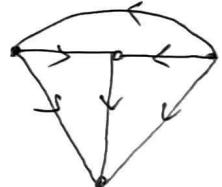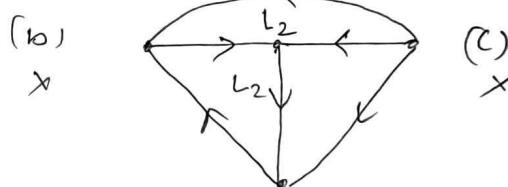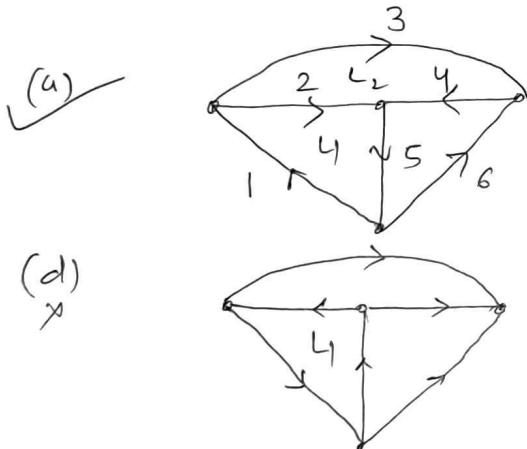

Q11 A reduced incidence matrix of a graph is given


$$A_n = \begin{bmatrix} 1 & 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 & 0 \\ -1 & 0 & -1 & -1 & 0 \end{bmatrix}$$

The no. of possible trees — [UPSC 2015]

Ans

8'


(2)

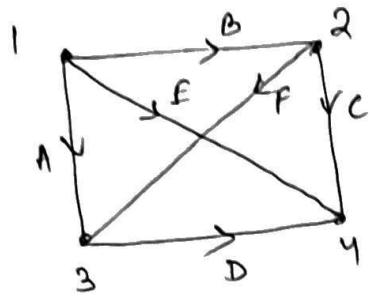Set of Twig \cup

- (a) EF (c) CDE
 (b) ABEF (d) None

$$\text{Branches in tree} = n-1 = 4-1 = 3$$

(3)

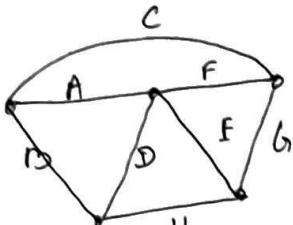

Tree of the graph

$$n-1 = 5-1 = 4 \text{ branches}$$

- (a) CDEH (b) ACFH (c) AFHb (d) AEFH

- (4) A n/w has 7 nodes and 5 independent loops. The no. of branches in the n/w $\Rightarrow L = b-n+1$ [gate 98]
 $\Rightarrow 5 = b-7+1 \Rightarrow b = 11$

- (5) For a n/w of 11 branches and 6 nodes, what is the no. of independent loops? [UPSC, 2005]

$$\Rightarrow L = b-n+1 = 11-6+1 = 6$$

- (6) 4 nodes & 3 ind. loops. The no. of branches [UPSC 07]
 $L = b-n+1 \Rightarrow 3 = b-4+1 \Rightarrow b = 6$

- (7) 10 nodes & 17 branches. The no. of node pair voltage would be [UPSC 2000]

$$\text{For number of pair} = {}^n C_2 = \frac{n(n-1)}{2} = 45$$

- (8) The no. of edges in a complete graph of 'n' vertices $\frac{\text{vertices}}{\text{nodes}}$. [UPSC, 03]

$$\text{no. of node pair} = \text{no. of edges} = {}^n C_2 = \frac{n(n-1)}{2}$$

- (9) For a connected graph of $\frac{V}{\text{nodes of graph}}$ vertices and $\frac{e}{\text{edges}}$, the no. of branches [UPSC 03]

$$L = b - n + 1 \Rightarrow e - V + 1$$

- (10) The graph of a n/w has 8m branches with three tree branches. The min. no. of eqn reqd. for the sol. of the n/w [UPSC 97]
 \rightarrow Twig = 3, $e_{eqn} = 6-3 = 3$ (3 loop eqn)
 \rightarrow In a n/w, 12 ckt elements and 5 nodes. What is the min. no. of mesh eqn. [UPSC 09]

- (11) In a n/w, $b=12$, $n=5$ $\Rightarrow L = b-n+1 = 8$

-ii-

(37)


Duality Principle

- The n/w and its dual are equal only w.r.t. the performance, but the elements and connection point of view they are not equal.

$$\begin{aligned}
 i(t) &\longleftrightarrow V(t) \\
 I &\longleftrightarrow V \\
 R &\longleftrightarrow G \\
 L &\longleftrightarrow C \\
 Z &\longleftrightarrow Y \\
 O.C &\longleftrightarrow S.C \\
 R i(t) &\longleftrightarrow G V(t)
 \end{aligned}$$

$$\begin{aligned}
 \text{Series} &\longleftrightarrow \text{Parallel} \\
 \text{Star} &\longleftrightarrow \text{Delta} \\
 \text{Thevenin's} &\longleftrightarrow \text{Norton's} \\
 \text{Nodal} &\longleftrightarrow \text{Mesh} \\
 \text{KCL} &\longleftrightarrow \text{KVL} \\
 L \frac{di(t)}{dt} &\longleftrightarrow C \frac{dV(t)}{dt} \\
 \frac{1}{C} \int i(t) dt &\longleftrightarrow \frac{1}{L} \int V(t) dt
 \end{aligned}$$

Q/H

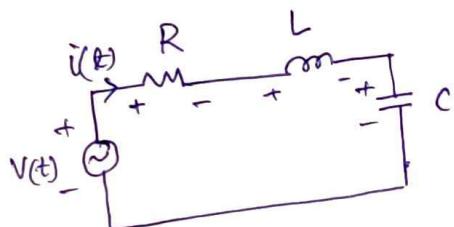


By KVL \Rightarrow

$$V(t) = R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$



\rightarrow A mesh eqn.

$$i(t) = G V(t) + C \frac{dV(t)}{dt} + \frac{1}{L} \int V(t) dt$$


\rightarrow A Nodal eqn.

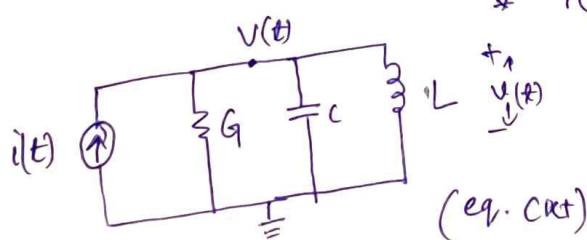

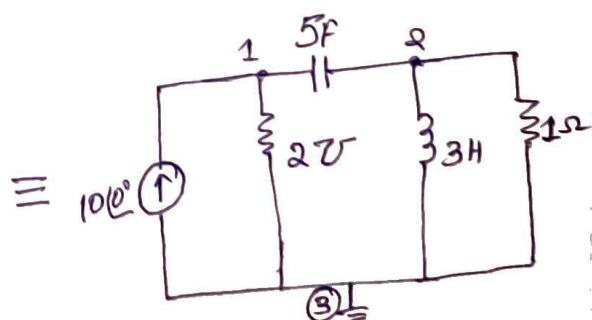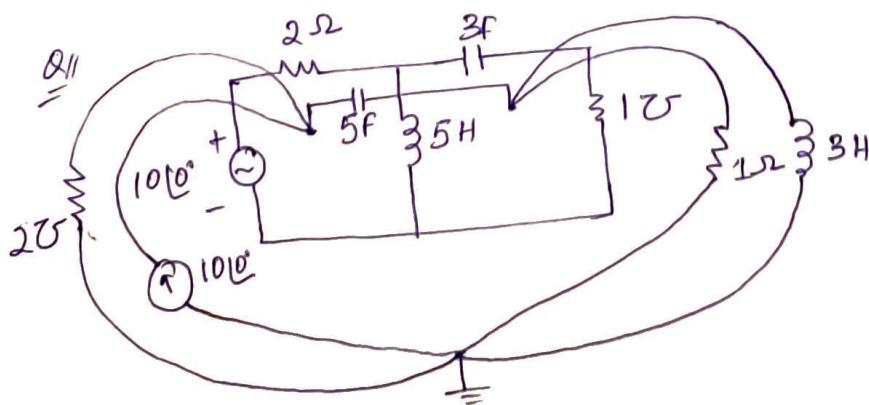
NOTE : The no. of mesh eqn in the original n/w are equal to the no. of nodal eqn in its dual n/w and vice versa.



Q11

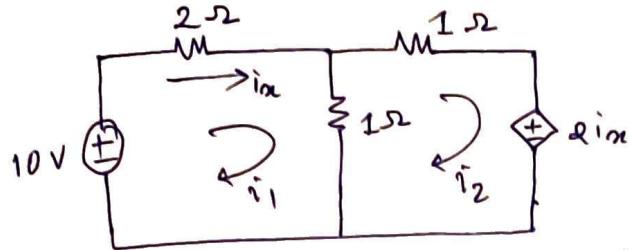
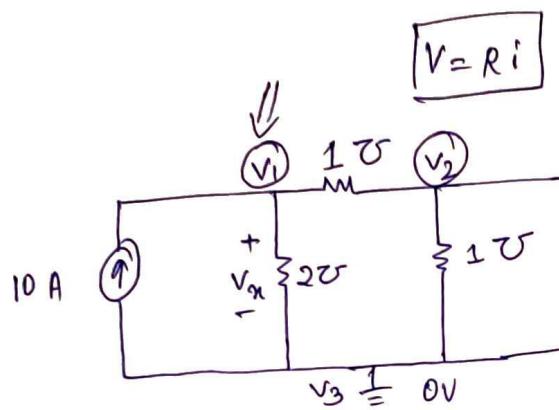
$$\begin{aligned} i_1 &= i_1 \\ \Rightarrow 10 &= 2i_1 + 1(i_1 - i_2) \rightarrow ① \\ 0 &= 1 \cdot i_2 + 2i_1 + 1(i_2 - i_1) \rightarrow ② \end{aligned} \quad \left. \begin{array}{l} \text{mesh eqn} \\ \text{eqn} \end{array} \right\}$$



$$V_x = V_1$$


$$\Rightarrow 10 = 2V_1 + 1 \cdot (V_1 - V_2) \rightarrow ③$$

$$\Rightarrow 0 = 1 \cdot V_2 + 2V_x + 1(V_2 - V_1) \rightarrow ④$$

$$i = Gv$$

Obs : In the above problems, both independent sources are delivering the energy and dependent sources are absorbing energy.


② The Substitution Thm.

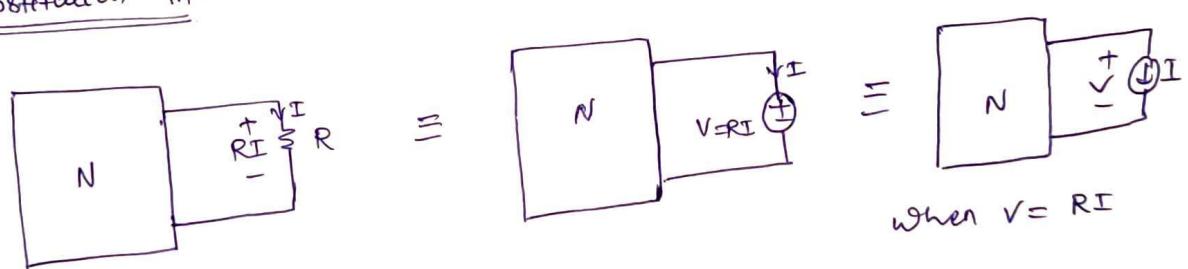

$$P_R = P_V = P_I = VI = RI \cdot I = I^2 R \quad \text{W (abs)}$$

→ In a linear n/w any passive element can be equivalently substituted by an ideal voltage source or an ideal current source, provided all the other branch currents and voltages are kept constant, which is possible only when the original passive element and the substituted active sources absorb the same power.

All

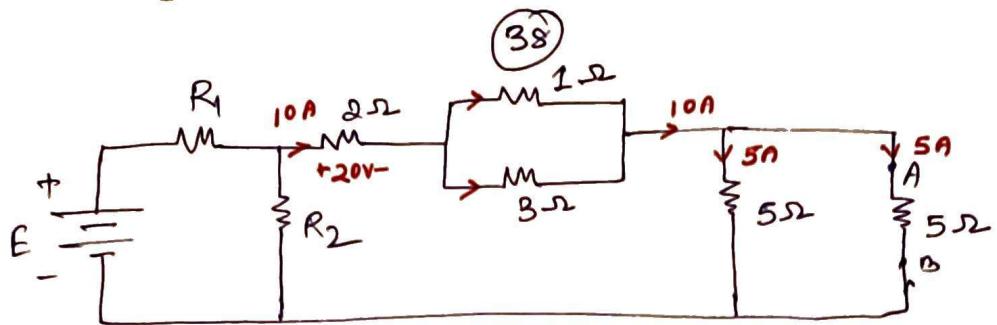

If the voltage across $2\ \Omega$ is $20V$, then $5\ \Omega$ resistor between terminals A, B can be replaced by

$$\equiv 25V \text{ (open terminal pair)} \quad \equiv 25V \text{ (closed terminal pair)}$$

$$P_{5\ \Omega} = P_{25V} = P_{5A} = 25 \times 5 = 125 \text{ W (abs)}$$


All go the above source if the power polarity of the source are reversed then

$$\begin{array}{ccc} 25V & \equiv & 25V \\ + & | & - \\ \hline 5\ \Omega & & 5A \end{array} \quad \equiv \quad \begin{array}{c} 25V \\ + \\ \hline - \\ 5A \end{array} \quad \equiv \quad \begin{array}{c} 25V \\ - \\ \hline + \\ 5A \end{array}$$

$$P_{5\ \Omega} = P_{25V} = P_{5A} = 25 \times 5 = 125 \text{ W}$$

All

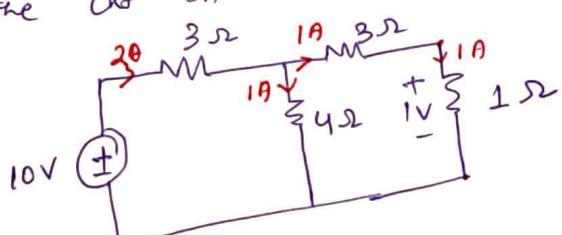in the circuit shown below the $1\ \Omega$ can be replaced by




$$P_{ab} = 1 \times 1 = 1 \text{ W (abs)}$$

The possible substitutions are

$$\begin{array}{c} 1A \\ \downarrow \\ 1V \\ \hline b \end{array} \quad \equiv \quad \begin{array}{c} + \\ 1V \\ \downarrow \\ 1A \\ - \end{array} \quad \equiv \quad \begin{array}{c} 1A \\ \downarrow \\ 0.5V \\ \hline 0.5\ \Omega \\ \hline b \end{array}$$


$$P_{ab} = 1 \times 1 = 1 \text{ W (abs)}$$
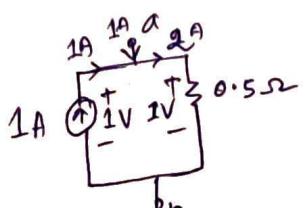
$$\begin{aligned} P_{ab} &= 1 \times 0.5 + 1 \times 0.5 \\ &= 1 \text{ W (abs)} \end{aligned}$$



$$\begin{aligned} P_{ab} &= 1 \times 1 \text{ (abs)} + 2 \times 1 \text{ (abs)} \\ &= 1 \text{ W (abs)} \text{ from the ext } 10V \text{ source} \end{aligned}$$


Q11

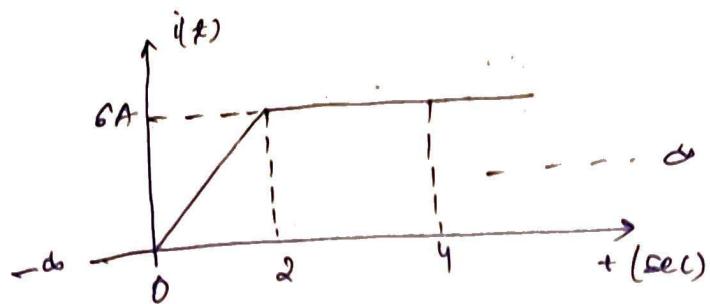

The current flowing through an inductor of resistance 1Ω and inductance $2H$. Determine the energy absorbed by the inductor upto the 1st 4 sec.

- (a) 98 J (b) 132 J (c) 144 J (d) 168 J

①

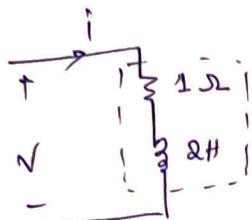

A coil or a practical inductor
or a Ckt.

②

$$\text{Slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{6-0}{2-0} = 3$$

③

$$i = 3t \text{ A for } 0 \leq t \leq 2 \text{ sec}$$

$$i = 6 \text{ A for } 2 \leq t \leq 4 \text{ sec}$$

$$R = 1\Omega : 0 \leq t \leq 2 \text{ sec} \quad i = 3t$$

$$E_{R1} = \int_0^2 i^2 R dt = \int_0^2 (3t)^2 \cdot 1 dt = 24 \text{ J}$$

$$E_{R2} = \int_2^4 i^2 R dt = \int_2^4 6^2 \cdot 1 dt = 72 \text{ J}$$

All on this problem, the
energy stored up to 4 sec is

④ only inductor will store
the energy $\rightarrow 36 \text{ J}$
it is same up to ' ∞ '.

$$L = 2H : 0 \leq t \leq 2 \text{ sec} : i = 3t$$

$$E_L = \int_0^2 L i \frac{di}{dt} dt = \int_0^2 2 \cdot 3t \cdot 3 dt = 36 \text{ J}$$

$$E_{L2} = \int_2^4 L i \left(\frac{di}{dt} \right) dt = \int_2^4 2 \cdot 6 \cdot 0 dt = 0 \text{ J}$$


$$E_{\text{abs}} \Big|_{t=4 \text{ sec}} = E_{R1} + E_{R2} + E_L + E_{L2} = 24 + 72 + 36 + 0 = 132 \text{ J}$$

Note: ① $E_L \Big|_{t=2 \text{ sec}} = E_{L1} = \frac{1}{2} L \cdot i^2 = \frac{1}{2} \cdot 2 \cdot 6^2 = 36 \text{ J}$
or from $-\infty$ to 2 sec

② $E_L \Big|_{t=4 \text{ sec}} = E_{L1} + E_{L2} = \frac{1}{2} \cdot L \cdot i^2 = \frac{1}{2} \cdot 2 \cdot 6^2 = 36 \text{ J}$
 $(E_{L2} = 0 \text{ J})$


When the current through the ideal inductive coil (2H) is constant then the energy of it is zero, since the instantaneous power is zero. $P = L i \frac{di}{dt} = 0 \text{ W}$. Similarly by constant capacitor voltage $P = C V \frac{dv}{dt} = 0 \text{ W}$.

Q11

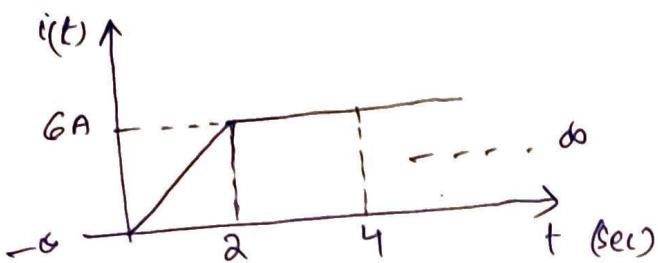

The charact. \rightarrow the current flowing through an inductor of resistance 1Ω and inductance $2H$. Determine the energy absorbed by the inductor upto the first 4 sec.
 (a) 98 J (b) 132 J (c) 144 J (d) 168 J.

Ans

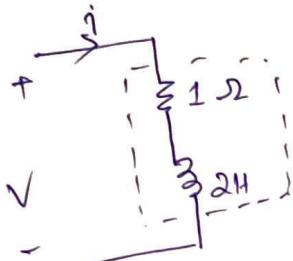

A coil of practical inductor

$$\text{Slope} = \frac{y_2 - y_1}{x_2 - x_1} = \frac{6 - 0}{2 - 0} = 3$$

$$i = 3(t) \text{ A for } 0 \leq t \leq 2 \text{ sec}$$

$$i = 6 \text{ A for } 2 \leq t \leq 4 \text{ sec.}$$

$$R = 1\Omega ; \quad 0 \leq t \leq 2 \text{ sec} ; \quad i = 3t$$

$$E_{R1} = \int_0^2 i^2 R dt = \int_0^2 (3t)^2 \cdot 1 dt = 24 \text{ J.}$$

$$E_{R2} = \int_2^4 i^2 R dt = \int_2^4 6^2 \cdot 1 dt = 72 \text{ J.}$$

$$L = 2H ; \quad 0 \leq t \leq 2 \text{ sec} ; \quad i = 3t$$

$$E_L = \int_0^2 L i \left(\frac{di}{dt} \right) dt = \int_0^2 2 \cdot 3t \cdot 3 dt = 36 \text{ J}$$

$$E_{L2} = \int_2^4 L i \left(\frac{di}{dt} \right) dt = \int_2^4 2 \cdot 6 \cdot 0 dt = 0 \text{ J.}$$

$$\begin{aligned} \text{Total } E_{\text{abs}} \Big|_{t=4 \text{ sec}} &= E_{R1} + E_{R2} + E_L + E_{L2} = 24 + 72 + 36 + 0 \\ &= 132 \text{ J.} \end{aligned}$$

$$E_{R3} = \int_4^\infty i^2 R dt = 24 \text{ J}$$

Note.

$$\textcircled{1} \quad E_L \Big|_{t=2\text{sec}} = E_{L1} = \frac{1}{2} L \cdot i^2 = \frac{1}{2} \cdot 2 \cdot 6^2 = 36 \text{ J}$$

from $-\infty$ to 2 sec

$$\textcircled{2} \quad E_L \Big|_{t=4\text{sec}} = E_{L1} + E_{L2} \xrightarrow{\text{as } t \rightarrow \infty} = \frac{1}{2} \cdot L \cdot i^2 = \cancel{36} \text{ J}$$

$\cancel{36}$
 $-\infty$ to 4 sec

\Rightarrow When the current through the ideal inductive coil (2H) is constant, then the energy of it is zero, since the instantaneous power zero. $P = L \cdot i \frac{di}{dt} = 0 \text{ W}$.

Similarly by constant capacitor voltage $P = C V \frac{dV}{dt} = 0 \text{ W}$.

Q1 In the above problem, the energy stored by the CKT ($1\text{R}, 2\text{H}$) up to the first 4 sec is

A only the inductive part (2H) in a practical inductor ($1\text{R}, 2\text{H}$) will store the energy, so it is 36 J .

The stored energy is same even upto ∞ .


Q2 In the above problem, the energy absorbed by the CKT upto ∞

$$\begin{aligned} E \Big|_{t=\infty} &= E_R \Big|_{t=\infty} + E_L \Big|_{t=\infty} \\ &= E_{R1} + \int_{2}^{\infty} i^2 \cdot R \cdot dt + 36 \\ &= 24 + \int_{2}^{\infty} 6^2 \cdot 1 \cdot dt + 36 \\ &= 60 + [36t]_2^{\infty} = 60 + 36(\infty - 2) = \underline{\underline{80 \text{ J}}} \end{aligned}$$

$$\boxed{\text{absorbed} = (\text{stored by L \& C}) + \text{dissipated by R}}$$

(2)

④

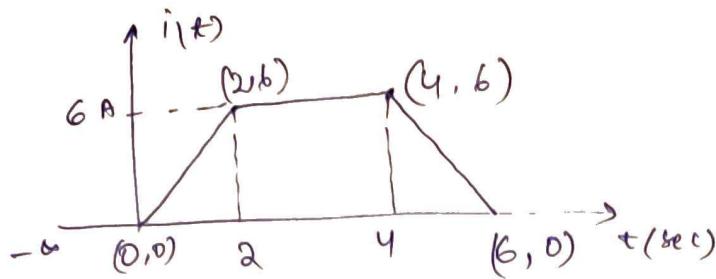

Energy stored by the CKT upto 6 sec.

Ans

$$\left[E_{\text{stored}} \Big|_{t=6 \text{ sec}} = E_L \Big|_{t=6 \text{ sec}} \right. \\ \left. = \frac{1}{2} L \cdot i^2 = \frac{1}{2} \cdot 2 \cdot 0^2 = \underline{0 \text{ J}} \right]$$

$$\begin{matrix} (4, 6) \\ y_1 \quad y_2 \\ \searrow \\ (6, 0) \\ x_1 \quad x_2 \end{matrix} \quad S = \frac{0 - 6}{6 - 4} = -3$$

Derivation / explanation

$$(6, 0) \quad S1 = -3$$

$$y - y_1 = m (x - x_1)$$

$$\Rightarrow i - 0 = -3(t - 6)$$

$$\Rightarrow i = -3(t - 6) \text{ A} \quad (4 \leq t \leq 6 \text{ sec})$$

$$E_{L3} = \int_4^6 L i \frac{di}{dt} dt = \int_4^6 2 \cdot -3(t-6) \cdot -3 dt \\ = 18 \left[\frac{t^2}{2} \right]_4^6 = 36 - 16 - 12 = 36 \text{ J}$$


$$E_{\text{stored}} \Big|_{t=6 \text{ sec}} = E_{L1} + E_{L2} + E_{L3} = 36 \text{ J} + 0 + (-36 \text{ J}) \\ = \underline{0 \text{ J}}$$

(ii) Energy absorbed by the CKT upto 6 sec.

$$E_{\text{abs}} \Big|_{t=6 \text{ sec}} = E_{R1} + E_{R2} + E_{R3} + E_{L1} + E_{L2} + E_{L3} \\ = 24 + 72 + 24 + 36 + 0 - 36 \Rightarrow \int_4^6 \{-3(t-6)\}^2 \cdot 1 dt \\ = 120 \text{ J}$$

$$E_{R3} = \int_4^6 i^2 \cdot R dt = 24 \text{ J}$$

Q11 Det. the relation betn
 v_1 & v_2

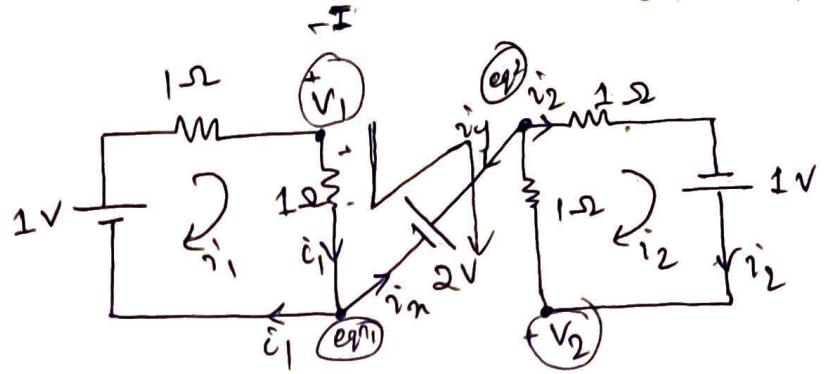

By KCL

$$\Rightarrow -i_1 + i_1 + i_m = 0 \quad \text{--- (I)}$$

$$\Rightarrow -i_2 + i_2 + i_y = 0 \quad \text{--- (II)}$$

$$\text{So, } i_m = i_y = 0$$

Since no current flows through 2V source, both the meshes are independent to each other.

By KVL

$$\Rightarrow 1 - 1i_1 - 1i_1 = 0 \quad \text{meth (I)}$$

$$\Rightarrow 1 = 2i_1 \Rightarrow i_1 = 0.5 \text{ A}$$

mesh (2)

$$1 - i_2 - i_2 = 0$$

$$i_2 = 0.5 \text{ A}$$

By KVL

$$v_1 - 1i_1 + 2 + 1i_2 - v_2 = 0$$

$$\Rightarrow \boxed{v_1 + 2 = v_2}$$

So, v_2 is 2V higher than v_1 .

(40)

Pending

→ The no. of ~~possible~~ ^{possible} trees of a complete graph with 'n' nodes
 $= n^{n-2}$

- The rank of incidence matrix = $n-1$ = rank of the graph
- The rank of f-loop matrix = $b-n+1$ = rank.
- For a complete graph there are n^{n-2} f-loop matrices
- f-loop : minimum no. of loop or mesh eqns required to solve the corresponding n/w.
- f-cutset : minimum no. of nodal eqns required to solve the corresponding n/w.
- The rank of the f-cutset matrix = $n-1$ = twigs
- For a complete graph there are n^{n-2} dc matrices.

Q11 A n/w consists of 17 branches and 10 nodes. Det. the no. of equations reqd. to solve the corresponding n/w.

(4) nodal eqn = f-cutsets = $n-1 = 9$
 mesh eqn = f-loops = $b-n+1 = 8$
 so, the no. of eqn reqd. = minimum of nodal, mesh eqn
 $= \underline{8}$

—o—

Coupled